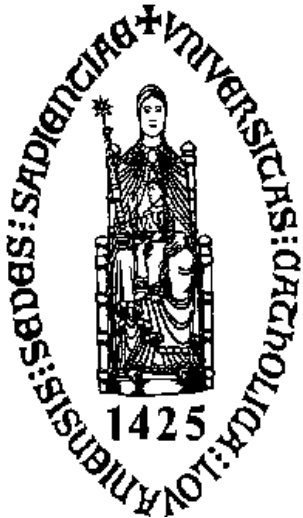

Distortion in elementary transistor circuits



Willy Sansen

KULeuven, ESAT-MICAS


Leuven, Belgium

willy.sansen@esat.kuleuven.be



Why distortion ?

**Non-linearity :
distortion**

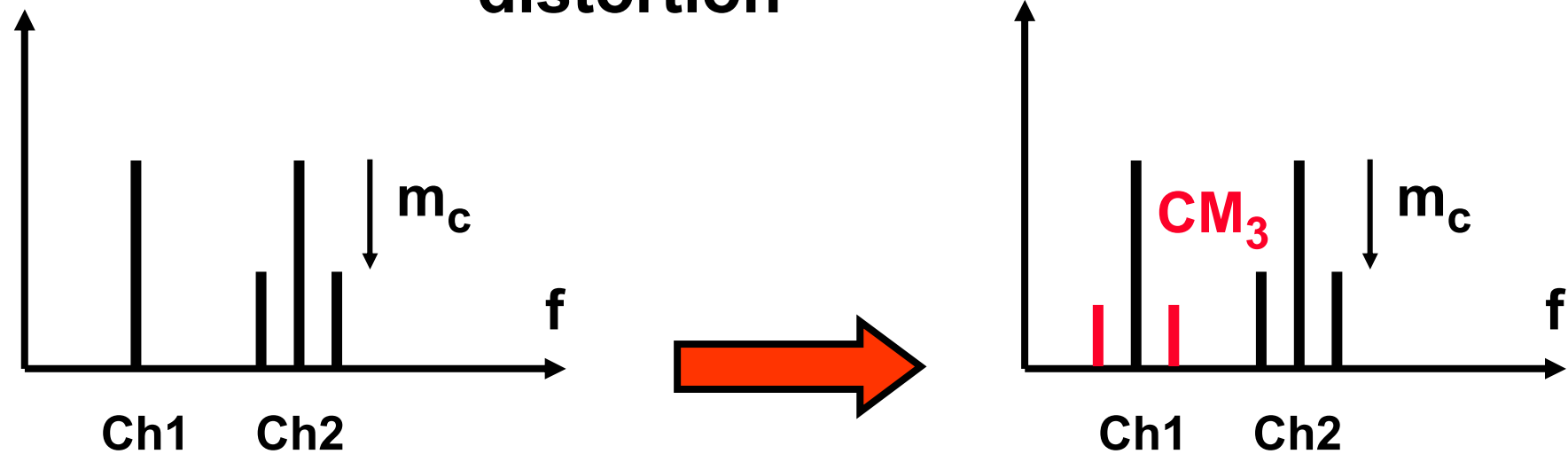

Mixing up channels !!!

Table of contents

☐ **Definitions : HD, IM, intercept point, ..**

☐ **Distortion in a MOST**

- **Single-ended amplifier**
- **Differential amplifier**


☐ **Distortion in a bipolar transistor**

☐ **Reduction of distortion by feedback**


☐ **Distortion in an opamp**

☐ **Other cases of distortion and guide lines**


Linear distortion

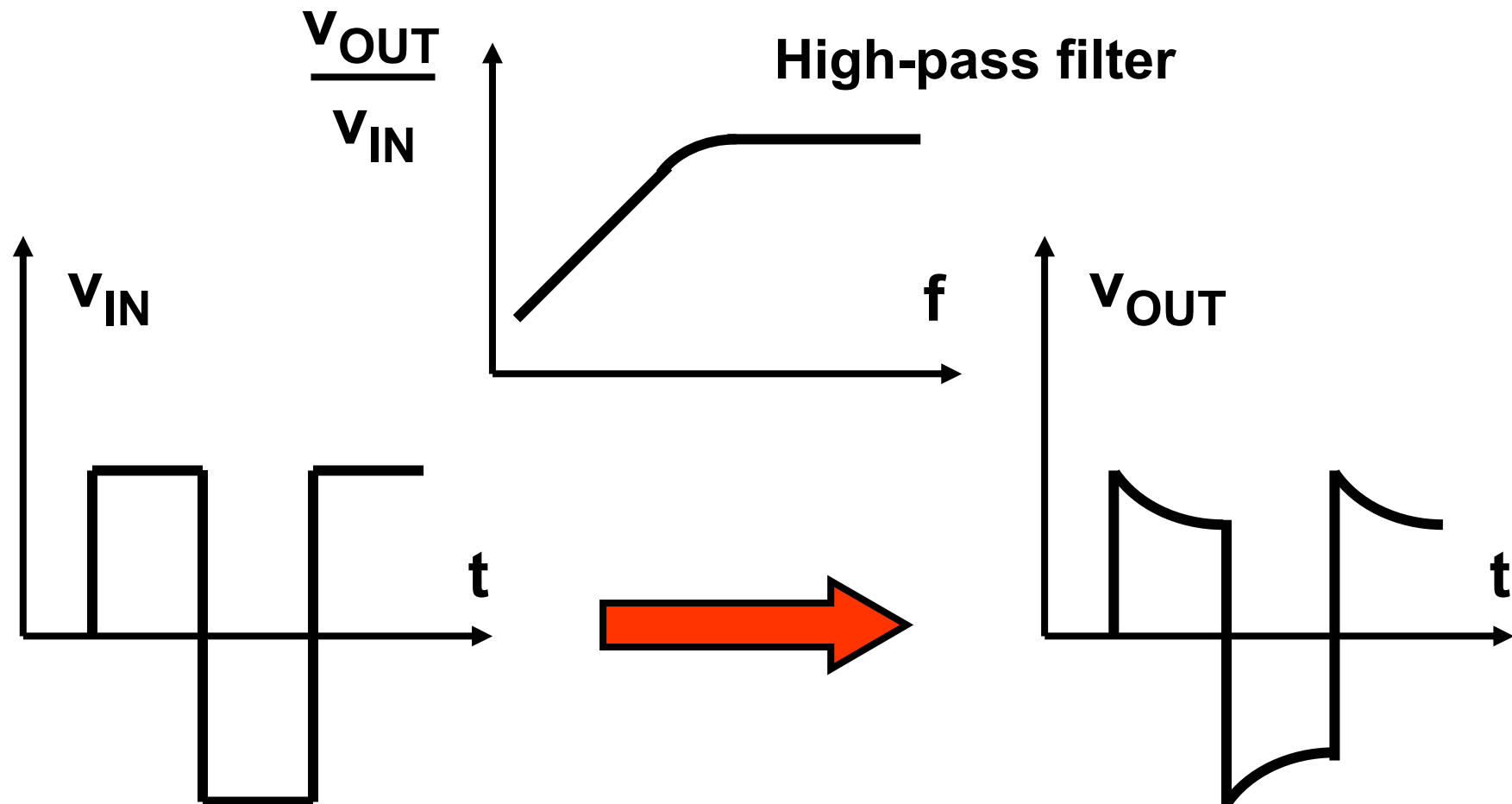



Linear distortion

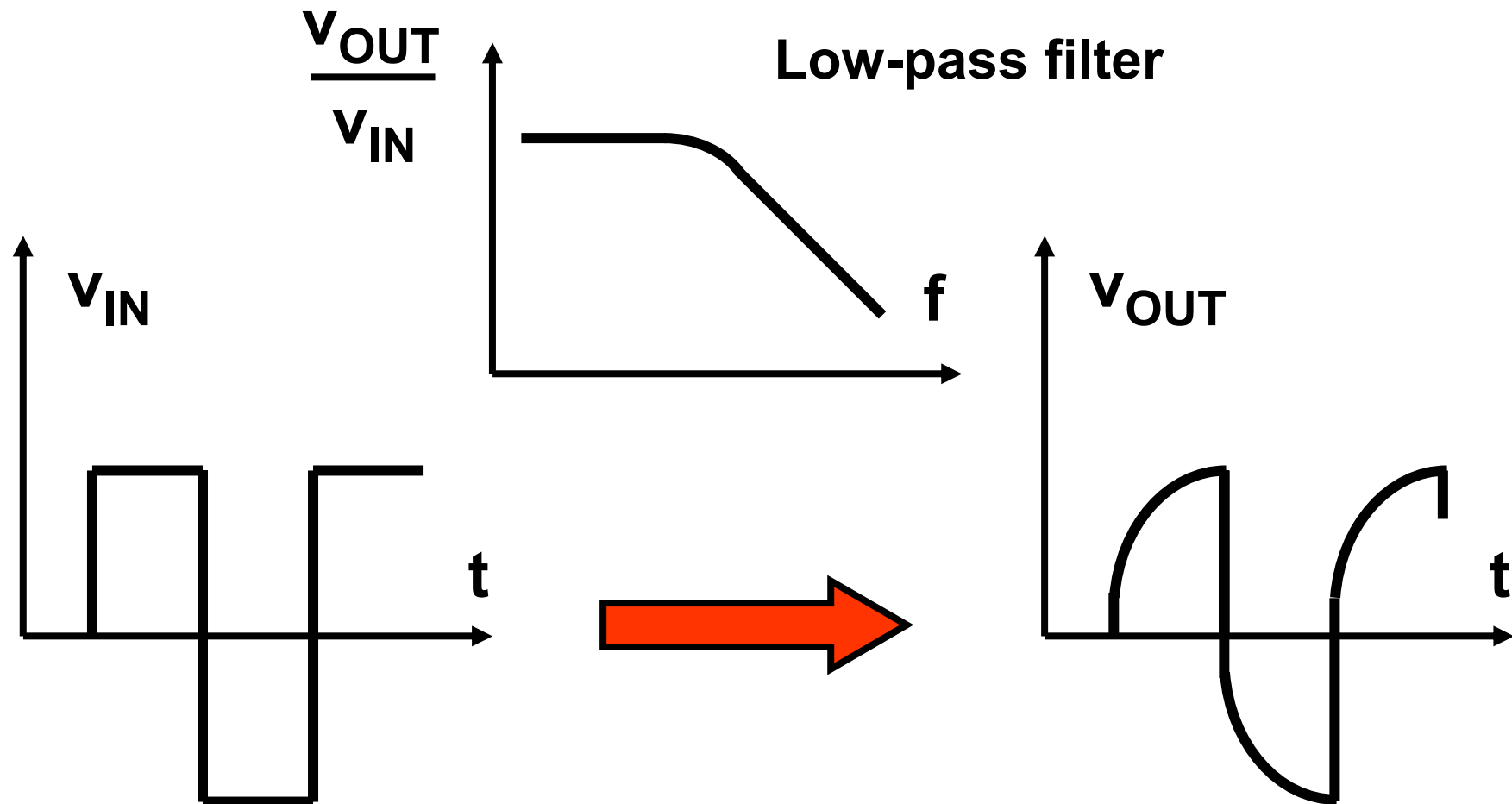


Non-linear distortion

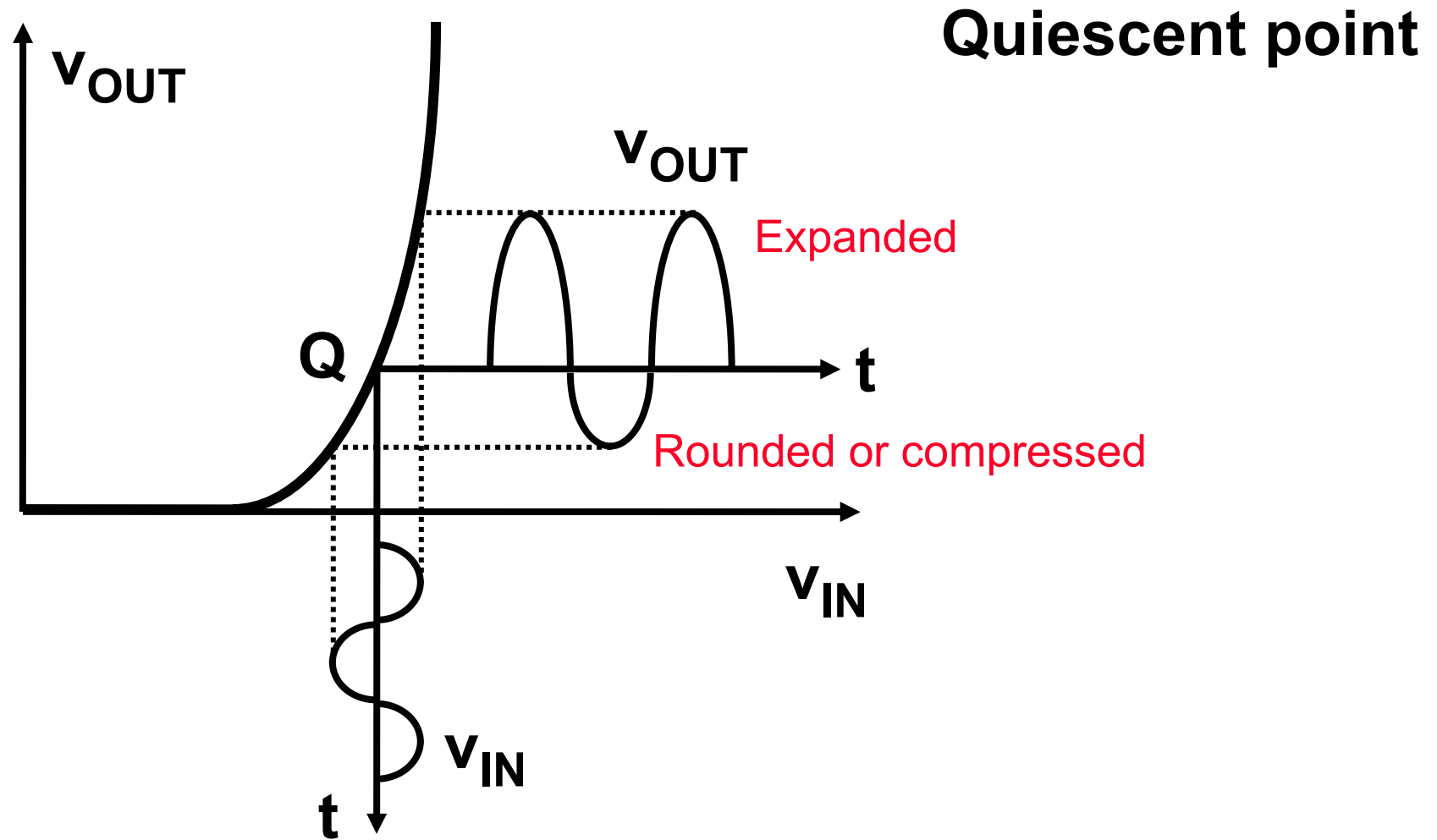

Soft and hard non-linearity

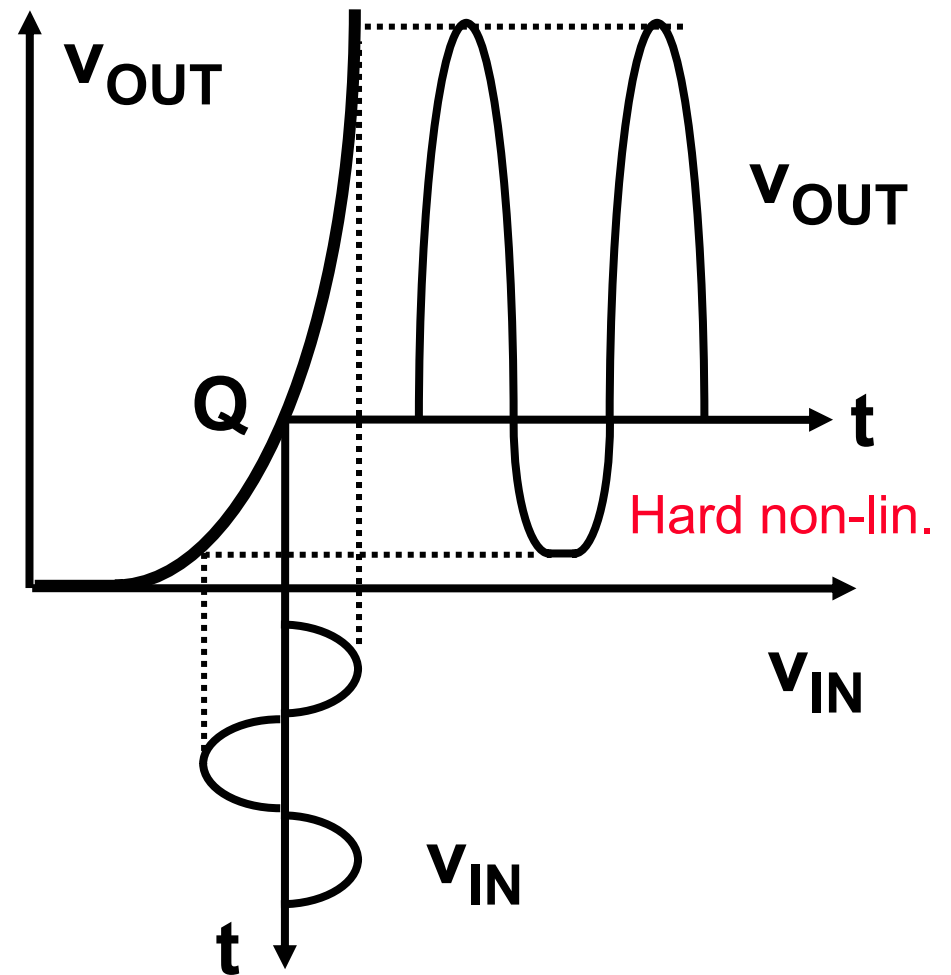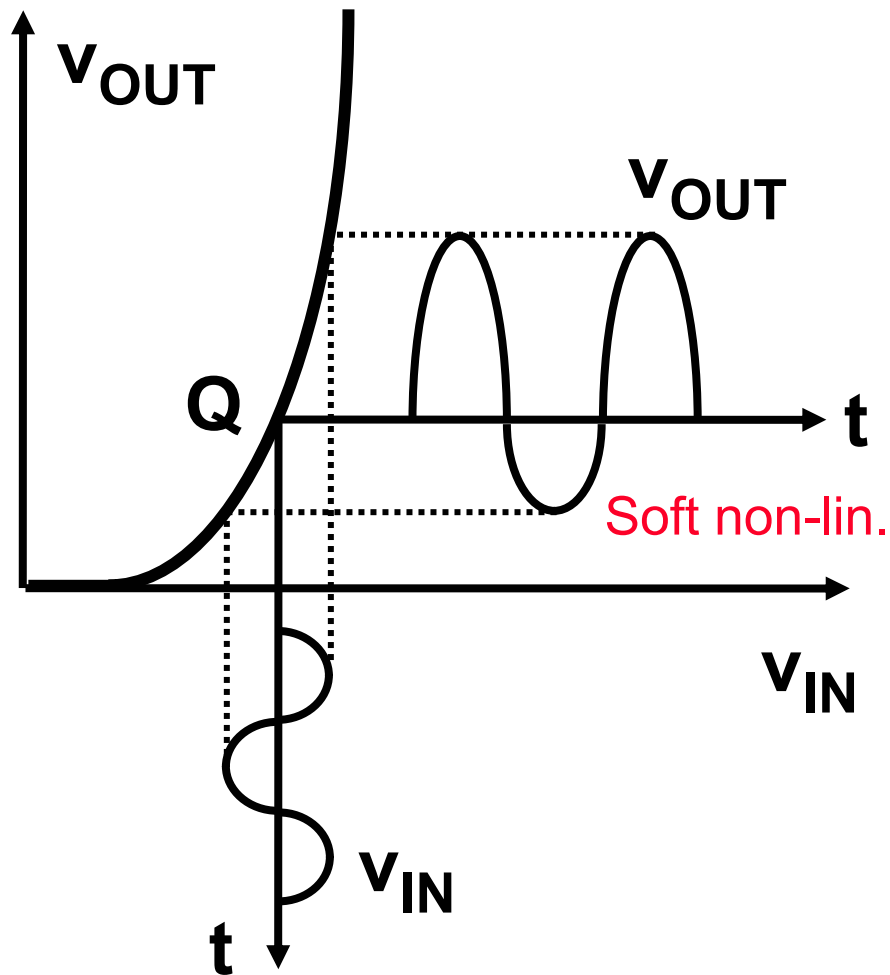

Non-linearity : by power series

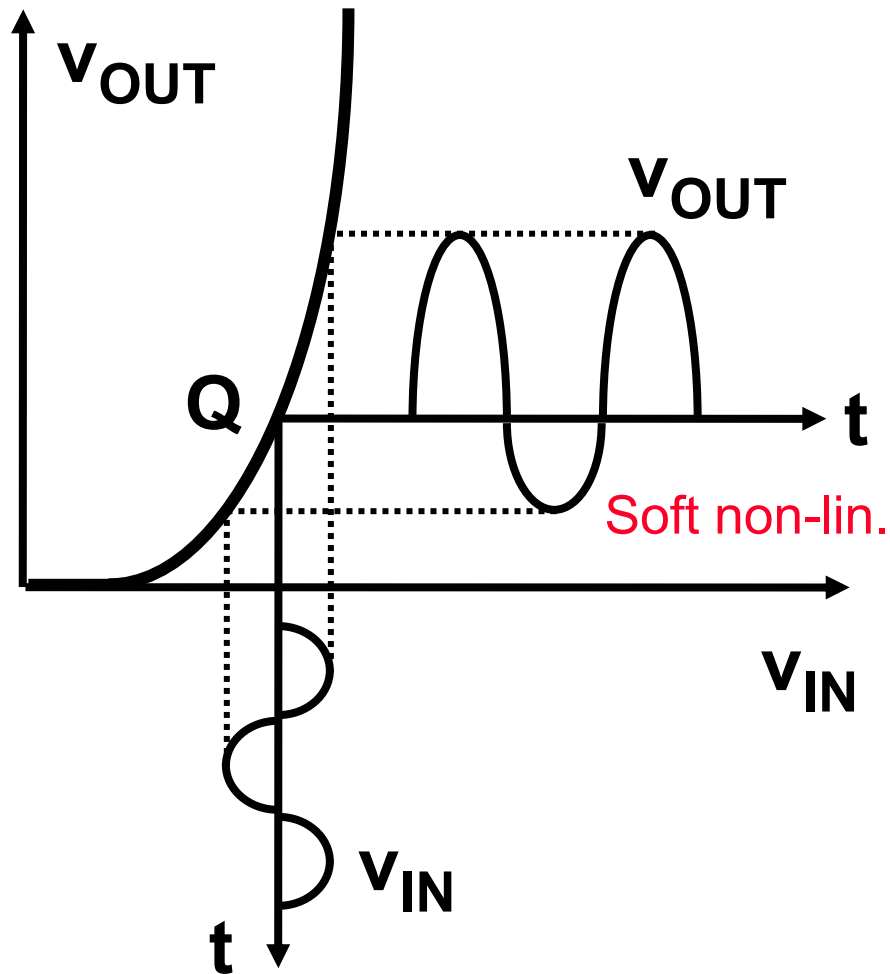

$$v_{IN}(t) \Rightarrow v_{OUT}(t)$$

$$v_{OUT} = a_0 + a_1 v_{IN} + a_2 v_{IN}^2 + a_3 v_{IN}^3 + \dots$$

How to find $a_0, a_1, a_2, a_3, \dots$

$$y = a_0 + a_1 u + a_2 u^2 + a_3 u^3 + \dots$$

$$a_0 = y \Big|_{u=0}$$

$$a_1 = \frac{dy}{du} \Big|_{u=0}$$

$$a_2 = \frac{1}{2} \frac{d^2 y}{du^2} \Big|_{u=0}$$

$$a_3 = \frac{1}{6} \frac{d^3 y}{du^3} \Big|_{u=0}$$

Definition of harmonic distortion HD

$$y = a_0 + a_1 u + a_2 u^2 + a_3 u^3 + \dots$$

With $u = U \cos \omega t$

$$\cos^2 x = 1/2 (1 + \cos 2x)$$

$$\cos^3 x = 1/4 (3 \cos x + \cos 3x)$$


$$y = a_0 + a_1 u + a_2 u^2 + a_3 u^3 + \dots = a_0 +$$

$$(a_1 + \frac{3}{4} a_3 U^2) U \cos \omega t + \frac{a_2}{2} U^2 \cos 2\omega t + \frac{a_3}{4} U^3 \cos 3\omega t$$


$$HD_2 = \frac{1}{2} \frac{a_2}{a_1} U$$

$$HD_3 = \frac{1}{4} \frac{a_3}{a_1} U^2$$


Amplitude HD versus input signal

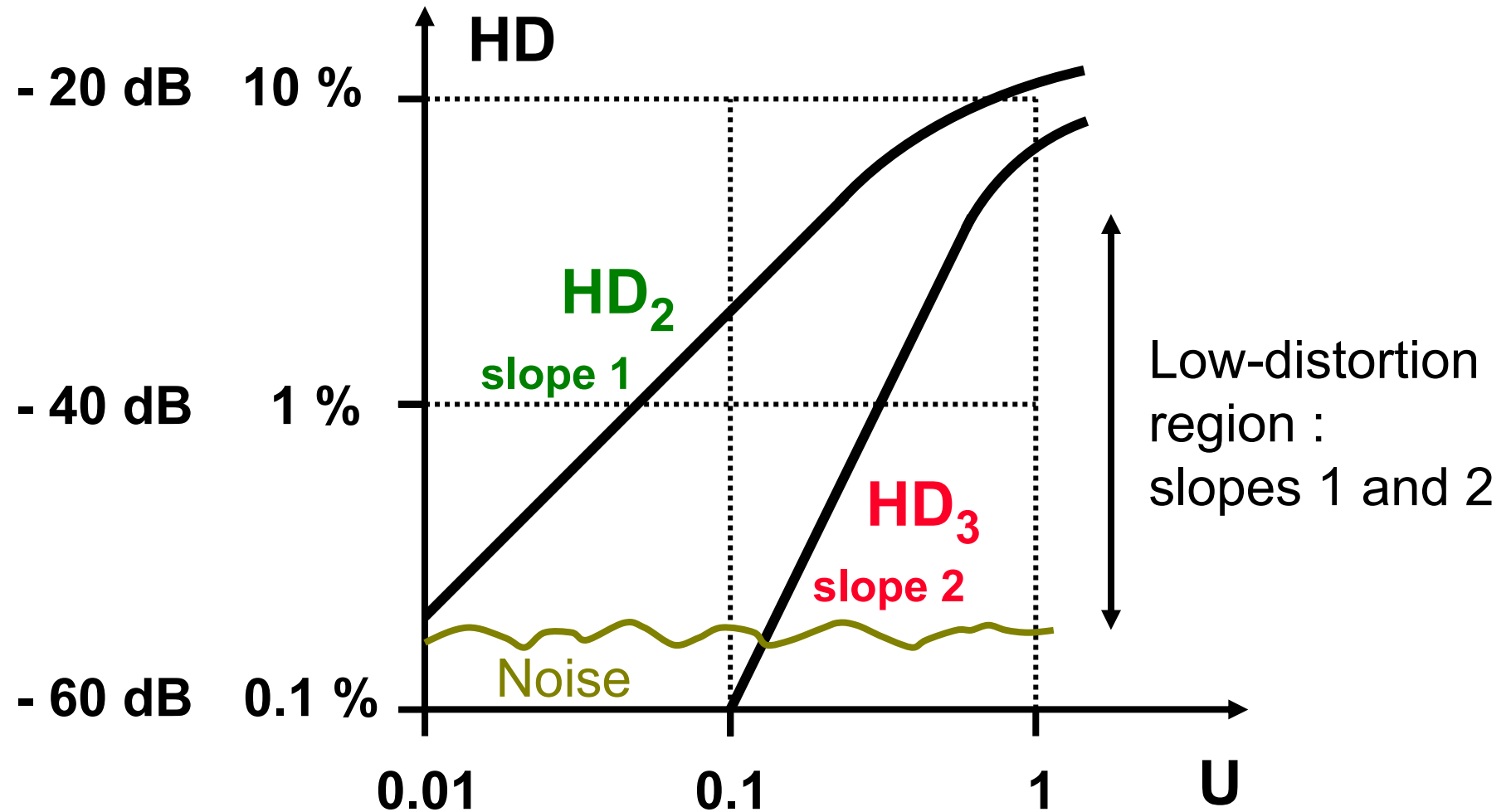

HD of a resistor

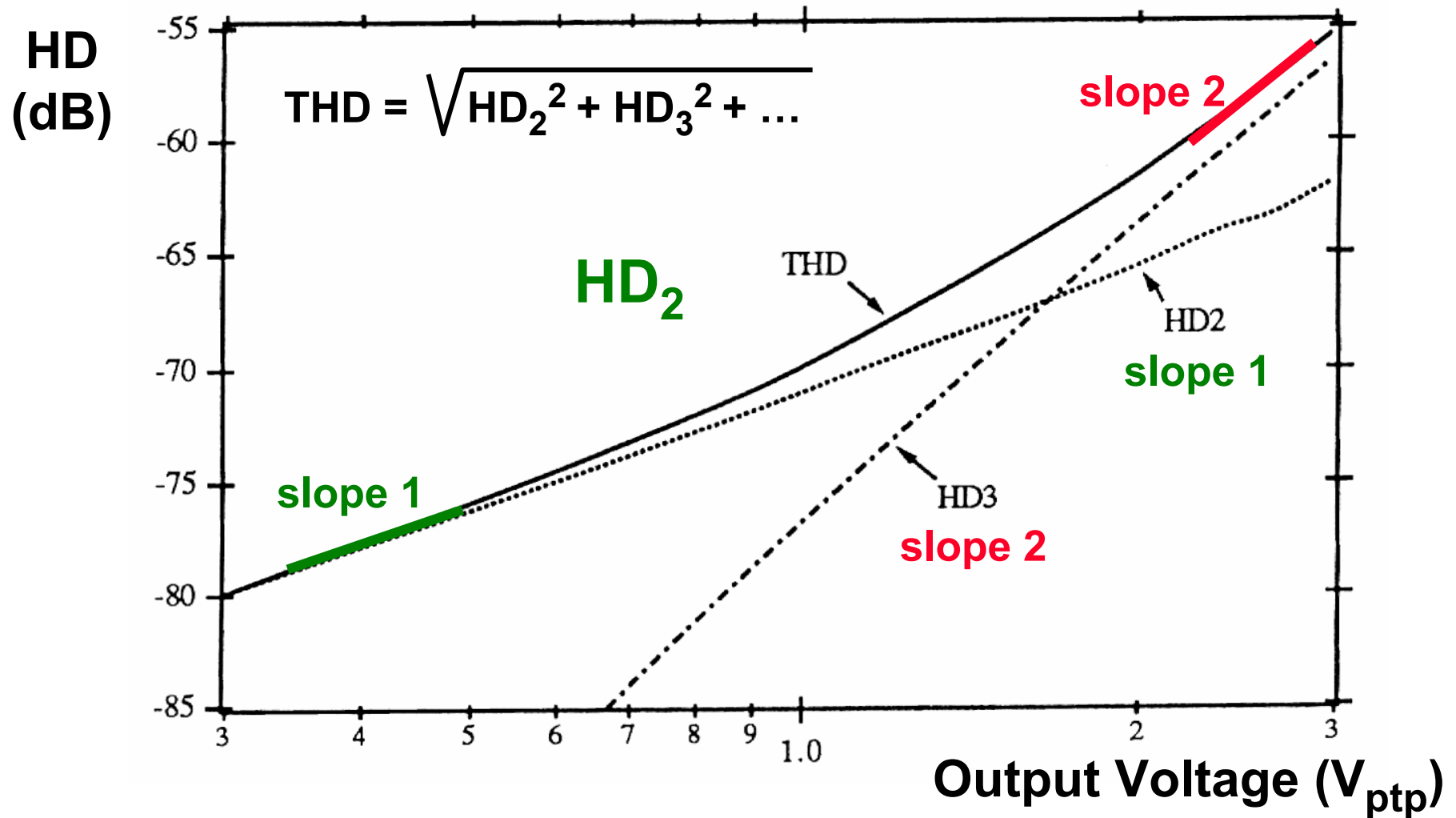

Output spectrum

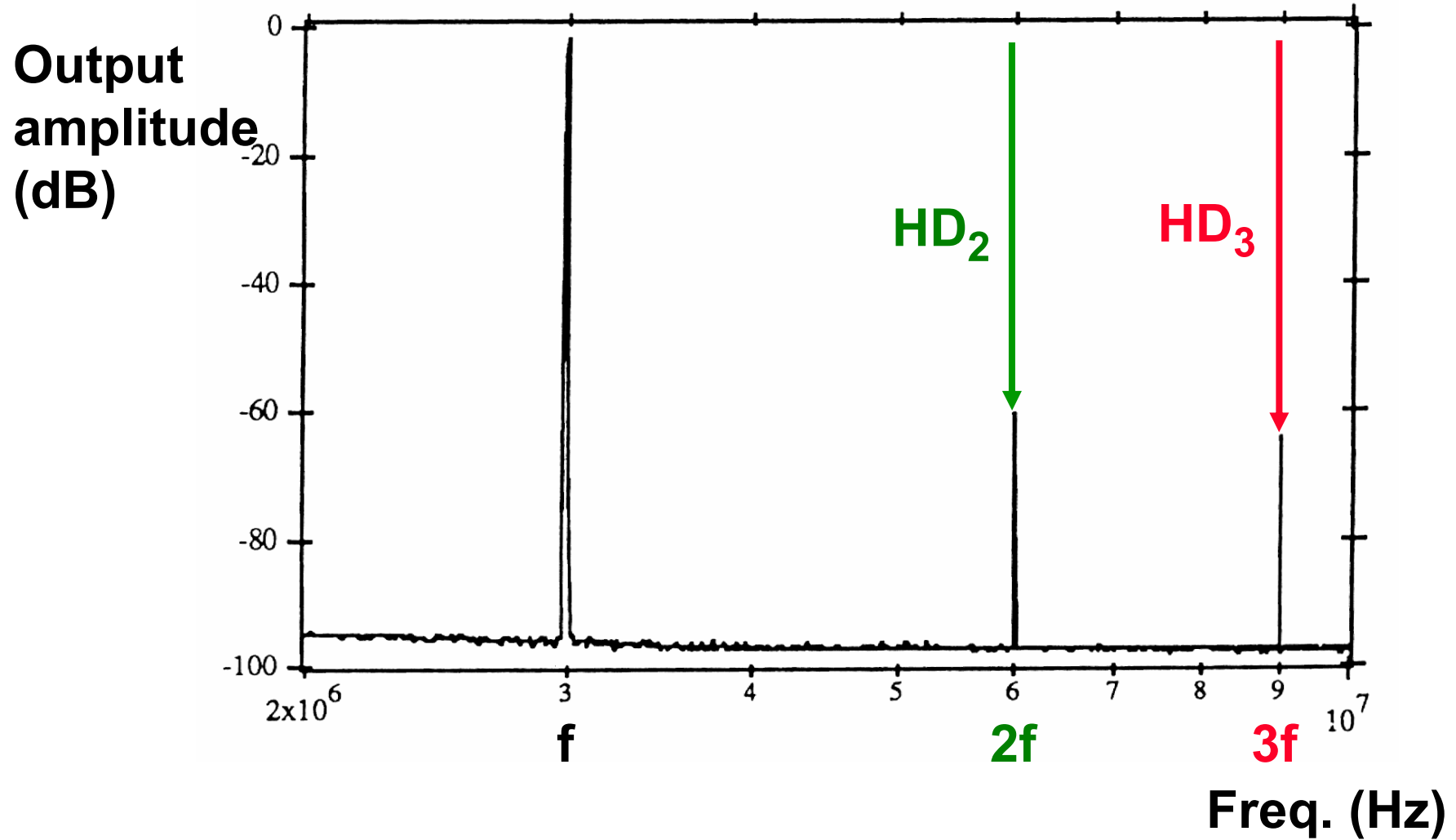

Definition of intermodulation distortion IM

$$y = a_0 + a_1 u + a_2 u^2 + a_3 u^3 + \dots$$

$$\text{with } u = U (\cos \omega_1 t + \cos \omega_2 t)$$

$$y = a_0 + \dots$$


$$\text{IM}_2 \text{ at } \omega_1 \pm \omega_2$$

$$\text{IM}_3 \text{ at } 2\omega_1 \pm \omega_2 \text{ and } \omega_1 \pm 2\omega_2$$


$$\text{IM}_2 = 2 \text{ HD}_2 = \frac{a_2}{a_1} U$$

$$\text{IM}_3 = 3 \text{ HD}_3 = \frac{3}{4} \frac{a_3}{a_1} U^2$$

IM components

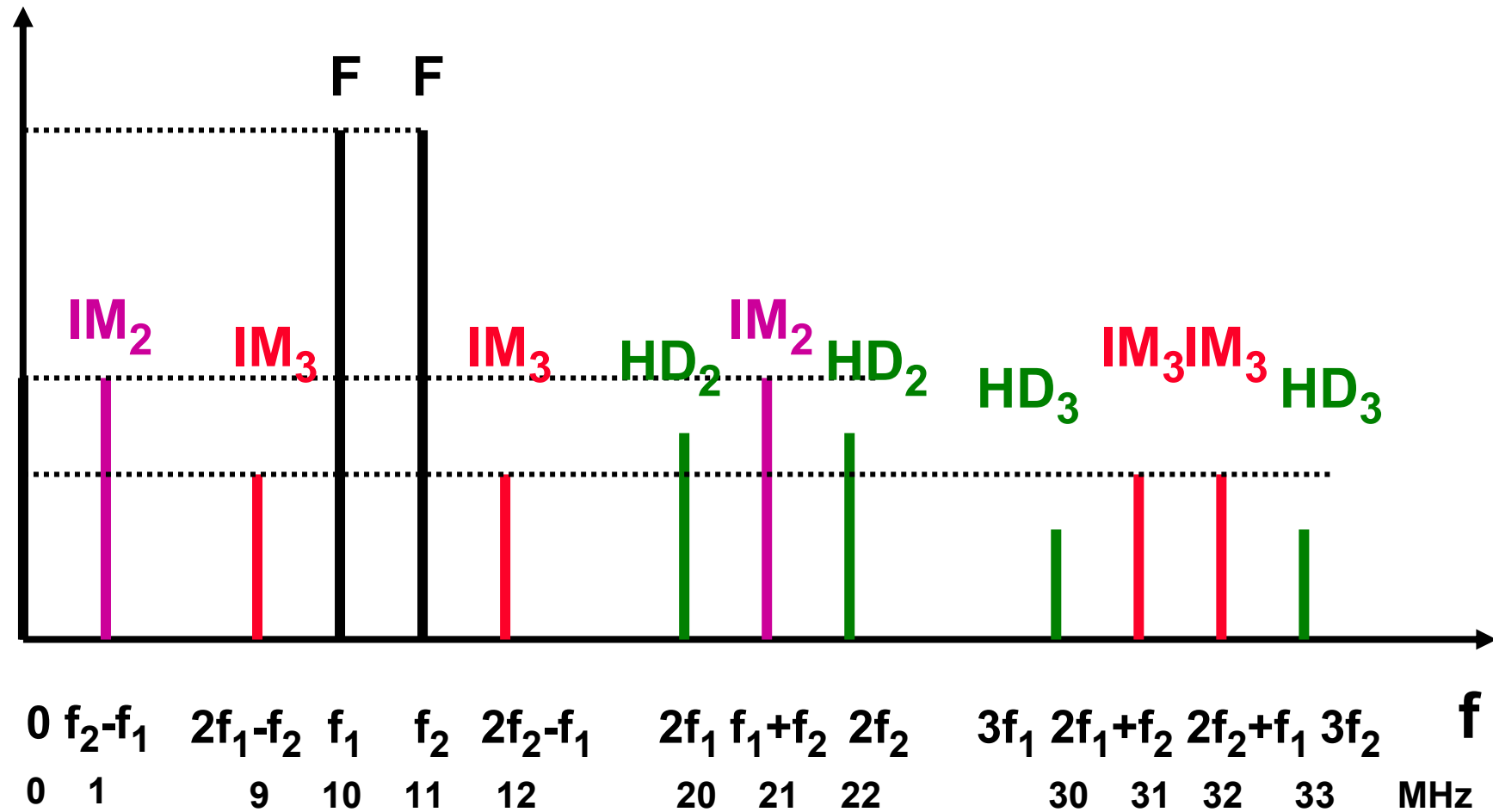


IM components

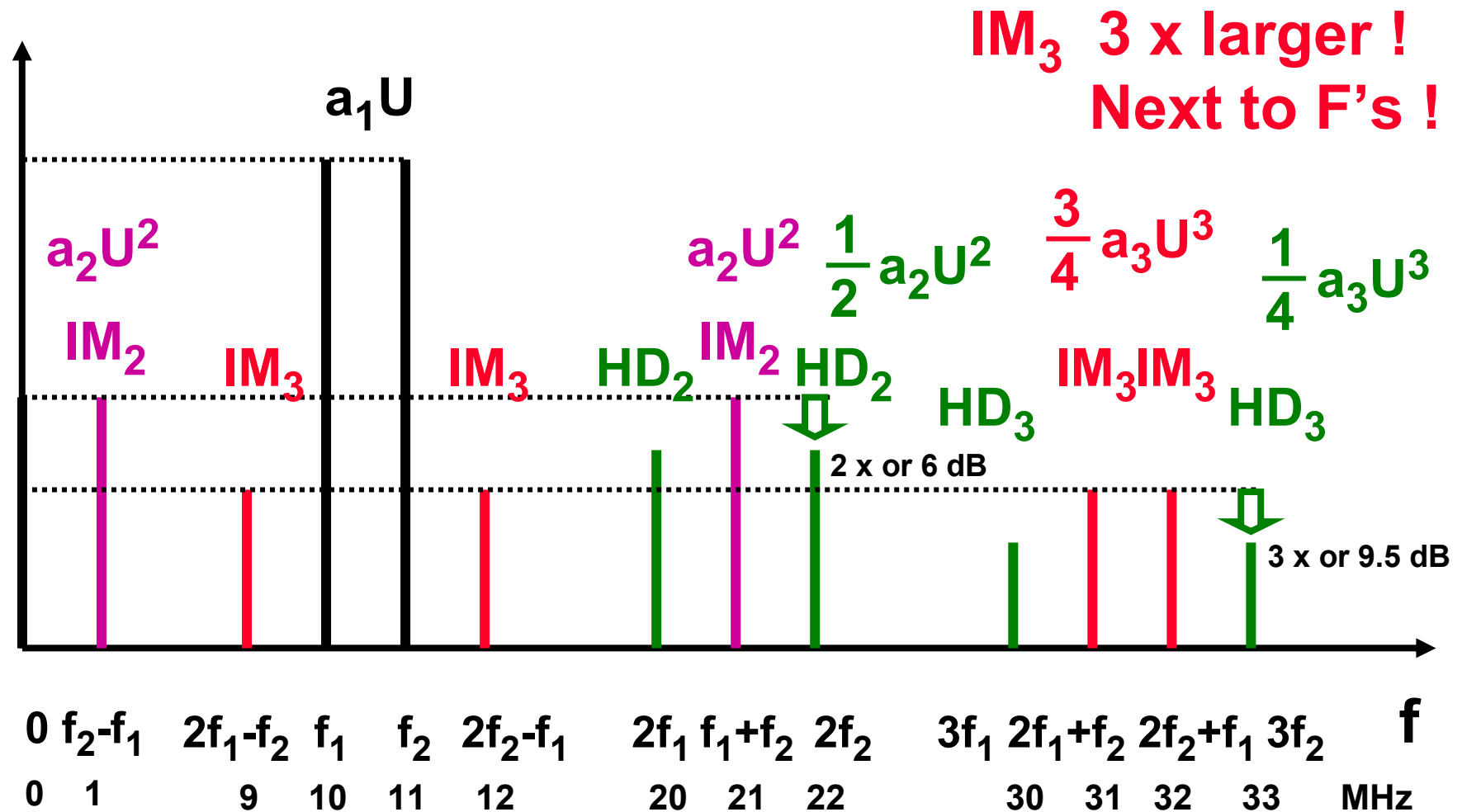

Output spectrum of amplifier for IM


Output
amplitude
(dB)

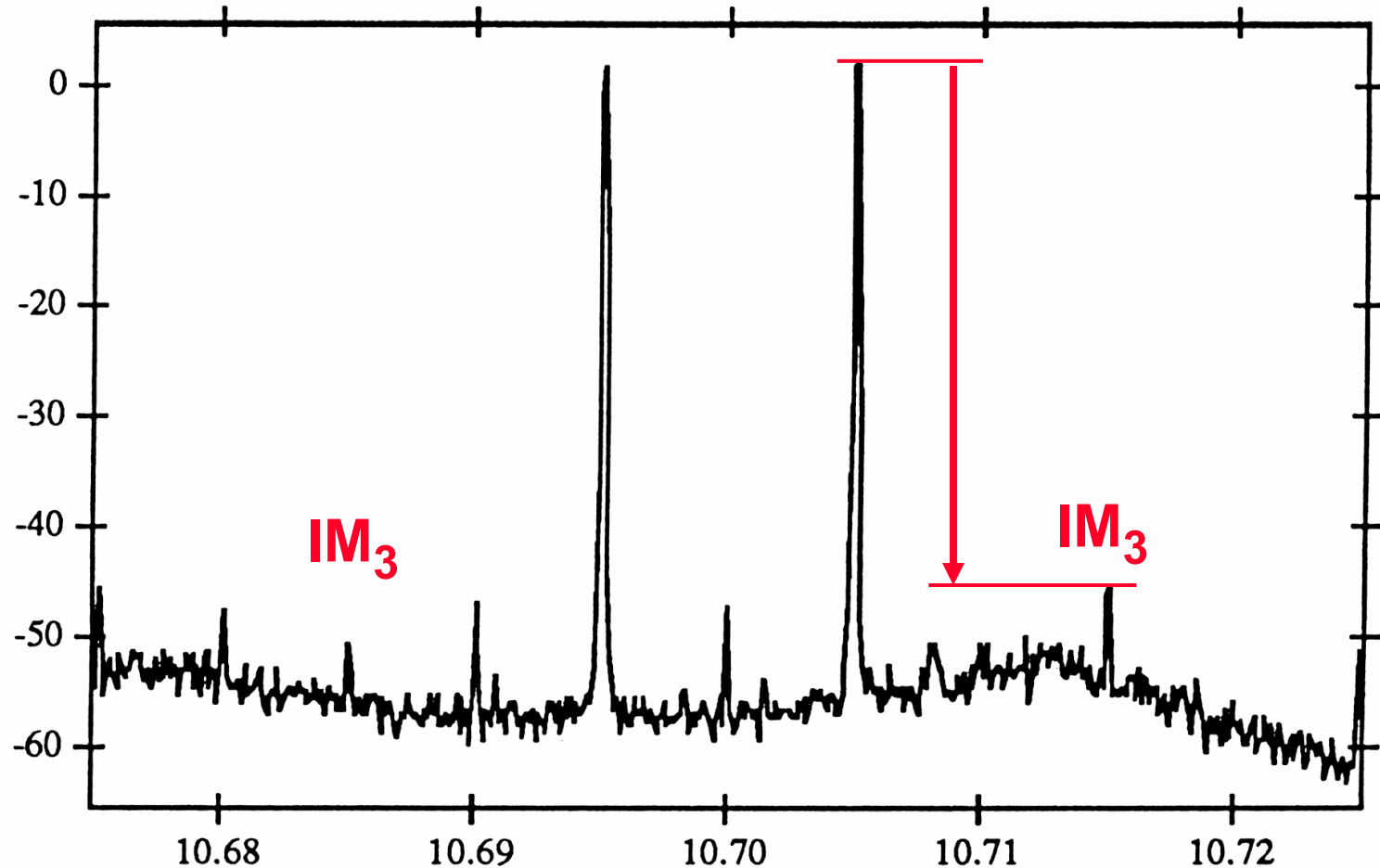


Ref.: J.Silva-Martinez, Kluwer 1993

Freq. (MHz)

Amplitude IM3 versus input signal

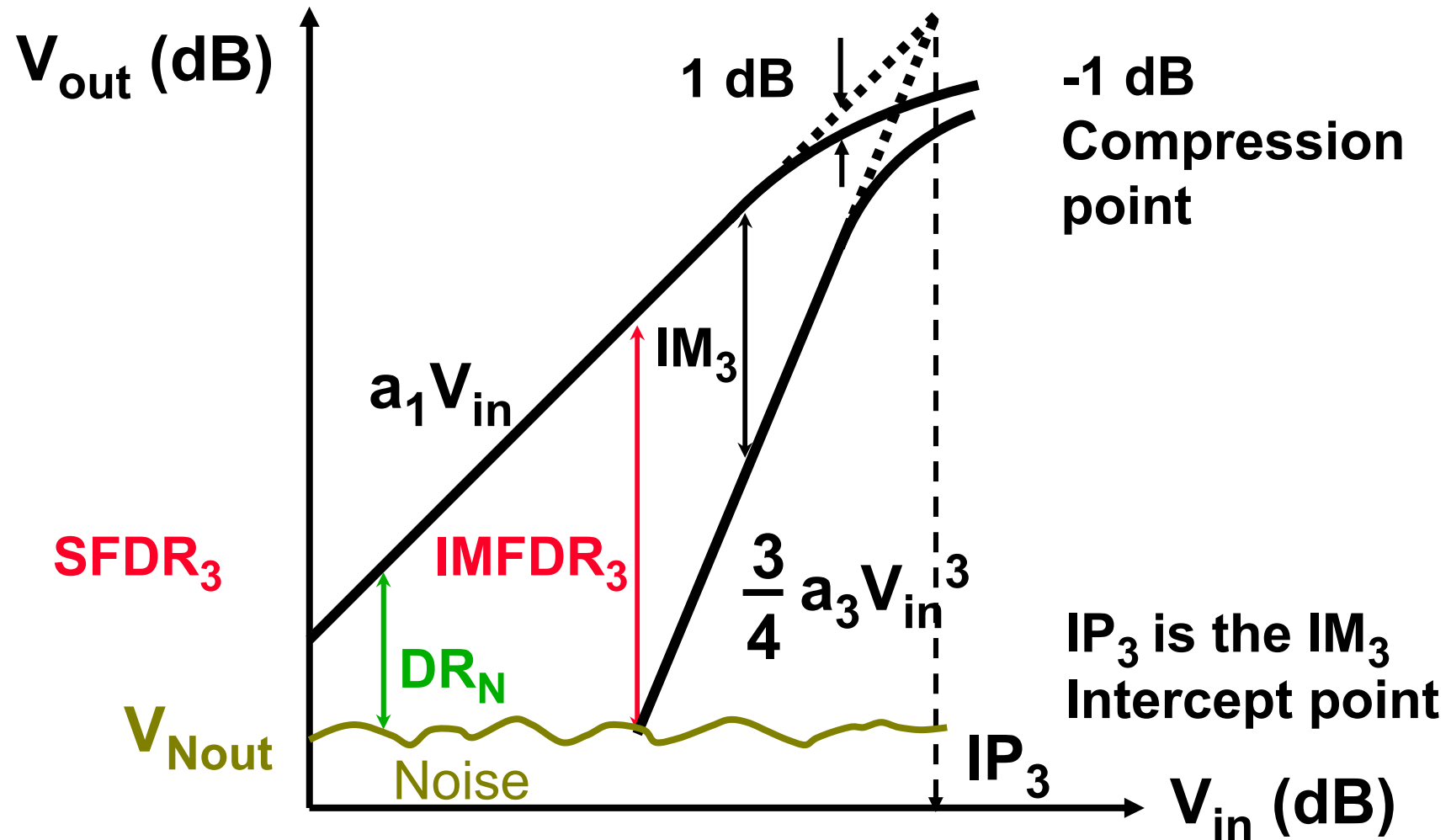


Relation IP_3 and IM_3

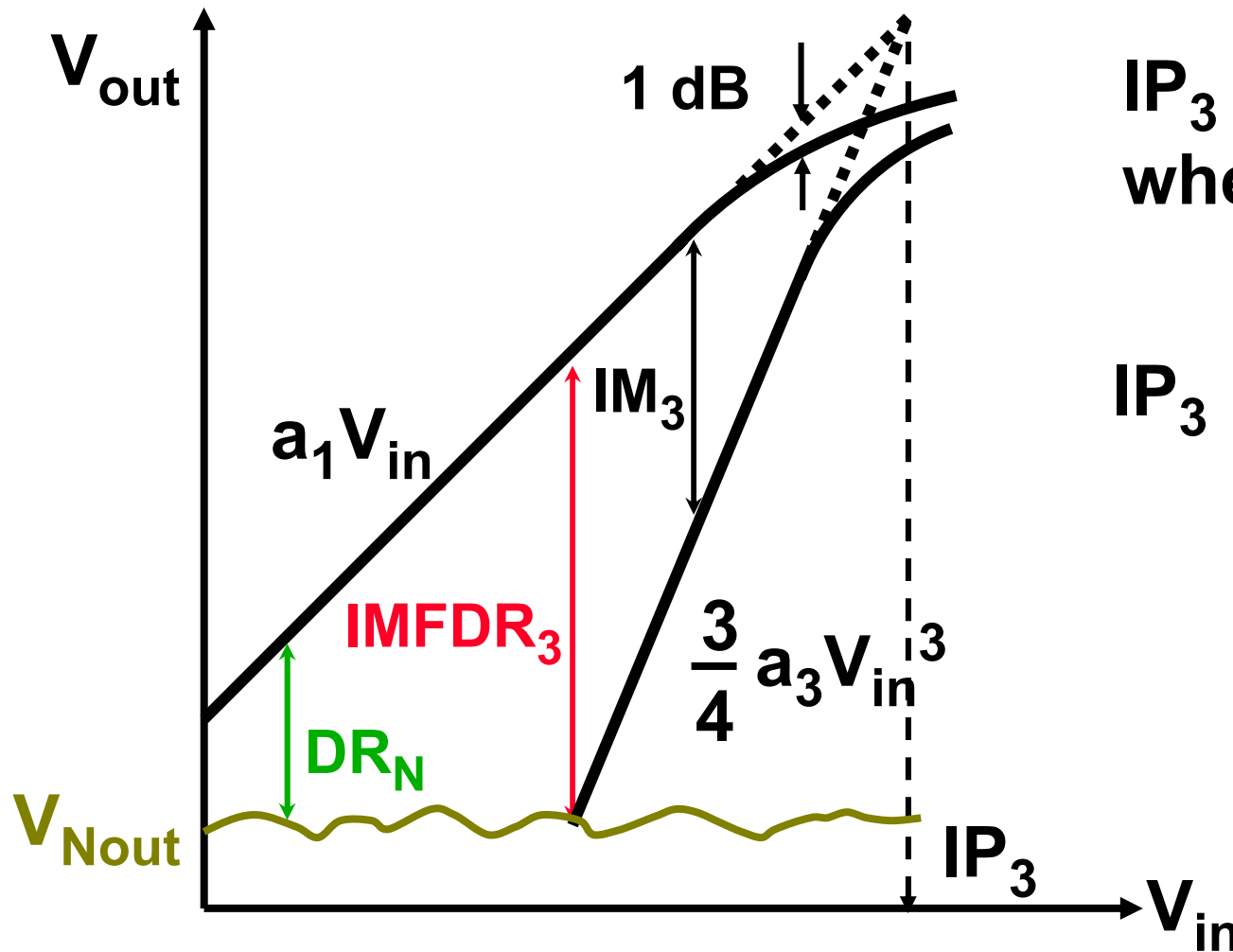

IP_3 is V_{in}
where $IM_3 = F$

$$\begin{aligned}
 IP_3 &= \sqrt{\frac{4}{3} \frac{a_1}{a_3}} \\
 &= V_{in} \frac{1}{\sqrt{IM_3}} \\
 &= V_{indB} - \frac{1}{2} IM_{3dB}
 \end{aligned}$$

Relation IMFDR₃ and IP₃

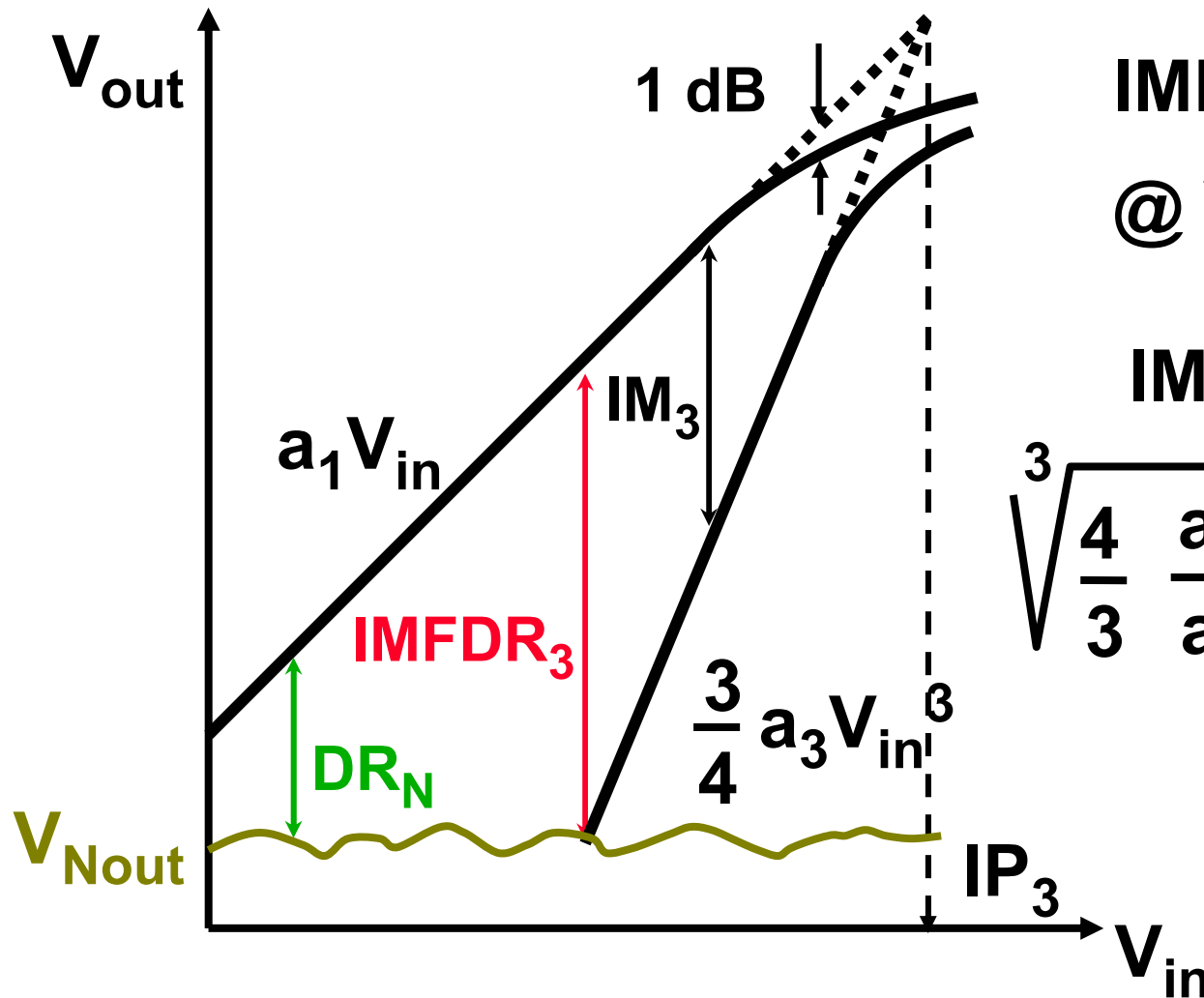

$$IMFDR_3 = \max DR$$


$$@ V_{Nout} = \frac{3}{4} a_3 V_{in}^3$$

$$IMFDR_3 =$$


$$\sqrt[3]{\frac{4}{3} \frac{a_1}{a_3} \frac{1}{V_{Nin}^2}} = \left(\frac{IP_3}{V_{Nin}} \right)^{2/3}$$

$$= \frac{2}{3} (IP_{3dB} - V_{Nin dB})$$

The IP₃ and -1 dB compression point

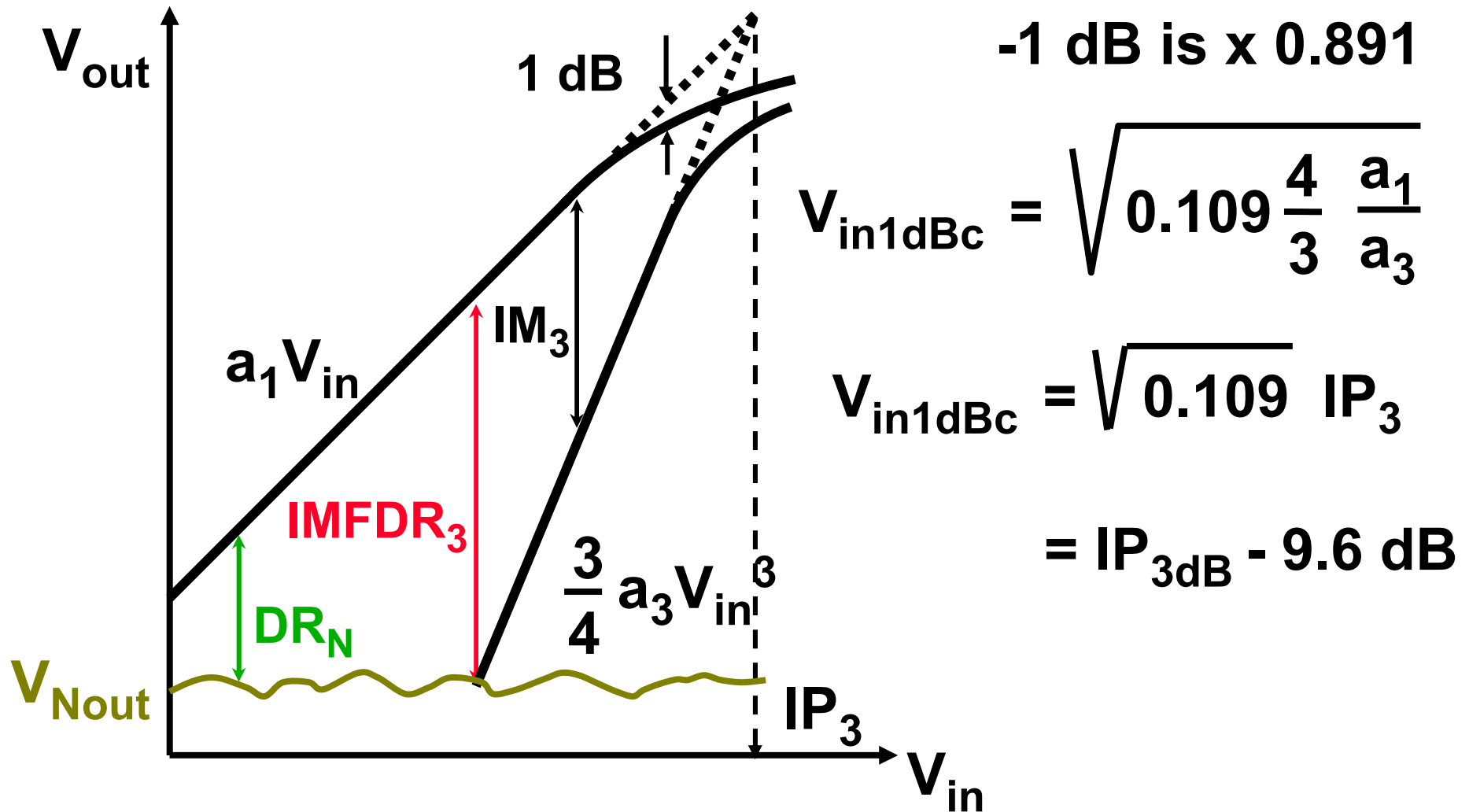

Relationship exercise

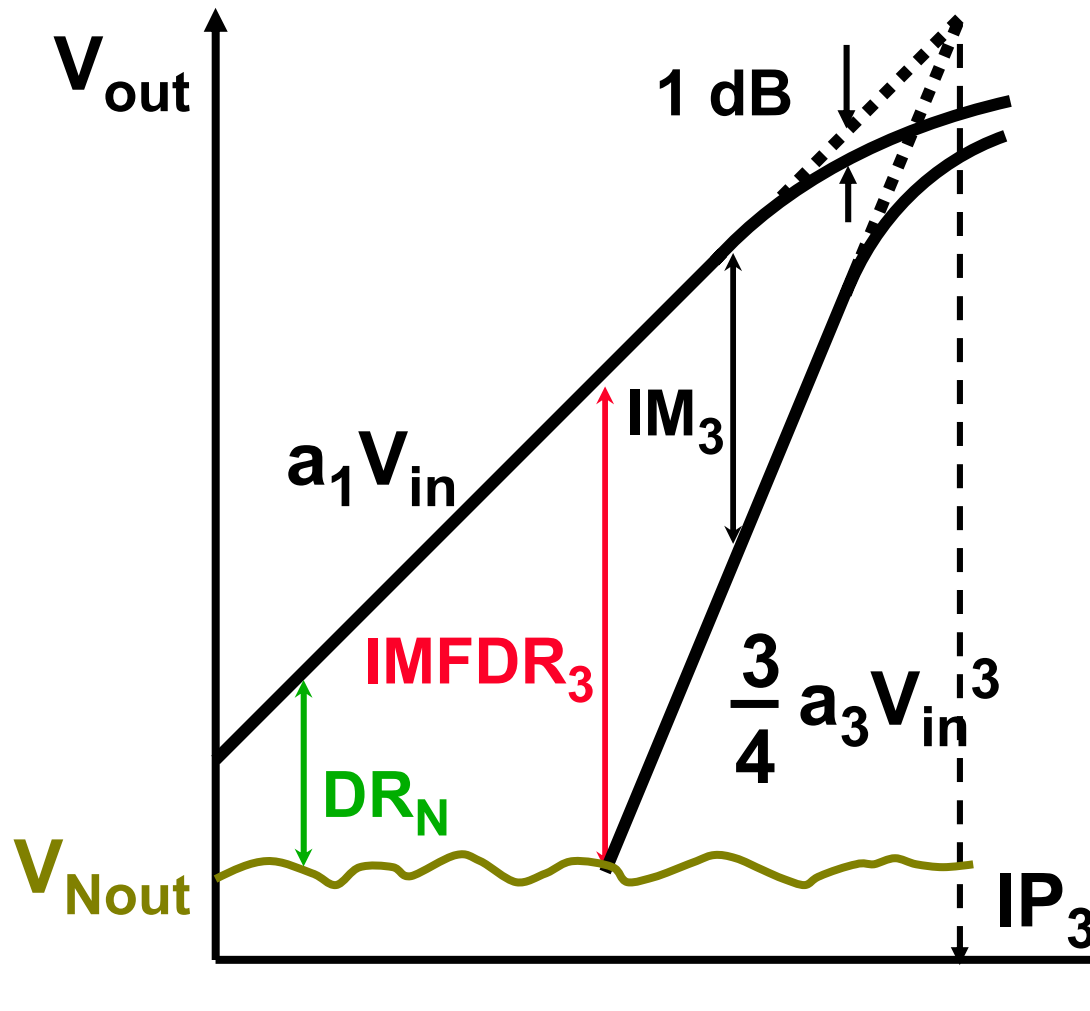

$$a_1 = 20 \quad a_3 = 0.4$$

$$V_{in} = 0.45 V_{RMS} \text{ or } 6 \text{ dBm}$$

$$IM_3 = 0.3 \% \text{ or } -50 \text{ dB}$$

$$IP_3 = 6 + 25 = 31 \text{ dBm}$$

$$V_{in1dBc} = 21 \text{ dBm}$$


$$V_{Nin} = 30 \mu V_{RMS} (-78 \text{ dBm})$$

$$IMFDR_3 = \frac{2}{3} 119 = 73 \text{ dB}$$

Definition of crossmodulation distortion CM

$$y = a_0 + a_1 u + a_2 u^2 + a_3 u^3 + \dots$$
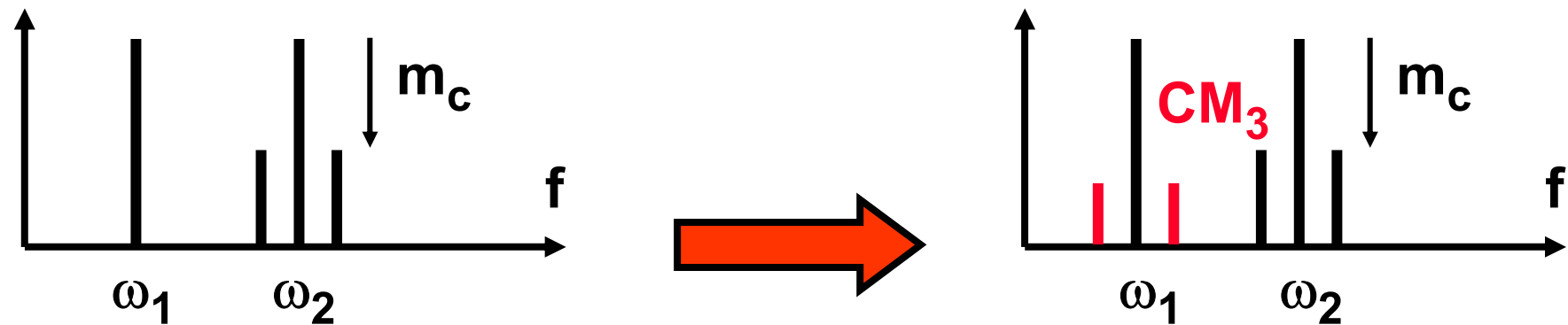
$$\text{with } u = U \cos \omega_1 t + U (1 + m_c \cos \omega_c t) \cos \omega_2 t$$



$$CM_3 = \frac{3}{4} m_c \frac{a_3}{a_1} U^2 = m_c IM_3$$

Table of contents

- ❑ Definitions : HD, IM, intercept point, ..
- ❑ Distortion in a MOST
 - Single-ended amplifier
 - Differential amplifier
- ❑ Distortion in a bipolar transistor
- ❑ Reduction of distortion by feedback
- ❑ Distortion in an opamp
- ❑ Other cases of distortion and guide lines

Distortion in a single-MOST amplifier

$$i_{DS} = K (v_{GS} - V_T)^2 \qquad K = K' \frac{W}{L}$$

$$I_{DS} + i_{ds} = K (V_{GS} + v_{gs} - V_T)^2$$


I_{DS} is the DC component

i_{DS} is the DC + ac component

i_{ds} is the ac component

I_{ds} is the amplitude of the ac component

DC and ac components

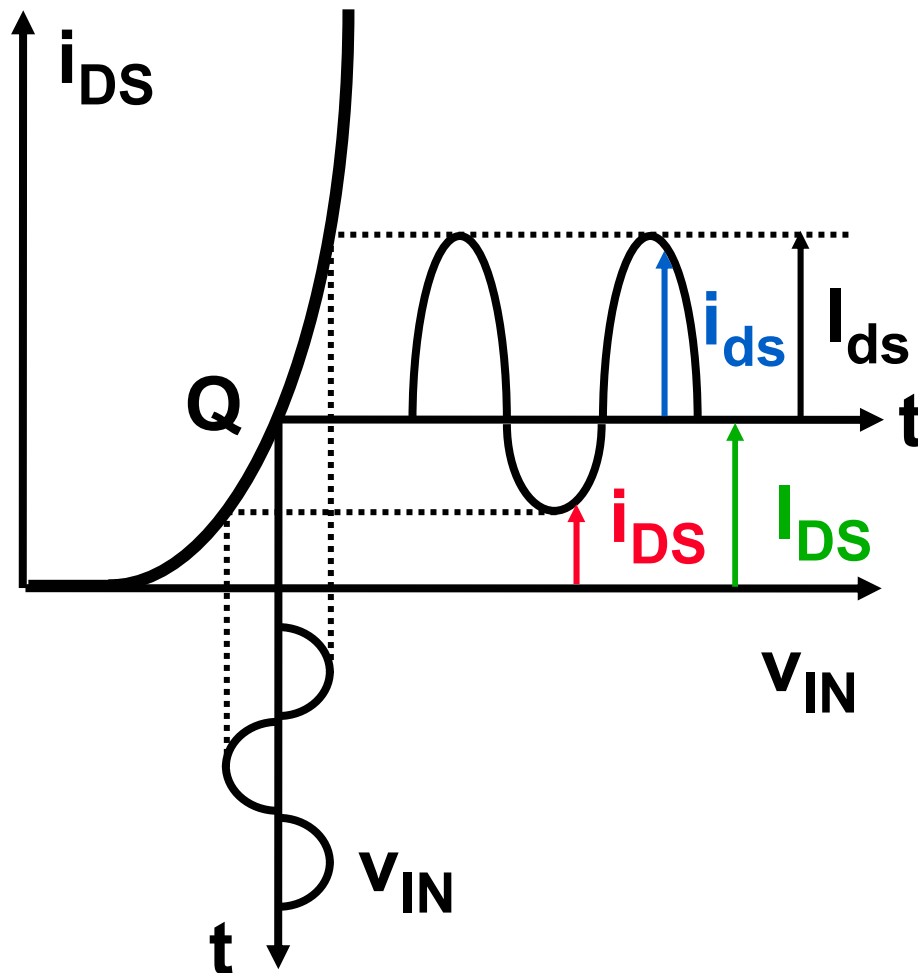

I_{DS} : DC component

i_{DS} : DC + ac component

i_{ds} : ac component

I_{ds} : amplitude of the ac component

Distortion in a single-MOST amplifier

$$I_{DS} = K (V_{GS} - V_T)^2 \quad K = K' \frac{W}{L}$$

$$I_{DS} + i_{ds} = K (V_{GS} + v_{gs} - V_T)^2$$

$$i_{ds} = K (V_{GS} + v_{gs} - V_T)^2 - K (V_{GS} - V_T)^2$$

$$i_{ds} = 2K (V_{GS} - V_T) v_{gs} + K v_{gs}^2$$

Coefficients a_1, a_2, a_3 by comparison

$$i_{ds} = 2K (V_{GS} - V_T) v_{gs} + K v_{gs}^2$$

$$\text{or } i_{ds} = g_1 v_{gs} + g_2 v_{gs}^2 + g_3 v_{gs}^3 + \dots$$

$$g_1 = 2K (V_{GS} - V_T)$$

$$g_2 = K$$

$$g_3 = 0$$

$$K = K' \frac{W}{L}$$

$$IM_2 = \frac{g_2}{g_1} v_{gs} = \frac{V_{gs}}{2(V_{GS} - V_T)} \quad \& \quad IM_3 = 0$$

Normalized current swing

$$i_{ds} = 2K (V_{GS} - V_T) v_{gs} + K v_{gs}^2 \quad I_{DS} = K (V_{GS} - V_T)^2$$

$$\text{or } y = a_1 u + a_2 u^2 + a_3 u^3 + \dots$$

$$y = \frac{i_{ds}}{I_{DS}} = \frac{2 v_{gs}}{V_{GS} - V_T} + \frac{1}{4} \left(\frac{2 v_{gs}}{V_{GS} - V_T} \right)^2$$

$$y = \frac{i_{ds}}{I_{DS}} = u + \frac{1}{4} u^2 \qquad U = \frac{V_{gs}}{(V_{GS} - V_T)/2}$$

y is the relative current swing !

Numerical example

The peak value of V_{gs} is $V_{gsp} = 100 \text{ mV}$

(then $V_{gsRMS} = 100 / \sqrt{2} = 71 \text{ mV}_{RMS}$)

if $V_{GS} - V_T = 0.5 \text{ V}$ then $V_{gsp} / [2(V_{GS} - V_T)] = 0.1$

gives $IM_2 = 10 \%$ ($HD_2 = 5 \%$) & $IM_3 = 0$

The relative current swing $U = 0.1/0.25 = 0.4 !$

More coefficients $a_1, a_2, a_3 \dots$

In general

$$\begin{aligned} i_{ds} = & g_m v_{gs} + K_{2gm} v_{gs}^2 + K_{3gm} v_{gs}^3 + \\ & g_o v_{ds} + K_{2go} v_{ds}^2 + K_{3go} v_{ds}^3 + \\ & g_{mb} v_{bs} + K_{2gmb} v_{bs}^2 + K_{3gmb} v_{bs}^3 + \\ & K_{2gm\&gmb} v_{gs} v_{bs} + K_{3,2gm\&gmb} v_{gs}^2 v_{bs} \\ & \quad + K_{3,gm\&2gmb} v_{gs} v_{bs}^2 + \\ & \dots + \\ & K_{3gm\&gmb\&go} v_{gs} v_{ds} v_{bs} \end{aligned}$$

Distortion of a MOST diode


$$i_{DS} = K (v_{DS} - V_T)^2$$

$$y = \frac{i_{ds}}{I_{DS}} = \frac{2 v_{ds}}{V_{DS} - V_T} + \frac{1}{4} \left(\frac{2 v_{ds}}{V_{DS} - V_T} \right)^2$$


$$y = \frac{i_{ds}}{I_{DS}} = u + \frac{1}{4} u^2 \qquad U = \frac{V_{ds}}{(V_{DS} - V_T)/2}$$

Same as for a MOST transistor amplifier !

The zero HD3 point for smaller L

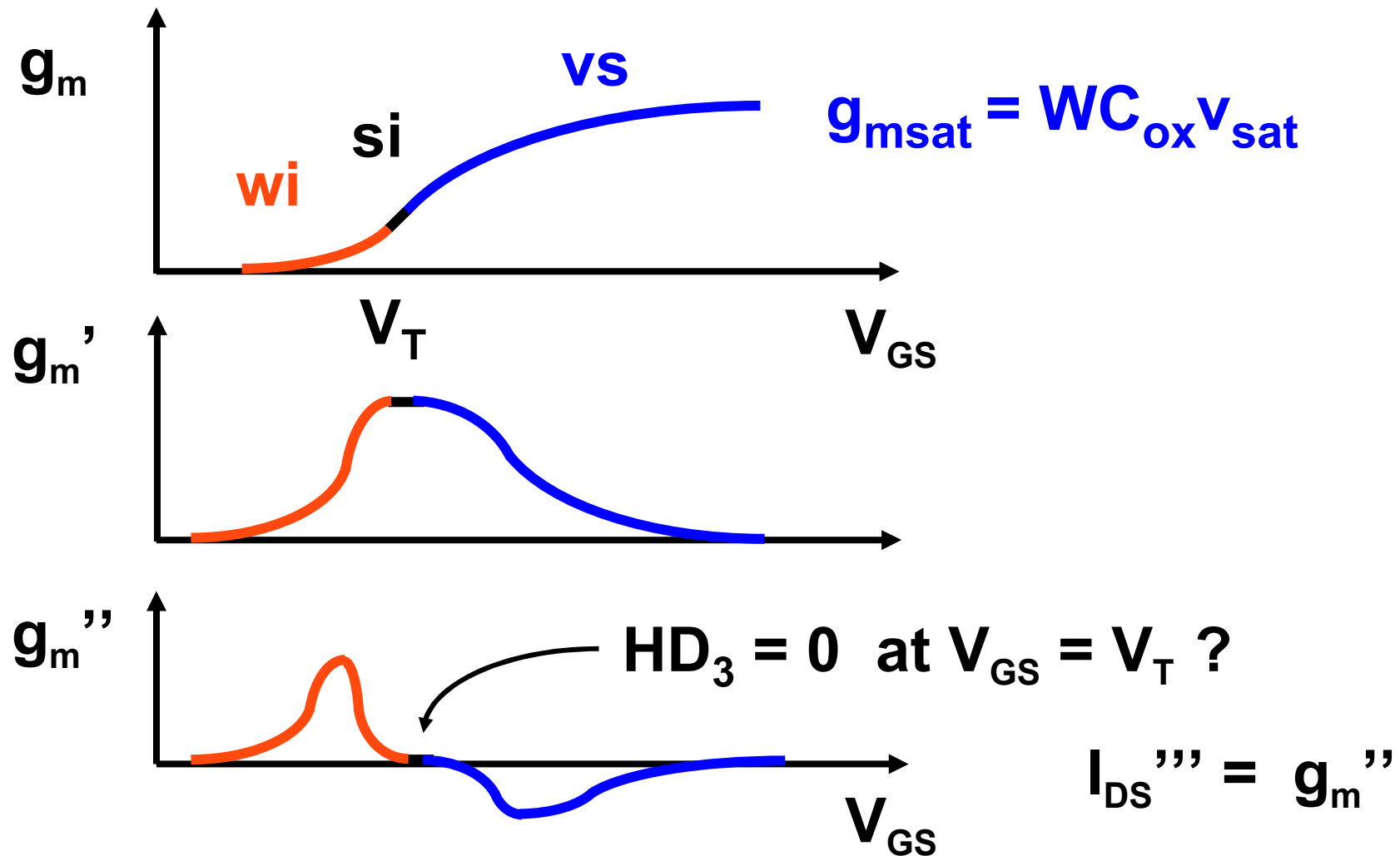


Derivatives of g_m

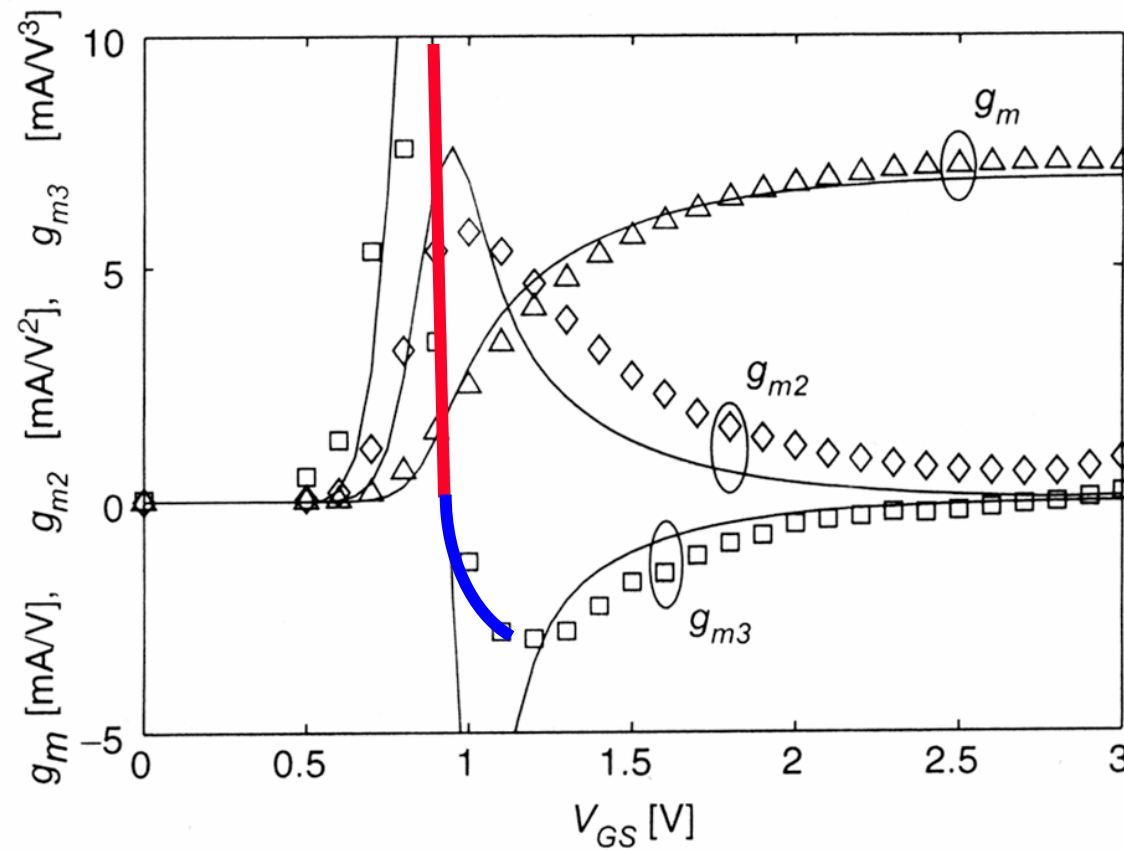

$W = 60 \mu\text{m}$
 $L = 0.6 \mu\text{m}$
 $V_{DS} = 2 \text{ V}$

Ref. Fager JSSC Jan. 2004, 24-33

A differential pair is symmetrical

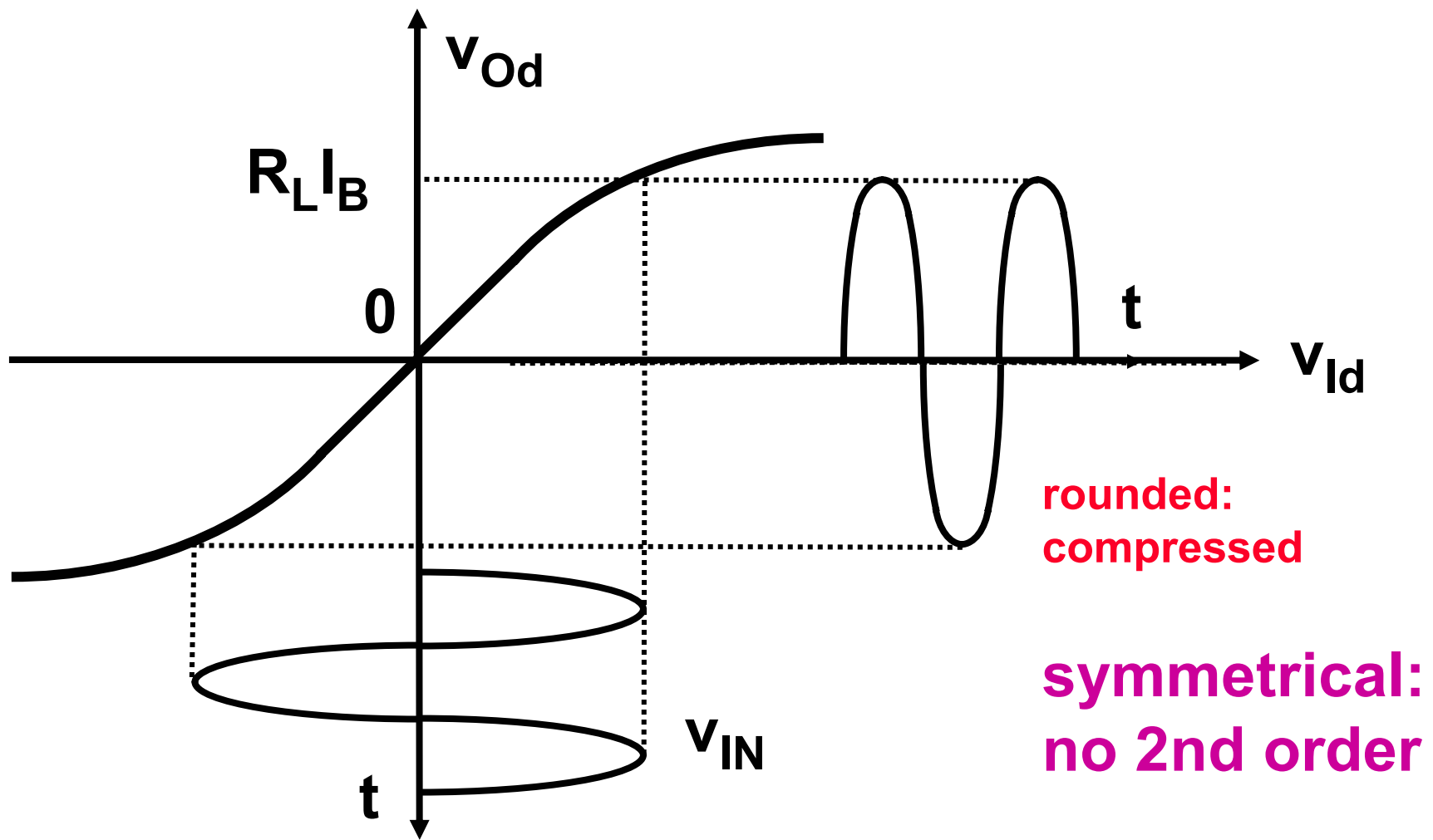

Distortion in MOST differential pair

$$y = \frac{i_{Od}}{I_B} = \frac{v_{Id}}{V_{GS} - V_T} \sqrt{1 - \frac{1}{4} \left(\frac{v_{Id}}{V_{GS} - V_T} \right)^2}$$

v_{Id} is the differential input voltage

i_{Od} is the differential output current ($g_m v_{Id}$) or
twice the circular current $g_m v_{Id} / 2$

I_B is the total DC current in the pair

Note that
$$g_m = \frac{I_B}{V_{GS} - V_T} = K' \frac{W}{L} (V_{GS} - V_T)$$

Distortion in MOST differential amplifier

$$y = \frac{i_{Od}}{I_B} = \frac{V_{Id}}{V_{GS} - V_T} \sqrt{1 - \frac{1}{4} \left(\frac{V_{Id}}{V_{GS} - V_T} \right)^2}$$

$$y = \frac{i_{Od}}{I_B} = U \sqrt{1 - \frac{1}{4} U^2} \approx U - \frac{1}{8} U^3 \quad \sqrt{1-x} \approx 1 - \frac{x}{2}$$


$$IM_2 = 0 \quad \boxed{IM_3 = \frac{3}{32} U^2}$$

$$U = \frac{V_{Id}}{V_{GS} - V_T}$$

U is the relative current swing

$$IP_3 = 4 \sqrt{\frac{2}{3}} (V_{GS} - V_T) \approx 3.3 (V_{GS} - V_T)$$

Distortion in linear region

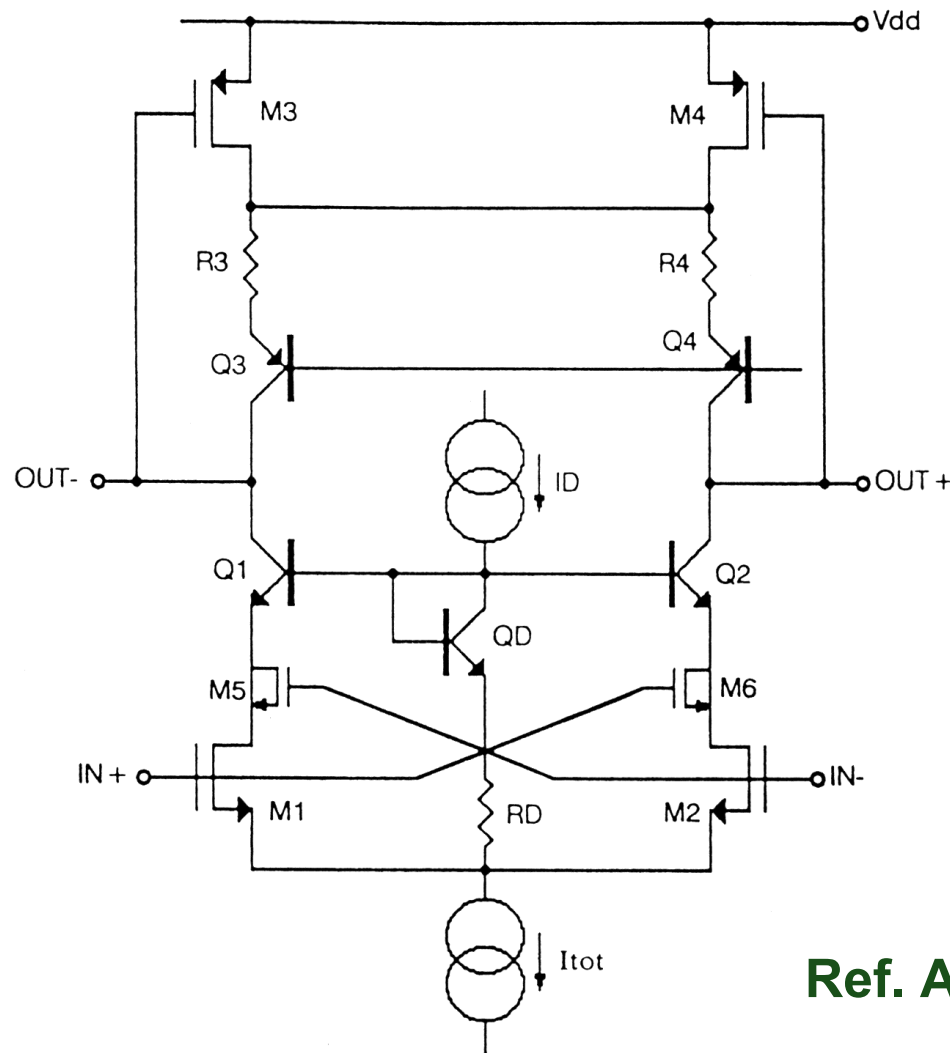

$$V_{DS1} = R_D I_D \approx 0.2 \text{ V}$$

$$I_{DS1} = \beta_1 V_{DS1} (V_{GS1} - V_T)$$

$g_{m1} = \beta_1 V_{DS1}$ is constant

Low distortion !

Ref. Alini,JSSC, Dec.92, pp.1905-1915

Table of contents

- ☐ Definitions : HD, IM, intercept point, ..
- ☐ Distortion in a MOST
 - Single-ended amplifier
 - Differential amplifier
- ☐ Distortion in a bipolar transistor
- ☐ Reduction of distortion by feedback
- ☐ Distortion in an opamp
- ☐ Other cases of distortion and guide lines

Distortion in a bipolar transistor amplifier

$$I_{CE} = I_S \exp\left(\frac{V_{BE}}{kT_e/q}\right)$$

I_{CE} DC component

i_{CE} DC + ac component

i_{ce} ac component

I_{ce} amplitude of
the ac component

$$I_{CE} + i_{ce} = I_S \exp\left(\frac{V_{BE} + v_{be}}{kT_e/q}\right)$$

$$1 + y = \exp\left(\frac{v_{be}}{kT_e/q}\right)$$

$$\approx \exp(u) = 1 + u + \frac{u^2}{2} + \frac{u^3}{6} + \dots \quad \text{if } u \ll 1$$

Distortion in a bipolar transistor amplifier

$$y \approx u + \frac{u^2}{2} + \frac{u^3}{6} + \dots \qquad U = \frac{V_{be}}{kT_e/q}$$

is the non-linear equation

y is the relative current swing !

$$a_1 = 1$$

$$a_2 = 1/2$$

$$a_3 = 1/6$$

$$IM_2 = \frac{a_2}{a_1} U = \frac{1}{2} \frac{V_{be}}{kT_e/q}$$

$$IM_3 = \frac{3}{4} \frac{a_3}{a_1} U^2 = \frac{1}{8} \left(\frac{V_{be}}{kT_e/q} \right)^2$$

Numerical example

1. Relative current swing is 10 %

$y_p = 0.1$ gives $IM_2 = 5\%$ ($HD_2 = 2.5\%$)

$$IM_3 = 0.125\% \text{ (} HD_3 = 0.04\% \text{)}$$

As a result $V_{bep} = y_p(kT_e/q) = 2.6 \text{ mV}_p$ (1.8 mV_{RMS})

$IP_3 = \sqrt{8} (kT_e/q) = 74 \text{ mV}_p$ or 50 mV_{RMS} or -13 dBm

2. $V_{bep} = 100 \text{ mV}$

then $y_p = 0.1/0.026 \approx 4$ (must be $\ll 1$!!)

gives $IM_2 = ??$ Too high distortion !!

Distortion in a diode

$$i_D = I_S \exp\left(\frac{V_D}{kT_e/q}\right) \quad y \approx u + \frac{u^2}{2} + \frac{u^3}{6} + \dots$$

$$y = \frac{I_d}{I_D} = u + \frac{u^2}{2} + \frac{u^3}{6} \quad U = \frac{V_d}{kT_e/q}$$

Same as for a Bipolar transistor amplifier !

Distortion in bipolar differential amplifier

$$y = \frac{i_{Od}}{I_B} = \tanh \frac{V_{Id}}{2kT_e/q}$$

$$\tanh x = \frac{e^x - e^{-x}}{e^x + e^{-x}} \\ \approx x - \frac{1}{3} x^3$$

$$y = \frac{i_{Od}}{I_B} \approx U - \frac{1}{3} U^3$$

$$U = \frac{V_{Id}}{2kT_e/q}$$

$$IM_2 = 0$$

$$IM_3 = \frac{1}{4} U^2$$

U is the relative current swing

$$IP_3 = 4 kT_e/q$$

Distortion in a resistor or capacitor


$$R = R_0 (1 + a_1 V + a_2 V^2 + \dots) \quad [\approx \text{JFET with large } V_P]$$

**For diffused resistors : $a_1 \approx 5 \text{ ppm/V}$
 $a_2 \approx 1 \text{ ppm/V}^2$**

$$C = C_0 (1 + a_1 V + a_2 V^2 + \dots)$$

**For poly-poly caps : $a_1 \approx 20 \text{ ppm/V}$
 $a_2 \approx 2 \text{ ppm/V}^2$**

Non-linearity depletion capacitance

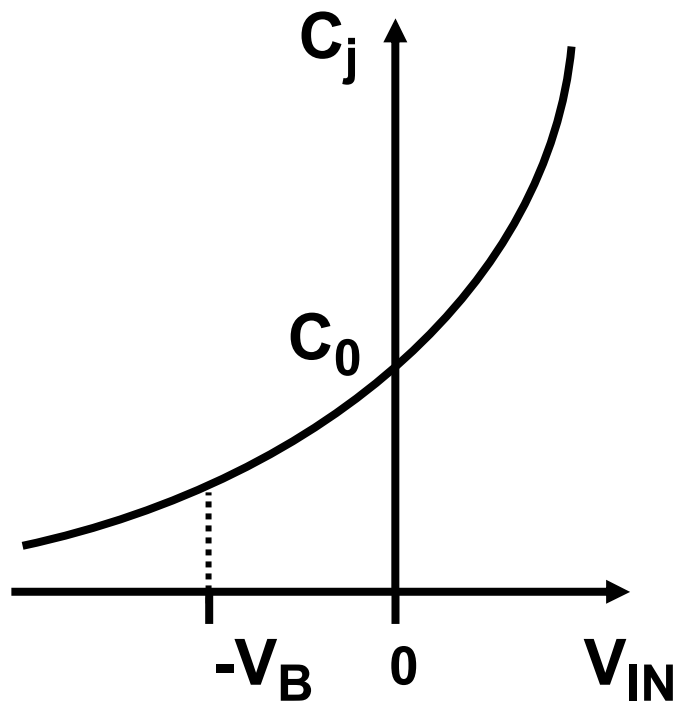

$$C_j = \frac{C_0}{\sqrt{1 - \frac{V_{IN}}{\Phi}}}$$

$$V_{IN} = V_B + v_{in}$$


$$C_j = \frac{C_0}{\sqrt{1 + \frac{V_B}{\Phi}}} \frac{1}{\sqrt{1 + \frac{v_{in}}{\underbrace{V_B + \Phi}_x}}}$$

$$C_j = C_{0B} (1 + x)^{-1/2} = C_{0B} (1 - 1/2 x + 3/8 x^2 - 5/16 x^3 + ..)$$

Table of contents

- ❑ **Definitions : HD, IM, intercept point, ..**
- ❑ **Distortion in a MOST**
 - **Single-ended amplifier**
 - **Differential amplifier**
- ❑ **Distortion in a bipolar transistor**
- ❑ **Reduction of distortion by feedback**
- ❑ **Distortion in an opamp**
- ❑ **Other cases of distortion and guide lines**

Distortion reduction by feedback

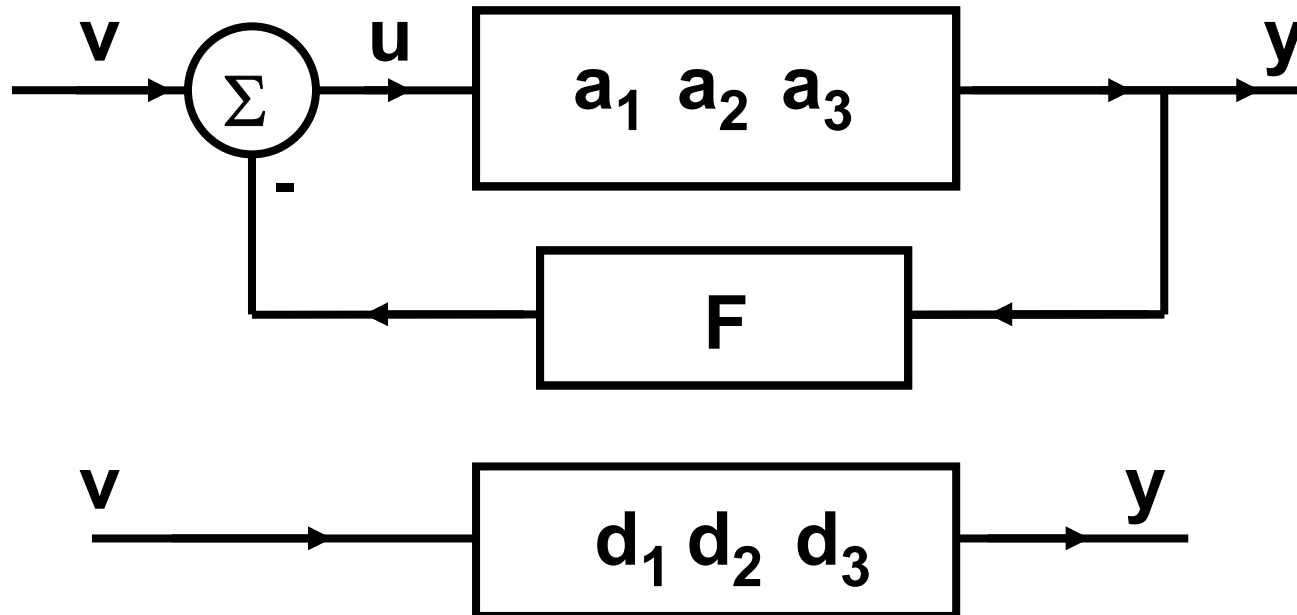

$$u = v - Fy$$


$$y = a_1 u + a_2 u^2 + a_3 u^3$$

$$y = d_1 v + d_2 v^2 + d_3 v^3$$

} elim. u

} elim. y {
coeff v : d_1
coeff v^2 : d_2
coeff v^3 : d_3

Distortion reduction by feedback

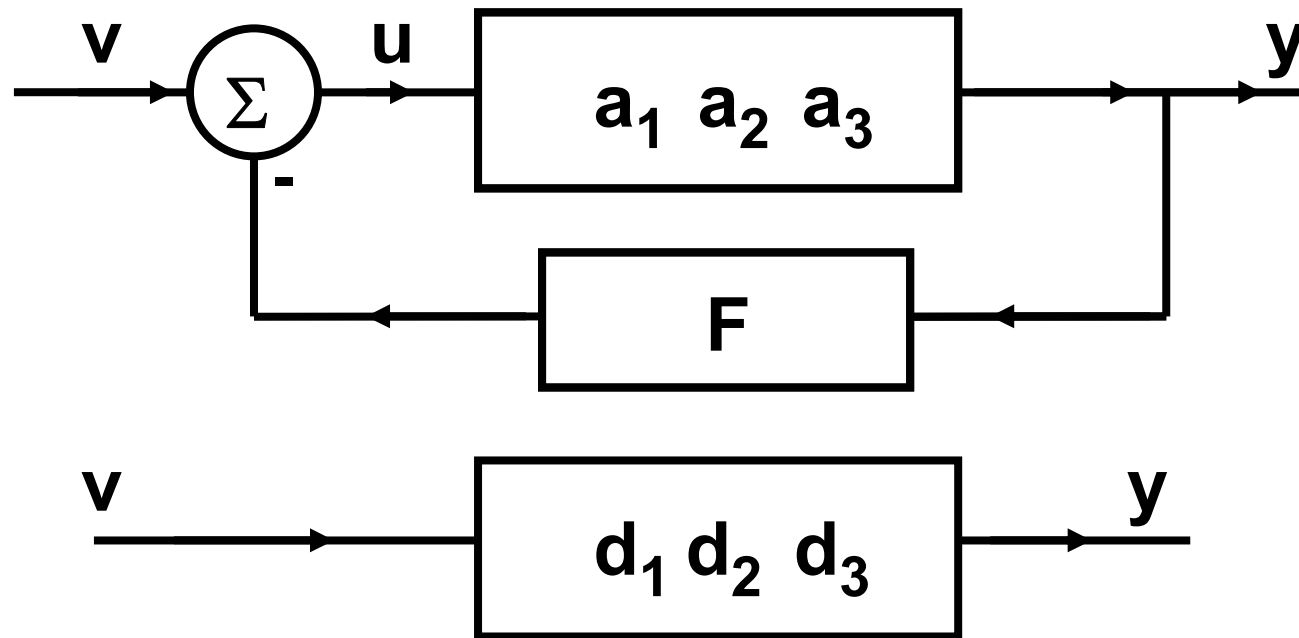

$$u = v - Fy$$

$$d_1 = \frac{a_1}{1 + T} \approx \frac{1}{F}$$

$$d_2 = \frac{a_2}{(1 + T)^3}$$

Loop gain $1+T = 1+a_1F$

u is $(1+T)$ times smaller than v :

v is reduced by loop gain $(1+T)$

$$d_3 = \frac{a_3 (1 + T) - 2F a_2^2}{(1 + T)^5}$$

Distortion components with feedback

$$IM_{2f} = \frac{d_2}{d_1} V = \frac{a_2}{a_1} \frac{V}{(1+T)^2} = \frac{a_2}{a_1} \underbrace{\frac{1}{(1+T)}}_{\text{reduction by loop gain}} \underbrace{\frac{V}{(1+T)}}_{\text{reduction in current swing}}$$

$$IM_{3f} = \frac{3}{4} \frac{d_3}{d_1} V^2 = \frac{3}{4} \left[\underbrace{\frac{a_3}{a_1} \frac{1}{(1+T)}}_{\text{compression}} - \underbrace{\left(\frac{a_2}{a_1} \right)^2 \frac{2T}{(1+T)^2}}_{\text{expansion}} \right] \underbrace{\frac{V^2}{(1+T)^2}}_{\text{reduction in current swing}}$$

Distortion components with feedback : examples

$$IM_{3f} = \frac{3}{4} \frac{d_3}{d_1} V^2 = \frac{3}{4} \left[\frac{a_3}{a_1} \frac{1}{(1+T)} - \left(\frac{a_2}{a_1} \right)^2 \frac{2T}{(1+T)^2} \right] \frac{V^2}{(1+T)^2}$$

For large T :

$$\frac{a_3 a_1 - 2 a_2^2}{a_1^2} \frac{1}{T} = \frac{a_3}{a_1} \left(1 - \frac{2 a_2^2}{a_1 a_3} \right) \frac{1}{T}$$

MOST : $a_3 = 0$: a_2 dominant

Bipolar : $a_1 = 1$ $a_2 = 1/2$ $a_3 = 1/6$: a_2 dominant

Diff. pair : $a_2 = 0$: a_3 dominant

Emitter resistor to reduce distortion IM_{2f}

$$T = g_m R_E = \frac{V_{RE}}{kT_e/q} \qquad \frac{a_2}{a_1} = \frac{1}{2}$$

$$IM_{2f} = \frac{1}{2} \frac{1}{(1+T)^2} \frac{V_{in}}{kT_e/q} = \frac{1}{(1+T)} \frac{U}{2}$$

$$U = \frac{1}{(1+T)} \frac{V_{in}}{kT_e/q} \text{ is the relative current swing}$$

IM_{2f} decreases linearly with T for constant U !

Emitter resistor to reduce distortion IM_{3f}

$$IM_{3f} = \frac{1 - 2T}{(1 + T)^2} \frac{U^2}{8}$$


$$\frac{a_2}{a_1} = \frac{1}{2} \quad \frac{a_3}{a_1} = \frac{1}{6}$$

$$U = \frac{1}{(1 + T)} \frac{V_{in}}{kT_e/q} \quad \text{is the relative current swing}$$

Null for $T = 0.5$

IM_{3f} also decreases with T for constant U
for large T !!

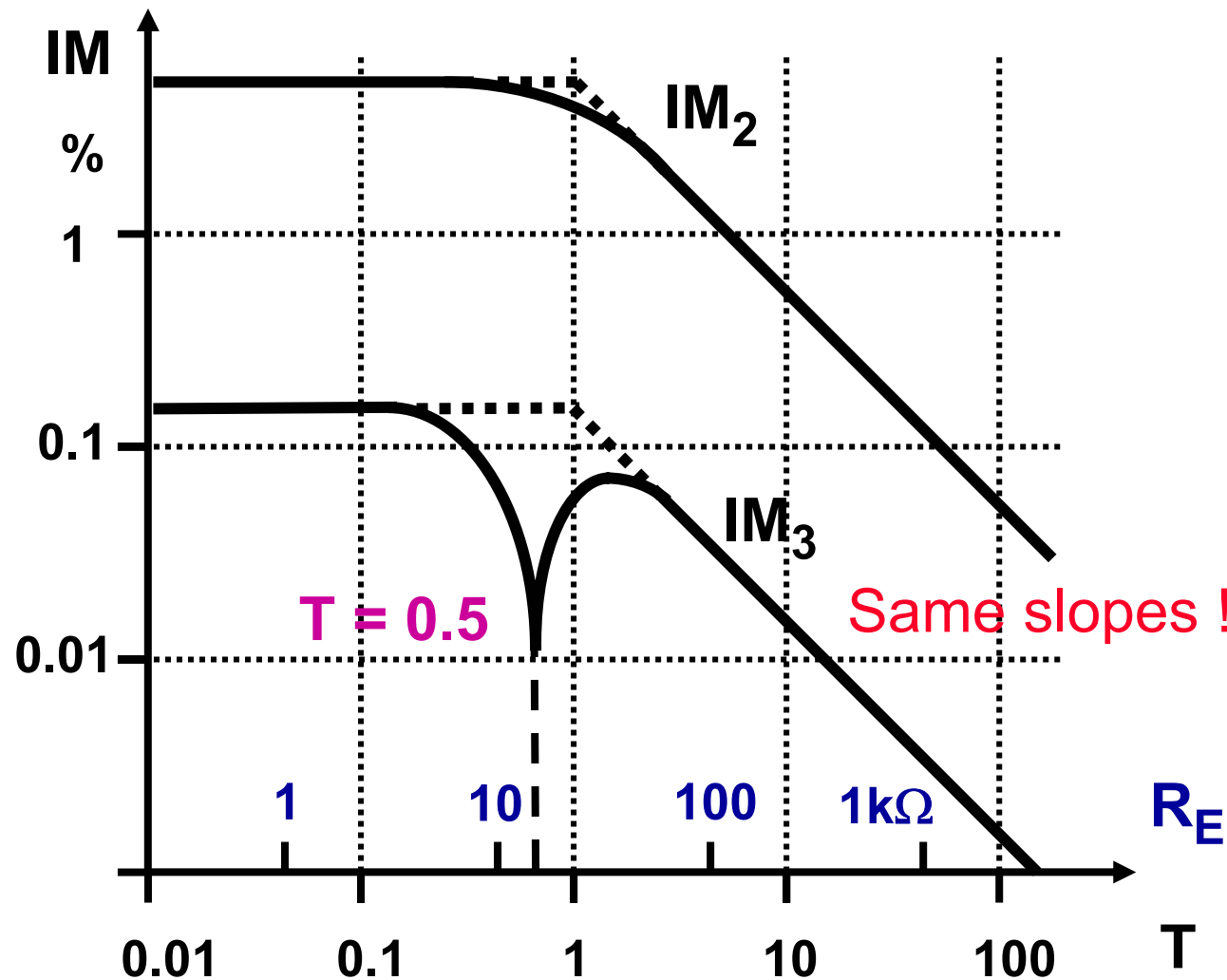Null in IM_3 by R_E (Bipolar trans. $I_{CE} = 1 \text{ mA}$)



Null in IM_3 if

$$a_3 (1 + T) = 2f a_2^2$$

$$a_3 (1 + T) = 2T \frac{a_2^2}{a_1}$$

$$T = \frac{1}{\frac{2a_2^2}{a_1 a_3} - 1}$$

Emitter resistor R_E reduces distortion for large T

$$U = \frac{1}{T} \frac{V_{in}}{kT_e/q} = \frac{V_{in}}{R_E I_{CE}}$$

$$IM_{2fT} = \frac{U}{2T} = \frac{V_{in}}{kT_e/q} \frac{1}{2T^2} = \frac{V_{in} kT_e/q}{2 (R_E I_{CE})^2}$$

$$IM_{3fT} = \frac{U^2}{4T} = \left(\frac{V_{in}}{kT_e/q} \right)^2 \frac{1}{4T^3} = \frac{V_{in}^2 kT_e/q}{4 (R_E I_{CE})^3}$$

Source resistor R_S to reduce distortion


$$T = g_m R_S = \frac{V_{RS}}{(V_{GS} - V_T)/2} \qquad \frac{a_2}{a_1} = \frac{1}{4} \quad a_3 = 0$$

$$U = \frac{1}{(1 + T)} \frac{V_{in}}{(V_{GS} - V_T)/2} \quad \text{is the relative current swing}$$

$$IM_{2f} = \frac{1}{(1 + T)} \frac{U}{4} \approx \frac{V_{in}}{(V_{GS} - V_T)/2} \frac{1}{4 T^2} = \frac{V_{in} (V_{GS} - V_T)/2}{4 (R_S I_{DS})^2}$$

$$IM_{3f} = \frac{T}{(1 + T)^2} \frac{3U^2}{32} \approx \frac{V_{in}^2}{(V_{GS} - V_T)^2/4} \frac{3}{32 T^3} = \frac{3V_{in}^2 (V_{GS} - V_T)/2}{32 (R_S I_{DS})^3}$$

Current source with series R

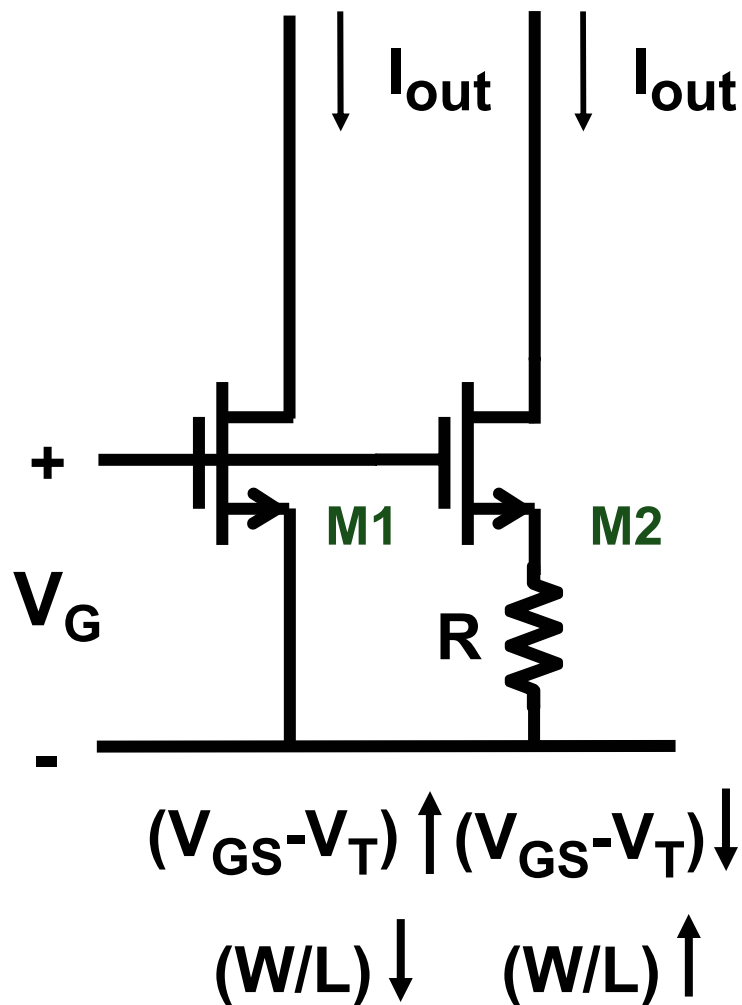

Same I_{out} & same V_G :


Same gain !

Same output noise !


Same distortion ?

$$\frac{IM_{2f}}{IM_2} = \frac{1 - \frac{V_R}{V_{GST1}}}{\left(1 + \frac{V_R}{V_{GST1}}\right)^2}$$

Source & Emitter Follower

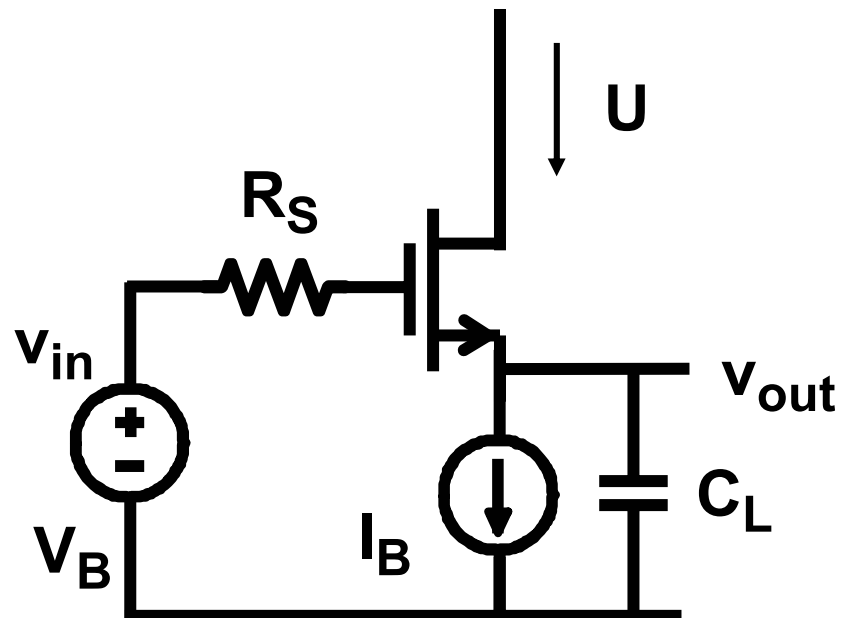

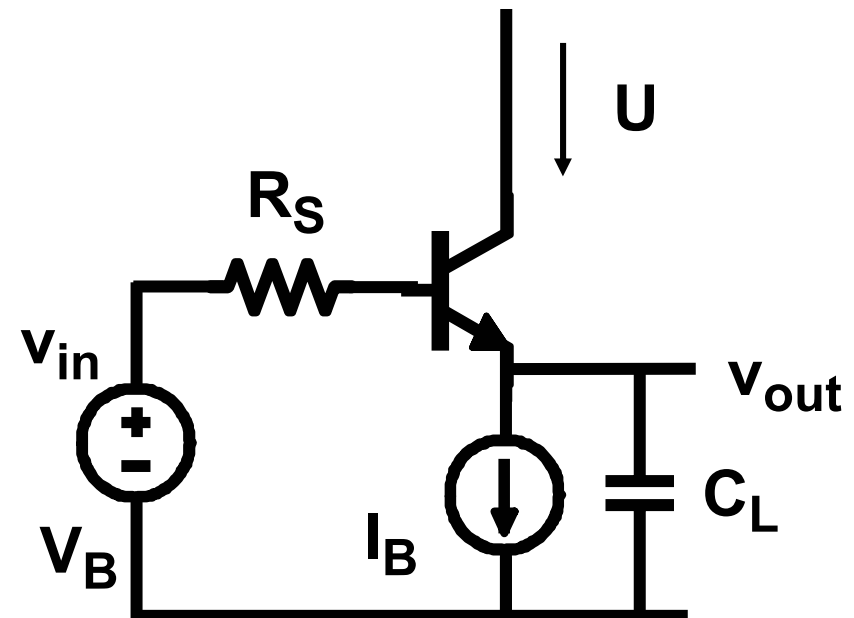
$$U = \frac{1}{g_m r_{DS}} \frac{V_{in}}{(V_{GS} - V_T)/2} = \frac{V_{in}}{V_{En} L}$$



$$U = \frac{1}{g_m r_o} \frac{V_{in}}{kT_e/q} = \frac{V_{in}}{V_E}$$

If $v_{BS} = 0$!!

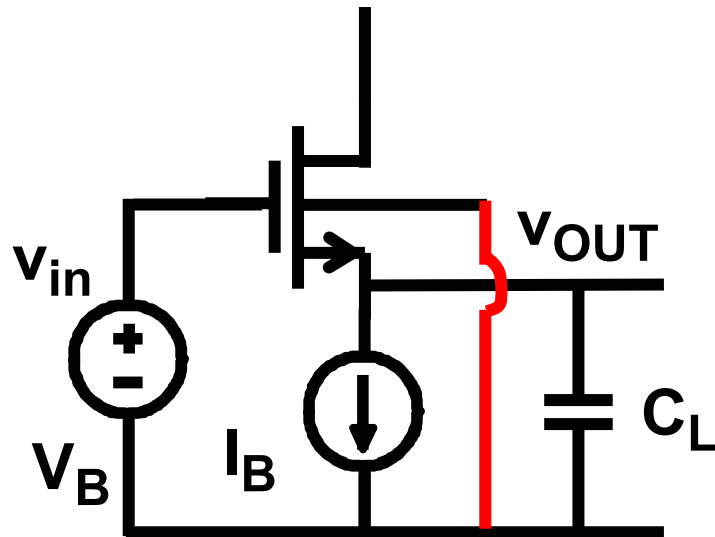Distortion Source follower with substrate effect



$$v_{OUT} = v_{IN} - v_{GS}$$

$$v_{GS} = V_T + \sqrt{\frac{I_B}{K'W/L}}$$

$$V_T = V_{T0} + \gamma [v_{OUTF}]$$

$$v_{OUTF} = \sqrt{|2\Phi_F| + v_{OUT}} - \sqrt{|2\Phi_F|}$$

$$v_{IN} = v_{OUT} + V_{T0} + \gamma [v_{OUTF}] + \sqrt{\frac{I_B}{K'W/L}}$$


Distortion Source follower - Example

$$v_{IN} = u^2 + \gamma u + B$$

$$u^2 = v_{OUT} + |2\Phi_F|$$

$$B = V_{GS0} - |2\Phi_F| - \gamma \sqrt{|2\Phi_F|}$$
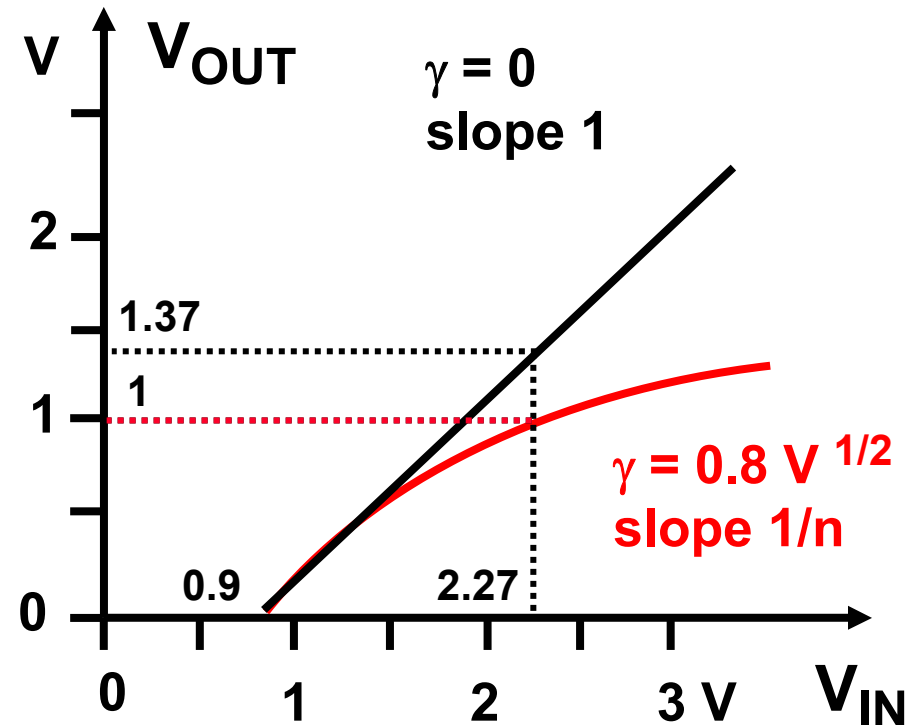
$$V_{GS0} = V_{T0} + \sqrt{\frac{I_B}{K'W/L}}$$





$$V_{T0} = 0.6 \text{ V} ; V_{GS0} = 0.9 \text{ V} ; 2\Phi_F = 0.7 \text{ V} ; B = -0.47 \text{ V} ; 1/n = 0.73$$

$$a_1 = 0.765 ; a_2 = 0.02 ; a_3 = -0.0035$$

$$V_{INp} = 1 \text{ V}_p ; HD_2 = 1.32 \% ; HD_3 = -0.114 \%$$


Increasing the IP_3 by feedback

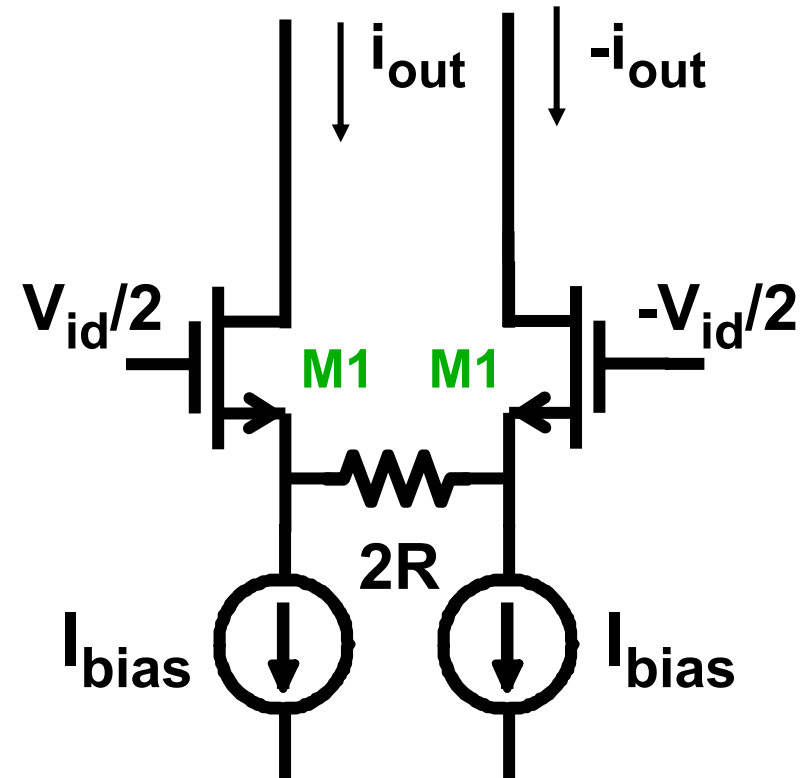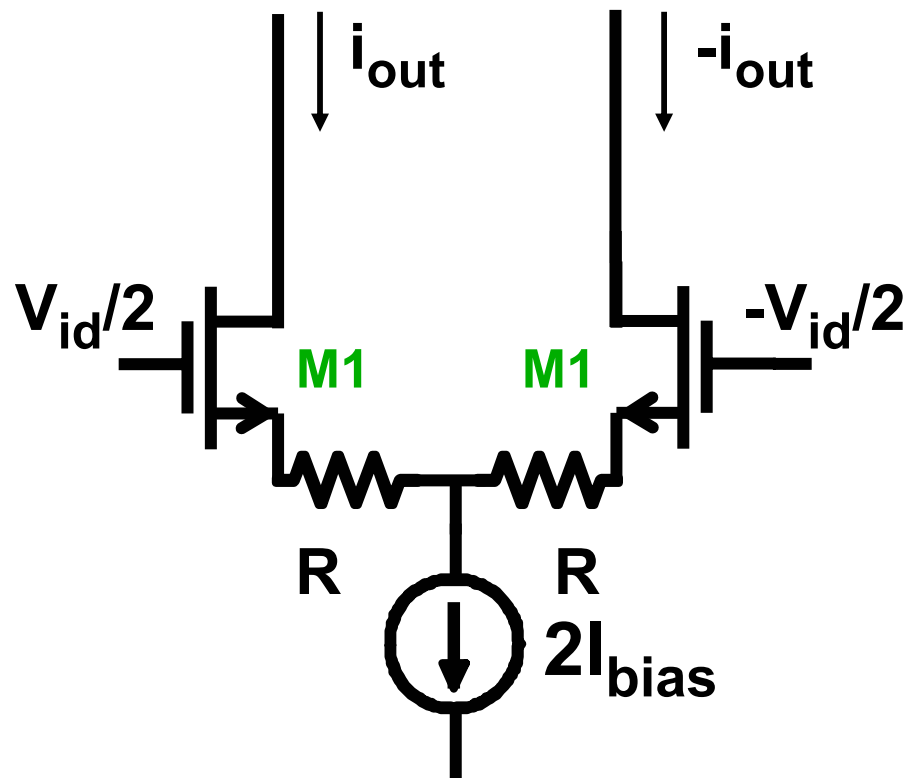


$$IP_3 \approx 3.3 (V_{GS} - V_T)(1 + g_{m1}R)^2 \quad HD_3/n^2 \quad n = 1 + g_{m1}R$$

$HD_3 = -60$ dB for $V_{id} = 1$ V requires $V_{GS} - V_T = 0.38$ V and $g_{m1}R = 3$!!!

Increasing the IP_3 by feedback

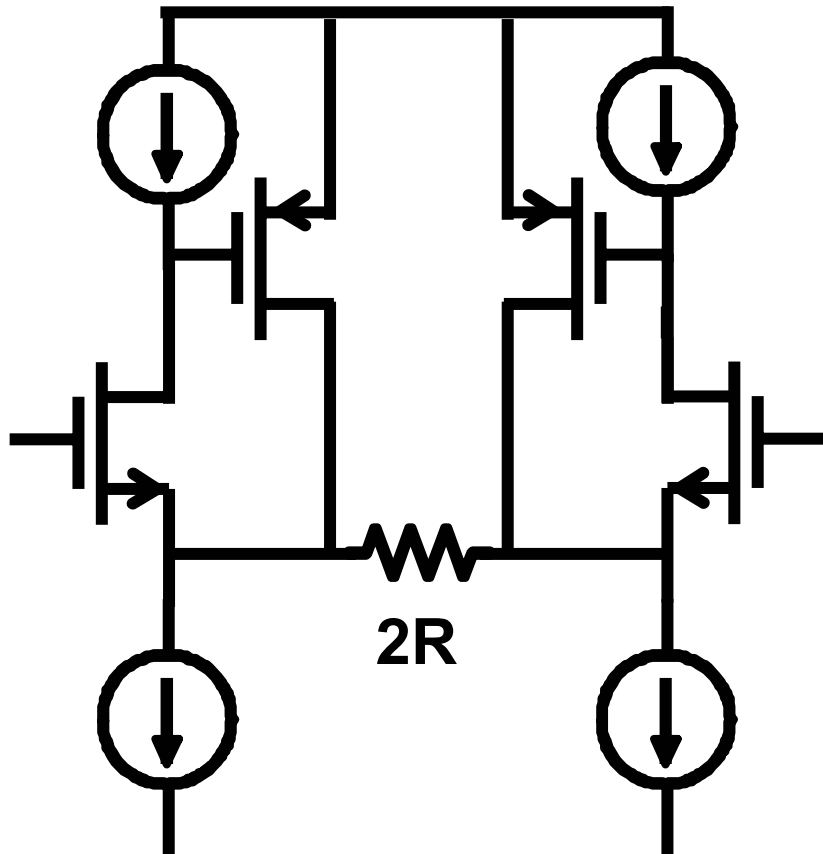


Additional local FB

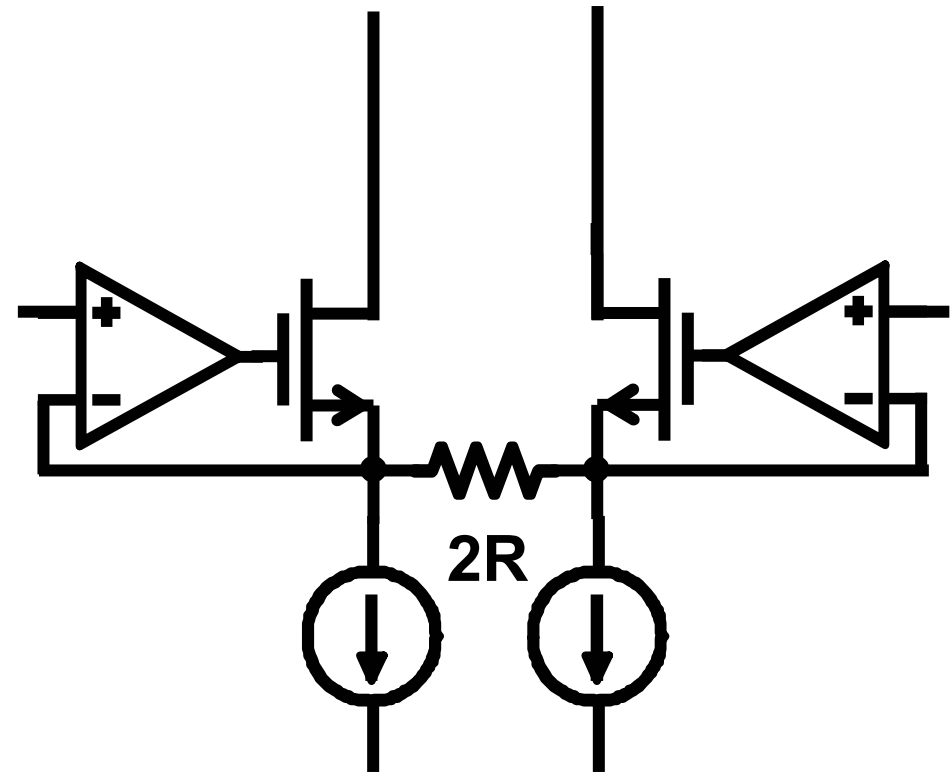

More FB with opamps

Distortion cancellation

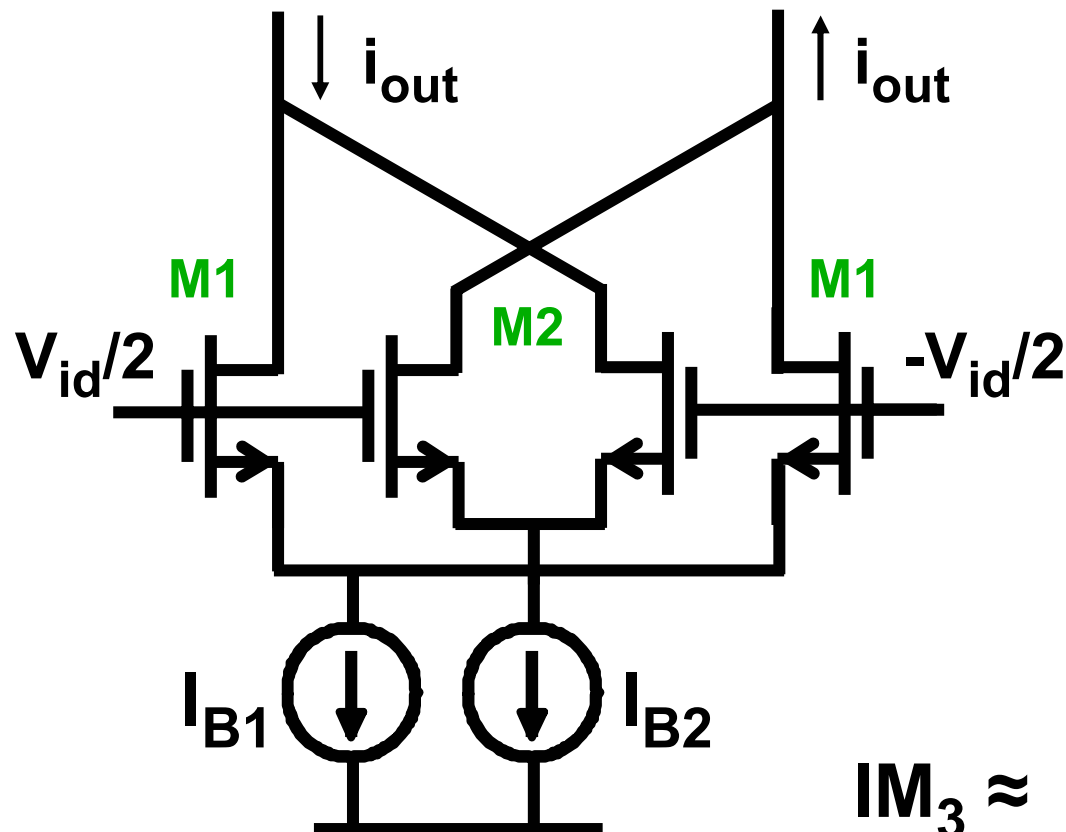

Parameters :

$$\alpha = I_{B2} / I_{B1}$$

$$\approx 0.25$$

$$v = V_{GST1} / V_{GST2}$$

$$\approx 1.6$$

$$V_{GST} = V_{GS} - V_T$$

$$IM_3 \approx 0 \quad \text{if} \quad v = \alpha^{-1/3}$$

$$\text{then } i_{out} = g_{m1} V_{id} (1 - \alpha^{2/3})$$

Distortion cancellation

$$i_{\text{out}} = 2 (i_{\text{DS1}} - i_{\text{DS2}})$$

$$\frac{i_{\text{DS}}}{I_B} = U - \frac{1}{8} U^3 \quad U = \frac{V_{\text{id}}}{V_{\text{GS}} - V_T} \quad \text{IM}_3 = \frac{3}{32} U^2$$

$$\text{IM}_3 \approx \frac{3}{32} \left(\frac{V_{\text{id}}}{V_{\text{GS1}} - V_T} \right)^2 \frac{1 - \alpha v^3}{1 - \alpha v}$$


$$\text{IM}_3 \approx 0 \quad \text{if} \quad v_{00} = \alpha^{-1/3}$$

$$\text{at which point} \quad i_{\text{out}} = g_{m1} V_{\text{id}} (1 - \alpha^{2/3})$$

Compensation of IM3

$$1 - \alpha v^3$$

$$1 - \alpha v$$

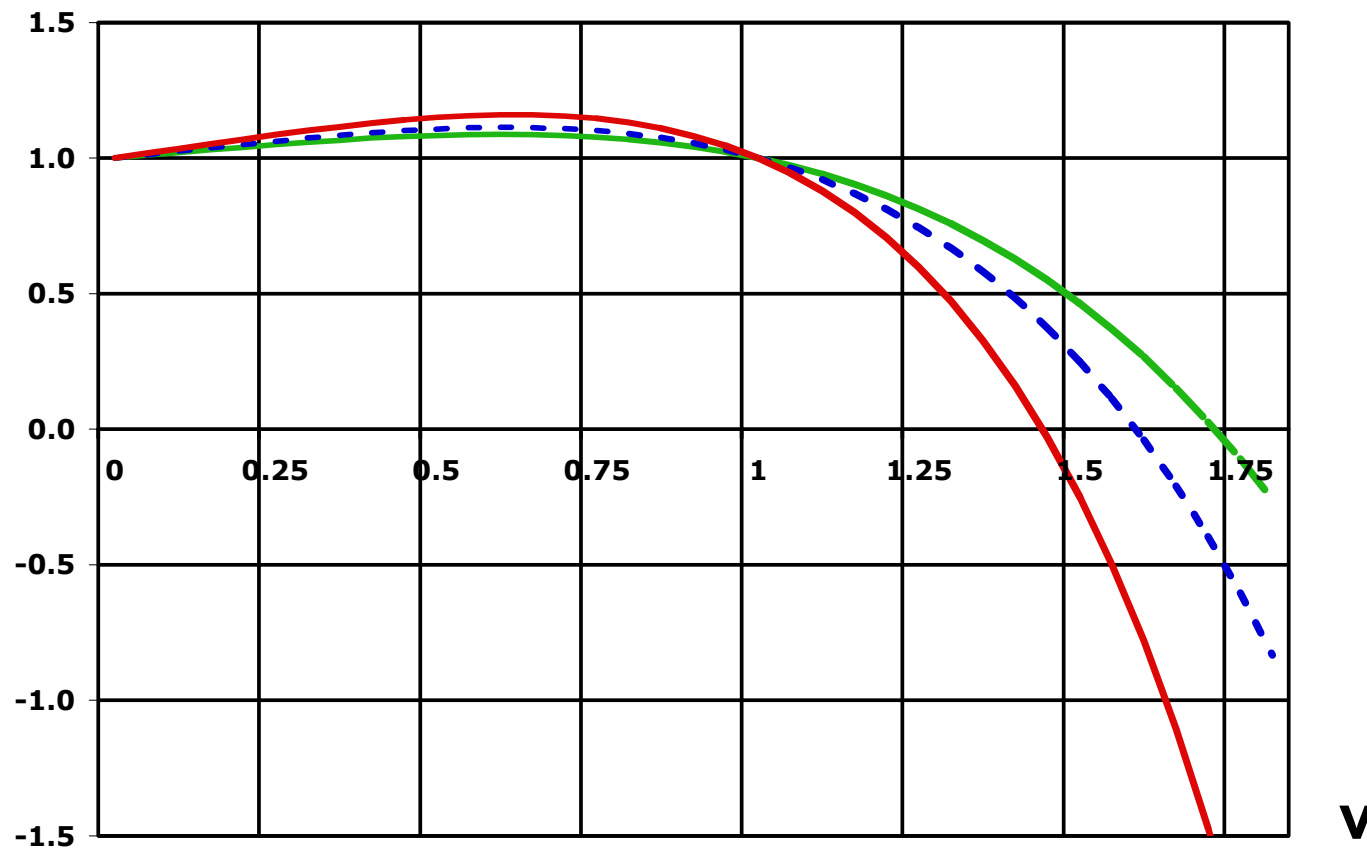

$$\alpha = 0.20$$
$$v_{00} = 1.71$$

$$\alpha = 0.25$$
$$v_{00} = 1.6$$

$$\alpha = 0.33$$
$$v_{00} = 1.44$$

Output signal vs current ratio


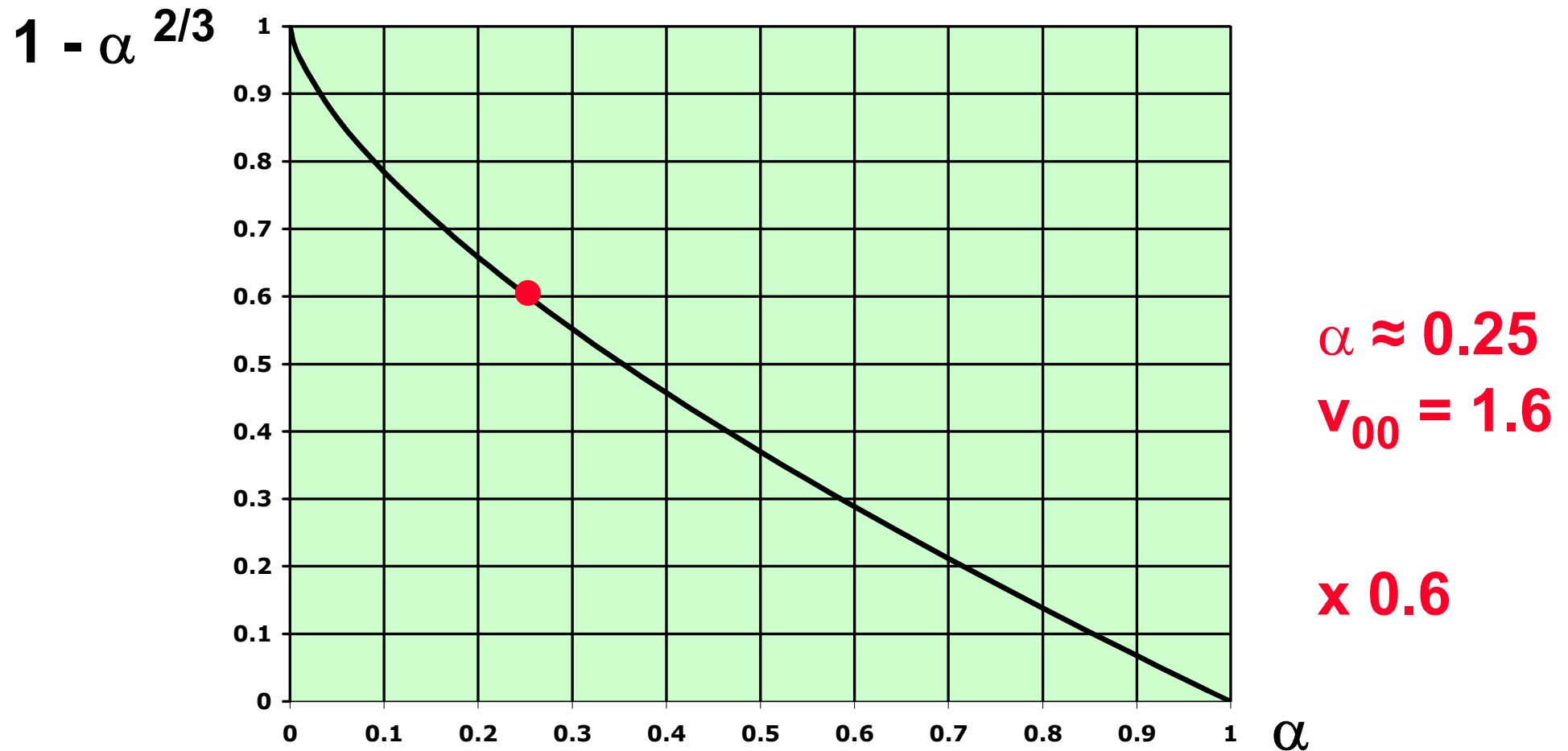
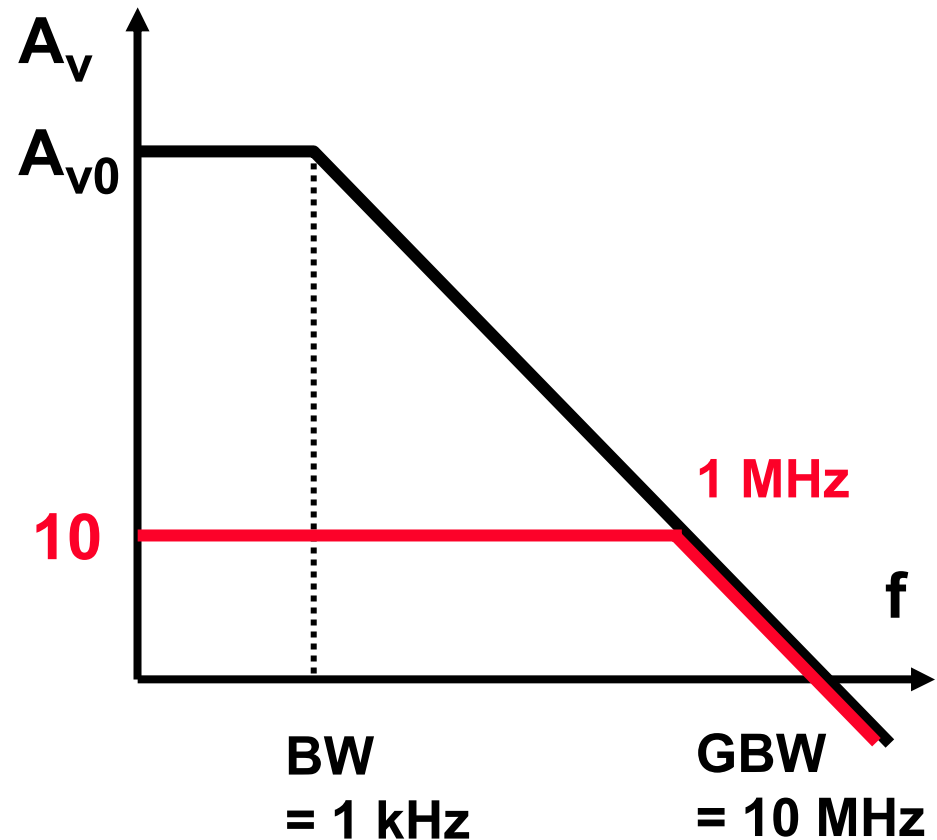


Table of contents



- ☐ **Definitions : HD, IM, intercept point, ..**
- ☐ **Distortion in a MOST**
 - **Single-ended amplifier**
 - **Differential amplifier**
- ☐ **Distortion in a bipolar transistor**
- ☐ **Reduction of distortion by feedback**
- ☐ **Distortion in an opamp**
- ☐ **Other cases of distortion and guide lines**

Miller CMOS opamp with Feedback

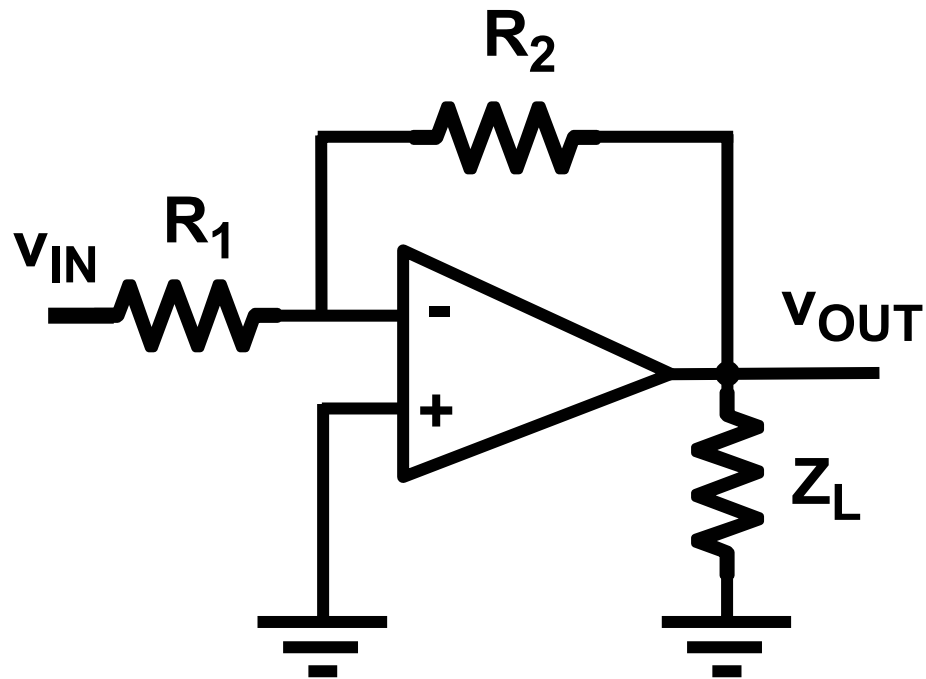

$GBW = 10 \text{ MHz}$ & $A_{vc} = 10$
 $Z_L = 100 \text{ k}\Omega // 5 \text{ pF}$

Distortion in input stage

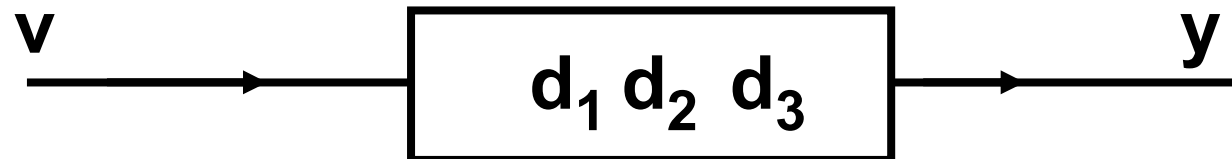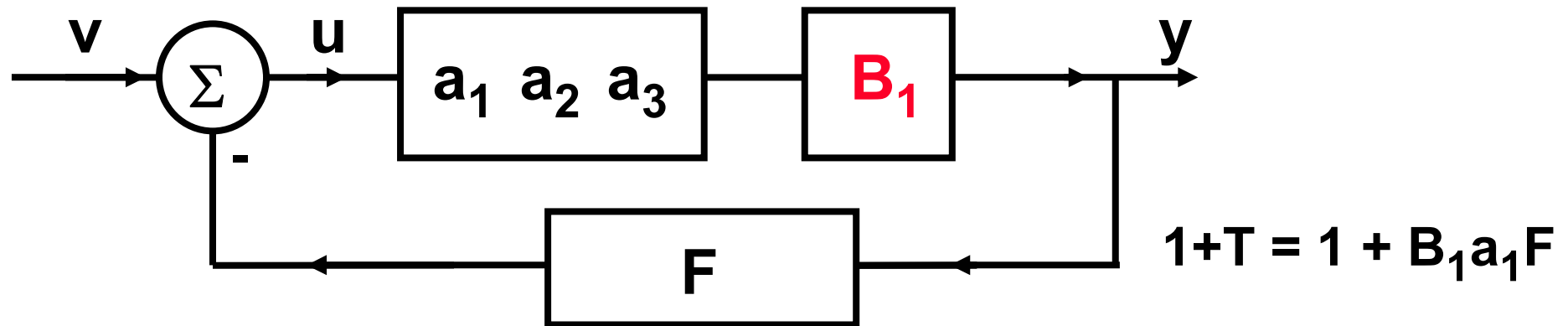

$$u = v - Fy$$

$$y = B_1(a_1 u + a_2 u^2 + a_3 u^3) \quad \left. \vphantom{y = B_1(a_1 u + a_2 u^2 + a_3 u^3)} \right\} \text{elim. } u$$

$$y = d_1 v + d_2 v^2 + d_3 v^3$$

$$\left. \vphantom{y = d_1 v + d_2 v^2 + d_3 v^3} \right\} \text{elim. } y \quad \left\{ \begin{array}{l} \text{coeff } v : d_1 \\ \text{coeff } v^2 : d_2 \\ \text{coeff } v^3 : d_3 \end{array} \right.$$

Distortion in input stage


$$IM_{2f} = \frac{d_2}{d_1} V = \frac{a_2}{a_1} \frac{V}{(1+T)^2} = \frac{a_2}{a_1} \frac{1}{(1+T)} \frac{V}{(1+T)}$$

$$IM_{3f} = \frac{3}{4} \frac{d_3}{d_1} V^2 = \frac{3}{4} \left[\frac{a_3}{a_1} \frac{1}{(1+T)} - \left(\frac{a_2}{a_1} \right)^2 \frac{2T}{(1+T)^2} \right] \frac{V^2}{(1+T)^2}$$

Same as before but with different Loop gain :

$$1+T = 1 + B_1 a_1 F$$

Distortion in input stage with LPF

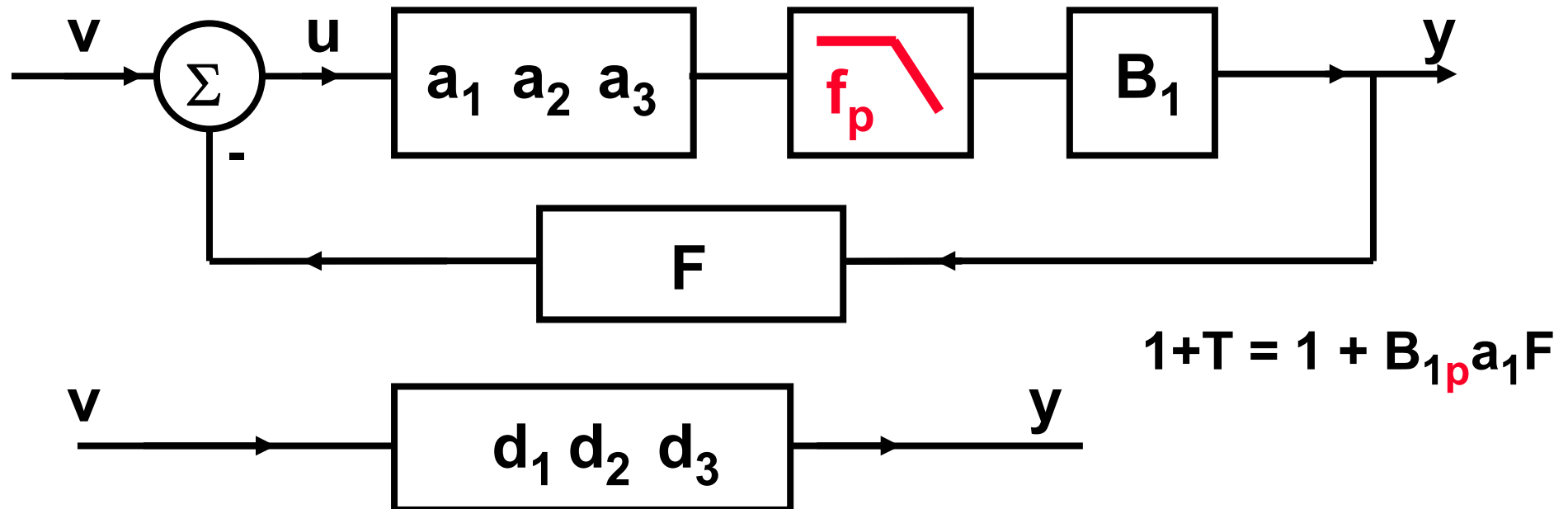

$$1+T = 1 + B_1 p a_1 F$$

$$u = v - Fy$$


$$y = B_1 p (a_1 u + a_2 u^2 + a_3 u^3) \quad \left. \vphantom{y = B_1 p (a_1 u + a_2 u^2 + a_3 u^3)} \right\} \text{elim. } u$$

$$y = d_1 v + d_2 v^2 + d_3 v^3$$

$$\left. \vphantom{y = d_1 v + d_2 v^2 + d_3 v^3} \right\} \text{elim. } y \quad \left\{ \begin{array}{l} \text{coeff } v : d_1 \\ \text{coeff } v^2 : d_2 \\ \text{coeff } v^3 : d_3 \end{array} \right.$$


Distortion in input stage with LPF
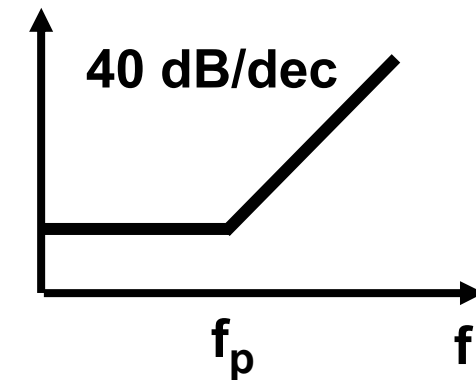
$$IM_{2f} = \frac{a_2}{a_1} \frac{V}{(1+T)^2} = \frac{a_2}{a_1} \frac{1}{(B_{1p} a_1 F)^2} V$$





$$IM_{3f} \Big|_{\text{diff.pair}} = \frac{3}{4} \frac{a_3}{a_1} \frac{1}{(1+T)} \frac{V^2}{(1+T)^2} = \frac{3}{4} \frac{a_3}{a_1} \frac{1}{(B_{1p} a_1 F)^3} V^2$$

$$IM_{3f} \Big|_{\text{Single trans.}} = \frac{3}{4} \frac{a_2^2}{a_1^2} \frac{2}{(B_{1p} a_1 F)^3} V^2$$

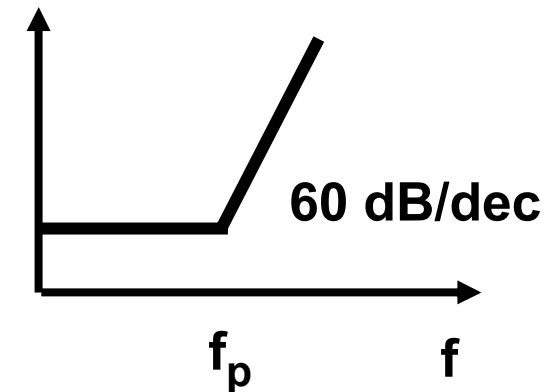

Distortion in output stage

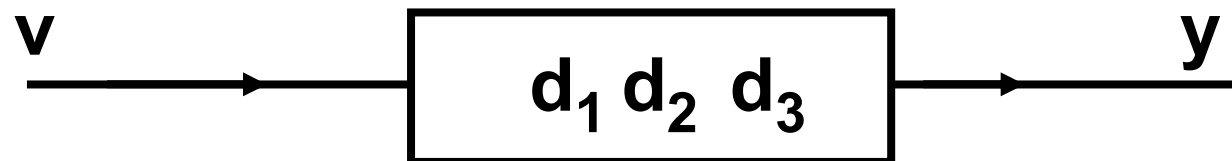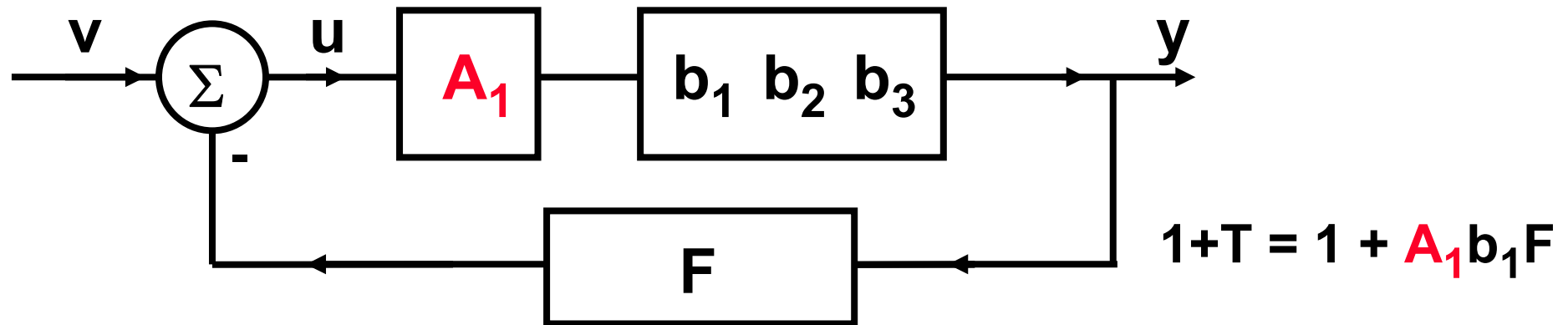


$$u = v - Fy$$

$$y = A_1 b_1 u + A_1^2 b_2 u^2 + A_1^3 b_3 u^3 \quad \left. \vphantom{y = A_1 b_1 u + A_1^2 b_2 u^2 + A_1^3 b_3 u^3} \right\} \text{elim. } u \quad \left. \vphantom{y = A_1 b_1 u + A_1^2 b_2 u^2 + A_1^3 b_3 u^3} \right\} \text{elim. } y \quad \left\{ \begin{array}{l} \text{coeff } v : d_1 \\ \text{coeff } v^2 : d_2 \\ \text{coeff } v^3 : d_3 \end{array} \right.$$

$$y = d_1 v + d_2 v^2 + d_3 v^3$$

Distortion in output stage

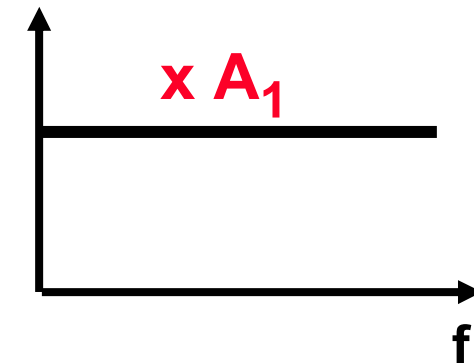
$$IM_{2f} = \frac{b_2}{b_1} \frac{V}{(1+T)^2} = \frac{b_2}{b_1} \frac{A_1}{(A_1 b_1 F)^2} V$$





$$IM_{3f} = \frac{3}{4} \left(\frac{b_2}{b_1} \right)^2 \frac{2T}{(1+T)^2} \frac{V^2}{(1+T)^2}$$

Single trans.


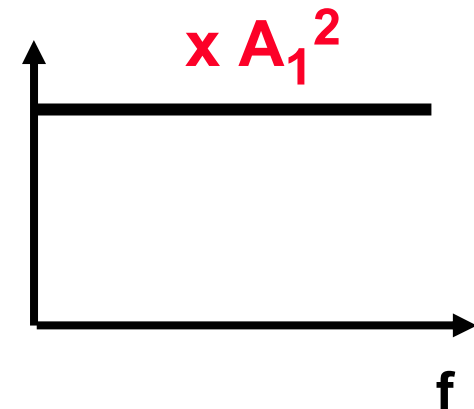
$$= \frac{3}{4} \frac{b_2^2}{b_1^2} \frac{2 A_1^2}{(A_1 b_1 F)^3} V^2$$




Two-stage opamp a & b

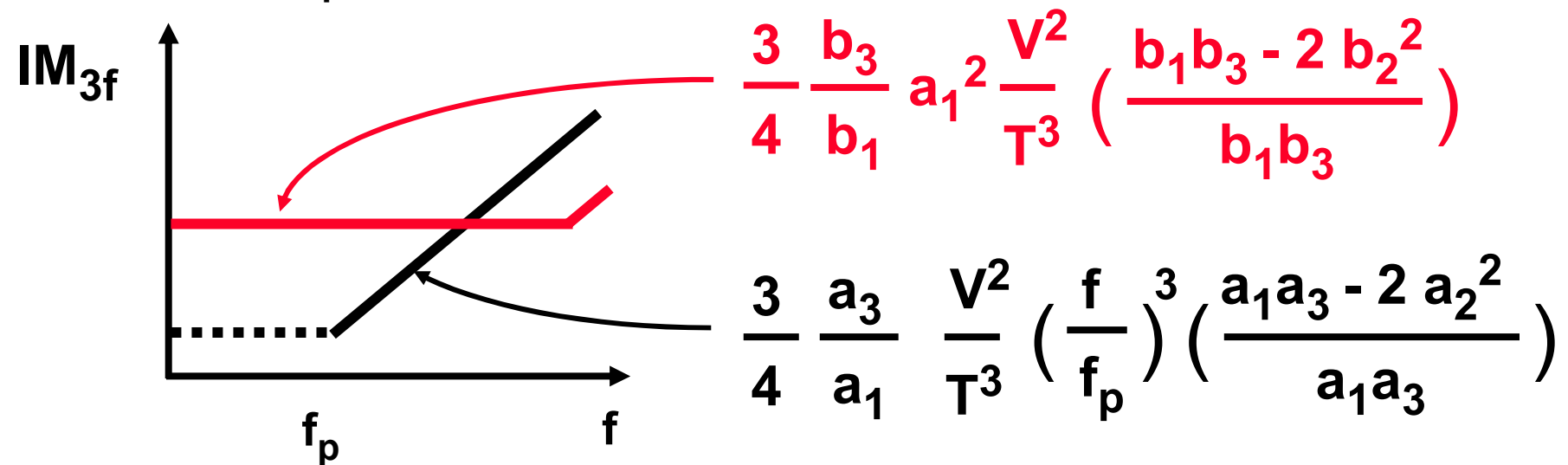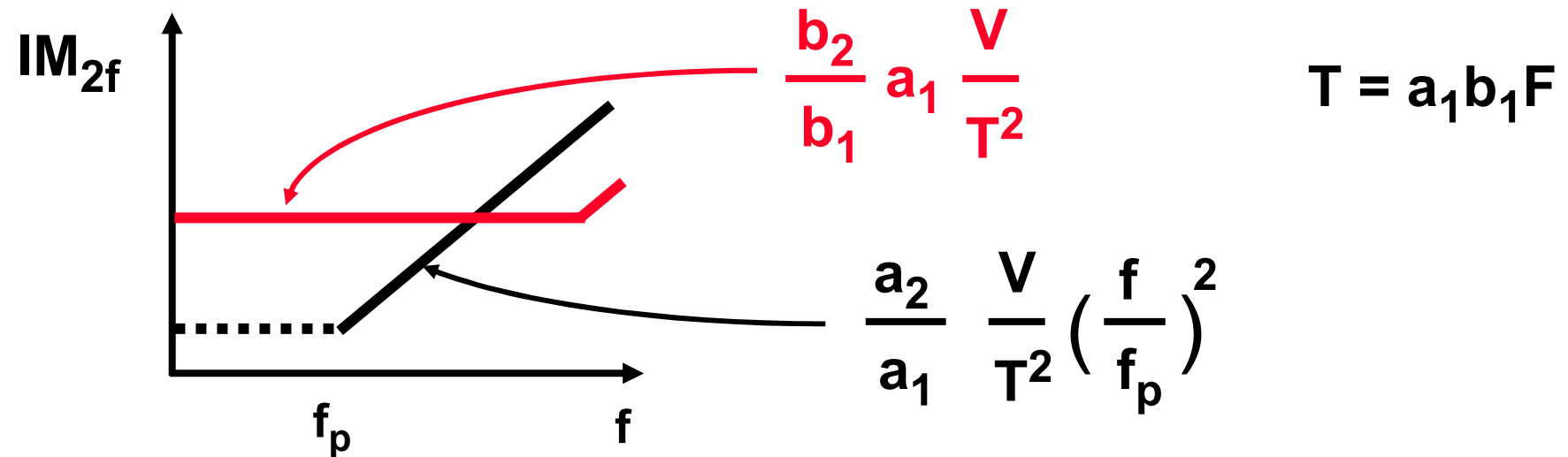

Three-stage opamp a & b & c

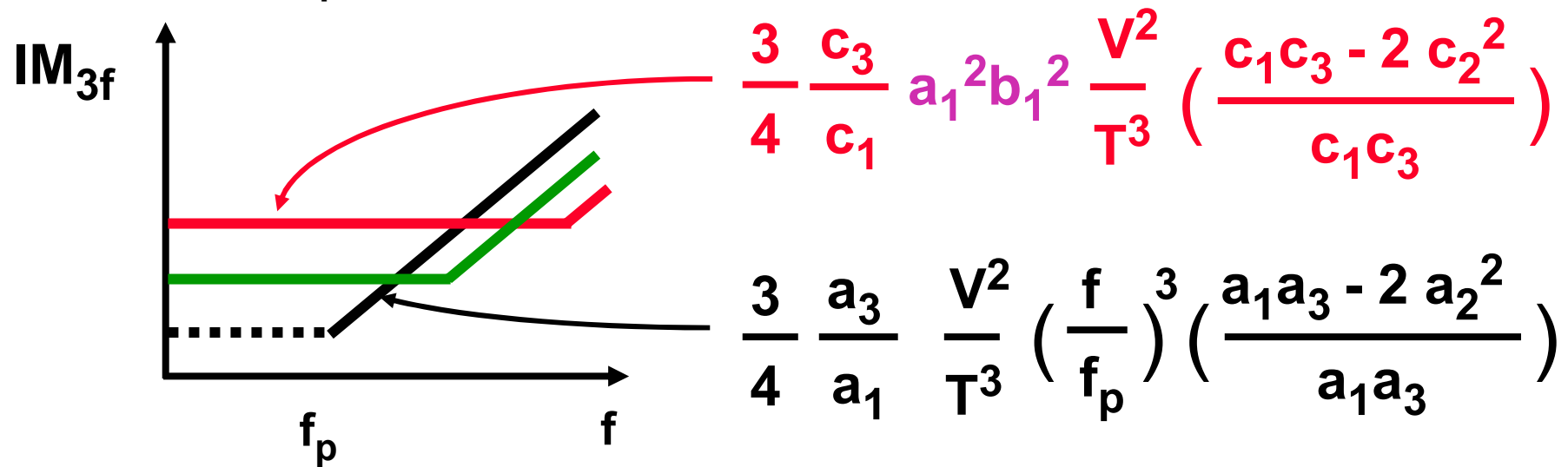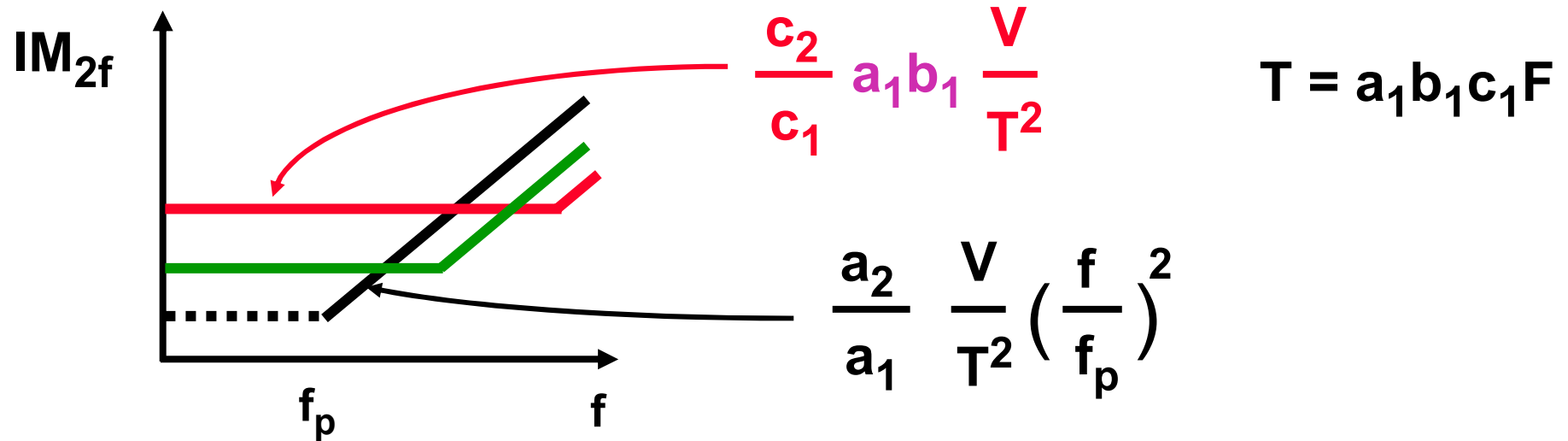

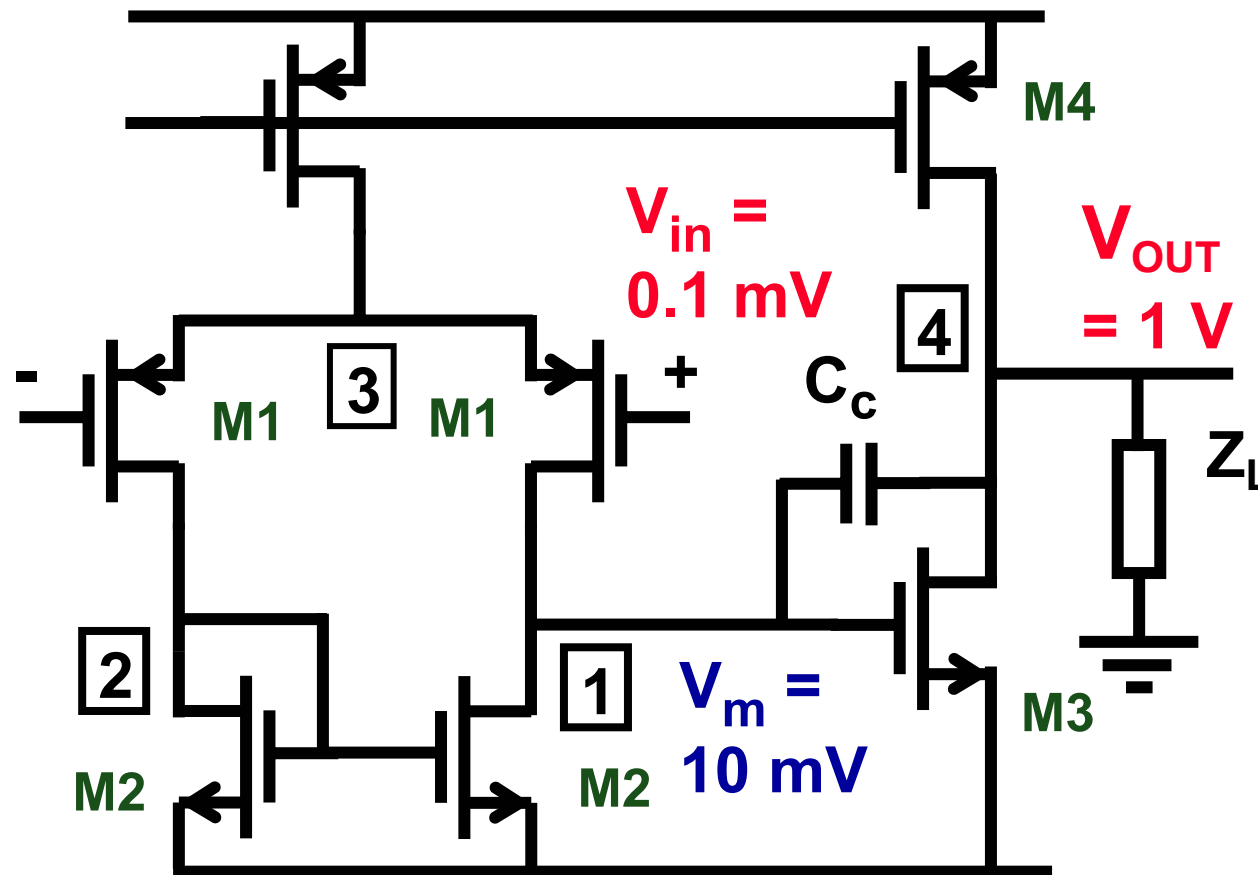Distortion in an opamp at low frequencies



$$\text{GBW} = 10 \text{ MHz}$$

$$A_{v0} = 10.000$$

$$\text{BW} = 1 \text{ kHz}$$

$$A_{vc} = 10$$

$$I_{DS1} = 6 \mu\text{A}$$

$$g_{m1} = 60 \mu\text{S}$$

$$I_{DS3} = 120 \mu\text{A}$$


$$g_{m3} = 1.2 \text{ mS}$$

$$R_L = 100 \text{ k}\Omega$$


$$C_L = 5 \text{ pF}$$

$$C_c = 1 \text{ pF}$$

Low-distortion amplifier

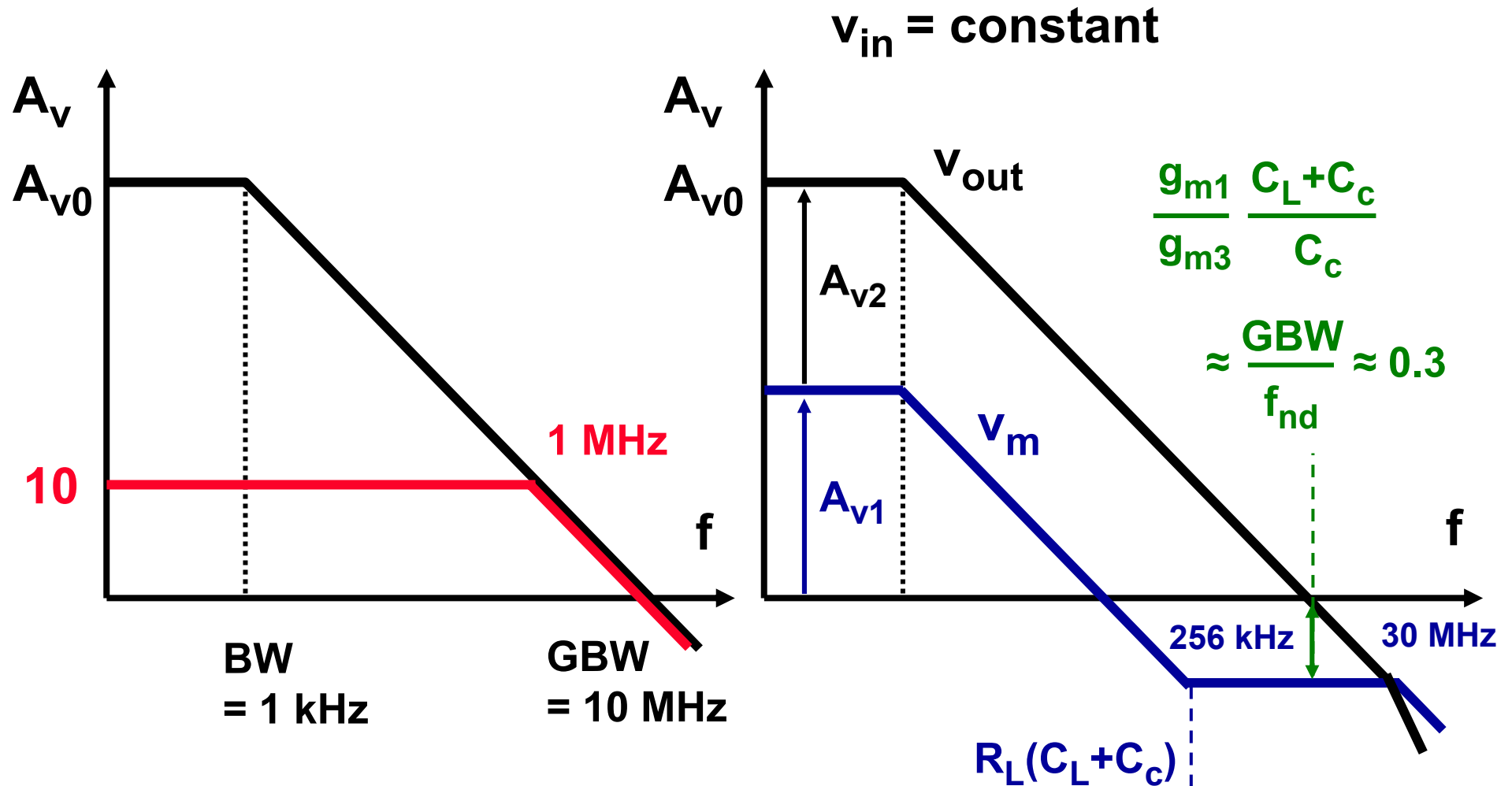

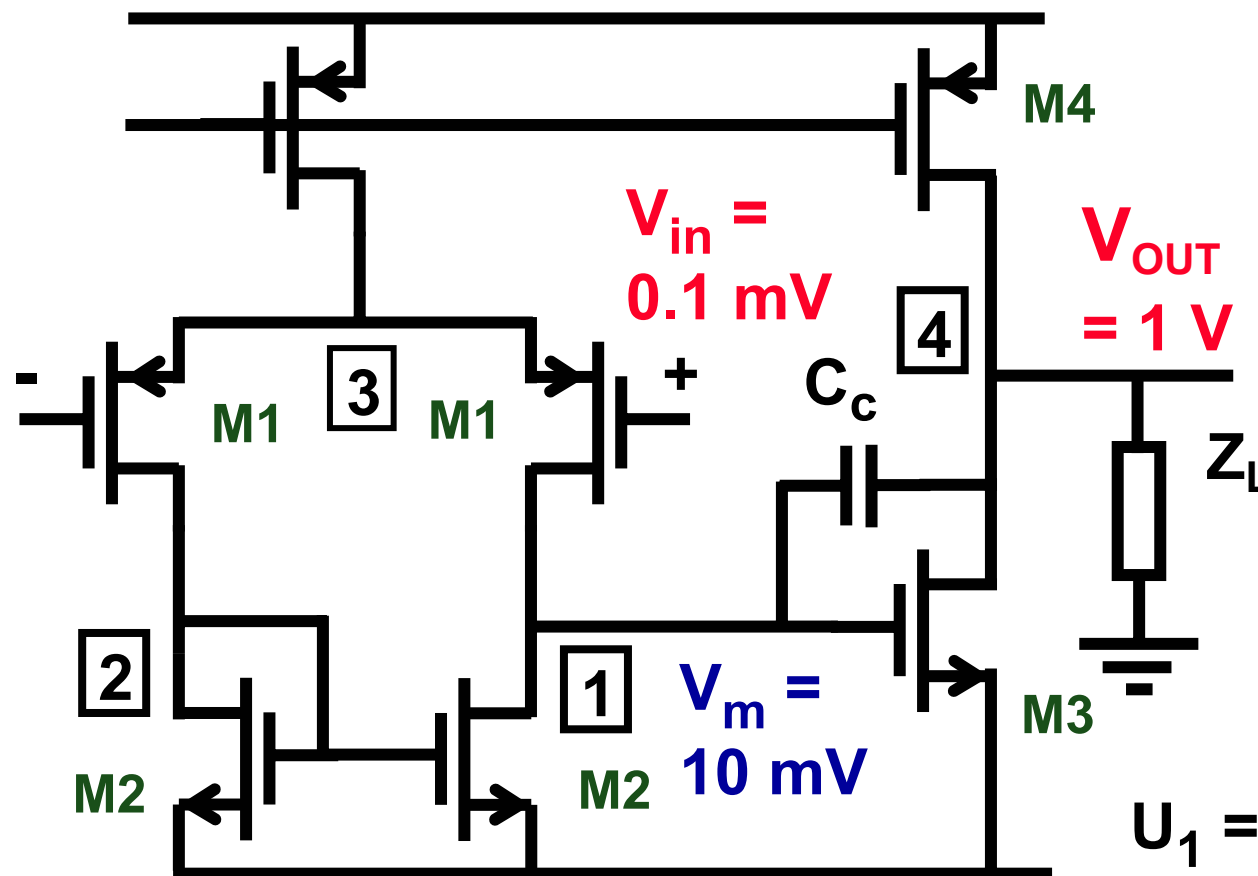Distortion in an opamp at low frequencies



$$GBW = 10 \text{ MHz}$$

$$A_{vc} = 10$$

$$I_{DS1} = 6 \mu\text{A}$$

$$I_{DS3} = 120 \mu\text{A}$$

V_{node} at 100 Hz ?

$$U_1 = g_{m1} V_{in} / I_{DS1} = 5 \cdot 10^{-4}$$

$$U_3 = g_{m3} V_m / I_{DS3} = 0.1$$

Distortion in an opamp at low frequencies

Distortion generation by nonlinear output stage :


$$U_3 = g_{m3} V_m / I_{DS3} = 0.1$$

$$IM_2 = U_3 / 4 = 0.25 \cdot 0.1 = 2.5 \%$$

Distortion reduction by feedback :

$$T = 1000 \quad IM_{2f} = 2.5 \% / 1000 = 0.0025 \% \text{ Negligible !}$$

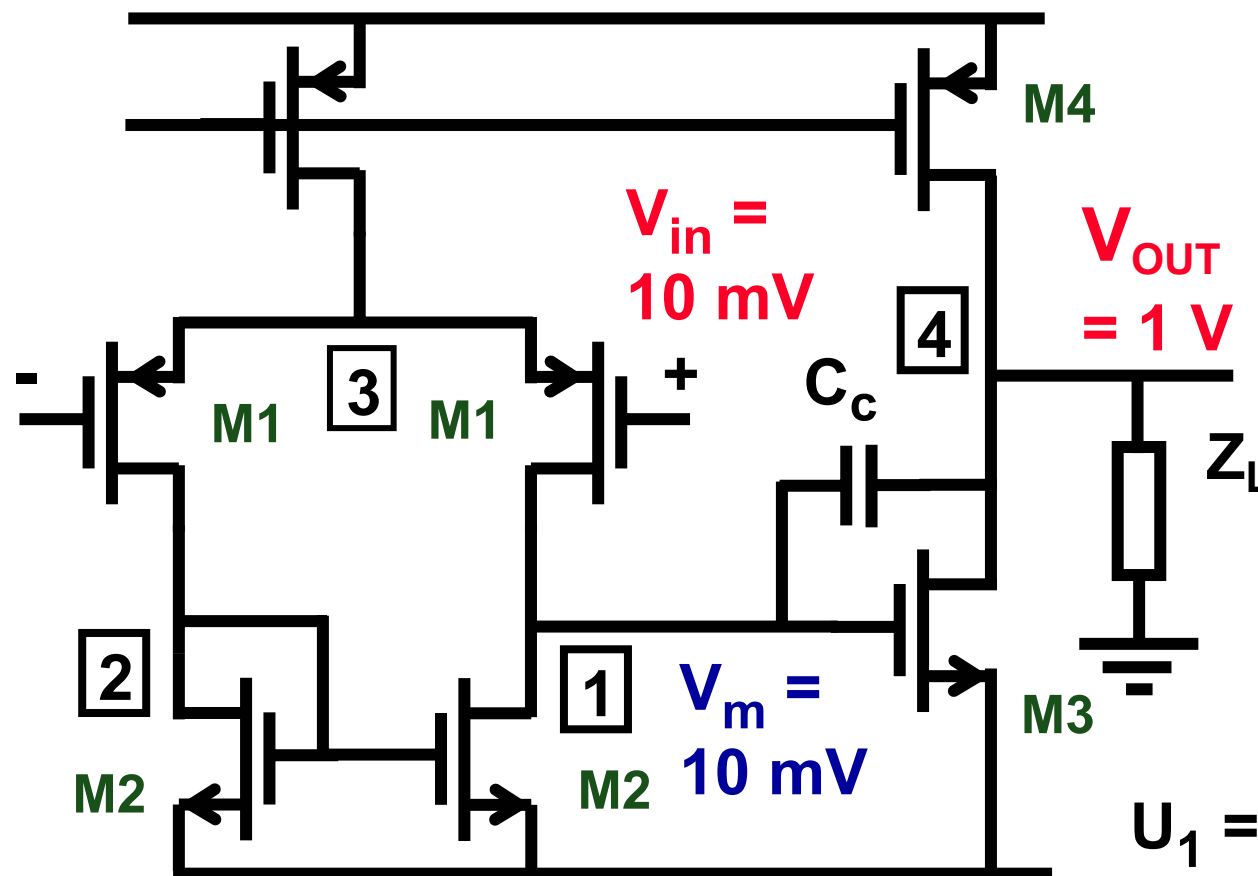Distortion in an opamp at high frequencies



$$GBW = 10 \text{ MHz}$$

$$A_{vc} = 10$$

$$I_{DS1} = 6 \mu\text{A}$$

$$I_{DS3} = 120 \mu\text{A}$$

V_{node} at 100 kHz ?

$$U_1 = g_{m1} V_{in} / I_{DS1} = 5 \cdot 10^{-2}$$

$$U_3 = g_{m3} V_m / I_{DS3} = 0.1$$

Distortion in an opamp at high frequencies

Distortion generation by nonlinear output stage :

$$U_3 = g_{m3}V_m/I_{DS3} = 0.1$$

$$IM_2 = U_3/4 = 0.25 \cdot 0.1 = 2.5 \%$$

Distortion generation by nonlinear input stage :

$$U_1 = g_{m1}V_m/I_{DS1} = 0.05$$


$$IM_3 = U_1^2/10 = 0.0025/10 = 0.025 \% \text{ Negligible !}$$

Distortion reduction by feedback :


$$T = 10 \quad IM_{2f} = 2.5 \% / 100 = 0.25 \%$$

Miller CMOS OTA Measured Distortion

HD₂ (dB)

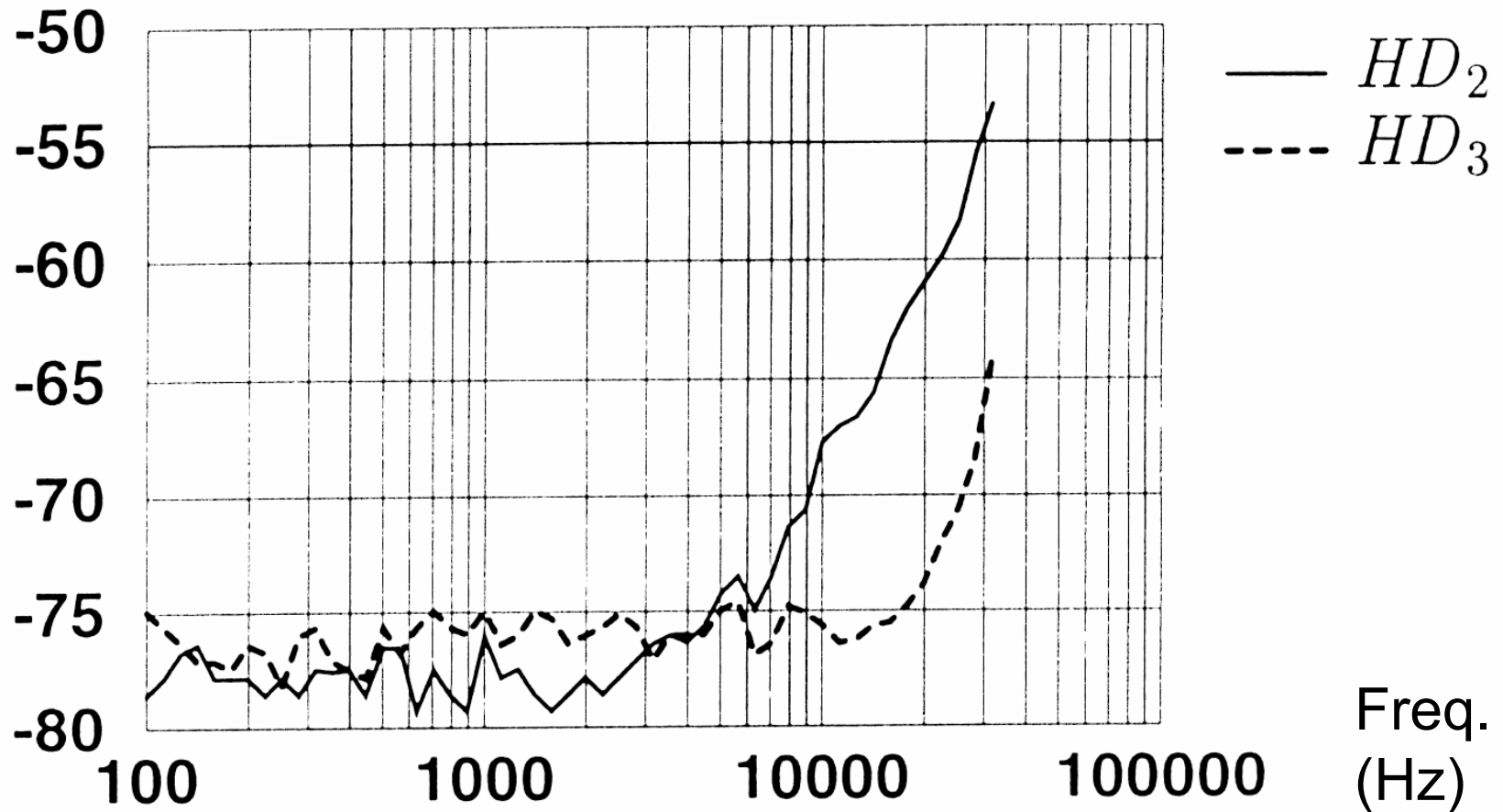

1.8 V Low distortion CMOS Opamp

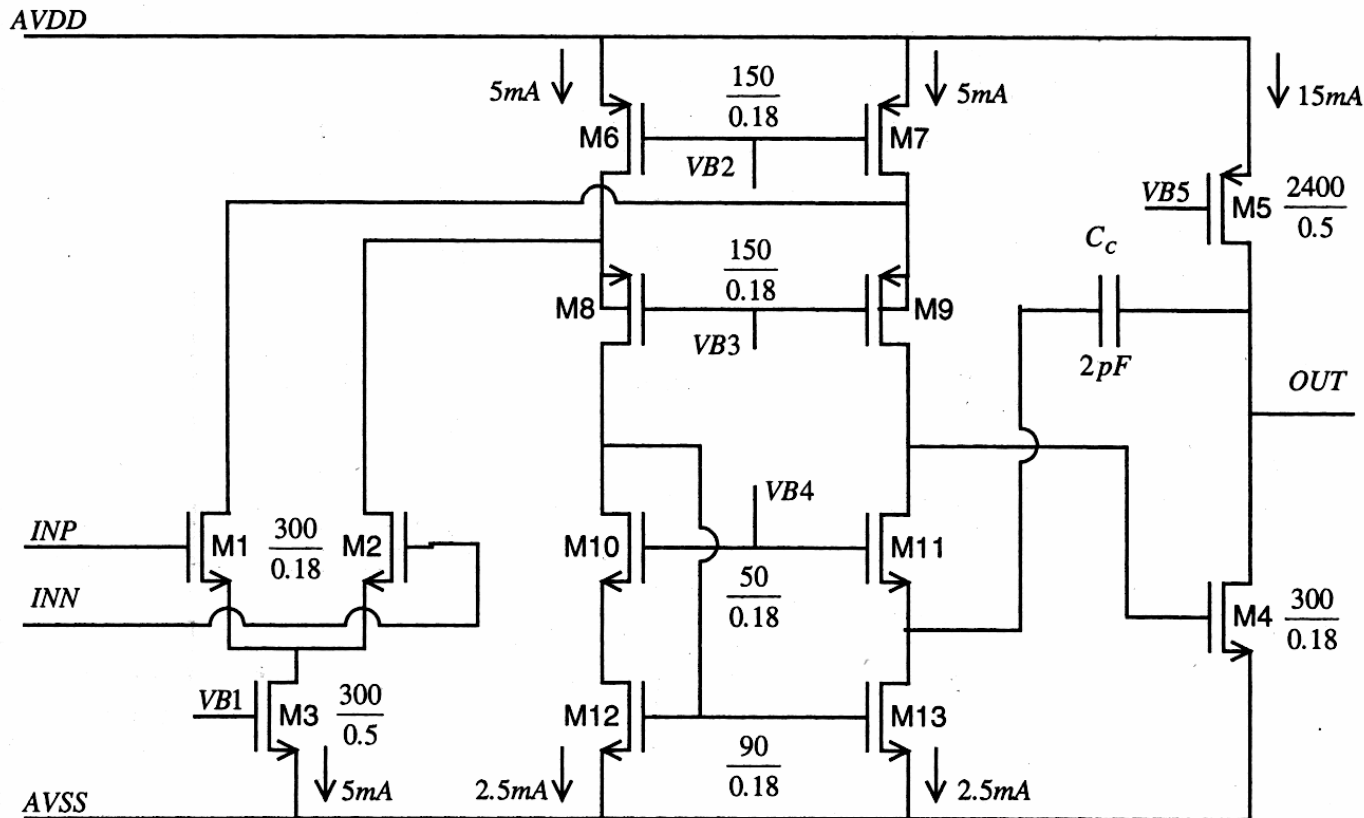

$$GBW \approx 3 \text{ GHz}$$

$$C_L = 8 \text{ pF}$$

$$SR \approx 900 \text{ V}/\mu\text{s}$$

$$f_p = \frac{SR}{2\pi V_{peak}}$$


$$f_p = 380 \text{ MHz}$$

at 0.38 V_{peak}

Large $V_{GS4} - V_T$

Ref. Hernes Kluwer 2003

HD2 & HD3 vs Amplitude

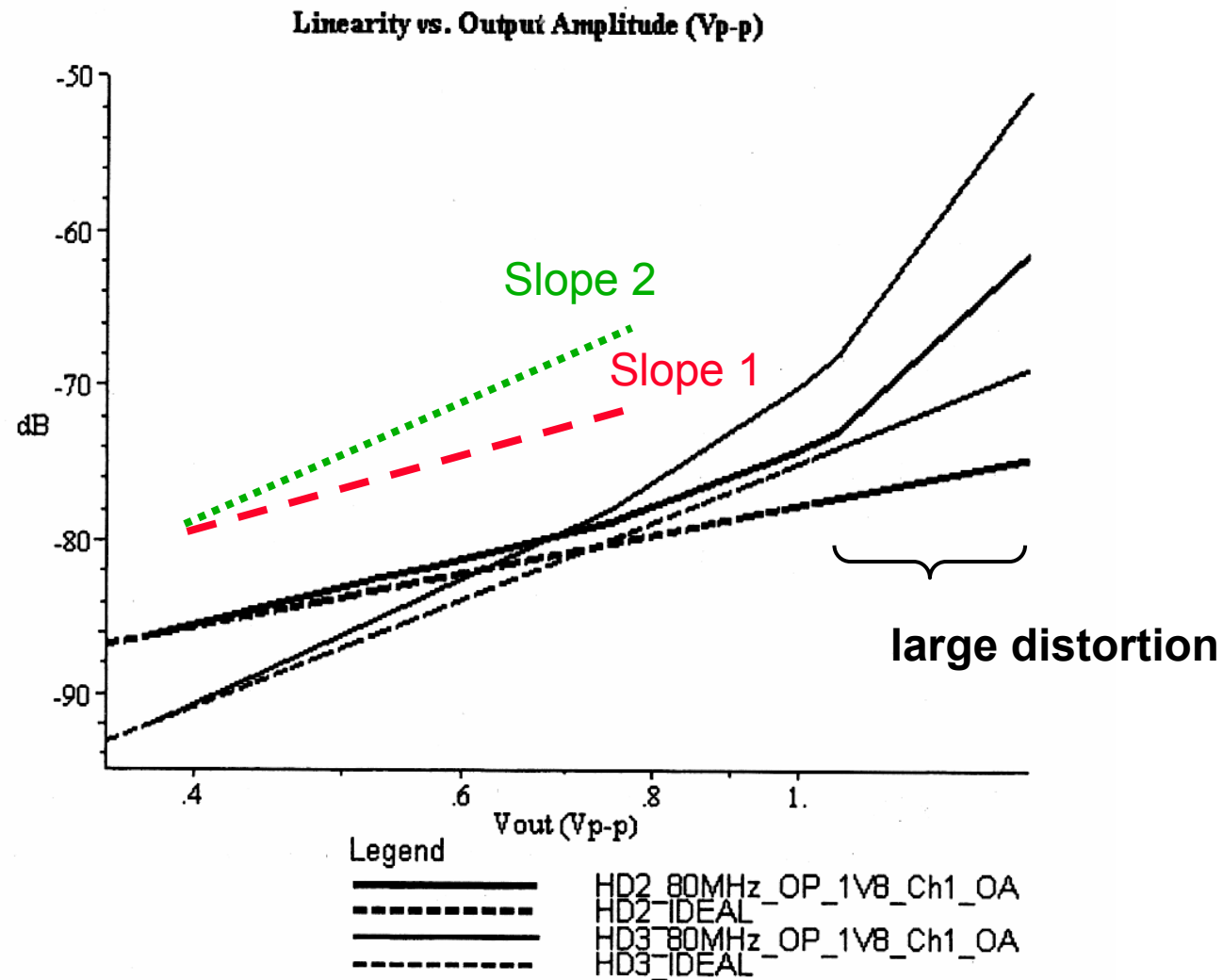

HD2 & HD3 vs Frequency

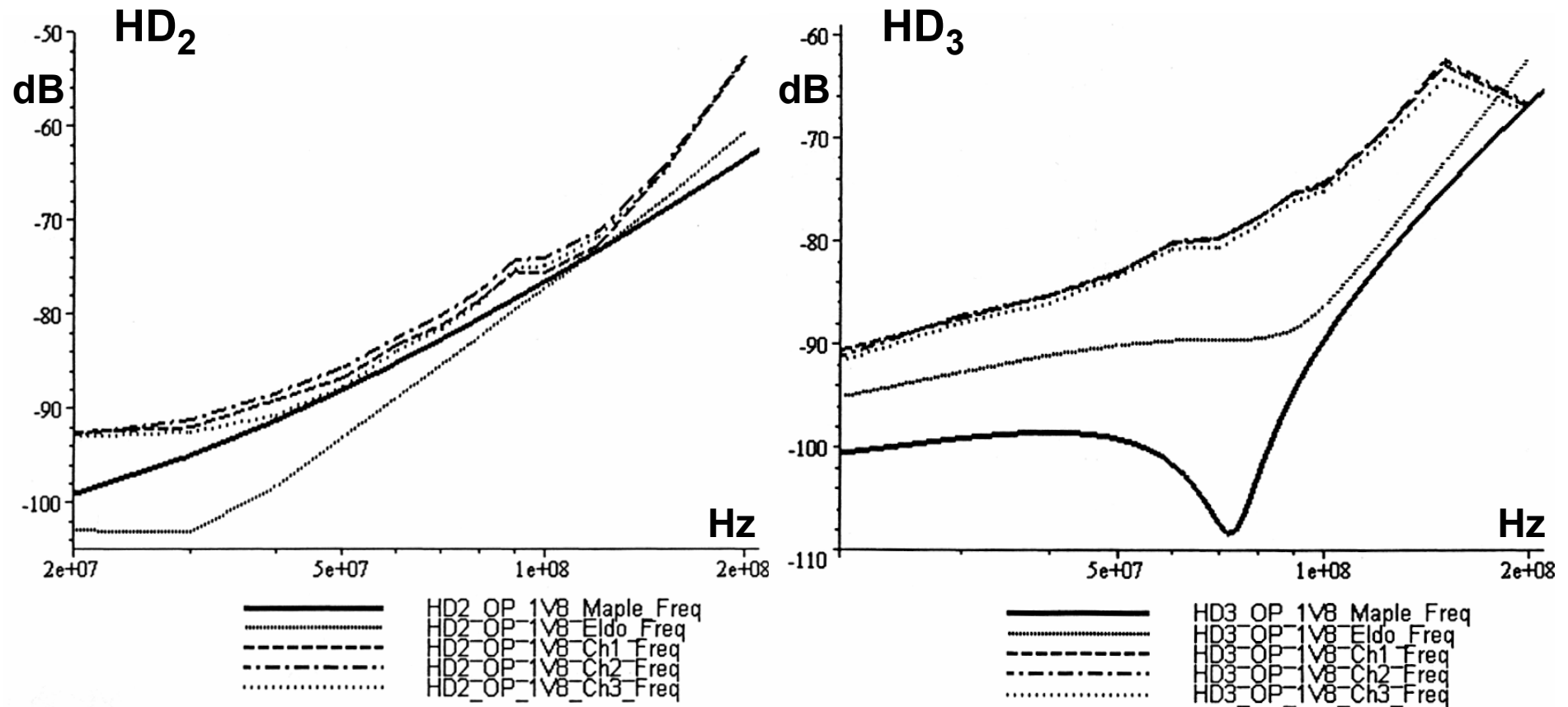


Table of contents

- ❑ **Definitions : HD, IM, intercept point, ..**
- ❑ **Distortion in a MOST**
 - **Single-ended amplifier**
 - **Differential amplifier**
- ❑ **Distortion in a bipolar transistor**
- ❑ **Reduction of distortion by feedback**
- ❑ **Distortion in an opamp**
- ❑ **Other cases of distortion and guide lines**

Other cases of distortion and guide lines

- **Distortion caused by limited SR**
- **Distortion of a switch**
- **Distortion at high frequencies :**
 - Volterra series instead of power series**
- **Distortion in continuous-time filters**
- **Guide lines**

Guide lines for low distortion

- **Scaling such that voltage amplitudes are limited**
- **Scaling such that relative current swings are limited**
- **Feedback**
- **All fully differential**

Distortion components

Distortion comp.	$IM_2 \times U_p$	$IM_3 \times U_p^2$	$U_p = \frac{V_{ip}}{V_{ref}} \quad V_{ref} =$
Bipolar	1/2	1/8	kT_e/q
MOST	1/4	0	$(V_{GS}-V_T)/2$
Bip. diff.pair	0	1/4	$2kT_e/q$
MOST diff.pair	0	3/32	$(V_{GS}-V_T)$

Distortion components with Feedback ($T > 5$)

Distortion comp.	IM_2 $\times U_p$	$-IM_3$ $\times U_p^2$	$U_p = \frac{V_{ip}}{V_{ref}} \quad V_{ref} =$
Bipolar	$1/2T$	$1/4T$	$kT_e/q \times T$
MOST	$1/4T$	$3/32T$	$(V_{GS}-V_T)/2 \times T$
Bip. diff.pair	0	$1/4T$	$2kT_e/q \times T$
MOST diff.pair	0	$3/32T$	$(V_{GS}-V_T) \times T$

References

P.Wambacq, W.Sansen : Distortion analysis of analog Integrated Circuits, Kluwer Ac. Publ. 1998

**W.Sansen : “Distortion in elementary transistor circuits”
IEEE Trans. CAS II Vol 46, No 3, March 1999, pp.315-324**

J. Silva-Martinez, etal : High-performance CMOS continuous-time filters, Kluwer Ac. Publ. 1993

B. Hernes, T. Saether : Design criteria for low-distortion in feedback opamp circuits, Kluwer Ac. Publ. 2003

G. Palumbo, S. Pennisi : Feedback amplifiers, Kluwer Ac. Publ. 2002

Table of contents

- ☐ **Definitions : HD, IM, intercept point, ..**
- ☐ **Distortion in a MOST**
 - **Single-ended amplifier**
 - **Differential amplifier**
- ☐ **Distortion in a bipolar transistor**
- ☐ **Reduction of distortion by feedback**
- ☐ **Distortion in an opamp**
- ☐ **Other cases of distortion and guide lines**