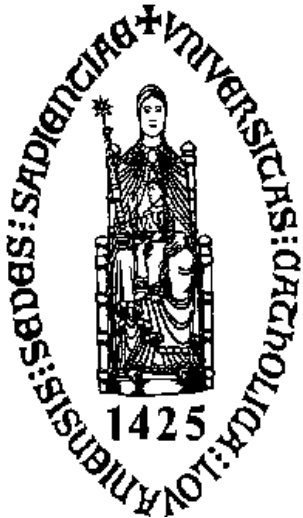

Design of crystal oscillators



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be



Table of contents

◆ Oscillation principles

◆ Crystals


◆ Single-transistor oscillator

◆ MOST oscillator circuits

◆ Bipolar-transistor oscillator circuits

◆ Other oscillators

The Barkhausen criterion

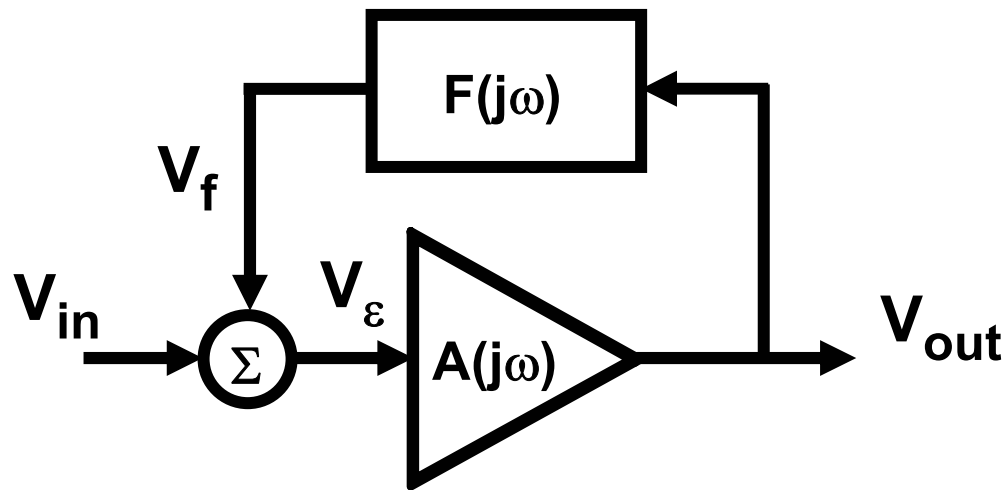

$$V_{out} = A(j\omega) V_\varepsilon$$

$$\begin{aligned} V_f &= F(j\omega) V_{out} \\ &= F(j\omega) A(j\omega) V_\varepsilon \end{aligned}$$


$$\frac{V_f}{V_\varepsilon} = A(j\omega) F(j\omega)$$

Oscillation if $V_{in} = 0$ or if $\left| \frac{V_f}{V_\varepsilon} \right| = |A(j\omega)| |F(j\omega)| \geq 1.0$
Positive FB !

$$\left\{ \frac{V_f}{V_\varepsilon} \right\} = \Phi_A + \Phi_F = 0^\circ$$

Ref. Barkhausen, Hirzel, Leipzig, 1935

Split analysis

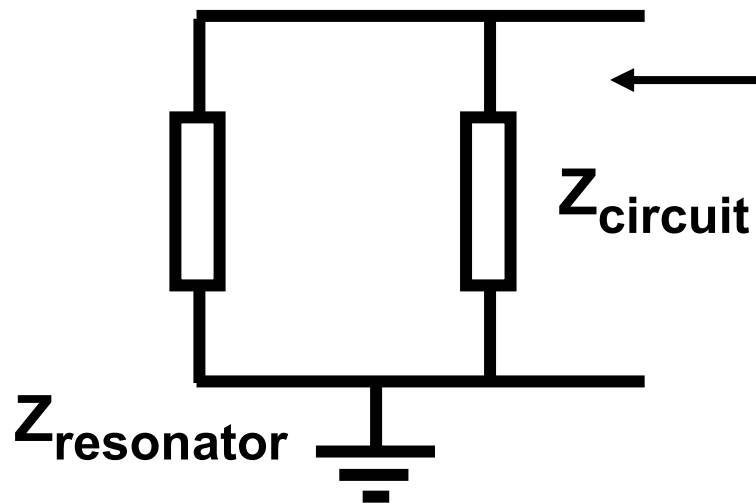

$$Y_{\text{res}} + Y_{\text{circuit}}$$

$$Y_{\text{res}} + Y_{\text{circuit}} = 0$$

$$\frac{1}{Z_{\text{res}}} + \frac{1}{Z_{\text{circuit}}} = 0$$

$$\frac{Z_{\text{circuit}} + Z_{\text{res}}}{Z_{\text{res}} Z_{\text{circuit}}} = 0$$

Oscillation if $\text{Re}(Z_{\text{circuit}} + Z_{\text{res}}) = 0$ sets the minimum gain !

$\text{Im}(Z_{\text{circuit}} + Z_{\text{res}}) = 0$ sets the frequency !

Table of contents

- ◆ Oscillation principles

- ◆ Crystals


- ◆ Single-transistor oscillator

- ◆ MOST oscillator circuits

- ◆ Bipolar-transistor oscillator circuits

- ◆ Other oscillators

Crystal as resonator

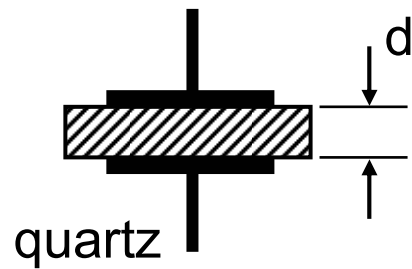


$$f_s = \frac{1.66}{d}$$

f_s in MHz if d in mm

$$C_p = A \frac{\epsilon_0 \epsilon_r}{d}$$

$\epsilon_r \approx 4.5$

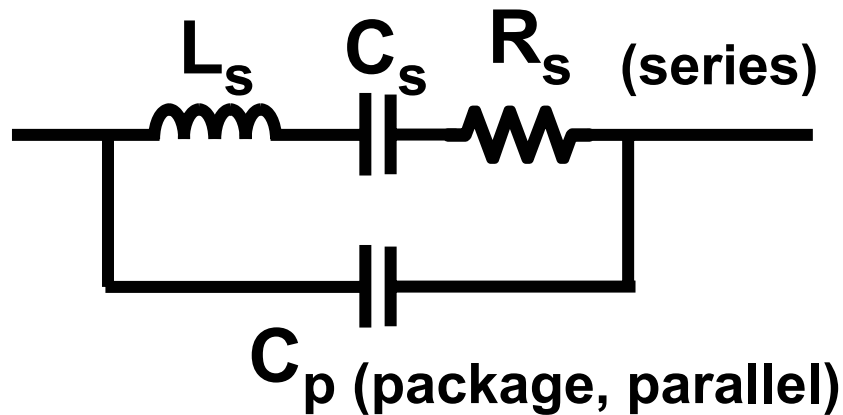


$$\omega_s^2 = \frac{1}{L_s C_s} \quad f_s = \frac{1}{2\pi \sqrt{L_s C_s}}$$

$$L_s \omega_s = \frac{1}{C_s \omega_s} \quad Q \omega_s = \frac{1}{R_s C_s}$$

$$Q = \frac{1}{R_s} \sqrt{\frac{L_s}{C_s}} \quad R_s = \frac{1}{Q C_s \omega_s}$$

Crystal parameters

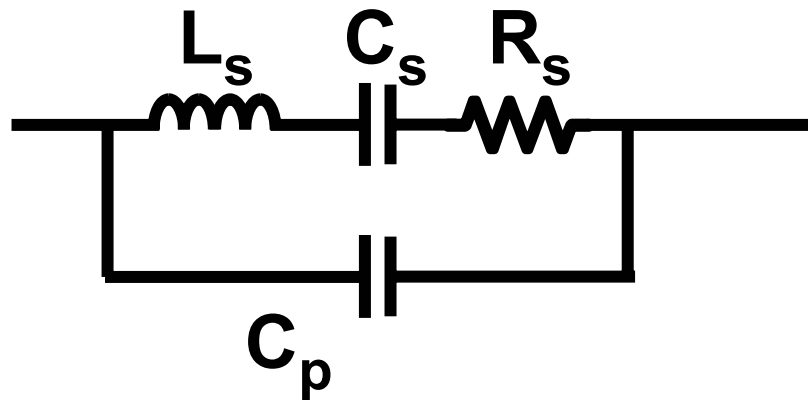

Xtal : $f_s = 10.000 \text{ MHz}$

$$Q = 10^5$$

$$C_s = 0.03 \text{ pF}$$


$$C_p \approx 6 \text{ pF } (\approx 200 C_s)$$

$$L_s \omega_s = \frac{1}{C_s \omega_s} \quad L_s \approx 8.4 \text{ mH}$$

$$R_s = \frac{1}{Q C_s \omega_s} = 5.3 \Omega$$


f_s	L_s	C_s	R_s	C_p	Q
100.0 kHz	52 H	49 fF	400 Ω	8 pF	$0.8 \cdot 10^5$
1.000 MHz	2 H	6 fF	24 Ω	3.4 pF	$5.3 \cdot 10^5$
10.00 MHz	10 mH	26 fF	5 Ω	8.5 pF	$1.2 \cdot 10^5$

Series and parallel resonance

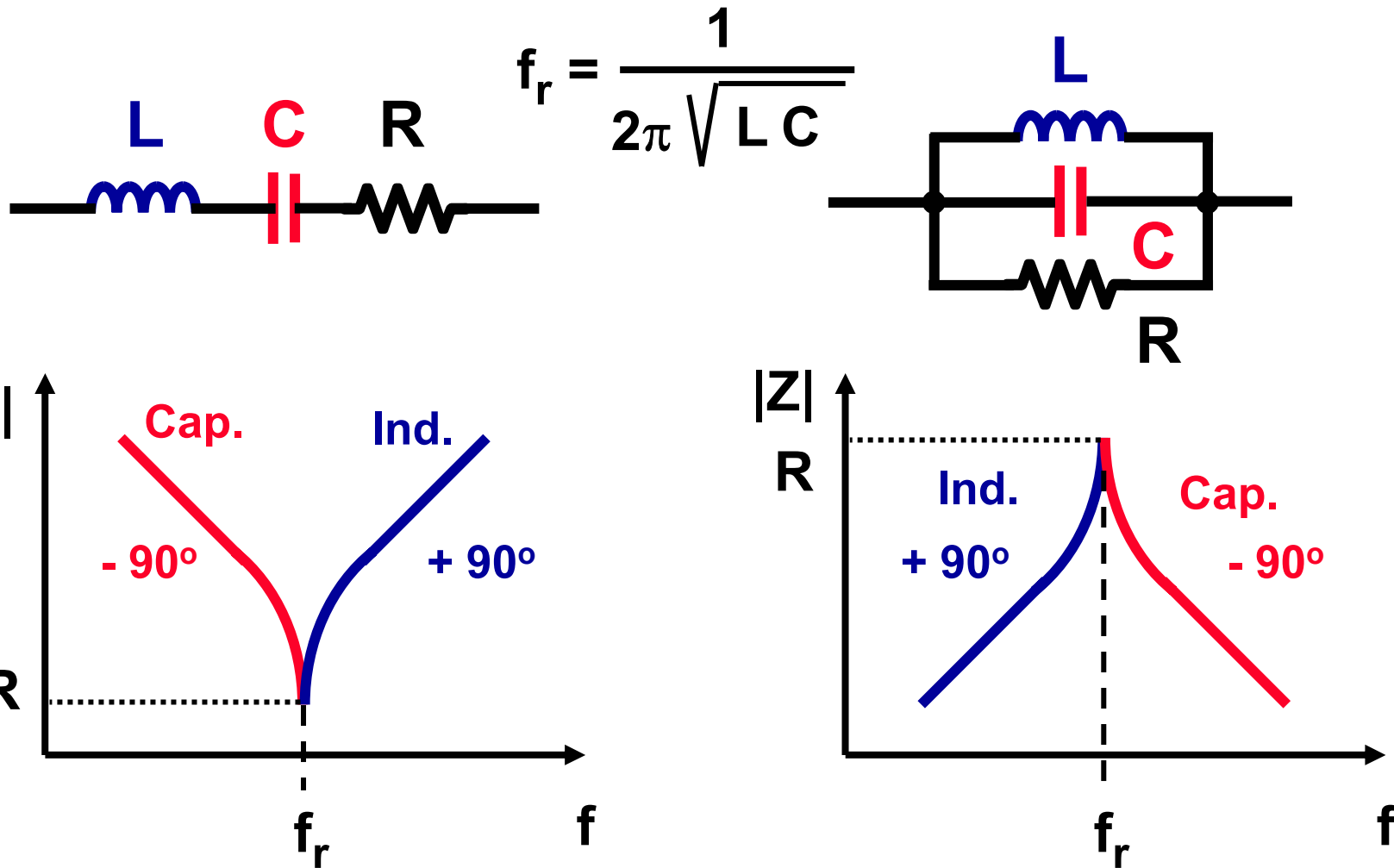


Crystal impedance
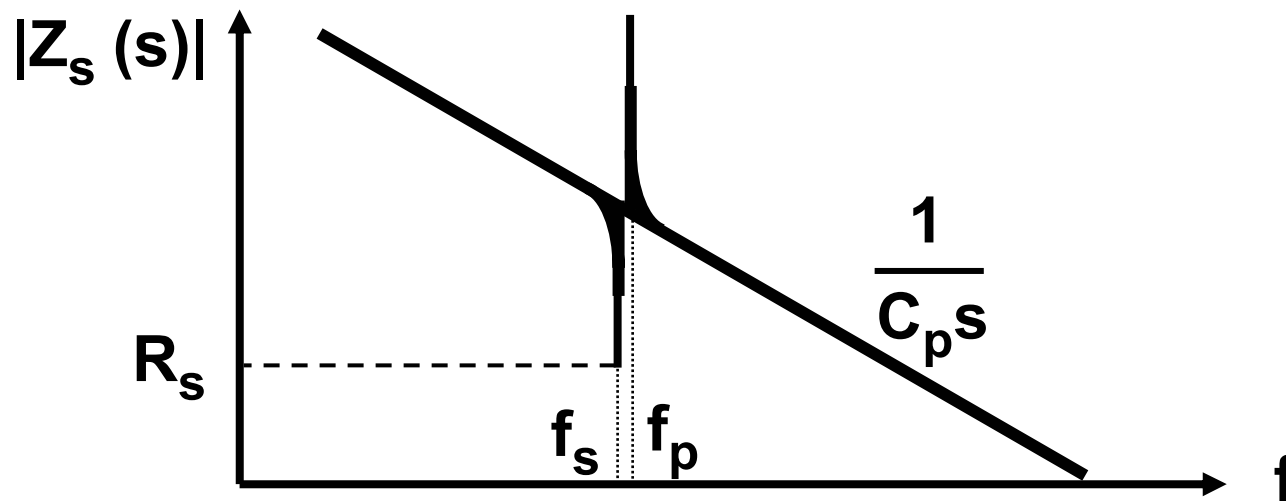
$$Z_s(s) = \frac{s^2 L_s C_s + s R_s C_s + 1}{s (C_s + C_p) \left(s^2 \frac{L_s C_s C_p}{C_s + C_p} + s \frac{R_s C_s C_p}{C_s + C_p} + 1 \right)}$$



Crystal impedance at resonance

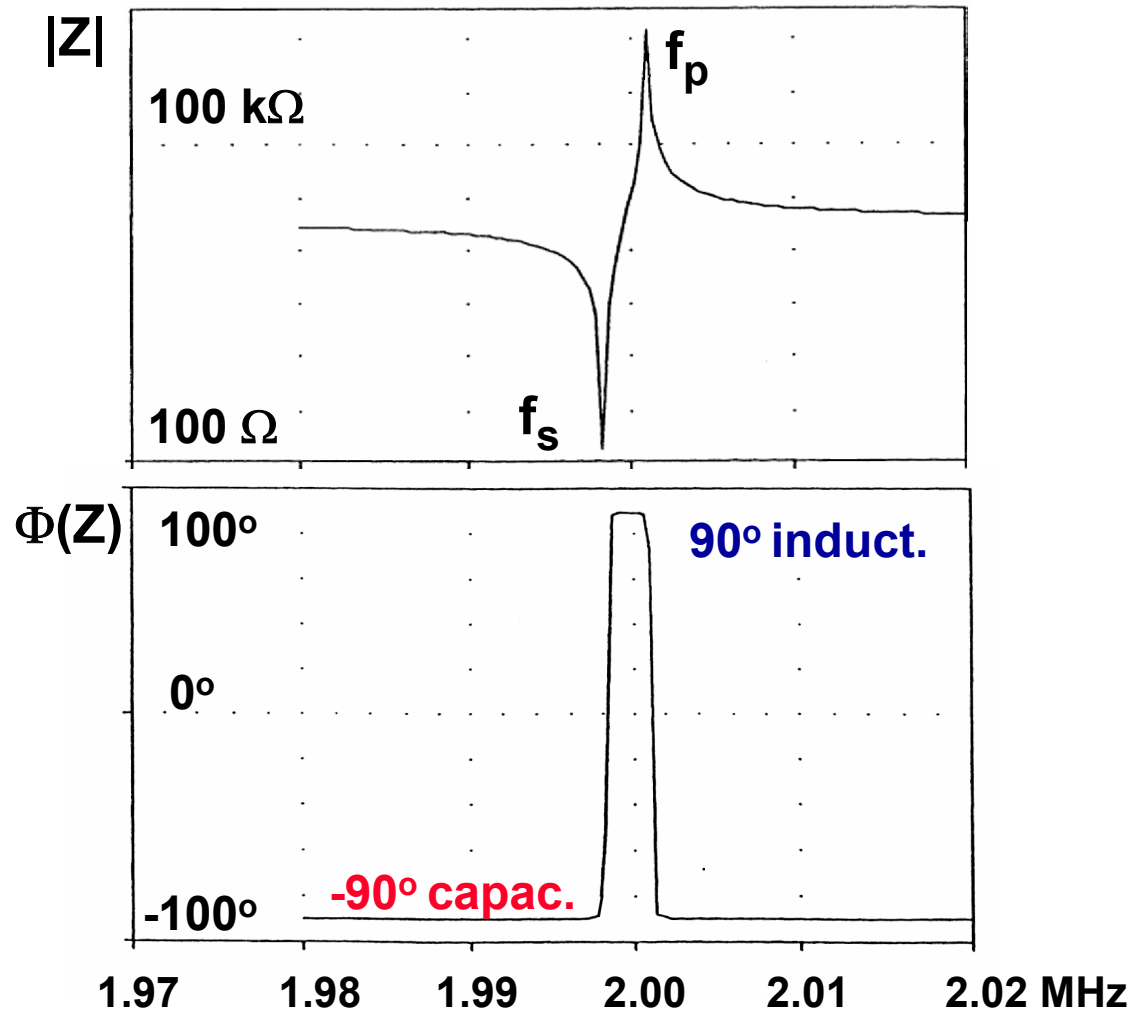

$$f_s = 1.998\text{ MHz}$$

$$C_s = 12.2\text{ fF}$$

$$L_s \approx 0.52\text{ H}$$

$$C_p = 4.27\text{ pF}$$

$$R_s = 82\text{ }\Omega$$

Crystal operates in
inductive region
if circuit is capacitive !

Series and parallel resonance

$$Z_s(\omega) = \frac{-j}{\omega C_p} \frac{\omega^2 - \omega_s^2}{\omega^2 - \omega_p^2} \quad \omega_s^2 = \frac{1}{L_s C_s} \quad \omega_p^2 = \frac{1}{L_s} \left(\frac{1}{C_p} + \frac{1}{C_s} \right)$$

series **parallel**

$$Z_s(\omega) = R_s + j\omega L_s + \frac{1}{j\omega C_s}$$

$$Z_s(\omega) = R_s + \frac{j}{\omega_s C_s} \left(\frac{\omega}{\omega_s} - \frac{\omega_s}{\omega} \right)$$


Frequency pulling factor

$$p = \frac{\omega - \omega_s}{\omega_s}$$

$$Z_s(\omega) \approx R_s + j \frac{2p}{\omega C_s}$$

Ref. Vittoz, JSSC June 88, 774-783

Series or parallel resonance ?

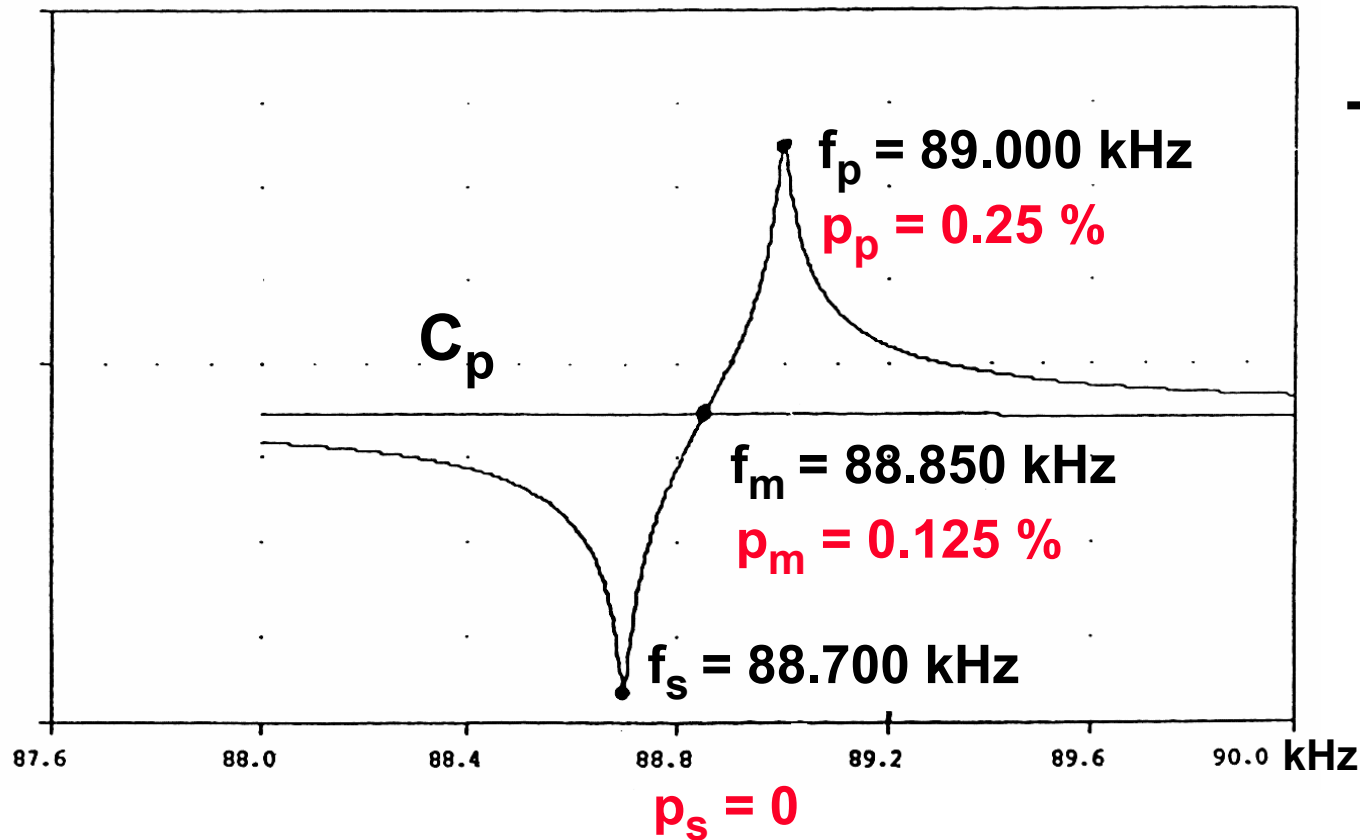

$$\frac{f_p}{f_s} = \sqrt{1 + \frac{C_s}{C_p}}$$

$$\approx 1 + \frac{C_s}{2C_p}$$

$$p_p = \frac{f_p - f_s}{f_s}$$


$$\frac{C_s}{2C_p} = 0.25\%$$

$$p_m = \frac{f_m - f_s}{f_s} = \frac{C_s}{4C_p} = 0.125\%$$




Table of contents

- ◆ Oscillation principles
- ◆ Crystals
- ◆ **Single-transistor oscillator**
- ◆ MOST oscillator circuits
- ◆ Bipolar-transistor oscillator circuits
- ◆ Other oscillators



Single-transistor X-tal oscillator

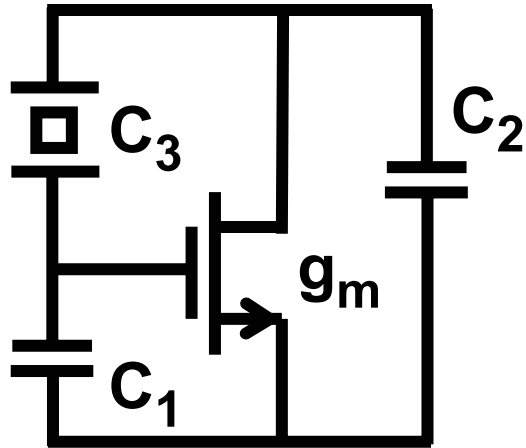

Basic three-point oscillator

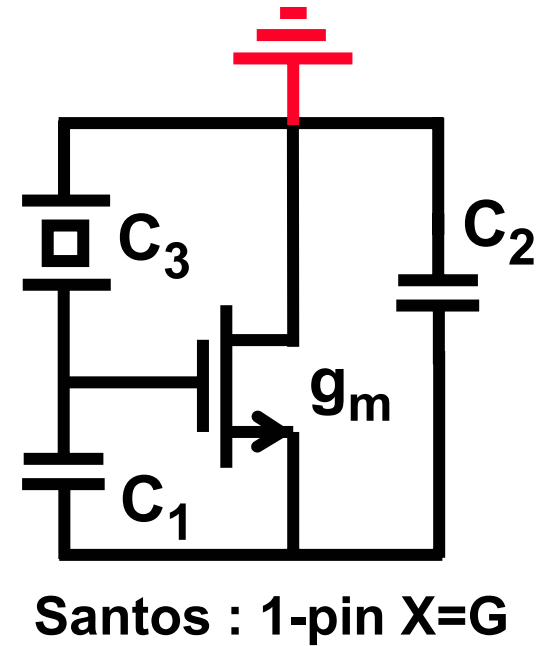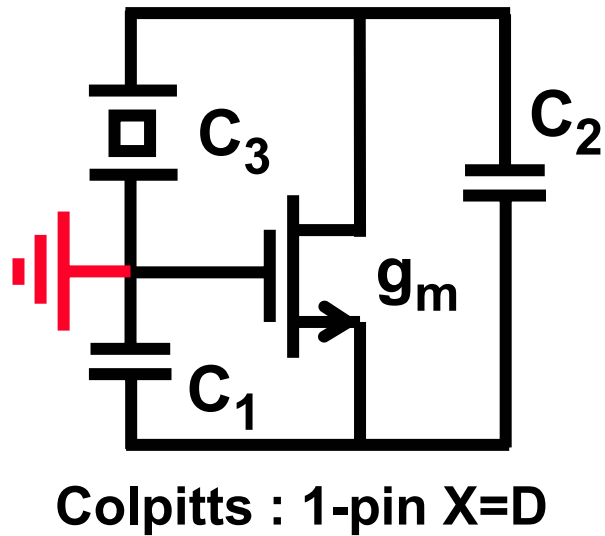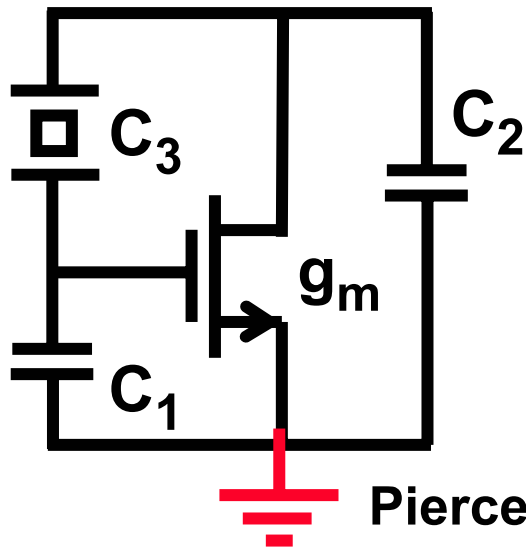

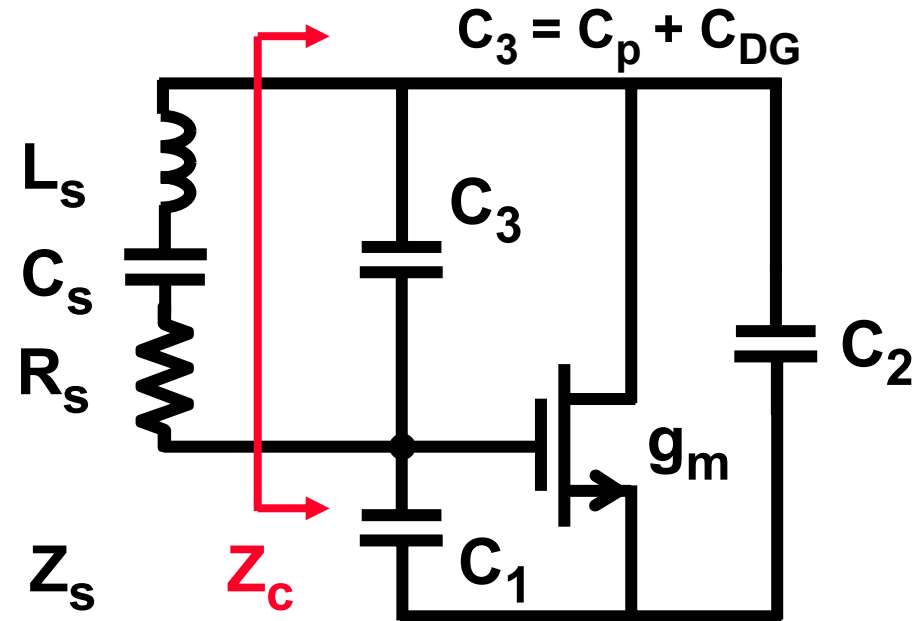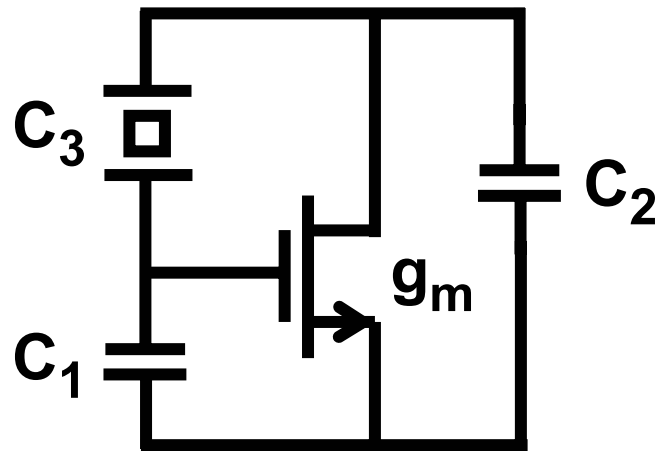Single-transistor X-tal oscillator analysis




Barkhausen : $Z_s + Z_c = 0$ $Z_s = R_s + j \frac{2p}{\omega C_s}$

$\text{Re}(Z_c) = -R_s$ yields g_m


$\text{Im}(Z_c) = - \frac{2p}{\omega C_s}$ yields f or p

Ref. Vittoz, JSSC June 88, 774-783

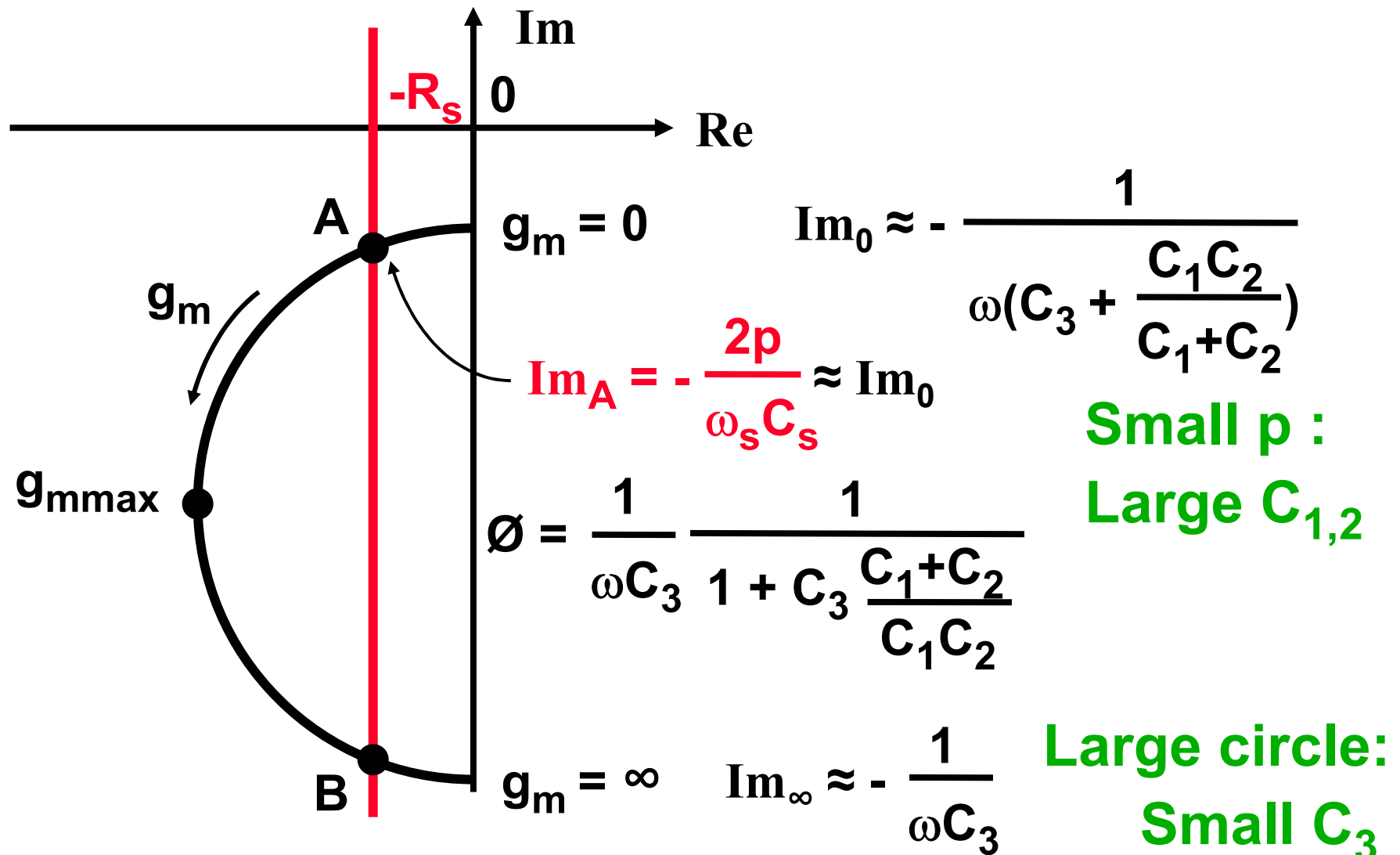
Complex plane for 3-pt oscillator : Design crit.



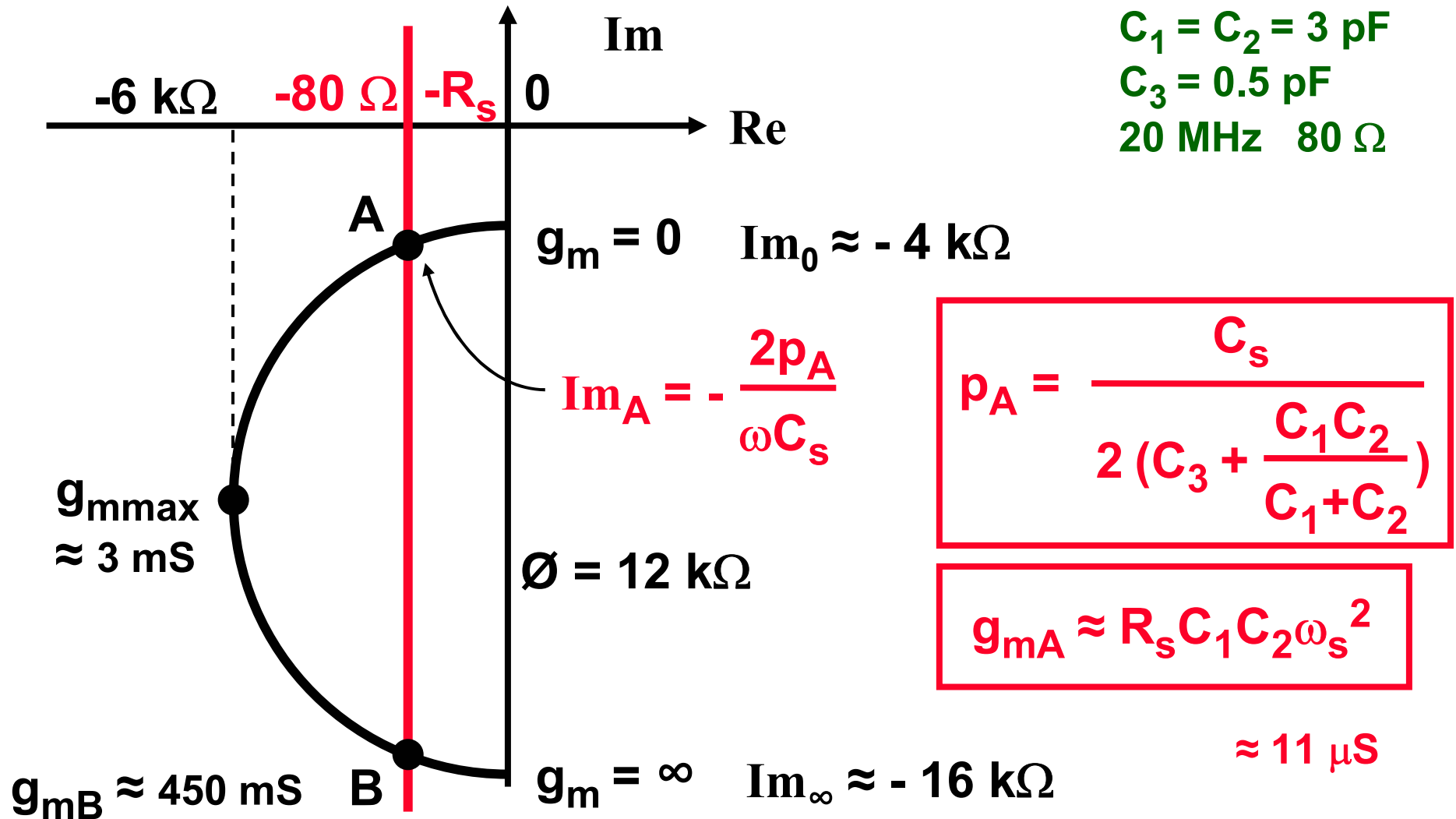Complex plane for 3-pt oscillator : Example



Amplitude of oscillation

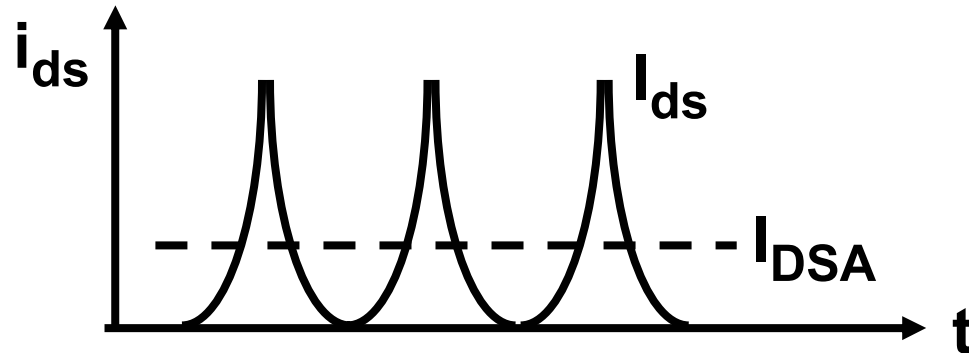

$$V_{gs} = \frac{I_{ds}}{g_{mA}} = \frac{I_{ds}}{I_{DSA}} \frac{I_{DSA}}{g_{mA}}$$

$$\frac{2}{\pi} \dots 2 \frac{V_{GS} - V_T}{2}$$

$$V_{gs} \approx$$

$$V_{GS} - V_T$$

Large !

$\frac{I_{ds}}{I_{DSA}}$ Nonlinear (Bessel)
More spiked for
higher $C_{1,2}$!!!

or $2n \frac{kT}{q}$ in wi

Start-up of oscillation

τ_{\min} occurs at $g_m \approx g_{m\max}$

$$\tau_{\min} = \frac{L_s}{\operatorname{Re}(Z_s) + R_s}$$

$\operatorname{Re}(Z_s)$ is half circle Ø

$$\operatorname{Re}(Z_s) = \frac{1}{2} \frac{1}{\omega_s C_3} \quad \text{if } C_3 \ll C_1$$

$$R_s \ll \operatorname{Re}(Z_s)$$

$$\tau_{\min} \approx \frac{2 C_3}{\omega_s C_s} \approx \frac{400}{\omega_s} \quad \text{since } C_3 \approx 200 C_s$$

or also $\tau_{\min} \approx 2Q R_s C_3$

Power dissipation

In MOST : $g_{mA} \approx \omega_s^2 R_s C_1 C_2 \approx R_s (C_1 \omega_s)^2$

$$I_{DSA} \approx g_{mA} \frac{V_{GS} - V_T}{2} \approx 2 \mu A \Rightarrow 6 \mu W$$

In X-tal : $I_c = \frac{V_{gs}}{Z_{C1}} = |V_{gs}| C_1 \omega_s \approx |V_{GS} - V_T| C_1 \omega_s$

$$P_c = \frac{R_s I_c^2}{2} = \frac{R_s}{2} |V_{GS} - V_T|^2 (C_1 \omega_s)^2$$

$$= |V_{GS} - V_T|^2 \frac{g_{mA}}{2} \approx 0.2 \mu W$$

Design procedure for X-tal oscillators - 1

X-tal : f_s f_p R_s C_p (or f_s Q C_s C_p) ($Q = 1/\omega_s C_s R_s$)

1. Take : $C_3 > C_p$ but as small as possible

$$\text{Pulling factor } p = \frac{1}{2} \frac{C_s}{C_3 + \frac{C_1 C_2}{C_1 + C_2}} \approx \frac{1}{2} \frac{C_s}{C_L} \quad C_L = \frac{C_1}{2} = \frac{C_2}{2}$$

If $p < \frac{C_s}{4C_p}$ it is a series oscillator (best !)

If $p > \frac{C_s}{4C_p}$ it is a parallel oscillator (not stable !)

Choose C_L large ($> C_3$), subject to power dissipation !

Design procedure for X-tal oscillators - 2

2. Calculate $g_{mA} \approx R_s C_L^2 \omega_s^2$ ($\approx \frac{\omega_s}{C_s Q} C_L C_L$)
and take $g_{mStart} \approx 10 g_{mA}$


3. Choose $V_{GS} - V_T$, which gives the amplitude V_{gs}

and current $I_{DS} = \frac{g_m(V_{GS} - V_T)}{2}$ and $\frac{W}{L}$




and power $P = (V_{GS} - V_T)^2 \frac{g_m}{2}$


4. Verify that biasing $R_B > 1 / (R_s C_3^2 \omega_s^2)$

Single-transistor X-tal oscillator

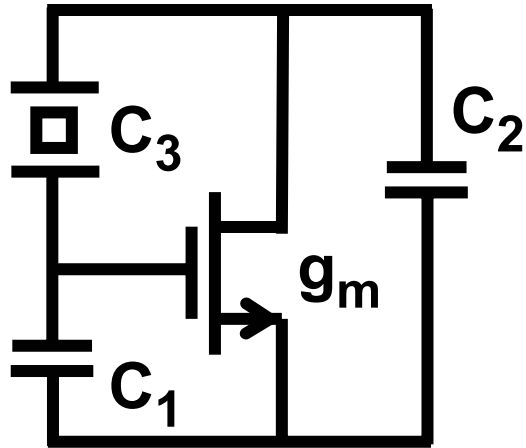



Basic three-point oscillator

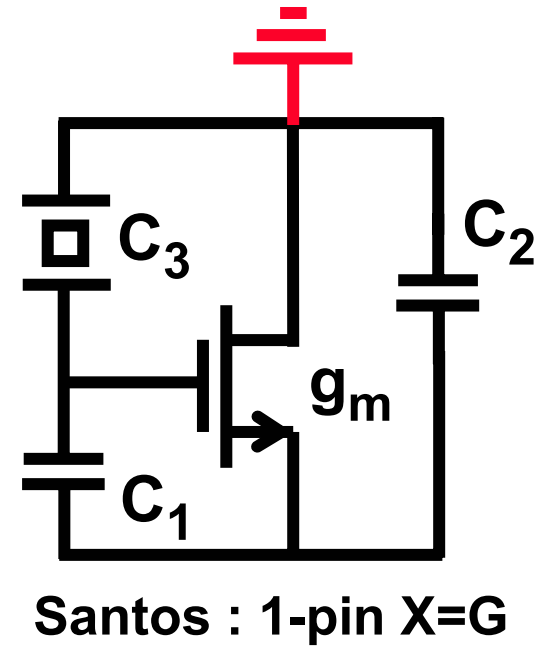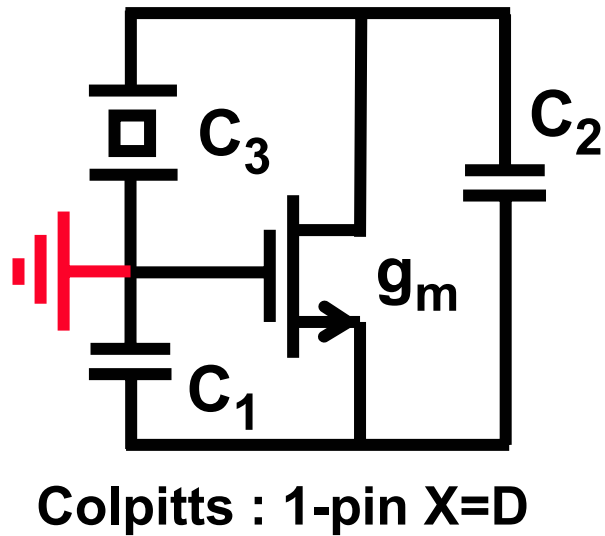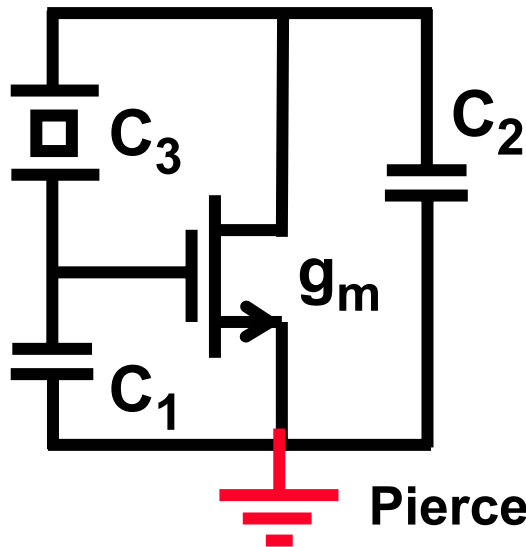

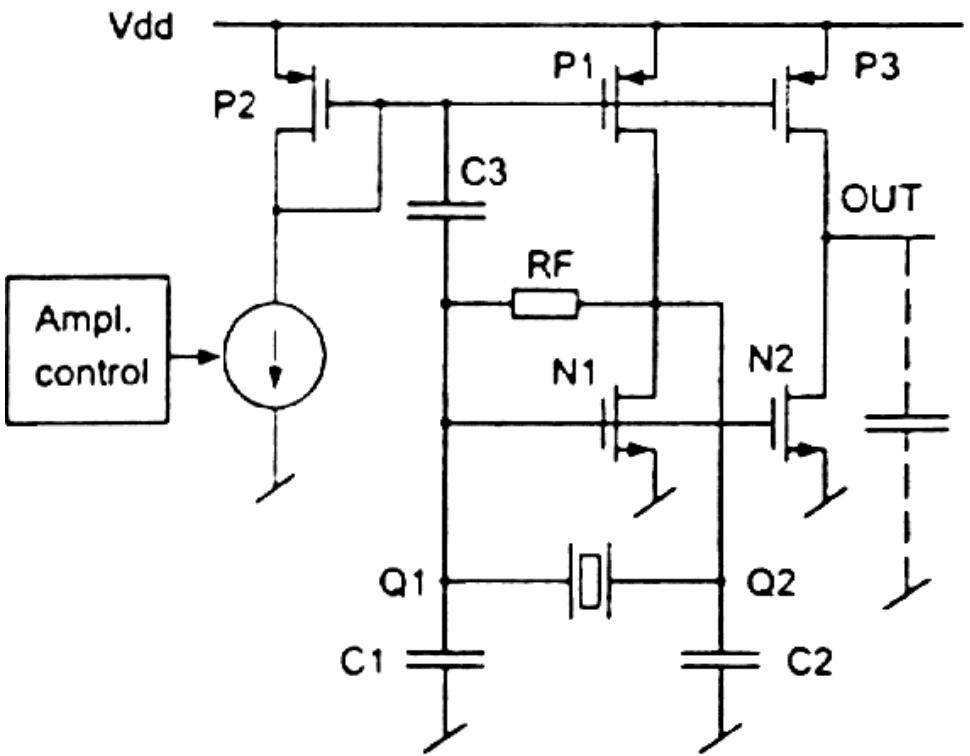


32 kHz 1.2 V 78 nA

Colpitts X-tal oscillator

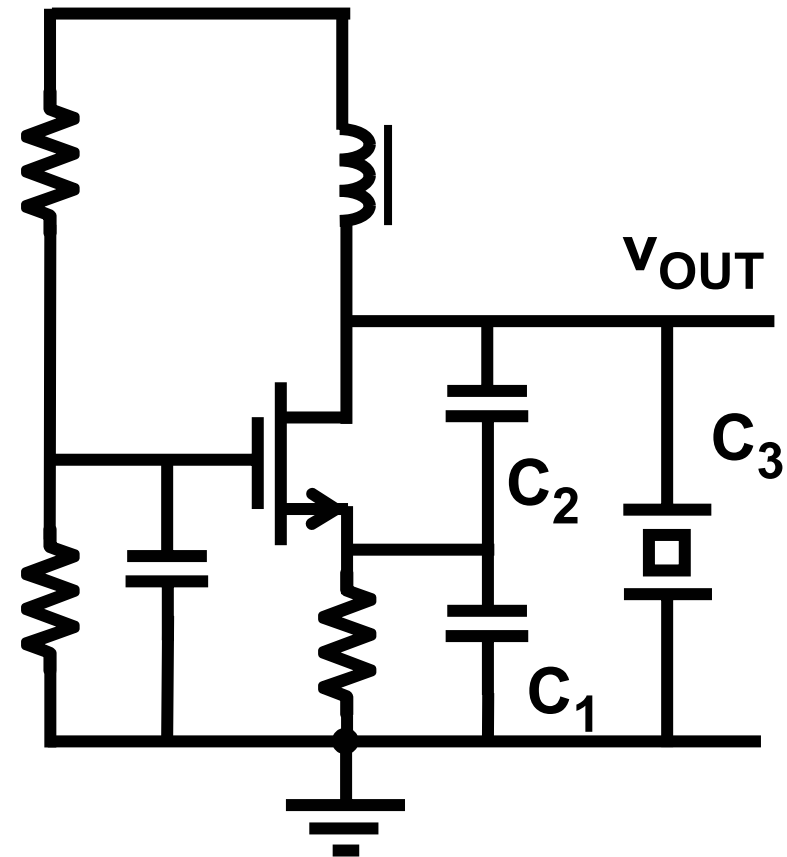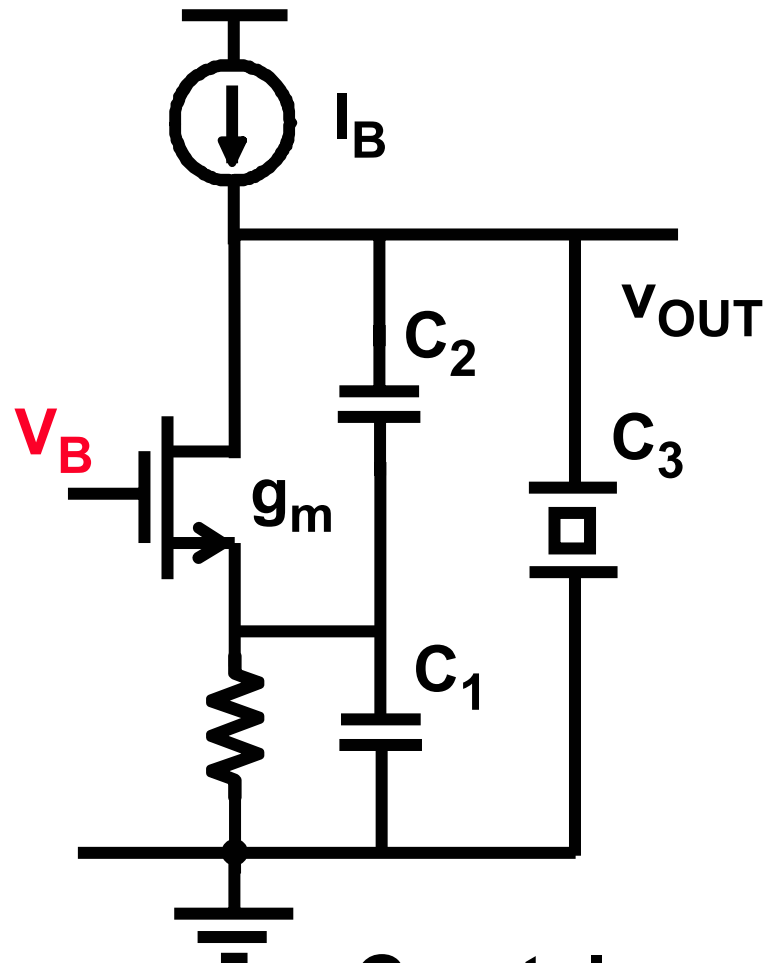

Crystal grounded : single-pin : $X = D$

Santos X-tal oscillator

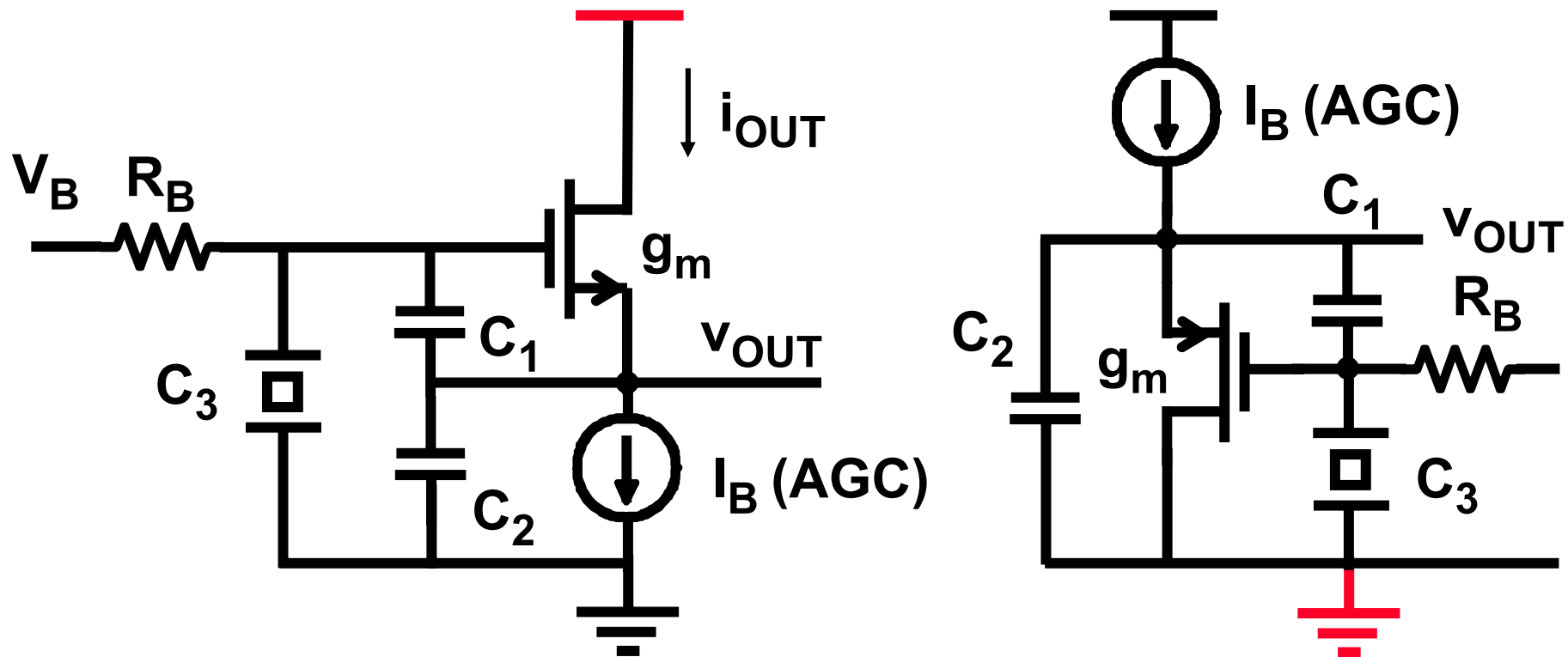


Crystal grounded : single-pin : $X = G$

Ref. Santos, JSSC April 84, 228-236 Ref. Redman-White, JSSC Feb.90, 282-288

Table of contents


- ◆ Oscillation principles
- ◆ Crystals
- ◆ Single-transistor oscillator
- ◆ **MOST oscillator circuits**
- ◆ Bipolar-transistor oscillator circuits
- ◆ Other oscillators

Practical Pierce X-tal oscillator

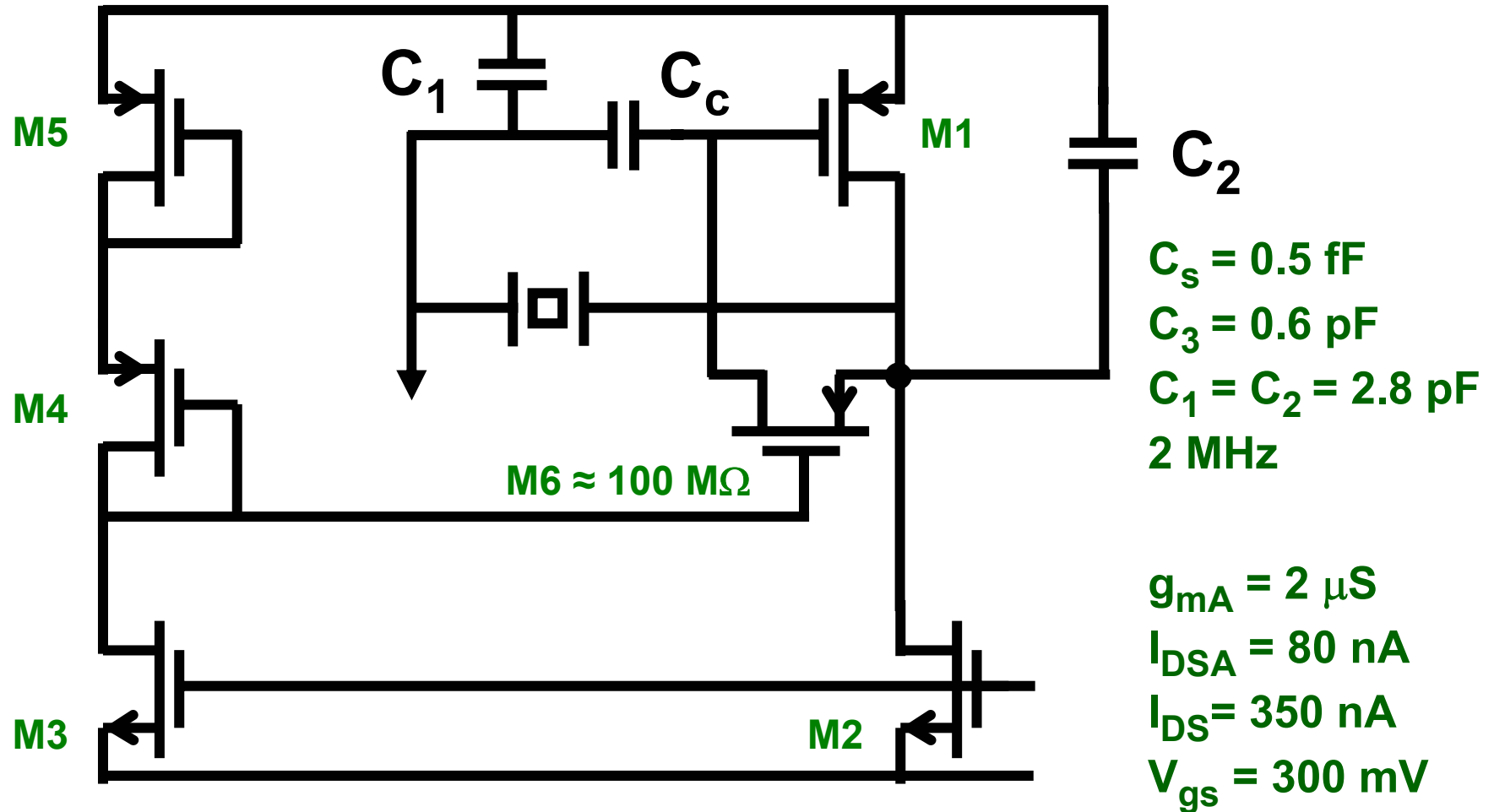


Ref. Vittoz, JSSC June 88, 774-783

Full schematic

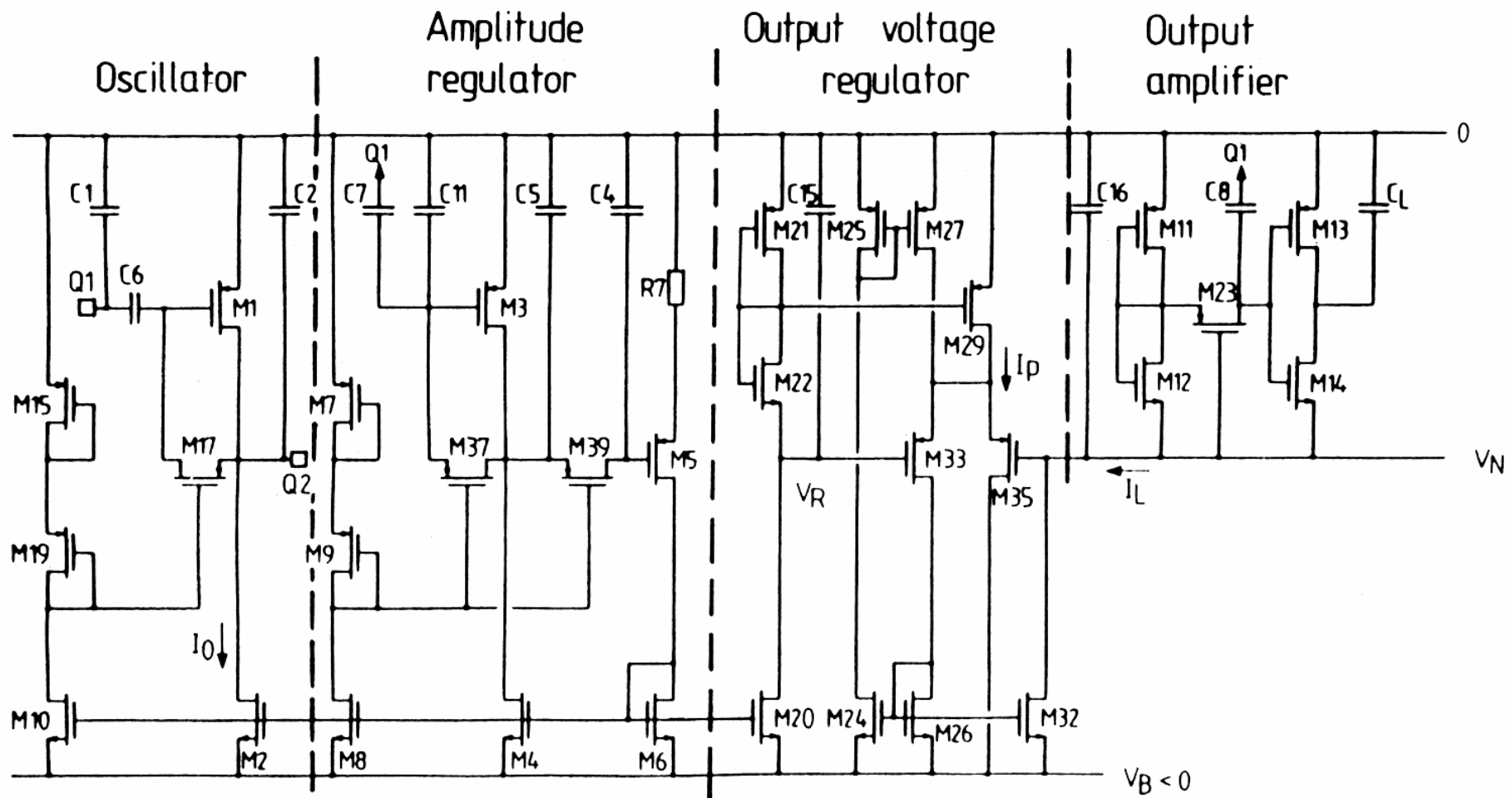

Ref. Vittoz, JSSC June 88, 774-783

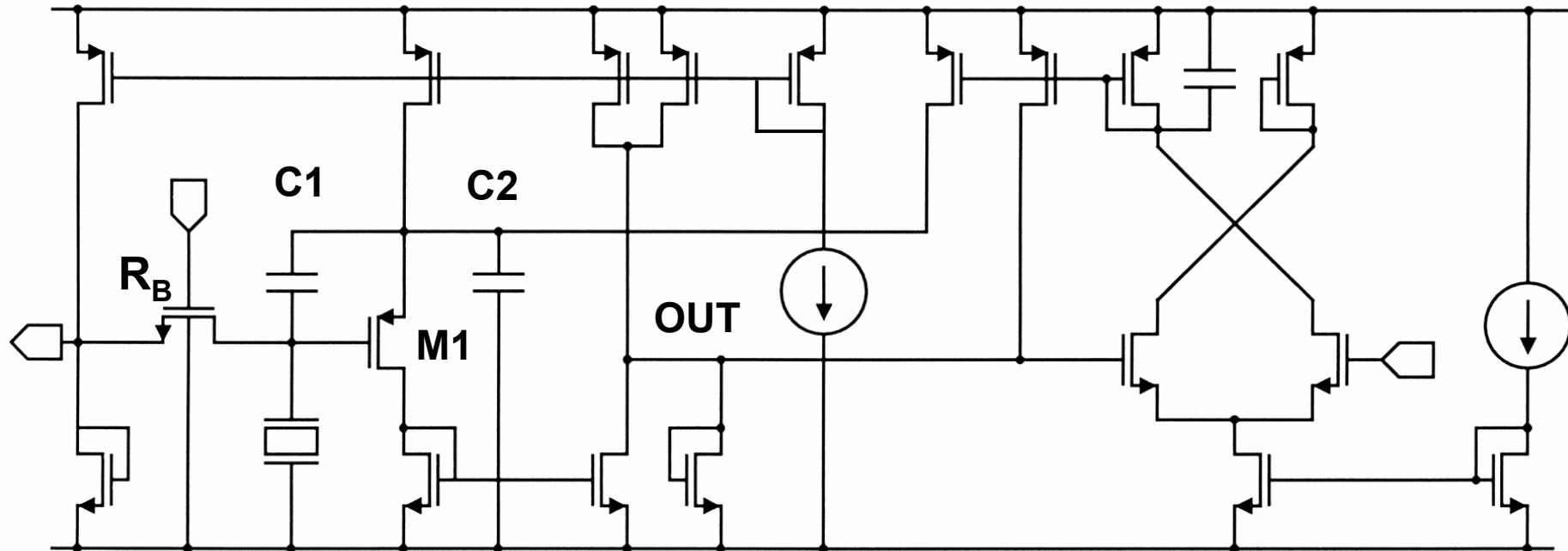Single-pin oscillator with crystal to Gate



$$f_s = 9.9956 \text{ MHz}$$

$$f_p = 10.012 \text{ MHz}$$

$$C_s = 24.3 \text{ fF}$$

$$C_o = 7.4 \text{ pF}$$

$$L = 10.4 \text{ mH}$$

$$R = 7.2 \text{ } \Omega \text{ (?)}$$


$$p = 0.8 \cdot 10^{-3}$$

$$C_1 = C_2 = 50 \text{ pF}$$

$$g_{mA} = 350 \text{ } \mu\text{S}$$

$$I_{DSA} = 90 \text{ } \mu\text{A} \text{ (} V_{GS} - V_T = 0.5 \text{ V)}$$

Single-pin oscillator - 1

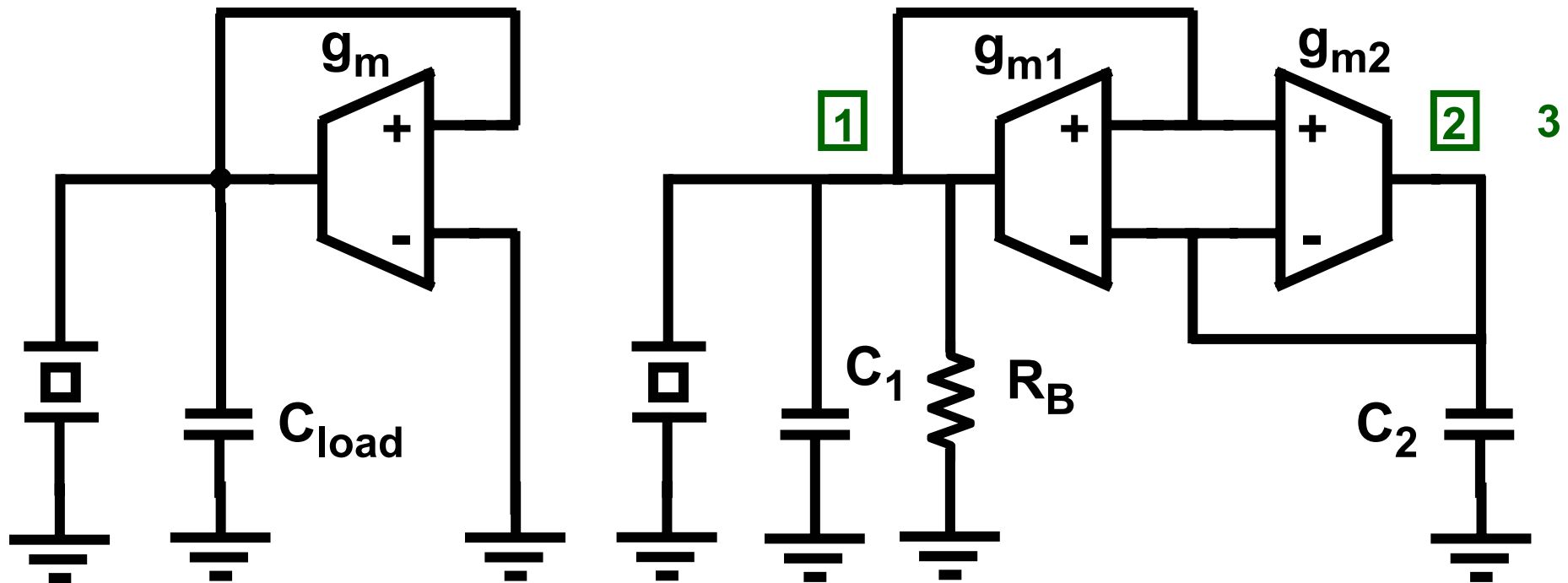


$g_m = R_s (C_s \omega_0)^2$
DC unstable !

Positive FB dominant
at crystal frequency !

Ref. van den Homberg, JSSC July 99, 956-961




Single-pin oscillator - 2

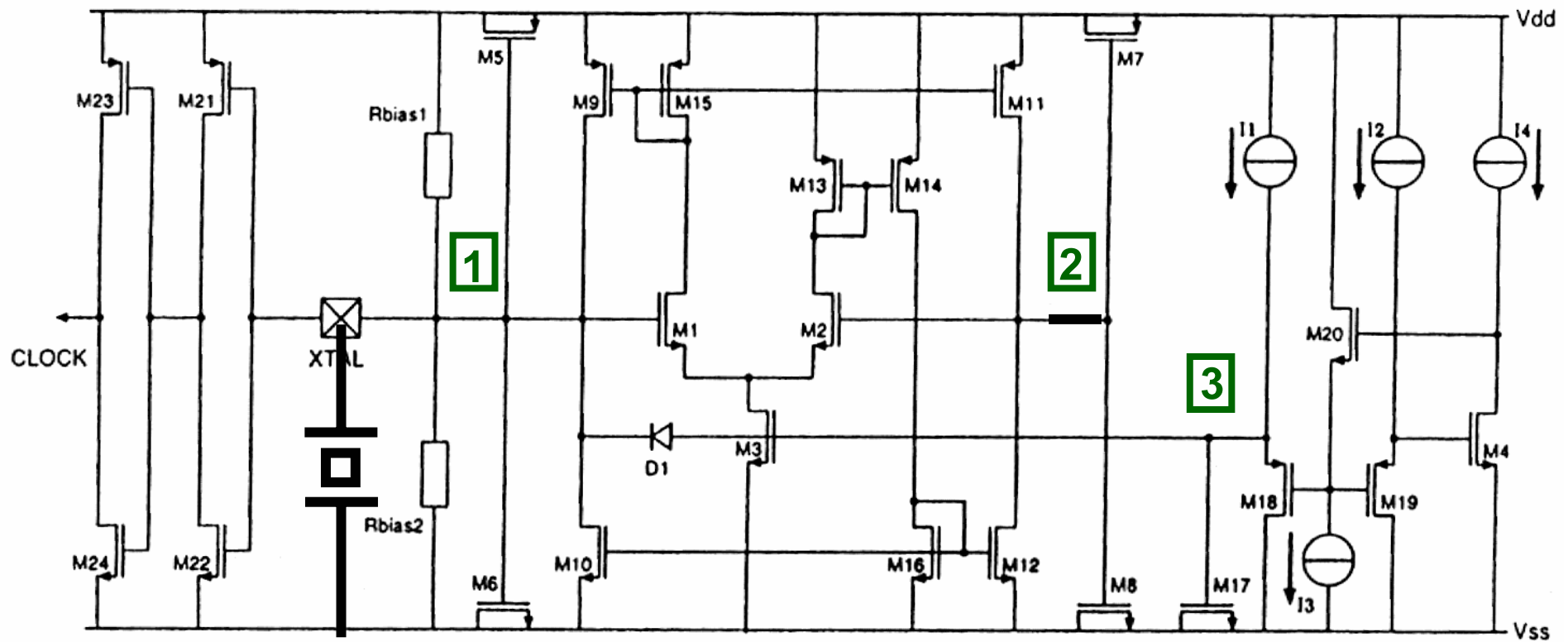

10 MHz, 3.3 V, 0.35 mA

Ref. van den Homberg, JSSC July 99, 956-961

X-tal oscillators with CMOS inverters

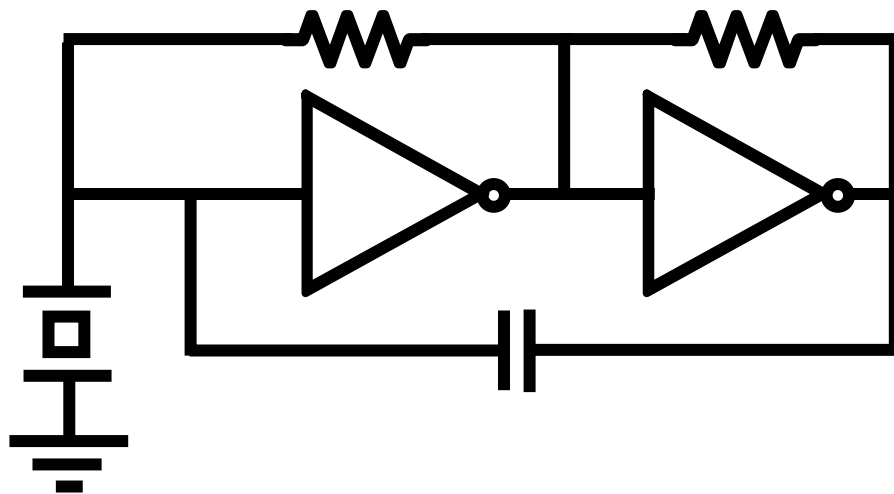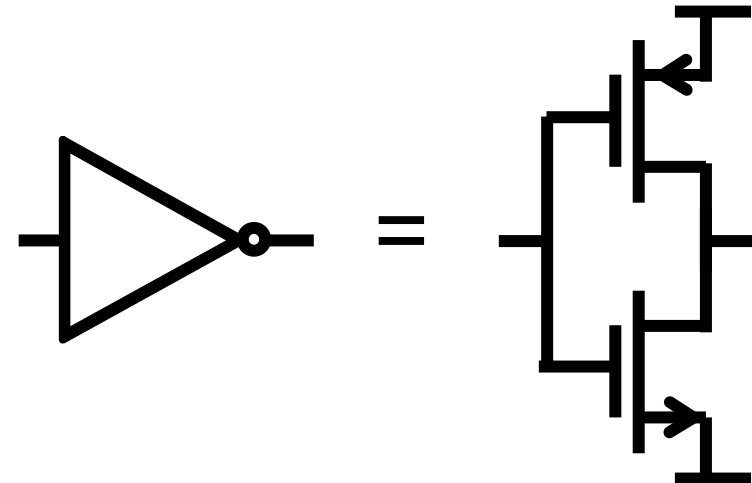
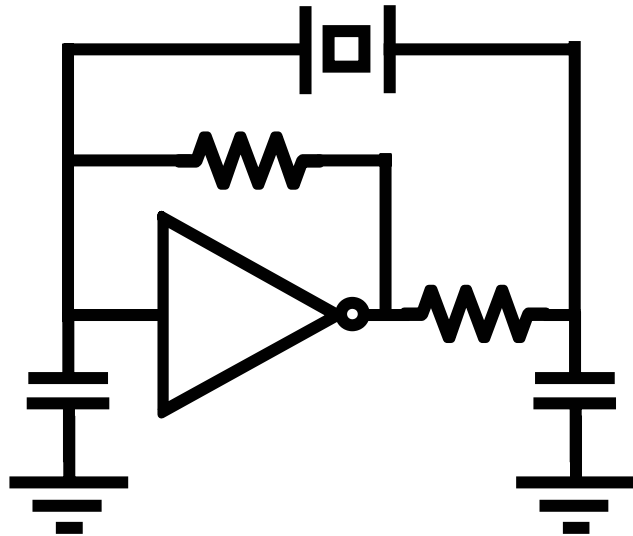


**Large current peaks !
Bad PSRR !!**



Table of contents

- ◆ Oscillation principles
- ◆ Crystals
- ◆ Single-transistor oscillator
- ◆ MOST oscillator circuits
- ◆ **Bipolar-transistor oscillator circuits**
- ◆ Other oscillators

Pierce X-tal oscillator

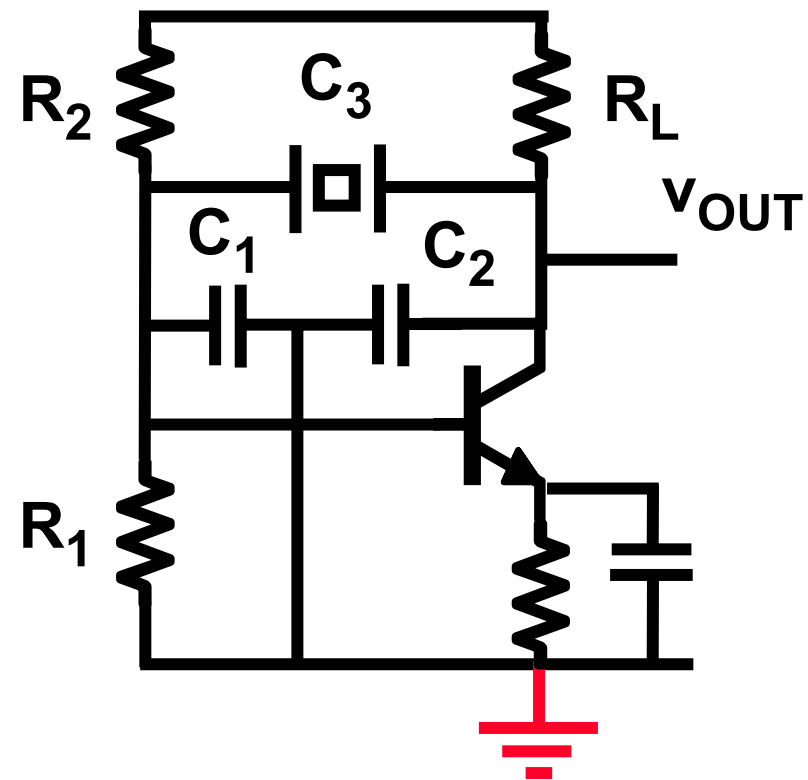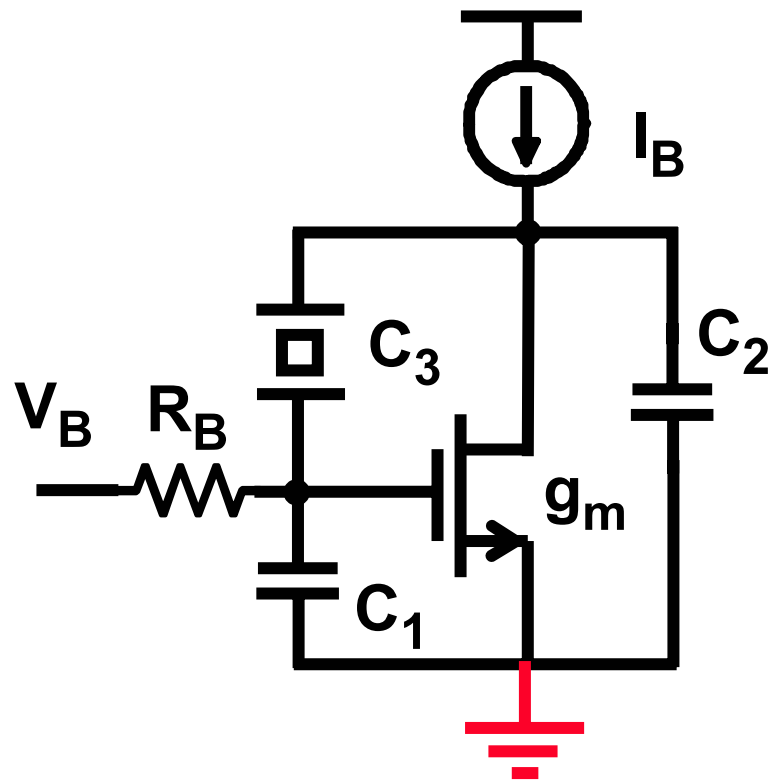


Colpitts X-tal oscillator

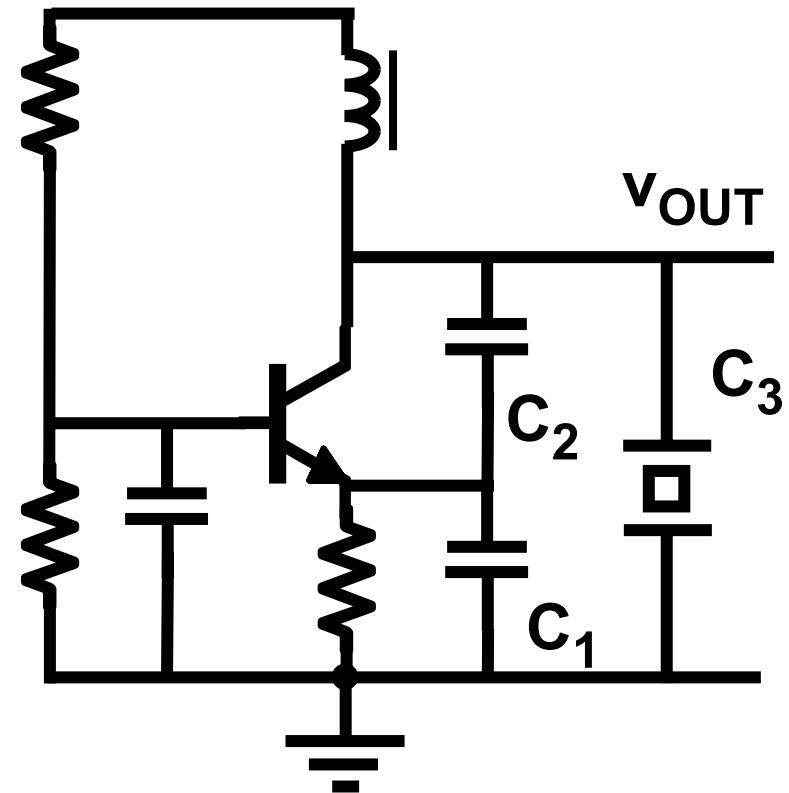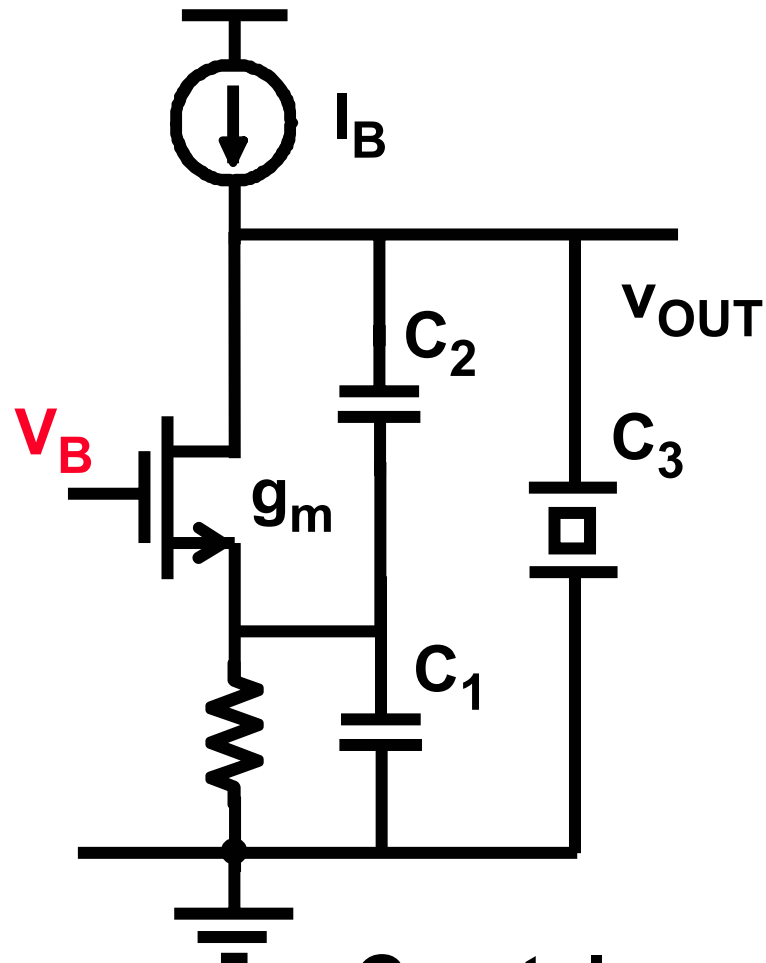

Crystal grounded : single-pin : $X = D$

Santos X-tal oscillator

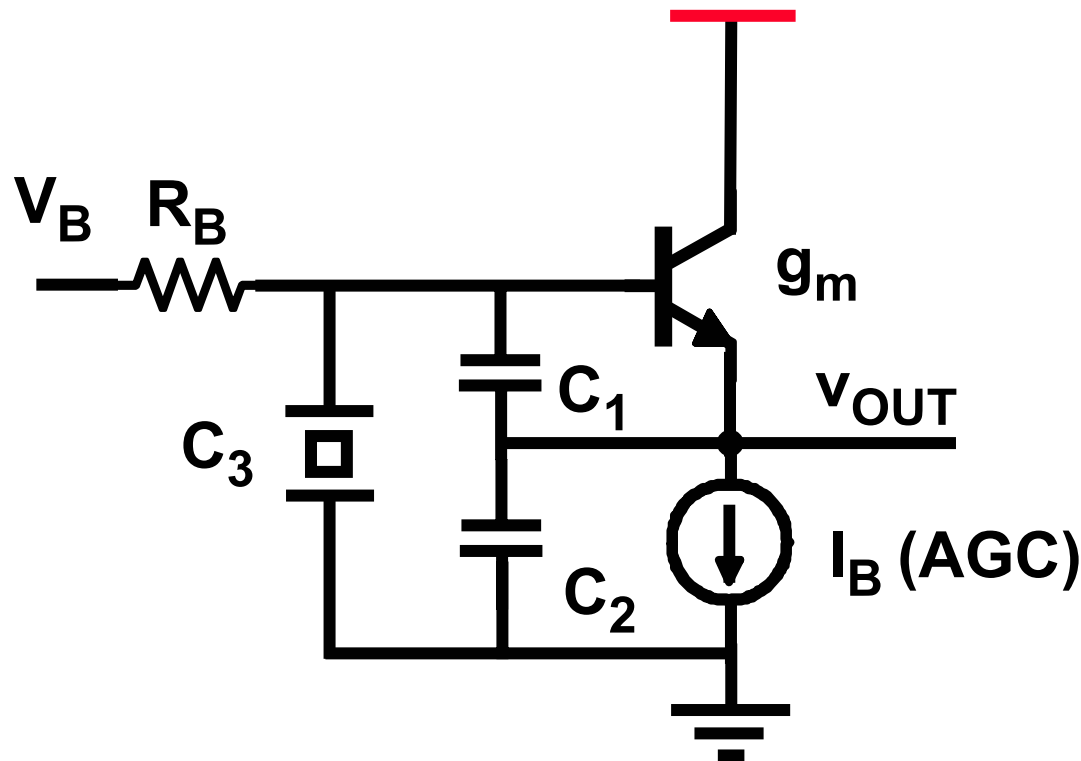



Crystal grounded : single-pin : $X = G$

Buffered output

Ref. Santos, JSSC April 84, 228-236


Ref. Redman-White, JSSC Feb.90, 282-288

98 GHz VCO in SiGe Bipolar technology

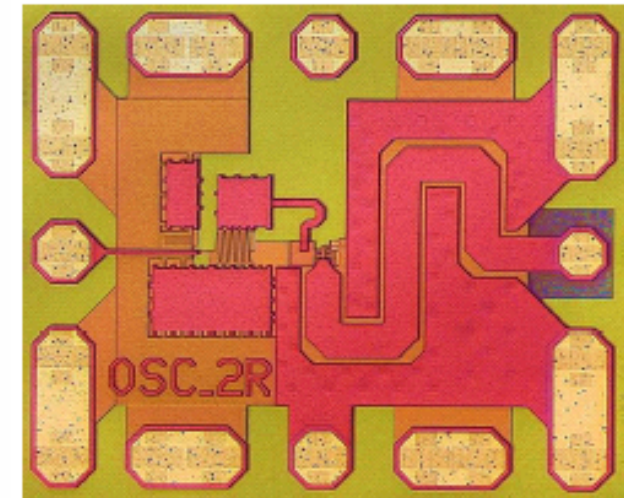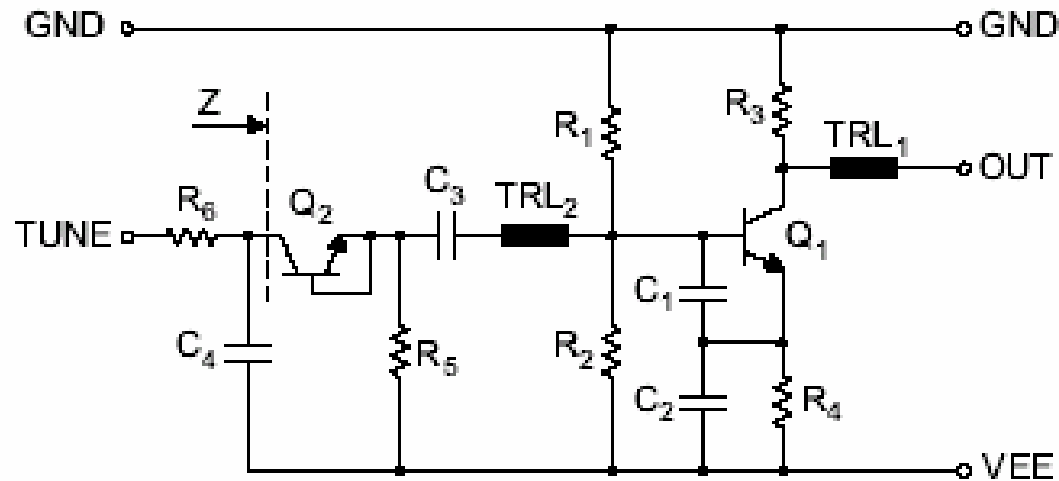

Colpitts


0.55 x 0.45 mm

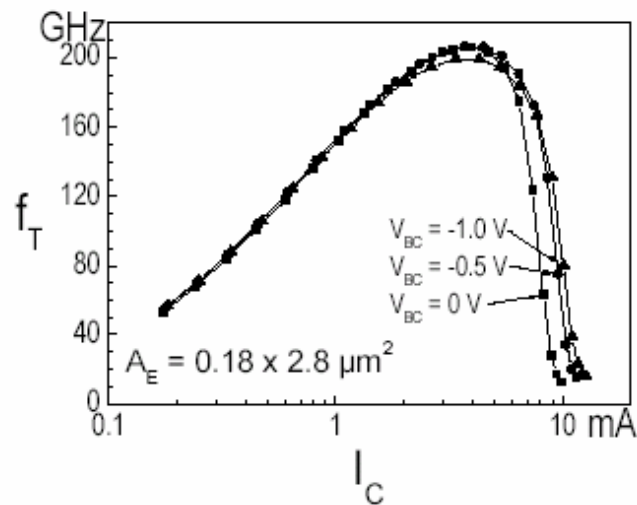

12 mA at - 5 V
-97 dBc/Hz at 1 MHz

Ref. Prendl BCTM Toulouse 03


Positive feedback circuits - 1

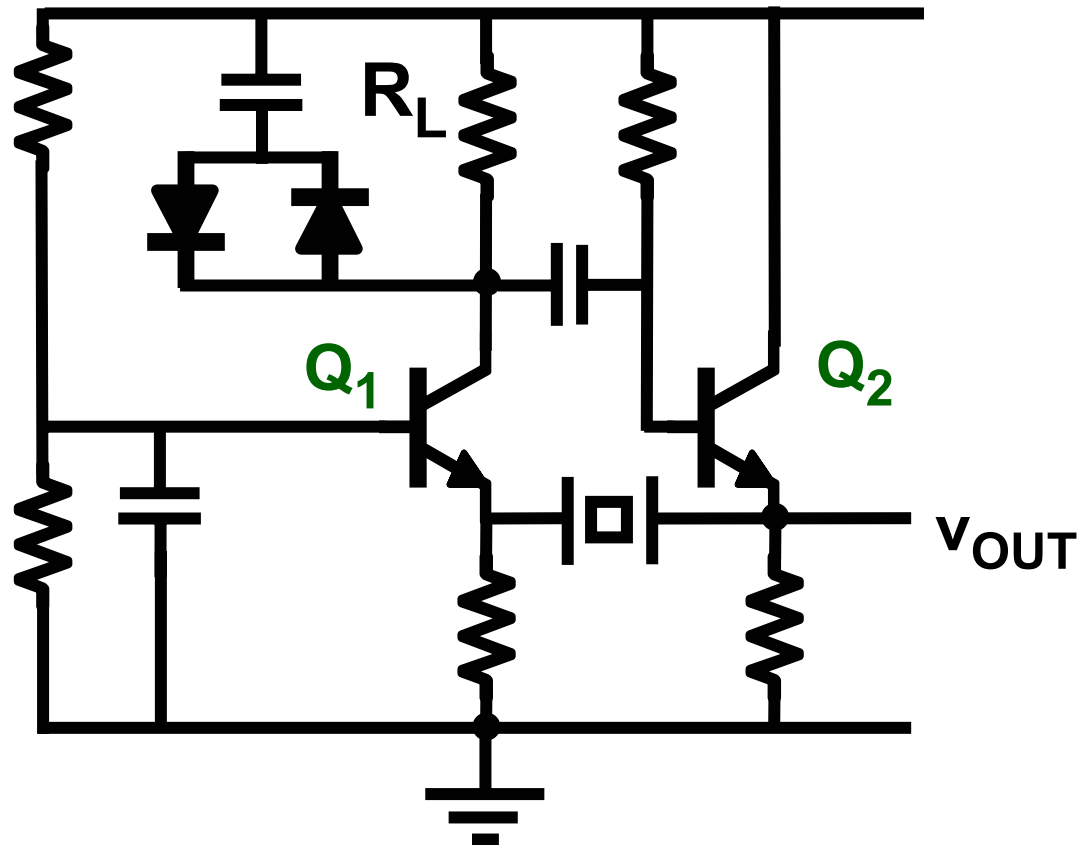

$$T = g_{m1} R_L$$
$$R_L > R_s$$

Ref. Nordholt, CAS 90, 175-182


Positive feedback circuits - 2

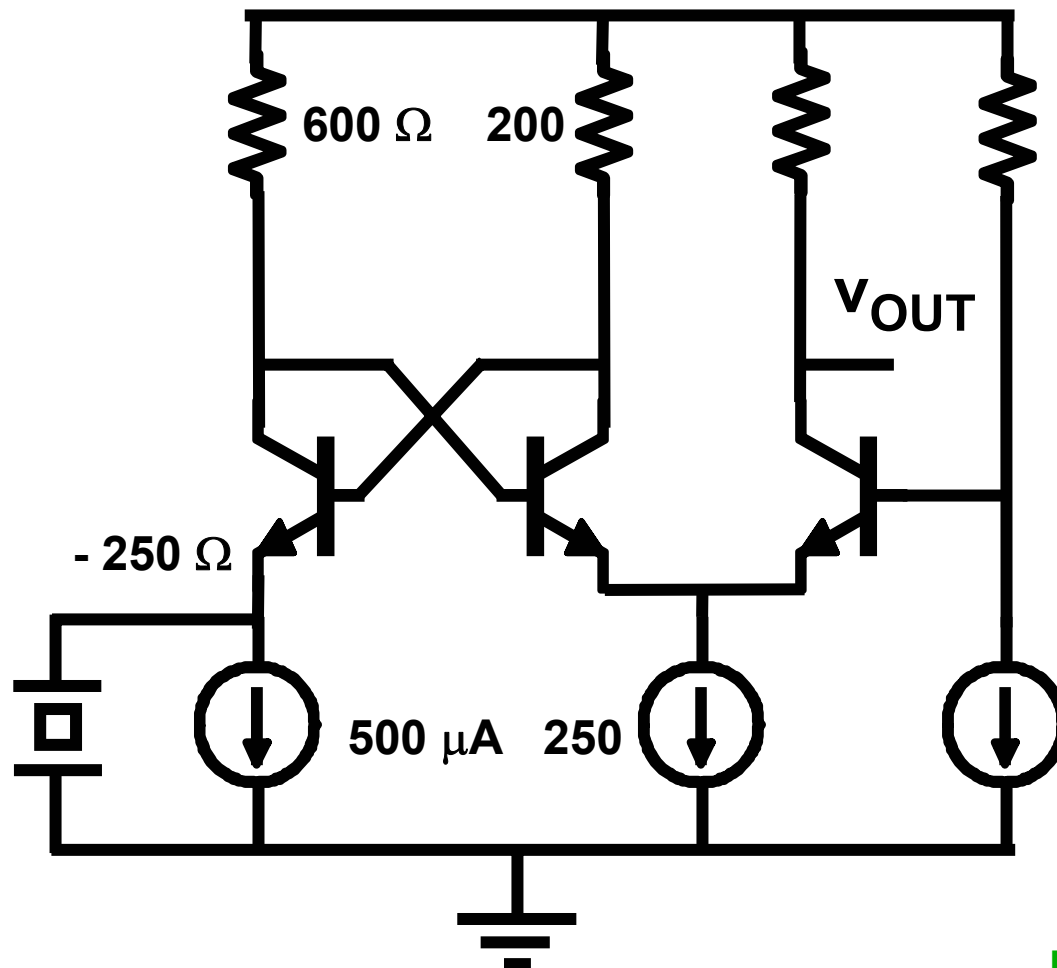

Buffered output !

Ref. Nordholt, CAS 90, 175-182

Positive feedback circuits - 3

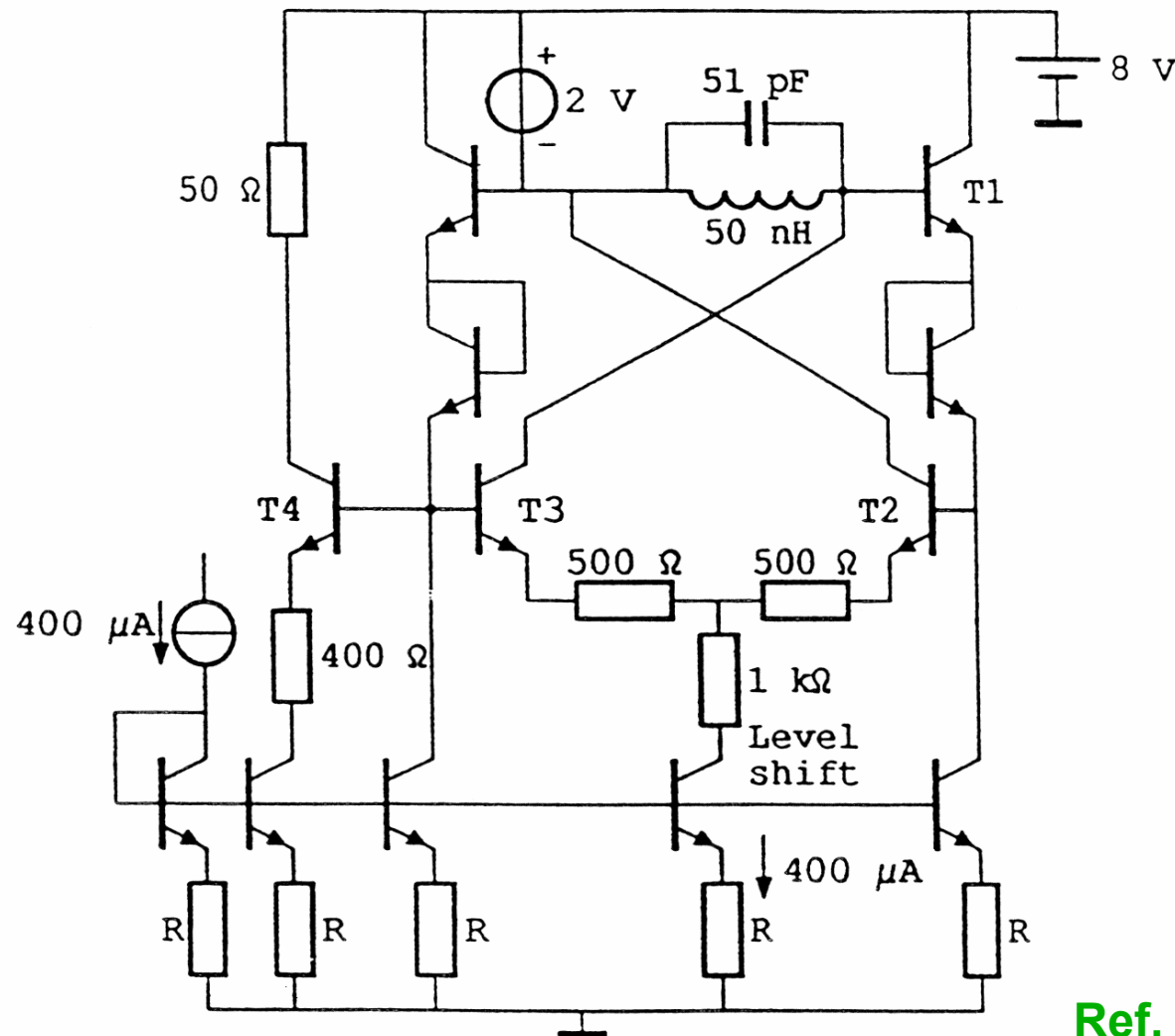

$$g_{mA} = 8 \text{ mS}$$


100 MHz

Ref. Nordholt, CAS 90, 175-182

Table of contents

- ◆ **Oscillation principles**
- ◆ **Crystals**
- ◆ **Single-transistor oscillator**
- ◆ **MOST oscillator circuits**
- ◆ **Bipolar-transistor oscillator circuits**
- ◆ **Other oscillators**

Voltage Controlled Oscillator

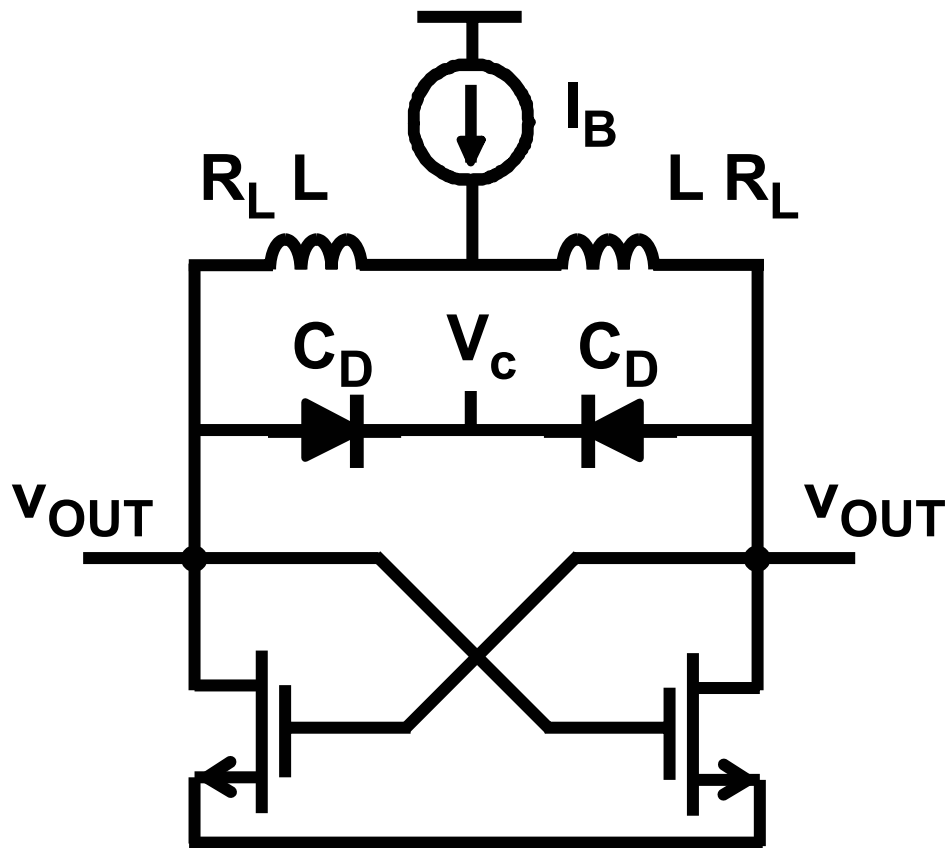


$$\omega_s = \frac{1}{\sqrt{LC_D}}$$

$$g_{mA} \approx R_L (C_D \omega_s)^2$$


$$\overline{dv_{out}^2 \{\Delta\omega\}} = 4kTR_L \left(1 + \frac{4}{3}\right) \left(\frac{\omega_s}{\Delta\omega}\right)^2 df$$

Ref. Craninckx, ACD Kluwer 96, 383-400 ; JSSC May 97, 736-744

Differential crystal Oscillator

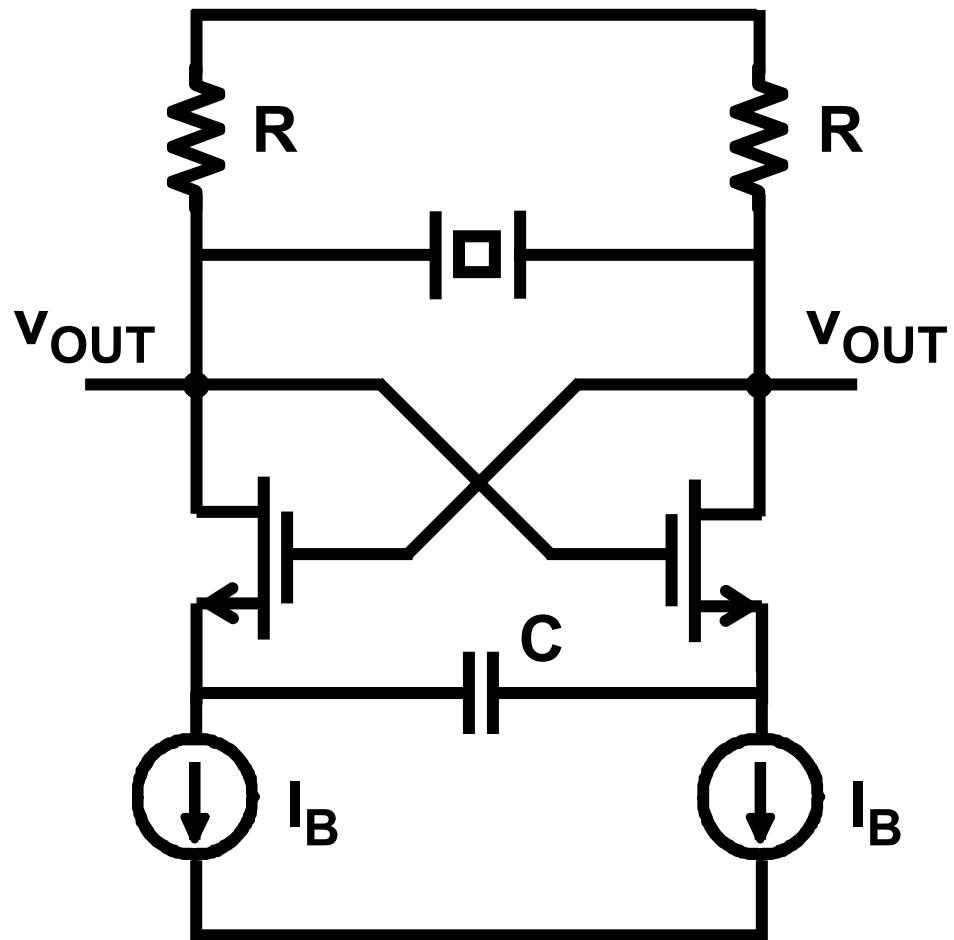


Relaxation Oscillator

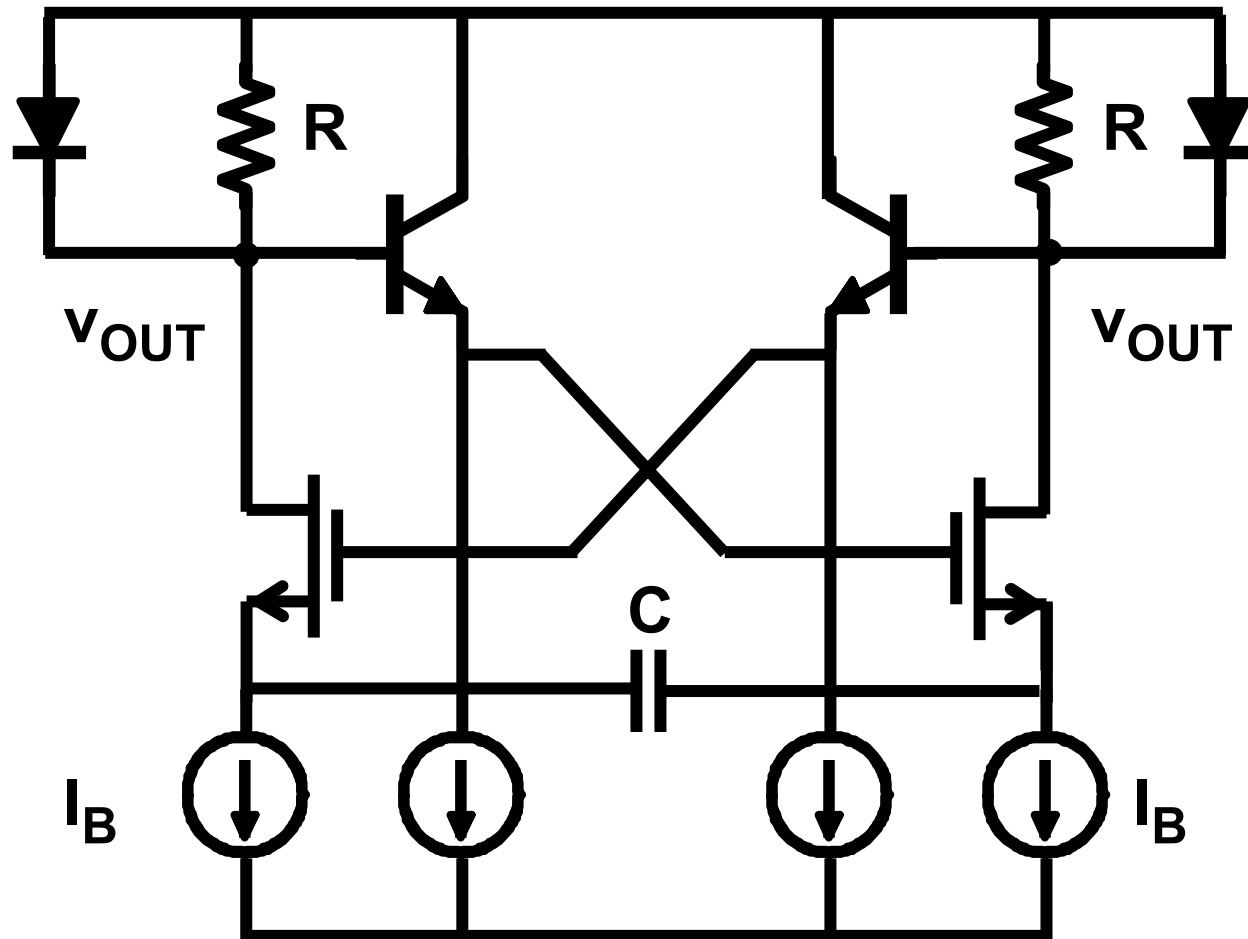


Ref. Grebene, JSSC, Aug.69, 110-122; Gray, Meyer, Wiley, 1984.

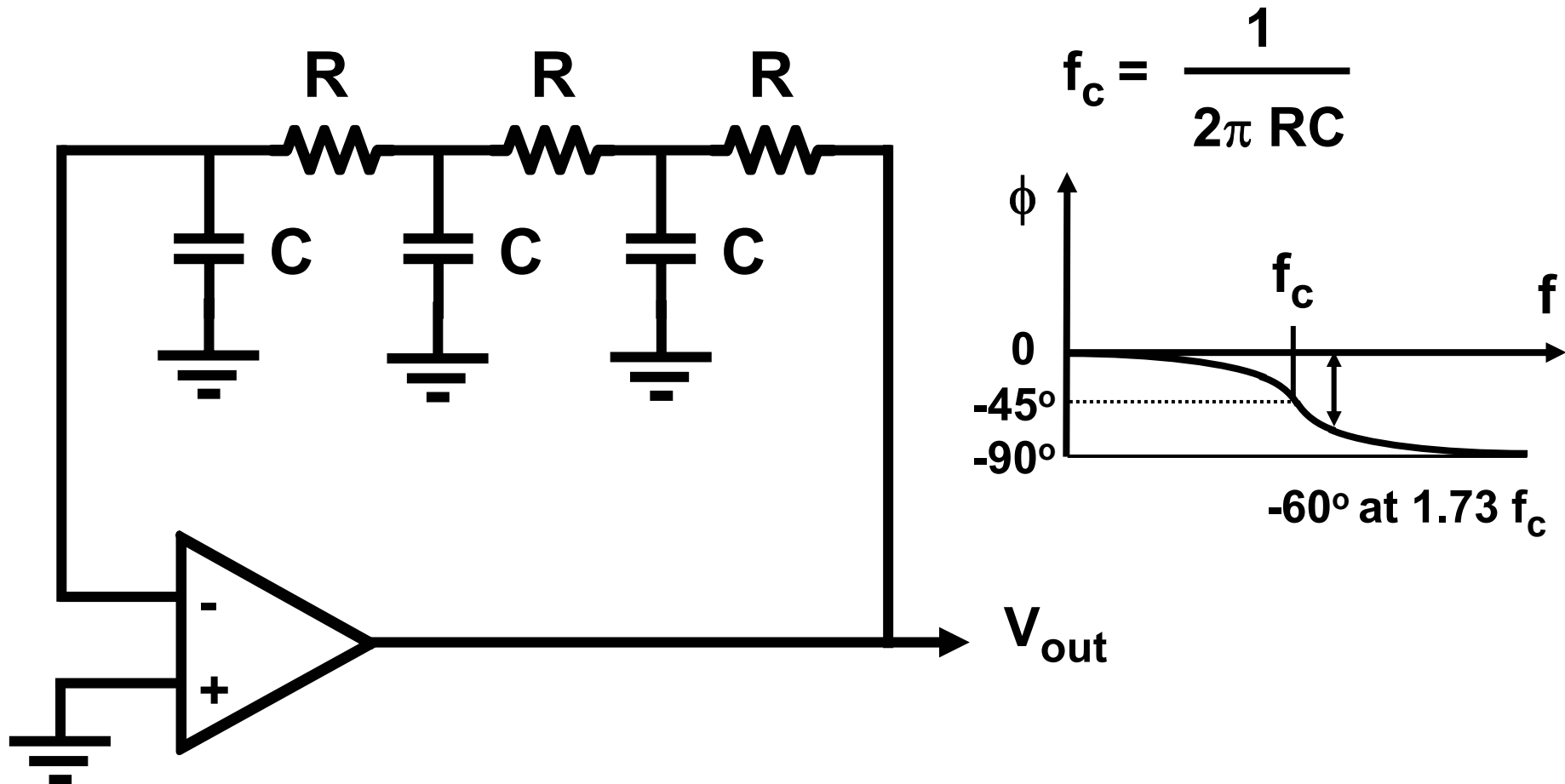RC Oscillators : $3 \times 60^\circ = 180^\circ$




Wien Oscillator : 3 x Gain required

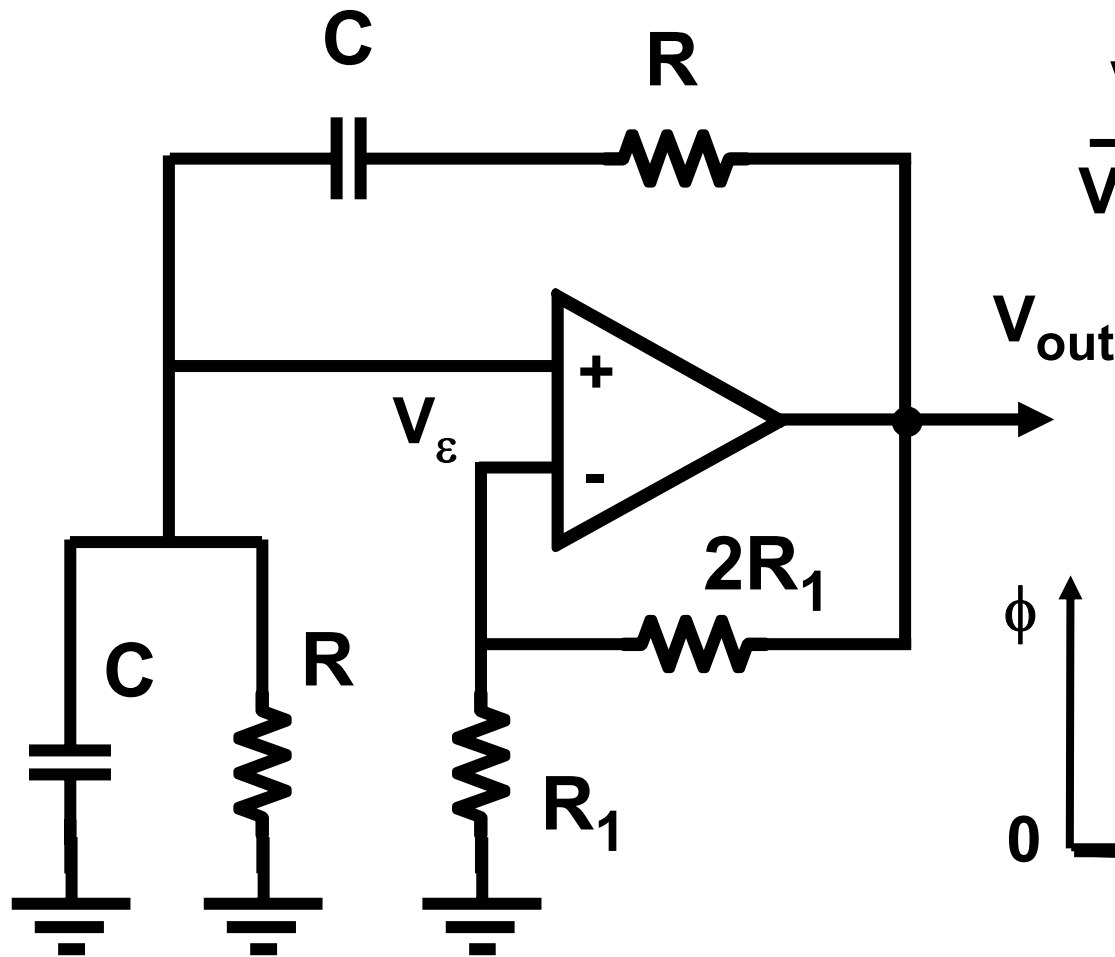


$$\frac{V_{\varepsilon}}{V_{out}} = \frac{1}{3} \frac{1 + 2\tau s + \tau^2 s^2}{1 + 3\tau s + \tau^2 s^2}$$

$$\tau = RC$$

$$f_{osc} = \frac{1}{2\pi \tau}$$

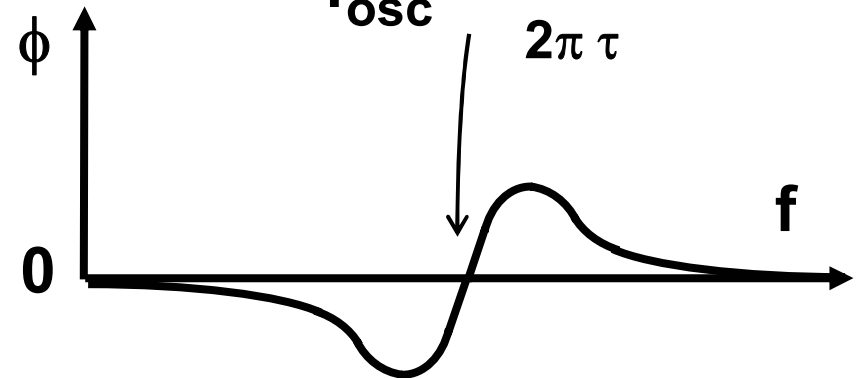


Voltage-controlled X-tal oscillator

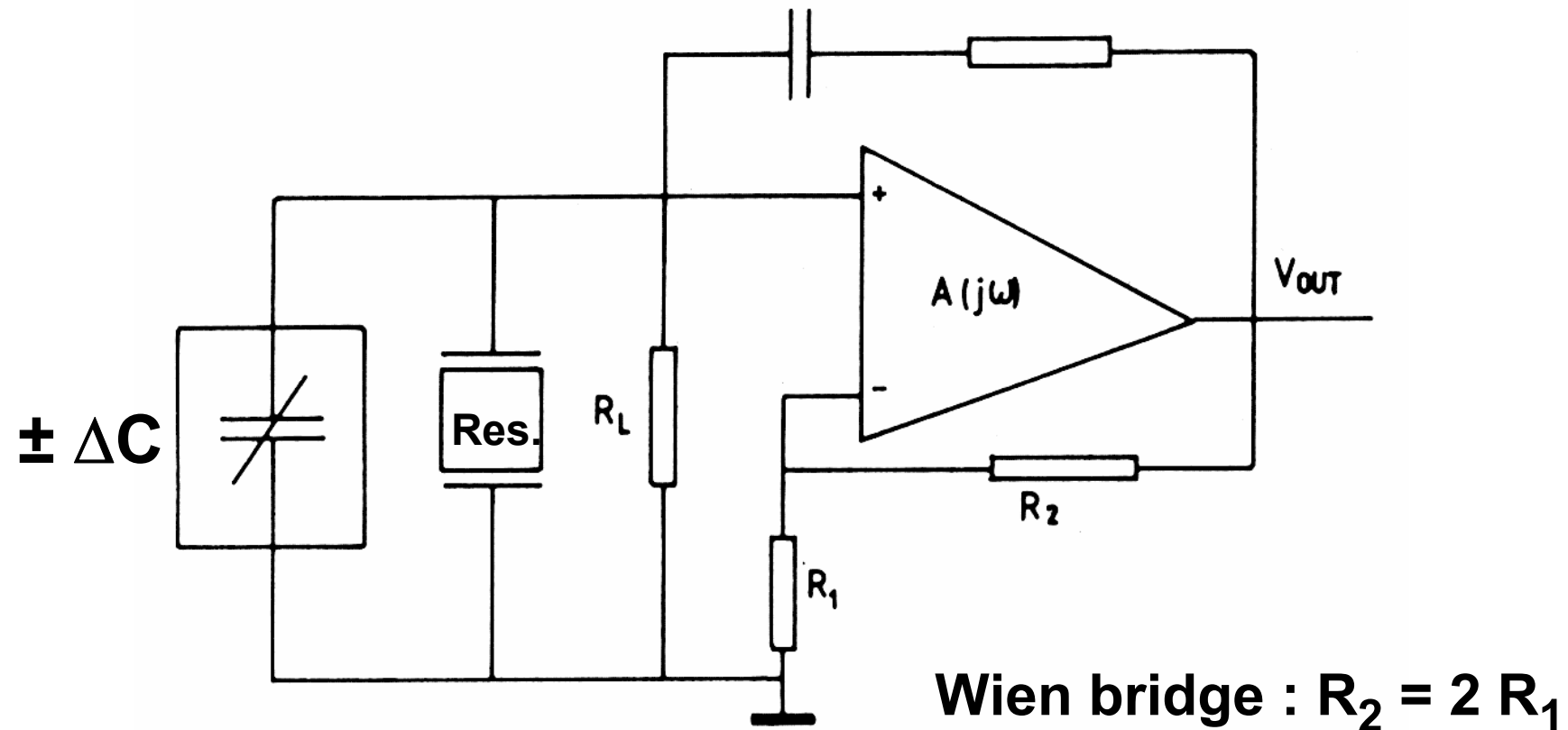

Resonator 457 kHz
Tuning ± 5 kHz


Ref. Huang, JSSC June 88, 784-793

Variable capacitance $\pm \Delta C$

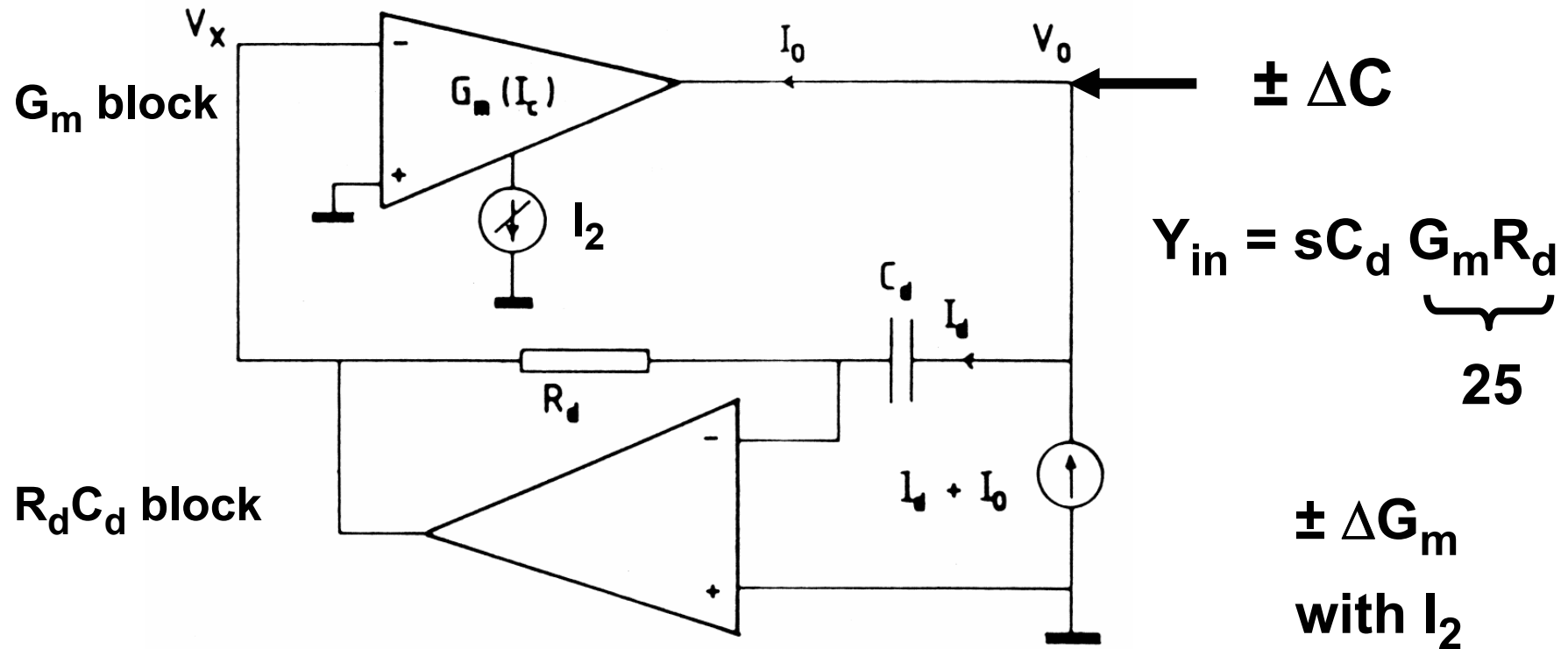

Ref. Huang JSSC June 88, 784-793

G_m block to generate $\pm \Delta G_m$

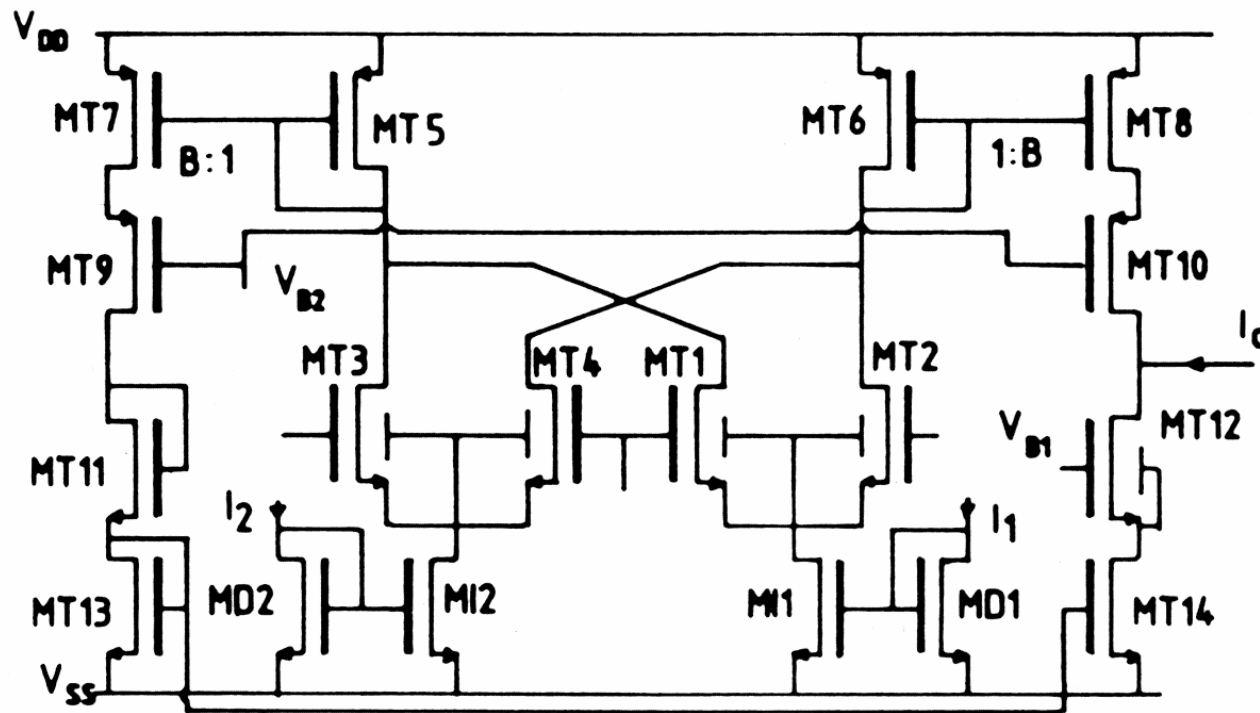


$$I_1 = 90 \mu\text{A}$$

$$I_2 = 0 \dots 180 \mu\text{A}$$

$$G_m = B [(2\beta I_1)^{1/2} - (2\beta I_2)^{1/2}]$$

$R_d C_d$ block as differentiator

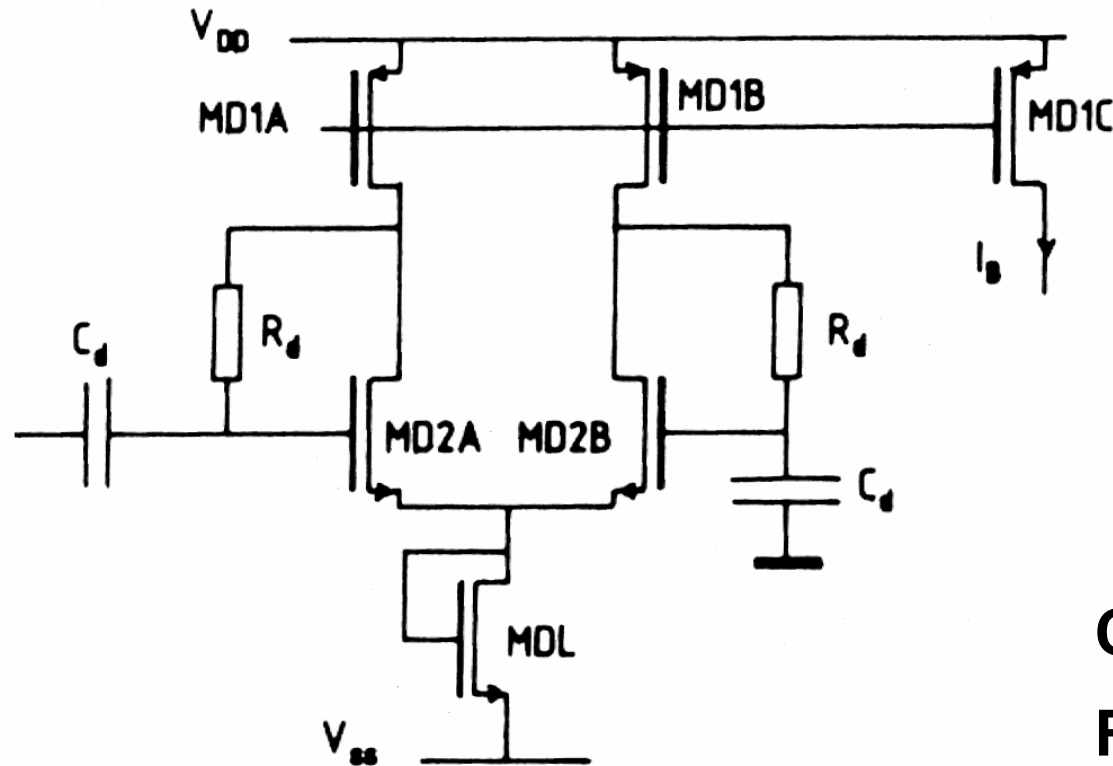

$$C_d = 4 \text{ pF}$$

$$R_d = 40 \text{ k}\Omega$$

Ref. Huang JSSC June 88, 784-793

Table of contents

- ◆ **Oscillation principles**
- ◆ **Crystals**
- ◆ **Single-transistor oscillator**
- ◆ **MOST oscillator circuits**
- ◆ **Bipolar-transistor oscillator circuits**
- ◆ **Other oscillators**

References X-tal oscillators -1

A.Abidi, "Low-noise oscillators, PLL's and synthesizers", in R. van de Plassche, W.Sansen, H. Huijsing, "Analog Circuit Design", Kluwer Academic Publishers, 1997.

J. Craninckx, M. Steyaert, "Low-phase-noise gigahertz voltage-controlled oscillators in CMOS", in H. Huijsing, R. van de Plassche, W.Sansen, "Analog Circuit Design", Kluwer Academic Publishers, 1996, pp. 383-400.

Q.T. Huang, W. Sansen, M. Steyaert, P.Van Peteghem, "Design and implementation of a CMOS VCXO for FM stereo decoders", IEEE Journal Solid-State Circuits Vol. 23, No.3, June 1988, pp. 784-793.

E. Nordholt, C. Boon, "Single-pin crystal oscillators" IEEE Trans. Circuits. Syst. Vol.37, No.2, Feb.1990, pp.175-182.

D. Pederson, K.Mayaram, "Analog integrated circuits for communications", Kluwer Academic Publishers, 1991.

References X-tal oscillators - 2

W. Redman-White, R. Dunn, R. Lucas, P. Smithers, "A radiation hard AGC stabilised SOS crystal oscillator", IEEE Journal Solid-State Circuits Vol. 25, No.1, Feb. 1990, pp. 282-288.

J. Santos, R. Meyer, "A one pin crystal oscillator for VLSI circuits", IEEE Journal Solid-State Circuits Vol. 19, No.2, April 1984, pp. 228-236.

M. Soyer, "Design considerations for high-frequency crystal oscillators", IEEE Journal Solid-State Circuits Vol. 26, No.9, June 1991, pp. 889-893.

E. Vittoz, M. Degrauwe, S. Bitz, "High-performance crystal oscillator circuits: Theory and application", IEEE Journal Solid-State Circuits Vol. 23, No.3, June 1988, pp. 774-783.


V. von Kaenel, E. Vittoz, D. Aebischer, " Crystal oscillators", in H. Huijsing, R. van de Plassche, W.Sansen, "Analog Circuit Design", Kluwer Academic Publishers, 1996, pp. 369-382.

Appendix: Polar diagrams

Willy Sansen

willy.sansen@esat.kuleuven.be

Amplitude, phase, Real & Imaginary

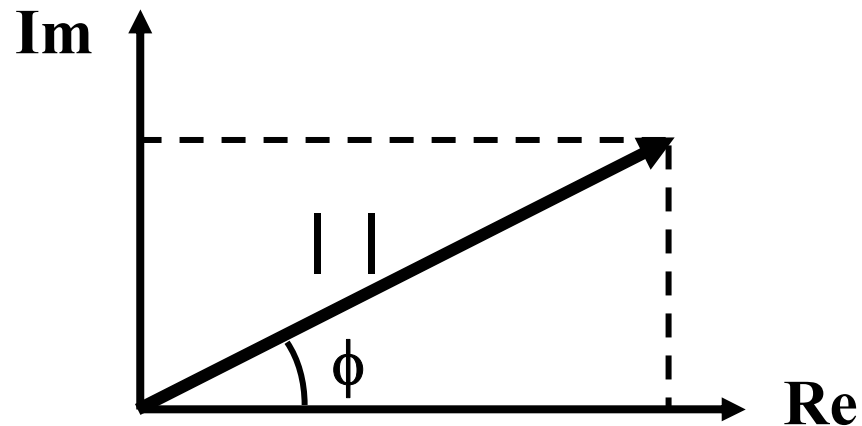



$$| | = \sqrt{\text{Re}^2 + \text{Im}^2}$$

$$\text{tg}(\phi) = \frac{\text{Im}}{\text{Re}}$$


$$\text{Re} = | | \cos(\phi)$$

$$\text{Im} = | | \sin(\phi)$$



Polar diagram of RC network - 1

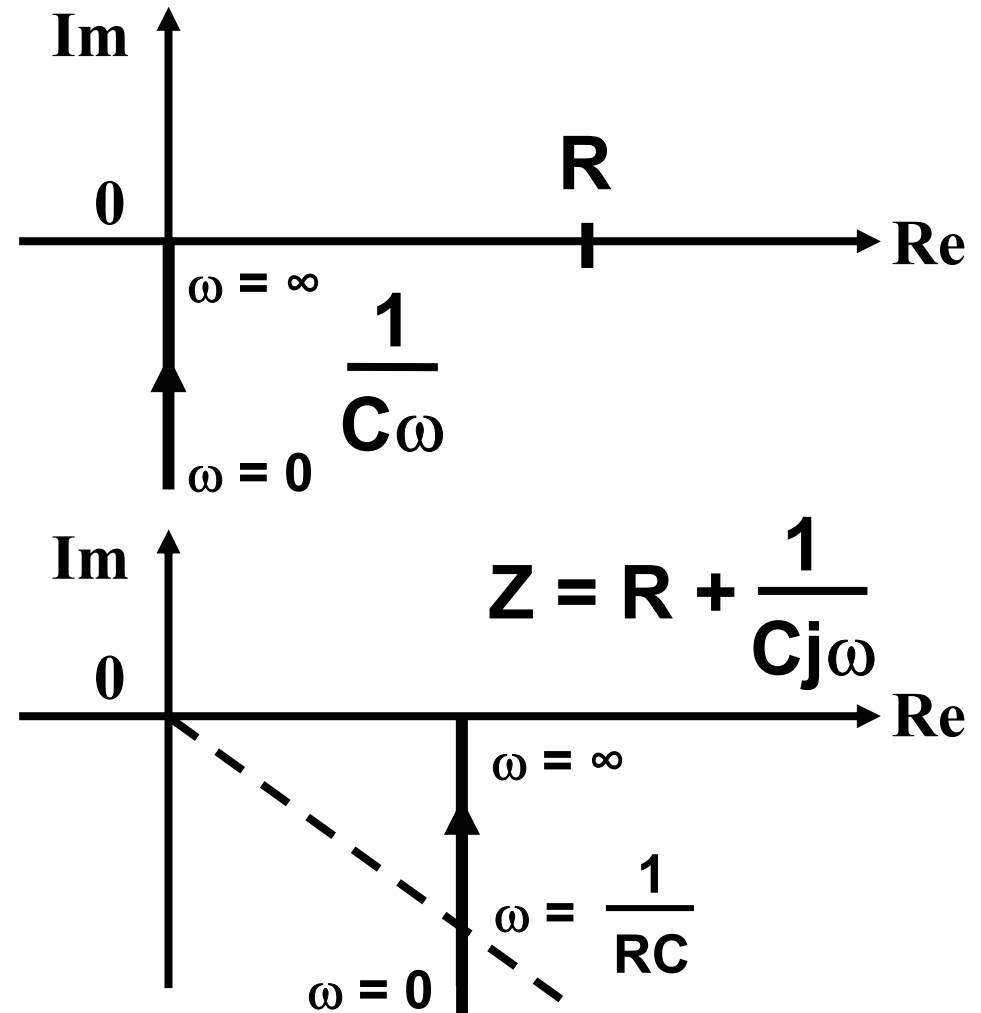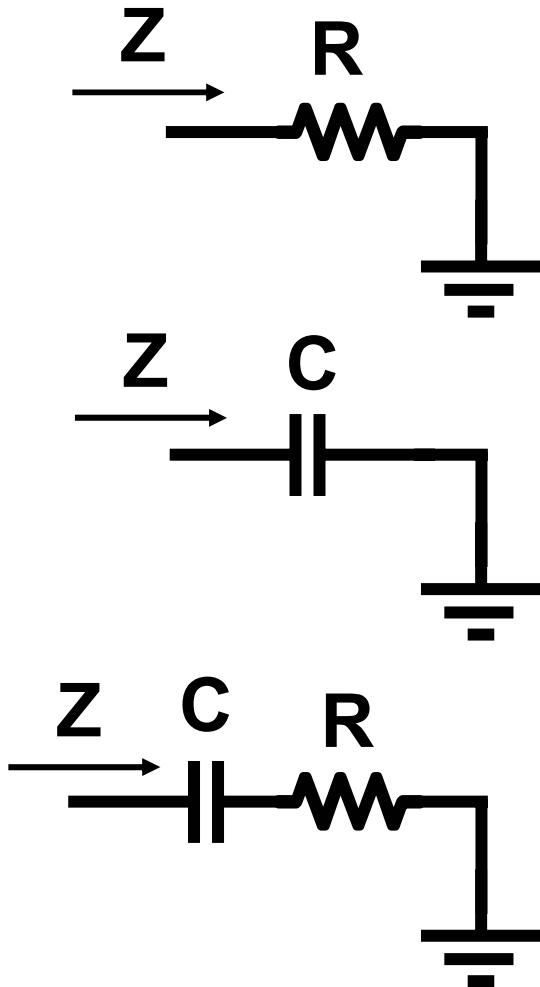


Polar diagram of RC network - 2

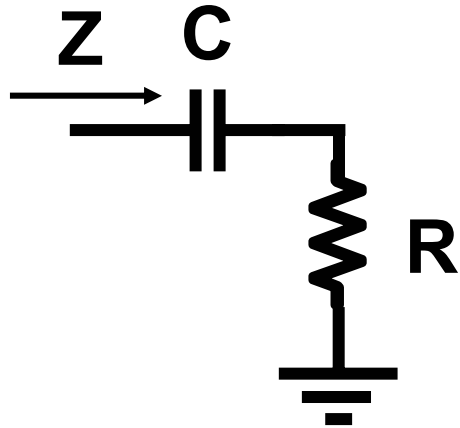


$$Z = R + \frac{1}{Cj\omega}$$

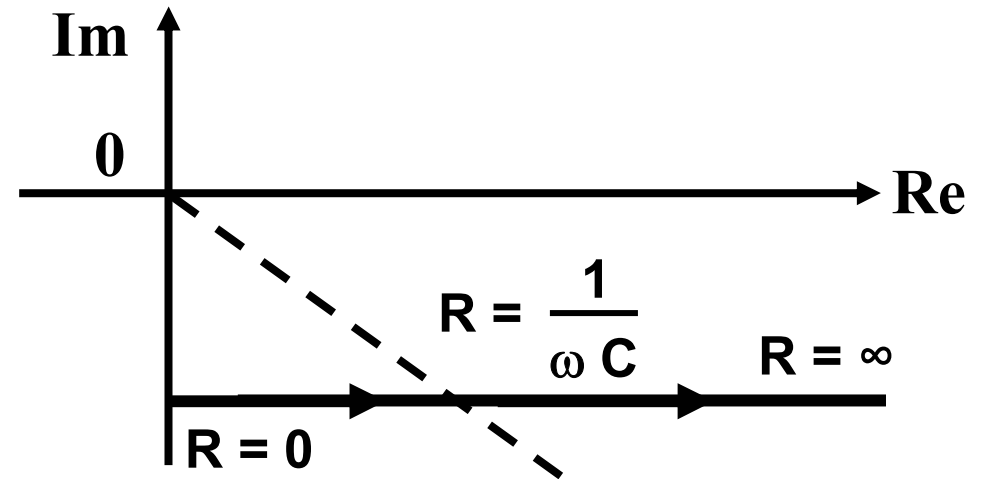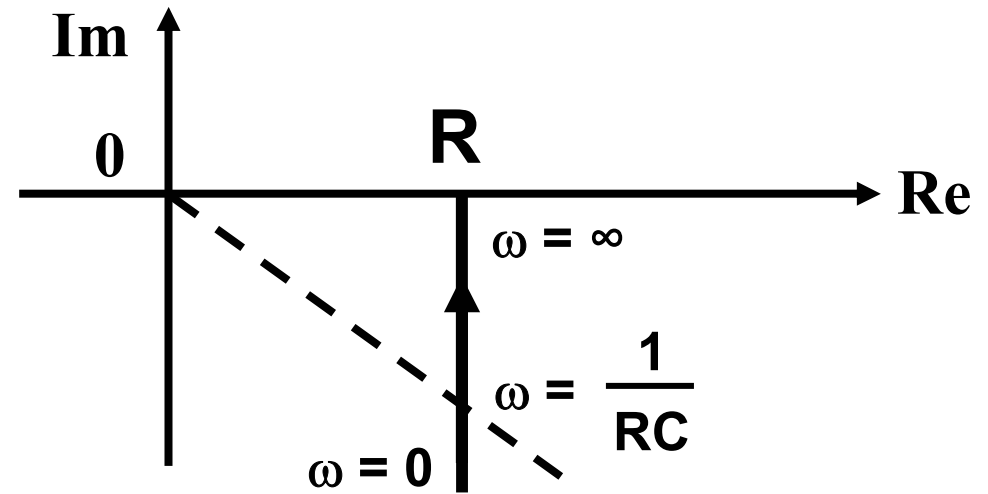


Polar diagram of RC network - 3

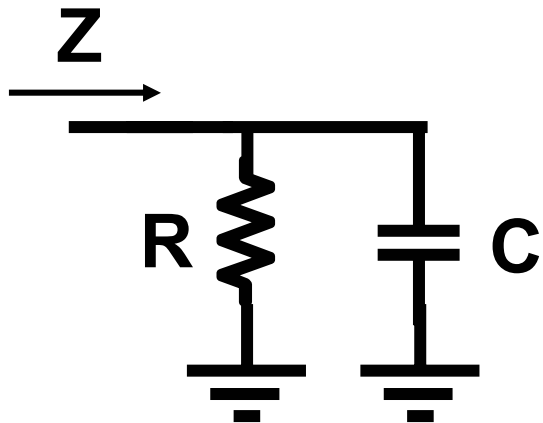

$$Z = \frac{R}{1 + RCj\omega}$$




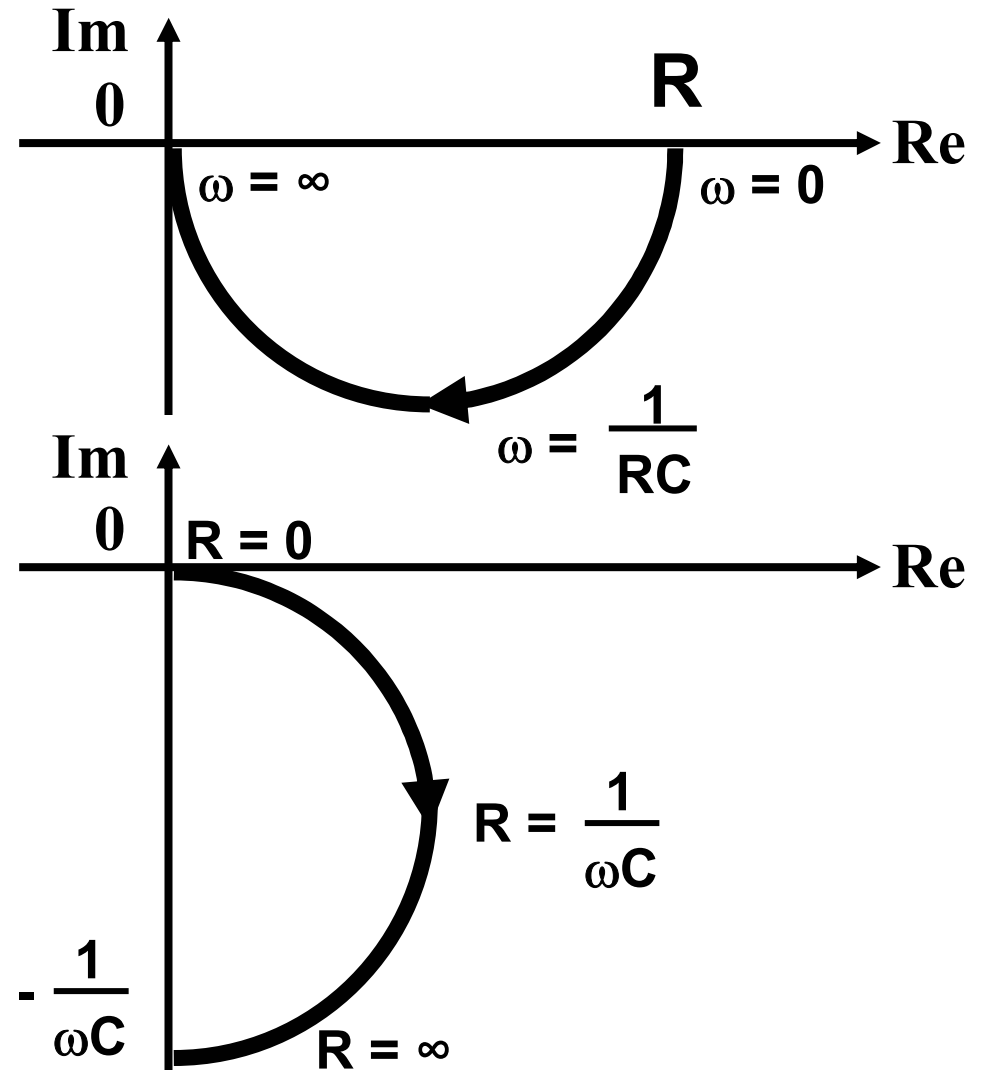


Polar diagram of RC network - 4

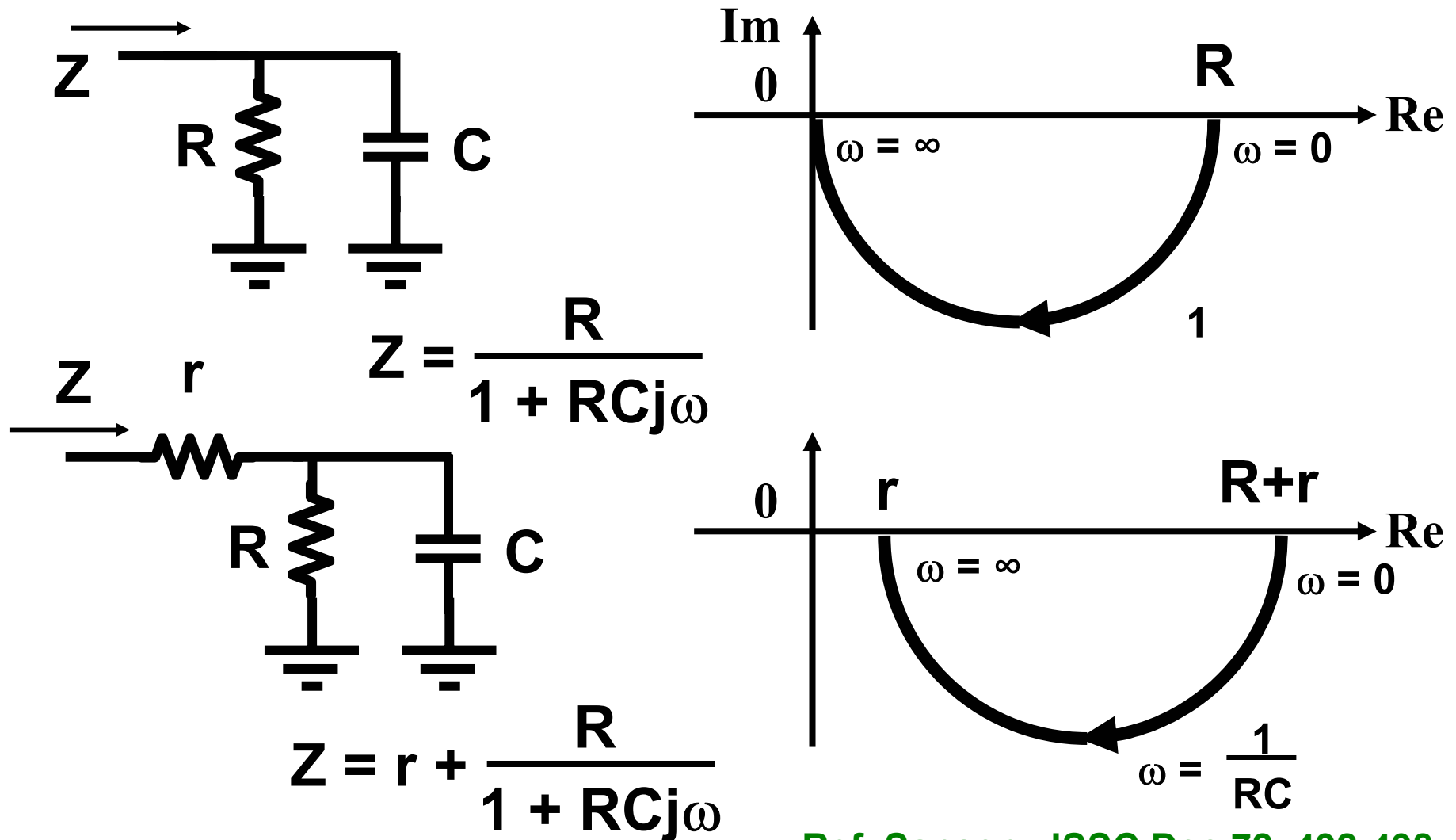

Ref. Sansen, JSSC Dec.72, 492-498

Polar diagram of RC network - 5

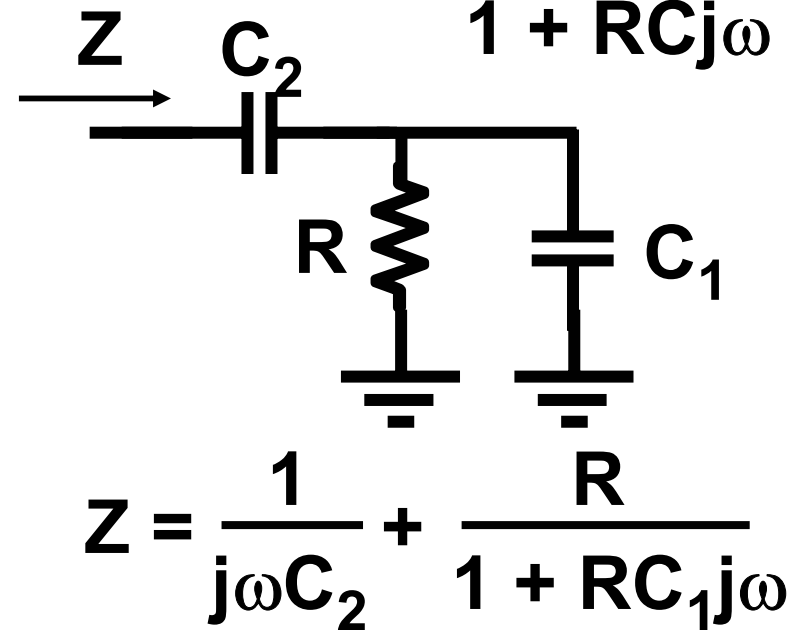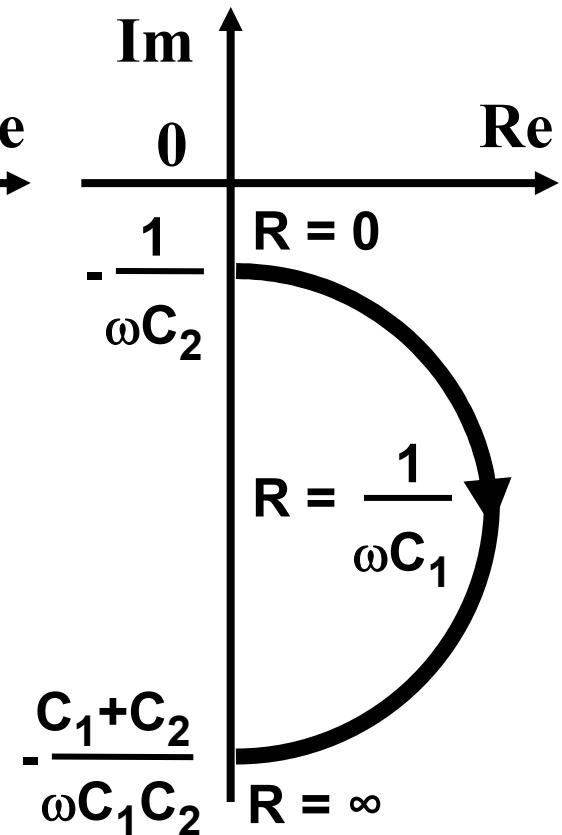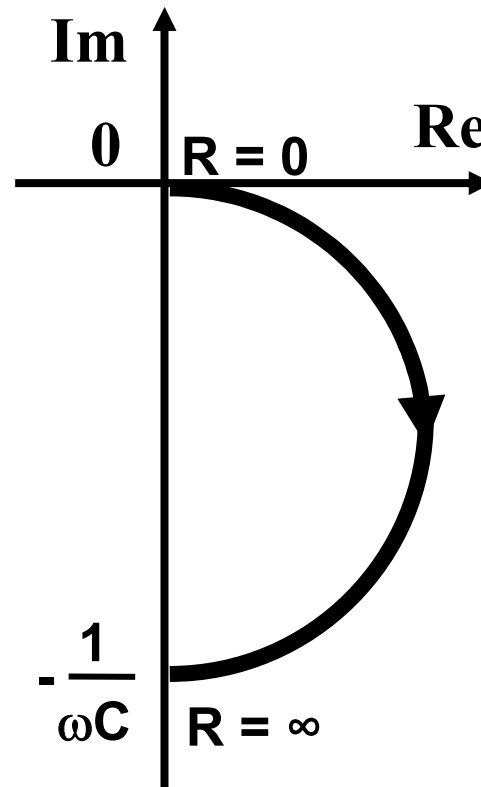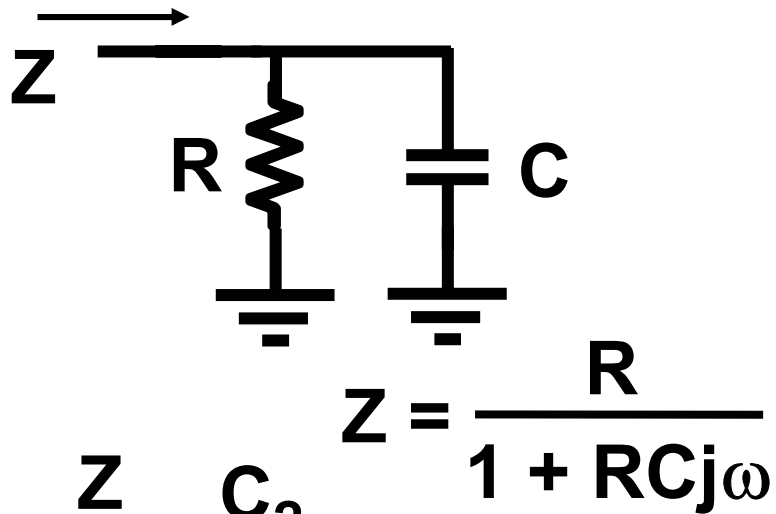


Circuit input impedance Z_c

$$Z_c \approx \frac{g_m + 2j\omega C_1}{j\omega C_3 \left(g_m + \frac{C_1}{C_3} j\omega C_1 \right)}$$


if $C_3 \ll C_1 = C_2$

For $g_m \approx 0$ $Z_{c0} \approx 2 / j\omega C_1$

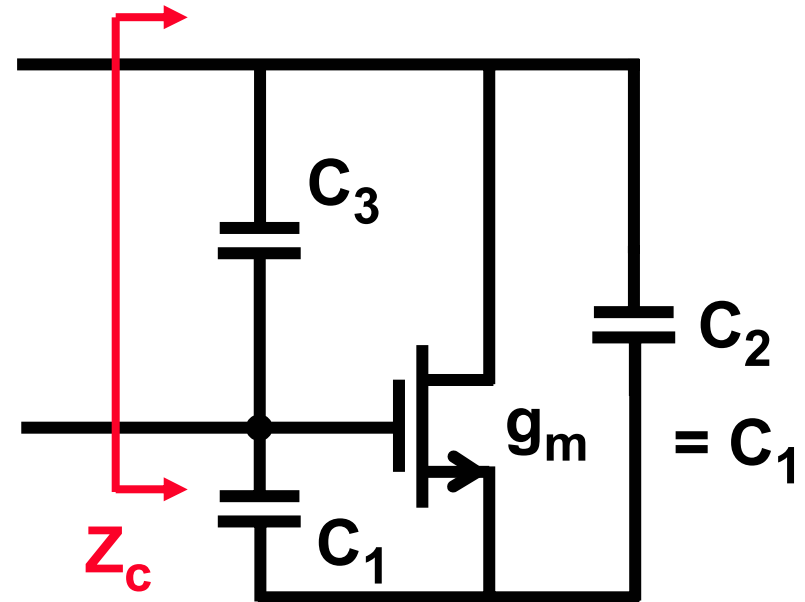
For $g_m \approx \infty$ $Z_{c\infty} \approx 1 / j\omega C_3$



Complex plane for 3-point oscillator

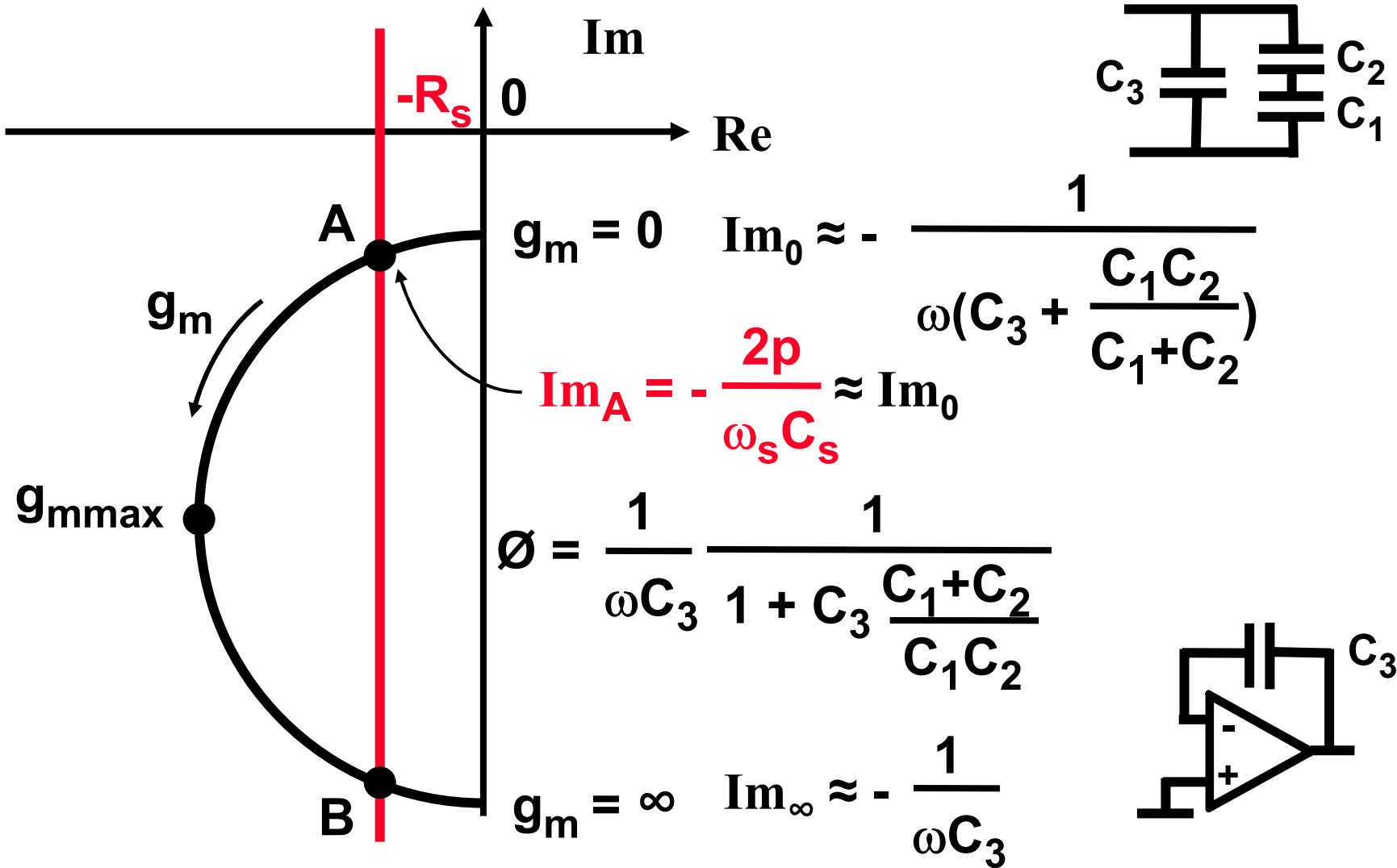

Calculation of g_{mA}

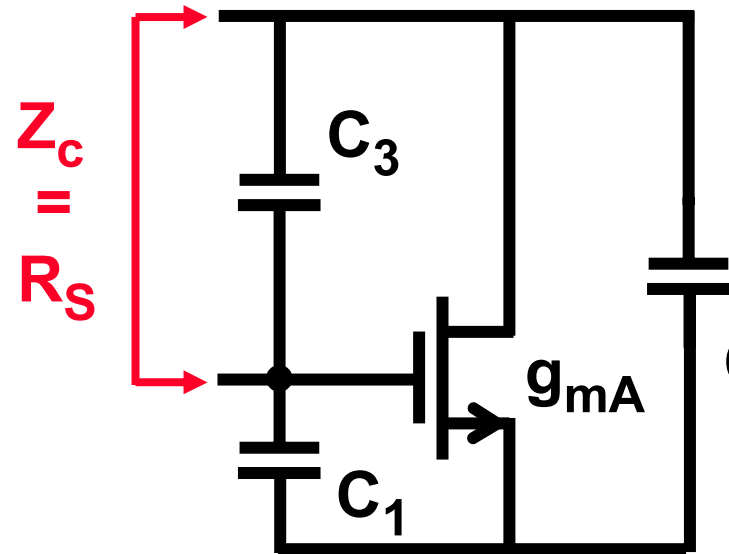

$$Z_c = \frac{1}{C_3 s} \frac{g_m + (C_1 + C_2)s}{g_m + (C_1 + C_2 + \frac{C_1 C_2}{C_3})s}$$

$$\text{Re}(Z_c) = R_s$$

For small g_m :

$$g_{mA} \approx R_s (C_{\text{eff}} \omega_s)^2$$

$$C_{\text{eff}} = C_1 \left(1 + \frac{2C_3}{C_1}\right) \approx C_1$$

Maximum negative resistance is $1/2\omega C_3$ at $g_{m\text{max}} = \frac{C_1}{C_3} \omega C_1$