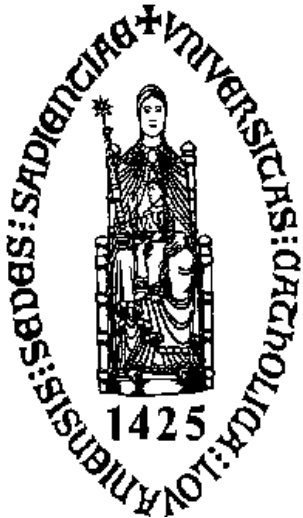

Feedback Voltage & Transconductance Amplifiers



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be

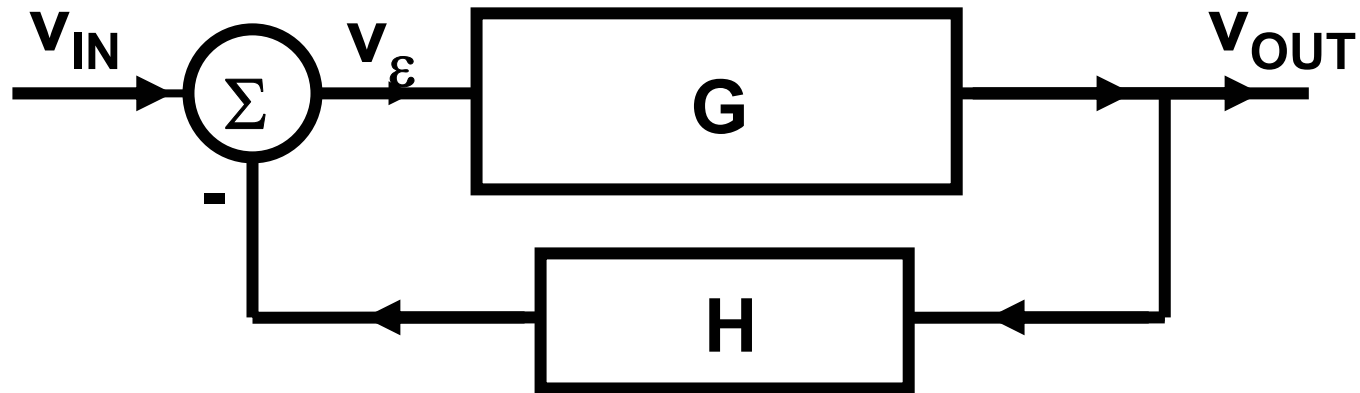


Table of contents

◆ Definitions

- ◆ Series-shunt FB for Voltage amplifiers.
- ◆ Series-series FB for Transconductance amps.

Ideal feedback




$$\left. \begin{aligned} V_{\epsilon} &= V_{IN} - H V_{OUT} \\ V_{OUT} &= G V_{\epsilon} \end{aligned} \right\} \quad \frac{V_{OUT}}{V_{IN}} = \frac{G}{1 + GH} \approx \frac{1}{H}$$

if the loop gain $LG = GH \gg 1$

Gray, Hurst, Lewis, Meyer: Design of analog integrated circuits, Wiley 2001

Shunt-shunt feedback configurations

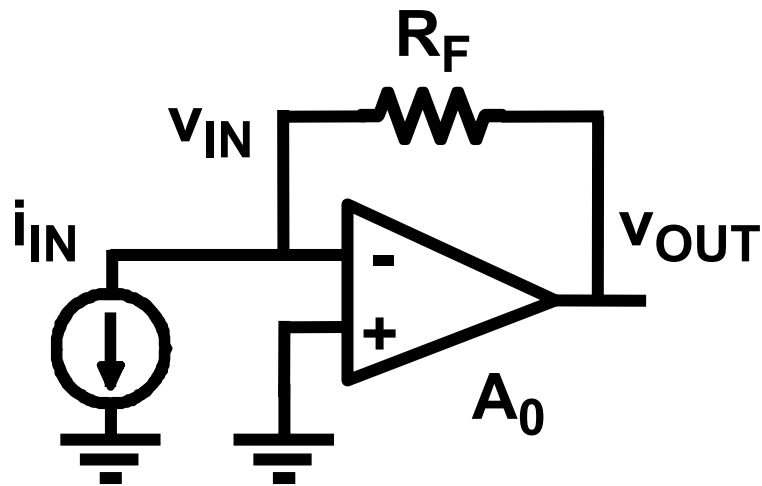

$$LG = \frac{V_{OUT}}{V_{IN}} = A_{vOL} = A_0$$

$$A_0 \approx 10^4 \dots 10^6$$

OL Open Loop

$$A_R = R_F$$


$$R_{IN} \approx 0$$

IN : shunt FB : $R_{IN} \Downarrow$
OUT : shunt FB : $R_{OUT} \Downarrow$

$$\text{Input shunt : } R_{IN} = \frac{R_{INOL}}{1+LG}$$

$$\text{Output shunt : } R_{OUT} = \frac{R_{OUTOL}}{1+LG}$$

Calculation loop gain or return ratio

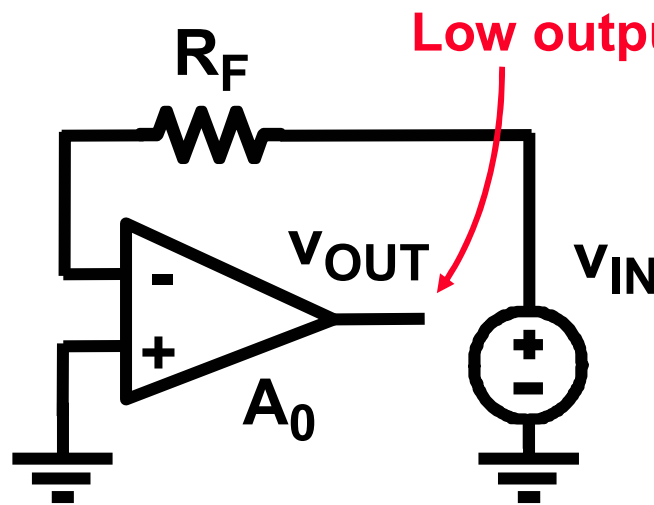

$$LG = \frac{V_{OUT}}{V_{IN}} = A_{VOL} = A_0$$


$$A_0 \approx 10^4 \dots 10^6$$

OL Open Loop

Independent sources : voltage source to zero
current source to infinity

Break loop where impedances are very different
Find the loop gain = return ratio

Calculation loop gain - alternate

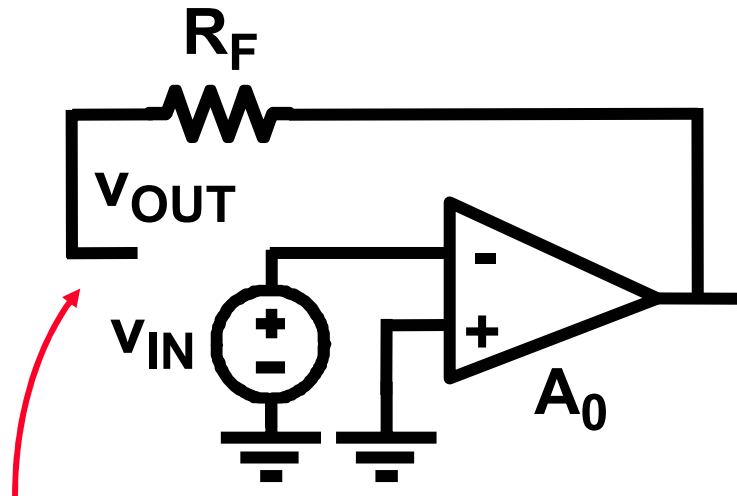


Ideal separation!

$$LG = \frac{V_{OUT}}{V_{IN}} = A_{vOL} = A_0$$

$$A_0 \approx 10^4 \dots 10^6$$

OL Open Loop


Shunt-shunt FB pair in CMOS

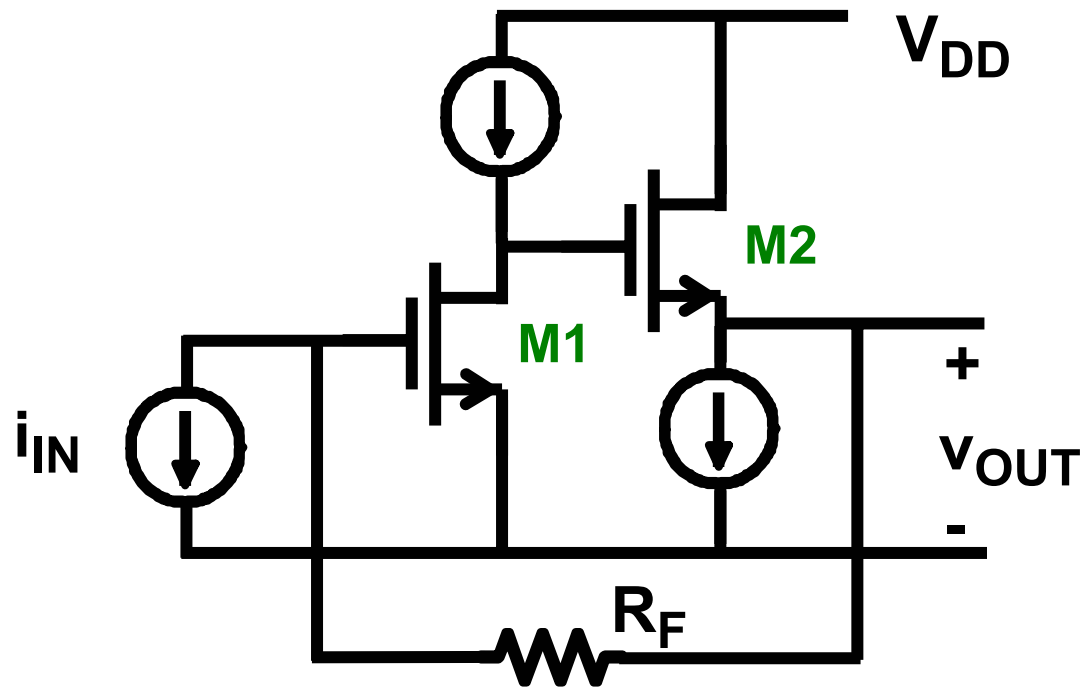

$$A_R = R_F$$

$$LG = g_{m1}r_{o1}$$


Shunt-shunt FB pair in bipolar

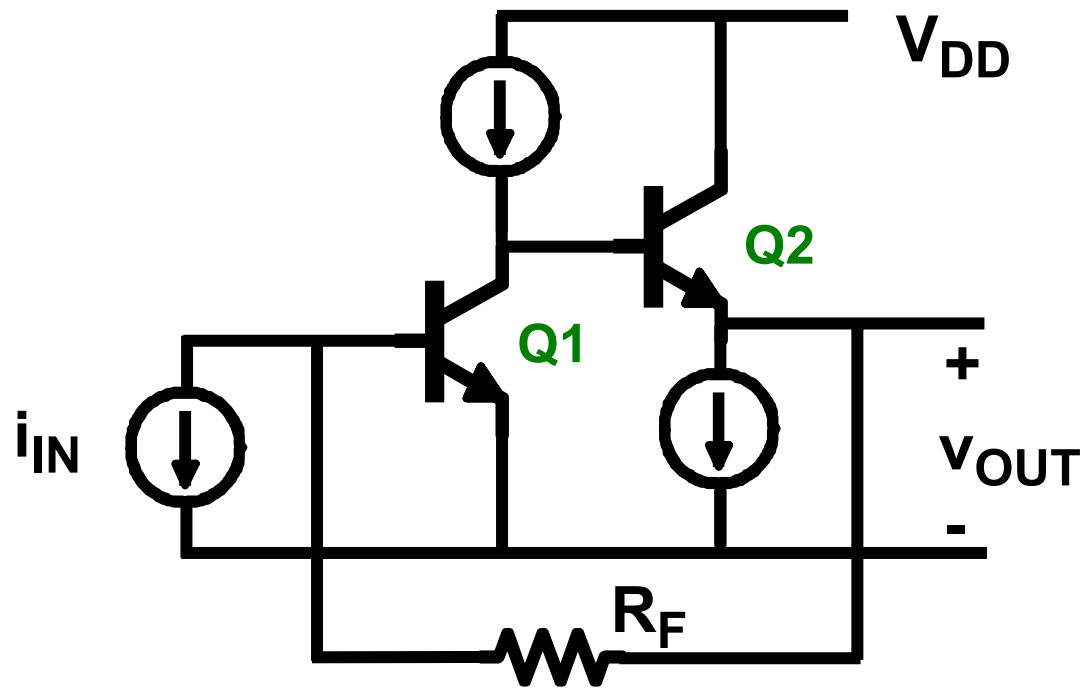

$$A_R = R_F$$

$$LG = g_{m1} r_{o1} \frac{r_{\pi 1}}{R_F + r_{\pi 1}}$$


Loop gain or return ratio

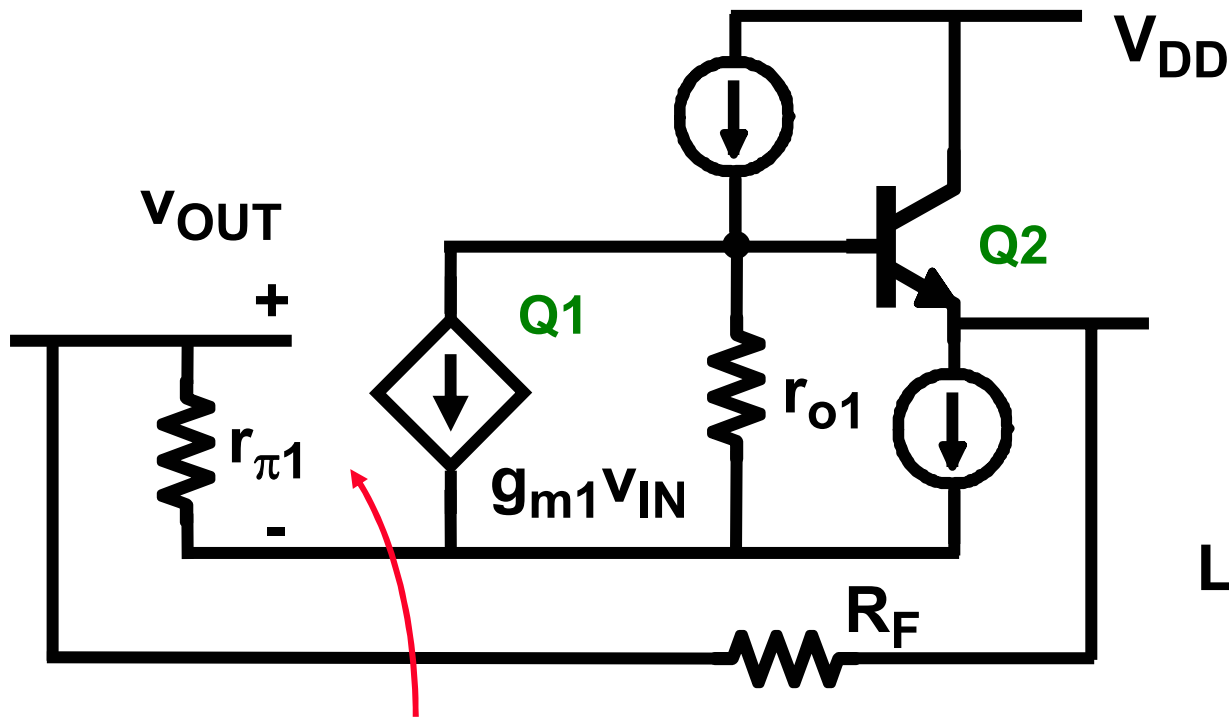

Ideal separation!

$$LG = g_{m1}r_{o1} \frac{r_{\pi 1}}{R_F + r_{\pi 1}}$$


Series-shunt feedback configurations

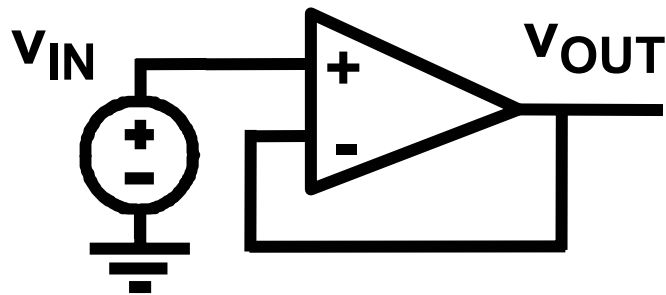

$$A_v = 1$$

$$R_{IN} = \infty$$

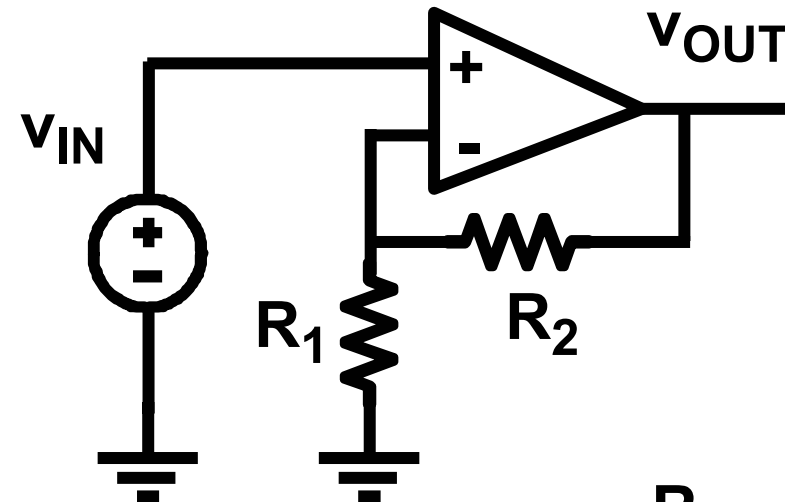IN : series FB : $R_{IN} \uparrow$
OUT : shunt FB : $R_{OUT} \downarrow$




$$A_v = 1 + \frac{R_2}{R_1}$$

$$R_{IN} = \infty$$

IN : series FB : $R_{IN} \uparrow$
OUT : shunt FB : $R_{OUT} \downarrow$

Calculation loop gain

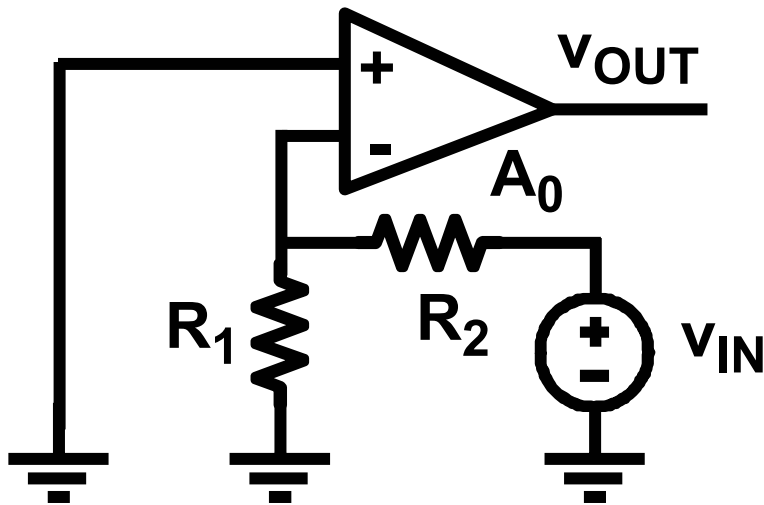

$$LG = \frac{V_{OUT}}{V_{IN}} = \frac{R_1}{R_1 + R_2} A_{VOL}$$

$$A_{VOL} \approx A_0 \approx 10^4 \dots 10^6$$

OL Open Loop

$$A_v = 1 + \frac{R_2}{R_1}$$


$$R_{IN} \approx \infty$$

IN : series FB : $R_{IN} \uparrow$
 OUT : shunt FB : $R_{OUT} \downarrow$


$$\text{Input series : } R_{IN} = R_{INOL} (1 + LG)$$

$$\text{Output shunt : } R_{OUT} = \frac{R_{OUTOL}}{1 + LG}$$

Shunt & series at input & output

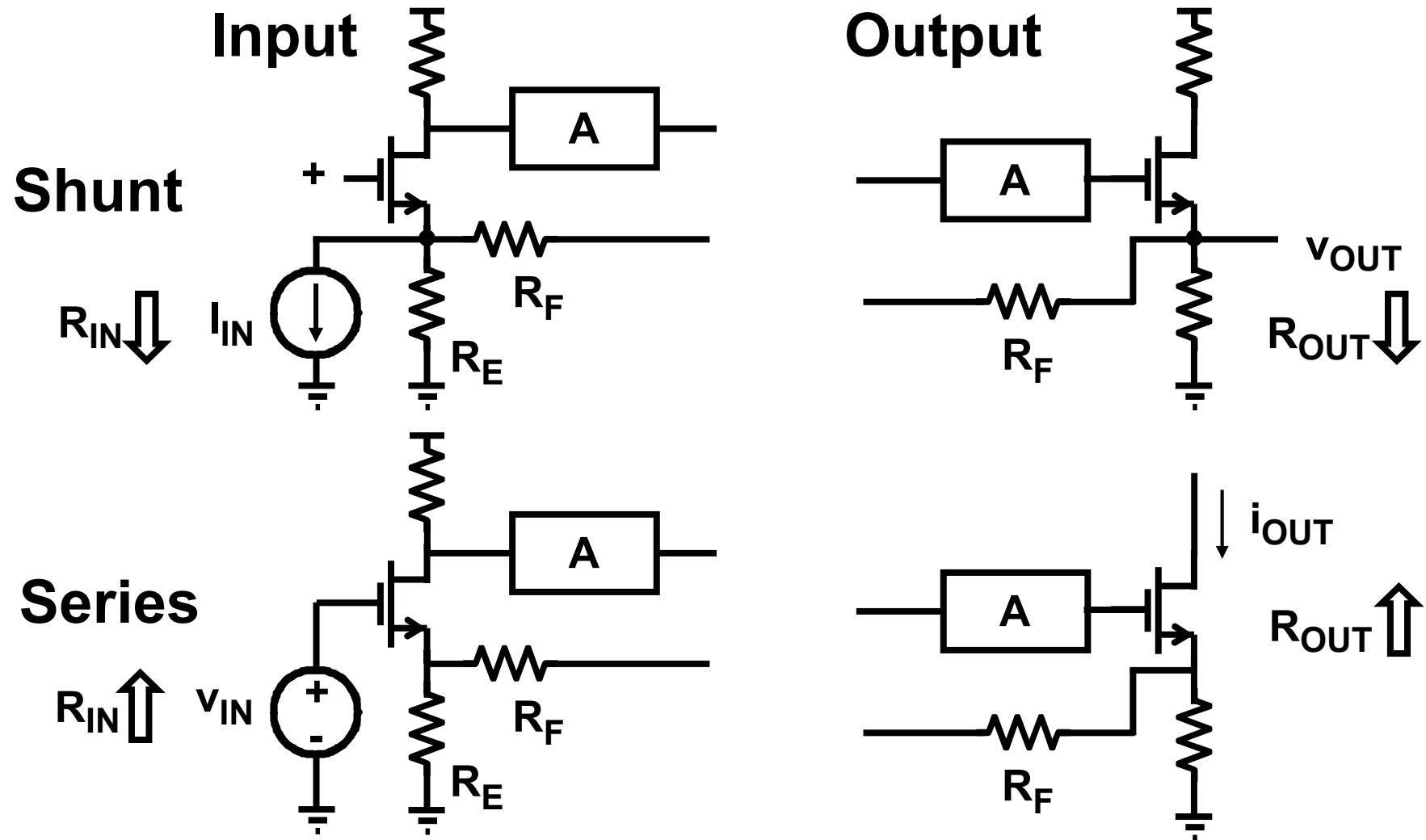


Shunt FB decreases the impedance

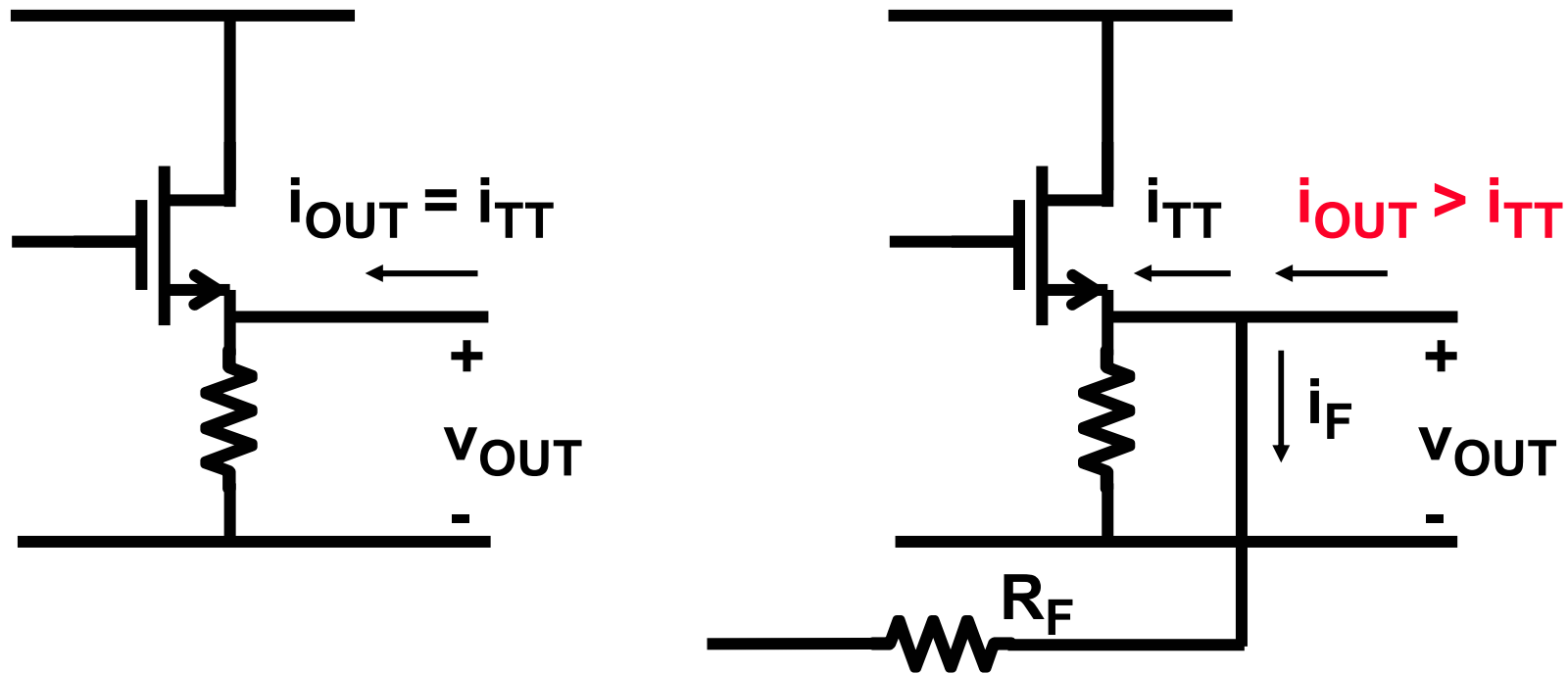

$$R_{OUT} = \frac{v_{OUT}}{i_{OUT}} \quad \Downarrow$$

Series FB increases the impedance

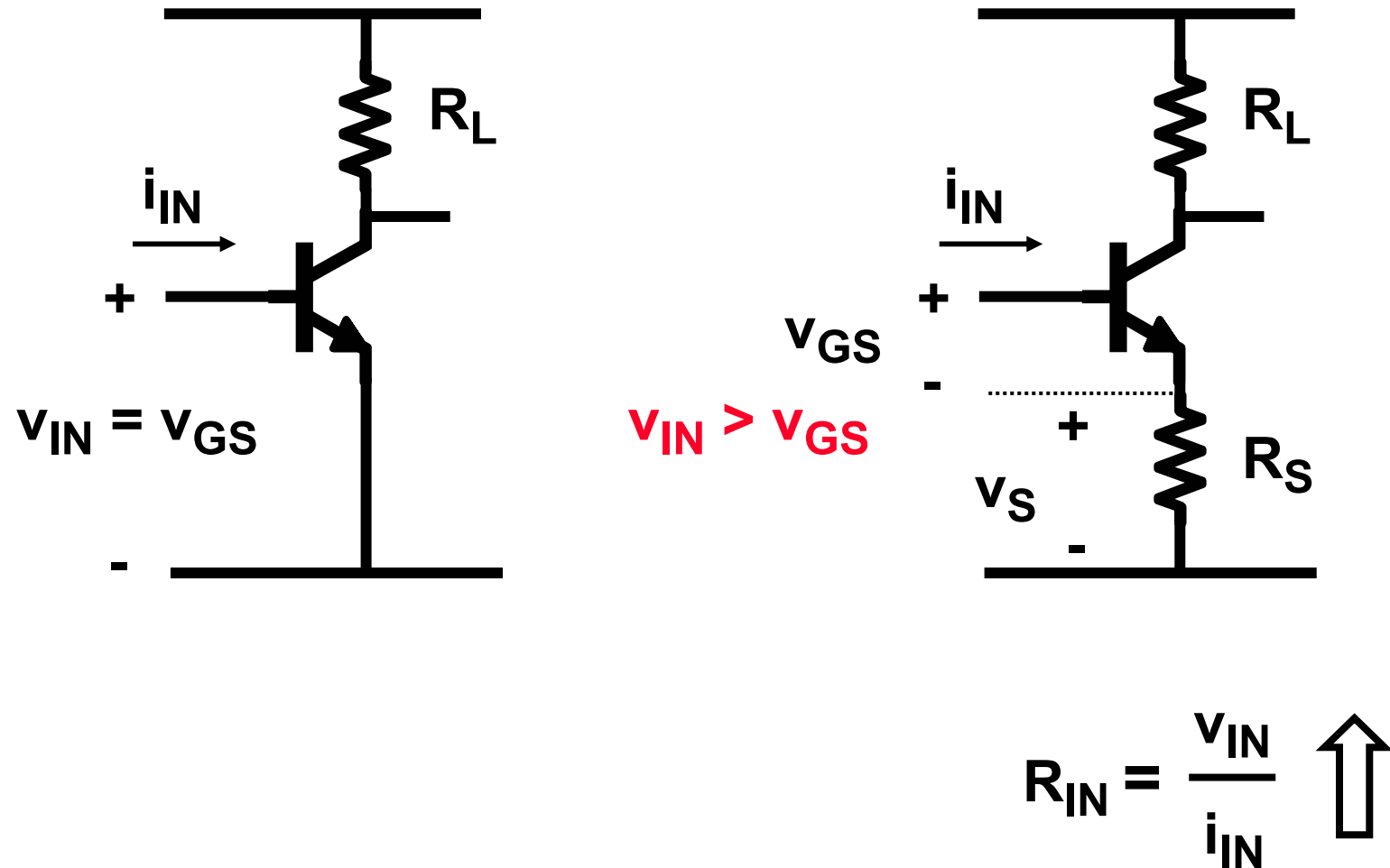

Input- & output impedances

$$\frac{1}{H} =$$

Output

Shunt

Series

Input

$$R_{OUT} = \frac{R_{OUTOL}}{1+LG}$$

$$R_{OUT} = R_{OUTOL}(1+LG)$$

Shunt $R_{IN} = \frac{R_{INOL}}{1+LG}$

$$\frac{v_{OUT}}{i_{IN}} = A_R$$

$$\frac{i_{OUT}}{i_{IN}} = A_I$$

Series $R_{IN} = R_{INOL}(1+LG)$

$$\frac{v_{OUT}}{v_{IN}} = A_V$$

$$\frac{i_{OUT}}{v_{IN}} = A_G$$

Shunt vs series feedback

Shunt feedback

lowers impedance levels : higher bandwidths


Series feedback

increases impedances : lower node poles


Output shunt best for interconnect to next stage !

Output series acts as current source !


Shunt versus series for sensors

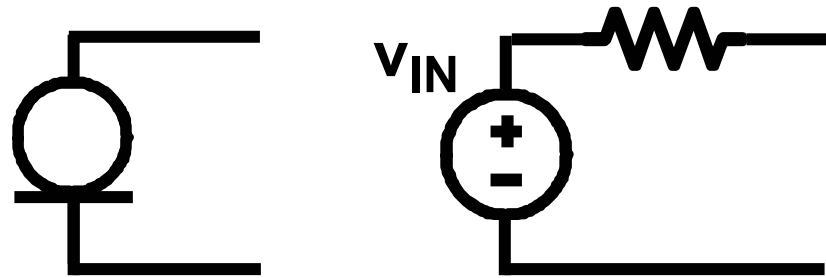

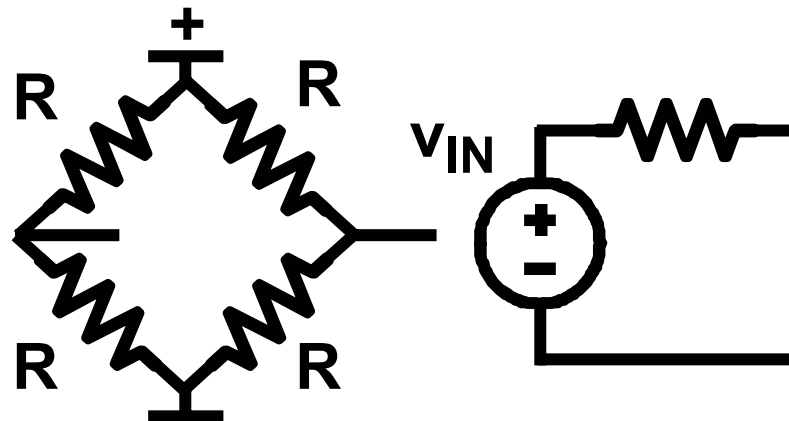Microphone
is a voltage source
requires a high R_{in} amplifier



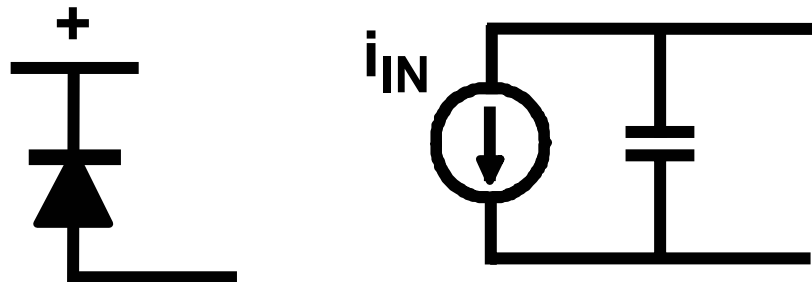Pressure- , temperature
sensors are voltage sources
require a high R_{in} amp.



Pixel-, photodiode , radiation
detectors are current sources,
require a low R_{in} amp.


Table of contents

- ◆ Definitions


- ◆ Series-shunt FB for Voltage amplifiers

- ◆ Series-series FB for Transconductance amps


Series-shunt FB configuration

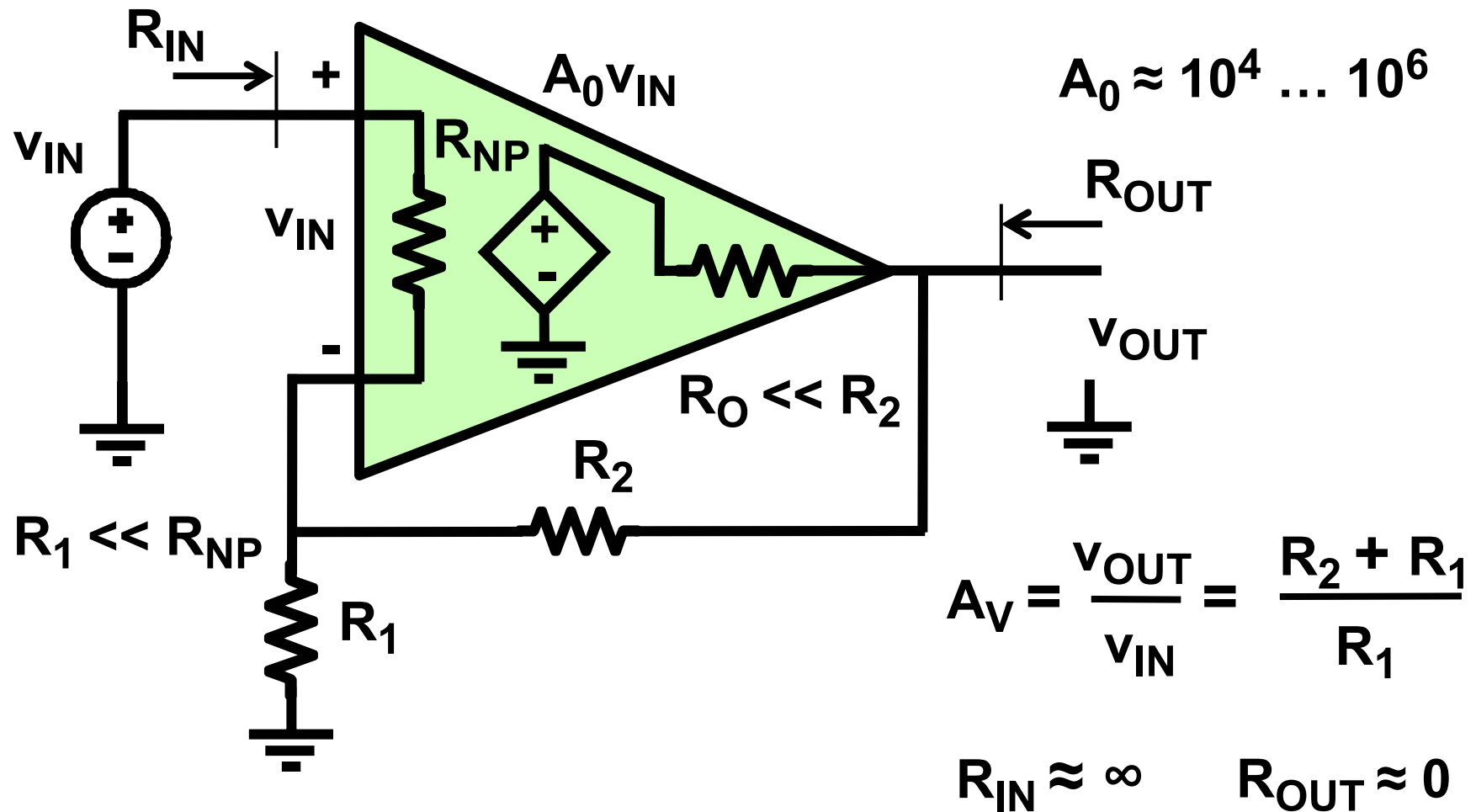


Series-shunt FB : loop gain

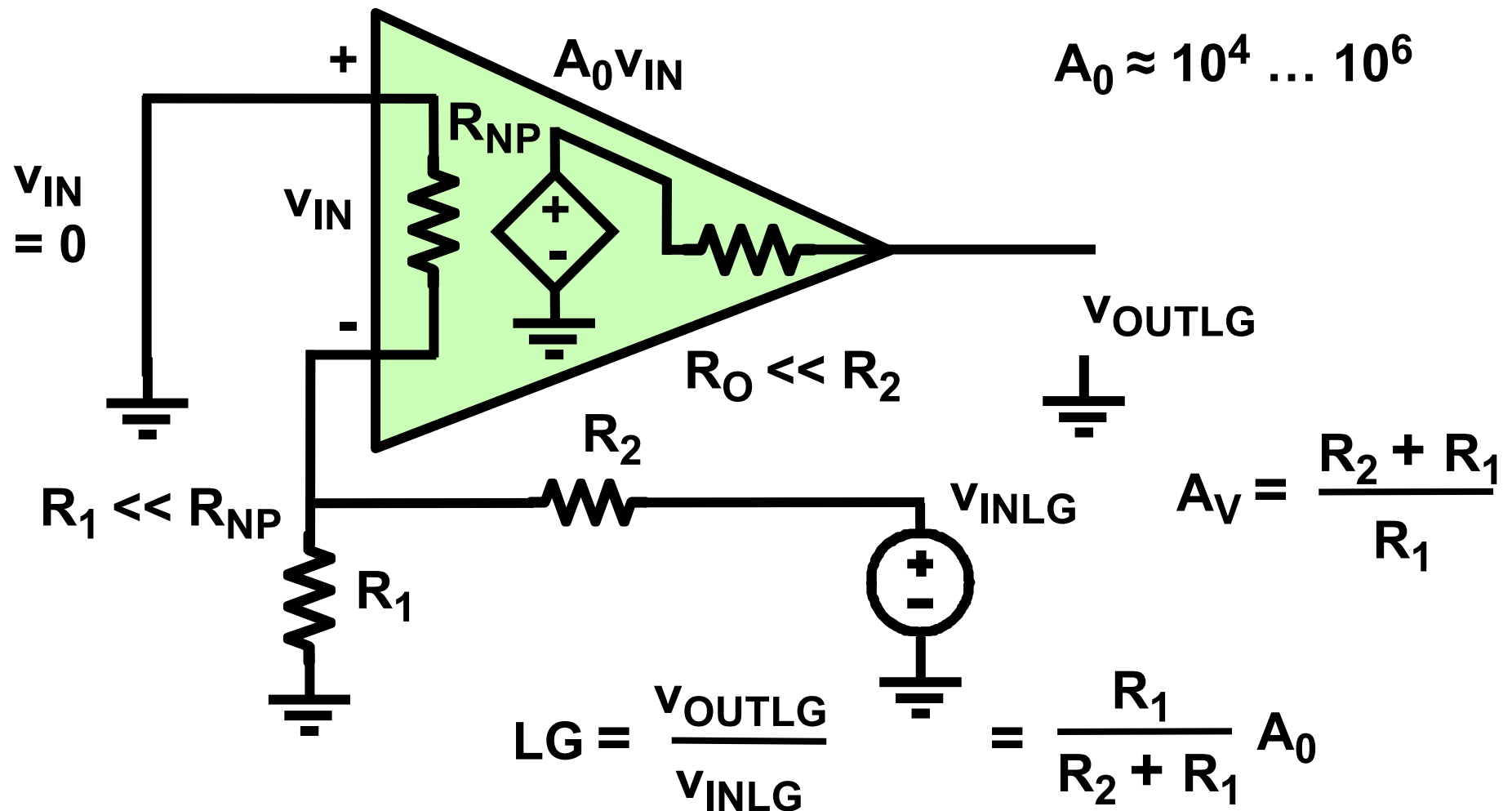


Series-shunt FB : input resistance

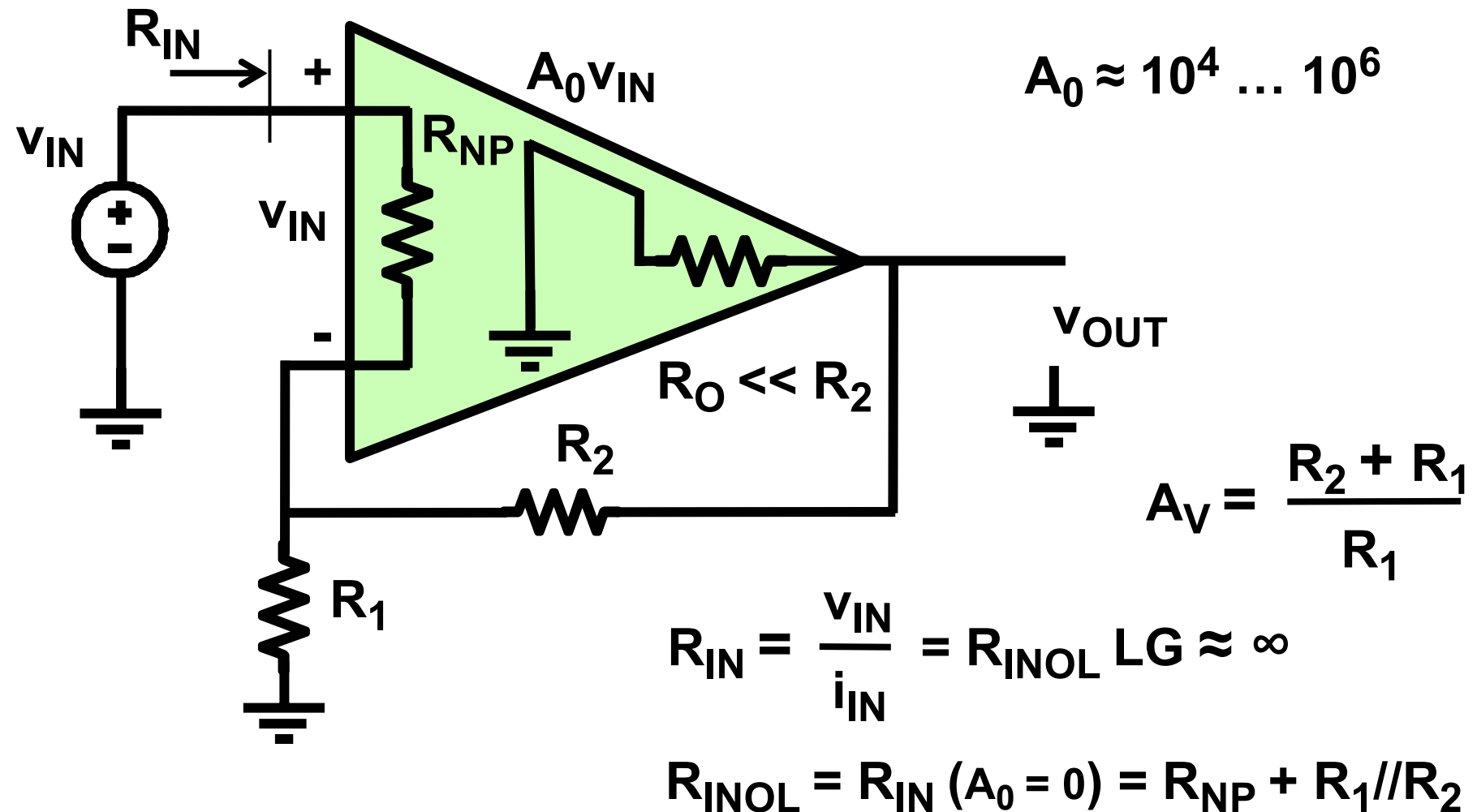

Series-shunt FB : output resistance

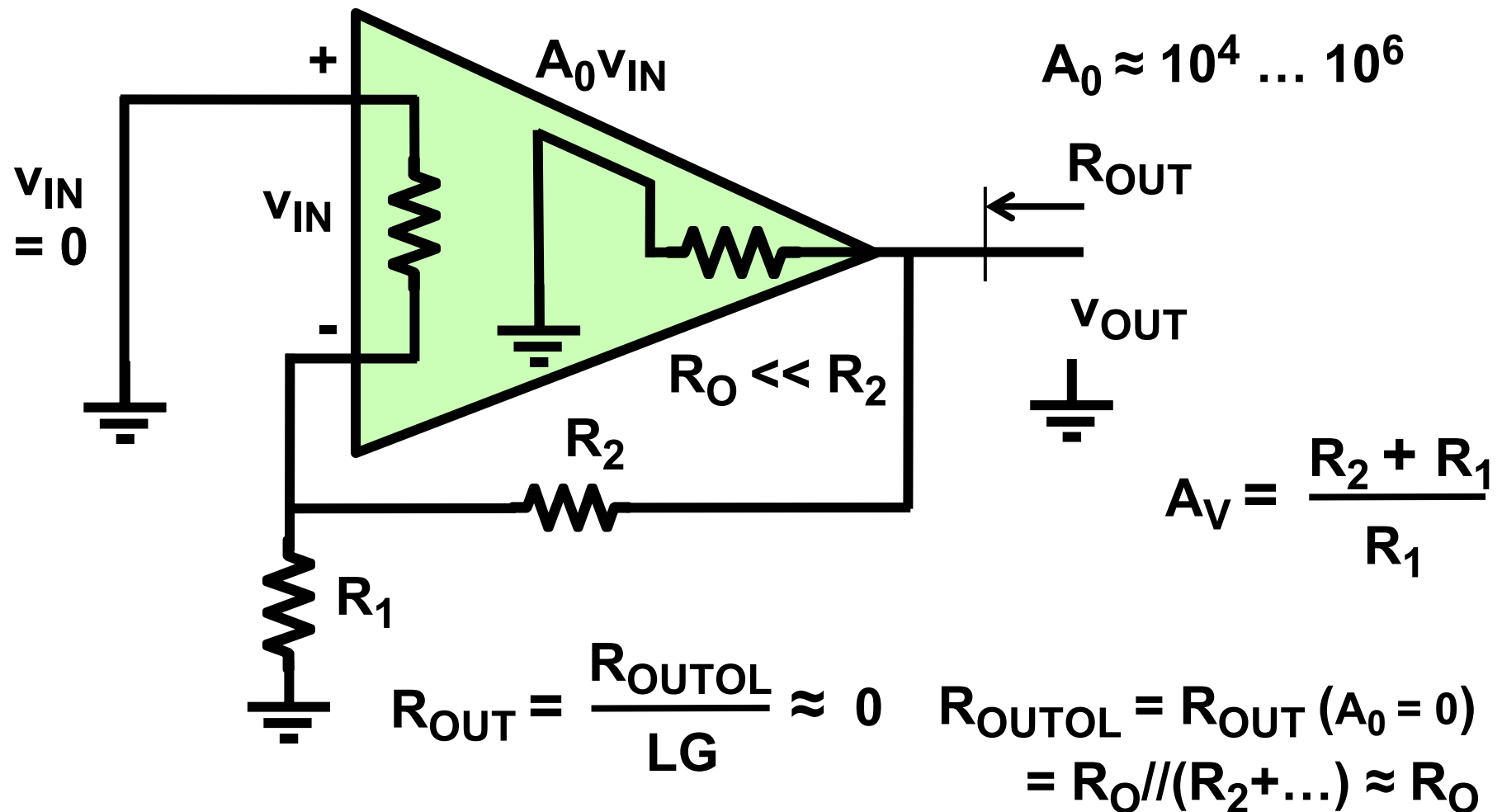


Series-shunt FB pair : loop gain

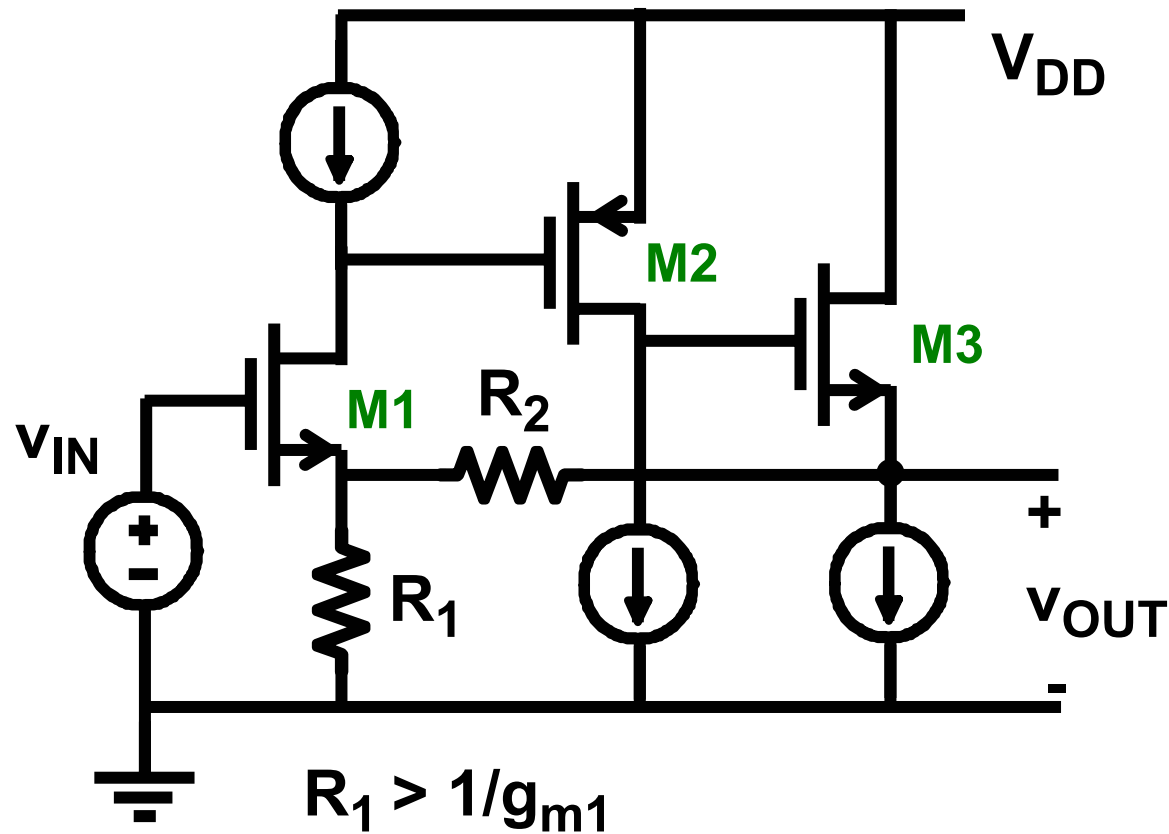


$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG = ?$$


Series-shunt FB pair : series input

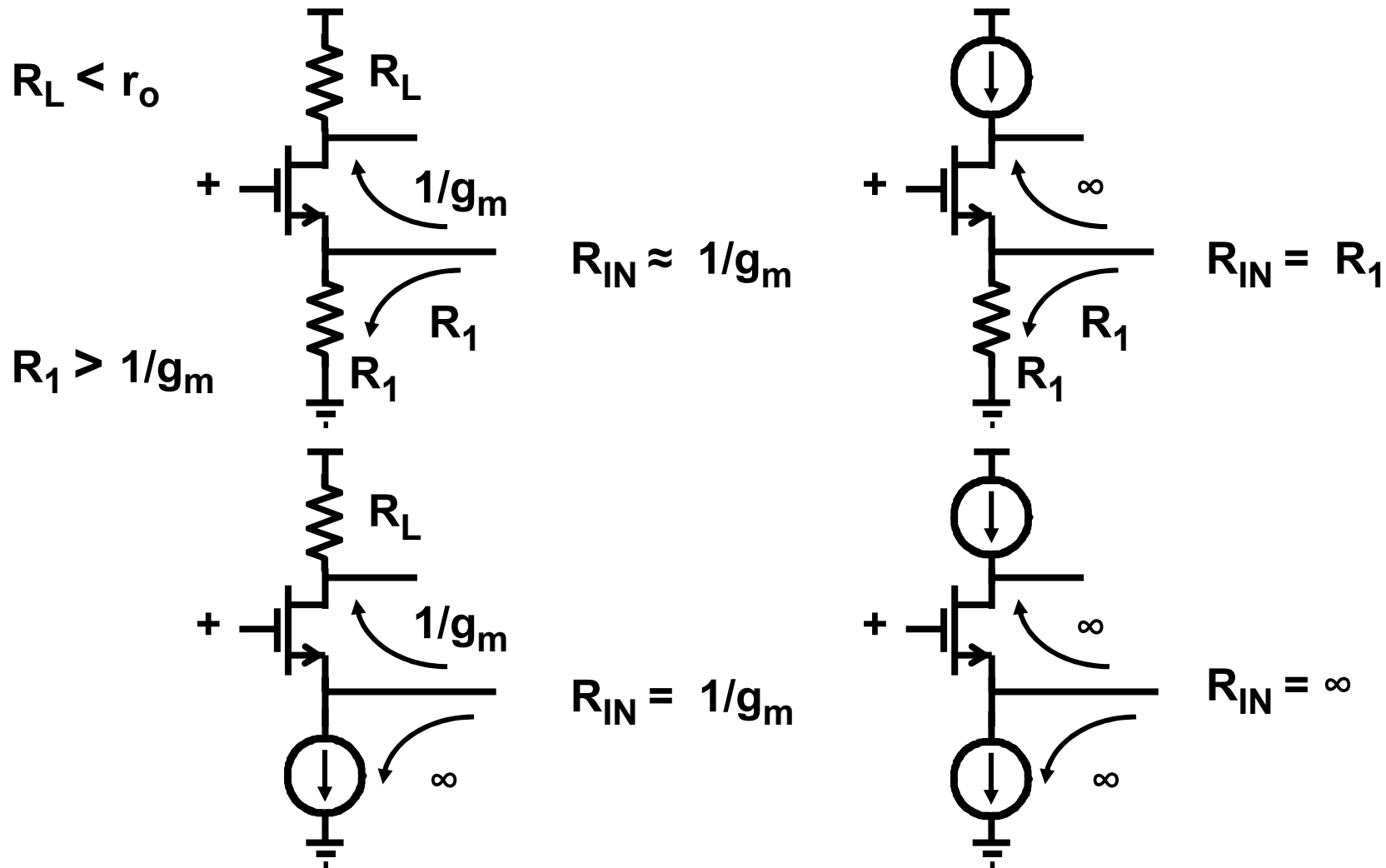

Series-shunt FB pair : gain input stage

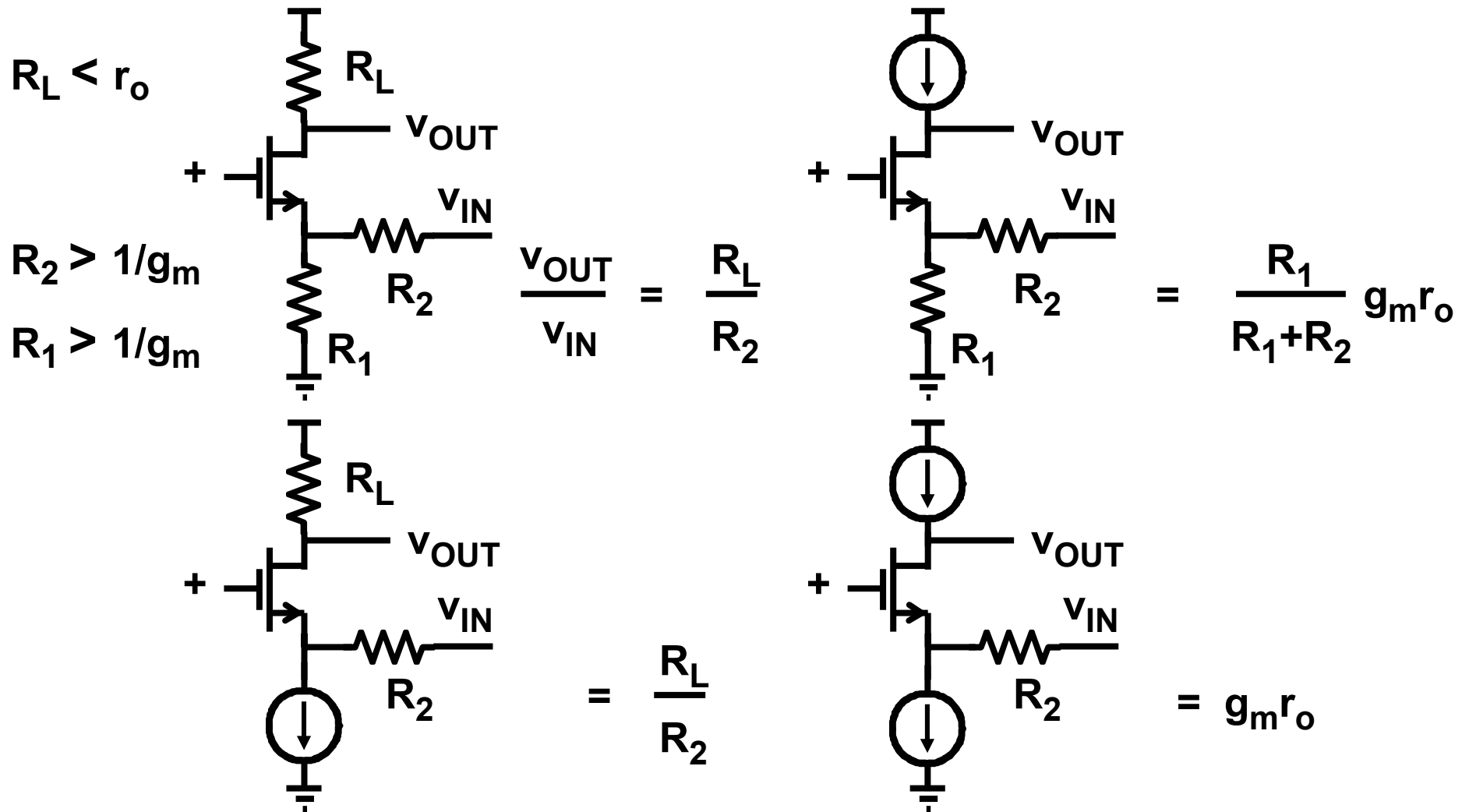

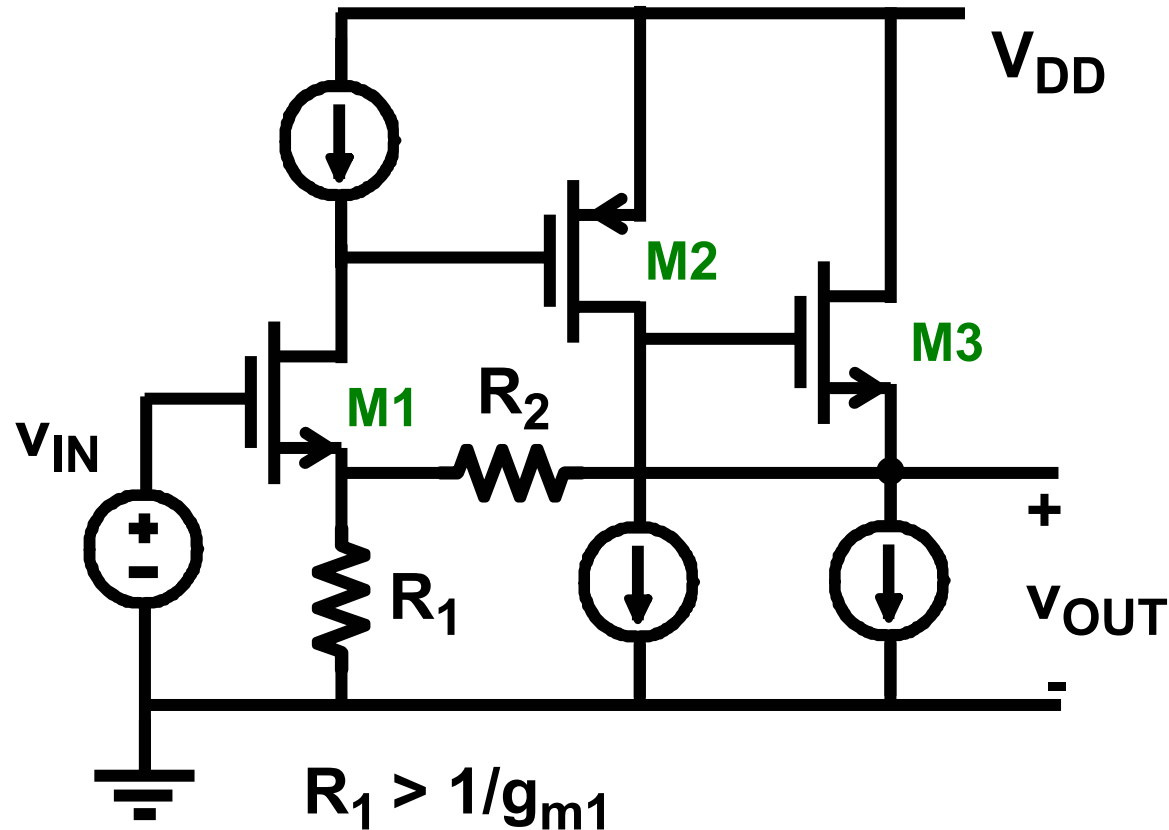Series-shunt FB pair : input & output resistance




$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG = g_{m1}r_{o1} g_{m2}r_{o2} \frac{R_1}{R_1 + R_2}$$

$$R_{IN} \approx \infty$$

$$R_{OUT} = \frac{1/g_{m3}}{LG} \approx 0$$


Series-shunt FB pair : loop gain

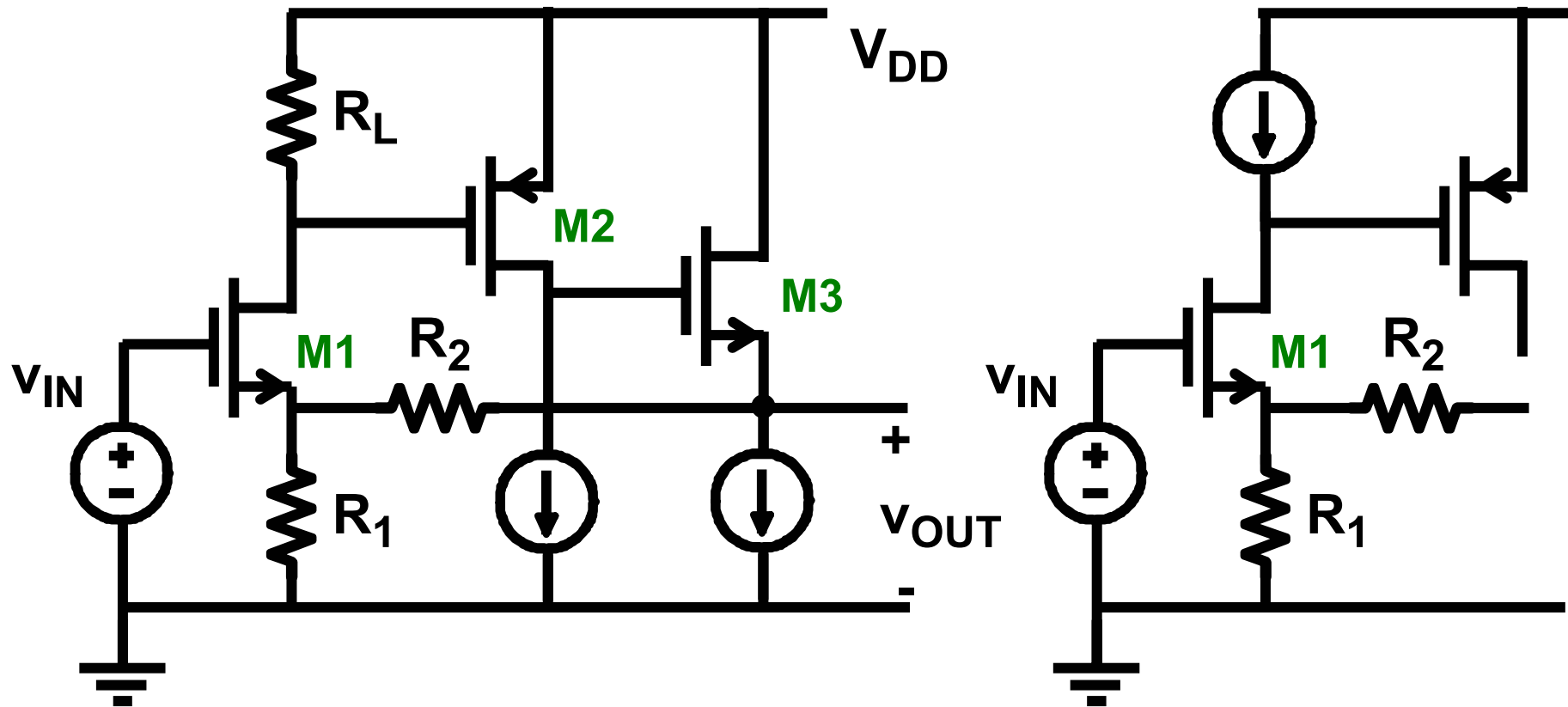

$$LG = g_{m2} r_{o2} \frac{R_L}{R_2}$$

$$LG = g_{m1} r_{o1} g_{m2} r_{o2} \frac{R_1}{R_1 + R_2}$$

Series-shunt FB pair : output loading

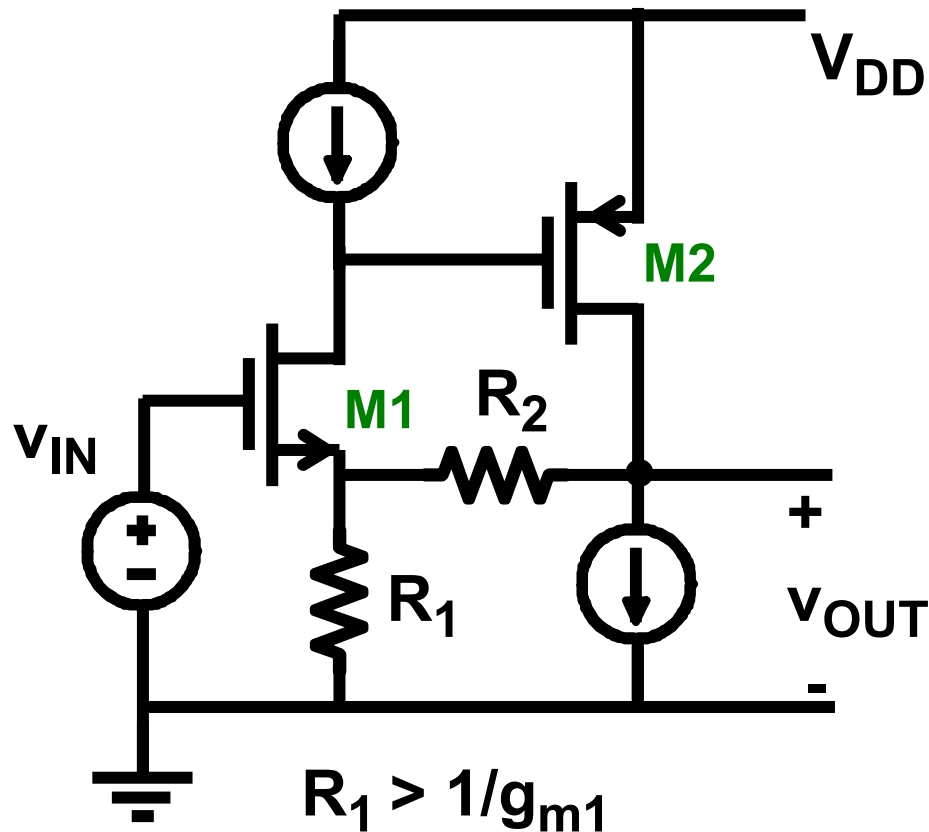

$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG =$$


$$g_{m1} r_{o1} g_{m2} \frac{r_{o2} R_1}{R_1 + R_2 + r_{o2}}$$

$$R_{IN} \approx \infty$$

$$R_{OUT} = \frac{(R_1 + R_2) // r_{o2}}{LG} \approx 0 \quad ??$$

Output loading : $R_2 \approx r_{o2}$

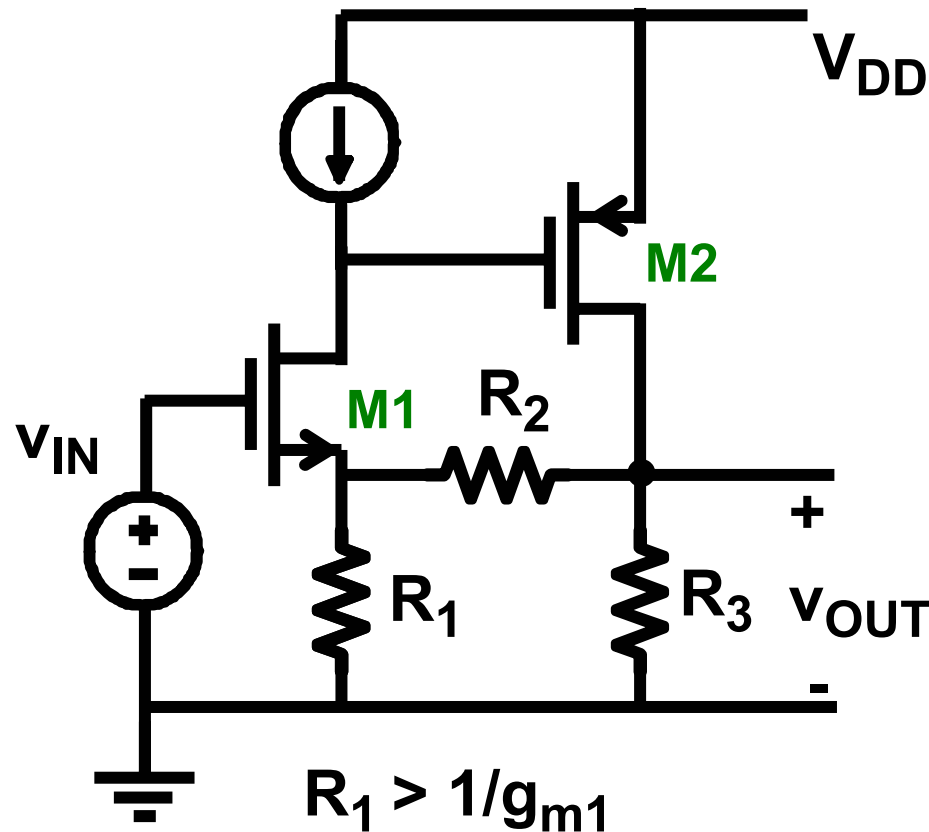Series-shunt FB pair : output loading with R



$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG =$$


$$g_{m1} r_{o1} g_{m2} \frac{r_{o2} // R_3}{R_1 + R_2 + r_{o2} // R_3} R_1$$

$$R_{IN} \approx \infty$$

$$R_{OUT} = \frac{(R_2 + R_1) // r_{o2} // R_3}{LG} \approx 0 ??$$

Output loading : $R_2 \approx R_3 \approx r_{o2}$

Series-shunt pair in BiCMOS

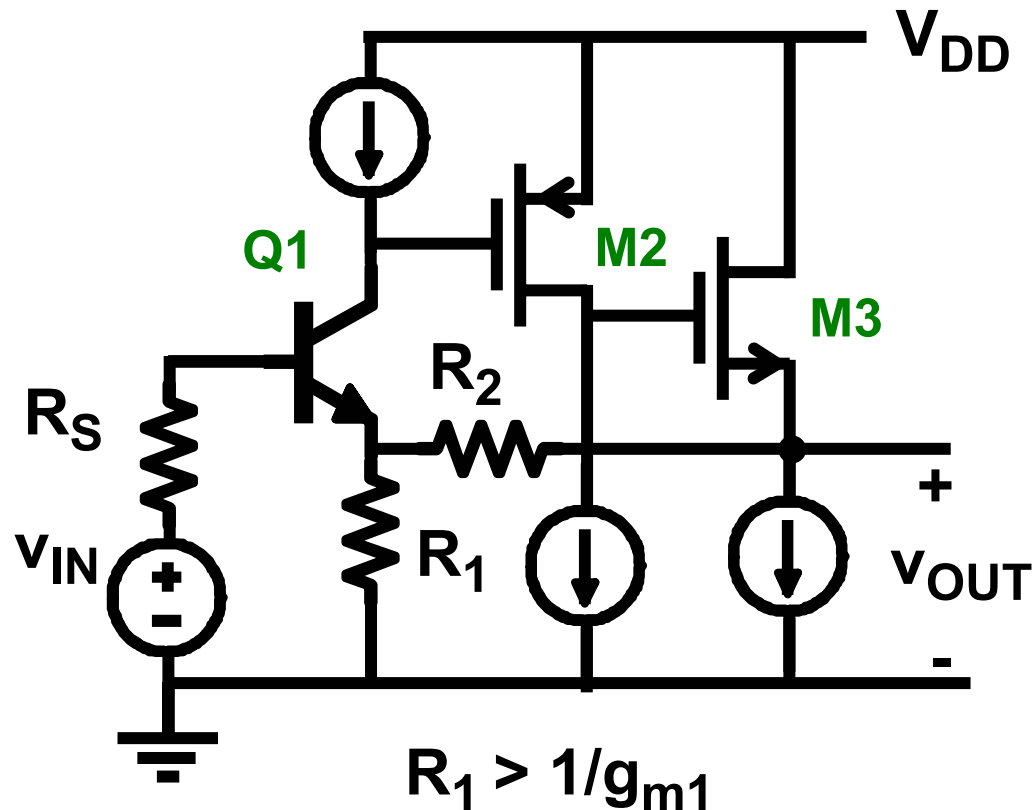

$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG =$$

$$g_{m1} r_{o1} g_{m2} r_{o2} \frac{R_1}{R_1 + R_2}$$


$$R_{IN} = R_{INOL} LG \approx \infty$$

$$R_{INOL} = r_{\pi 1} + \beta (R_1 // R_2)$$

$$R_{OUT} = \frac{1/g_{m3}}{LG} \approx 0$$

Input loading : $R_{IN} < \infty$

Series-shunt FB pair with resistances

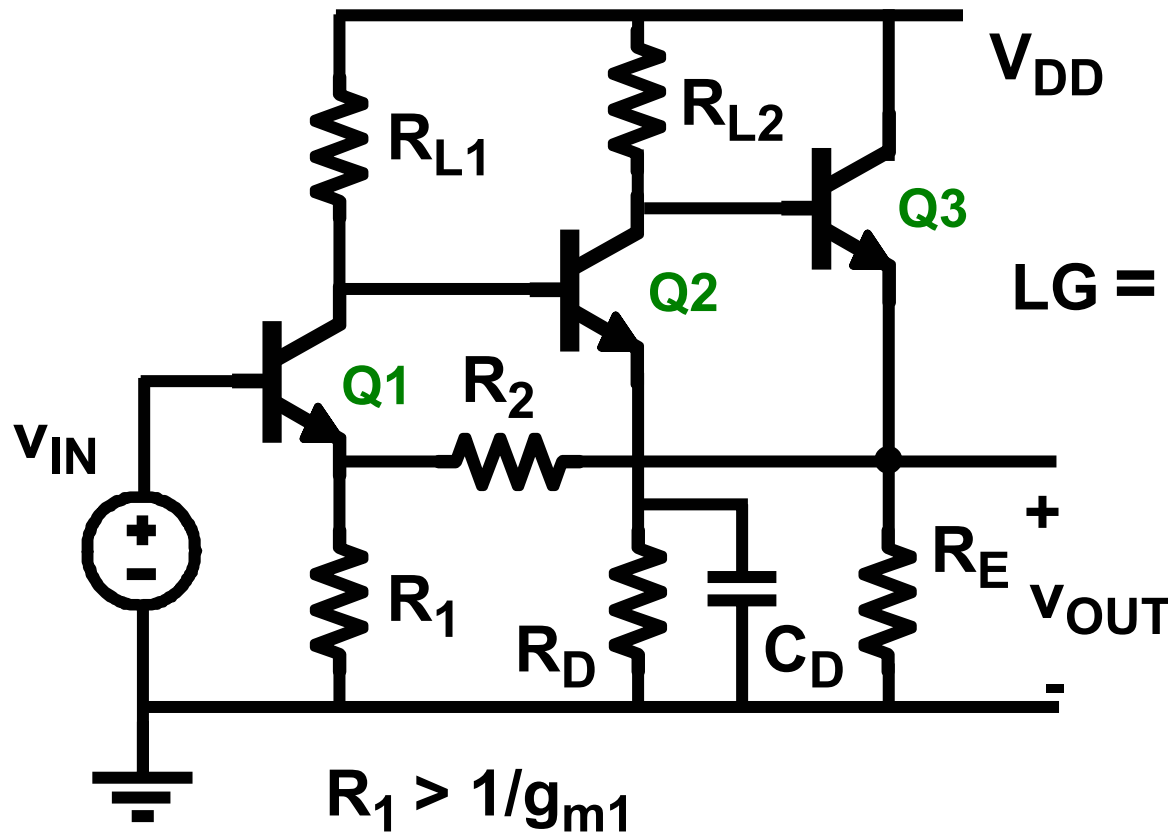

$$A_V = \frac{R_2 + R_1}{R_1}$$

$$LG = \frac{R_{L1} // r_{\pi 2}}{R_2} g_{m2} r_{o2} \frac{R_{L2}}{R_{L2} + r_{o2}}$$

$$R_{IN} = R_{INOL} \quad LG \approx \infty$$

$$R_{INOL} = r_{\pi 1} + \beta (R_1 // R_2)$$

$$R_{OUT} = \frac{R_{OUTOL}}{LG} \approx 0$$


Input loading : $R_{IN} < \infty$

$$R_{OUTOL} = \frac{1}{g_{m3}} + \frac{R_{L2} // r_{o2}}{\beta}$$

Table of contents

- ◆ Definitions
- ◆ Series-shunt FB for Voltage amplifiers.
- ◆ Series-series FB for Transconductance amps.

Series-series feedback : gain

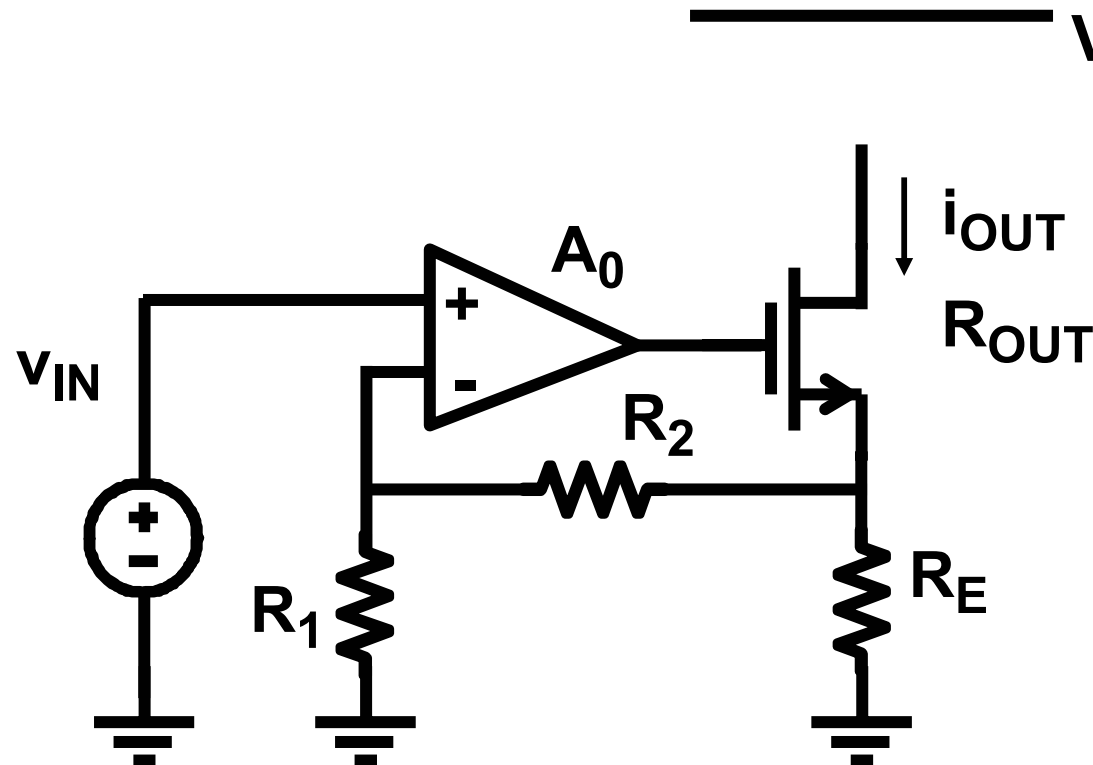

$$R_{E12} = R_E \parallel (R_1 + R_2)$$


$$LG = A_0 \frac{R_1}{R_2 + R_1}$$

$$A_{GOL} = A_0 \frac{1}{R_{E12}}$$

$$A_G = \frac{R_2 + R_1}{R_1} \frac{1}{R_{E12}}$$

$$= \frac{R_2 + R_1 + R_E}{R_1} \frac{1}{R_E}$$

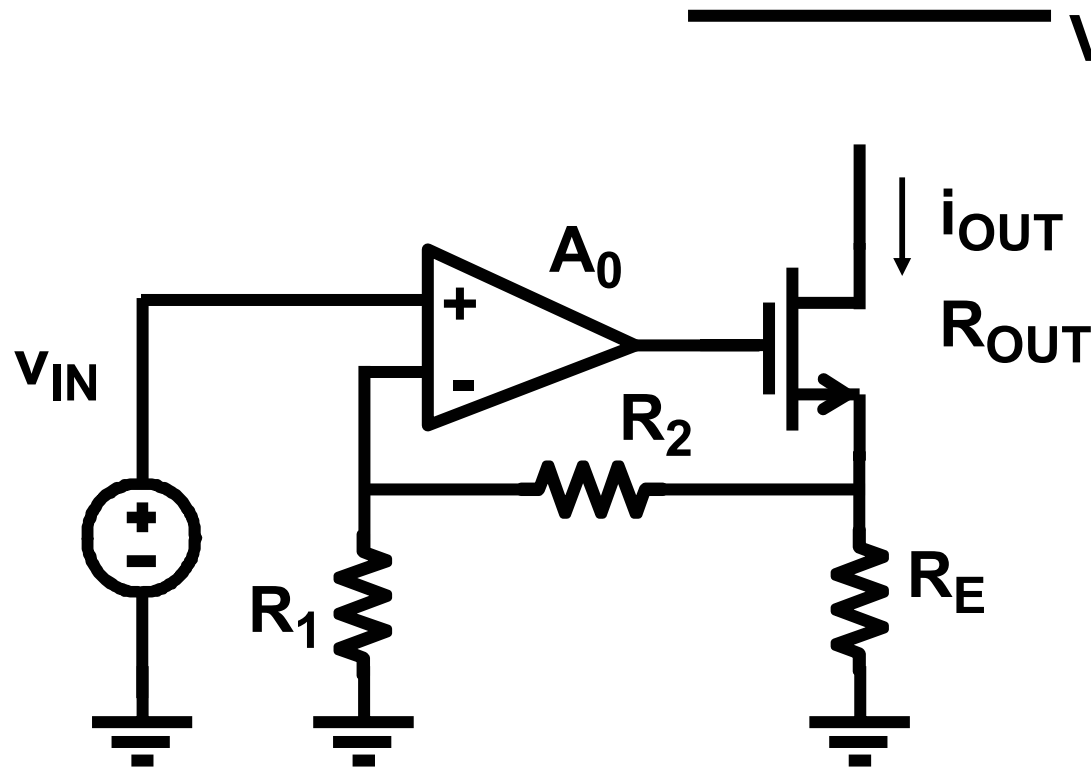Series-series feedback : in- & output resistances



$$LG = A_0 \frac{R_1}{R_2 + R_1}$$


$$R_{IN} = \infty$$

$$R_{OUTOL} = r_o (1 + g_m R_{E12})$$

$$R_{OUT} = R_{OUTOL} LG \approx \infty$$

$$R_{E12} = R_E // (R_1 + R_2)$$

Series-series feedback with load R_L

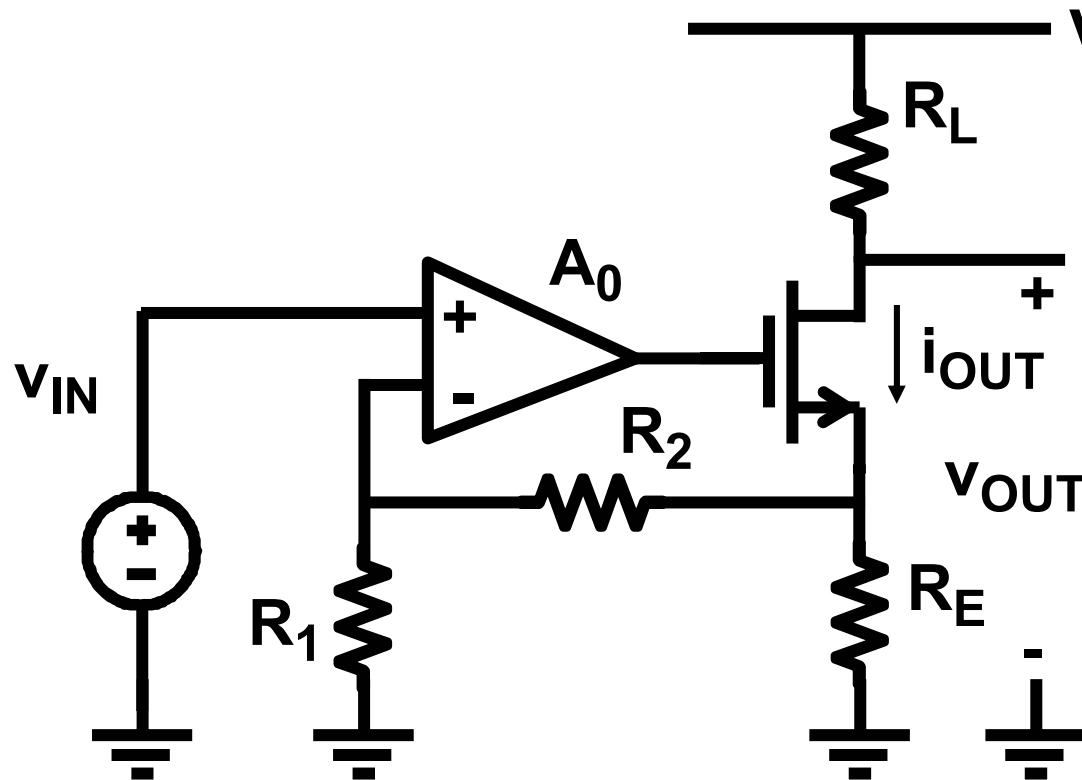

$$R_{E12} = R_E \parallel (R_1 + R_2)$$

$$A_G = \frac{R_2 + R_1}{R_1} \frac{1}{R_{E12}}$$


$$A_V = - \frac{R_2 + R_1}{R_1} \frac{R_L}{R_{E12}}$$

$$= - \frac{R_2 + R_1 + R_E}{R_1} \frac{R_L}{R_E}$$

$$R_{IN} = \infty$$

$$R_{OUT} = R_L$$

Ideal current source

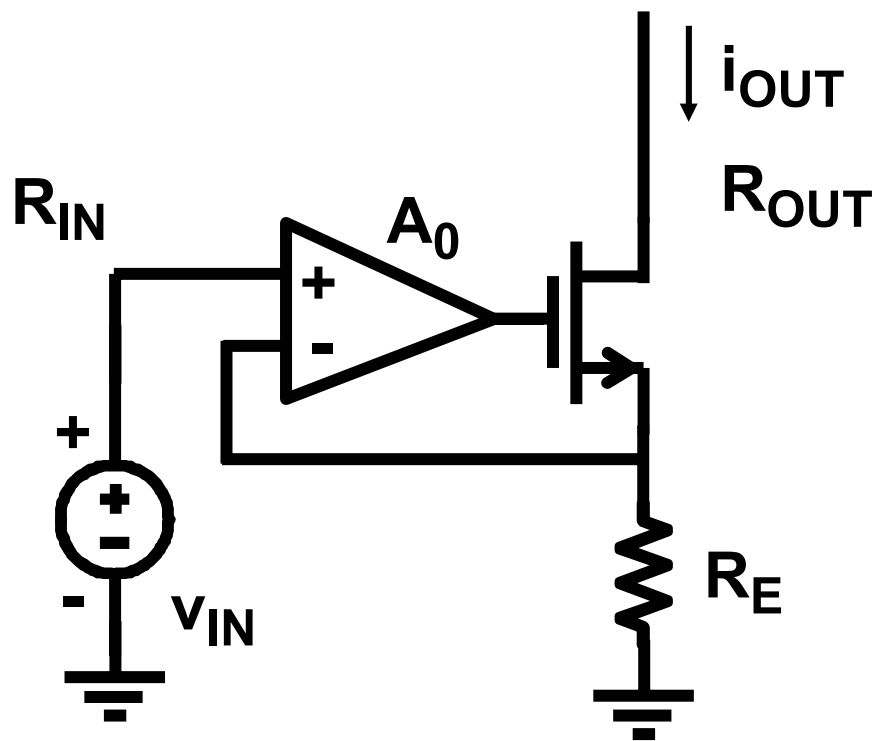

$$i_{OUT} = \frac{V_{IN}}{R_E}$$


$$LG = A_0$$

$$R_{IN} \approx \infty$$


$$R_{OUT} = R_{OUTOL} LG$$

$$R_{OUTOL} \approx r_o (1 + g_m R_E)$$

Series-series feedback : two outputs

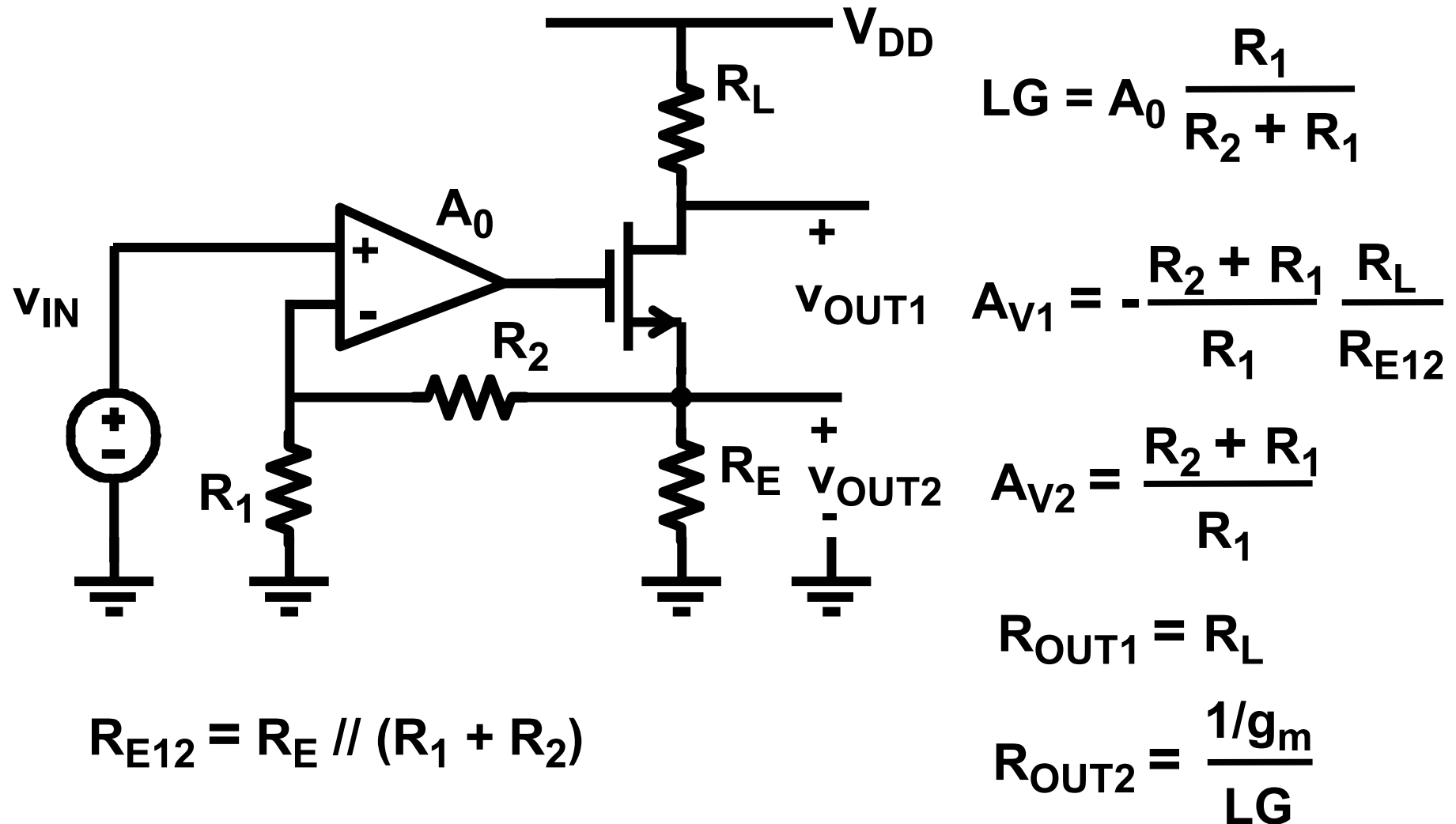

Series-series FB triple

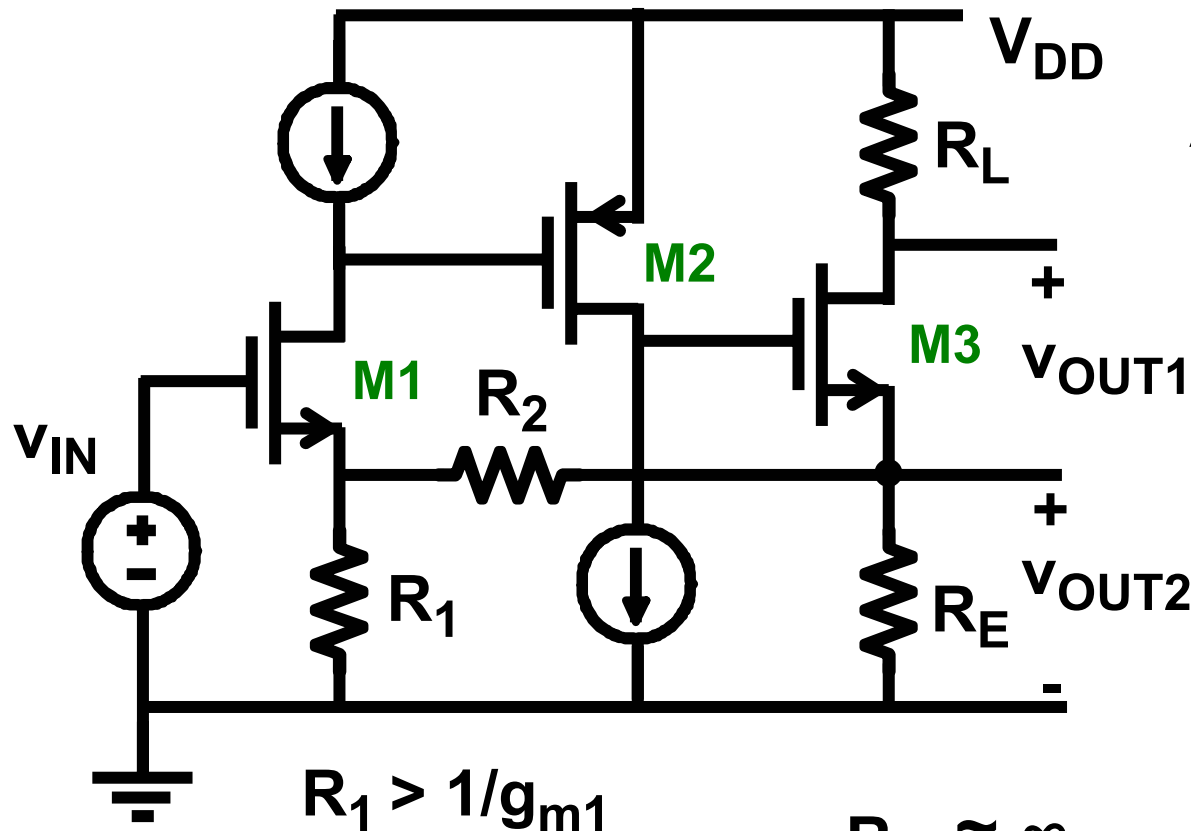

$$A_{V1} = -\frac{R_2 + R_1}{R_1} \frac{R_L}{R_{E12}}$$


$$A_{V2} = \frac{R_2 + R_1}{R_1}$$

$$LG = A_1 A_2 \frac{R_1}{R_2 + R_1}$$

$$A_i = g_{mi} r_{oi}$$

$$R_{E12} = R_E // (R_1 + R_2) \quad R_{IN} \approx \infty \quad R_{OUT1} = R_L \quad R_{OUT2} = \frac{1/g_{m2}}{LG} \approx 0$$

Series-series FB triple

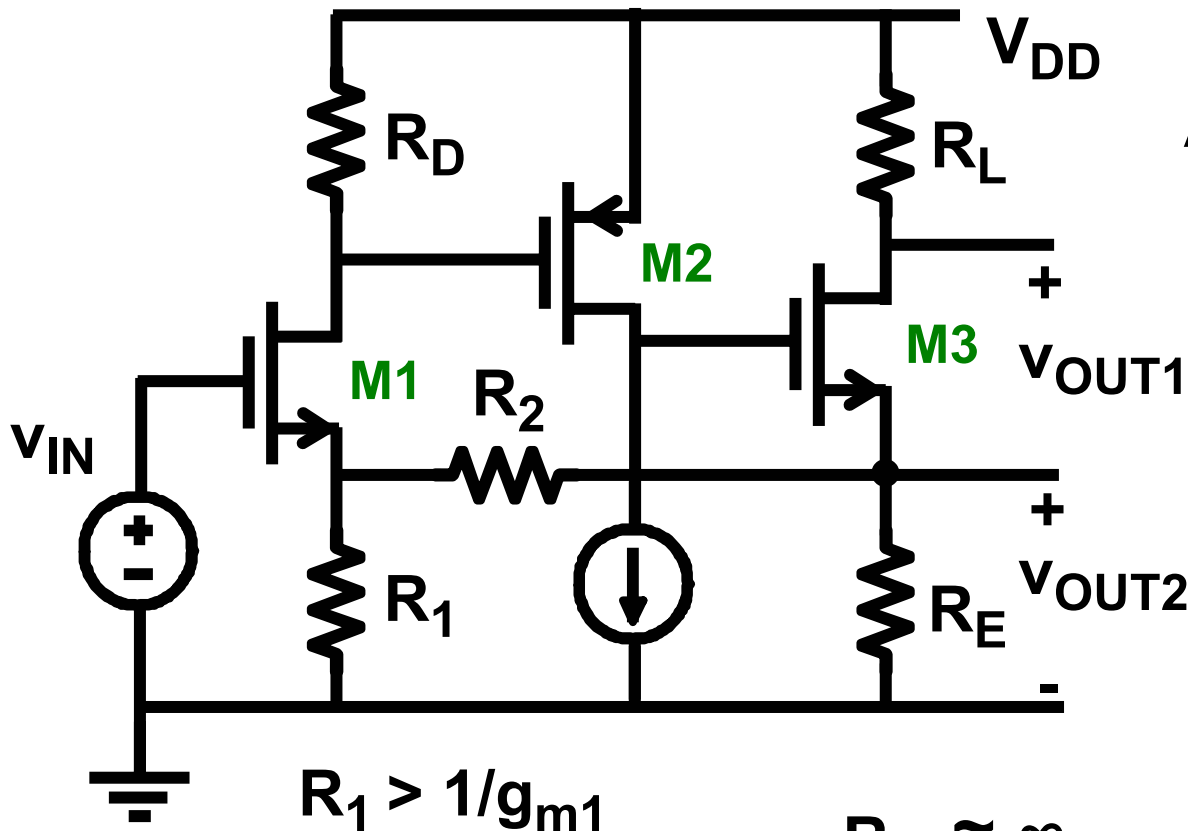


$$A_{V1} = - \frac{R_2 + R_1}{R_1} \frac{R_L}{R_{E12}}$$

$$A_{V2} = \frac{R_2 + R_1}{R_1}$$

$$LG = g_{m2} r_{o2} \frac{R_D}{R_2}$$

Series-series triple

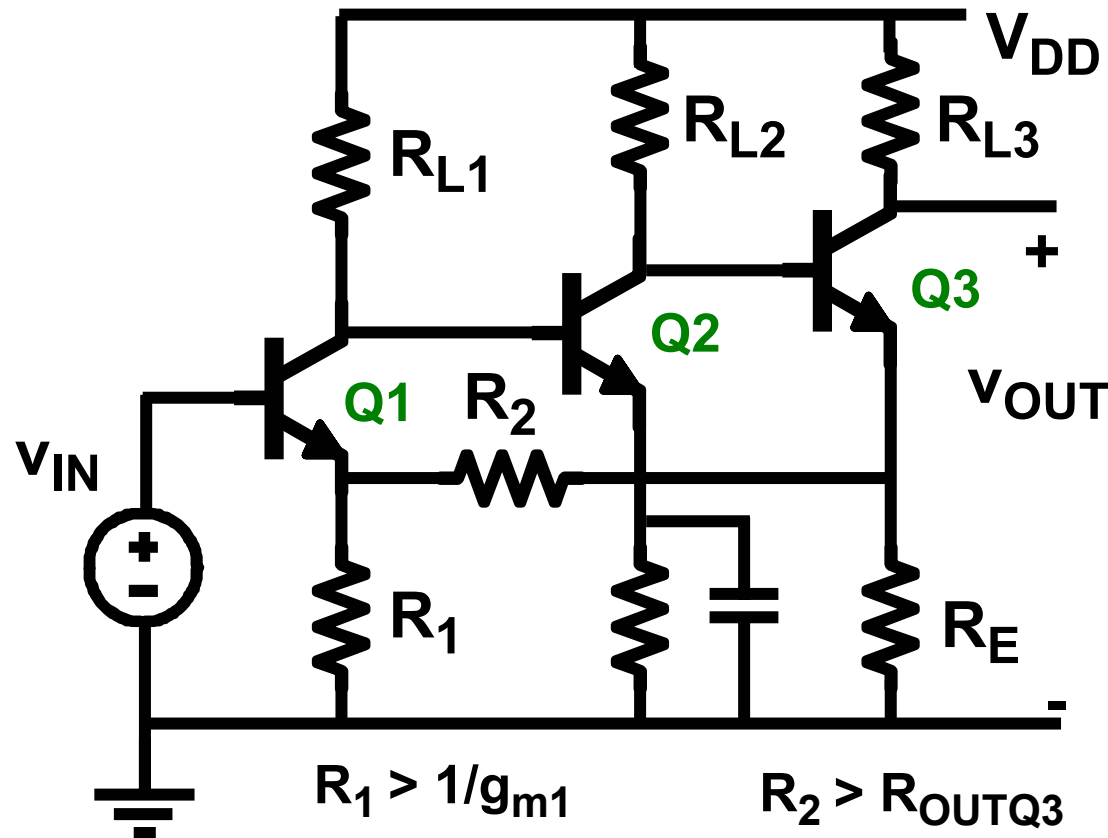

Input loading : $R_{IN} < \infty$

Wooley, JSSC Feb.71, 24-34

$$A_V = - \frac{R_2 + R_1}{R_1} \frac{R_{L3}}{R_{E12}}$$

$$R_{E12} = R_E // (R_1 + R_2)$$

$$LG \approx$$


$$g_{m2}(r_{o2} // R_{L2}) \frac{R_{L1} // r_{\pi 2}}{R_2}$$

$$R_{IN} = R_{INOL} \quad LG \approx \infty$$

$$R_{INOL} = r_{\pi 1} + \beta (R_1 // R_2)$$

$$R_{OUT} = R_{L3}$$

Nonideal single-transistor FB

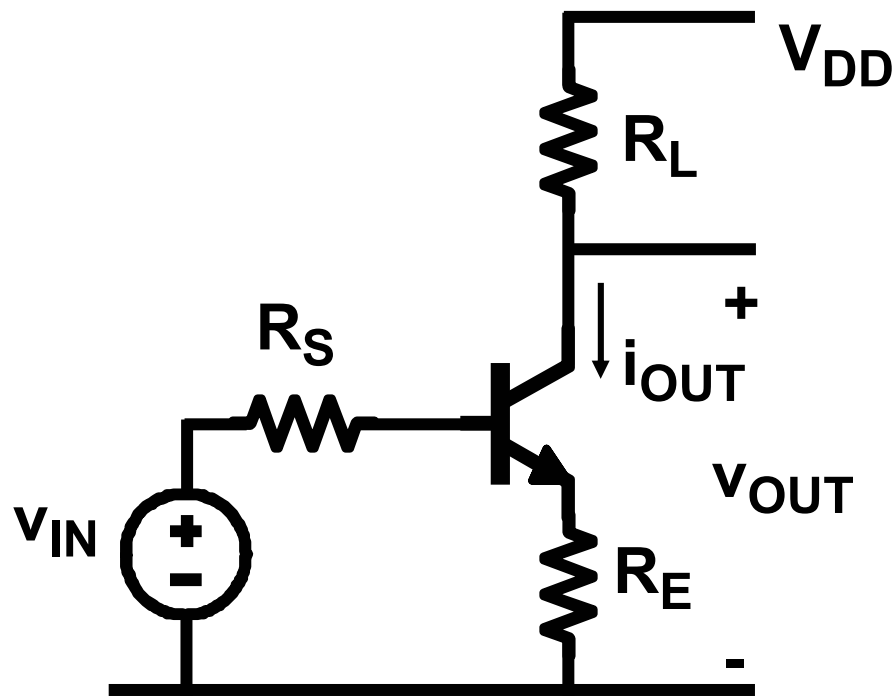

$$A_G \approx \frac{1}{R_E} \quad A_V \approx -\frac{R_L}{R_E}$$

$$LG = g_m R_E \quad (>>1)$$


$$R_{IN} = r_\pi + \beta R_E$$

$$R_{OUT} = R_L // r_{oL}$$


Output loading : $R_L \approx r_{oL}$ $r_{oL} = r_o (g_m R_E)$

Input loading : $R_S < R_{IN}$ $R_{IN} = r_\pi + \beta R_E$

Decreasing distortion by feedback

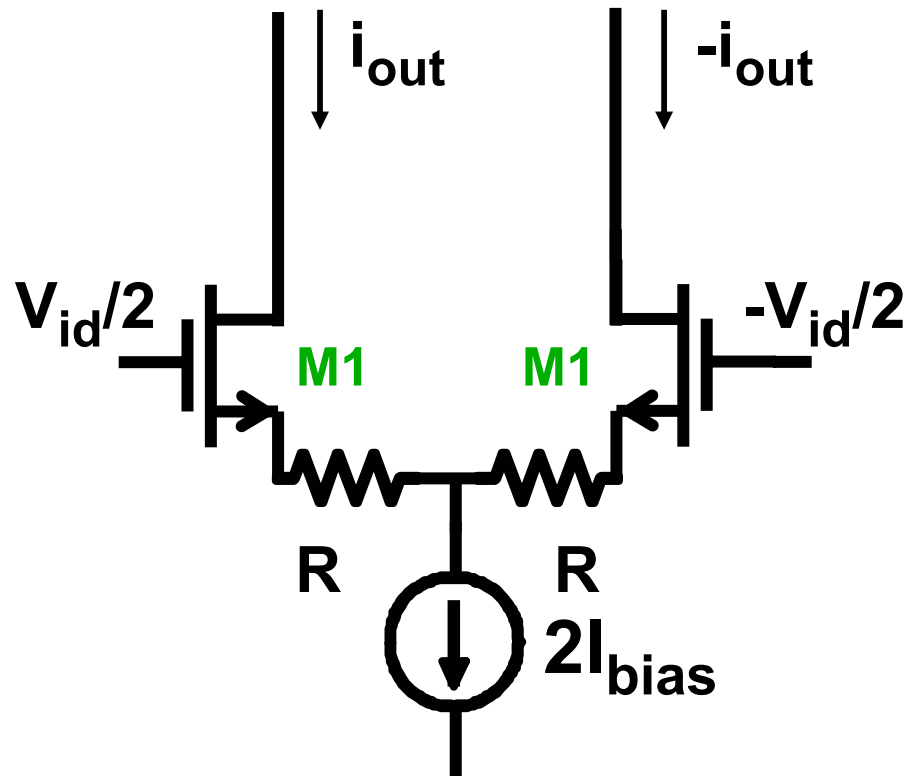


$$LG = g_m R \quad (>>1)$$

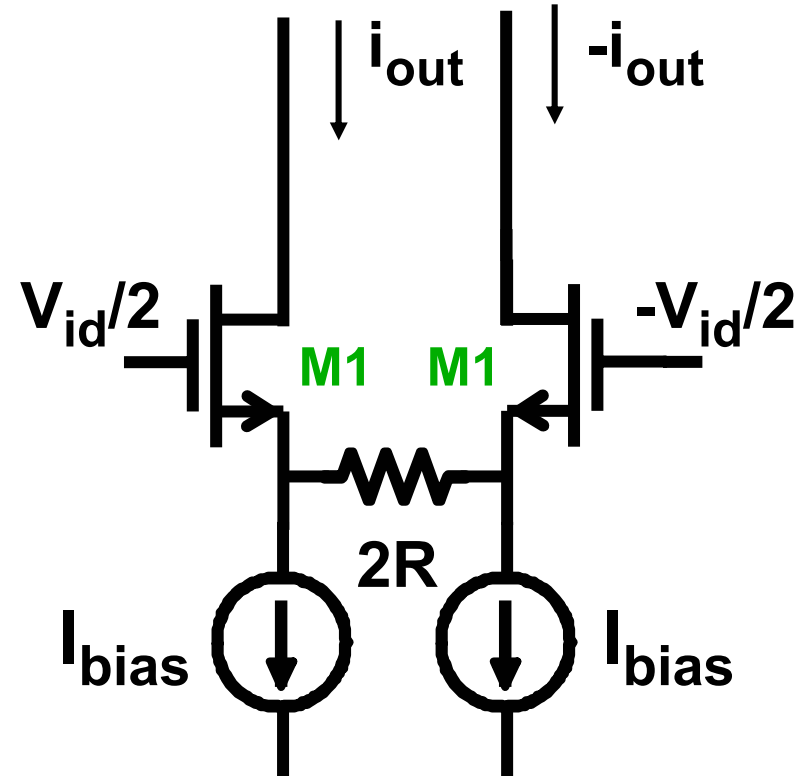

$$A_G \approx \frac{1}{R}$$

By tunable feedback

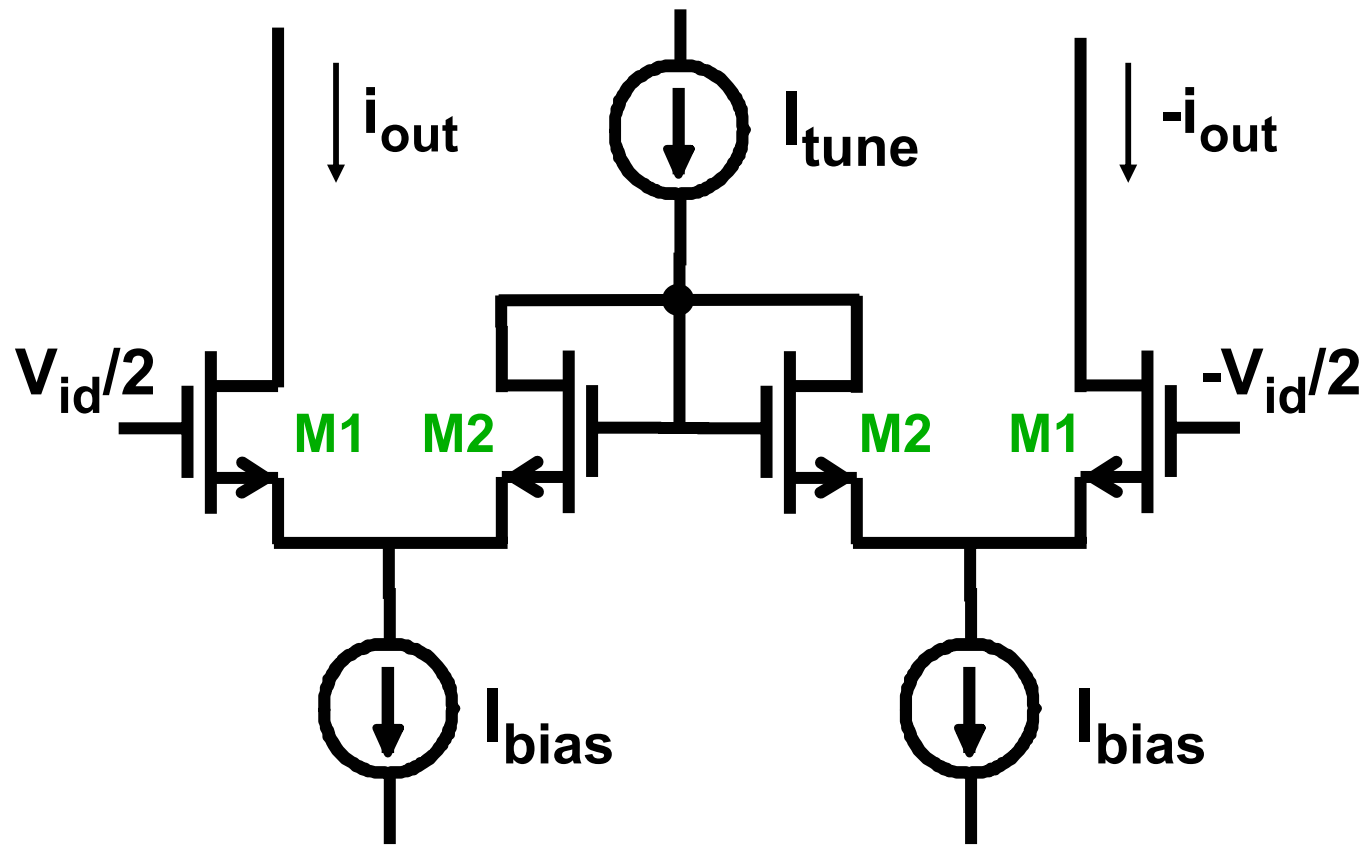


$$R = 1/g_{m2}$$

$$A_G \approx \frac{1}{R}$$


$$LG = g_m R \ (\gg 1)$$

Ref. Torrance et al CAS Nov.85, 1097-1104

Decreasing distortion by more feedback

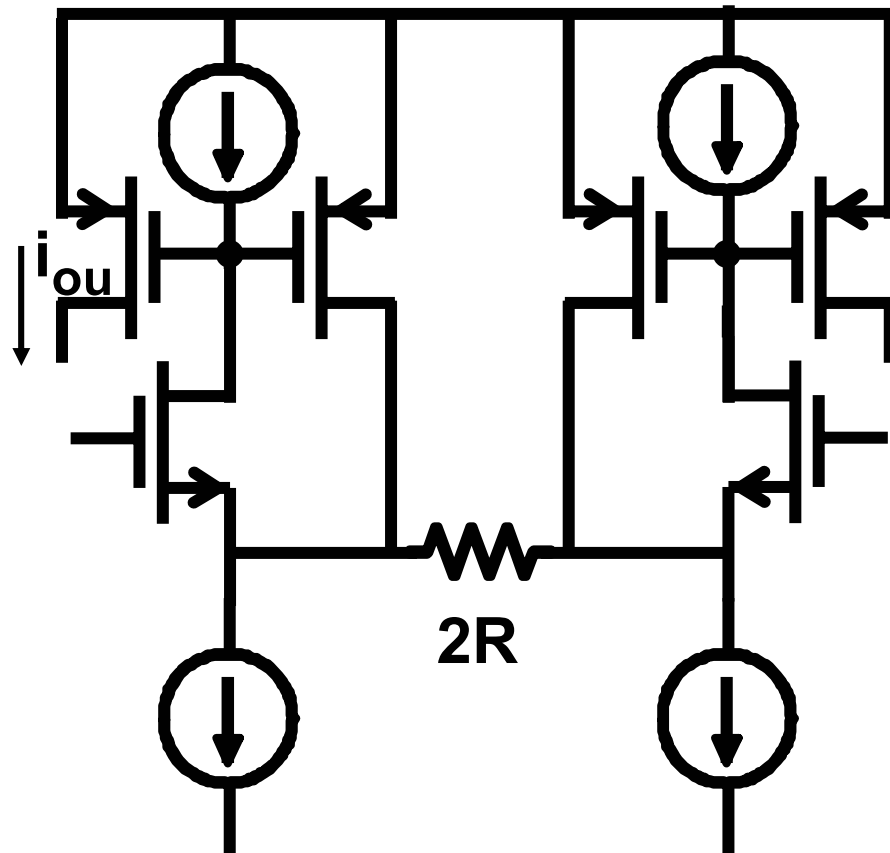


Additional local FB

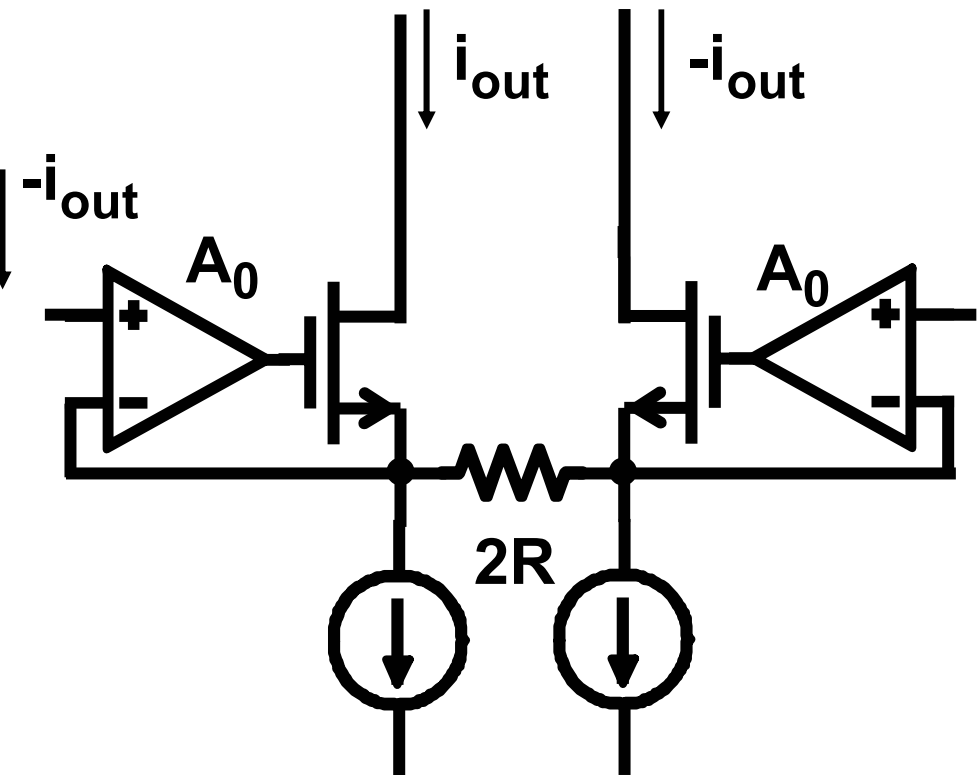

More FB with opamps


Low-pass filter

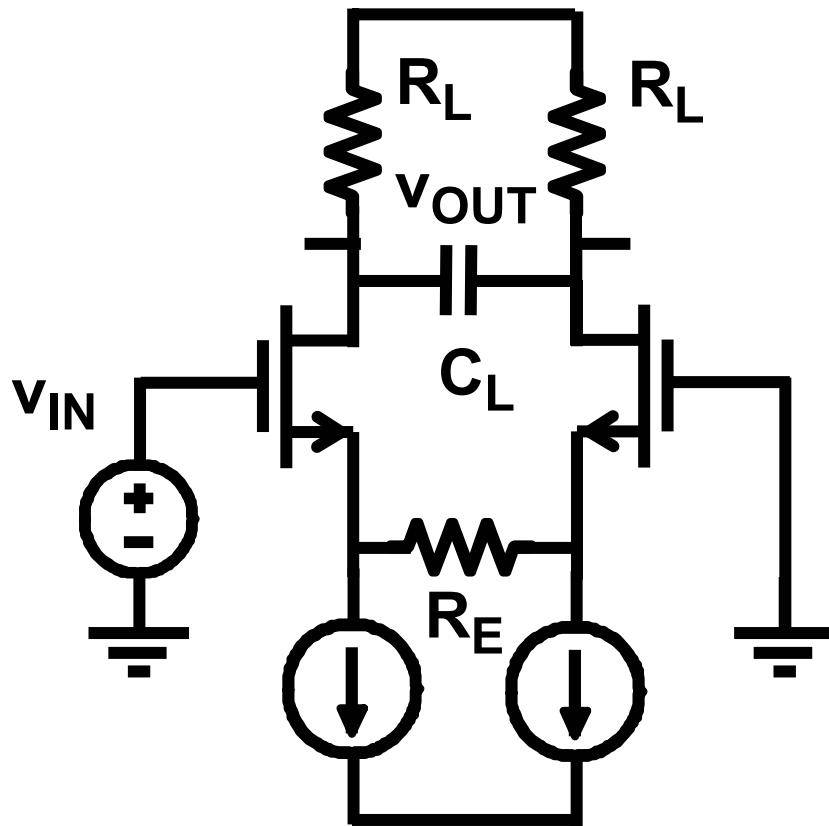



$$A_{v0} = 2 R_L / R_E$$

$$A_v = \frac{A_{v0}}{(1 + j \frac{f}{f_p})}$$

$$f_p = \frac{1}{2\pi 2R_L C_L}$$

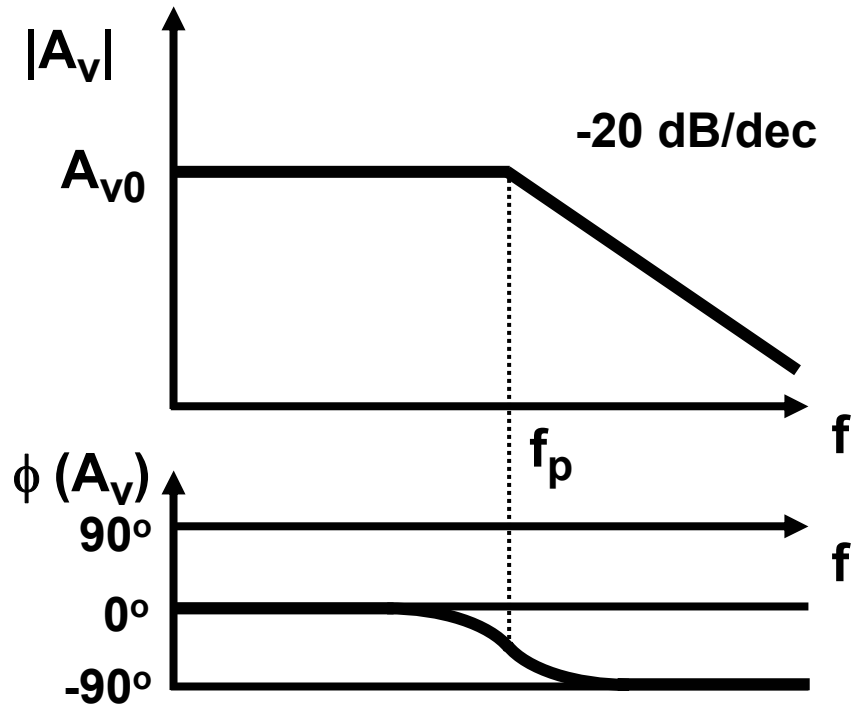

High-frequency booster

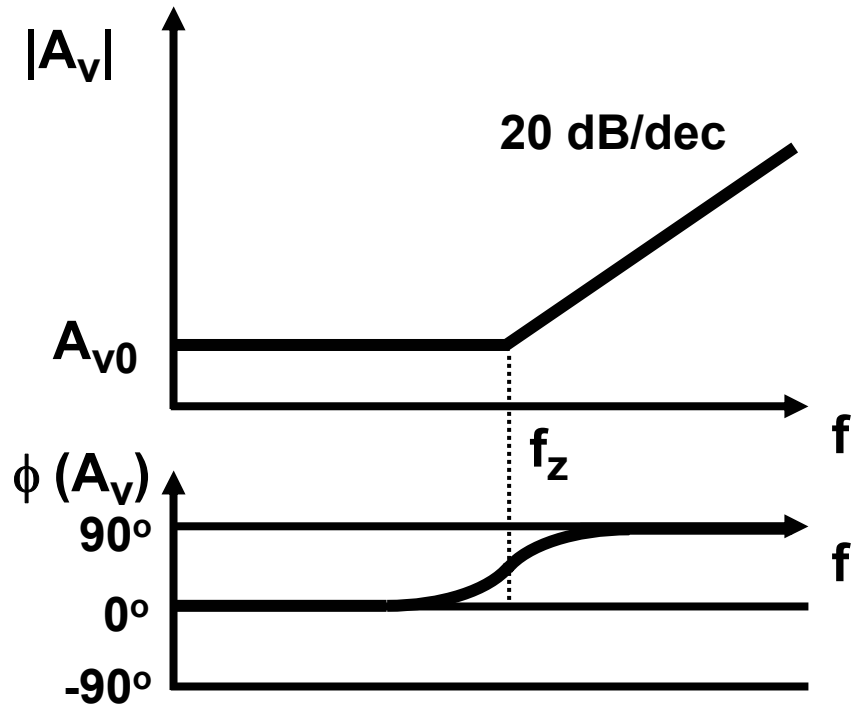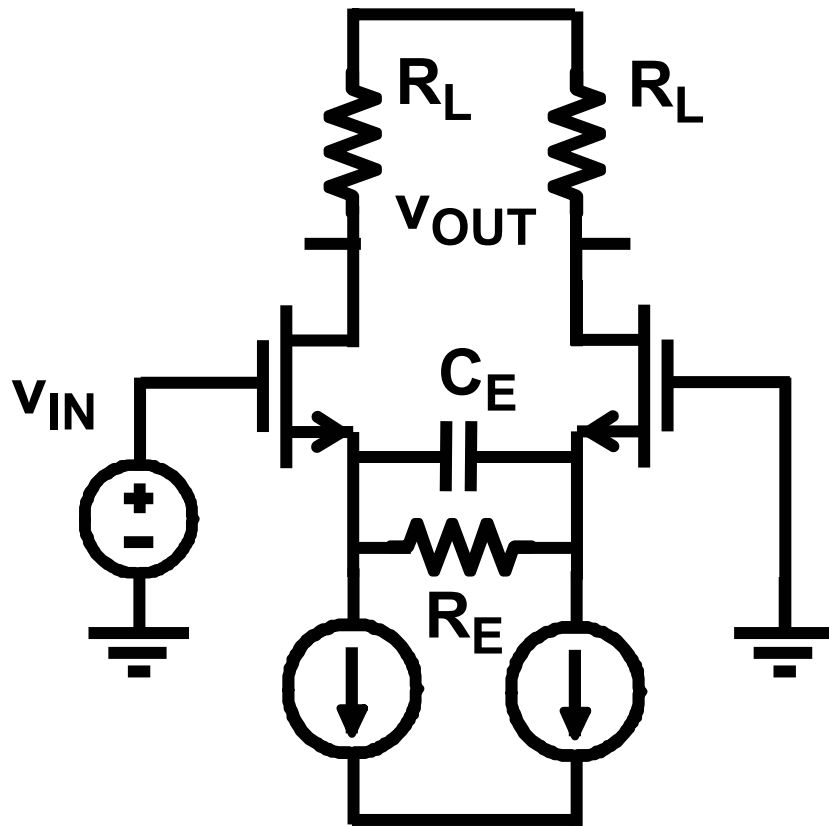


$$A_{V0} = 2 R_L / R_E$$

$$A_V = A_{V0} \left(1 + j \frac{f}{f_z} \right)$$

$$f_z = \frac{1}{2\pi R_E C_E}$$

Single-transistor FB with two outputs

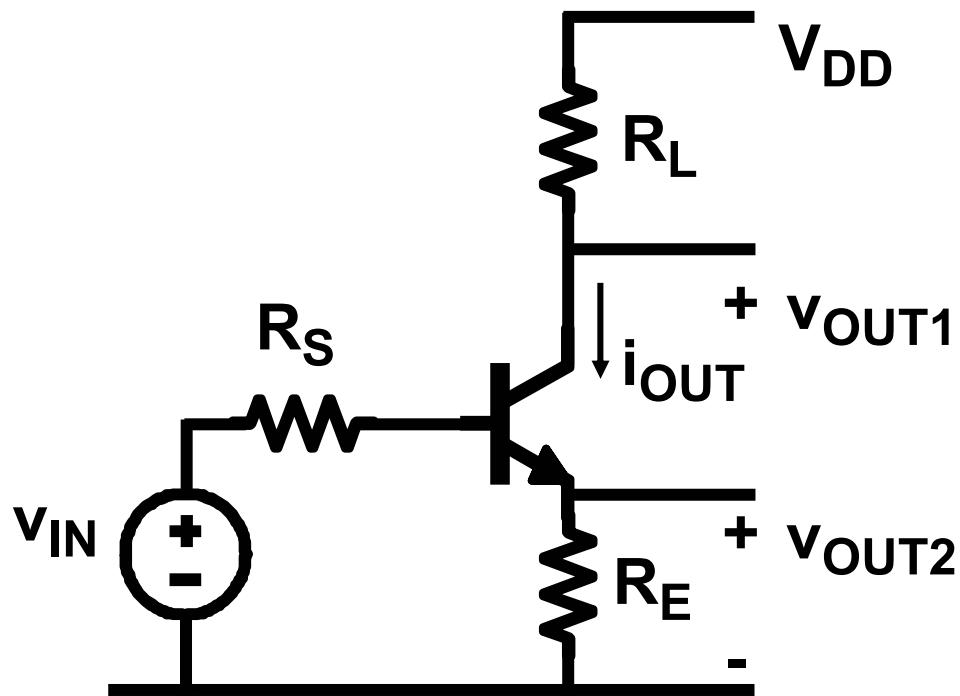

$$A_{v1} \approx -\frac{R_L}{R_E} \quad A_{v2} \approx 1$$

$$LG = g_m R_E \quad (>>1)$$

$$R_{IN} = r_\pi + \beta R_E$$

$$R_{OUT1} = R_L // r_{oL}$$

$$R_{OUT2} = 1/g_m + R_S/\beta$$

Output loading : $R_L \approx r_{oL}$ $r_{oL} = r_o (g_m R_E)$

Input loading : $R_S < R_{IN}$ $R_{IN} = r_\pi + \beta R_E$

Table of contents

- ◆ **Definitions**
- ◆ **Series-shunt FB for Voltage amplifiers.**
- ◆ **Series-series FB for Transconductance amps.**