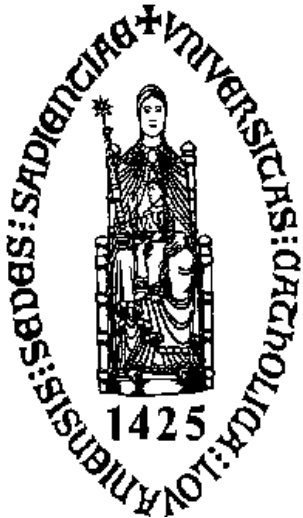

Low-power Sigma-Delta AD Converters



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be



Table of contents

♦ Delta-sigma modulation

- ♦ The switch problem
- ♦ The switched-opamp solution
- ♦ Other low-power Delta-sigma converters

Ref. Norsworthy, Delta-Sigma Converters, Wiley 1996


Ref. Op 't Eynde, Peluso, Geerts, Marquez, Geerts, Yao,
Kluwer/Springer

Sigma-Delta ADC


**Sigma-Delta ADC exchanges resolution with speed
by means of :**

Oversampling

Noise shaping

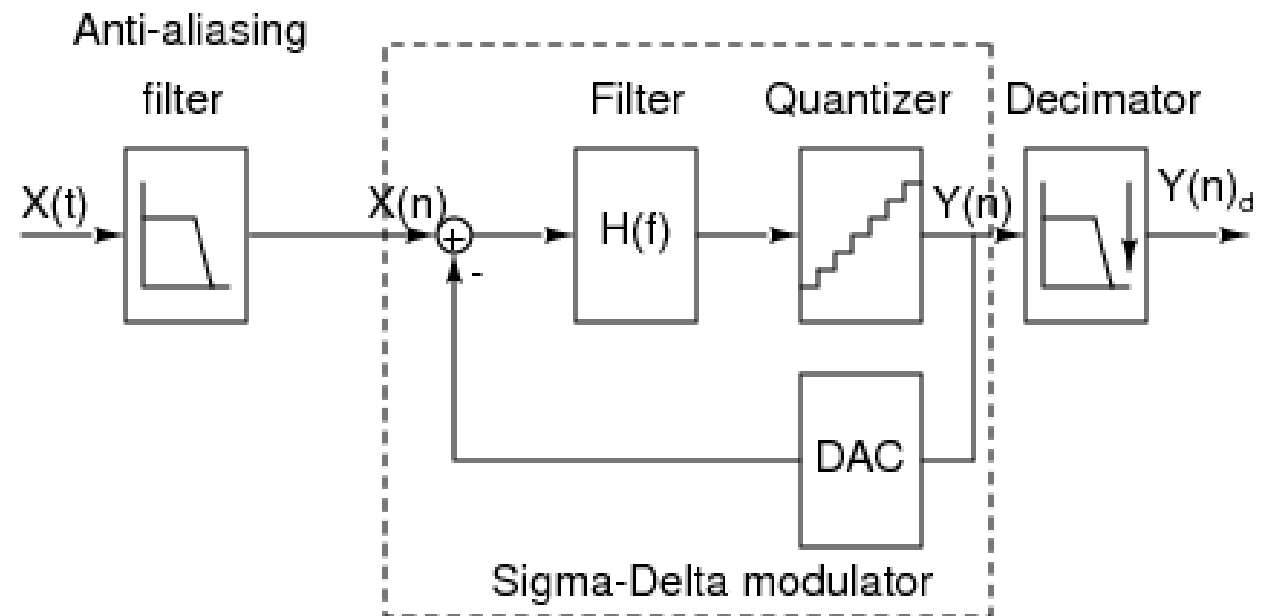

Quantization noise (4 bit)

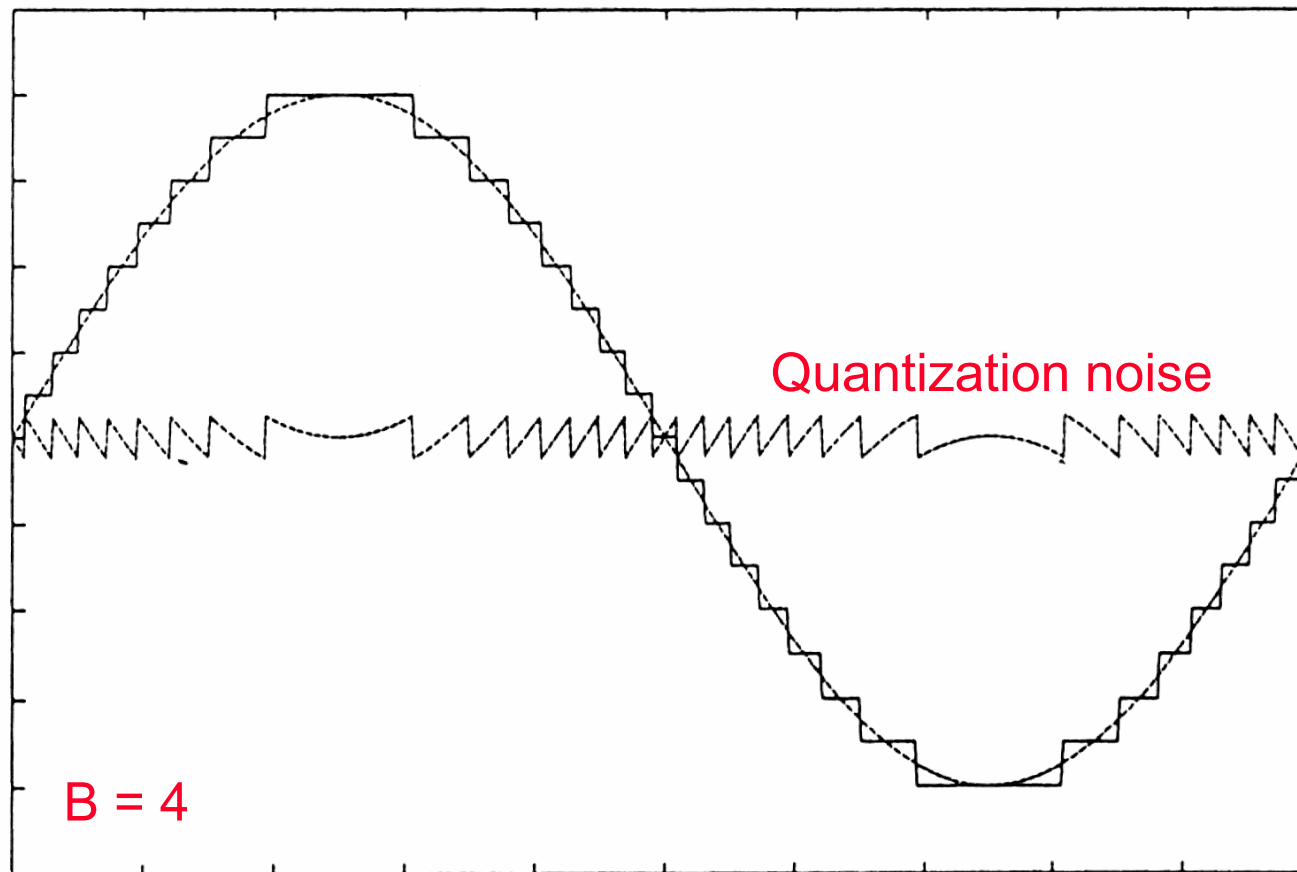

Number bits ↑
Quant. noise ↓


$$\text{Step} = \frac{V_{\text{ref}}}{2^B}$$

$B = 8$ bits
 $\text{SNR} = 50$ dB

$B = 16$ bits
 $\text{SNR} = 98$ dB

$$\text{SNR} \approx 2 + 6B$$


Sigma-Delta modulator

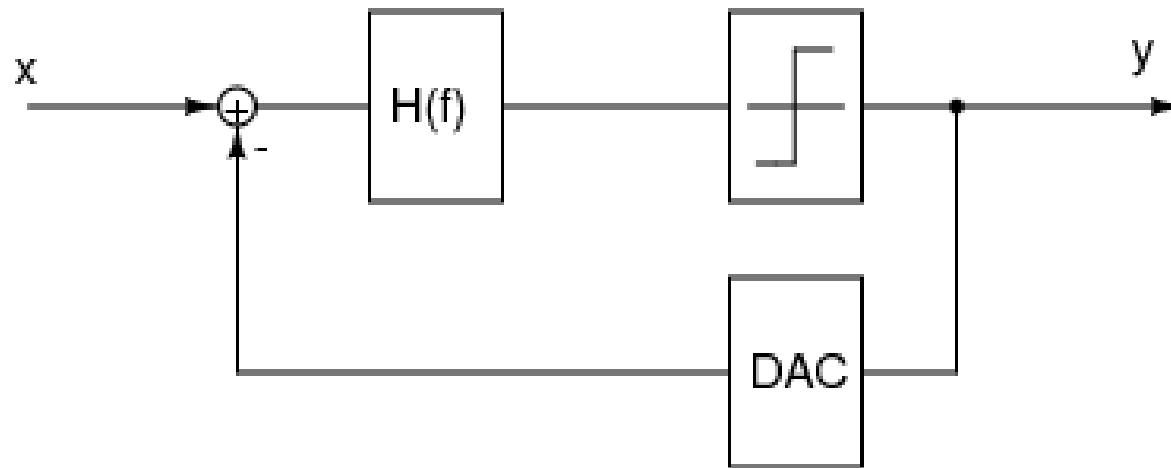

Signal transfer function: $H_x(z) = \frac{H(z)}{1 + H(z)}$

Noise transfer function: $H_e(z) = \frac{1}{1 + H(z)}$

Noise filtering

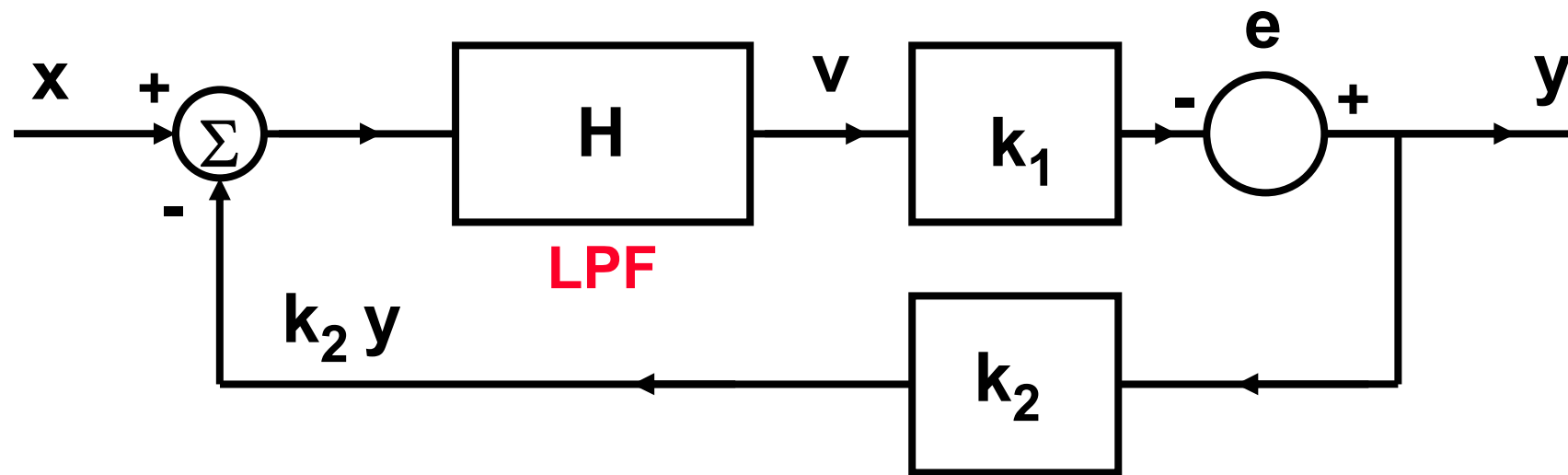


$$v = H (x - k_2 y)$$

$$y = k_1 v + e$$

Noise shaping

$$y = \frac{k_1 H}{1 + k_1 k_2 H} x + \frac{1}{1 + k_1 k_2 H} e \approx \frac{1}{k_2} x + \frac{1}{k_1 k_2 H} e$$


Feedback loop with low-pass filter

 


$$y \approx \frac{1}{k_2} x + \frac{1}{k_1 k_2 H} e$$

Noise shaping


Higher-order Sigma-delta converters

 

(a) Second order structure

 


(b) Third order structure

 


(c) Fourth order structure


Mash Sigma-delta topologies (2-1-1)

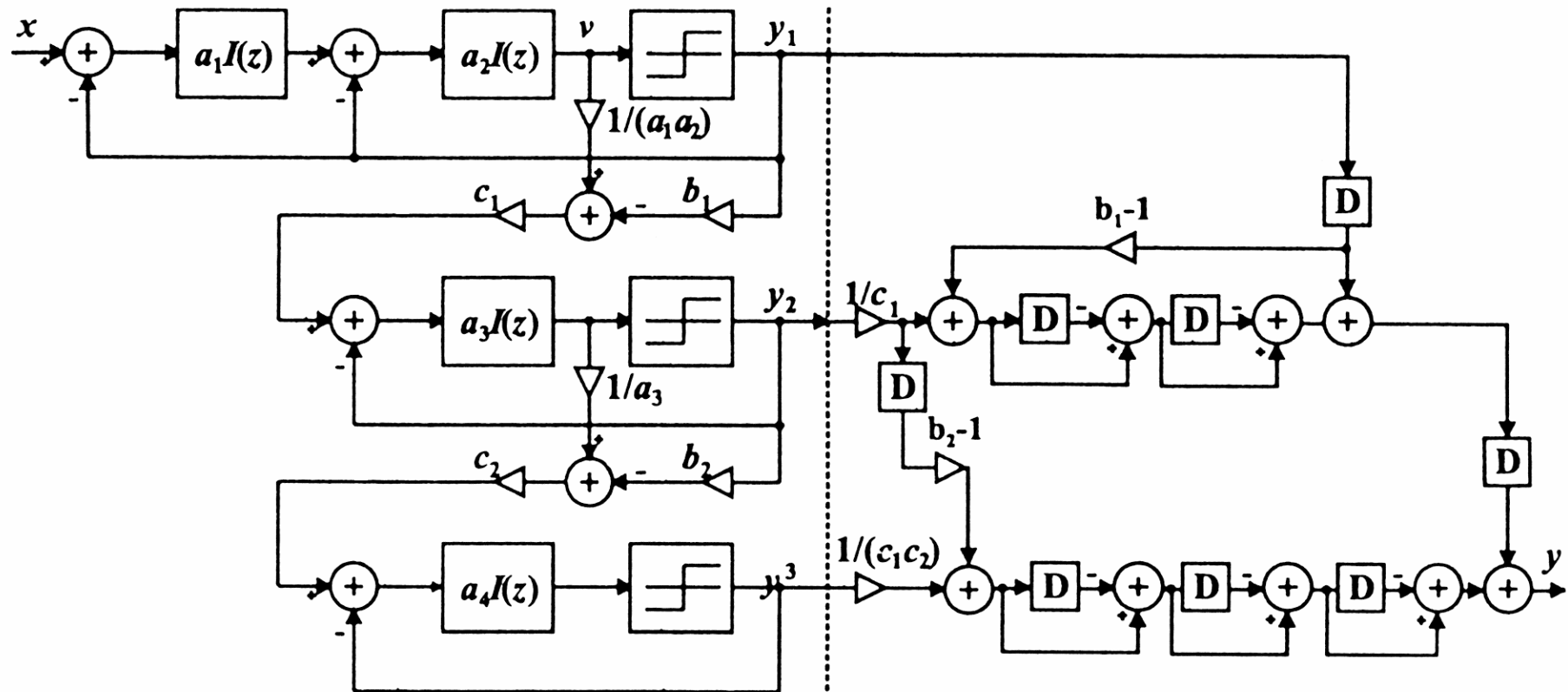

SNR vs OSR for single-bit $\Sigma\Delta$

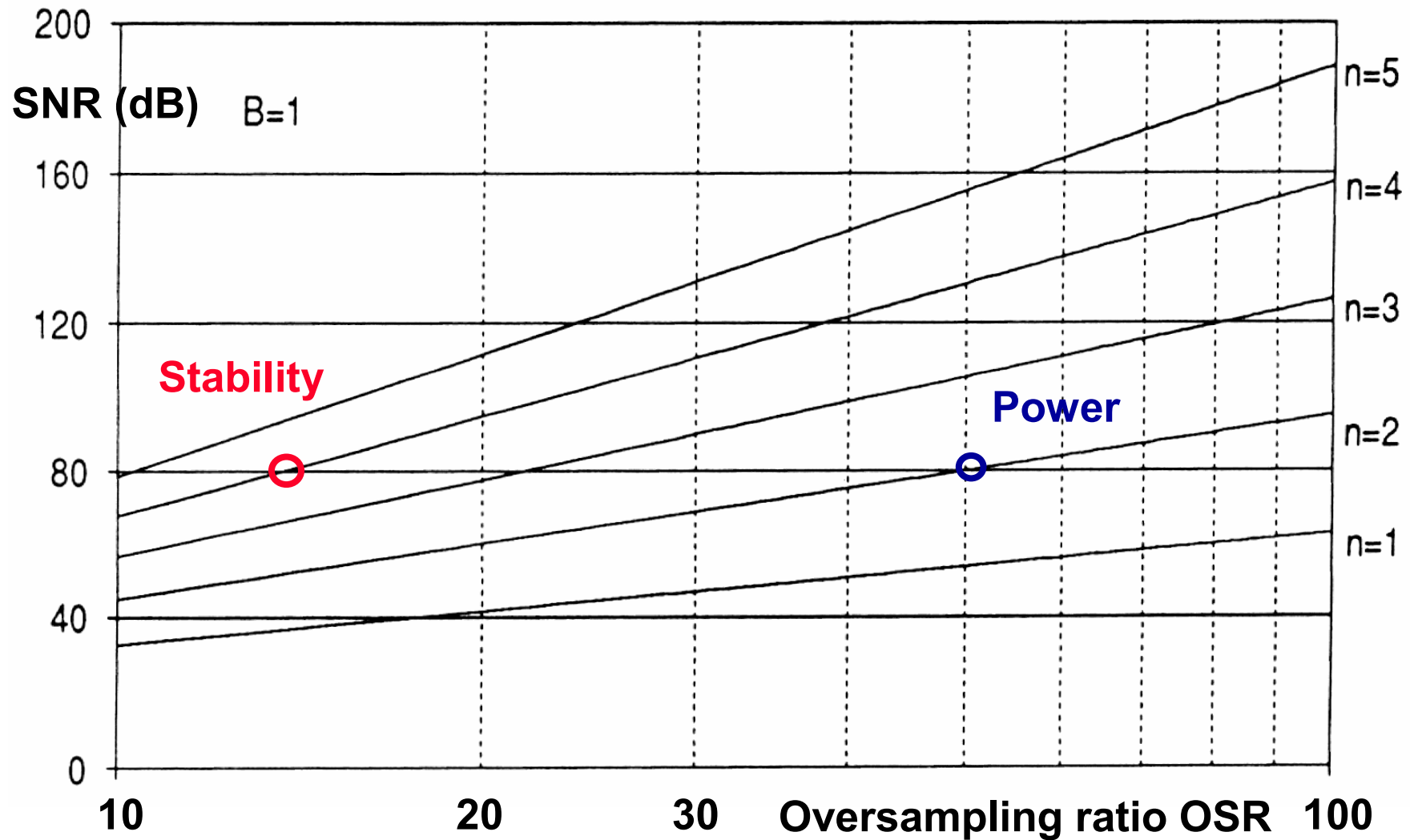

Multibit versus Single-bit

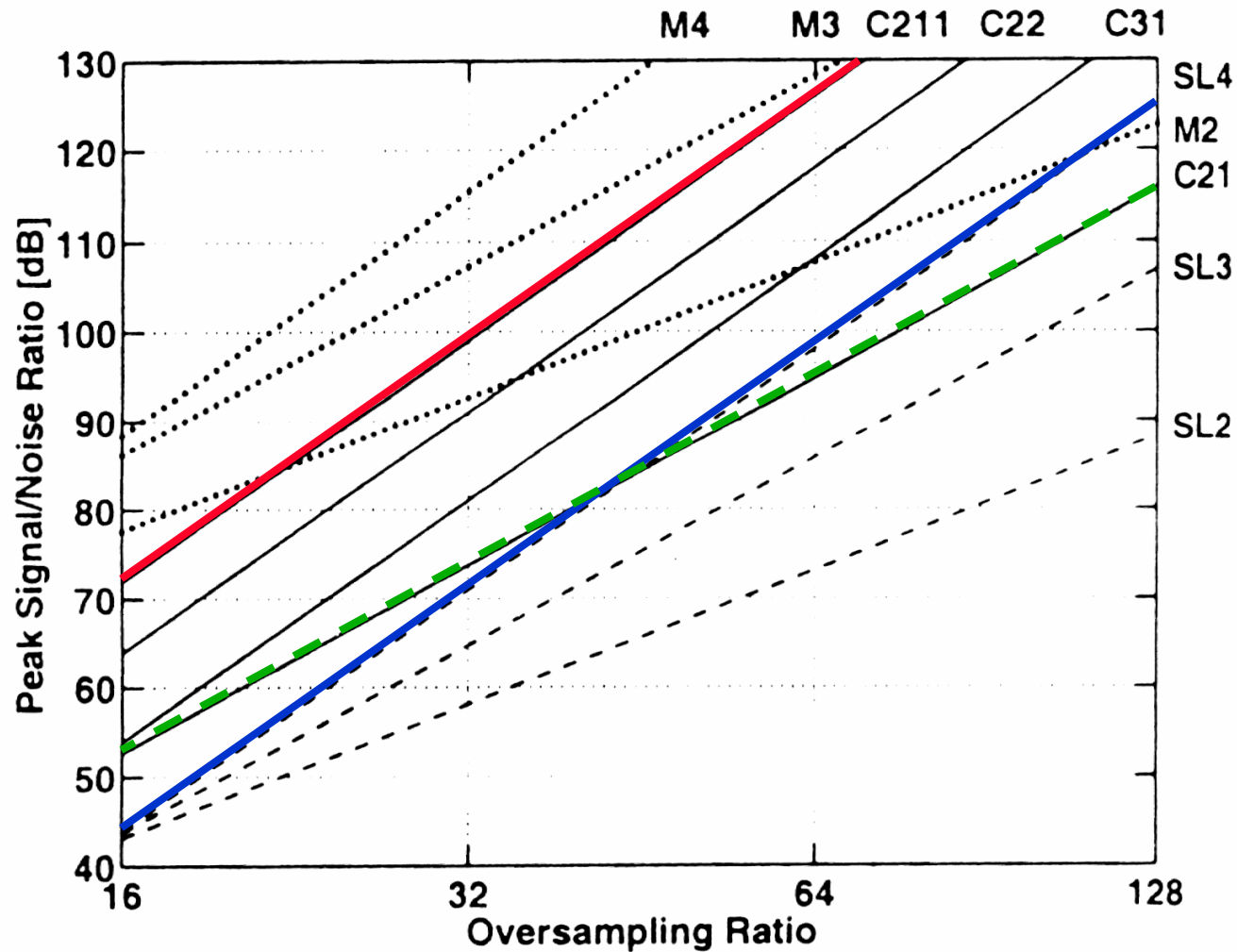

Cascaded 2-1-1

Single loop 4th

Cascaded 2-1

Multibit (4 bit)

**Ref. Marquez
CAS Sept 98,
1232-1241**

Table of contents

- ♦ **Delta-sigma modulation**


- ♦ **The switch problem**

- ♦ **The switched-opamp solution**

- ♦ **Other low-power Delta-sigma converters**

Low Voltage SC: problem

Switch:

 



nMOS: $V_{in} < V_{DD} - V_{GSn} \approx V_{DD} - 0.8 \text{ V}$

pMOS: $V_{in} > V_{GSp} \approx 0.8 \text{ V}$


Limit : $V_{DD} - V_{GSn} = V_{GSp}$

→ $V_{DDmin} > 1.6 \text{ V}$

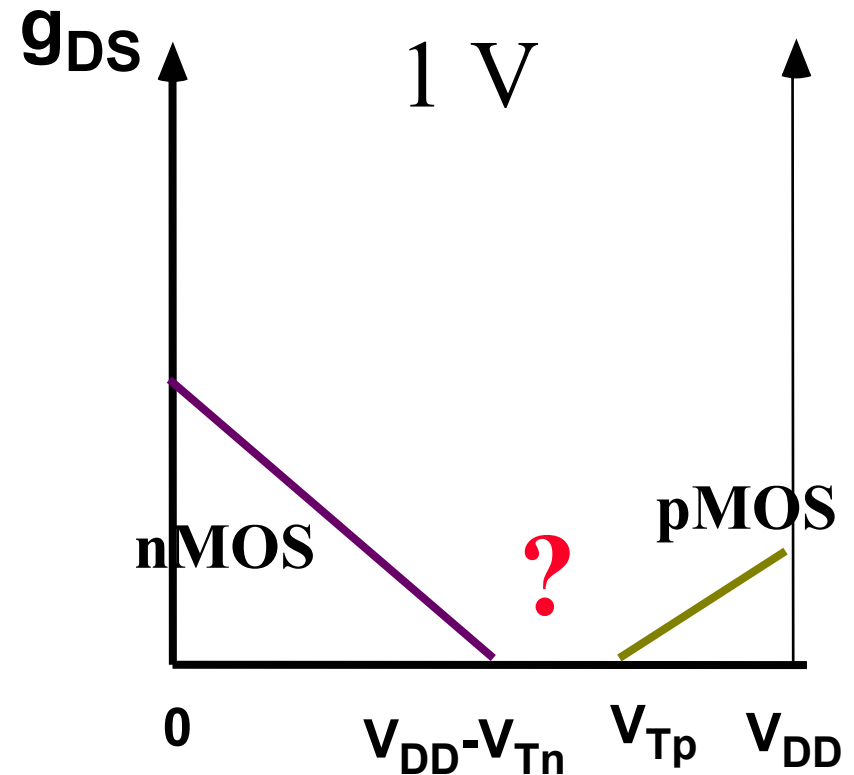 
Low Voltage switch : g_{DS} versus input voltage



Low Voltage switch : ON- resistance

 

$V_{DD} = 5\text{ V}$

 

$V_{DD} = 1.8\text{ V}$


Low Voltage SC: solutions

- ♦ **Low V_T technology**
 - special technology : cost
 - switch-off leakage
- ♦ **On-Chip voltage multipliers**
 - poor power efficiency
 - applicability in submicron technologies ?
- ♦ **Switched Opamp** Ref.Crols, ESSCIRC 93, JSSC Aug.94

Smaller V_{DD} require smaller V_T

Smaller V_T is not possible because

 
- 1. Leakage : wi curve crosses axis !
Minimum value : 0.3 V**
- 2. Temperature variations : + 0.2 V**
- 3. Mismatch : + 0.1 V**



>>> V_T cannot be smaller than 0.3 ... 0.4 V

On-chip voltage multipliers

Dickson, ...,
JSSC June 76,
pp.374-378

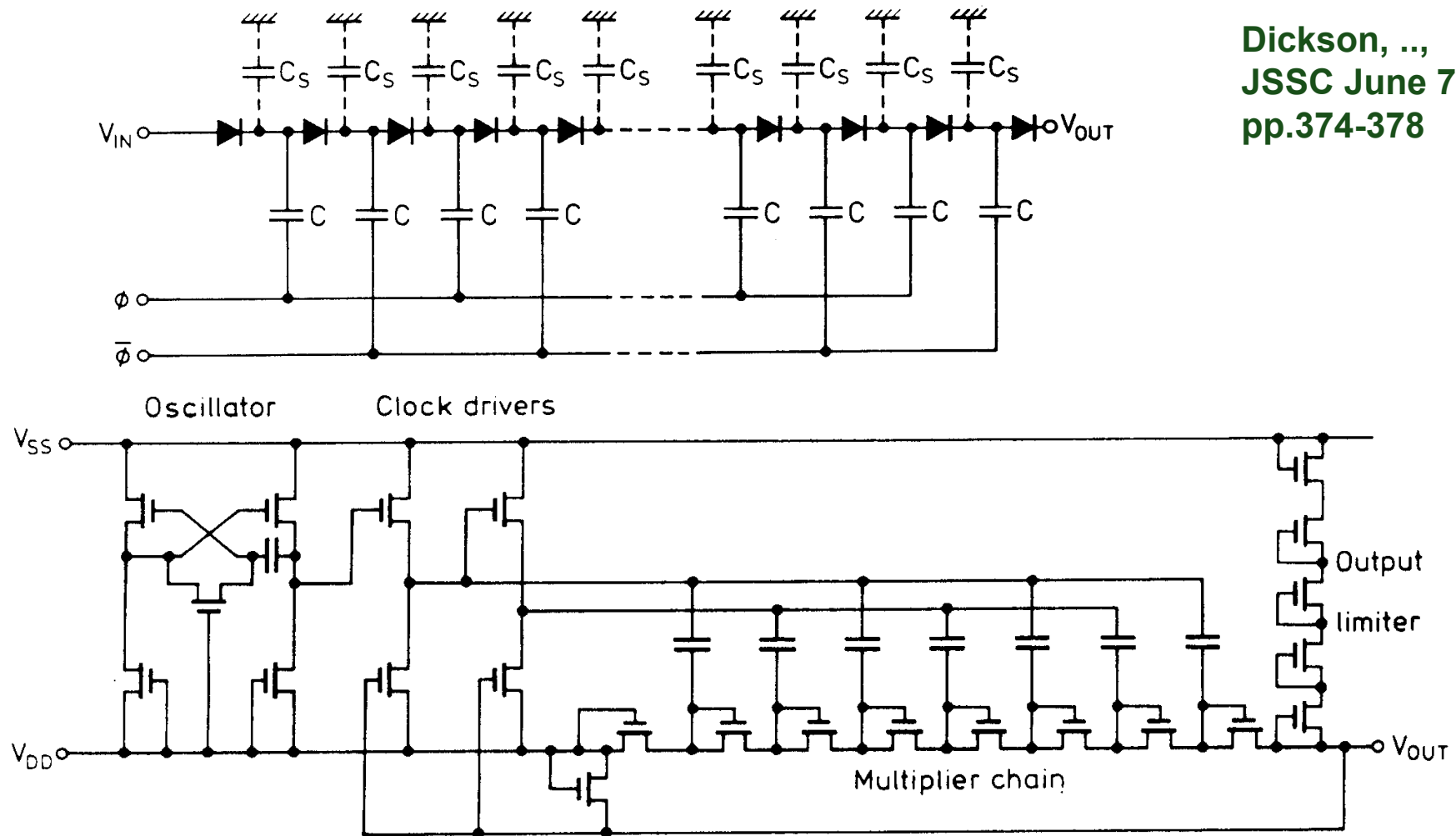

Voltage multipliers : power efficiency

$$P_{\text{loss}} \approx R_{\text{eq}} I_{\text{out}}^2$$


$$P_{\text{VDD}} \approx I_{\text{out}} V_{\text{DD}} \quad \eta \approx 1 - \frac{R_{\text{eq}} I_{\text{out}}}{V_{\text{DD}}} \approx 50 \%$$

$$R_{\text{eq}} \approx \frac{n}{fC} \frac{1}{\tan(2f R_{\text{on,sw}} C)}$$

Drawbacks of voltage multipliers

- ♦ **High voltage technology:**
 - In deep submicron : $V_{DD} < 1.8 \text{ V}$ in $0.18 \text{ } \mu\text{m}$ CMOS
 - Oxide cannot take more !! $800 \text{ V}/\mu\text{m}$ or $0.8 \text{ V}/\text{nm}$
- ♦ **Requires high-speed clock drivers**
- ♦ **Injection in substrate : coupling to Analog**
- ♦ **Low power-efficiency**

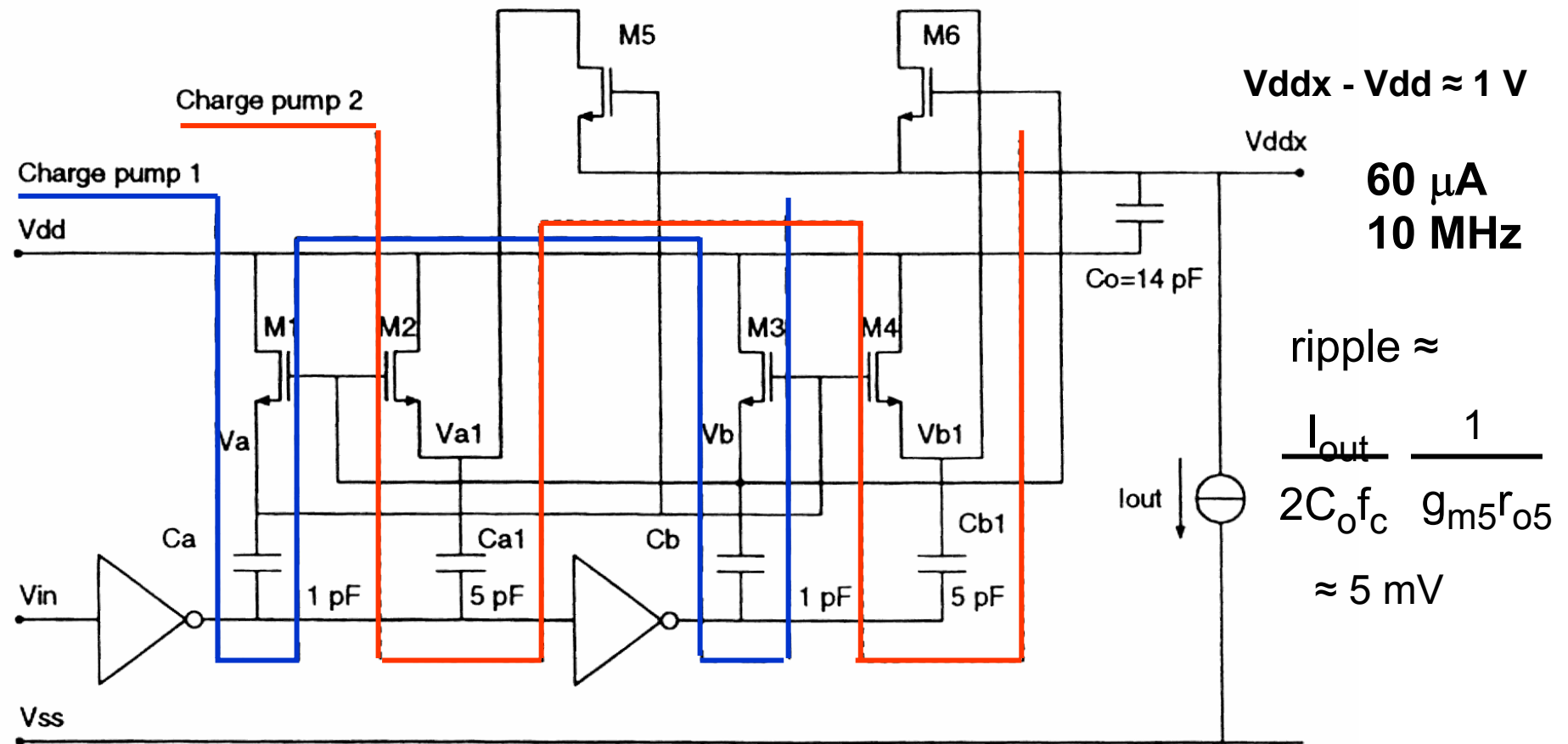Voltage multiplier for rail-to-rail opamp




Duisters, ..., JSSC July 98, pp.947-955

Table of contents


- ♦ **Delta-sigma modulation**
- ♦ **The switch problem**
- ♦ **The switched-opamp solution**
 - **Principle : Switched-opamp filter**
 - Improved switching
 - 0.9 V - 40 μ W 12 bit CMOS SO $\Sigma\Delta$
- ♦ **Other low-power Delta-sigma converters**

Conventional SC Integrator

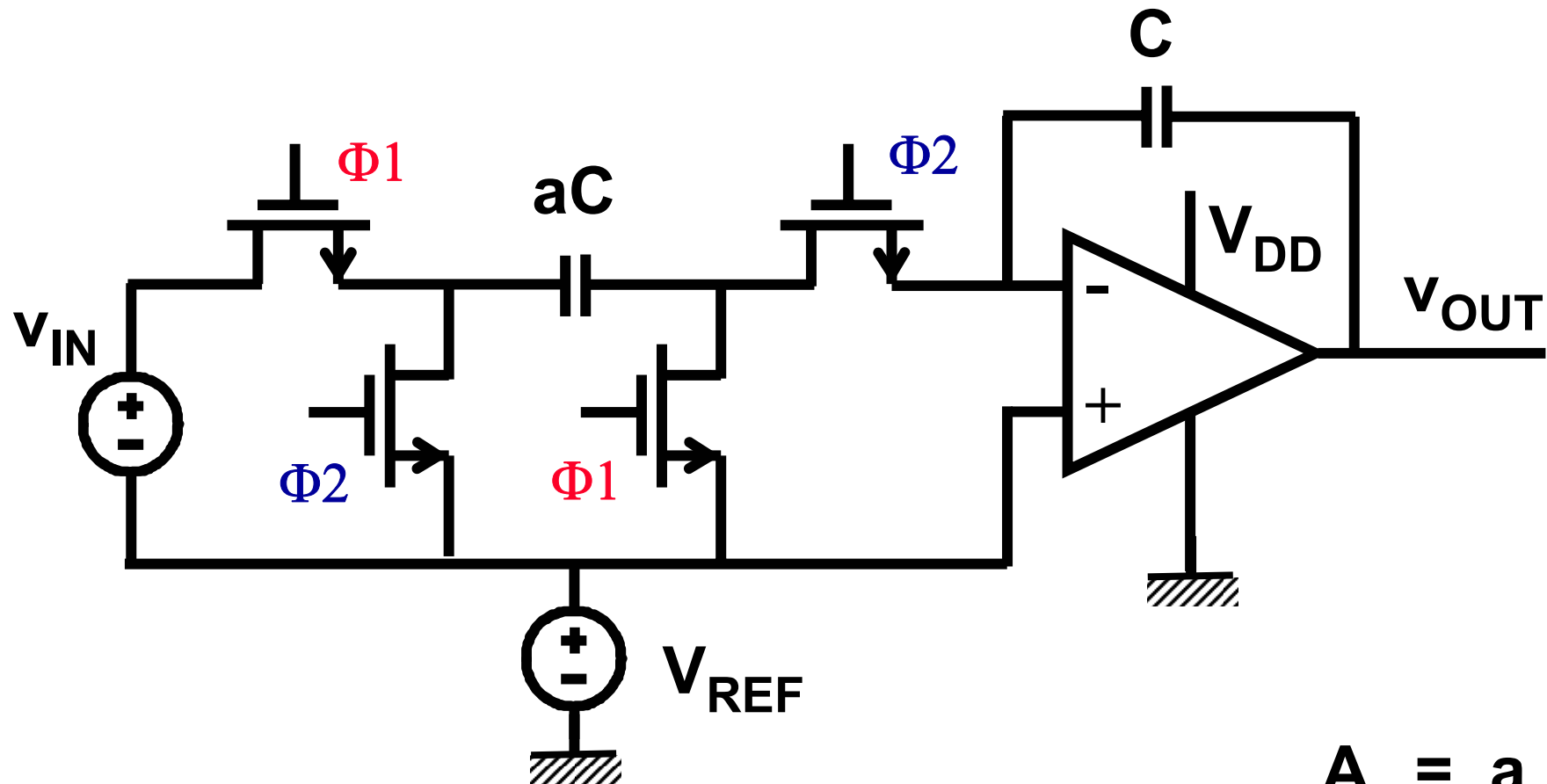


Switched Opamp

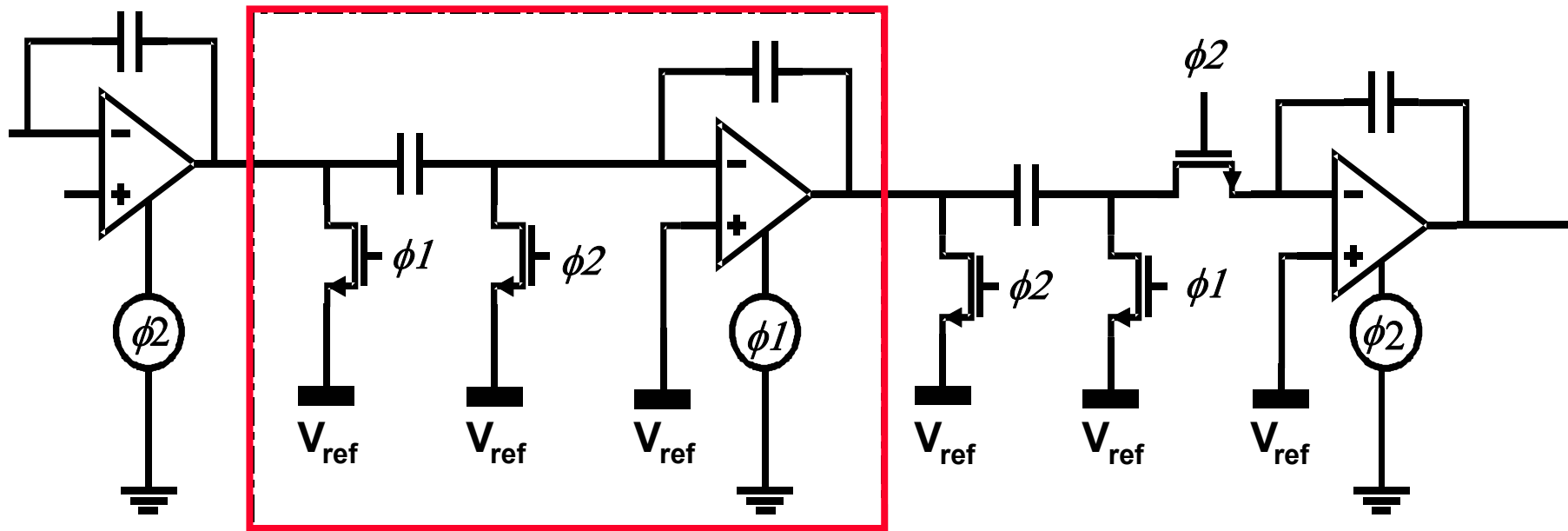**Critical input switch
is replaced by a switched opamp**




Crols, .., JSSC Aug.94, 936-942

Switched-opamp schematic

 


Crols, .., JSSC Aug.94, 936-942

Switched-Opamp response

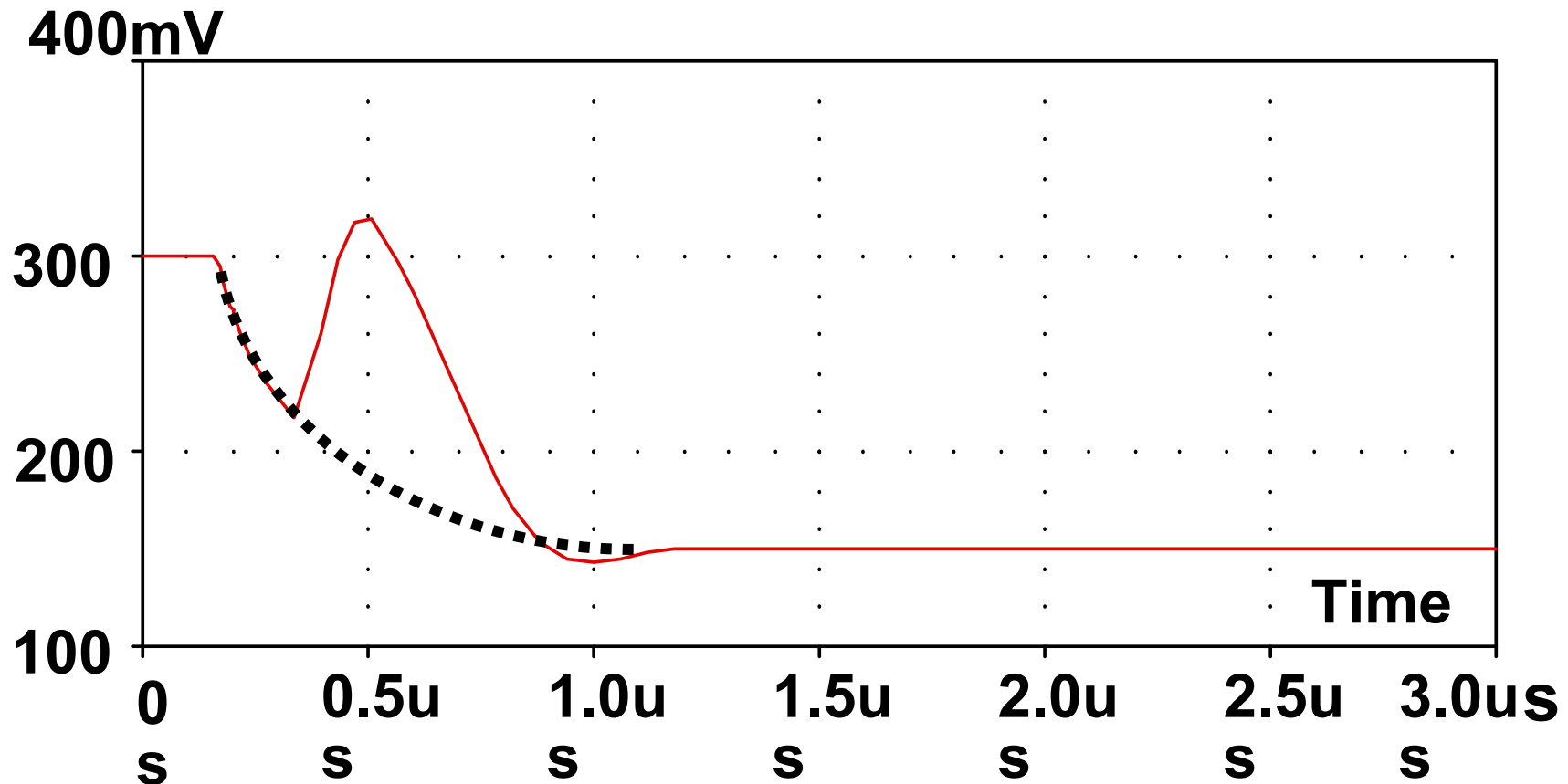

Switched-opamp low-pass biquad

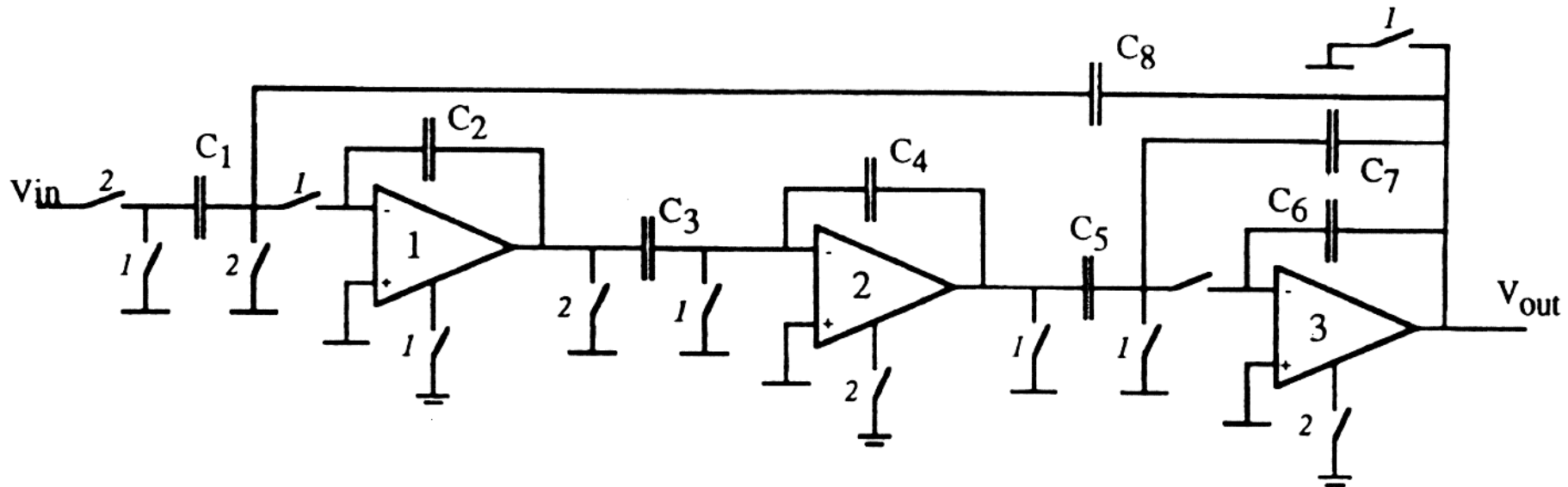

One extra opamp per biquad


$$V_{DD} > V_{GS} + V_{\text{signal}}$$

$$1.2 \text{ V} + 0.3 \text{ V} = 1.5 \text{ V} \quad (0.6 \text{ V}_{\text{ptp}})$$


Standard 2.4 μm CMOS ($V_{Tn} \approx V_{Tp} \approx 0.9 \text{ V}$)

Crols, ..., JSSC
Aug.94, 936-942

Measured transfer characteristic

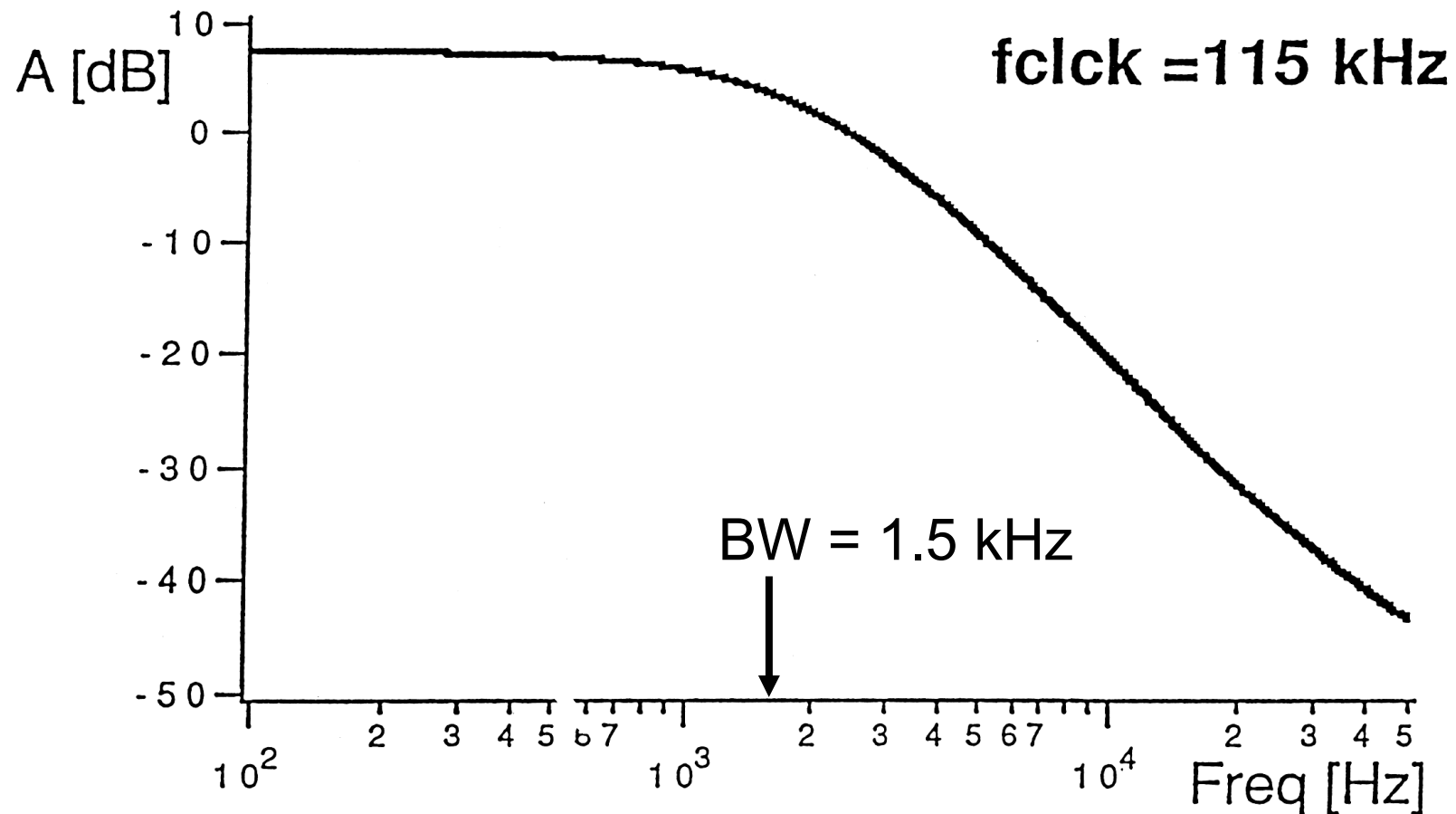

THD versus input signal swing

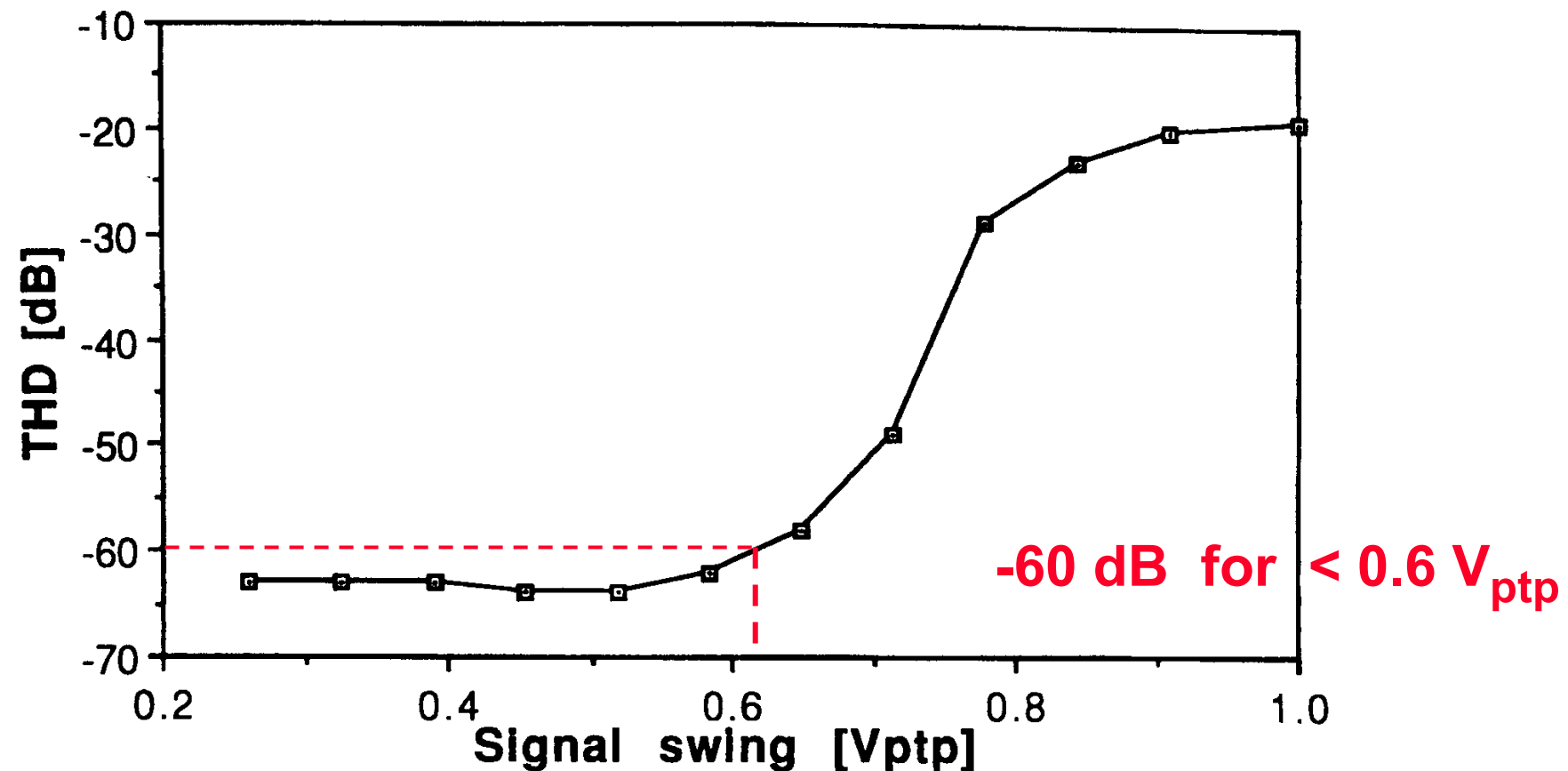


Input noise $140 \mu V_{RMS}$: DR > 70 dB

Crols, .., JSSC
Aug.94, 936-942

Table of contents

- ◆ **Delta-sigma modulation**
- ◆ **The switch problem**
- ◆ **The switched-opamp solution**
 - Principle : Switched opamp filter
 - Improved switching
 - 0.9 V - 40 μ W 12 bit CMOS SO $\Sigma\Delta$
- ◆ **Other low-power Delta-sigma converters**

1 Volt OTA

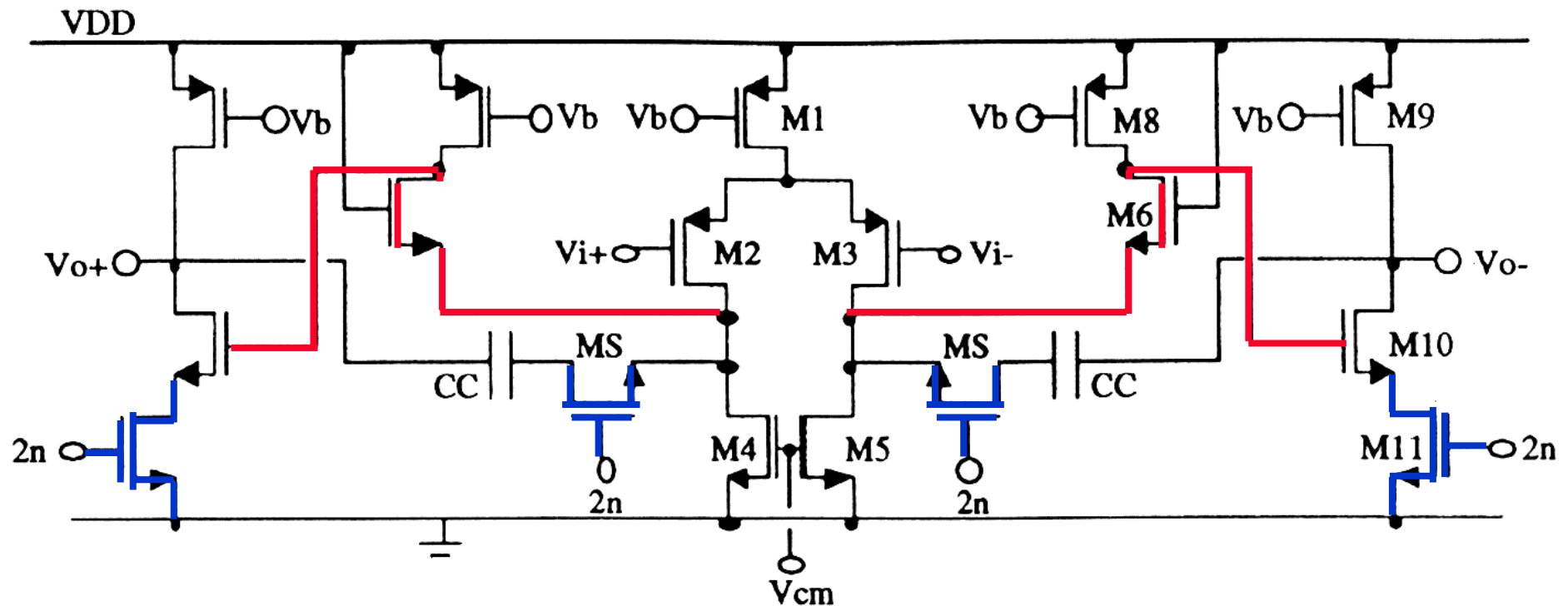


1 V (min: $V_T + 2V_{DSsat}$)
 Fully differential : 75 dB
 30 MHz 1 pF 80 μ A
 < 100 ns

4 Switches 2n :
 Only 2nd stage switched off !

Baschirotto, .. JSSC Dec.97, pp.1979-1986

SO SC integrator

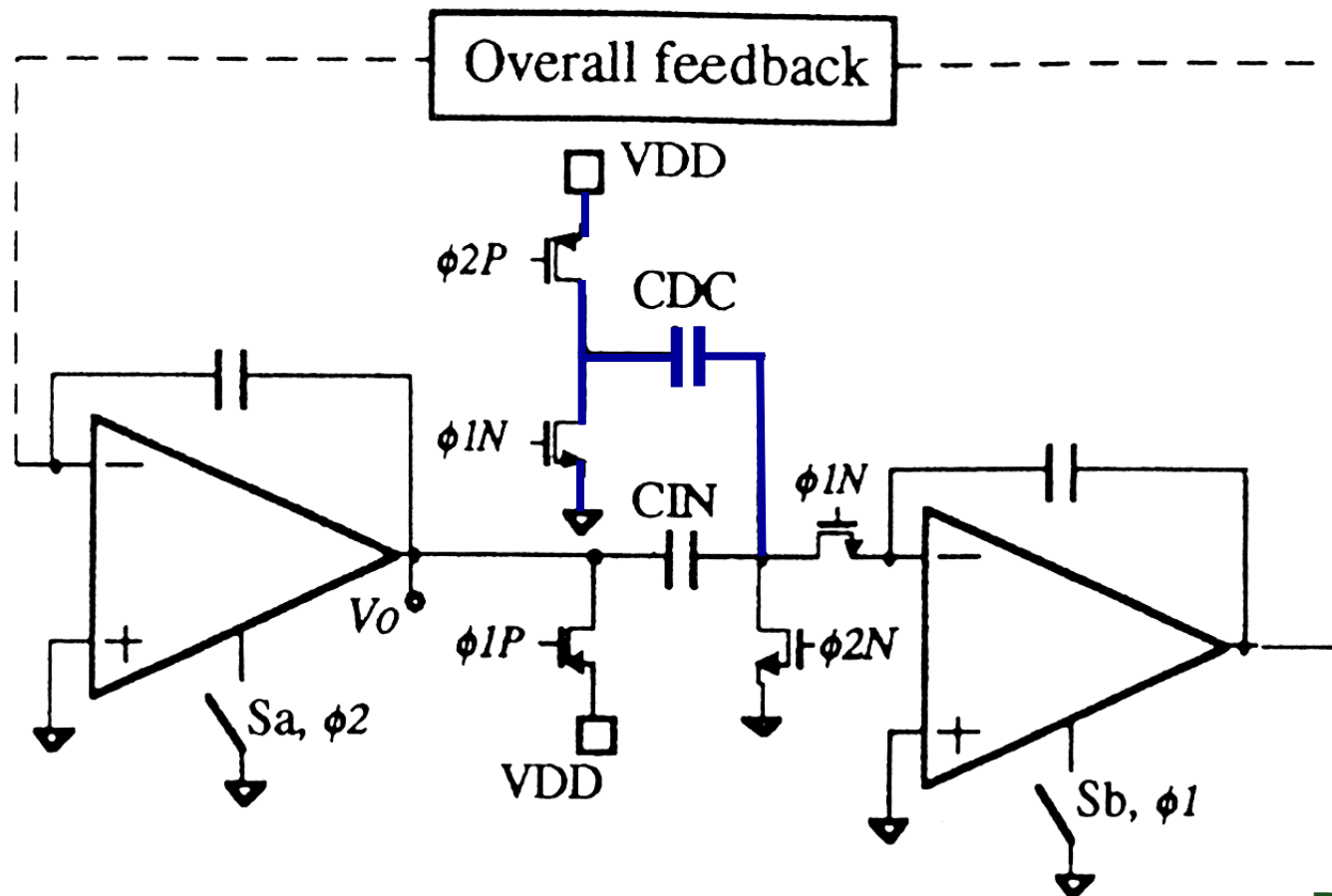


**CDC for
level shift :
CDC= CIN**


$$V_{O,DC} = V_{DD}/2$$

**Baschirotto, .. JSSC
Dec.97, pp.1979-1986**

SO SC integrator : $\Phi 1$ closed

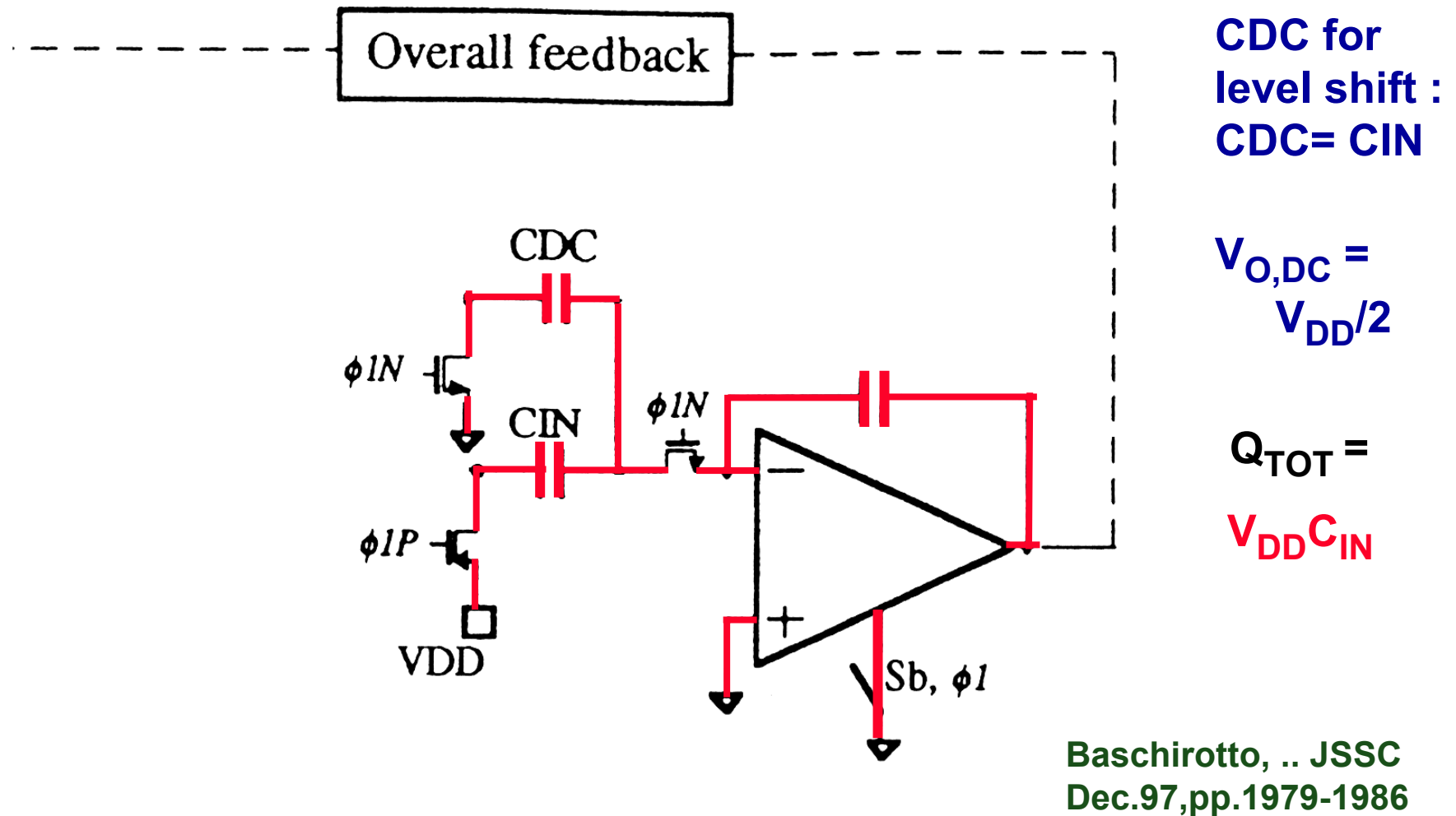

SO SC integrator : $\Phi 2$ closed

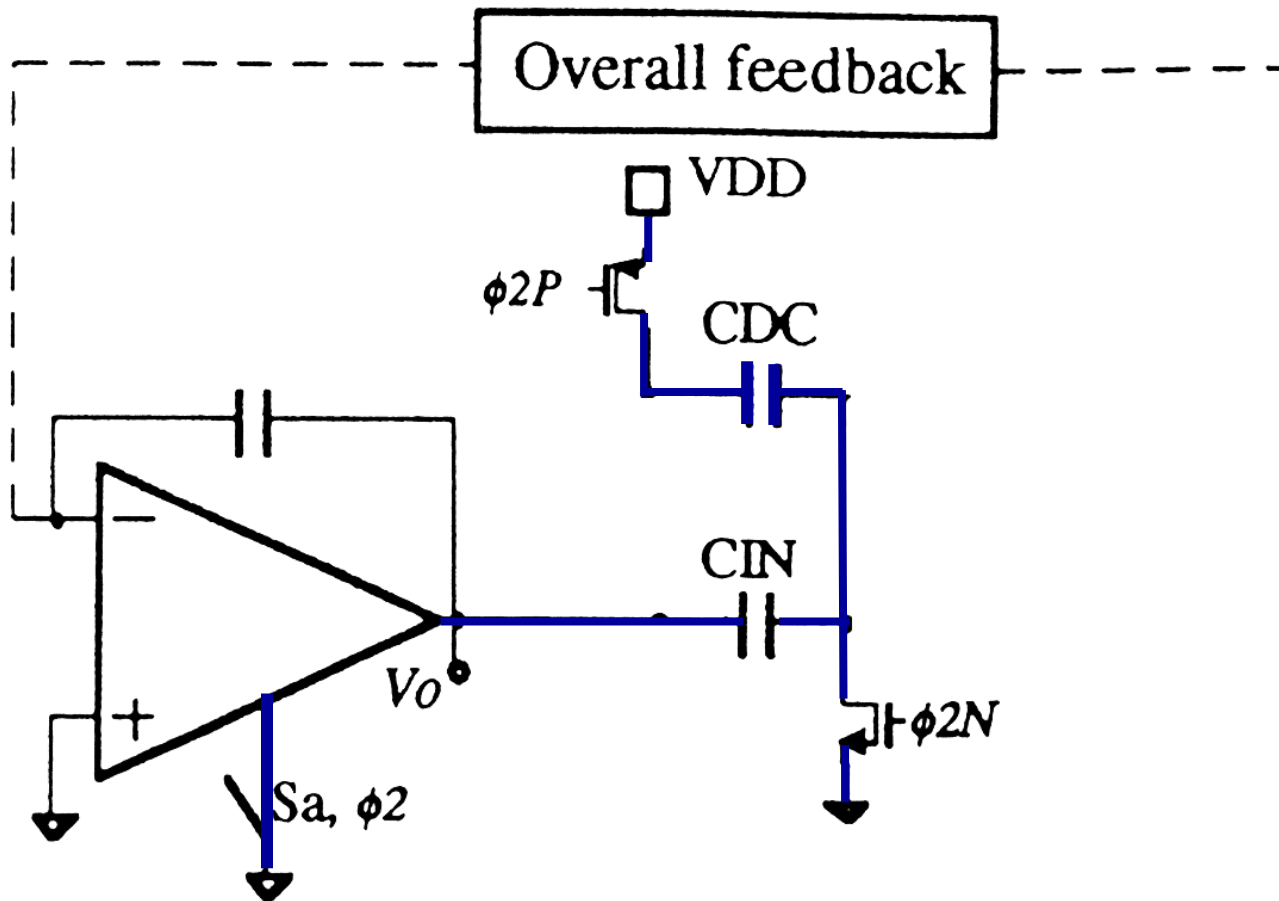

CDC for
level shift :
 $C_{DC} = C_{IN}$

$$V_{O,DC} = V_{DD}/2$$


$$Q_{TOT} = V_{DD}C_{DC} + V_OC_{IN}$$

if $C_{DC} = C_{IN}$

$$V_{DD}/2 = V_O$$

Baschirotto, .. JSSC
Dec.97, pp.1979-1986

CMFB with level shifting

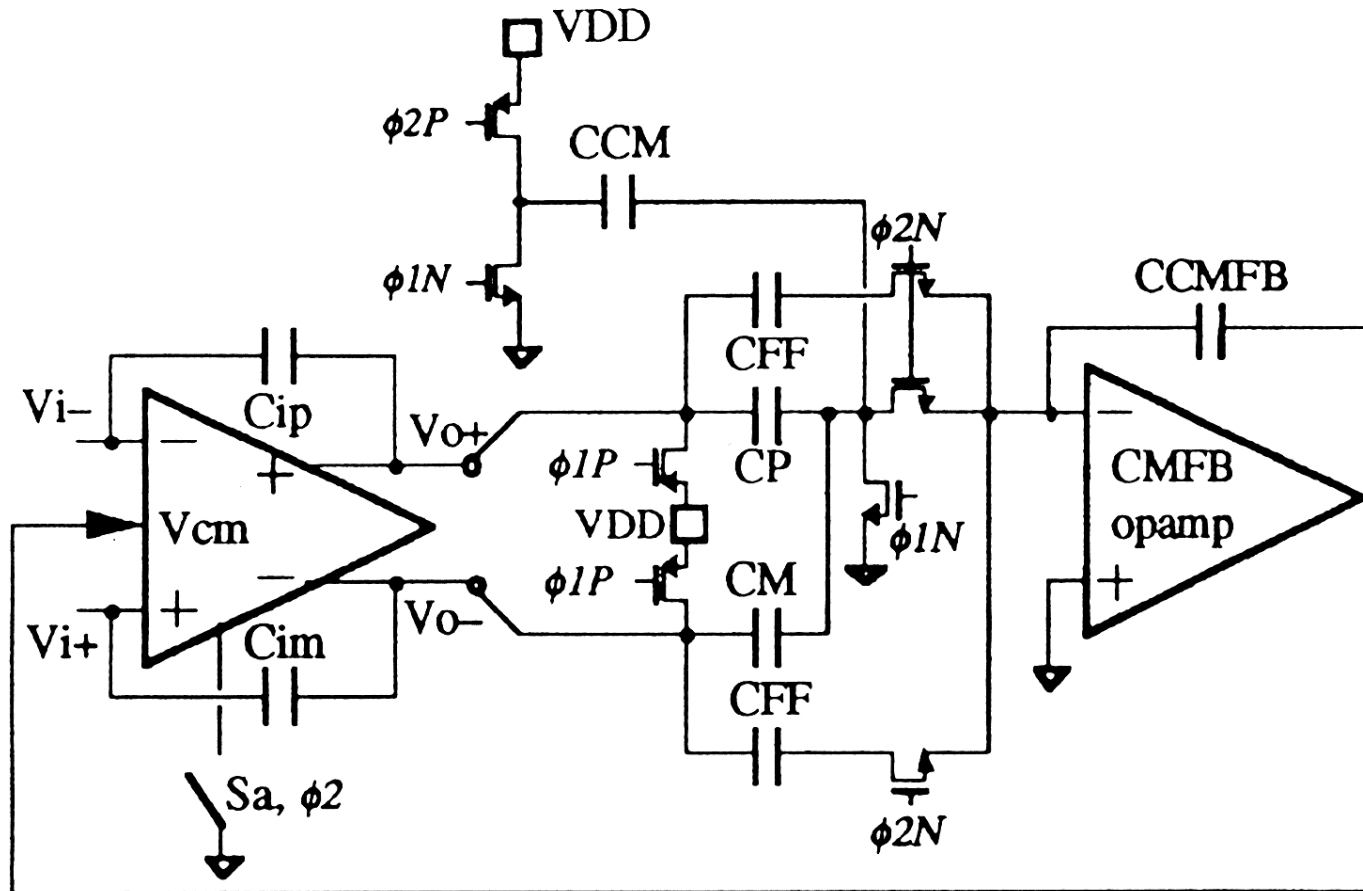

$$C_M = C_P = 0.1 \text{ pF}$$

$$C_{CM} = 0.1 \text{ pF}$$

$$C_{CMFB} = 2 \text{ pF}$$

$$C_{FF} = 0.1 \text{ pF}$$


provides zero

$$V_{OUT,DC} = V_{DD}/2$$

Table of contents

- ♦ **Delta-sigma modulation**
- ♦ **The switch problem**
- ♦ **The switched-opamp solution**
 - **Principle : Switched opamp filter**
 - **Improved switching**
 - **0.9 V - 40 μ W 12 bit CMOS SO $\Sigma\Delta$**
- ♦ **Other low-power Delta-sigma converters**

Differential SO integrator

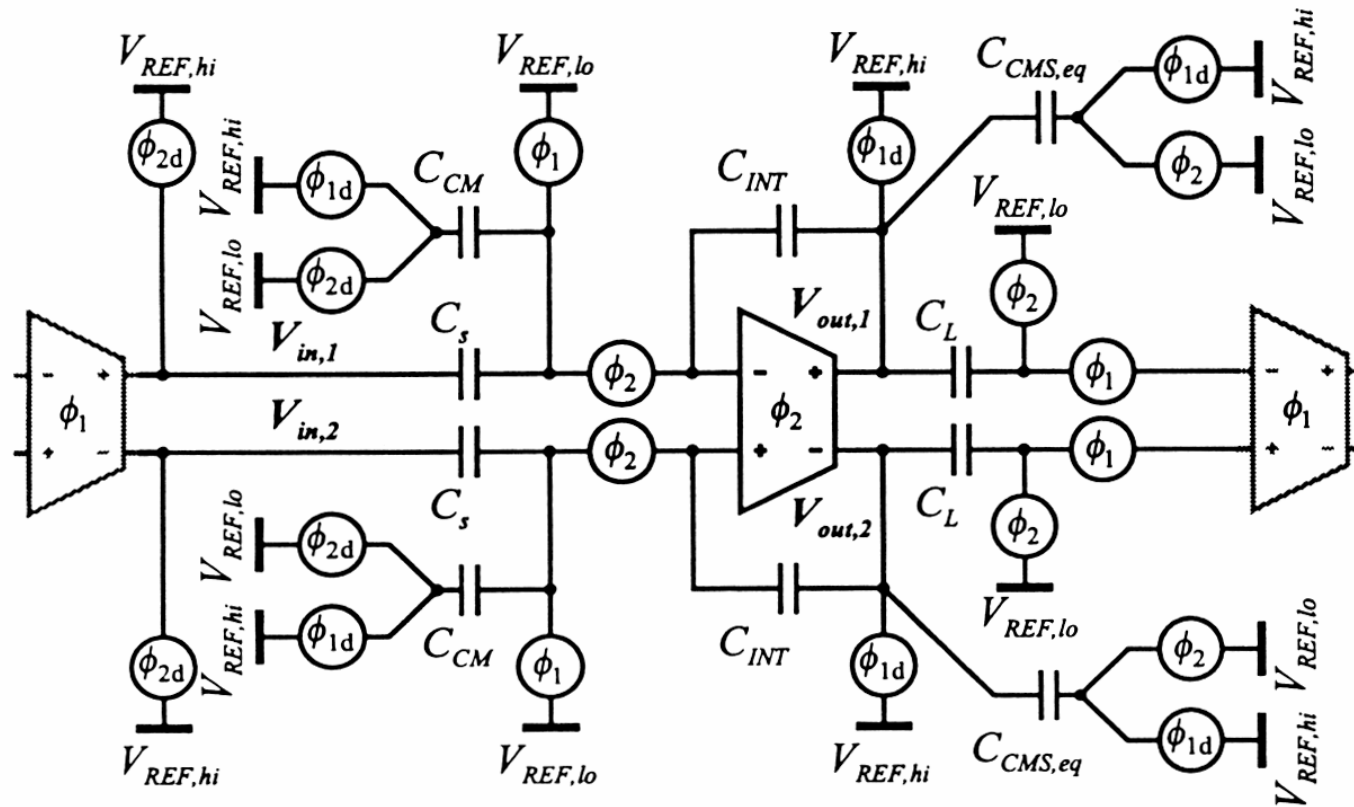


C_S Sampling
 C_{INT} Integrat.
 C_L Load
 C_{CM} Level shift
 $C_{CMS,eq}$ CMFB

$$\begin{aligned}
 V_{REF,hi} &= V_{DD} \\
 V_{REF,lo} &= 0
 \end{aligned}$$

Peluso, ..., JSSC, Dec.98, 1887-1896


Peluso et al "Design of low-voltage low-power CMOS Delta-Sigma ADC's", Kluwer 1999

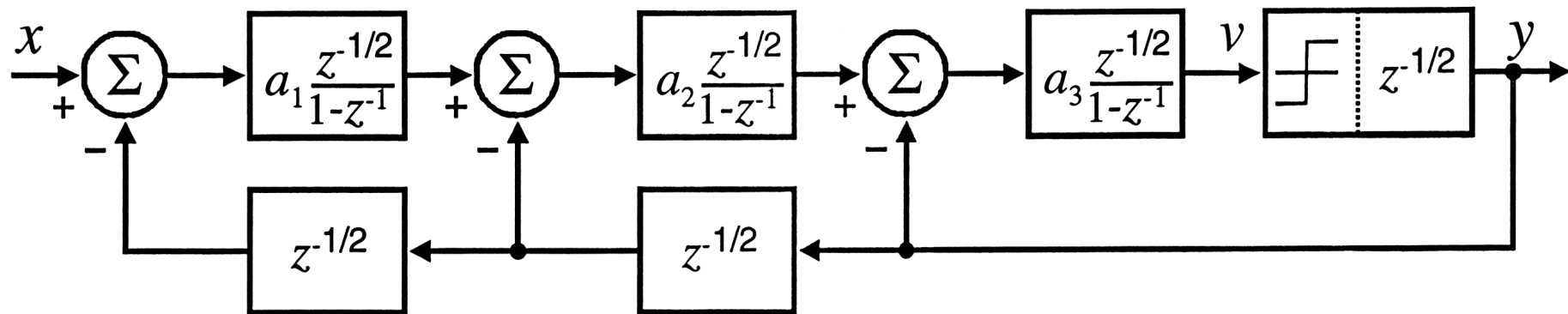□ $\Sigma\Delta$ topology with half-delay integrators



- 3rd order single-loop implementation
- coefficients $a_1 = 0.2$; $a_2 = 0.5$; $a_3 = 0.5$
- 1/2 phase delays in feedback path

Class AB differential Voltage amplifier

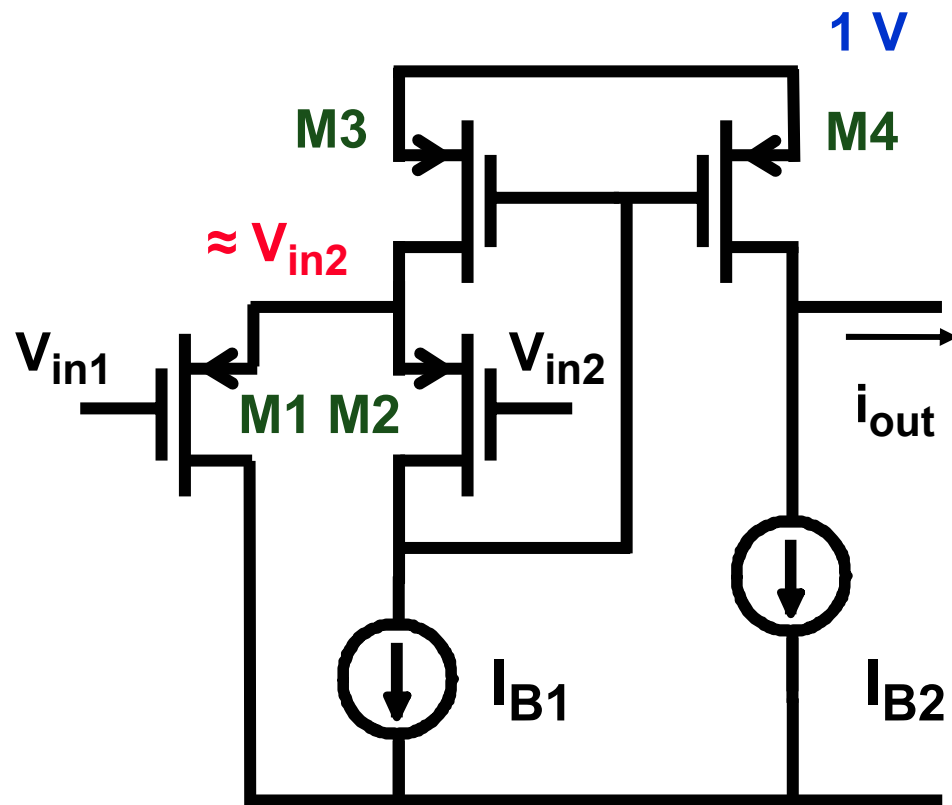

$$V_T = 0.6 \text{ V}$$

$$V_{GS} - V_T = 0.2 \text{ V}$$

$$V_{GS} = 0.8 \text{ V}$$

$$V_{DSsat} = 0.2 \text{ V}$$

M2 is source follower


$$V_{GS1} = V_{in1} - V_{in2}$$

$$i_{out} \sim (V_{in1} - V_{in2})^2$$


>>> Class AB

Peluso, ..., JSSC, Dec.98, pp.1887-1896


Differential class AB OTA

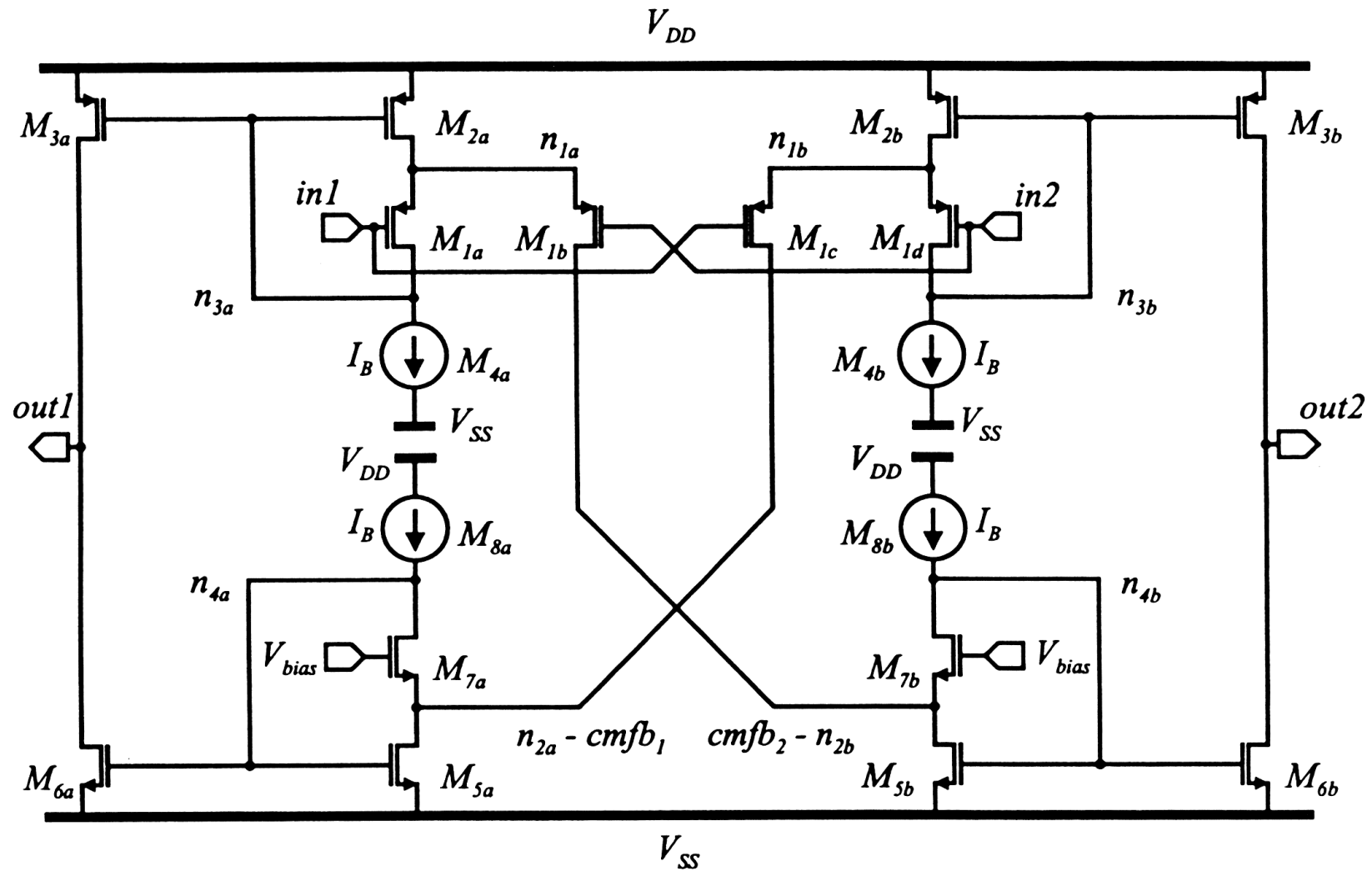

Class AB characteristic

 


Larger input W/L

 


Larger current source W/L

CMFB and level-shift

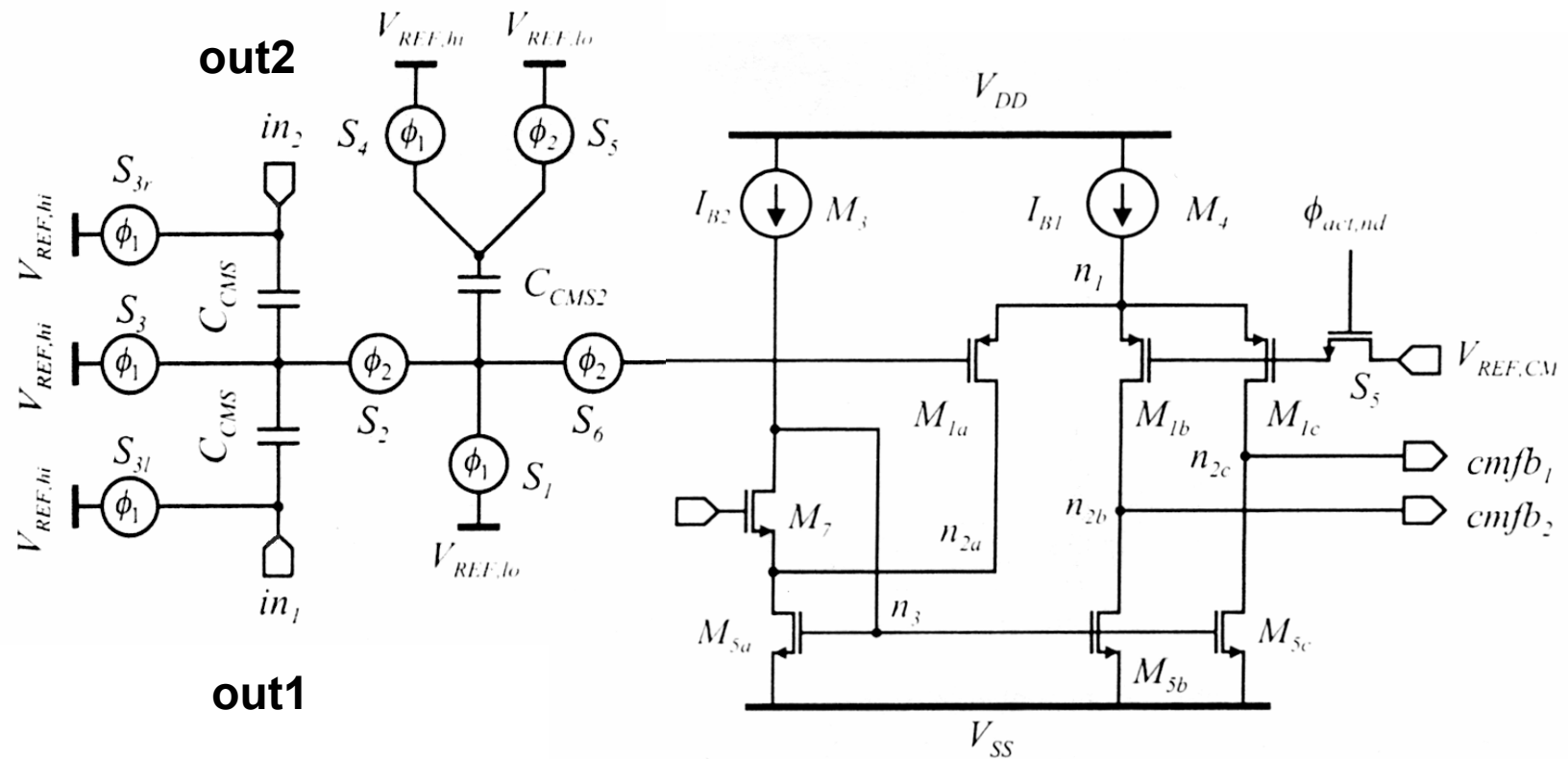

 
Low voltage comparator (level shift omitted)



Two switches

Input at V_{SS}


The input integrator

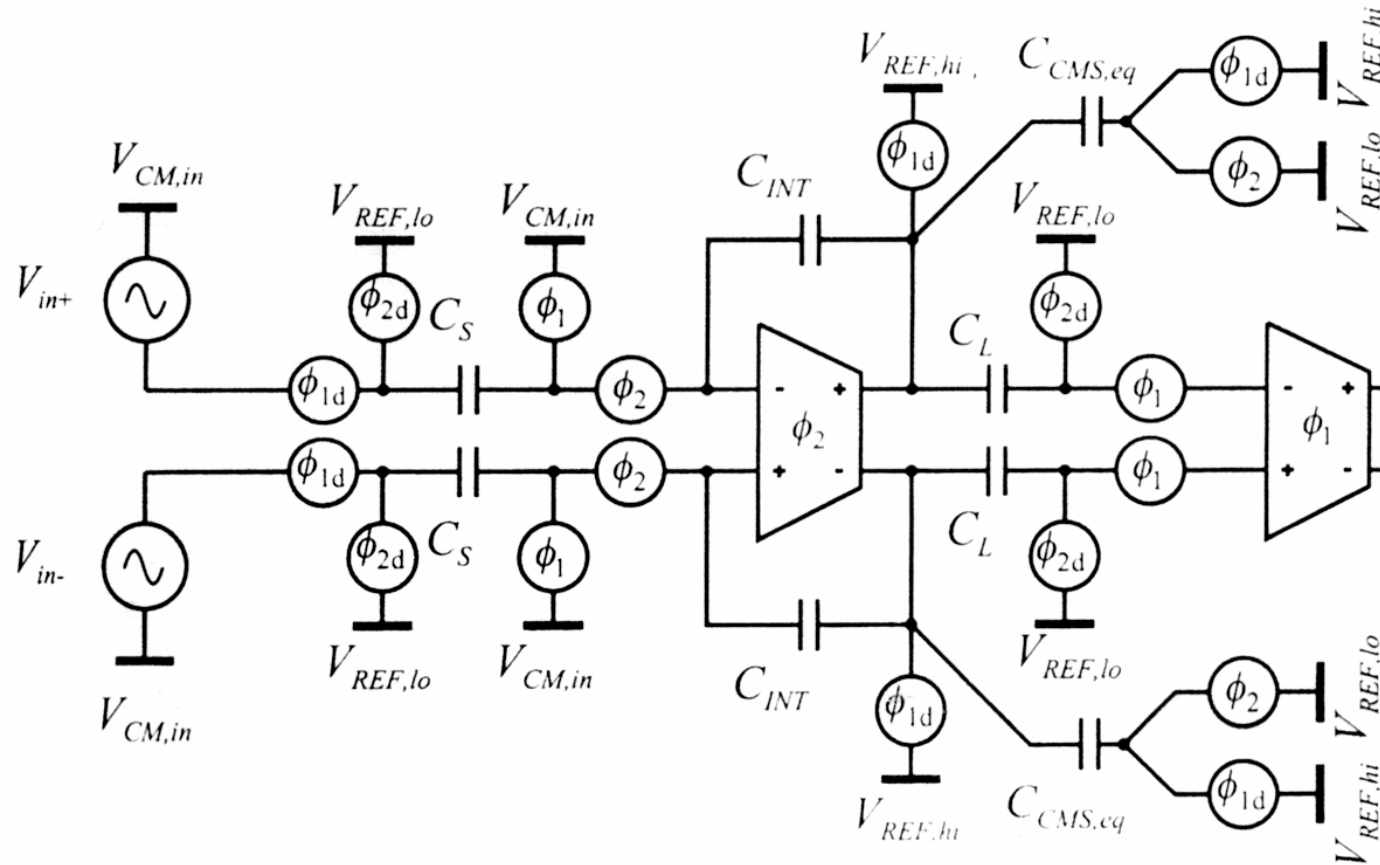

$$V_{REF,hi} = V_{DD}$$

$$V_{REF,lo} = 0$$

 
Spectrum for maximum input signal (470 mV_{ptp})



BW 16 kHz
Clock freq. 1.5 MHz
Peak SNR 76 dB
Peak SNDR 62 dB

Peluso, ..., JSSC
Dec.98, pp.1887-1896

SNDR versus input signal level

 


Peak SNR = 76 dB

DR = 77 dB

SNDR = 62 dB

 SO 12 bit 0.9 V 40 μ W CMOS $\Sigma\Delta$



0.5 μ m CMOS

$V_{Tn} = 0.62$ V

$V_{Tp} = 0.55$ V

$V_{DD} = 0.9$ V


40 μ W

Peluso,
JSSC Dec.98,
pp.1887-1896

Table of contents

- ◆ **Delta-sigma modulation**
- ◆ **The switch problem**
- ◆ **The switched-opamp solution**
- ◆ **Other low-power Delta-sigma converters**
 - **Unity-gain-reset**
 - **Optimized input switching**
 - **Switched input resistor**
 - **Full feedforward**

Reset-opamp integrator

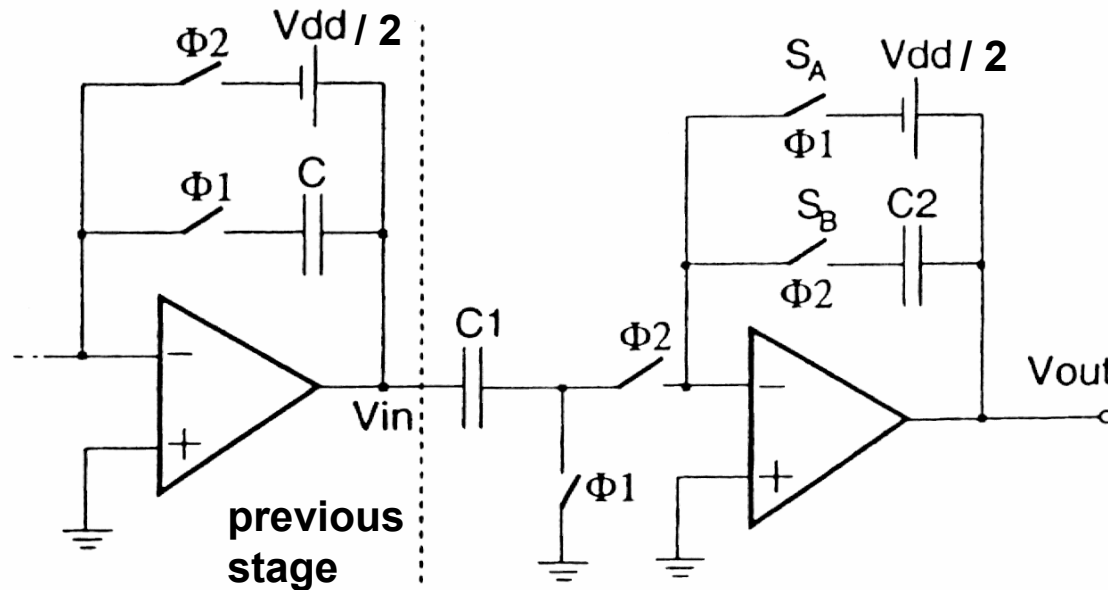

$$V_{\text{out}} = 0 \dots 1 \text{ V}$$

$$V_{\text{out,av}} \approx 0.5 \text{ V}$$

$$V_{\text{in}} \approx 0 \text{ V}$$

$$V_{\text{dd}}/2 \approx 0.5 \text{ V}$$

On Φ_1 :

$$Q_1 = C_1 V_{\text{in}}$$

Q_2

$$V_{\text{out}} = 0$$

On Φ_2 :

$$Q_1 = 0$$


$$Q_2 + C_1 V_{\text{in}}$$

$$V_{\text{out}}$$

Level shift needed to avoid forward biased junctions !

Keskin, ..., JSSC July 02, 817-824

Pseudo-differential opamp

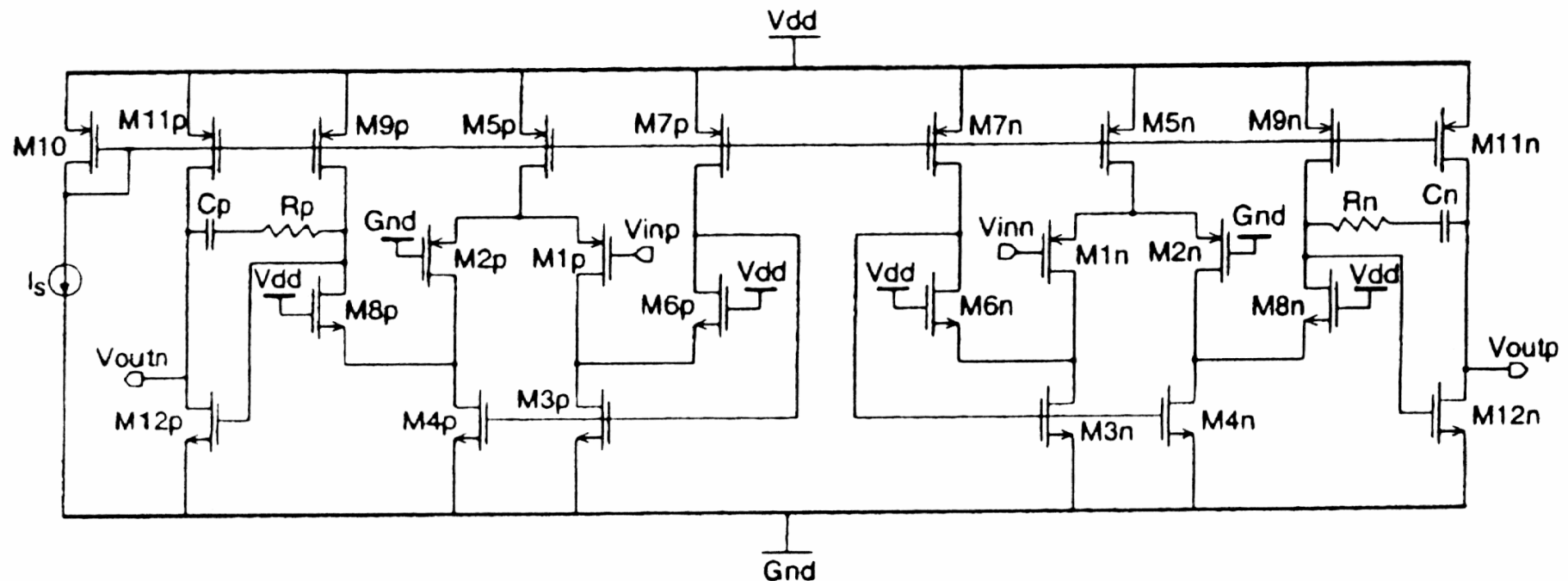

170 MHz 100 V/ μ s 3.5 pF 1 V 200 μ A

0.35 μ m CMOS $V_{Tn} \approx 0.52$ V $V_{Tp} \approx 0.45$ V

Ref.Keskin, JSSC July 2002, 817-824

1-Volt 2nd-order 13-bit $\Sigma\Delta$ modulator


 
 
 


Table of contents

- ♦ **Delta-sigma modulation**
- ♦ **The switch problem**
- ♦ **The switched-opamp solution**
- ♦ **Other low-power Delta-sigma converters**
 - **Unity-gain-reset**
 - **Optimized input switching**
 - **Switched input resistor**
 - **Full feedforward**

 $\Sigma\Delta$ Modulator on 1 Volt in 90 nm CMOS




- ♦ **Single-loop third-order single-bit topology**
 - Simple and robust
 - Tolerance to building block non-idealities
- ♦ **Coefficients selected not sensitive to capacitance mismatches**

Yao, ..., JSSC Nov.04, 1809-1818


Yao. etal. "Low-Power Low-Voltage $\Sigma\Delta$ modulators in Nanometer CMOS", Springer '06

Gain enhancement

 

$$A = \frac{2}{(1 - k)(V_{GS} - V_T)_1 \cdot \lambda_3} = \frac{A_0}{1 - k}$$

Stability

 


The non-dominant pole
must be $> 3GBW$
for sufficient phase margin

$$P_{nd} = \frac{gm_2}{2\pi \cdot C_c} = \frac{2(1-k)I_1}{2\pi \cdot C_c \cdot (V_{GS} - V_T)_2}$$

$$GBW = \frac{B \cdot gm_1}{2\pi \cdot C_L} = \frac{2B \cdot I_1}{2\pi \cdot C_L \cdot (V_{GS} - V_T)_1}$$


$$P_{nd} > 3GBW \Rightarrow k < 1 - 3B \frac{C_c}{C_L}$$

Full OTA circuit

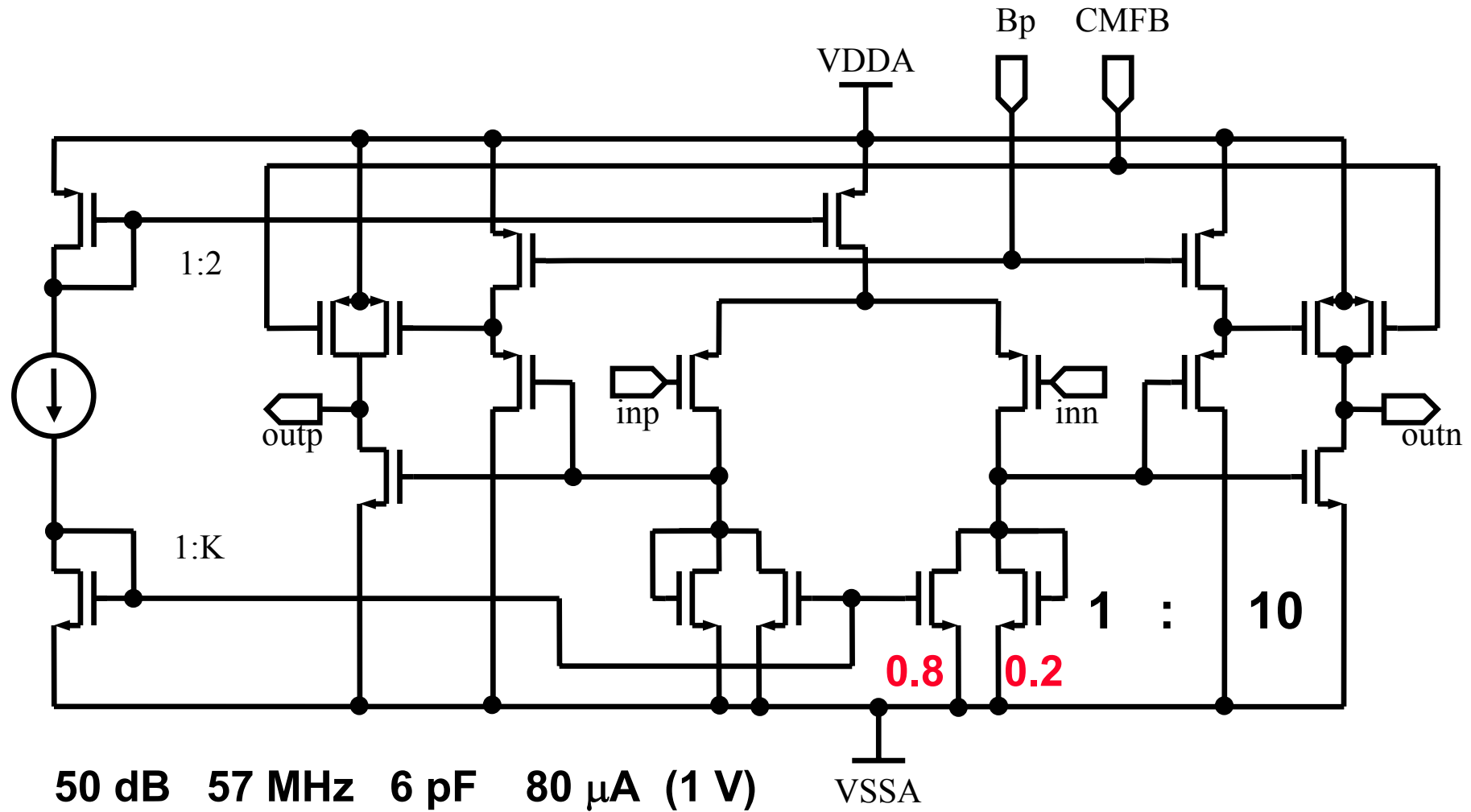


Yao, ..., JSSC Nov.04, 1809-1818

Full modulator circuits

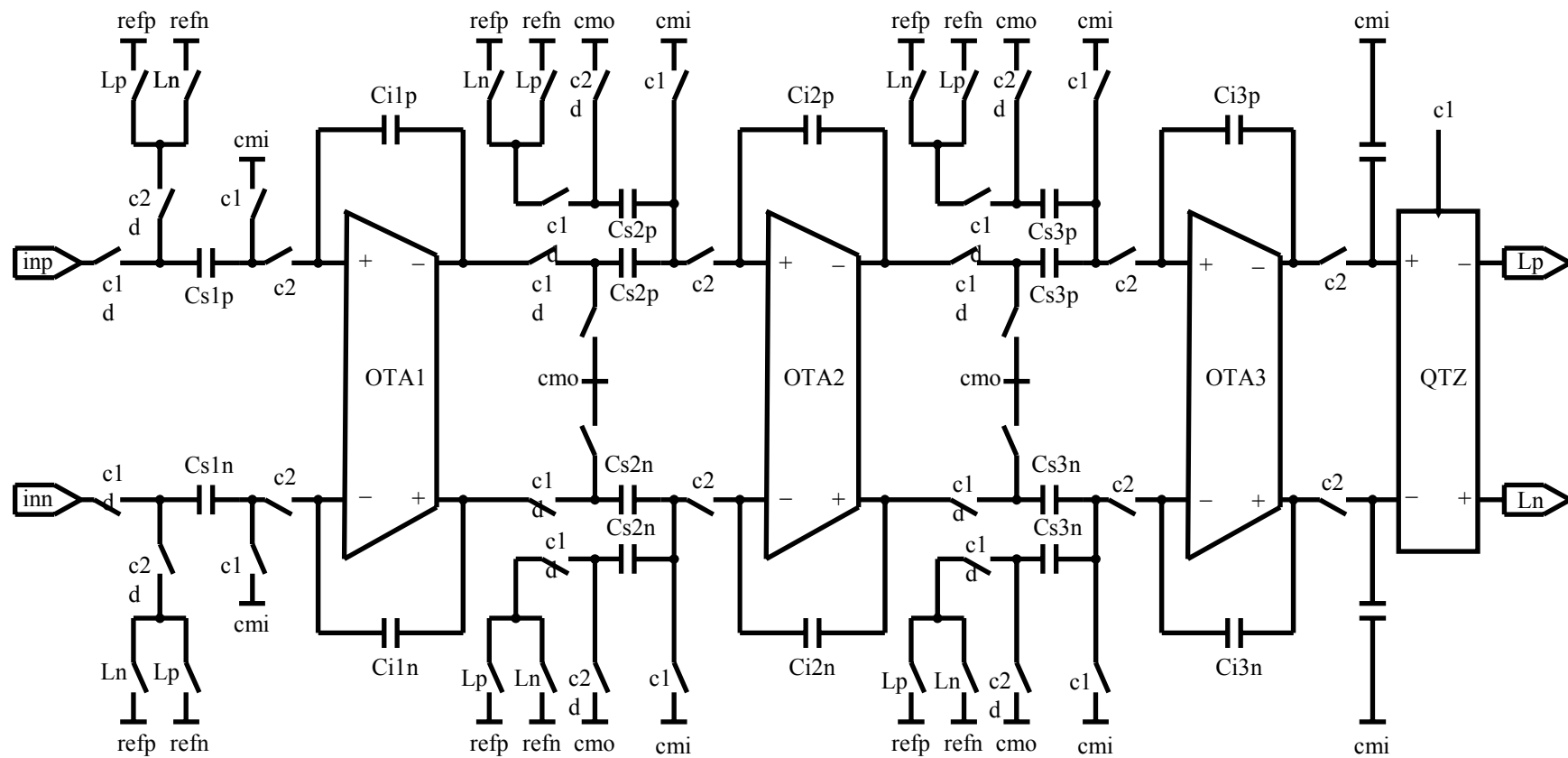


Measurement Output spectrum

 

Output spectrum of a 5 kHz input signal

Measured SNR and SNDR vs input amplitude

 


Yao, ..., JSSC Nov.04, 1809-1818

Table of contents

- ◆ **Delta-sigma modulation**
- ◆ **The switch problem**
- ◆ **The switched-opamp solution**
- ◆ **Other low-power Delta-sigma converters**
 - **Unity-gain-reset**
 - **Optimized input switching**
 - **Switched input resistor**
 - **Full feedforward**

Switched-resistor integrator

 


**Input switch
replaced by resistor R**

**Larger resistor for better linearity
Smaller resistor for higher speed**


Ahn, .. ISSCC 05, 166-167

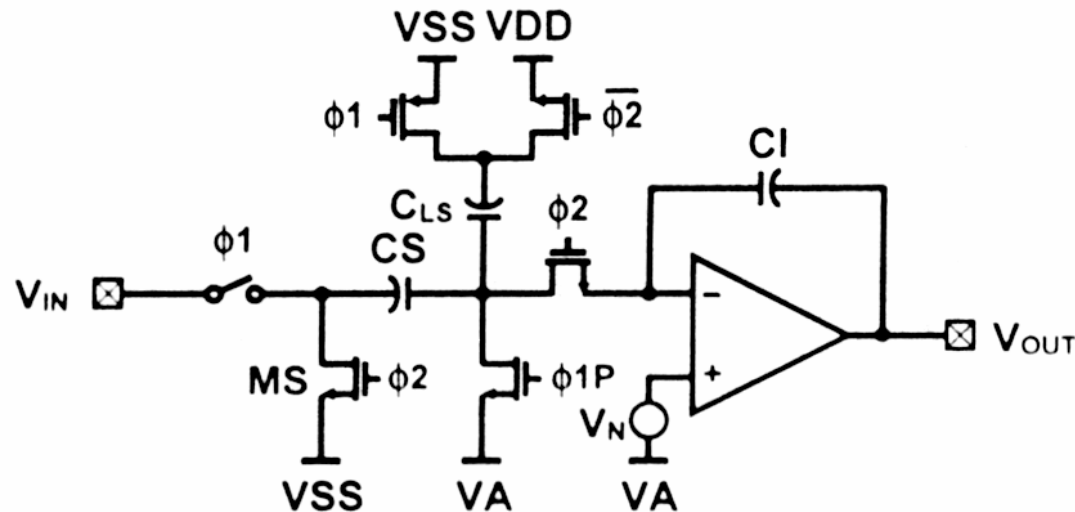Input sampling : maintain constant V_{INCM}



C_{LS} added


Baschirotto, JSSC
Dec.1997, 1979-1986

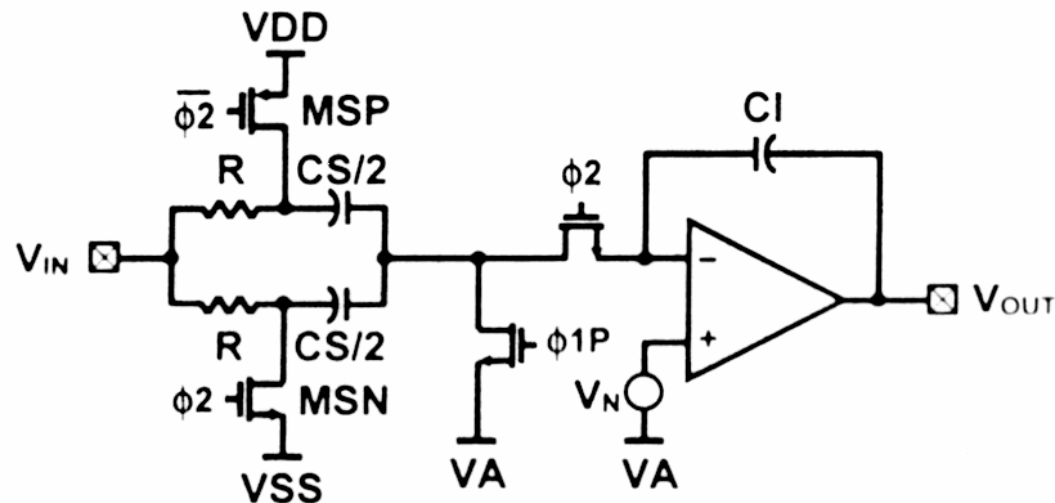

R & C_S doubled

Ahn, .. ISSCC 05, 166-167

Mash 2-2 $\Sigma\Delta$ Audio ADC

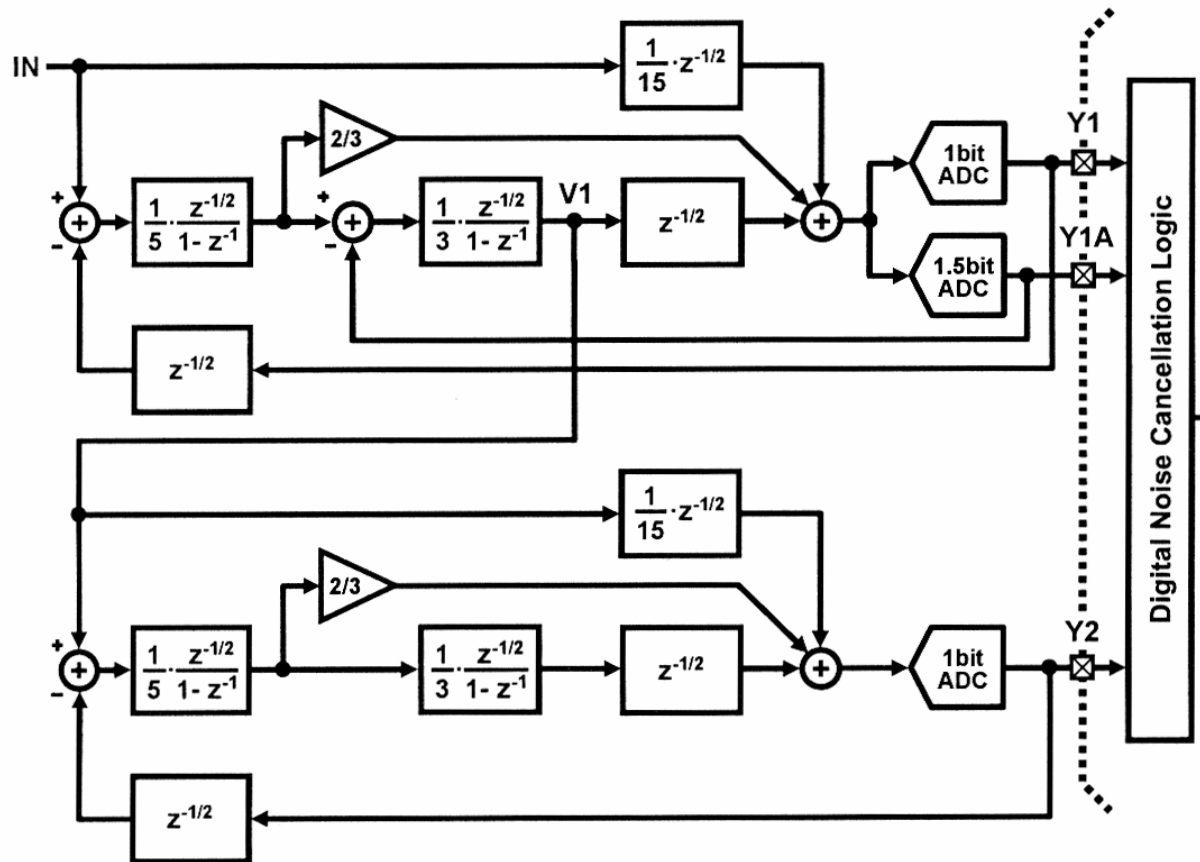

Low-distortion :

- switched resistor
- loop filter processes only quantization error

OSR = 64

25 kHz

3 MHz clock

SNDR = 78 dB


0.35 μm CMOS

0.6 V

1 mW

**Ahn, .. ISSCC 05, 166-167
Silva, Electronic Letters,
June 01, 737-738**

4-th order $\Sigma\Delta$ converter with switched-resistors

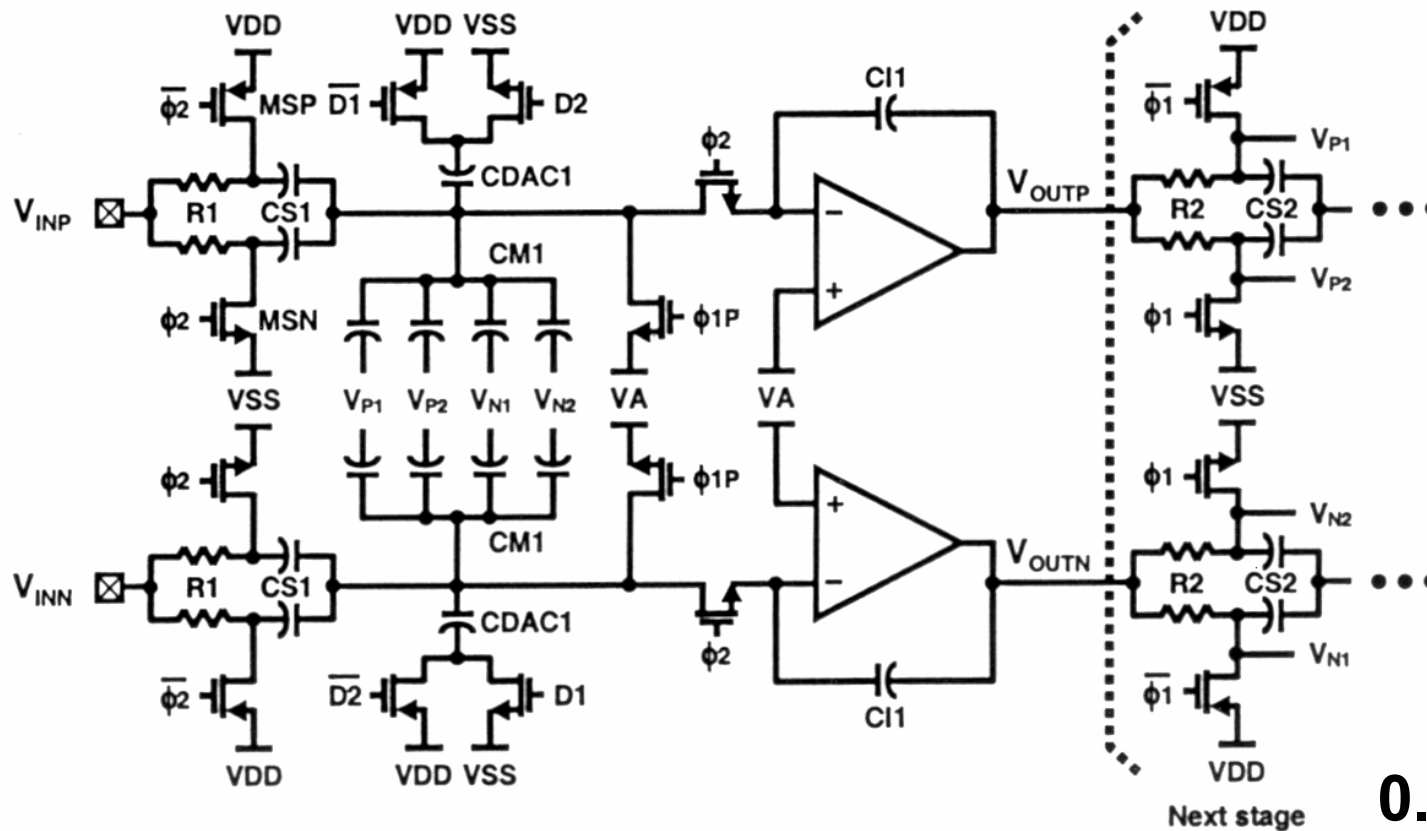


Mash 2-2
OSR = 64

Two-stage opamp with folded cascode
0.6 V 1 mW 24 kHz BW

0.35 μm CMOS

Measured SNDR

 



**Low-distortion :
Vref = 0.6 V**

**SNR \approx SNDR
= 78 dB
at 1 kHz**

Table of contents

- ♦ **Delta-sigma modulation**
- ♦ **The switch problem**
- ♦ **The switched-opamp solution**
- ♦ **Other low-power Delta-sigma converters**
 - **Unity-gain-reset**
 - **Optimized input switching**
 - **Switched input resistor**
 - **Full feedforward**

Full Feedforward Topology

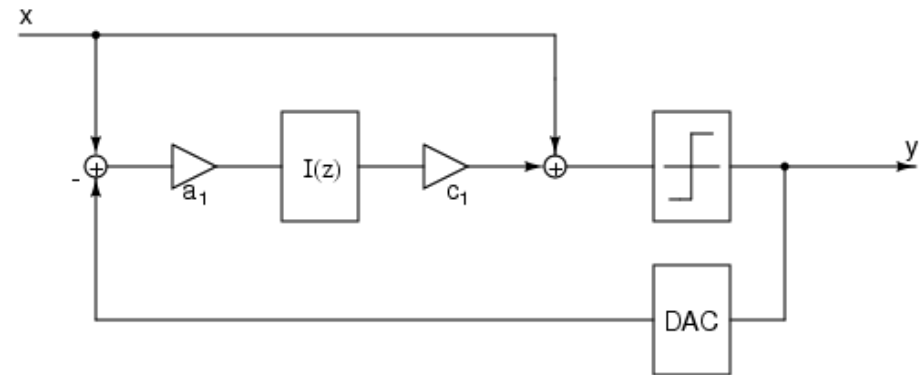 

Convent. Sigma-Delta topology

Full feedforward topology

$$H_x(z) = \frac{a_1 I}{1 + a_1 I}$$


$$H_e(z) = \frac{1}{1 + a_1 I}$$

$$H_x(z) = 1$$

$$H_e(z) = \frac{1}{1 + a_1 c_1 I}$$

Silva, Electronic Letters, June 01, 737-738

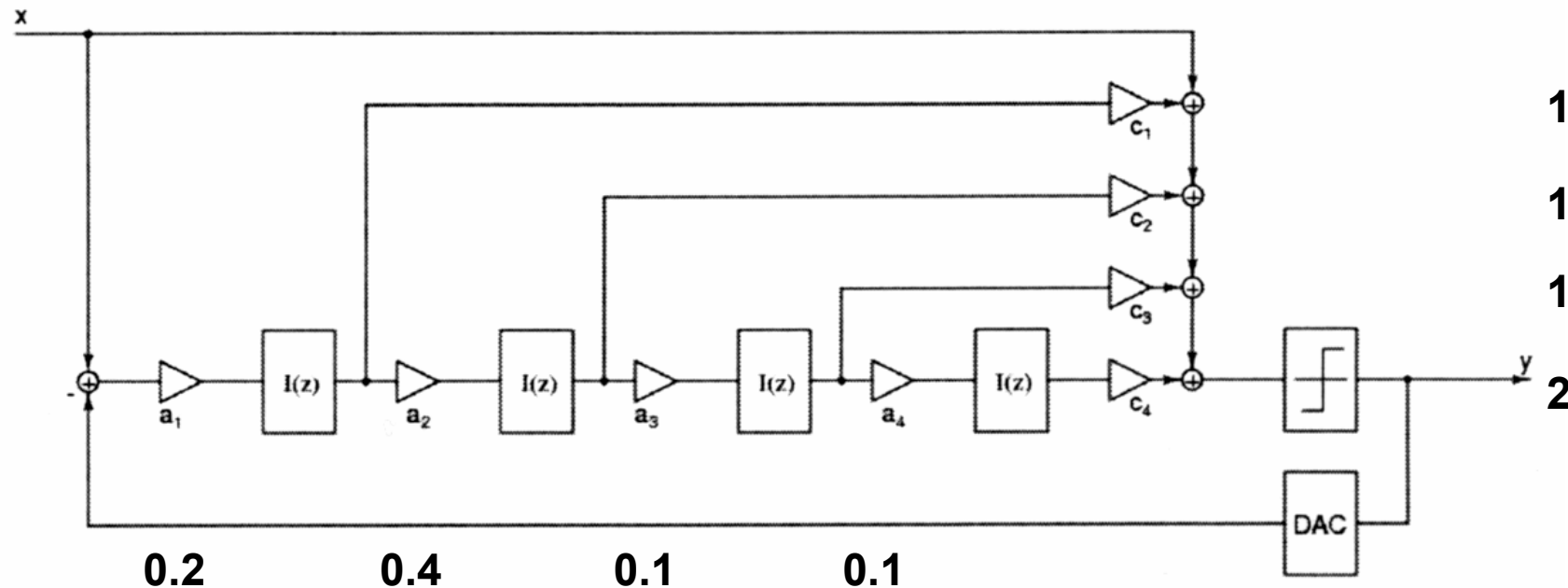4th-Order single-bit 1 Ms/s $\Sigma\Delta$ modulator



Single feedback loop : processes quantization noise only

Full feedforward : unity-gain transfer


4th order - single bit

Optimization coefficients or equal swing


Yao, .., VLSI Circuits '05
Yao. etal. "Low-Power Low-Voltage $\Sigma\Delta$ modulators in Nanometer CMOS", Springer '06

Performance comparison

 
- ◆ 4th-order conventional topology
- ◆ Behavioral simulation with:
 $a_1=-0.1$, $a_2=-0.1$, $A_0=40$ dB



 
- ◆ 4th-order full feedforward topology
- ◆ Behavioral simulation with:
 $a_1=-0.1$, $a_2=-0.1$, $A_0=40$ dB



Output swing of integrators

 


 **Output swings of each
integrator in the
conventional topology**



**Output swings of each
integrator in the
full-feedforward topology**

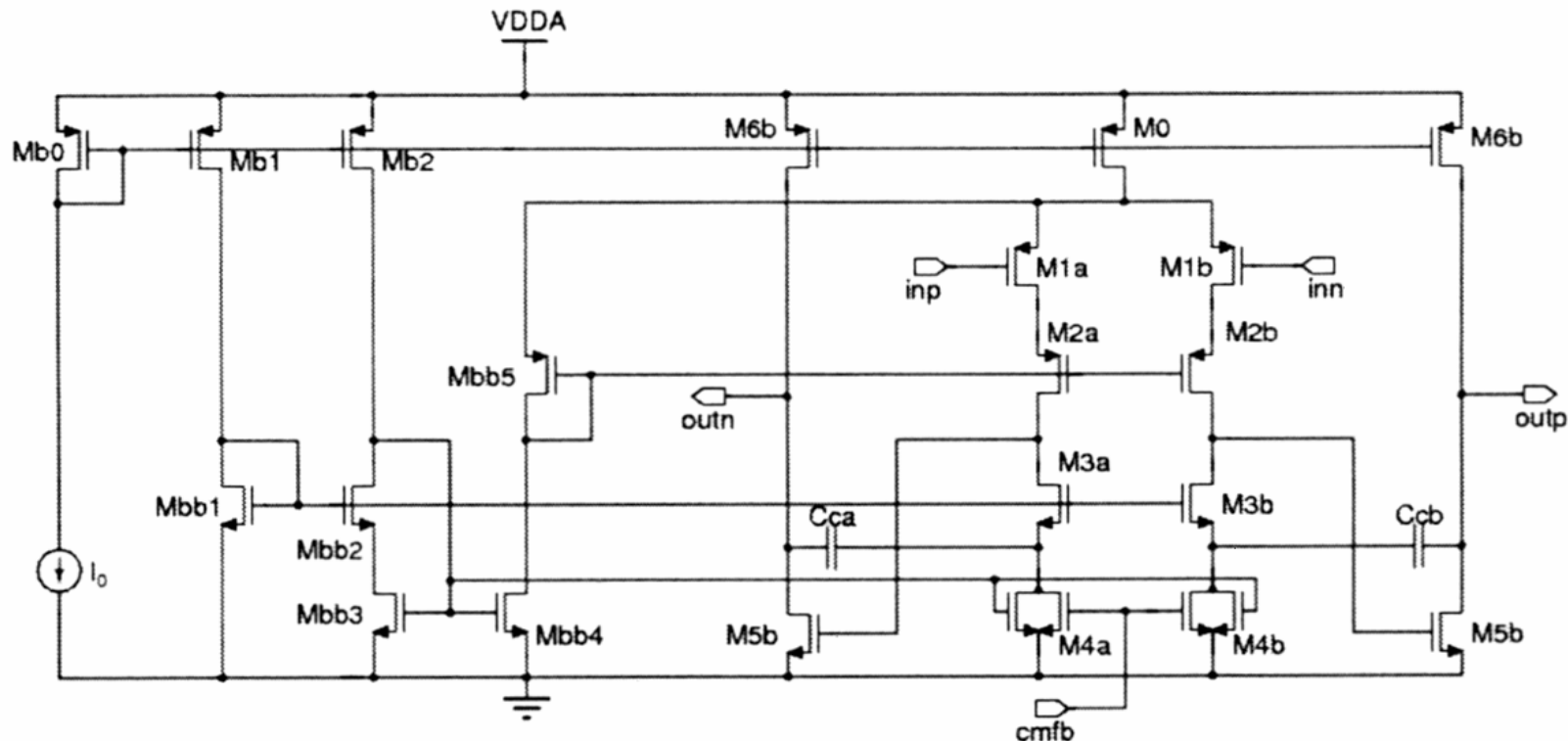
Single-stage OTA for fast settling (0.13 μm)



Yao, .., VLSI Circ.05

Yao. etal. "Low-Power Low-Voltage $\Sigma\Delta$ modulators in Nanometer CMOS", Springer '06

Circuit Realization

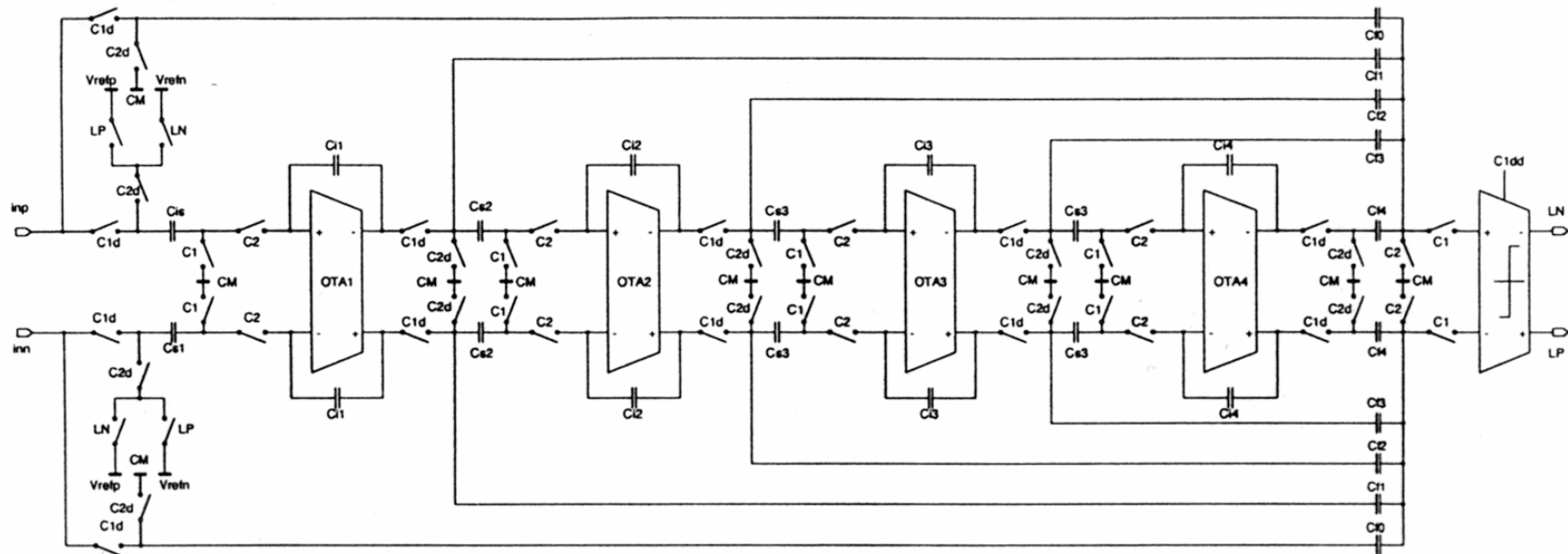

OSR = 64


Clock of 64 MHz

1 V 6.1 mA + 1.3 mA


Yao, .., VLSI Circuits, '05

Yao. etal. "Low-Power Low-Voltage $\Sigma\Delta$ modulators in Nanometer CMOS", Springer '06

Measured output spectrum

 

Measured SNR versus Input voltage

 


Comparison of Low-power $\Sigma\Delta$ converters

Ref.	Type	V _{DD} V	DR dB	BW kHz	P μ W	FOM $\times 10^{-6}$
Ahn 05	SwR	0.6	78	24	1000	20
Sauerbrey 02	SO, LV	0.7	75	8	80	53
Peluso 98	SO	0.9	77	16	40	330
Dessouky 01	LV	1	88	25	950	275
Keskin 02	ResetOp.	1	74	20	5600	6
Yao 04	LV	1	88	20	140	1490
Rabii 96	SC, VM	1.8	92	25	5400	121
Yin 94	211	5	97	750	180k	346
Geerts 00	211	5	92	1100	200k	144
Vleugels 01	221	2.5	95	2000	150k	700
Gaggl 04	4	1.5	88	300	8k	400
Yao 05	4	1	88	500	7.4k	706
Doerrer 05	Track	1.5	74	2000	3k	280
Hezar 05	5	1.3	86	600	5.4k	737

$$\text{FOM} = 4kT \text{ DR BW} / P$$

Low-voltage low-VT comparison

 

Sauerbrey, ...,
JSSC Dec.02
1662-1669

Table of contents

- ◆ **Delta-sigma modulation**
- ◆ **The switch problem**
- ◆ **The switched-opamp solution**
- ◆ **Other low-power Delta-sigma converters**