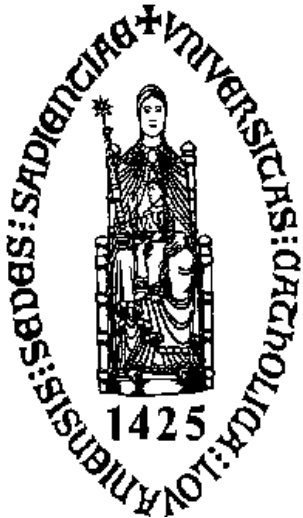

Continuous-time filters



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium

willy.sansen@esat.kuleuven.be



Applications and problems

- **Applications**
 - **Anti-aliasing filters**
 - **Video and HF filters : hard-disk drives**
 - **Channel select filters**
 - **Low-power filters**
- **Problems:**
 - **Tuning for high precision: mismatch $< 5 \%$**
 - **Distortion : THD < -60 dB**
 - **Low power supply voltages**
 - **High quality factors : $Q > 50$?**

Table of contents

◆ Active RC filters

◆ MOSFET-C filters


◆ GmC filters

◆ Comparison

Ref.: Tsividis, Voorman, Integrated Cont.-time filters, IEEE Press 1993
J. Silva-Martinez, Kluwer 1993,
W. Dehaene, JSSC, July 1997, 977-988

Active RC filters

Opamps and passive components (R, C)

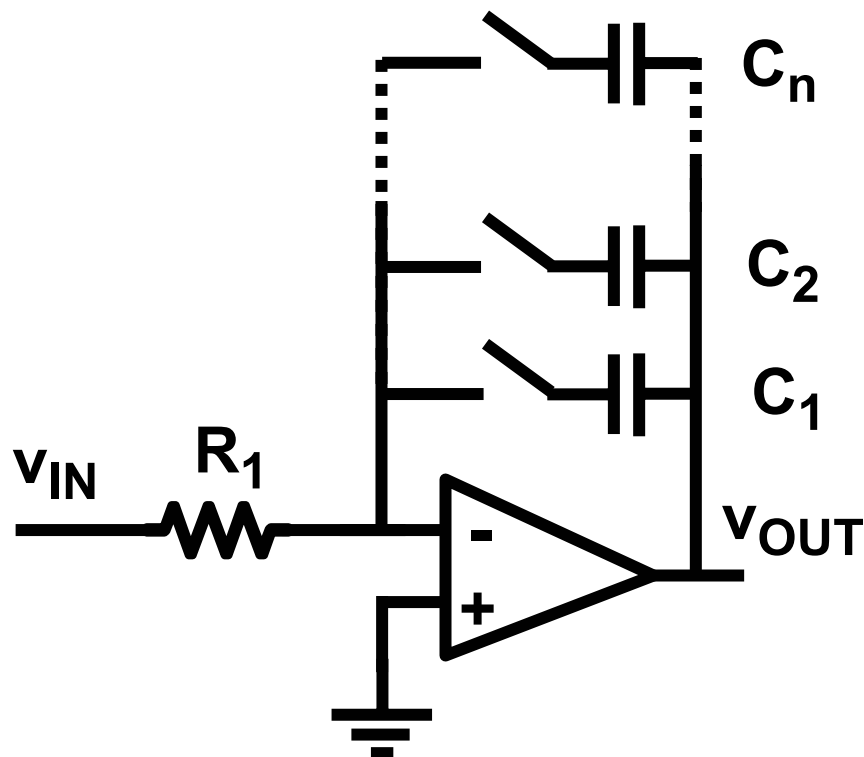

Advantages :

S/N up to 100 dB

THD very low < -90 dB

Disadvantages :

Opamps :

only for low frequencies

Errors on R, C ≈ 20 %

\gg tune C's

Table of contents

◆ Active RC filters


◆ MOSFET-C filters

◆ GmC filters



◆ Comparison

Ref.: Silva-Martinez, Dehaene, ..


MOST resistors

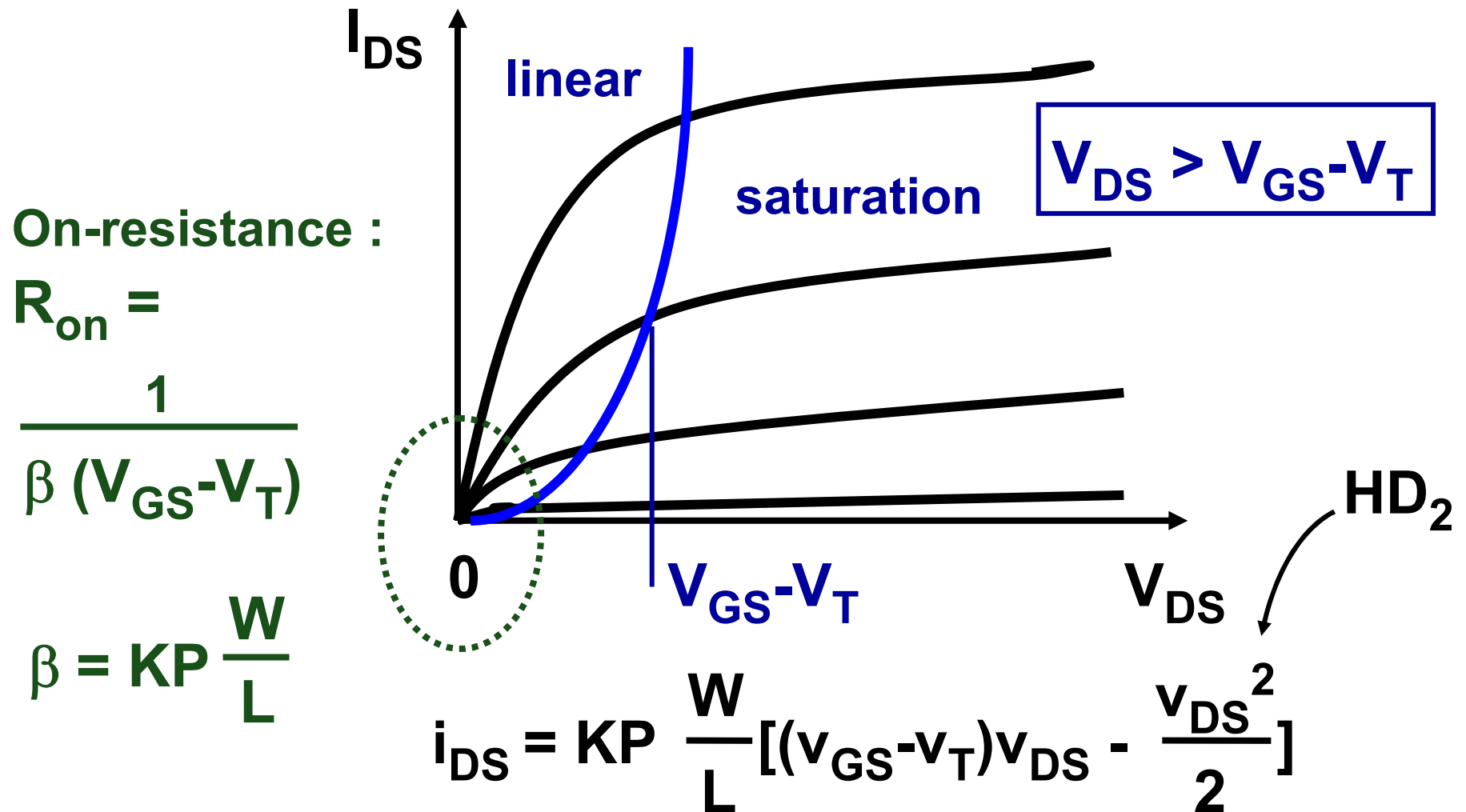

Examples of differential MOST-R's

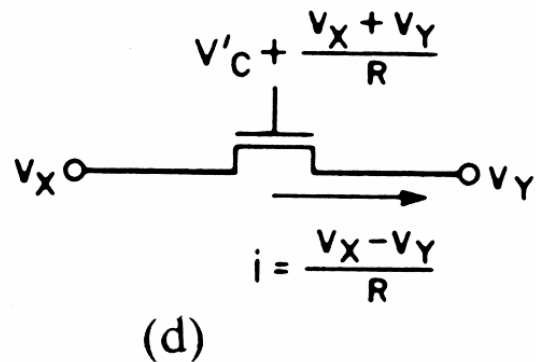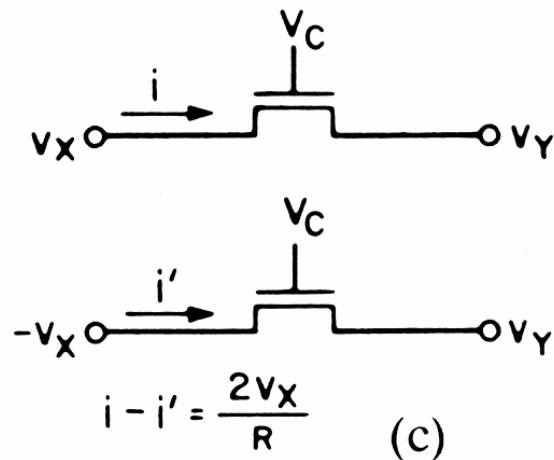



partial cancellation of even nonlin

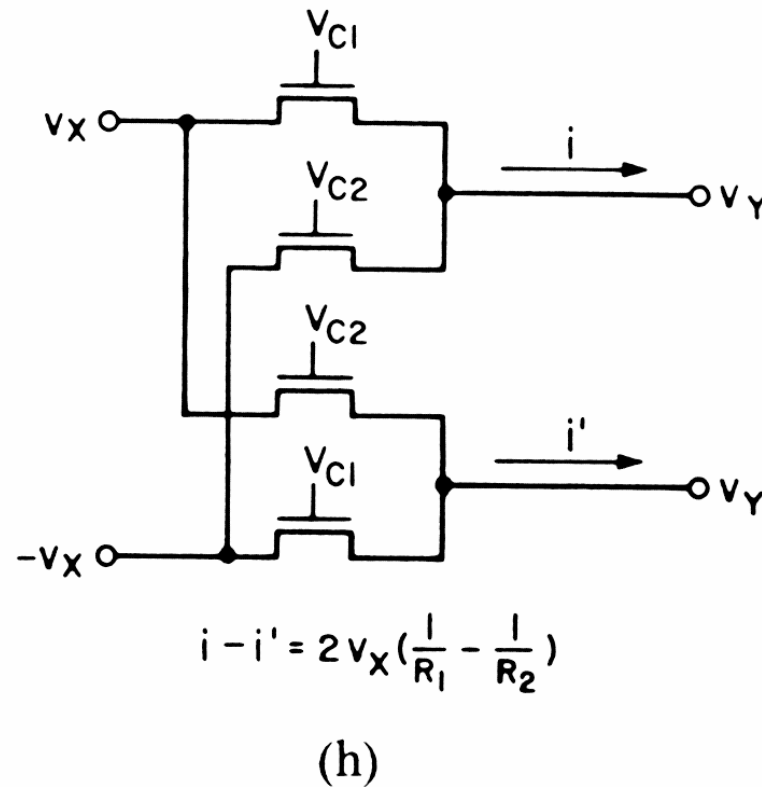

cancellation of even
and odd nonlinearities

Ref. Tsividis JSSC Feb.86, 15-30; Ma.94, 166-176

From active RC to MOSFET-C filter

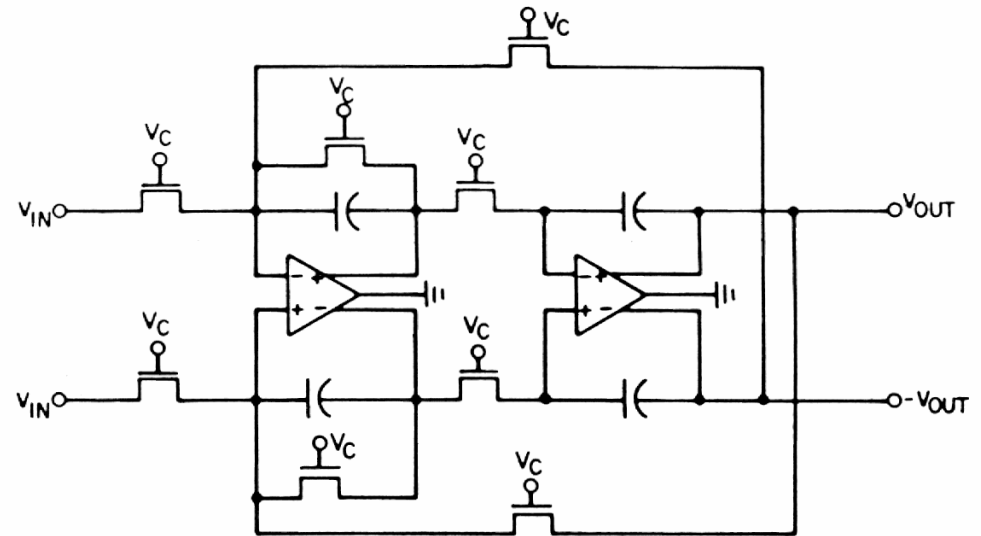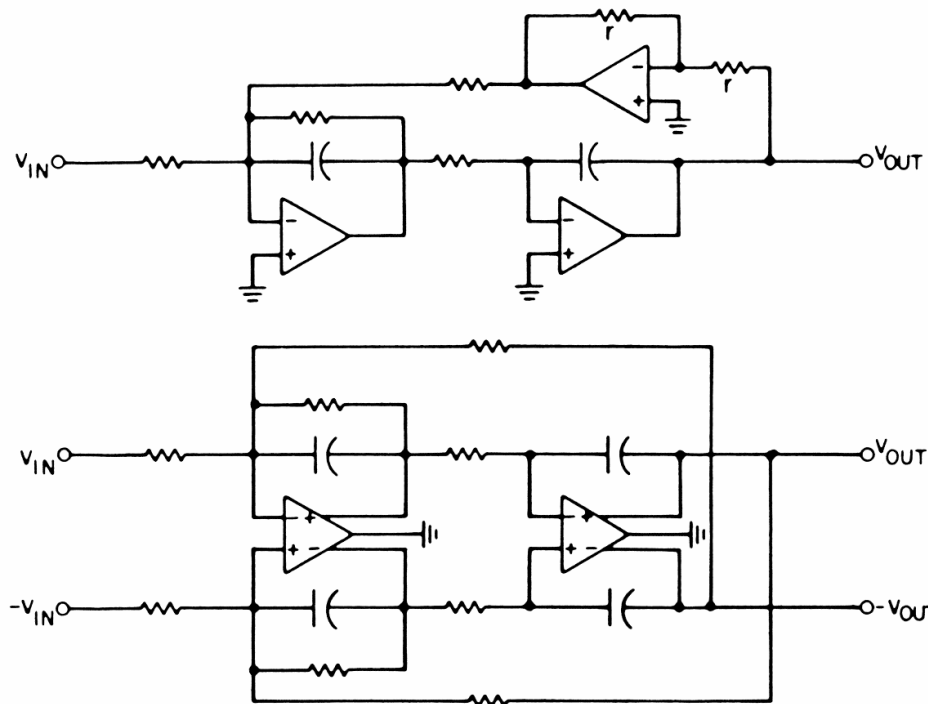

Ref. Tsividis JSSC Feb.86, 15-30

Large R_{ON} values at high frequencies

For low-frequency low-pass filter with f_{-3dB}


$$f_{-3dB} = \frac{1}{2\pi R_{on} C} \approx \frac{KP \ W/L \ (V_{GS}-V_T)}{2\pi C}$$

For $f_{-3dB} = 4 \text{ kHz}$; $KP = 60 \ \mu\text{A/V}^2$; $V_{GS}-V_T = 1 \text{ V}$; $W = 2 \ \mu\text{m}$; $C = 10 \text{ pF}$
 $R_{on} = 4 \text{ M}\Omega$. For matching $W = 2 \ \mu\text{m}$: $L \approx 500 \ \mu\text{m}$! The area is 10^{-5} cm^2

For $C_{ox} = 5 \cdot 10^{-7} \text{ F/cm}^2$ ($0.35 \ \mu\text{m}$); $C_{GS} = 5 \text{ pF}$;


High-frequency limit at $\approx 8 \text{ kHz}$ or $f_T \approx 8 \text{ kHz}$!!!!!

LC ladder filter

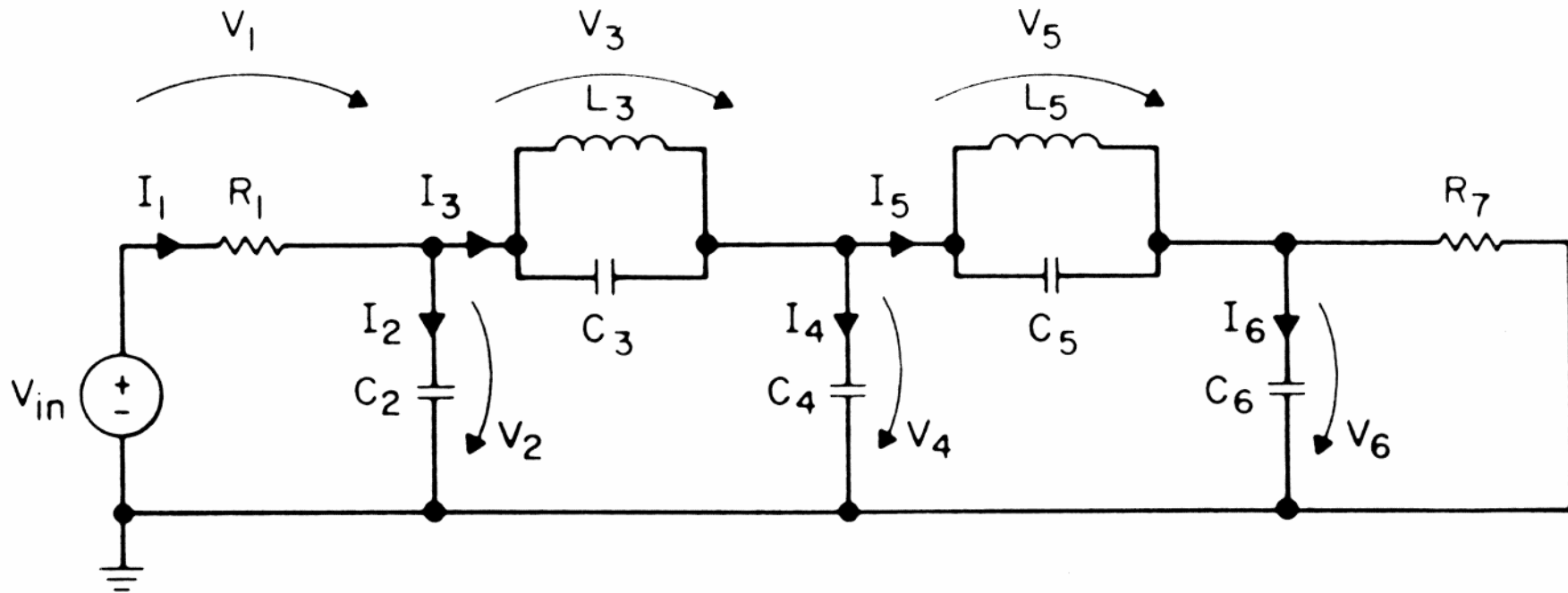


Ref. Banu
JSSC Dec.85,
1114-1121

Fifth-order low-pass filter

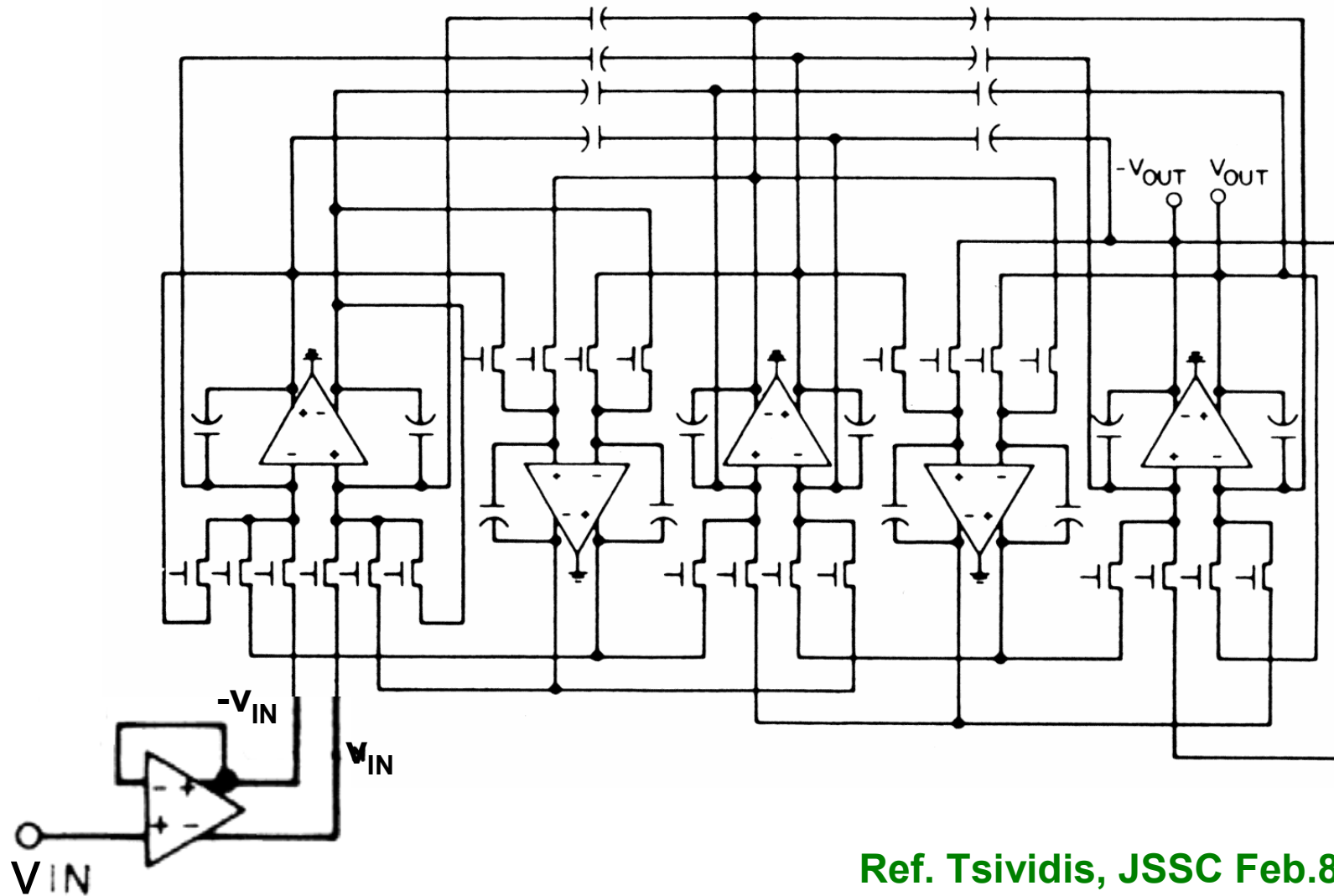


Ref. Tsividis, JSSC Feb.86, 15-30

Fifth-order elliptic low-pass filter

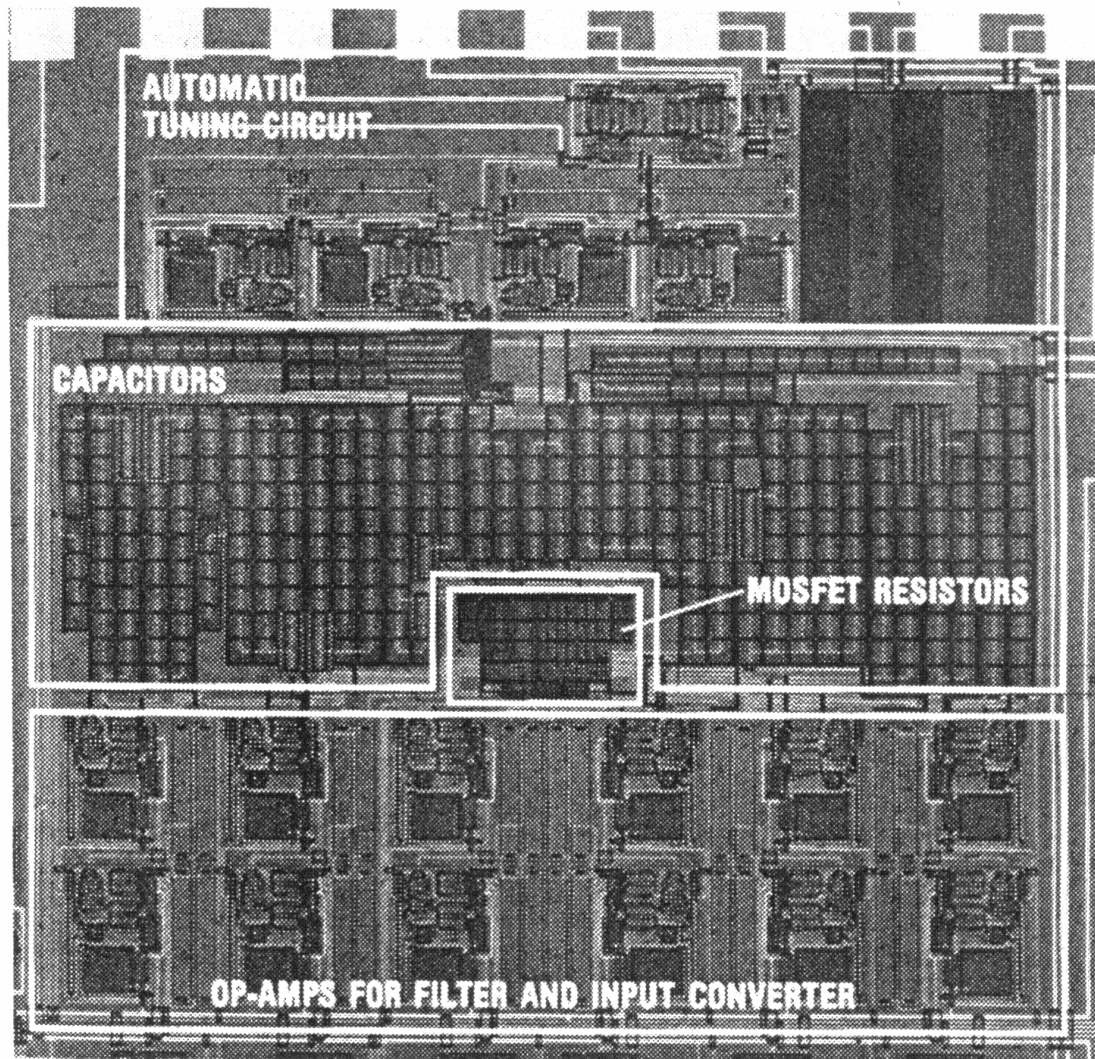

Ref. Tsividis
JSSC Feb.86,
15-30

PLL tuning

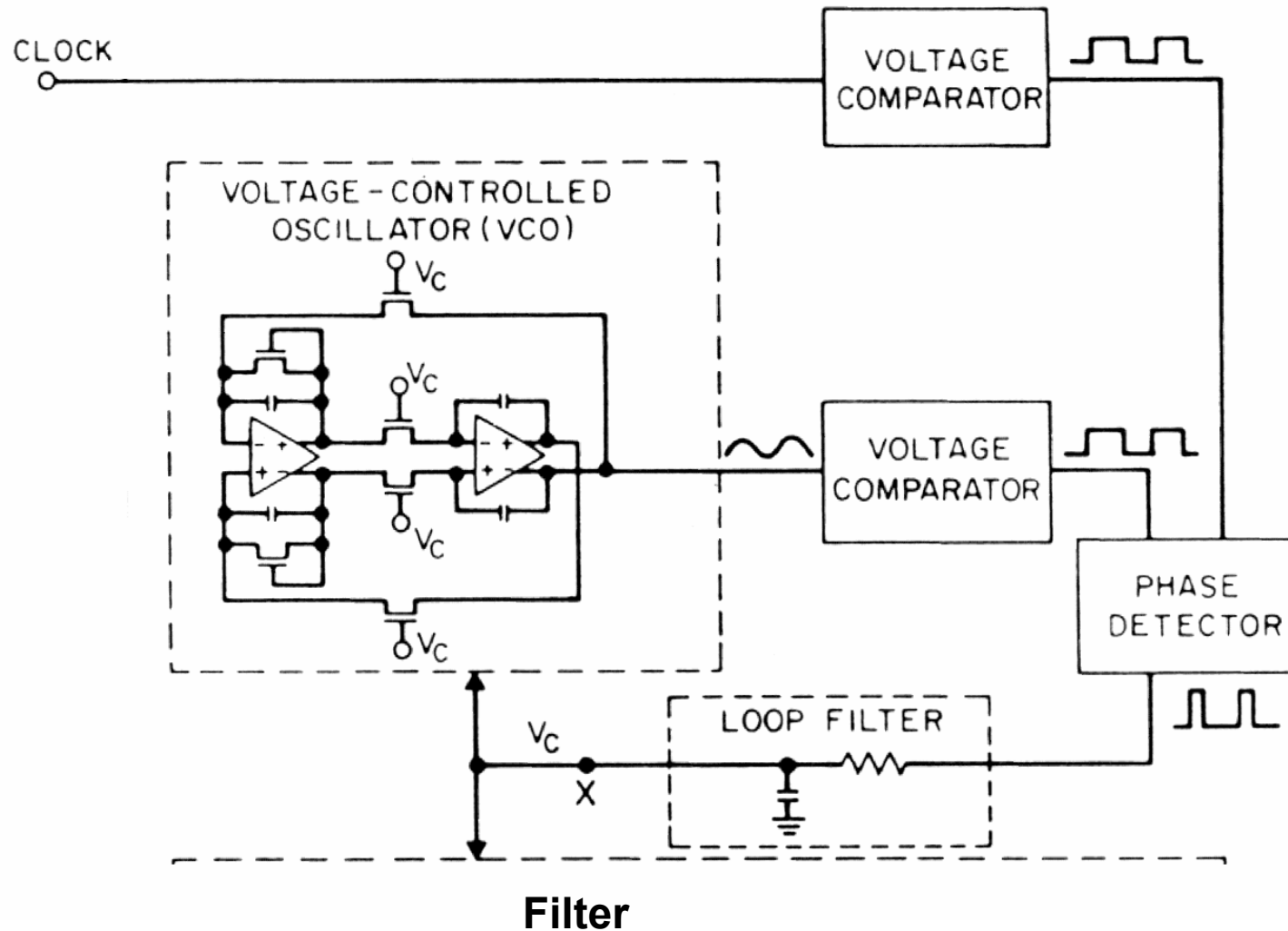

Problems:

**Master/slave for
each pole/zero**

VCO + PLL at f_c

**Signal feedthrough
at f_c**

Ref.

**Banu JSSC Dec.85,
1114-1121**

**Krummenacher, JS
SC June 88, 750-758**


**Khoury, JSSC
Dec.91, 1988-1997**

Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
 - Transconductors
 - Tuning
- ◆ Comparison


Ref.: Silva-Martinez, Dehaene, ..

Some GmC filters

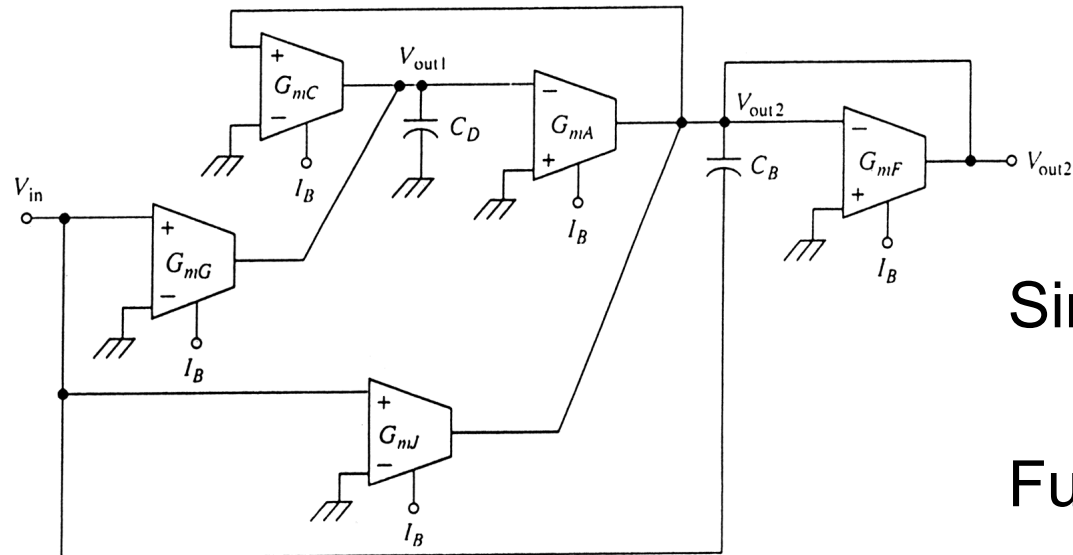

Single-ended GmC filters


Fully-differential ...

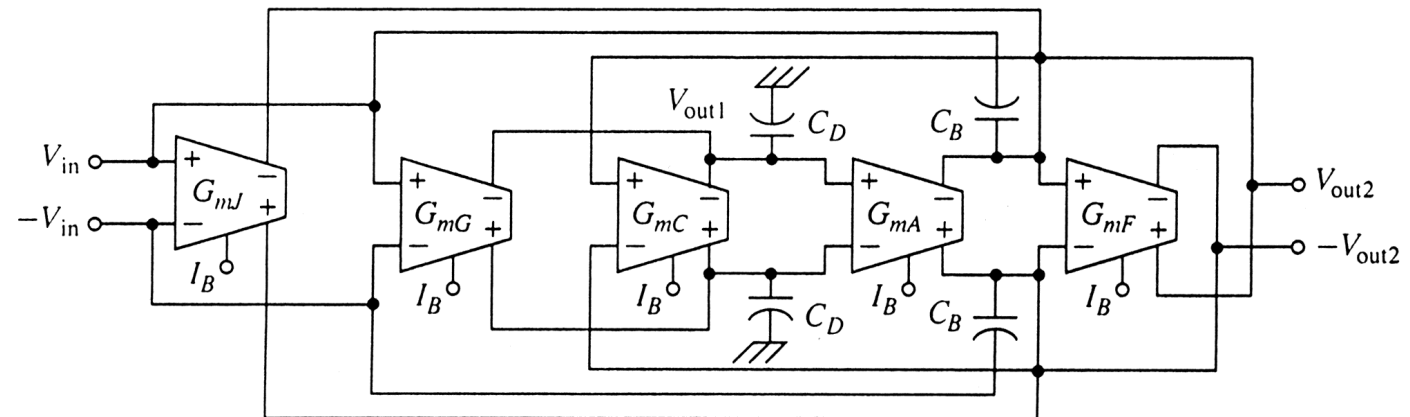

GmC filter definition

Opamp

Operational
amplifier

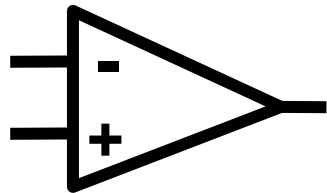


$$A_v = \frac{V_{OUT}}{V_{IN}}$$

$$A_v =$$


OTA

Operational
Transconduct.
amplifier

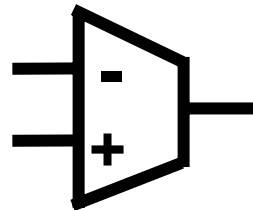

$$A_g = \frac{i_{OUT}}{V_{IN}}$$



$$= A_g R_L$$

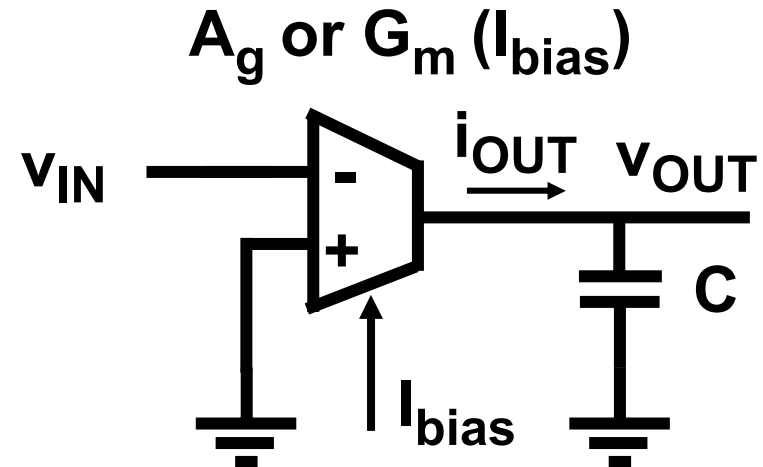


Adv.: High freq. operation
Easy tuning

Disadv.: Distortion
Mismatch errors
Parasitic C's (low Q)

Simple GmC filters

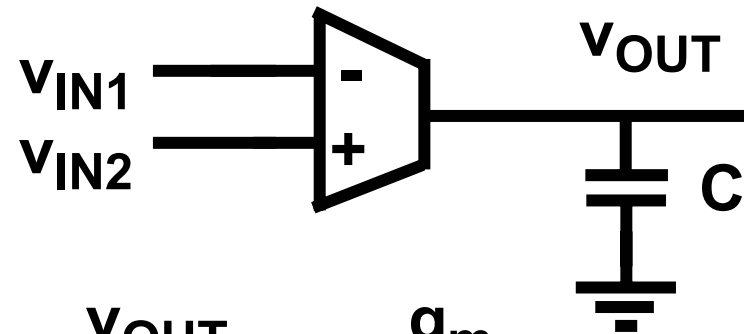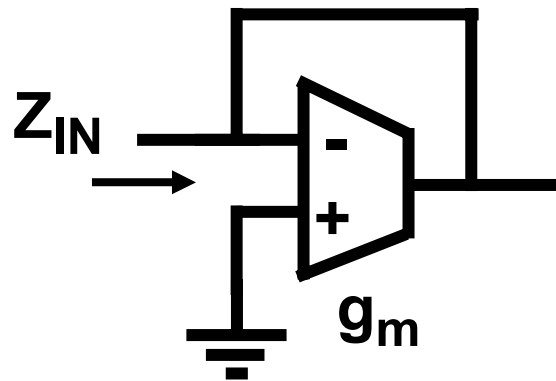

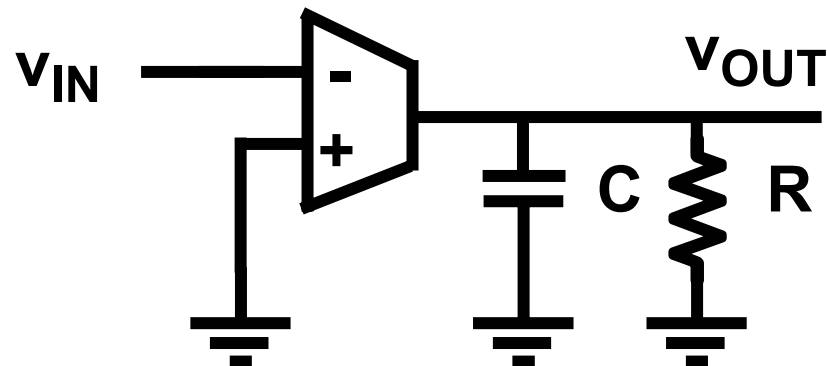
$$\frac{V_{OUT}}{V_{IN1} - V_{IN2}} = \frac{g_m}{sC}$$




$$\frac{V_{OUT}}{V_{IN}} = \frac{g_m R}{1 + sRC}$$


Simple GmC filters

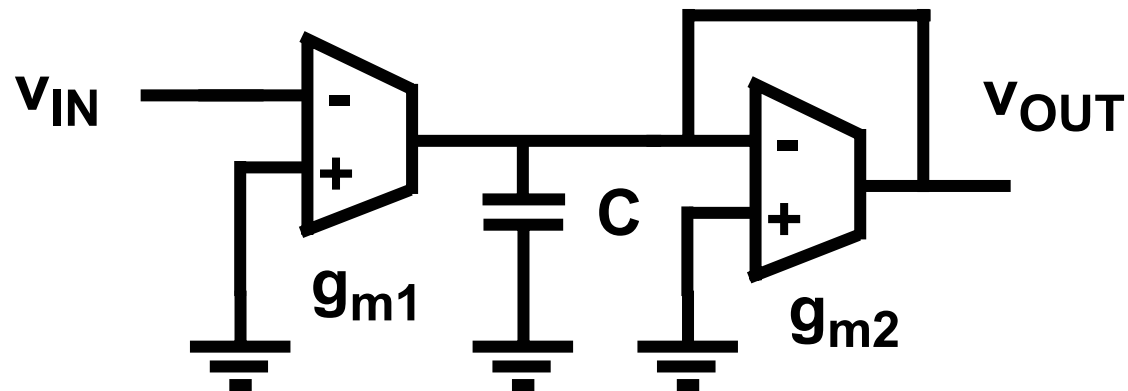


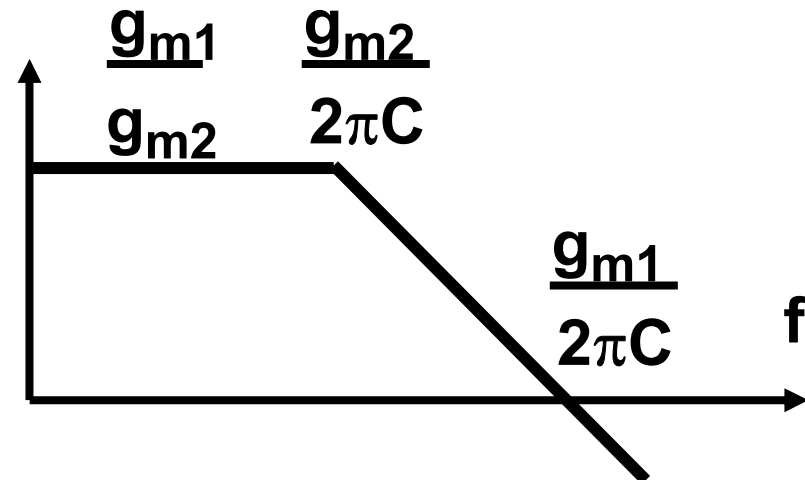
$$\frac{V_{OUT}}{V_{IN}} = \frac{g_{m1}}{g_{m2} + sC}$$




Simple fully-differential GmC filters

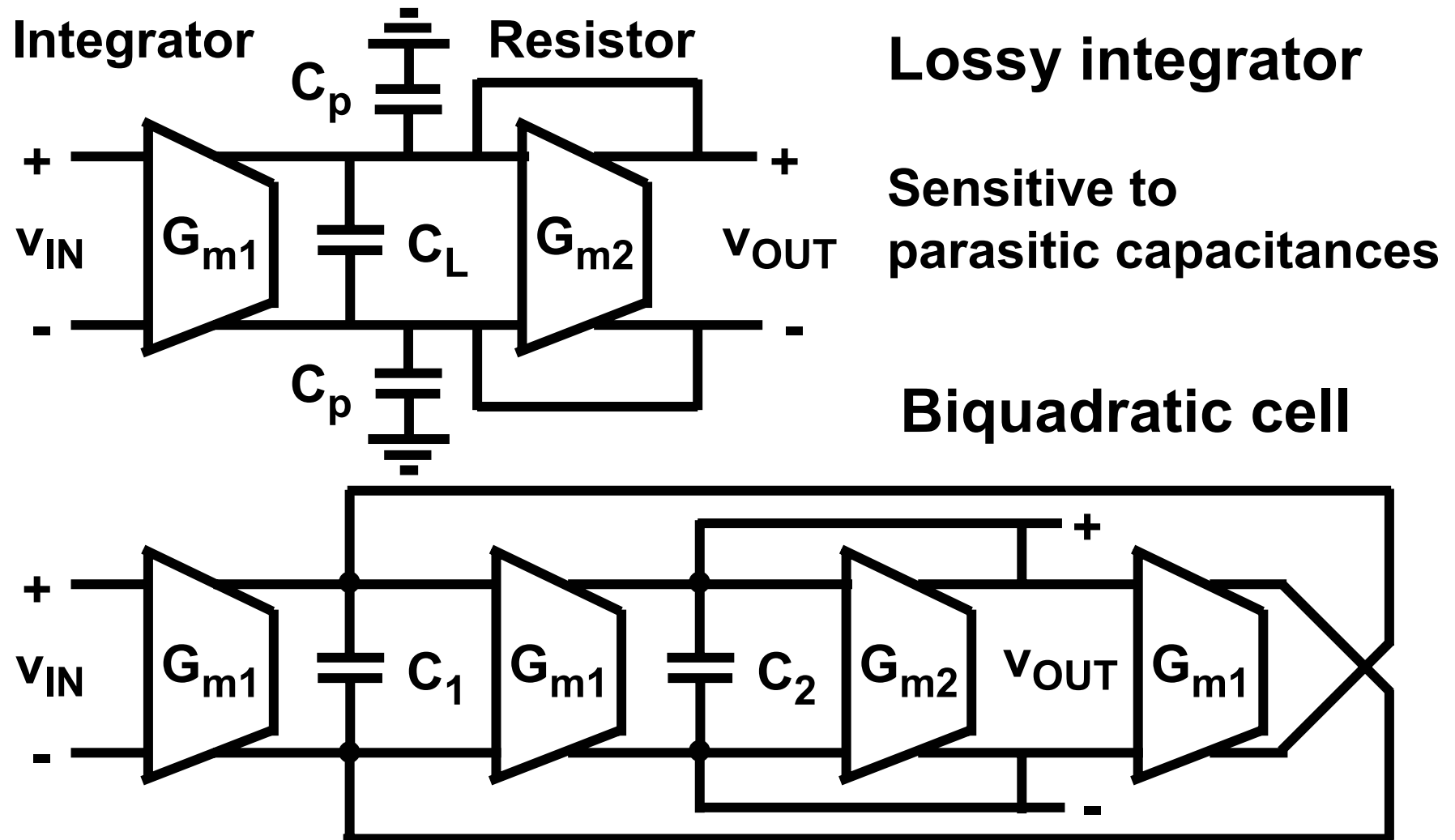

Voltage-mode & current-mode filters

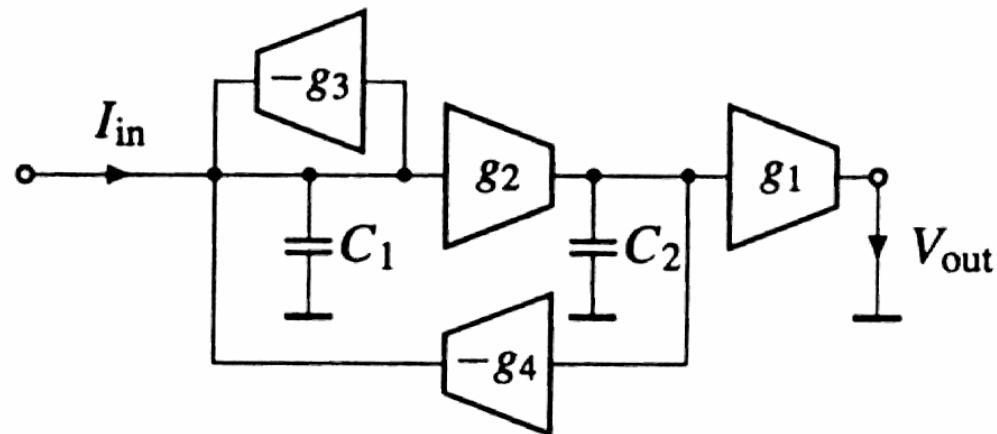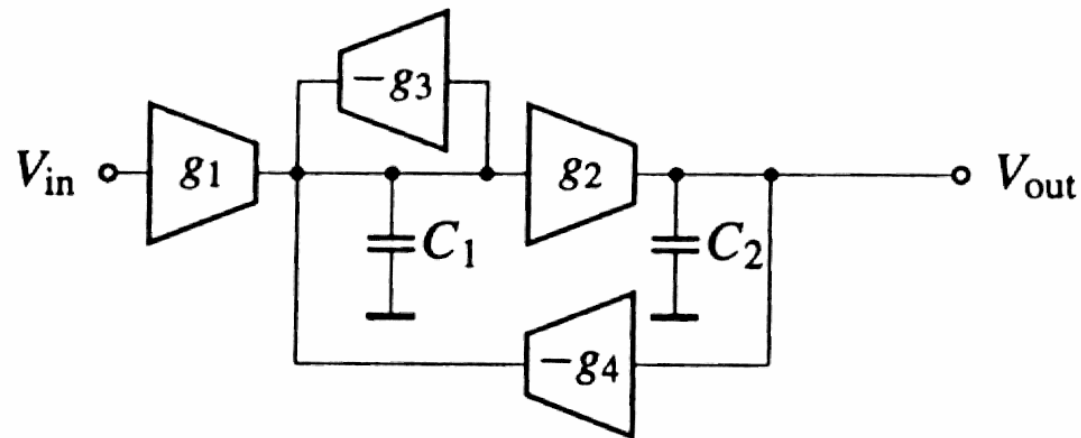

A differential pair as a transconductor

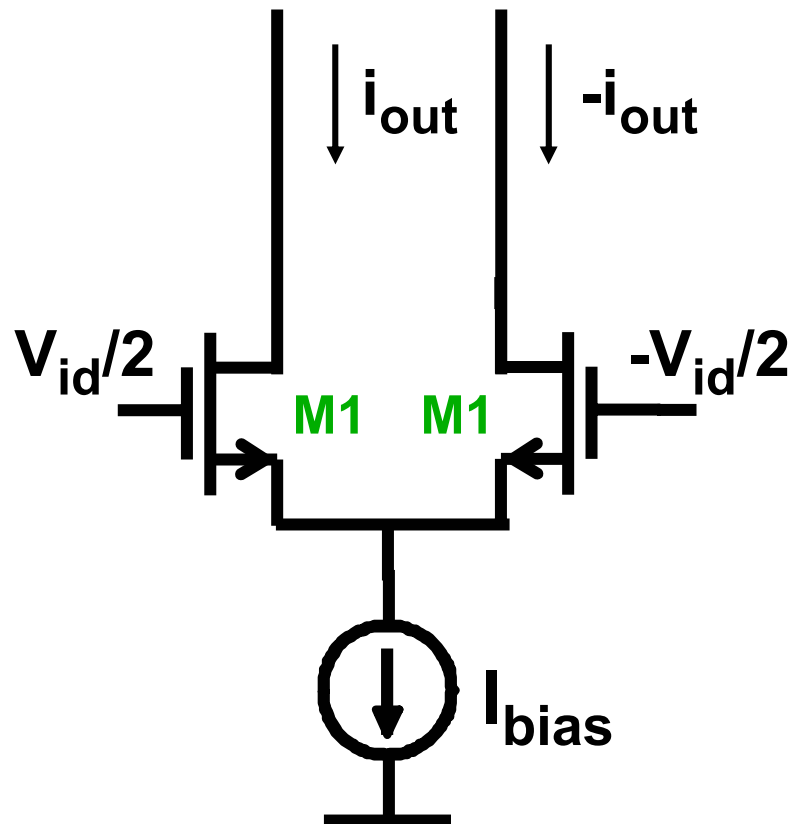

$$IM_3 = 3HD_3 = \frac{3}{32} U^2$$

$$U = \frac{V_{Id}}{V_{GS} - V_T}$$


U is the relative current swing

$$\text{Max. } V_{idptp} \approx 2\sqrt{2} (V_{GS} - V_T)$$

$$IP_3 \approx 3.3 (V_{GS} - V_T)$$

$HD_3 = -60$ dB for $V_{id} = 1$ V requires $V_{GS} - V_T = 6$ V !!!

Amplifier or transconductor ?

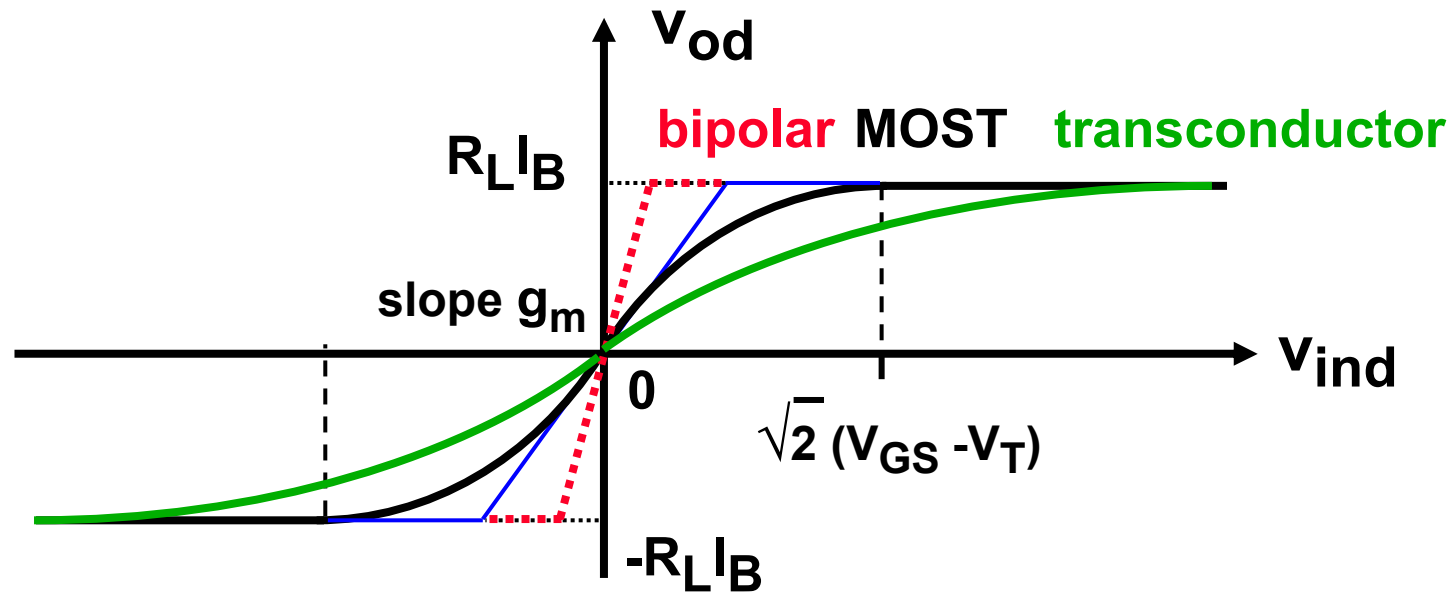

Transconductor :



Wide input range : low distortion

Small gain g_m

Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
 - Transconductors
 - use of transconductors
 - local feedback
 - parallel differential pairs
 - others
 - Tuning
- ◆ Comparison


Increasing the IP₃ by feedback

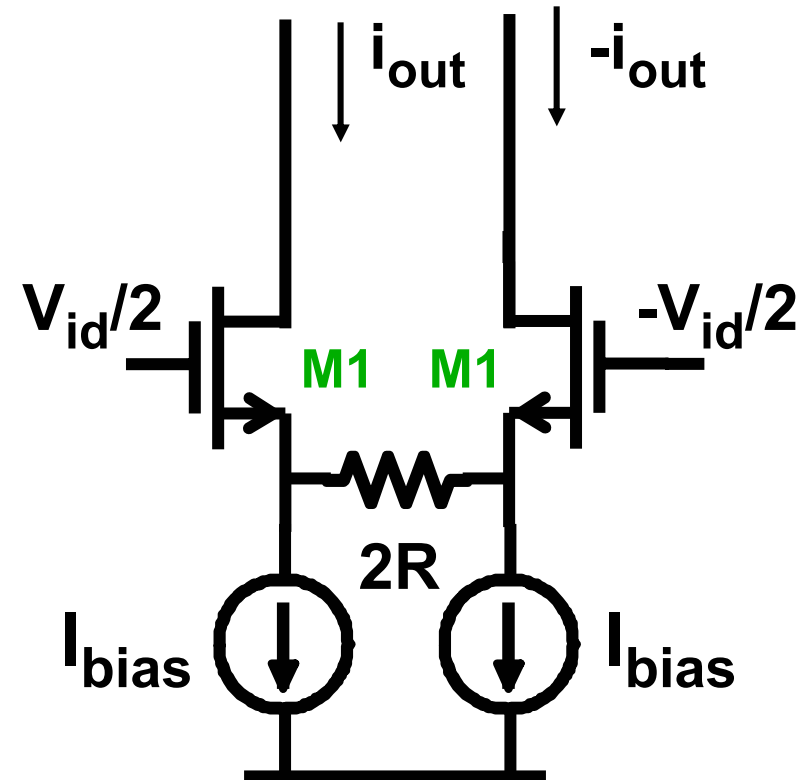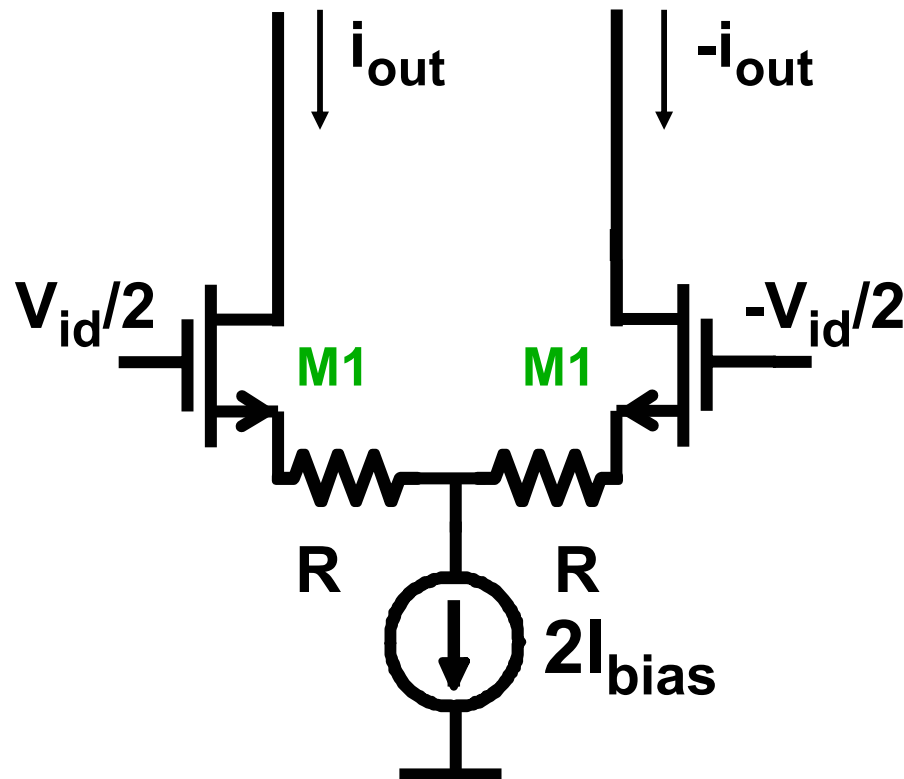


$$IP_3 \approx 3.3 (V_{GS} - V_T)(1 + g_{m1}R)^2 \quad HD_3/n^2 \quad n = 1 + g_{m1}R$$

$HD_3 = -60$ dB for $V_{id} = 1$ V requires $V_{GS} - V_T = 0.38$ V and $g_{m1}R = 3$!!!

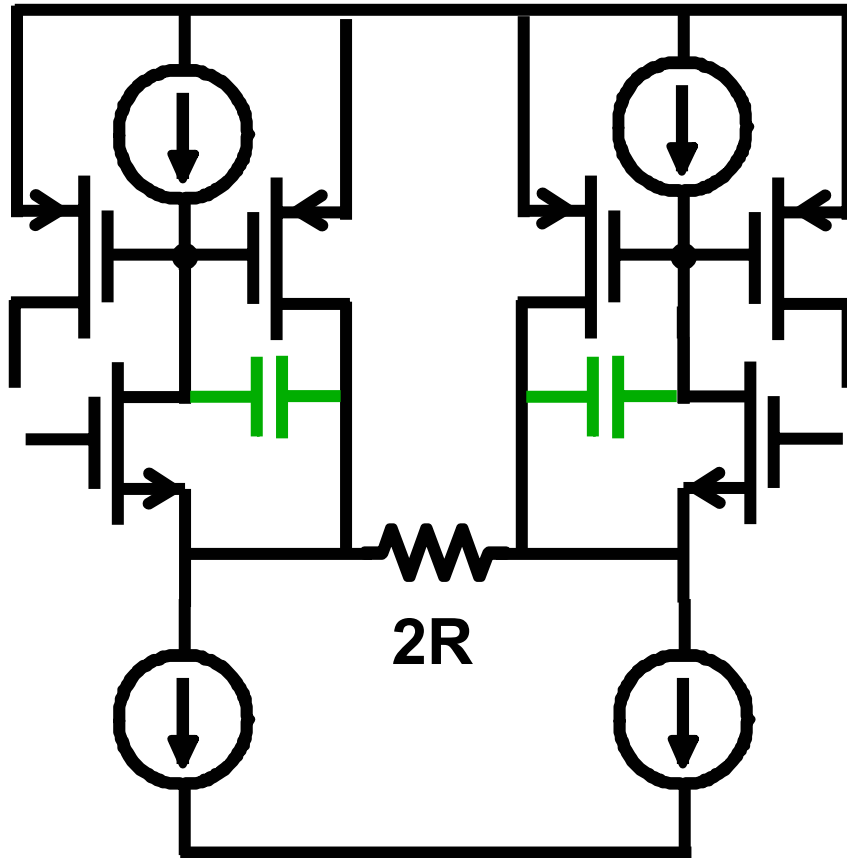Increasing the IP_3 by FB and high loop gain




Additional local FB

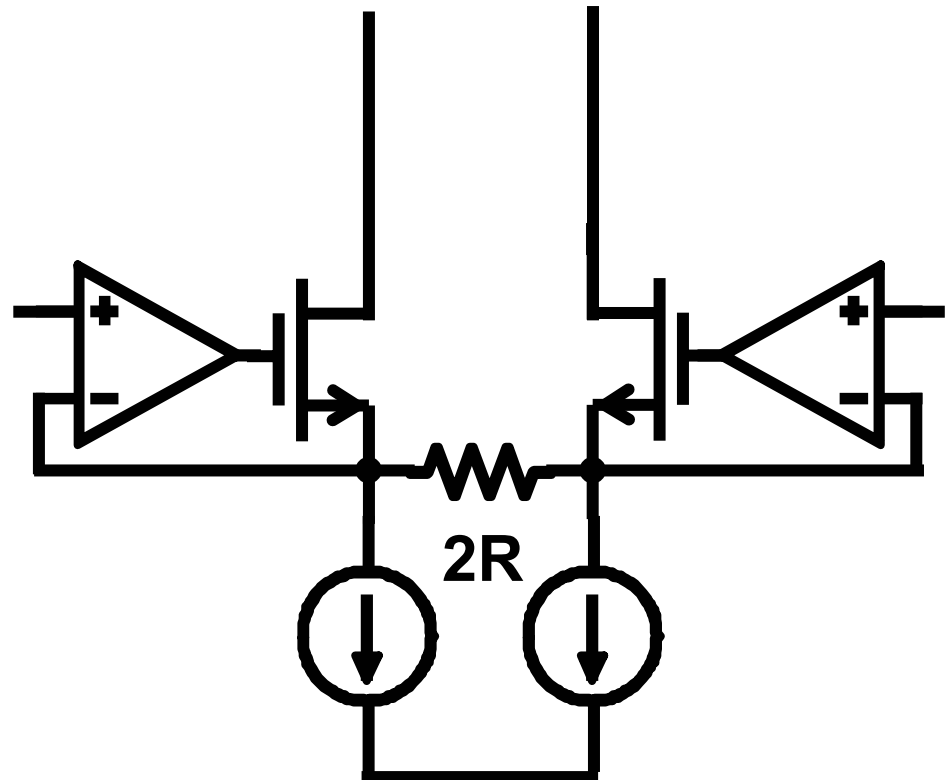


More FB with opamps

Tuneable resistances

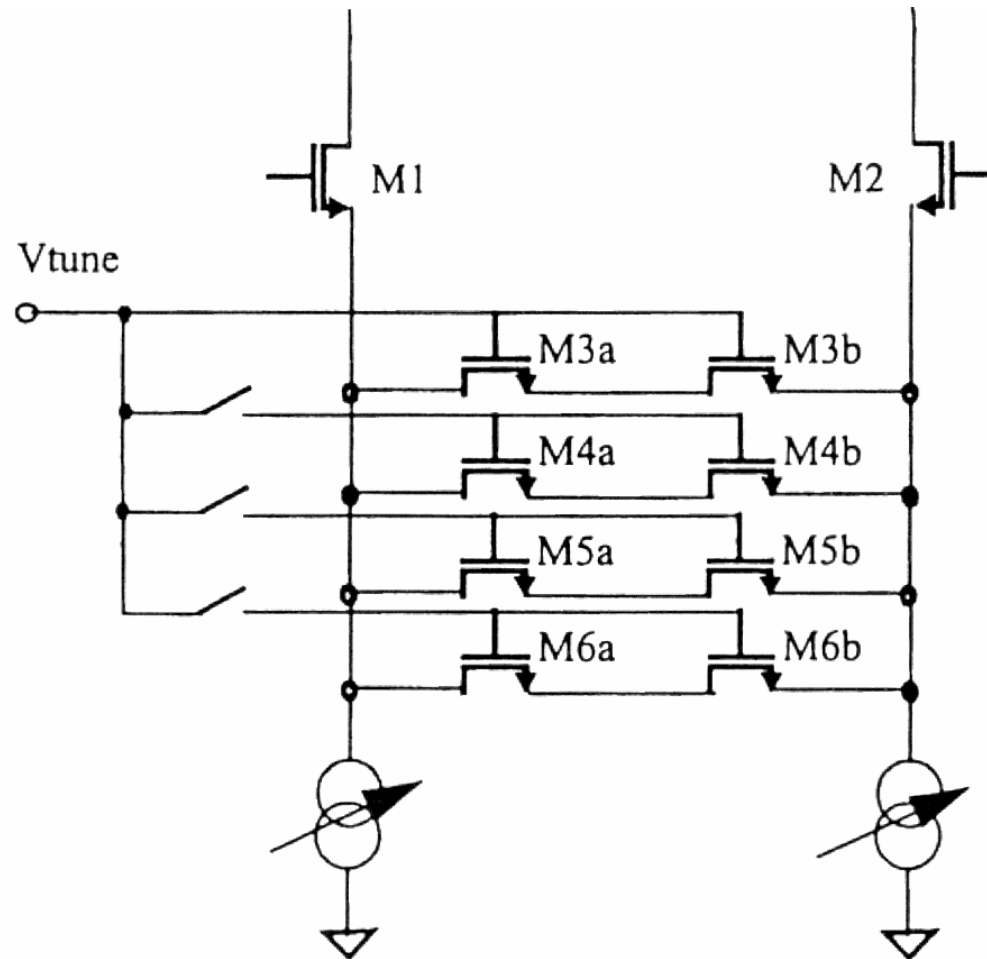

By tuneable feedback

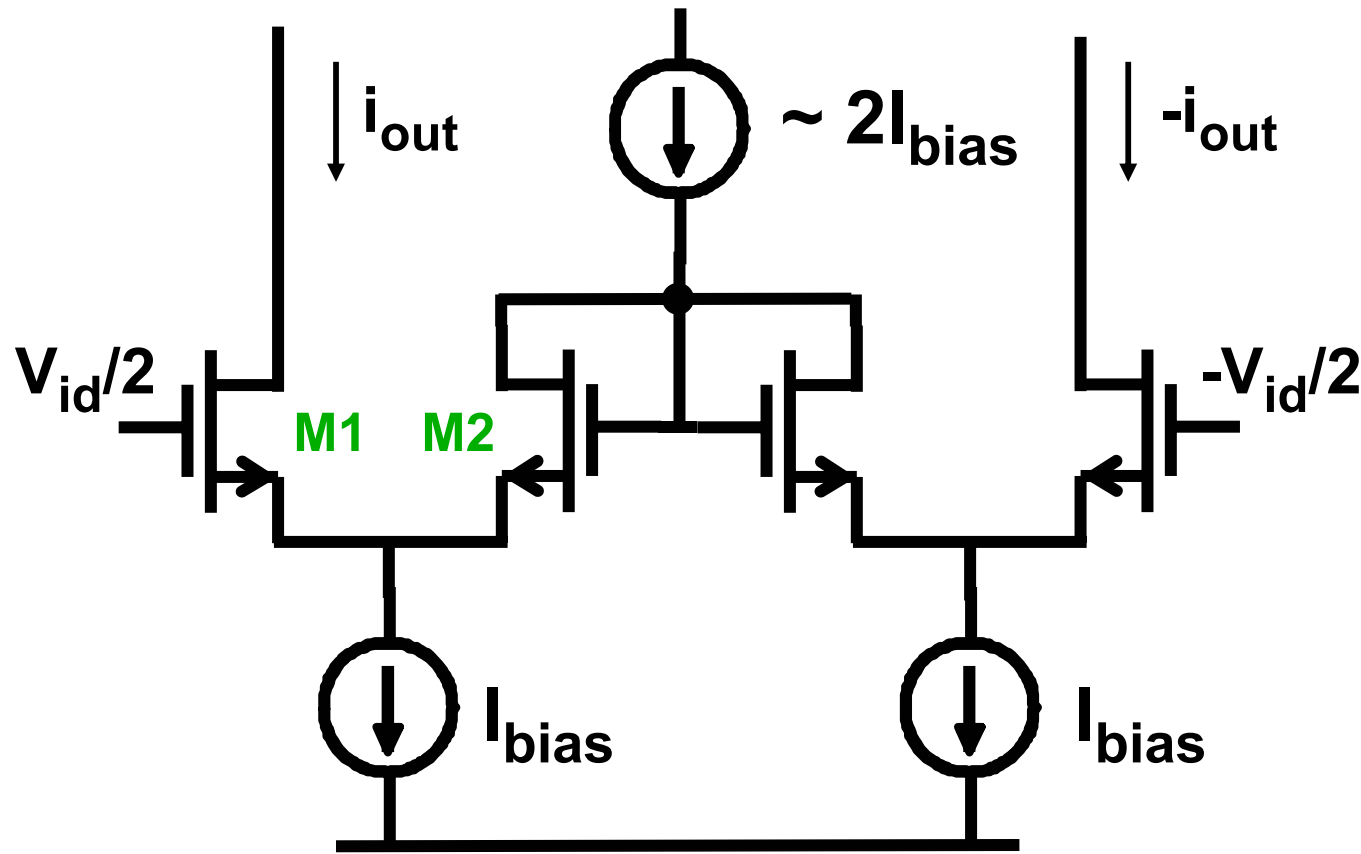


$$\frac{HD_3}{n^2}$$

$$n = 1 + \frac{g_{m1}}{g_{m2}}$$

$$IP_3 \approx 3.3 (V_{GS} - V_T)n^2$$

Ref. Torrance et al CAS Nov.85, 1097-1104

By nonlinear feedback (input)

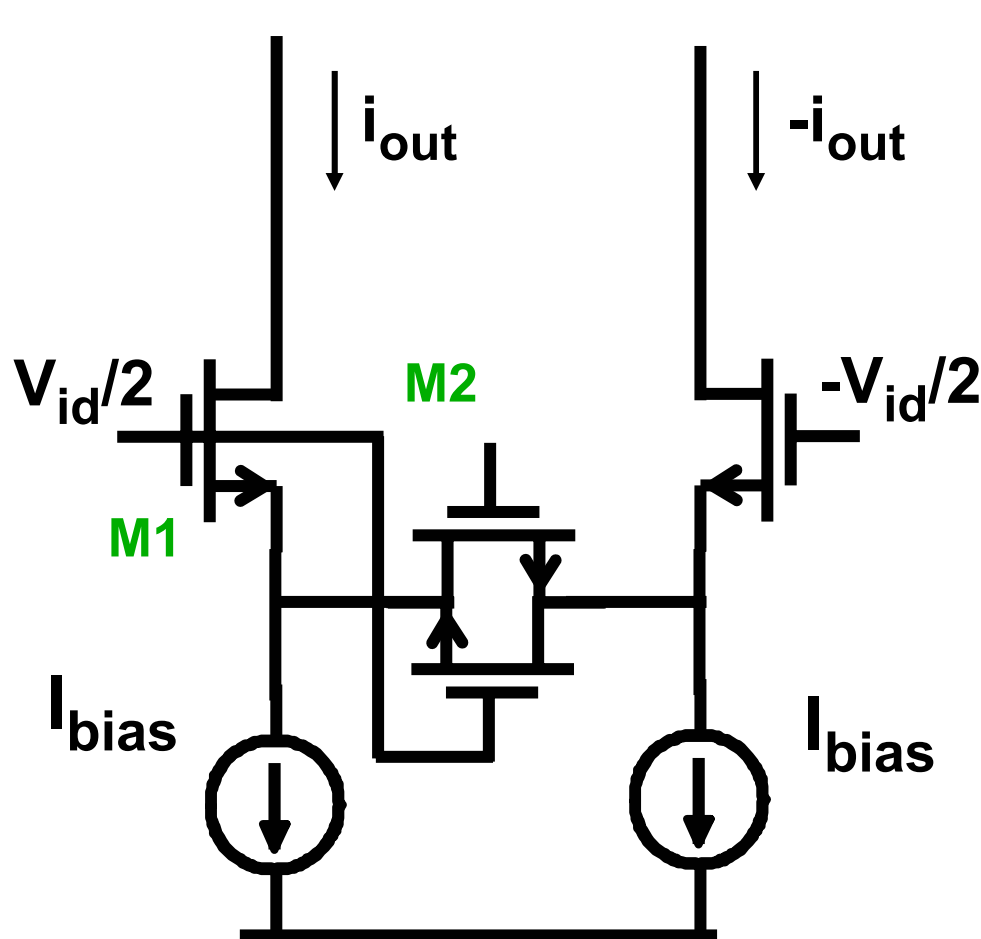

$$g_{mtot} = \frac{I_{bias}}{n (V_{GS1} - V_T)}$$

$$n = 1 + \frac{\beta_1}{4\beta_2} \frac{HD_3}{n^2}$$

$$IP_3 \approx 3.3 (V_{GS1} - V_T) n^2$$


No extra current

No extra CM node !

But limited $V_{GS}-V_T$!


Ref. Krummenacher JSSC June 88, 750-758

By nonlinear feedback (as load)

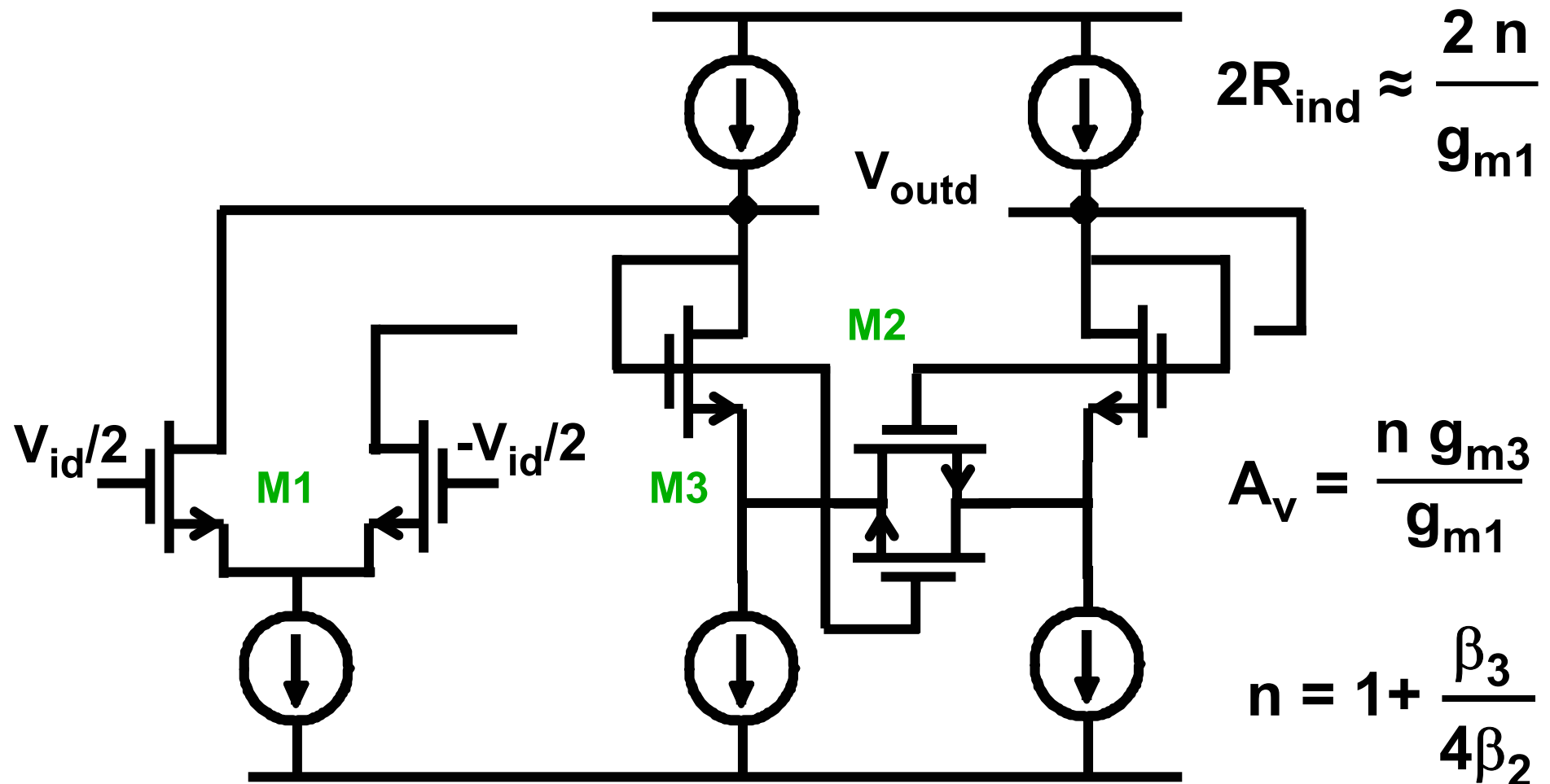


Ref. Menolfi JSSC July 97, 968-976

Low-distortion combination : power !

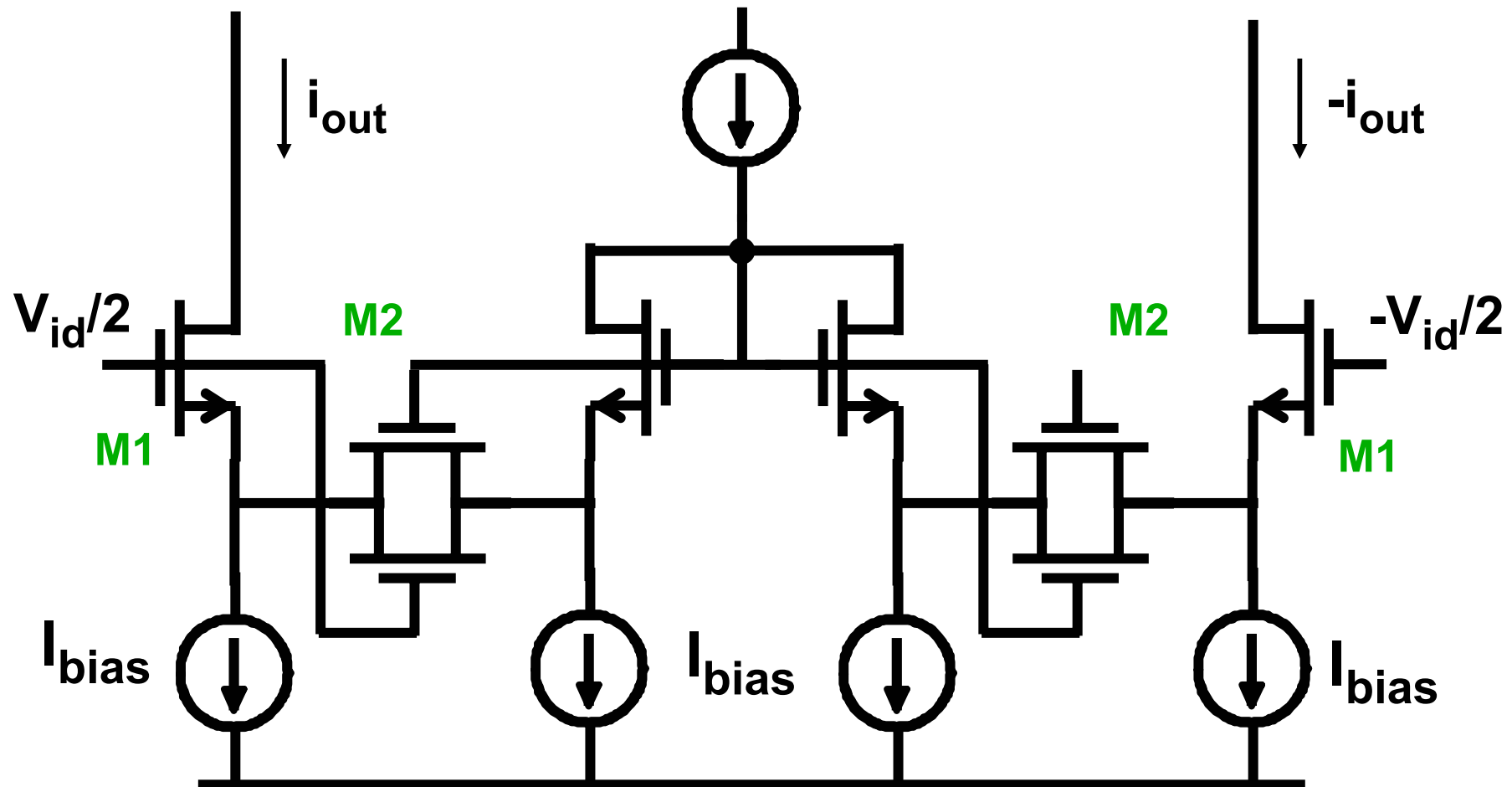


Reduced distortion by cross-coupling

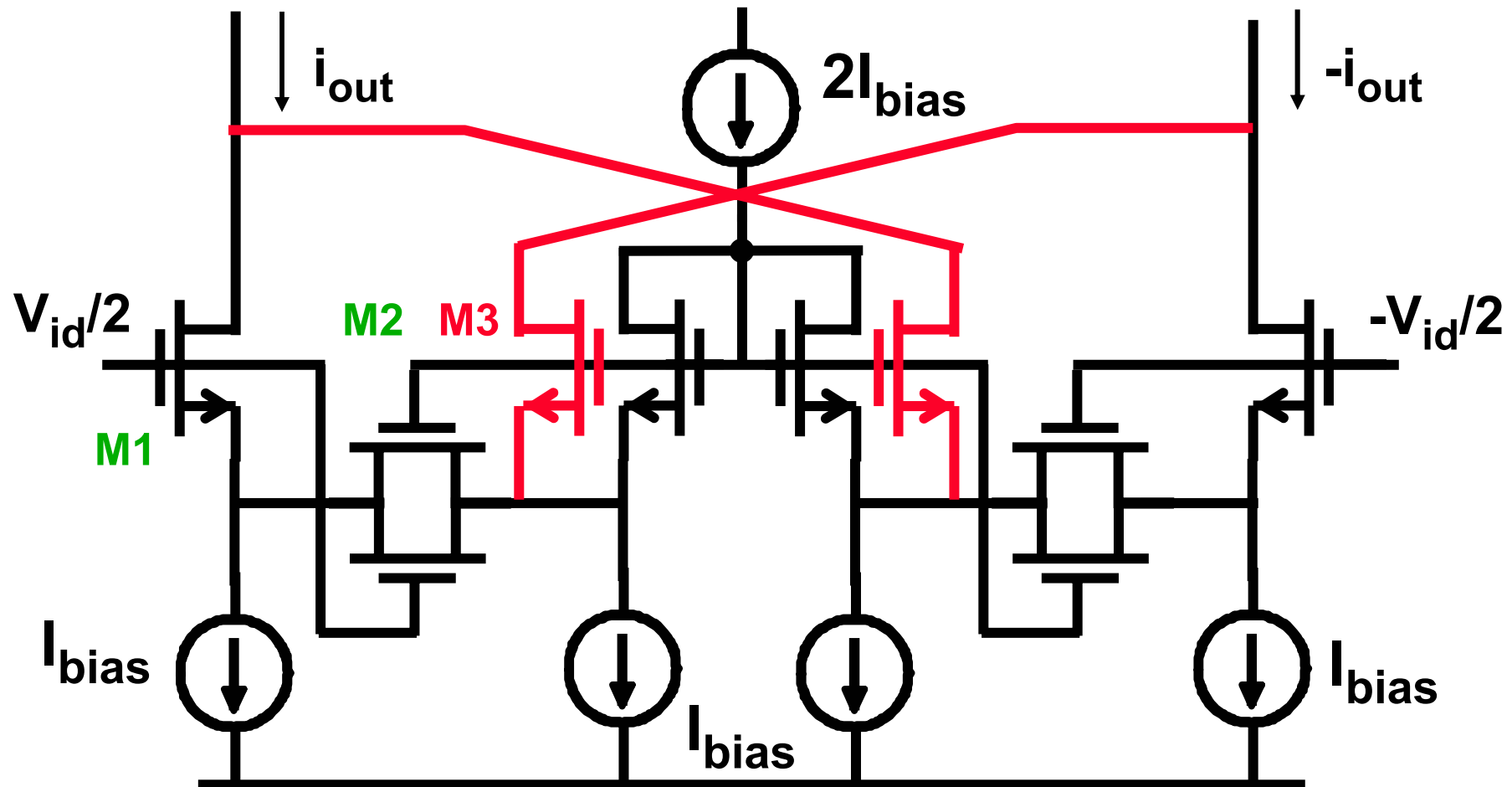


Ref. Silva-Martinez JSSC July 91,946-955

Comparison (simulations)

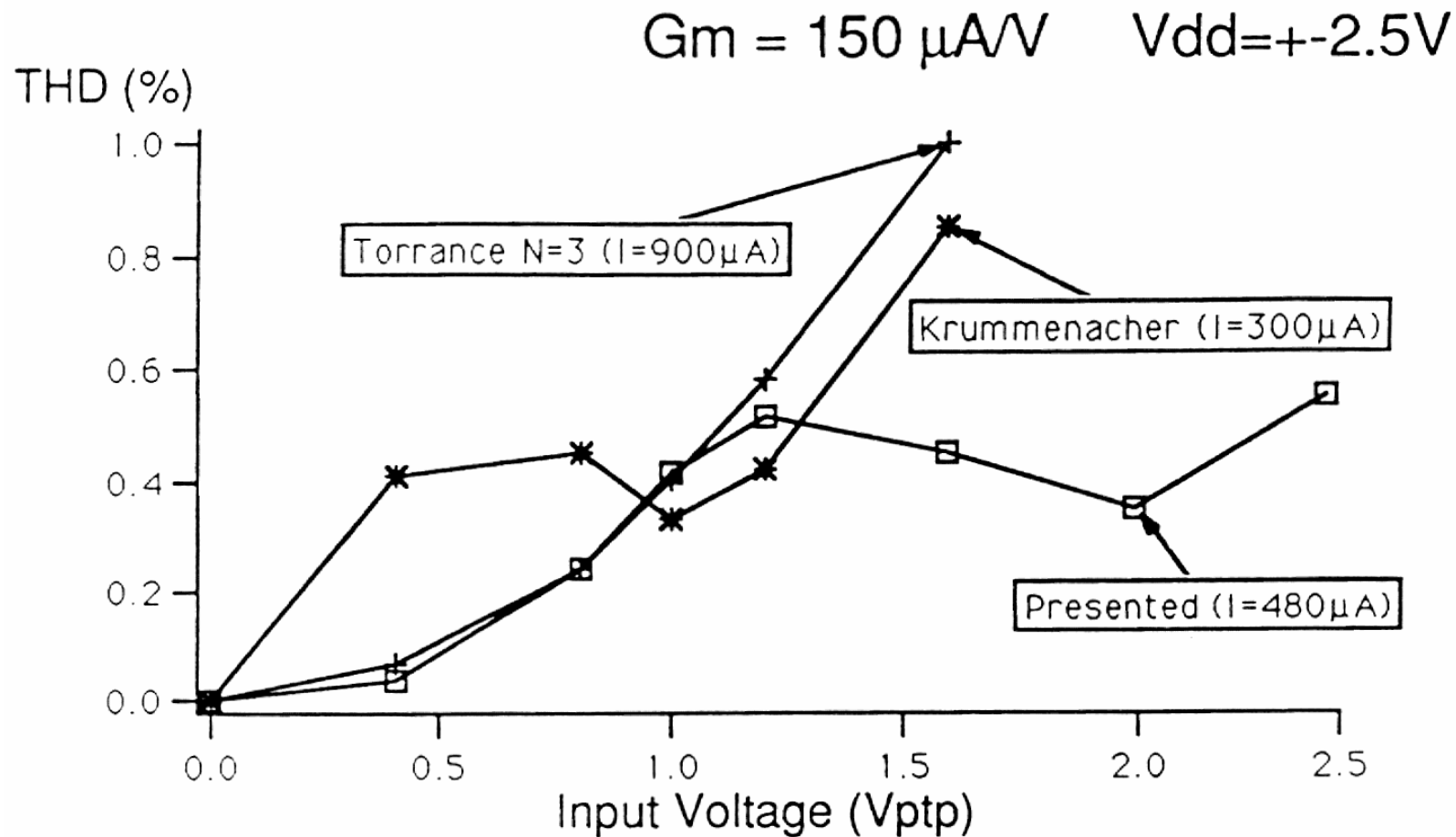


Measured THD for transconductor

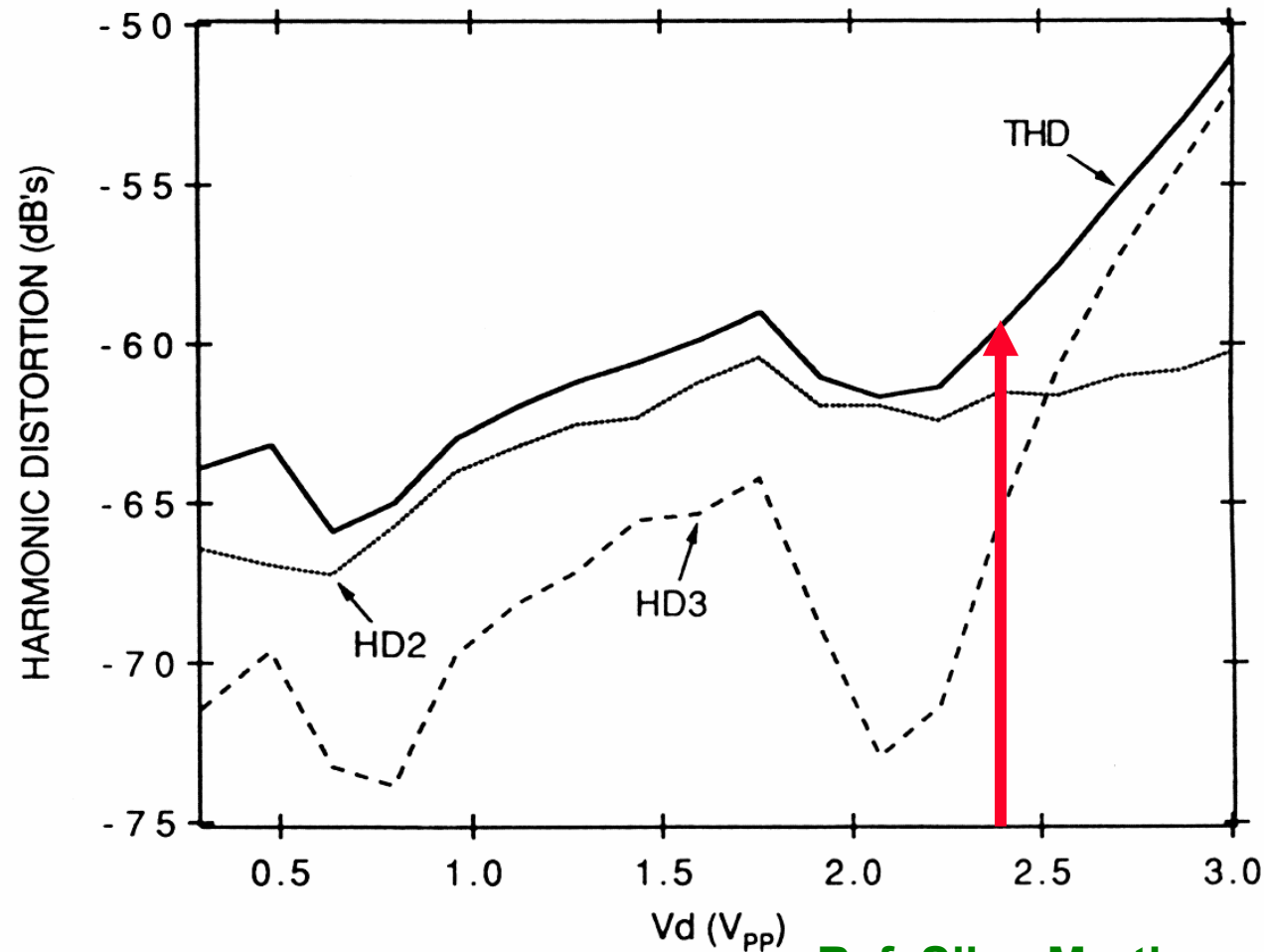

**THD \approx
- 60 dB
2.4 V_{ptp}
Input Voltage**

Ref. Silva-Martinez JSSC July 91,946-955

Linear transconductor with opamps

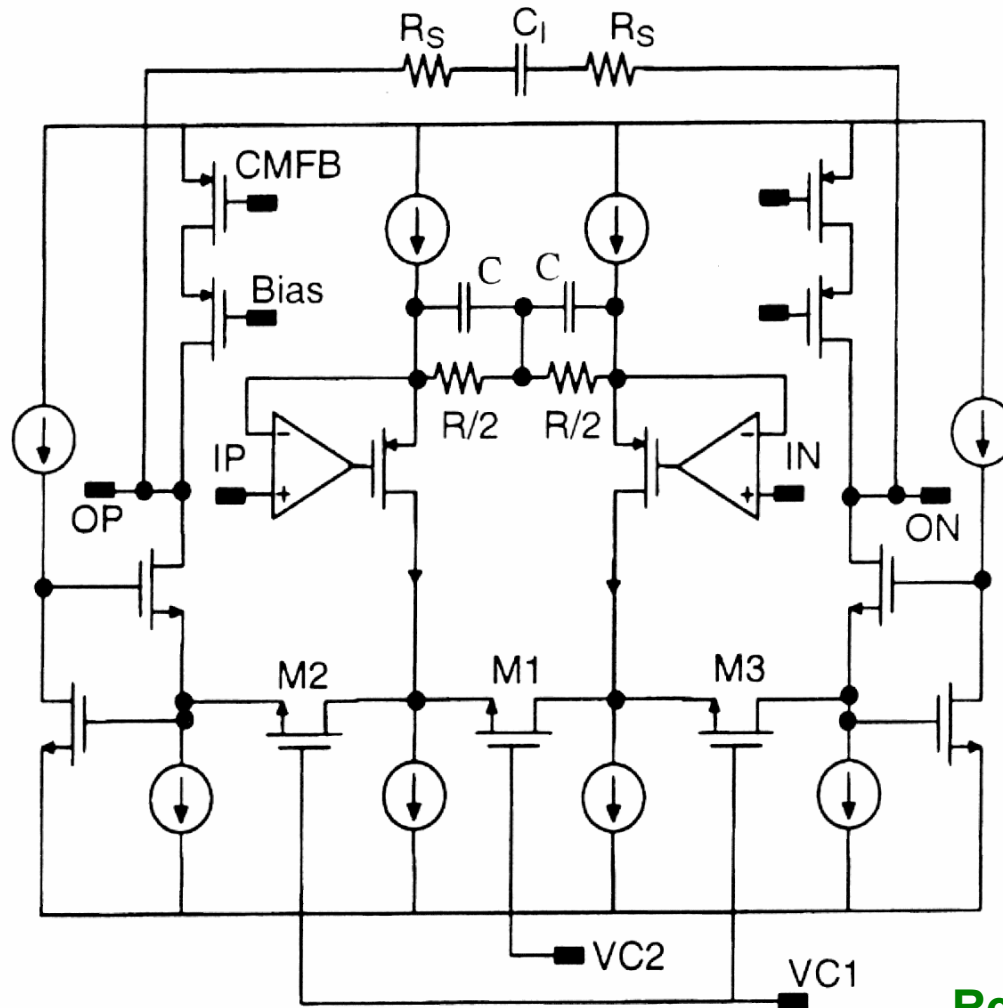


Ref. Chang JSSC March 97,388-397

Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
 - Transconductors
 - use of transconductors
 - local feedback
 - parallel differential pairs
 - others
 - Tuning
- ◆ Comparison

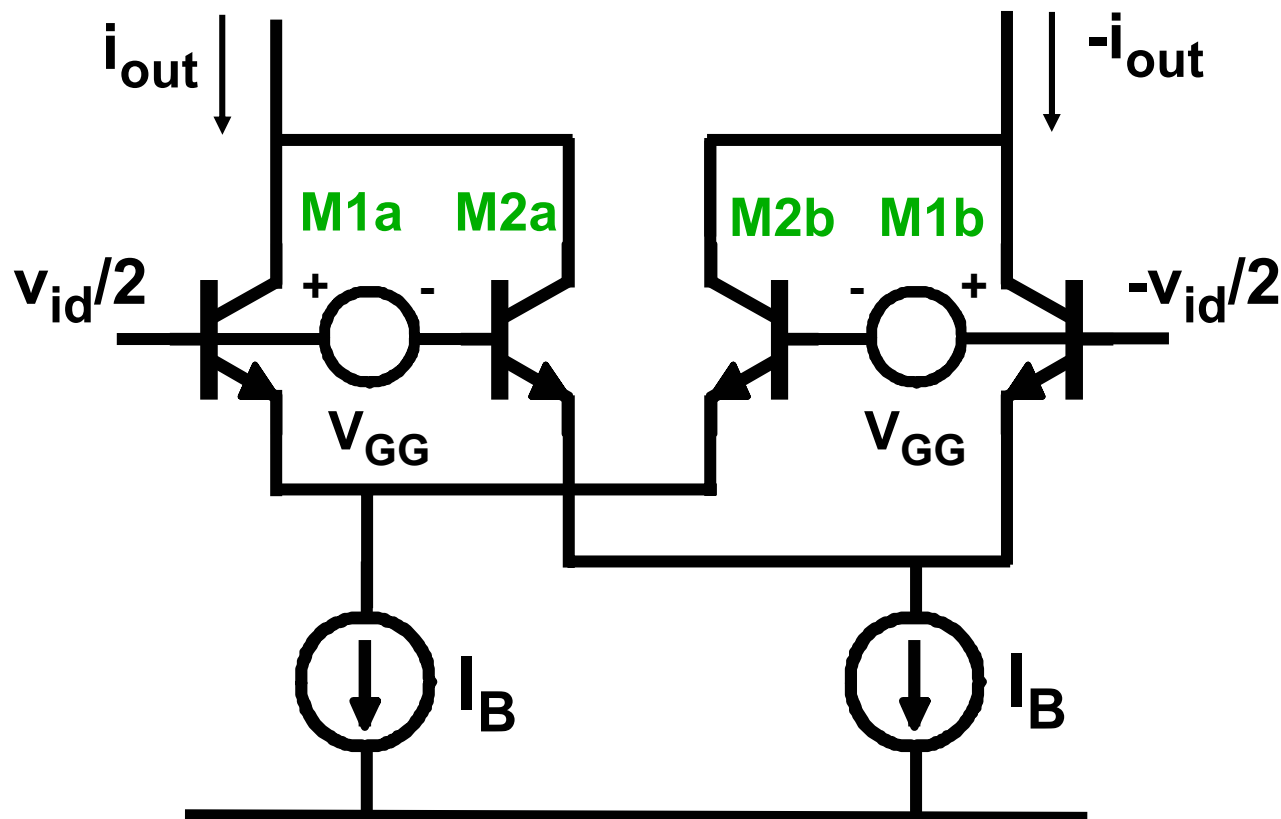
Parallel differential pairs with offset Voltages




$$V_{GG} \approx 1.3 kT/q$$
$$\approx 34 \text{ mV}$$

Ref. Gilbert, JSSC
Dec. 82, 1179-1191
Voorman ECCTD 83
Tanimoto, .. JSSC
July 91, 937-945

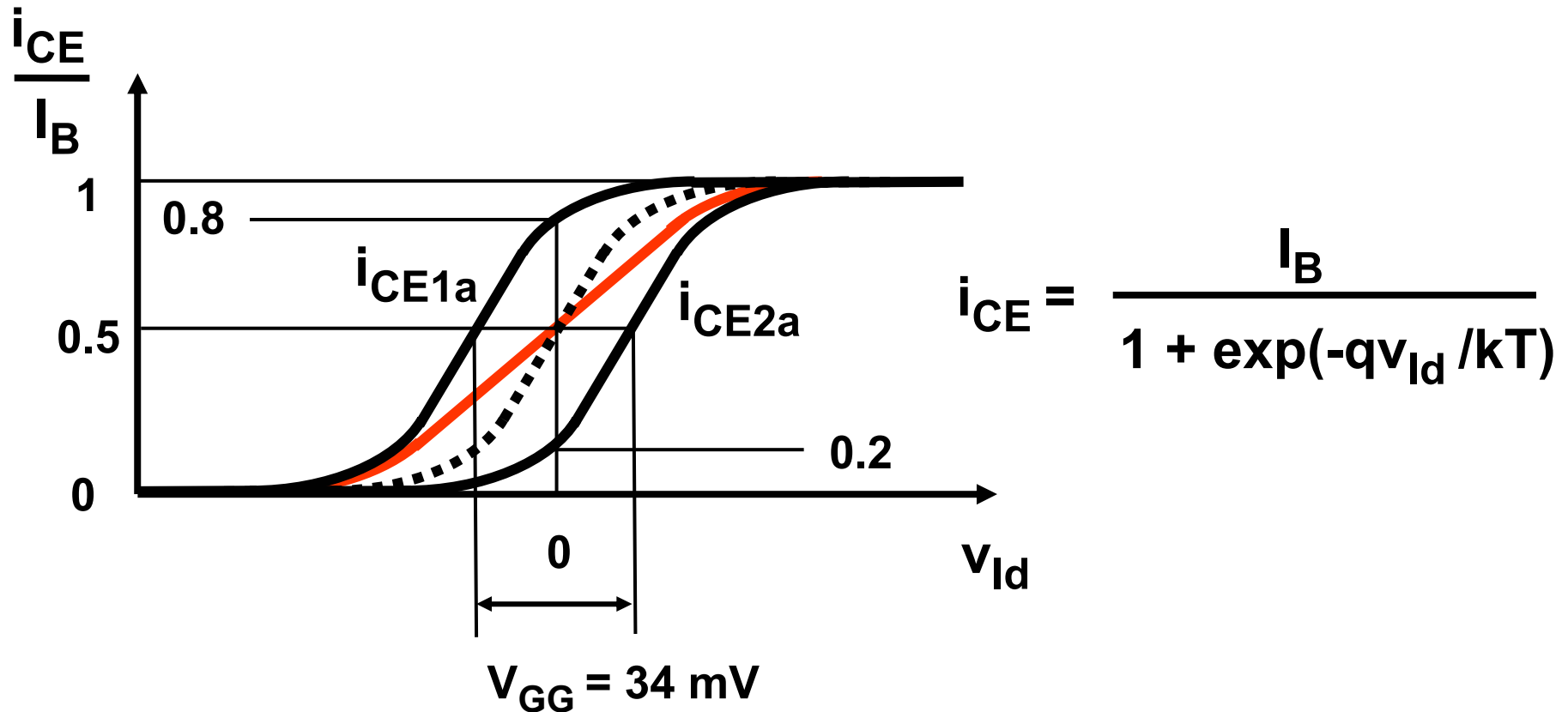Transfer characteristics of parallel diff. pairs



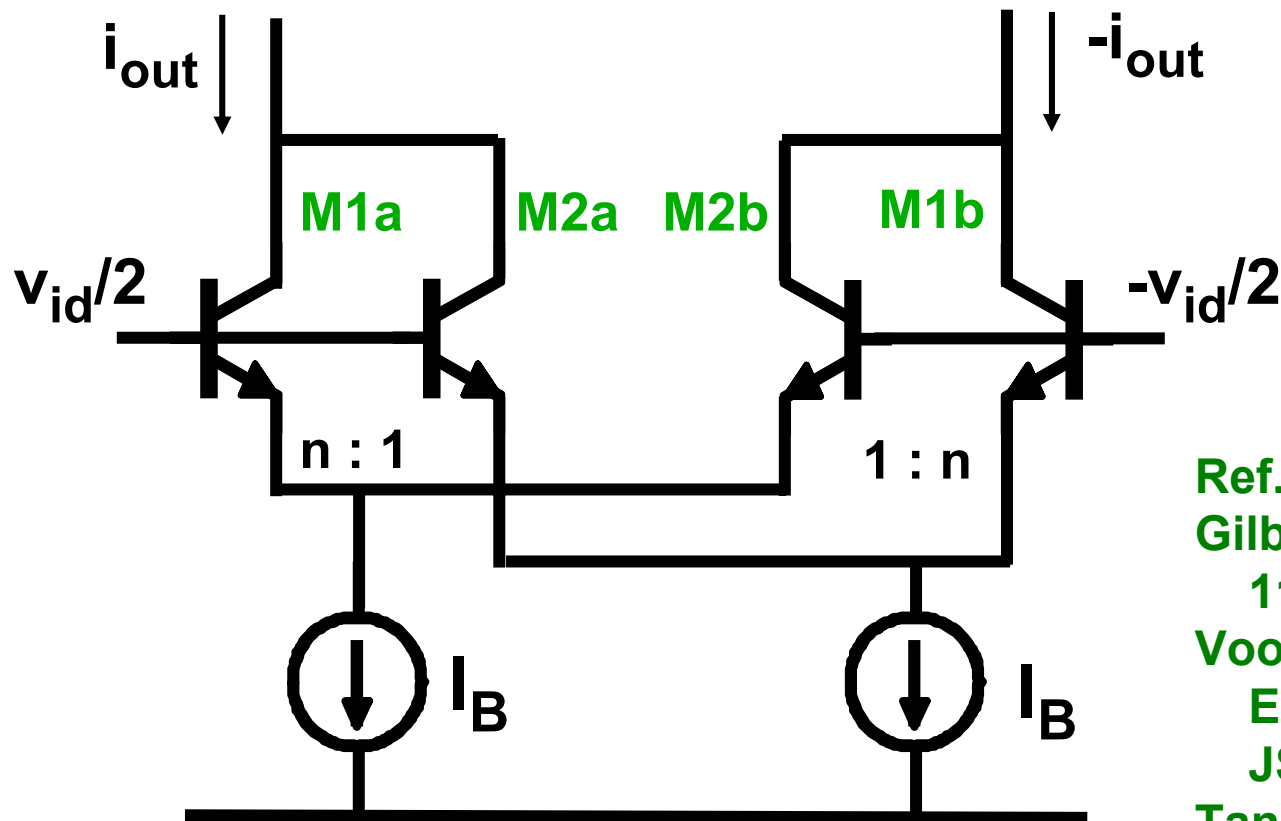
Parallel diff.pairs with different transistor sizes



Bipolar : $n \approx 4$

Ref. in bipolar :
Gilbert, JSSC, Dec. 82,
1179-1191
Voorman, ECCTD 83
ESSCIRC 85
JSSC, Aug.00, 1097-1108
Tanimoto, .. JSSC
July 91, 937-945
De Veirman, JSSC
March 92, 324-331


Paralleling four differential pairs

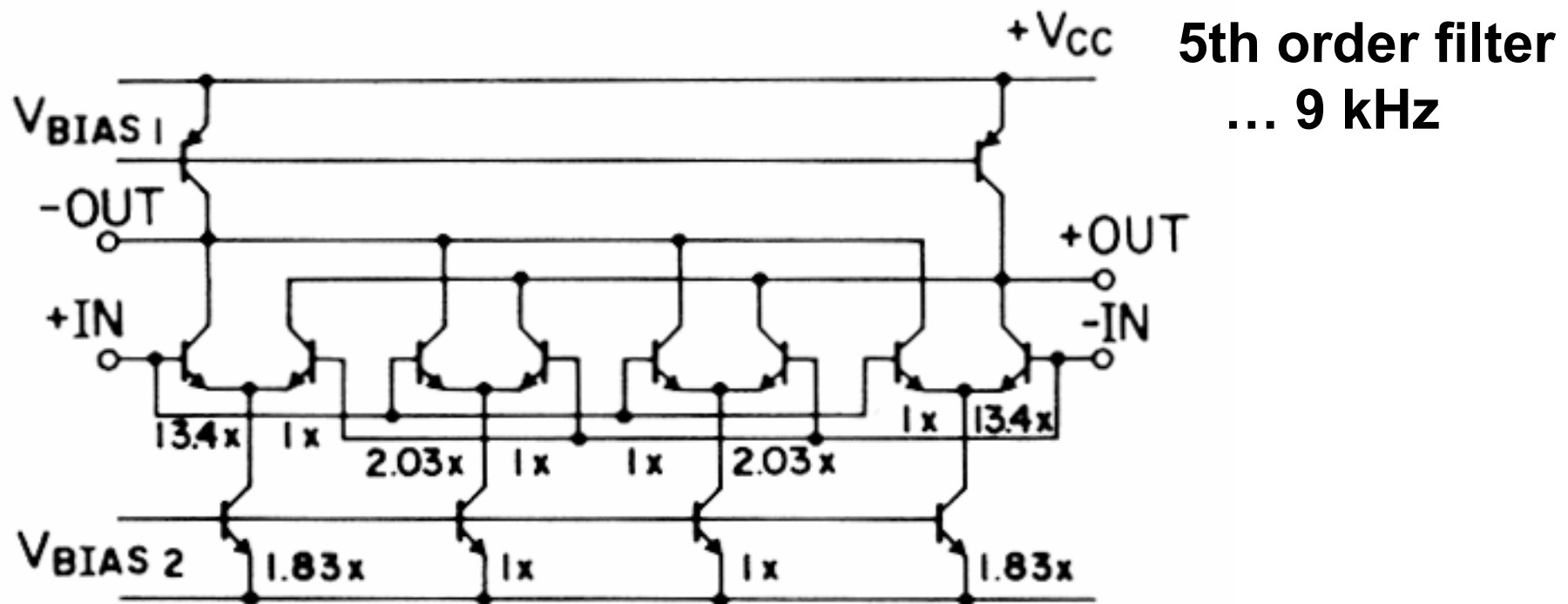


Input range 160 mV_{ptp} (1% THD)

Ref. Tanimoto,... JSSC July 91, 937-945

Dual-input transconductor

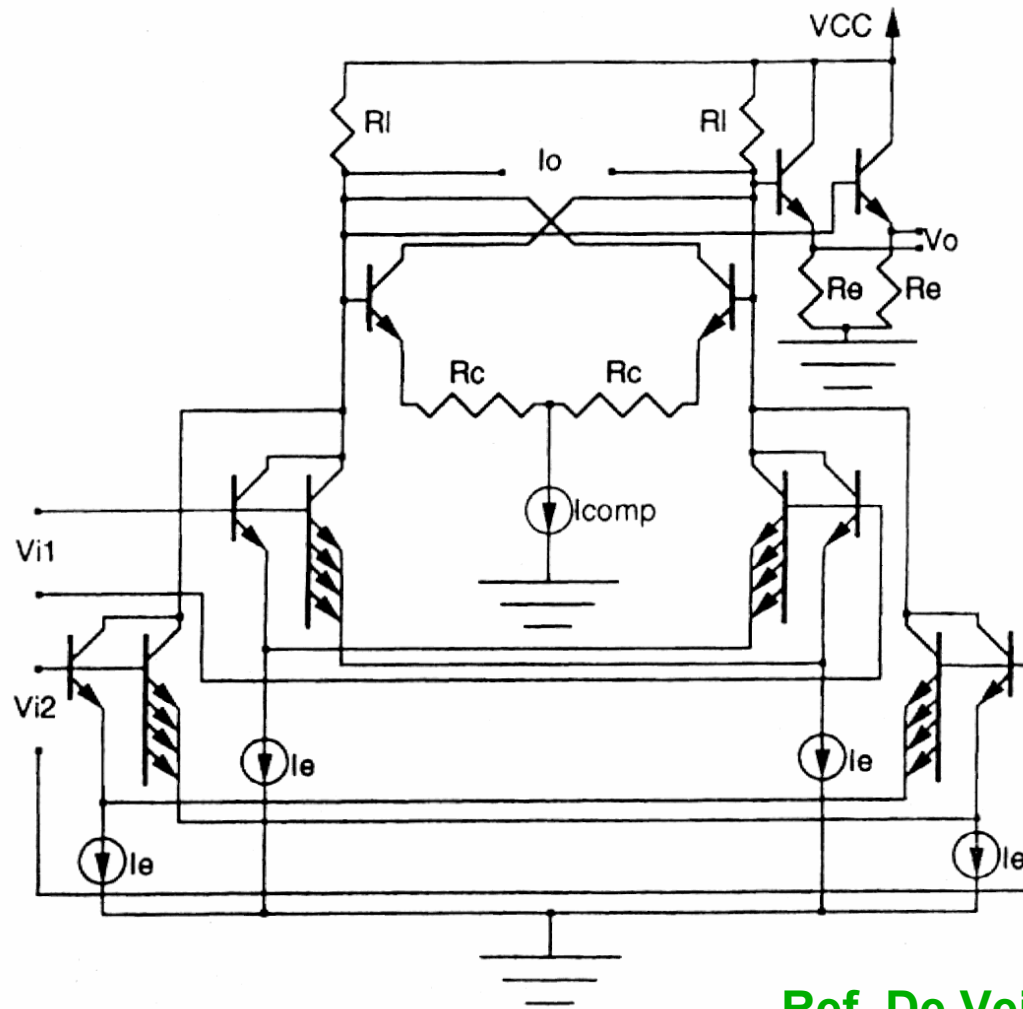


**7th order filter
2 ... 10 MHz**

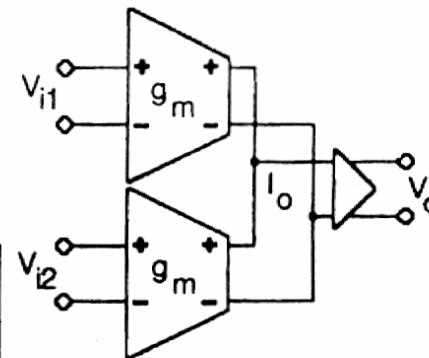

**Input range
96 mV_{ptp} (1% THD)**

Ref. De Veirman, JSSC, March 92, 324-331

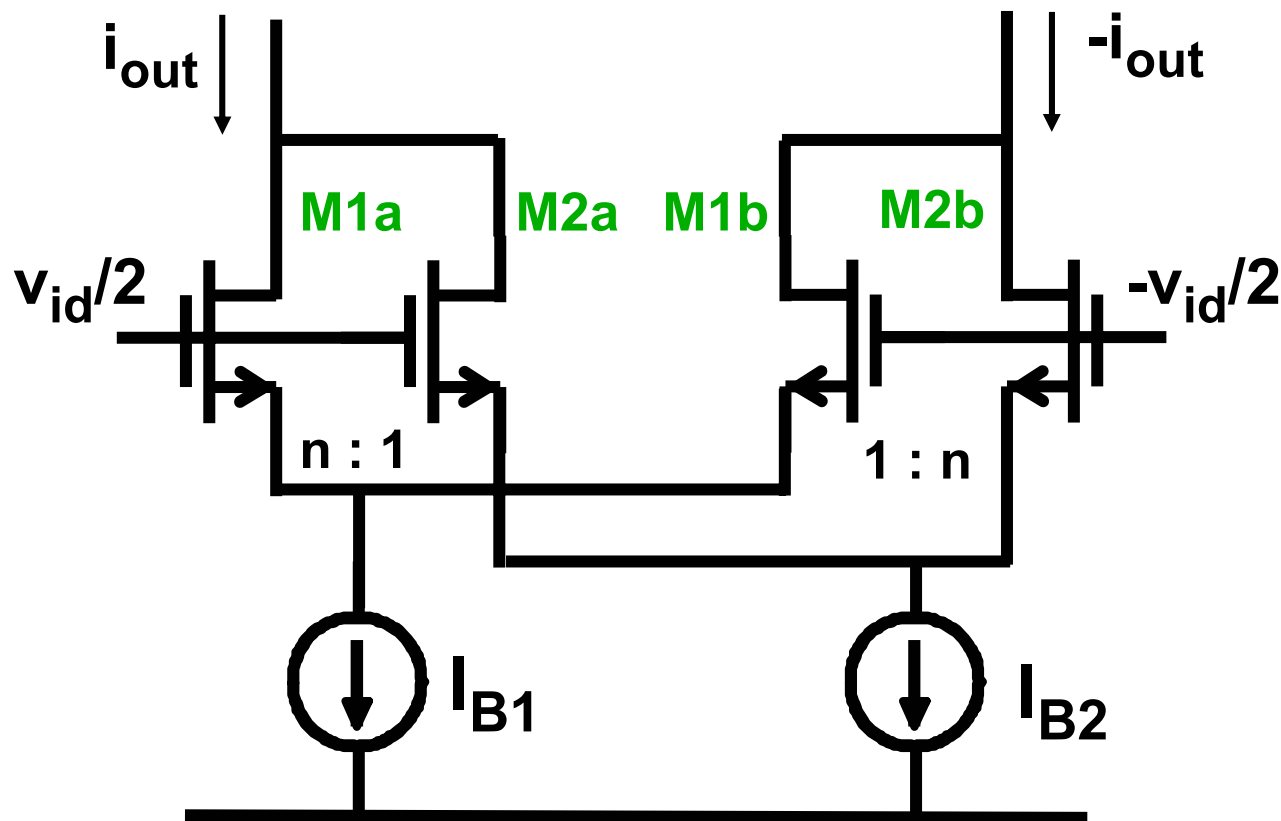Parallel diff.pairs with different transistor sizes



MOST : $n \approx 5$

Parameters :

$$\alpha = I_{B2} / I_{B1}$$

$$v = V_{GST1} / V_{GST2}$$

$$V_{GST} = V_{GS} - V_T$$

$$n = \alpha v^2$$

Ref. in CMOS :

Nedungadi, CAS


Oct 84, 891-894

Voorman, JSSC

Aug.00, 1097-1108


Luh, ESSCIRC 00

Cross-coupling for linearity and swing

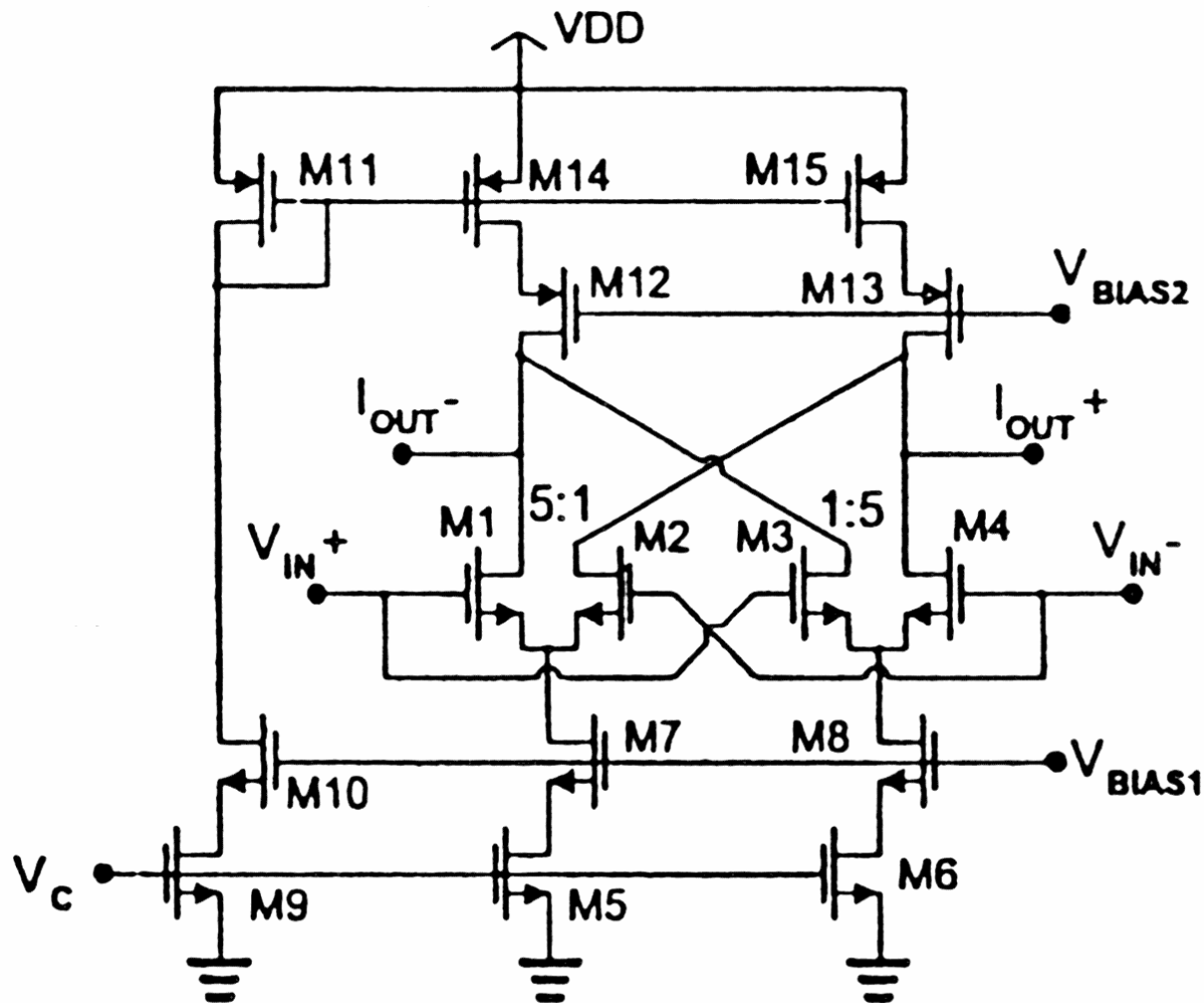

Ref. Luh, USC, ESSCIRC 2000, 72-75

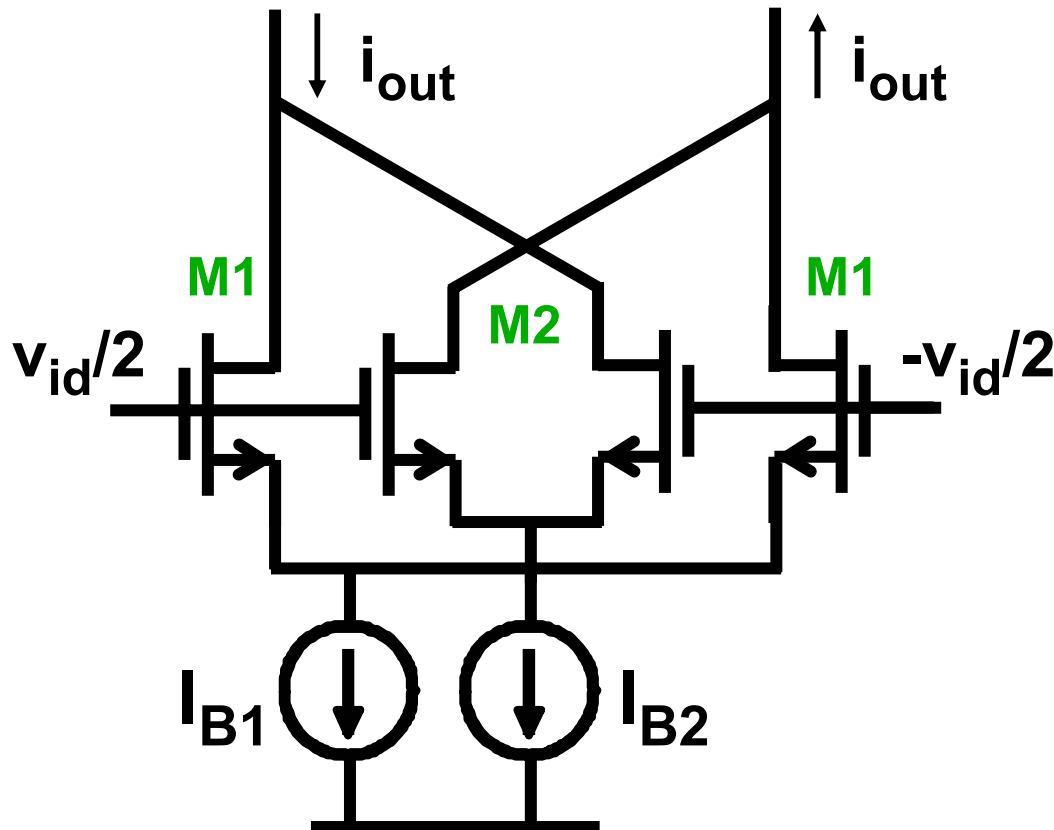Multiplier or Amp. with distortion cancellation



Parameters :


$$\alpha = I_{B2} / I_{B1}$$

$$v = V_{GST1} / V_{GST2}$$

$$V_{GST} = V_{GS} - V_T$$


Ref. Gilbert, JSSC Dec. 68, 365-373

Cross-coupling and source resistors

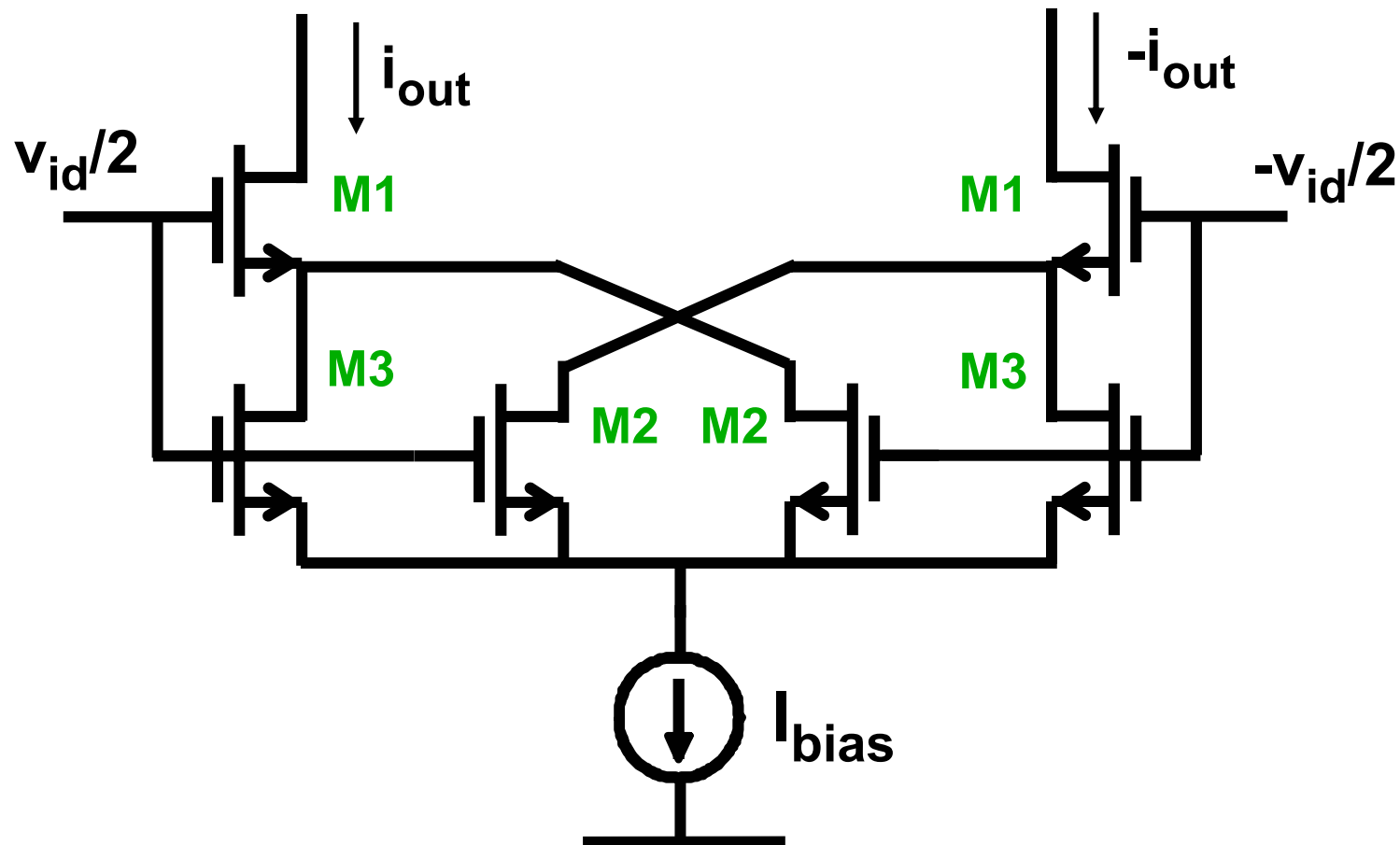

Ref. Prodanov, ESSCIRC 2001, 488-491

Cross-coupling and source followers

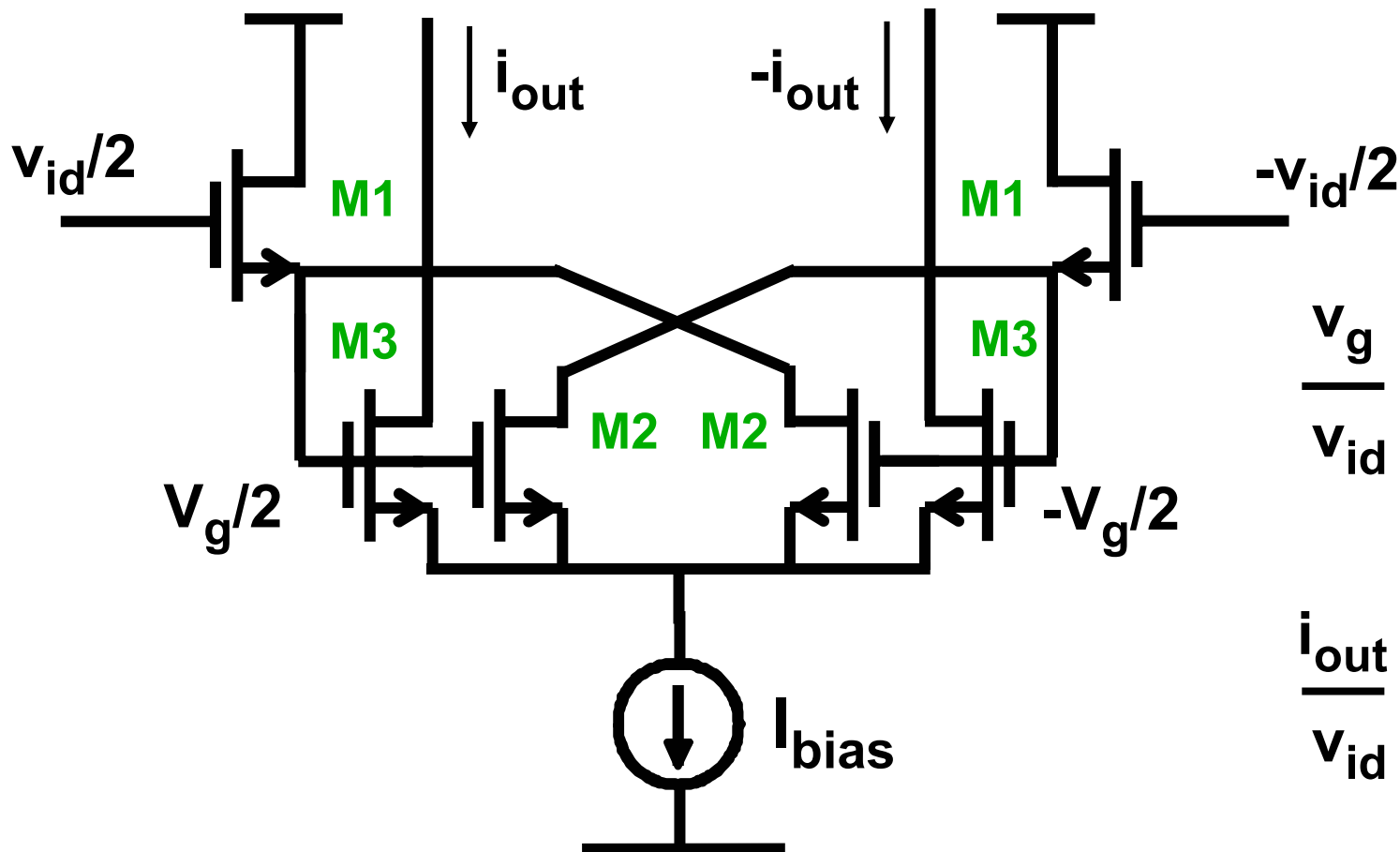

$$\frac{v_g}{v_{id}} = \frac{1}{1 - \frac{g_{m2}}{g_{m1}}}$$



$$\frac{i_{out}}{v_{id}} = \frac{g_{m3}}{1 - \frac{g_{m2}}{g_{m1}}}$$

Ref. Van Engelen, JSSC Dec.99, 1753-1764

Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
 - Transconductors
 - use of transconductors
 - local feedback
 - parallel differential pairs
 - others
 - Tuning
- ◆ Comparison



Linearity CMOS amplifier

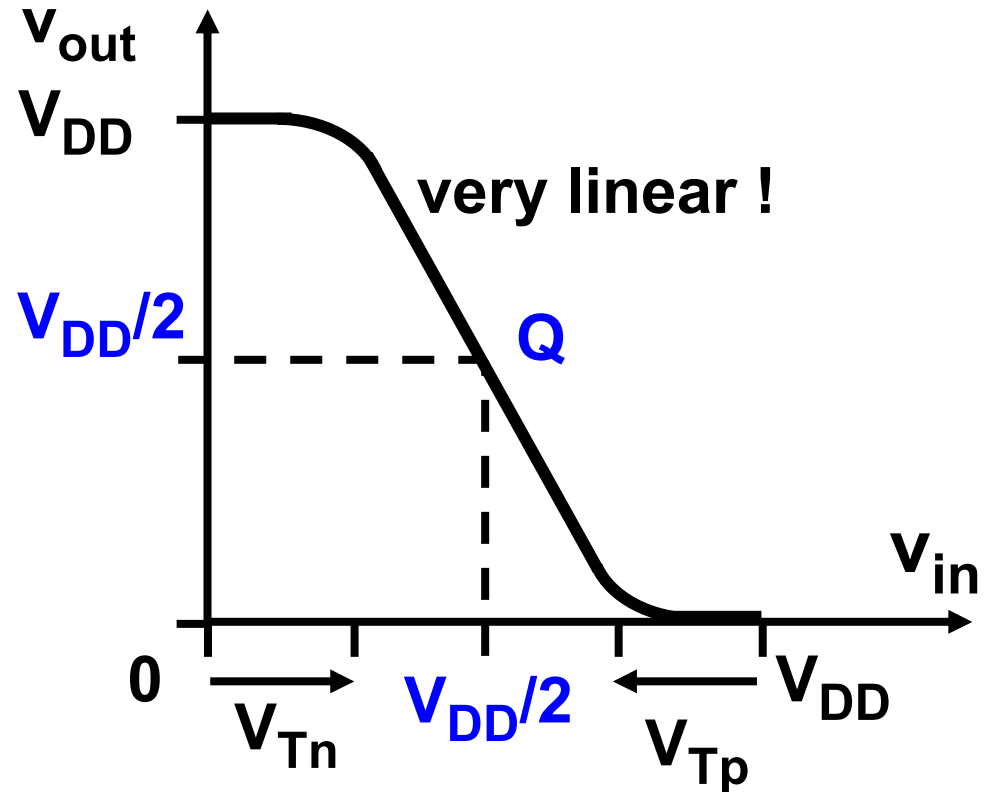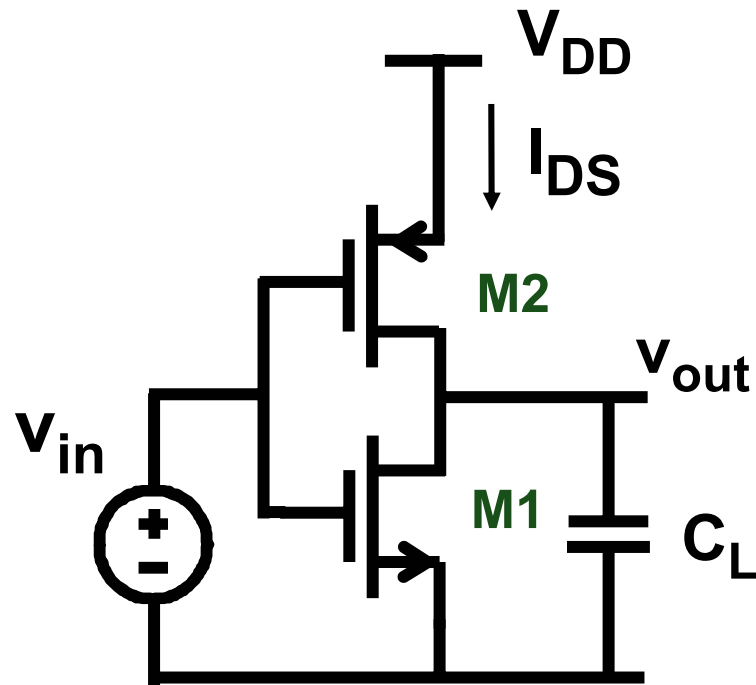

$$\text{if } K'_n \frac{W_n}{L_n} = K'_p \frac{W_p}{L_p}$$


$$V_{in} = V_{out} = \frac{V_{DD}}{2}$$

Linearized transconductors

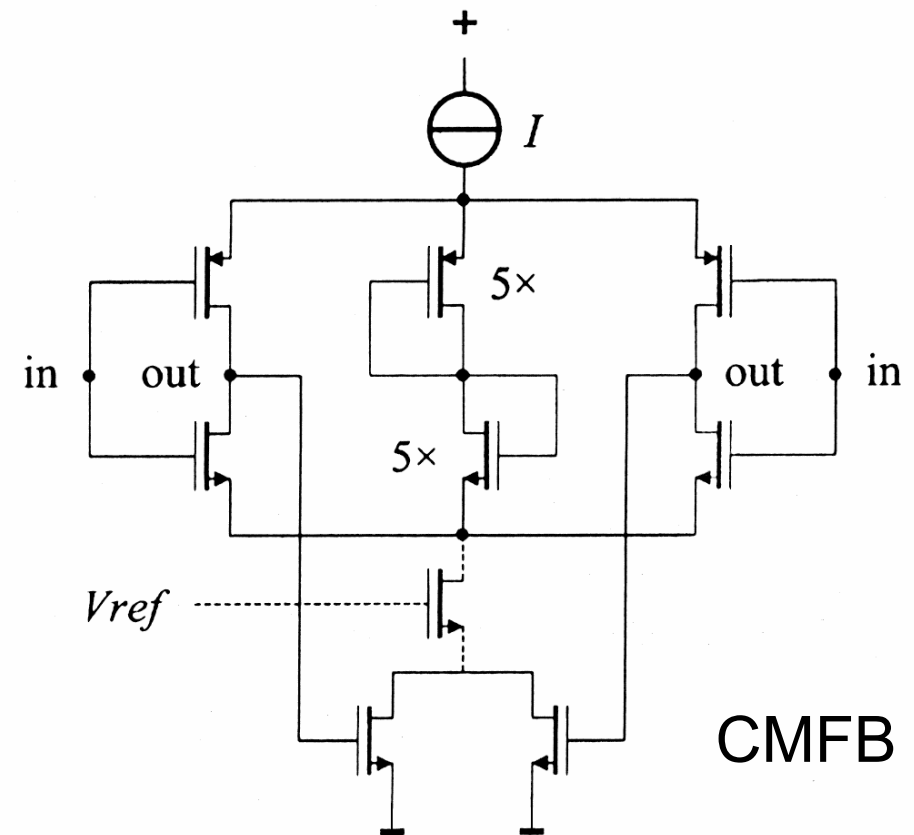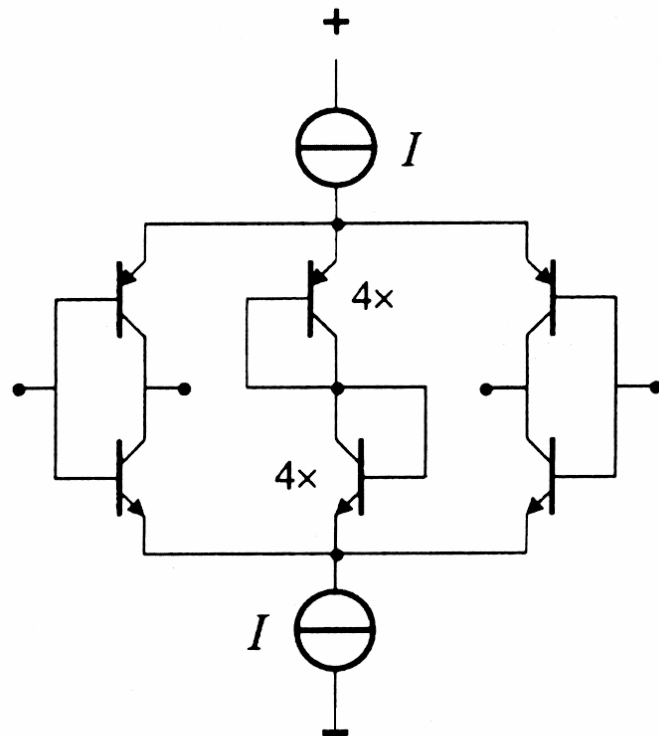


Ref. Voorman, JSSC, Aug.2000, 1097-1108

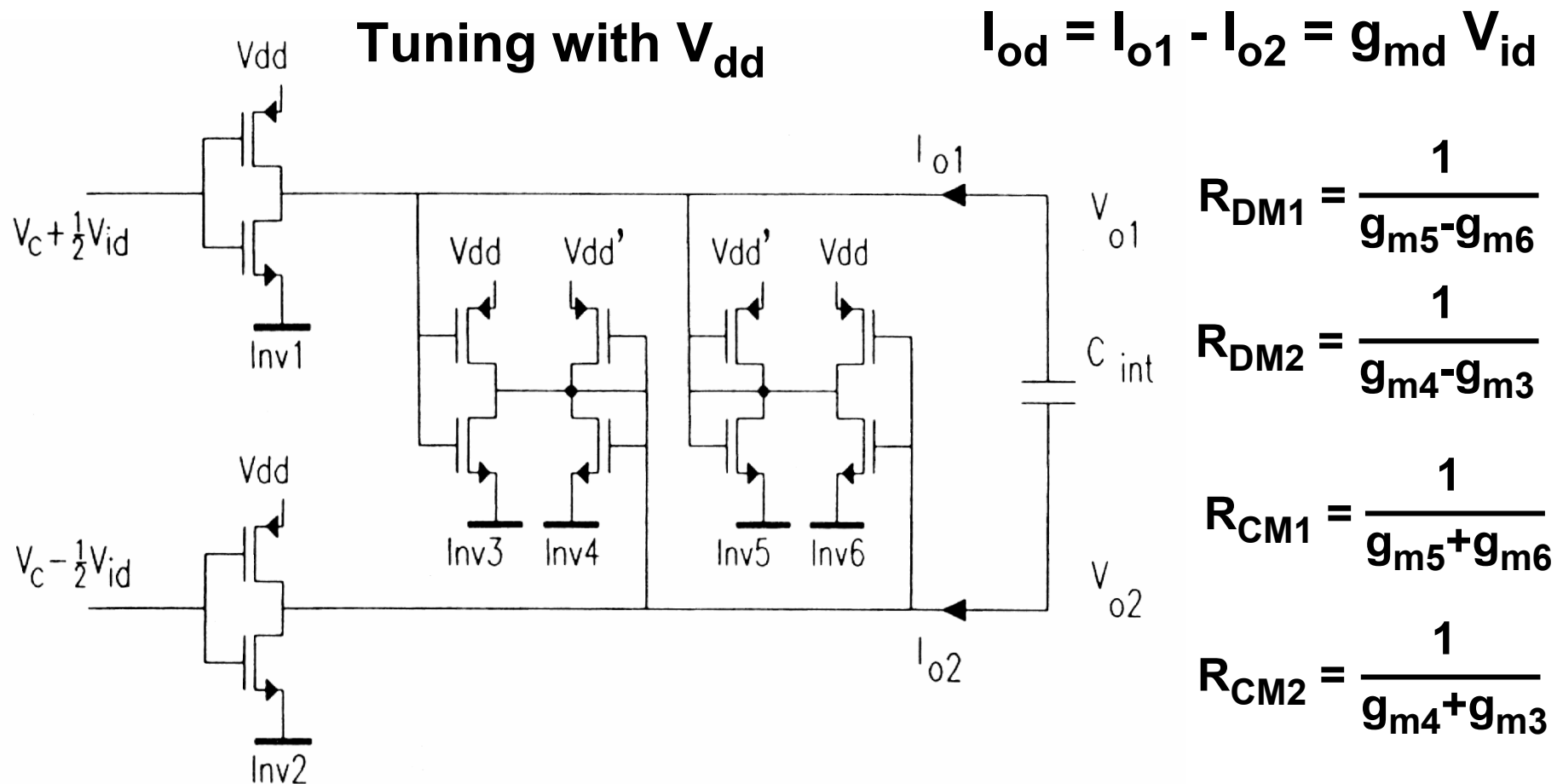Transconductor for High Frequencies (2 nodes)



Ref. Nauta JSSC Febr.92,142-146

Transconductors with linear MOSTs

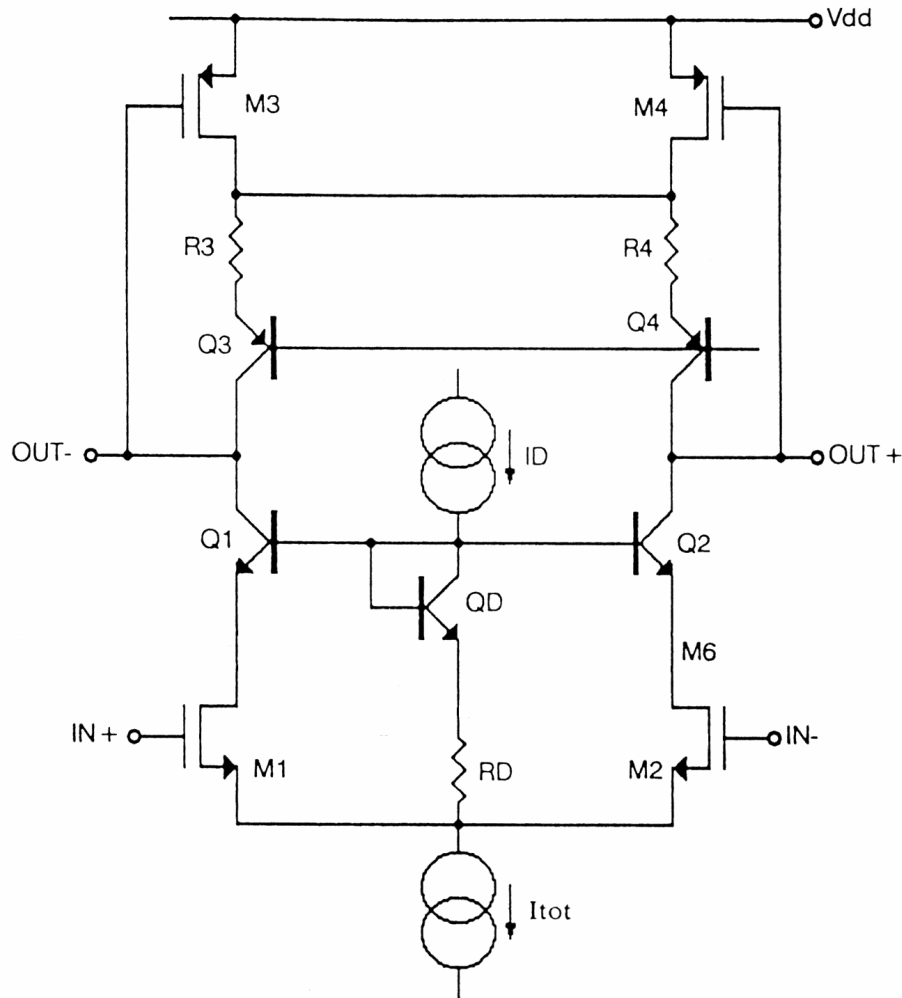

$$V_{DS1} = R_D I_D \approx 0.2 \text{ V}$$


$$I_{DS1} = \beta_1 V_{DS1} (V_{GS1} - V_T)$$

$g_{m1} = \beta_1 V_{DS1}$ is constant

over wide range !

Alini, JSSC, Dec.92, pp.1905-1915

□ Alternative solutions

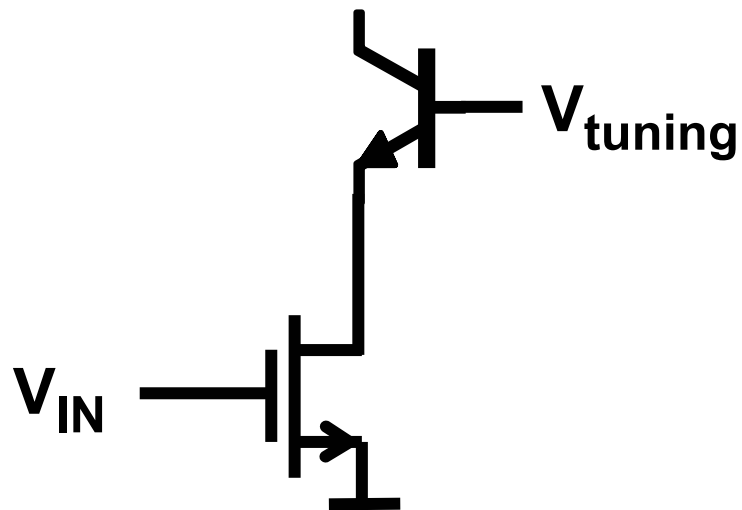


Larger tuning range

Controls V_{DS}

$V_{DSmin} \approx 0$

V_{tuning} down to 0

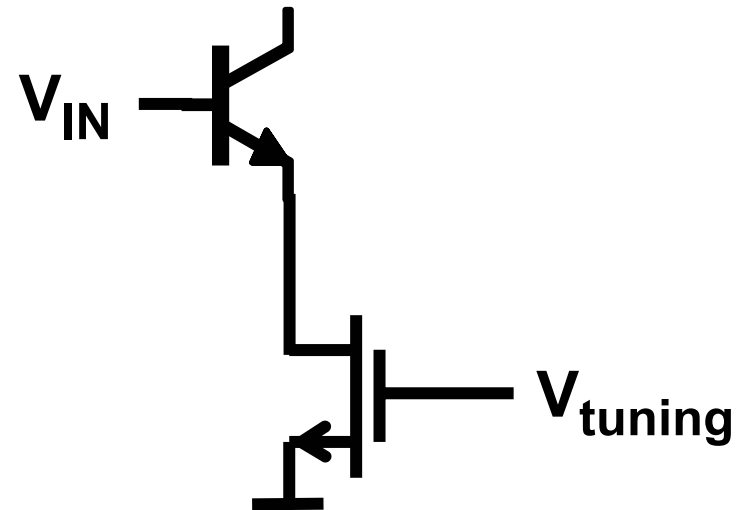


Smaller tuning range

Controls $V_{GS} - V_T$

V_{GSTmin} limited by linearity

V_{tuning} from V_T up

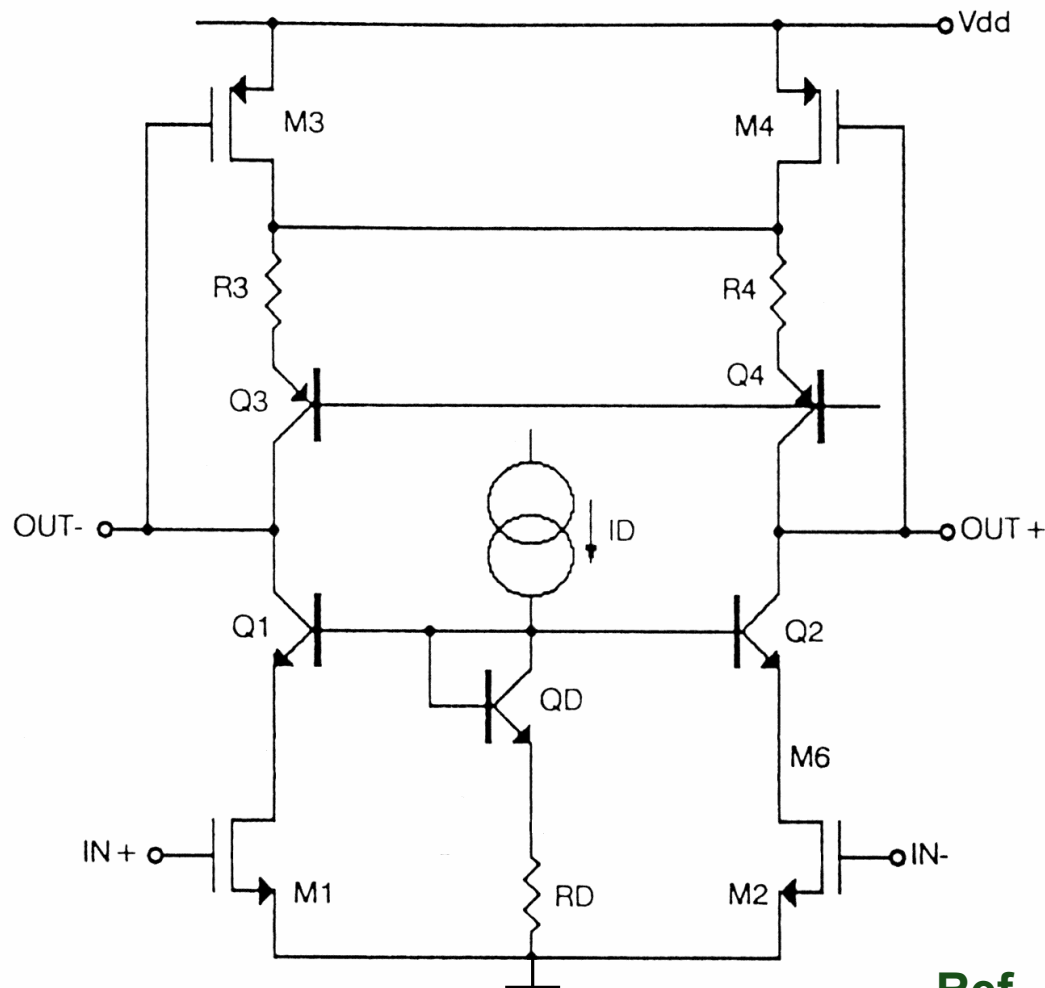Pseudodifferential transc. with linear MOSTs




Biasing imposed by previous circuit !

No rejection of CM signals (CMRR = 0 dB)

Ref. Alini, JSSC, Dec.92, pp.1905-1915

Transconductors with linear MOSTs

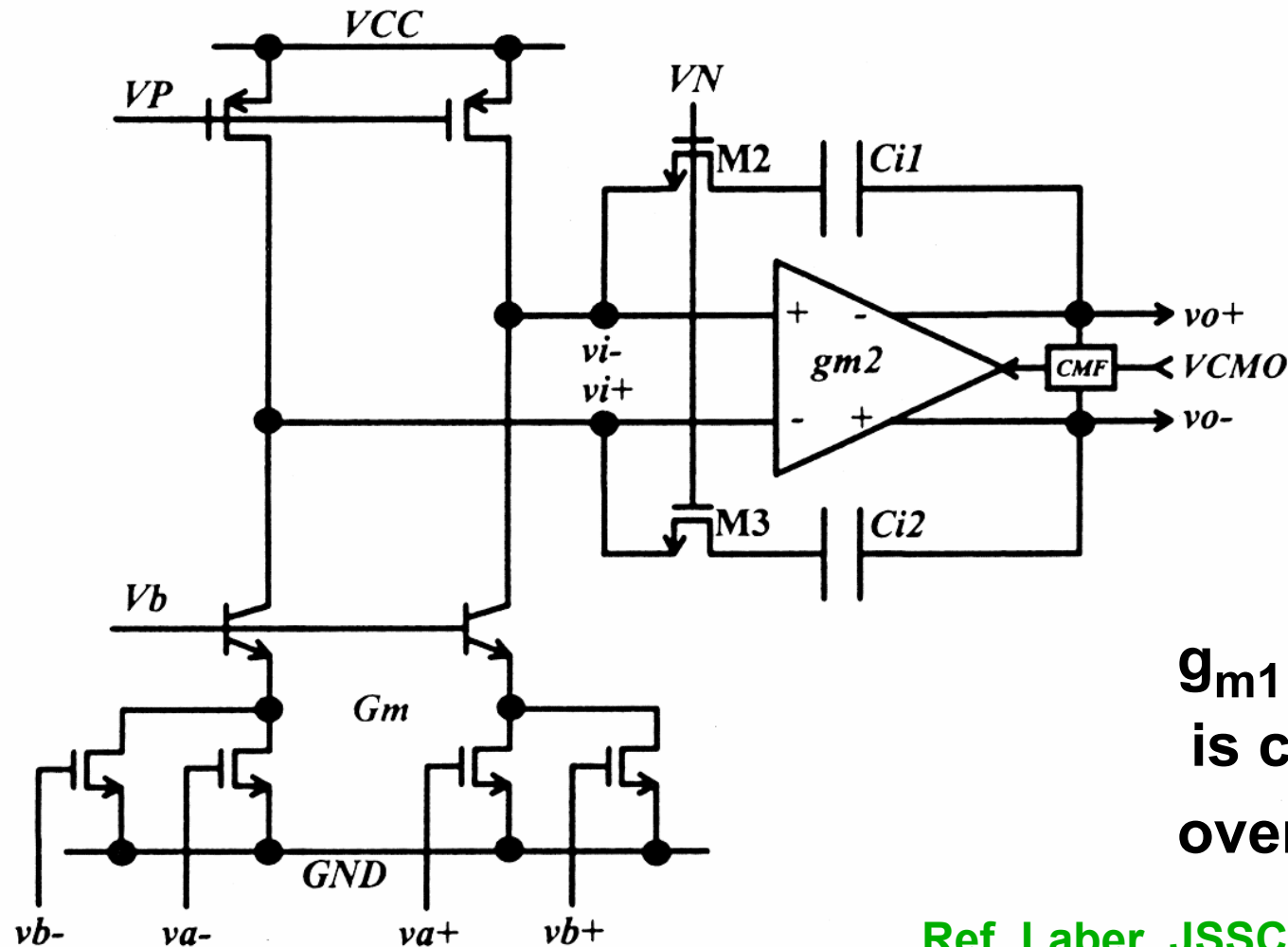

$g_{m1} = \beta_1 V_{DS1}$
is constant
over wide range !


Ref. Laber, JSSC, April 93, 462-470

Table of contents


- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
 - Transconductors
 - Tuning
- ◆ Comparison

Ref.: Silva-Martinez, Dehaene, ..

Gm-R-C versus Gm-C filters

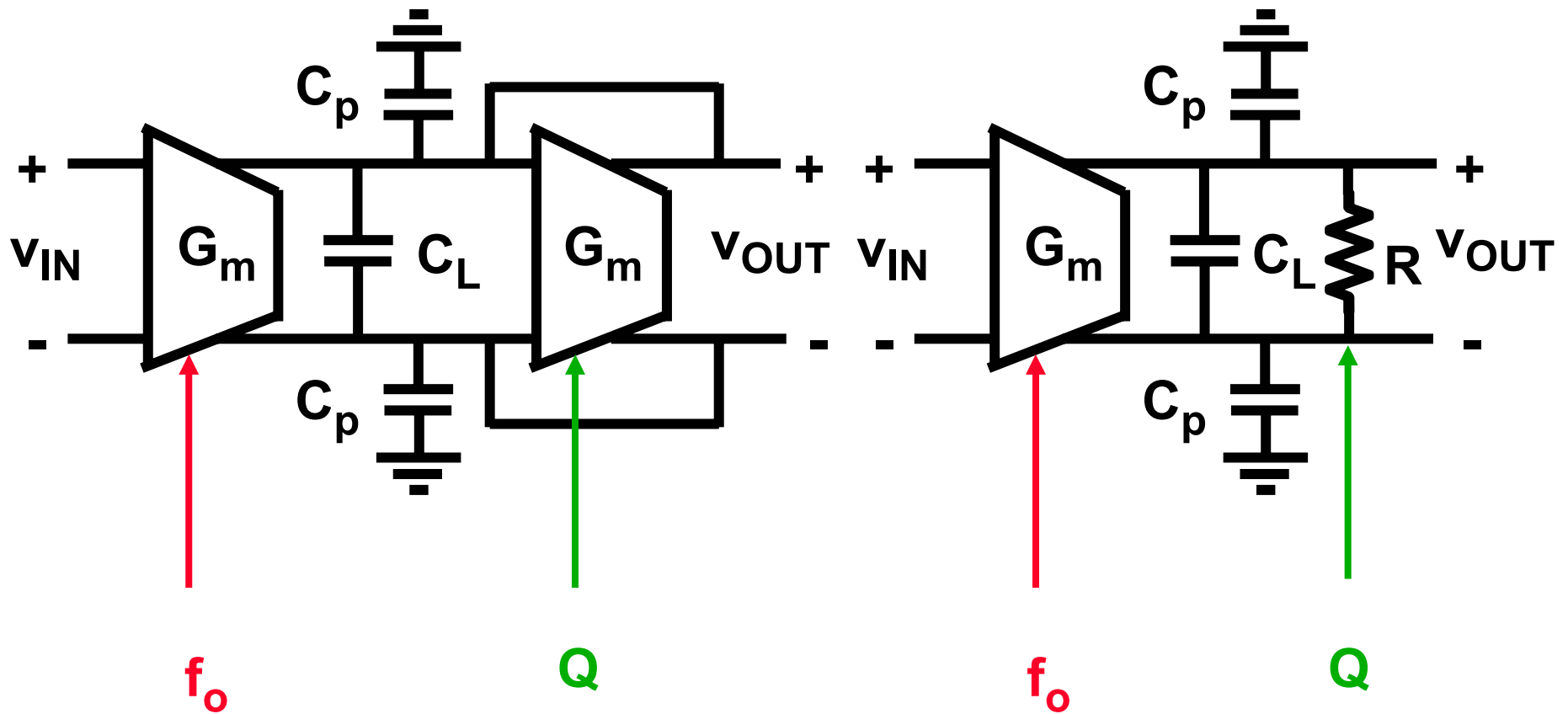

Gm-R-C filters

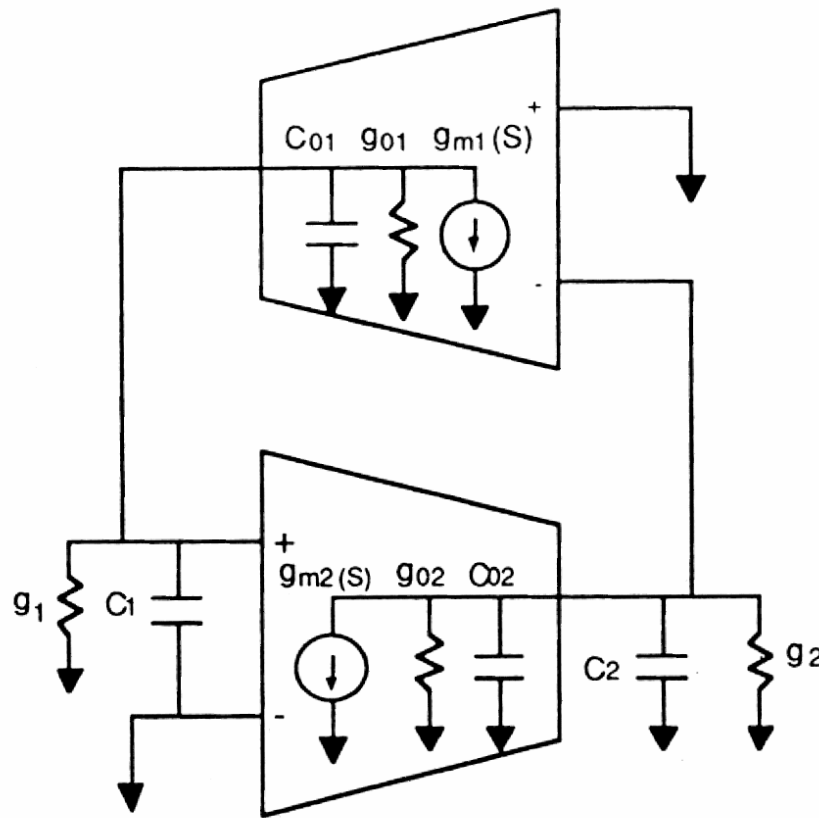

$$f_o \approx \frac{1}{2\pi} \sqrt{\frac{g_{m1}g_{m2}}{C_1C_2}}$$


if $f_o \ll f_{par}$

$$Q \approx \frac{g_{m2}}{g_2 + g_{o2}}$$

if $g_1 \approx 0$ (casccodes)


Ref. Silva-Martinez JSSC July 91,946-955

Tunable R to tune Q

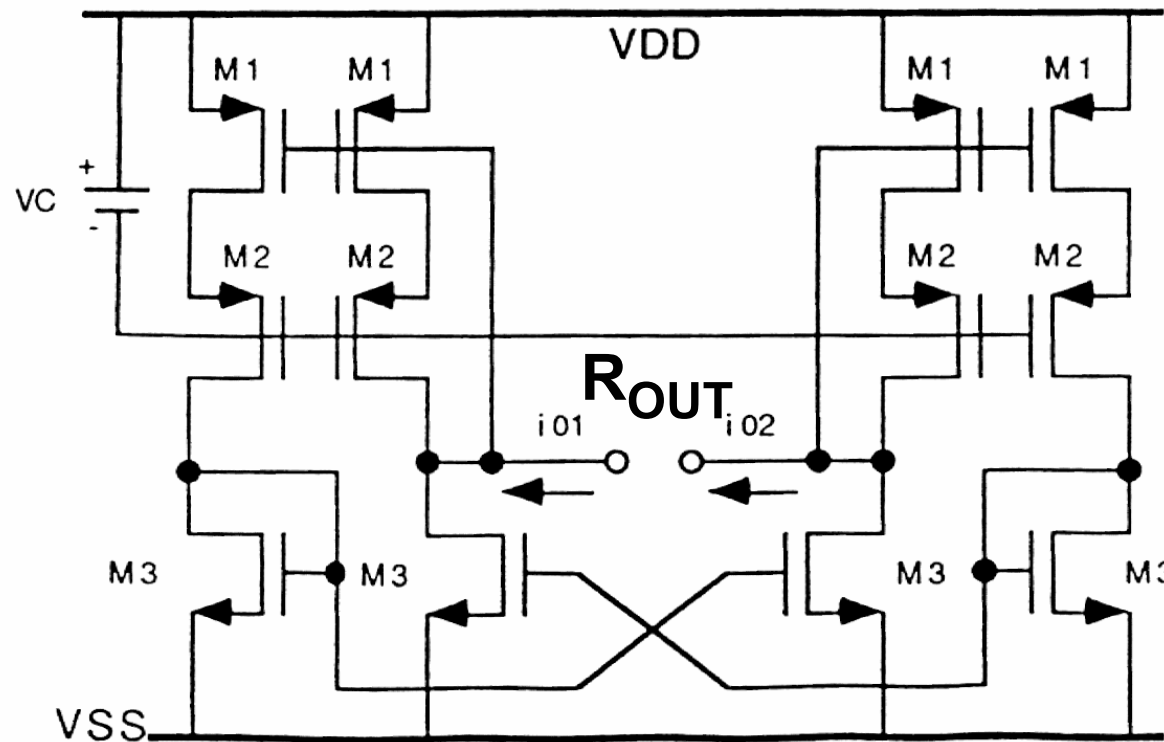


$$R_{OUT} \approx \frac{1}{KP_1 \frac{W_1}{L_1} (V_C - V_{GS2})}$$

Tuning systems : transconductance tuning

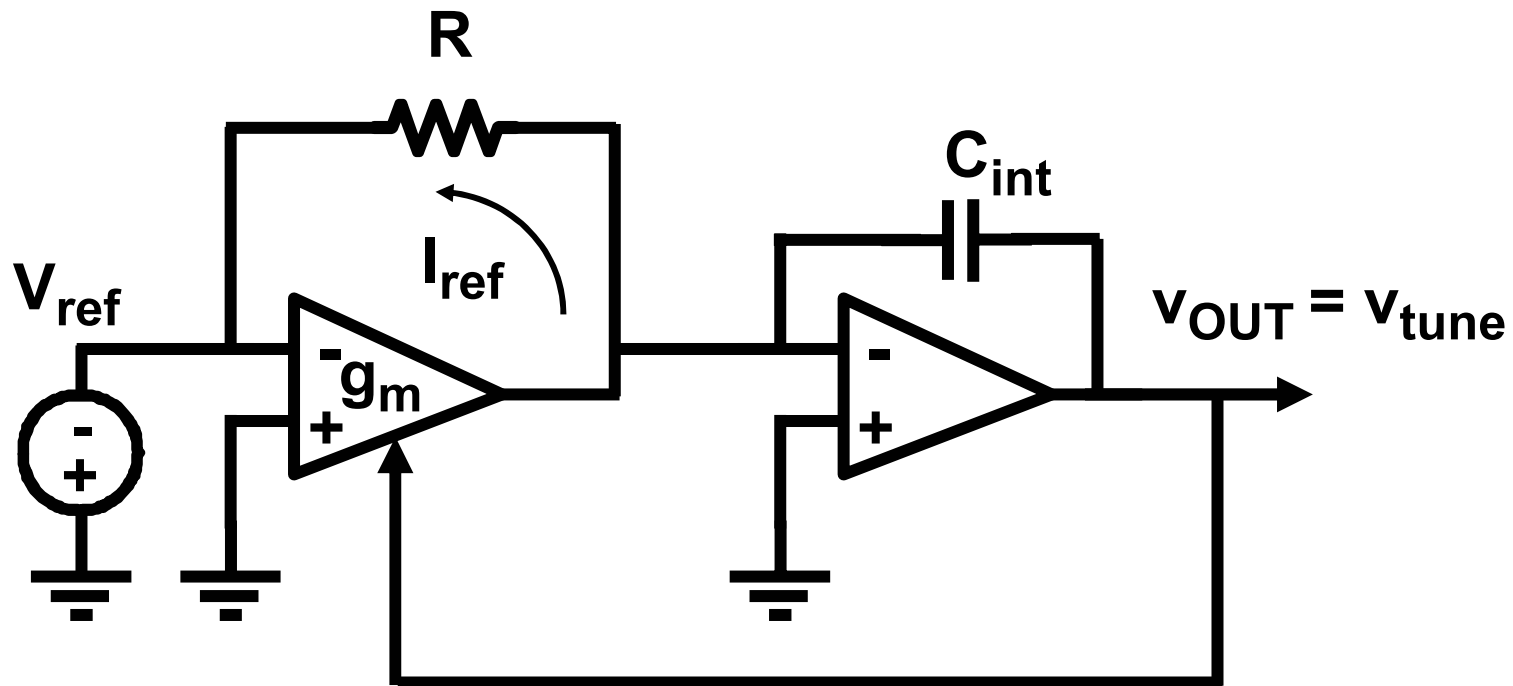

$$\left. \begin{aligned} I_{ref} &= V_{ref} / R \\ I_{ref} &= g_m V_{ref} \end{aligned} \right\} g_m = 1 / R$$


Tuning systems : frequency tuning

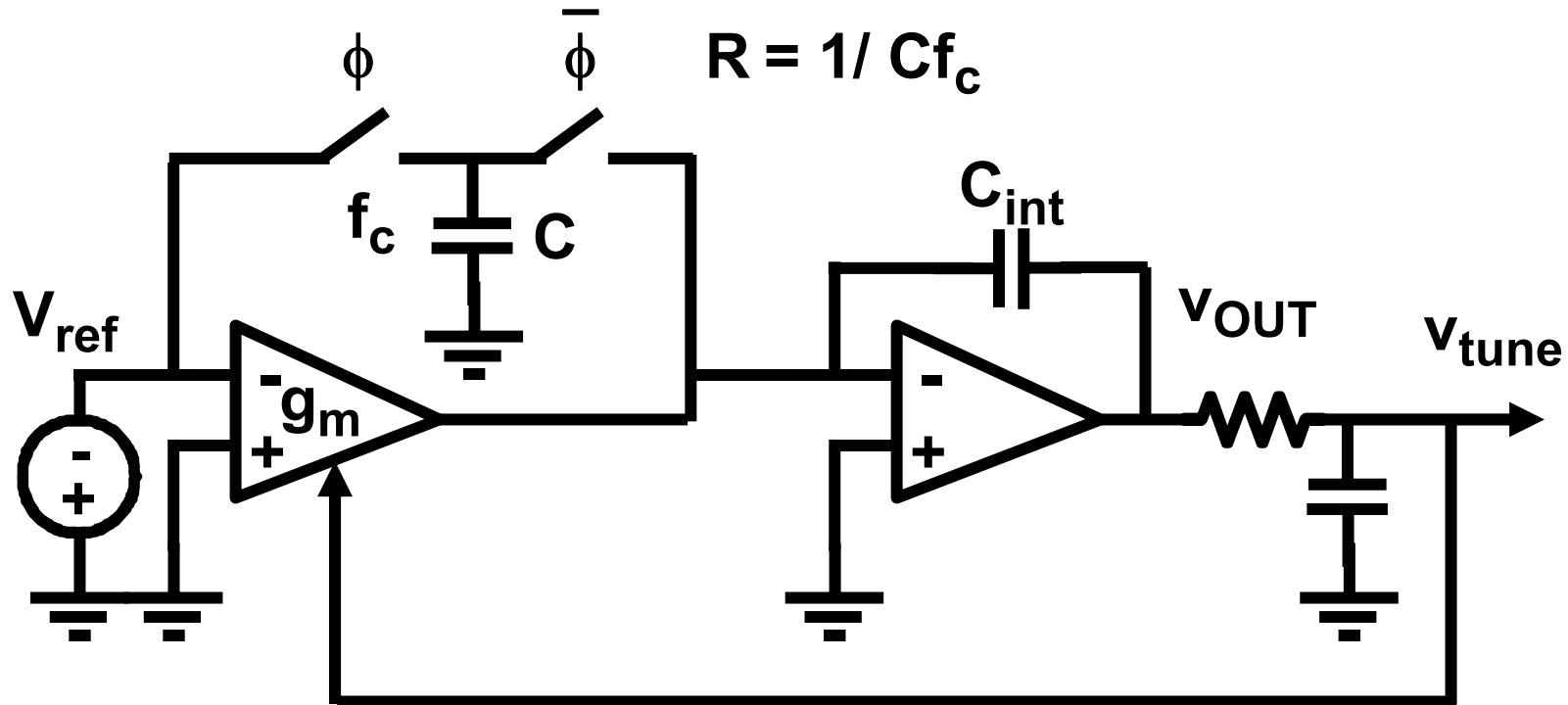

$$\left. \begin{aligned} I_{\text{ref}} &= C f_c V_{\text{ref}} \\ I_{\text{ref}} &= g_m V_{\text{ref}} \end{aligned} \right\} g_m = C f_c$$



Ref. Viswanathan, JSSC Aug.82, 775-778
Silva, JSSC Dec. 92, 1843-1853

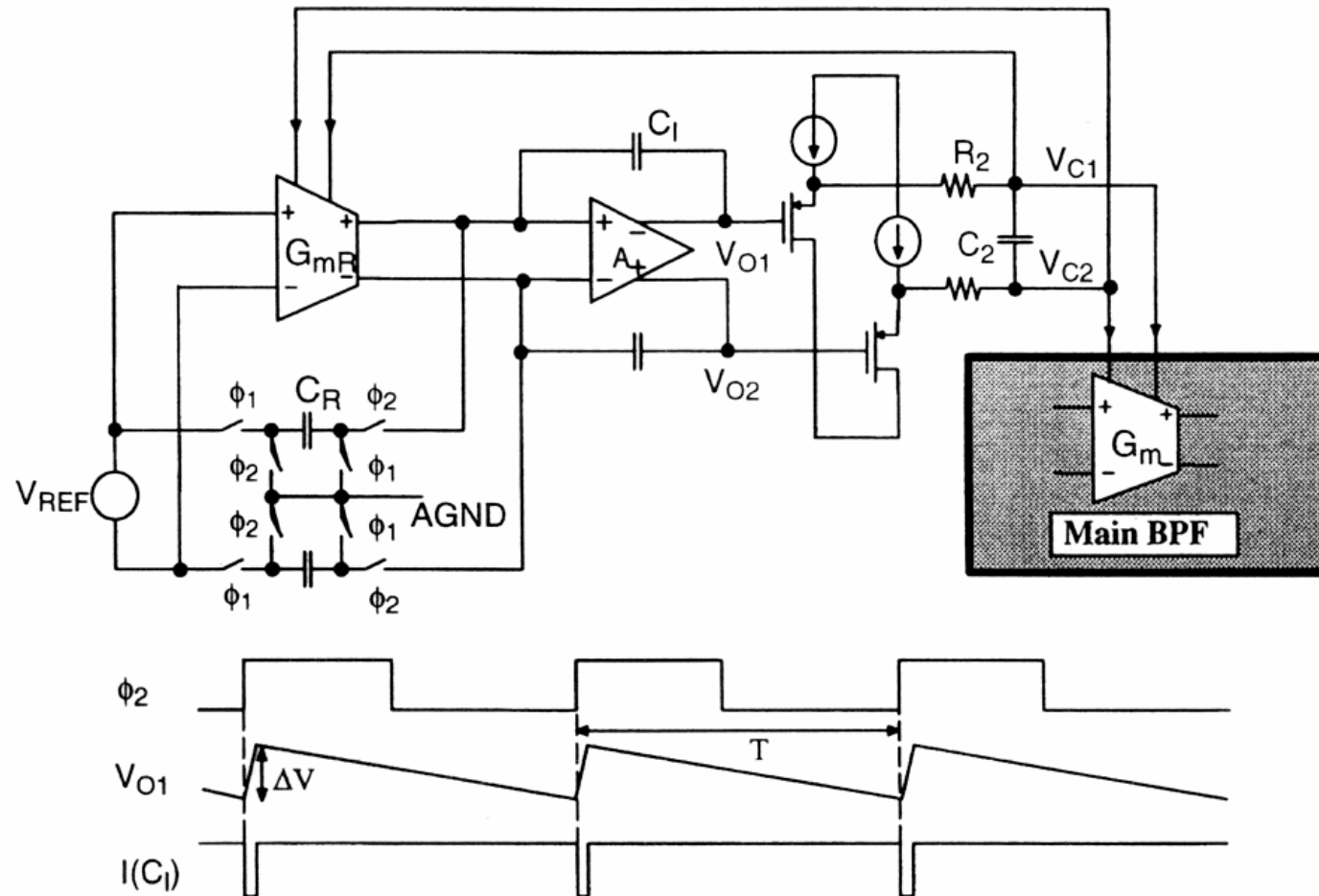Fully-differential tuning system realization



Ref. Chang, JSSC March 1997, 388-397

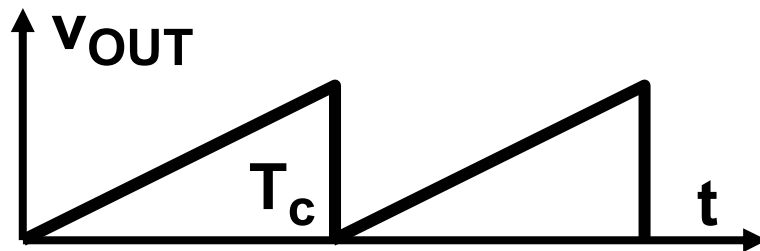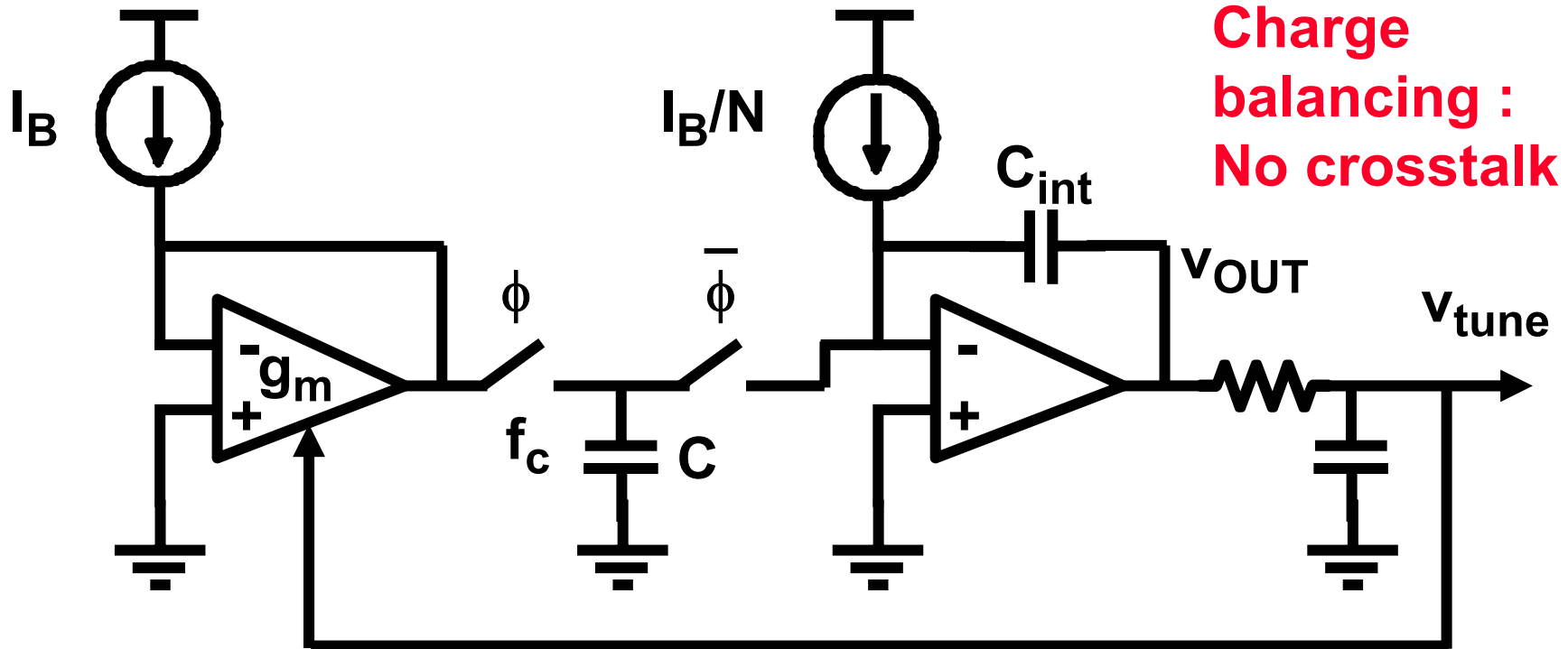Tuning systems : frequency tuning with low f_c




$$Q_{gm} = C I_B / g_m$$

$$Q_{IBN} = I_B / N T_c$$

$$\left. \begin{array}{l} Q_{gm} = C I_B / g_m \\ Q_{IBN} = I_B / N T_c \end{array} \right\} \frac{g_m}{C} = N f_c$$

Ref. Silva

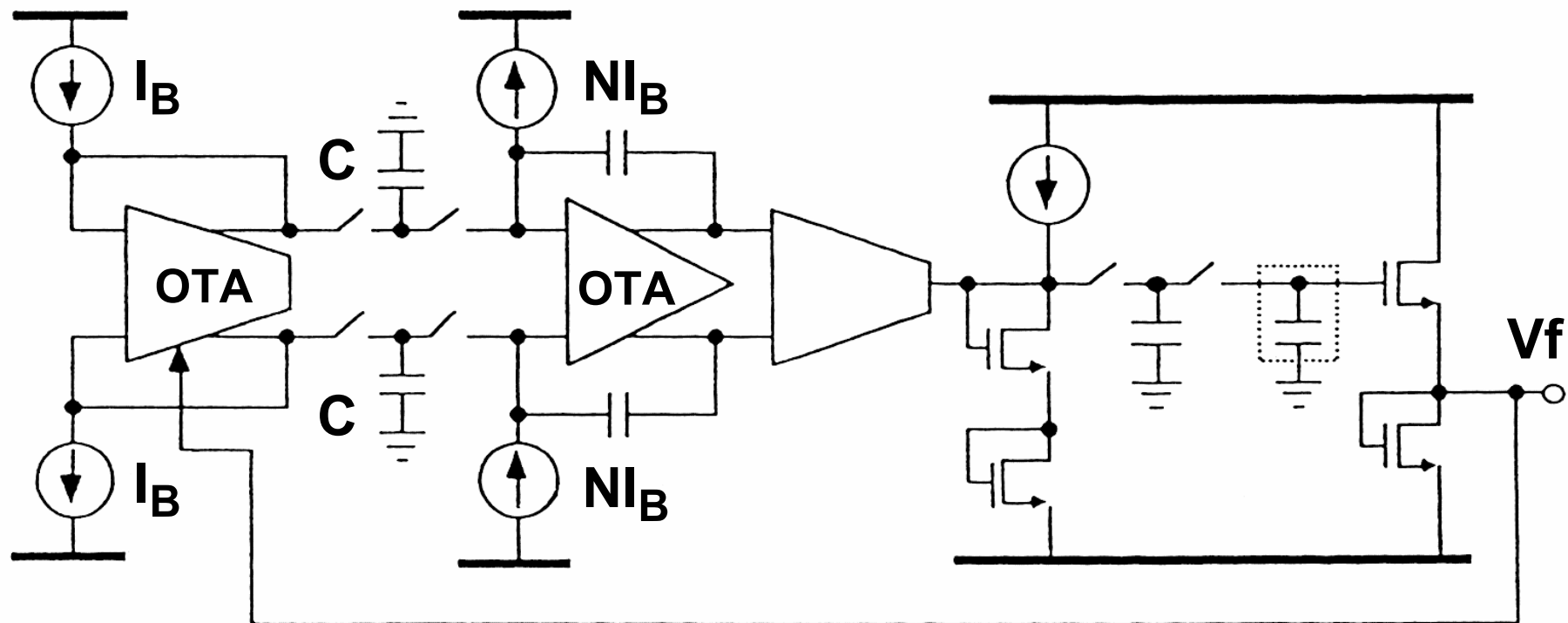Fully-differential frequency tuning system




$$\frac{g_m}{C} = Nf_c$$

Ref. Silva, JSSC Dec. 92, 1843-1853

Tuning systems : Q tuning


Unity-pulse response Biquad :
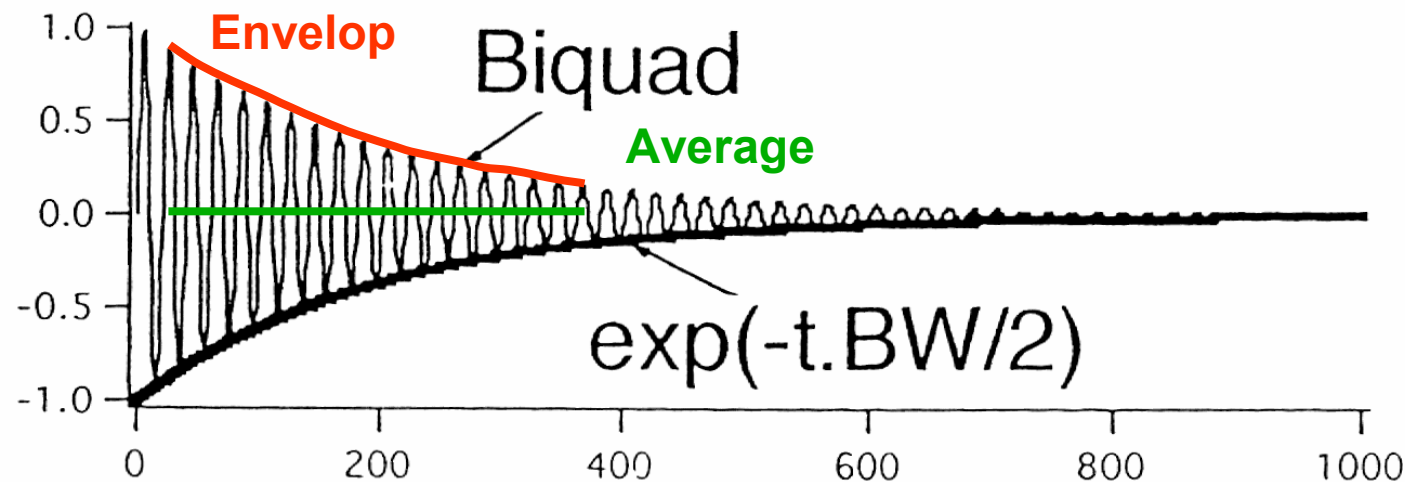
$$H(t) = \frac{1}{\sqrt{1 - \frac{1}{4Q^2}}} \exp\left(-\frac{t.BW}{2}\right) \sin\left(\sqrt{1 - \frac{1}{4Q^2}} \omega_o t + \theta\right)$$



**No HF PLL
or VCO !
Detection
at f_c !**


Q tuning with active resistor

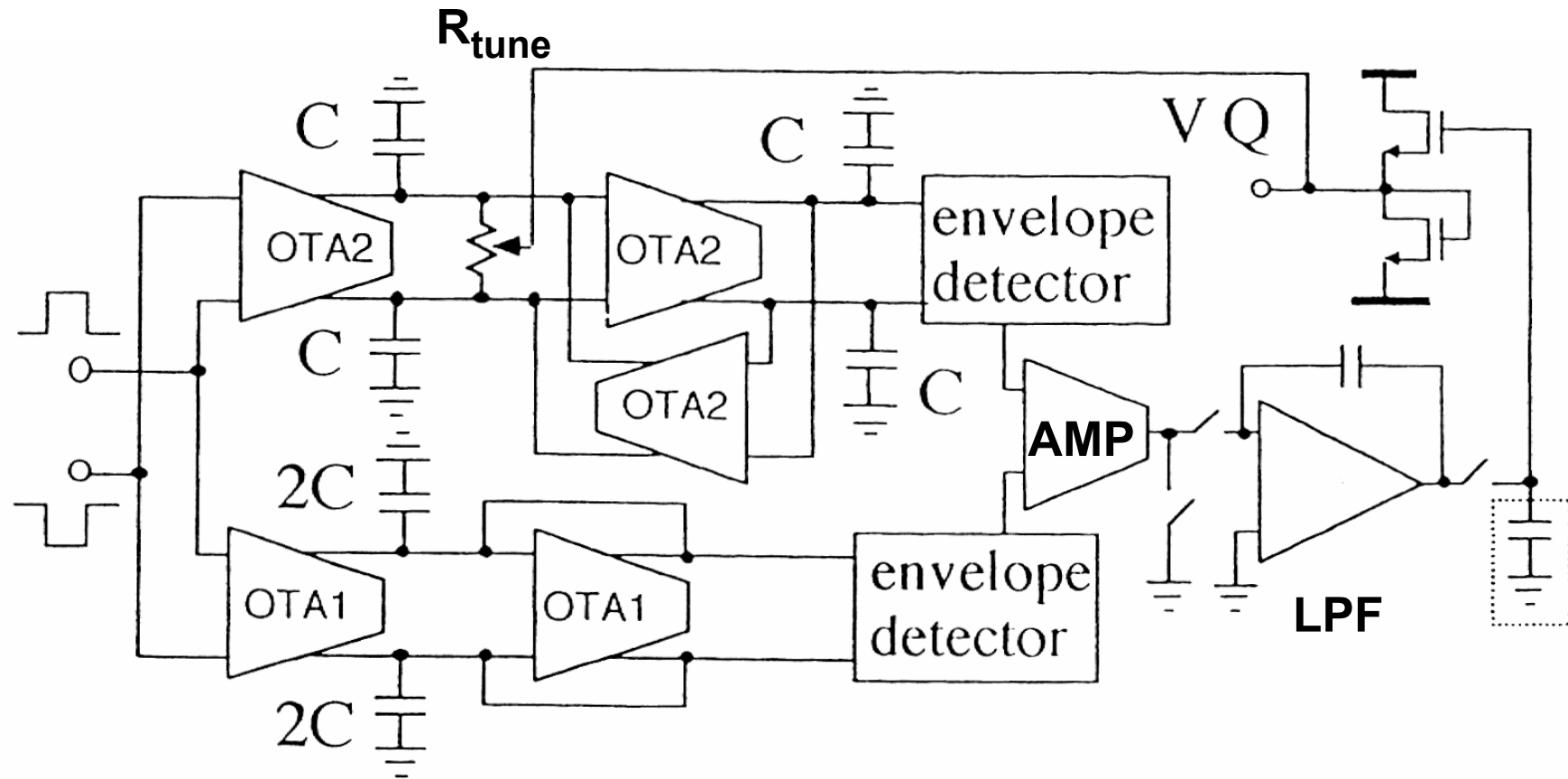

Comparison of 10.7 MHz filters

	SC	OTA-C	Gm-RC
f_c (BW = 250 kHz)	10.7 MHz	12.5 MHz	10.7 MHz
Order filter	6	4	4
Vin @ IM3= 1%	0.24 V _{RMS}	0.32 V _{RMS}	0.71 V _{RMS}
DR @ IM3= 1%	34 dB	51 dB	68 dB
Power (\pm V)	500 mW(\pm 5)	360 mW(\pm 6)	220 mW(\pm 2.5)
Chip area	2 mm ²	7.8 mm ²	6 mm ²

Biquad for 7th-order Filter at 50 MHz

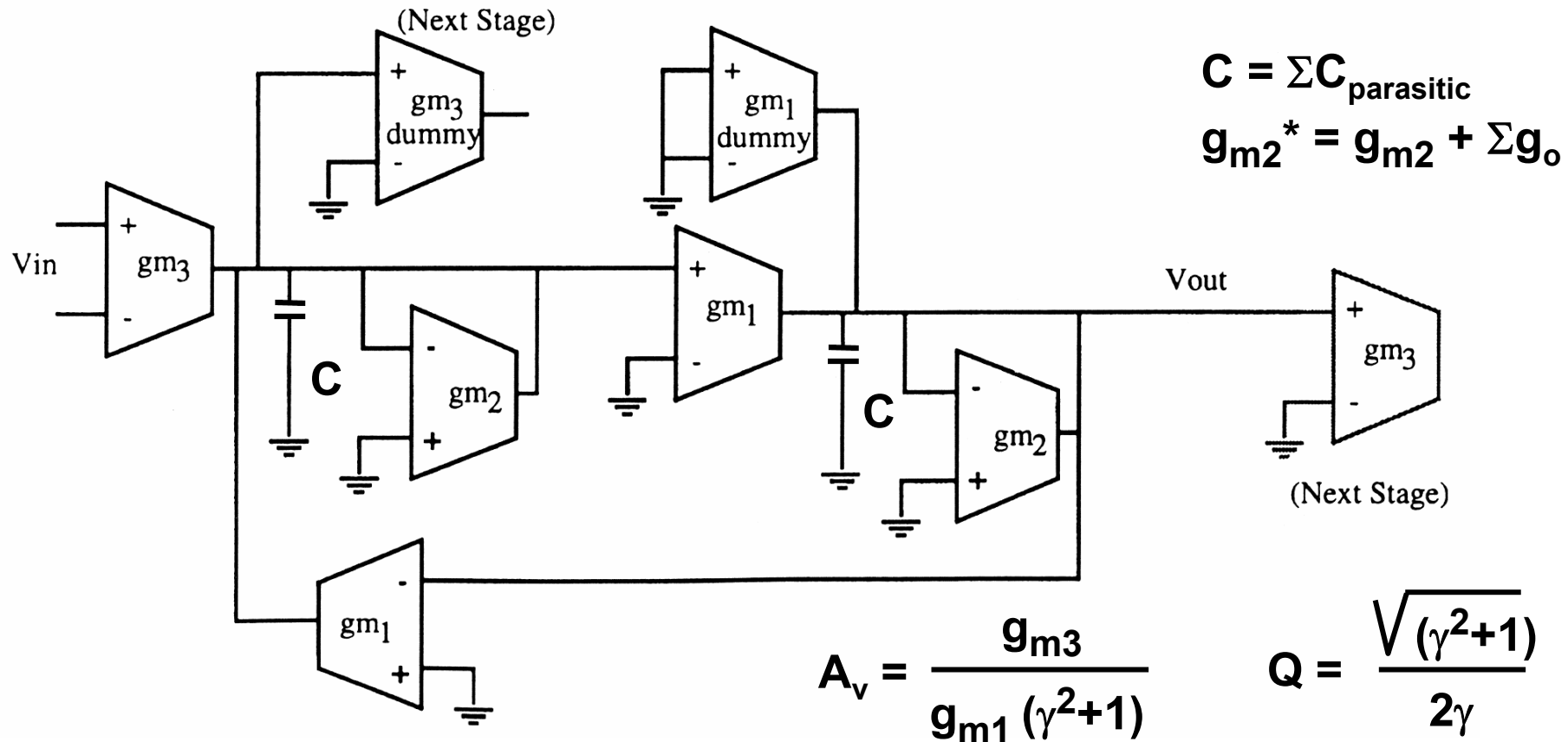

Biquad with matched nodes


Ref. Dehaene JSSC July 97, 977-988

$$A_v = \frac{g_{m3}}{g_{m1}(\gamma^2 + 1)}$$

$$Q = \frac{\sqrt{\gamma^2 + 1}}{2\gamma}$$

$$f_o = \frac{1}{2\pi\tau} \frac{\sqrt{(\gamma^2+1)}}{\gamma} \quad \tau = \frac{C}{g_{m2}^*} \quad \gamma = \frac{g_{m2}^*}{g_{m1}}$$

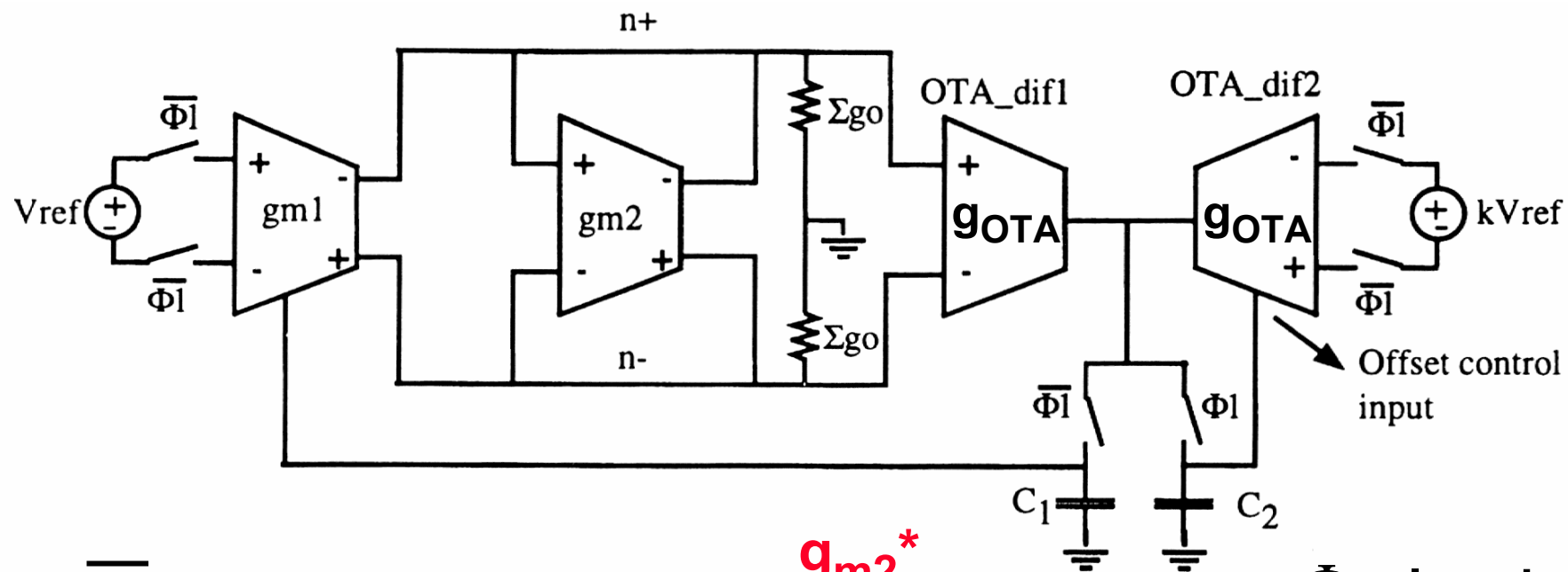Tuning system for Q : conductance ratio γ




$\overline{\Phi_1}$ closed : γ tuning mode $\gamma = \frac{g_{m2}^*}{g_{m1}}$

$$V_{n+,n-} = \frac{g_{m1}}{g_{m2}^*} g_{OTA} V_{ref} = k V_{ref} g_{OTA} \Rightarrow \gamma = \frac{1}{k}$$

**Φ_1 closed :
offset calibration
mode for all OTA's
(Vref set to 0)**

Ref. Dehaene JSSC July 97, 977-988

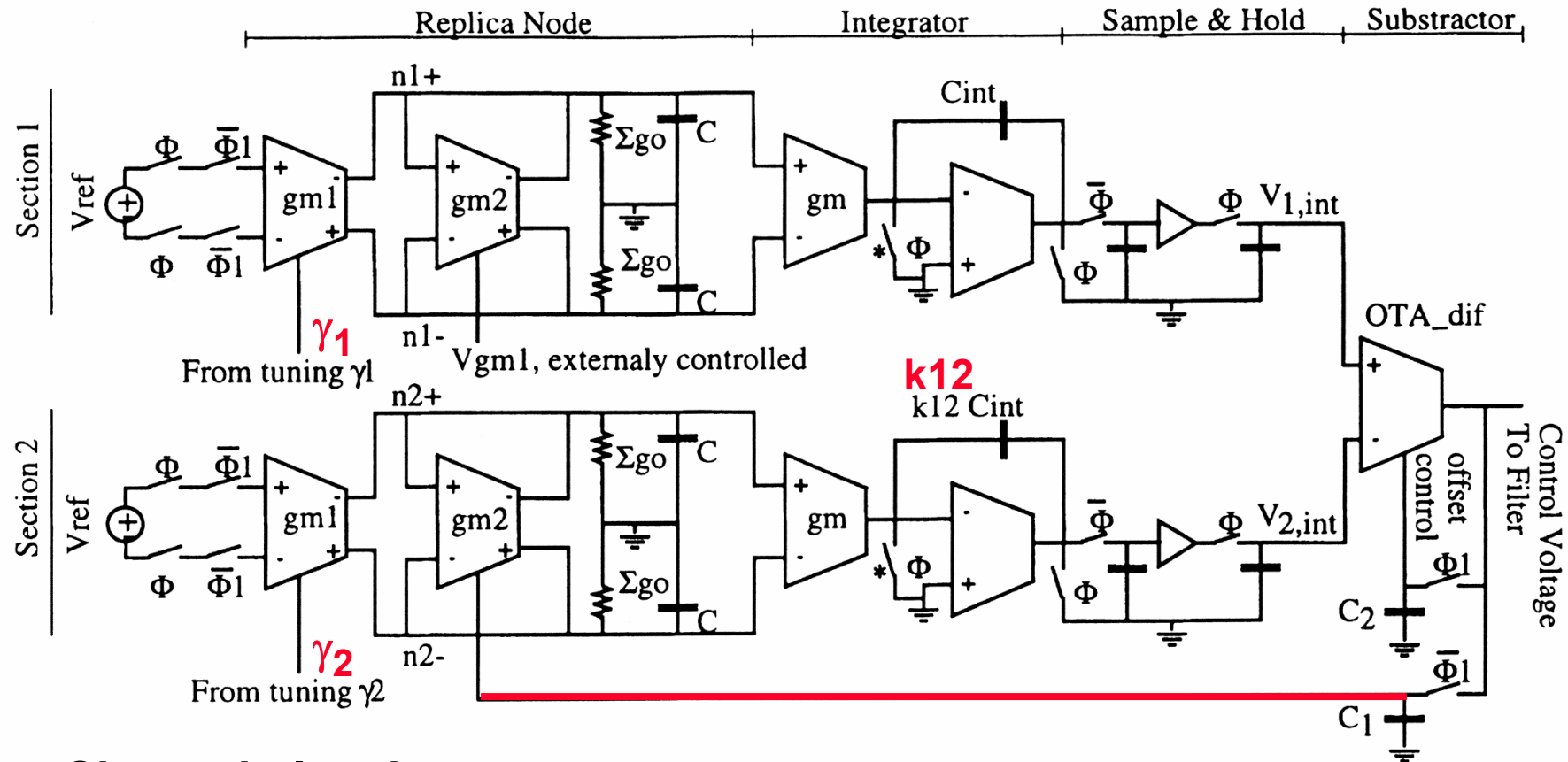Tuning system for the ratio of time constants



Charge balancing :

$$V_{1,int} = V_{2,int} \text{ or}$$

$$\frac{V_{ref}}{\gamma_1} \frac{g_m}{C_{int}} \tau_1 = \frac{V_{ref}}{\gamma_2} \frac{g_m}{k_{12} C_{int}} \tau_2 \Rightarrow \frac{\tau_2}{\tau_1} = k_{12} \frac{\gamma_2}{\gamma_1}$$

Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
- ◆ Comparison

Ref.: Tsividis, Voorman, Integrated Cont.-time filters, IEEE Press 1993
J. Silva-Martinez, Kluwer 1993,
W. Dehaene, JSSC, July 1997, 977-988

Signal to Noise + Distortion ratio

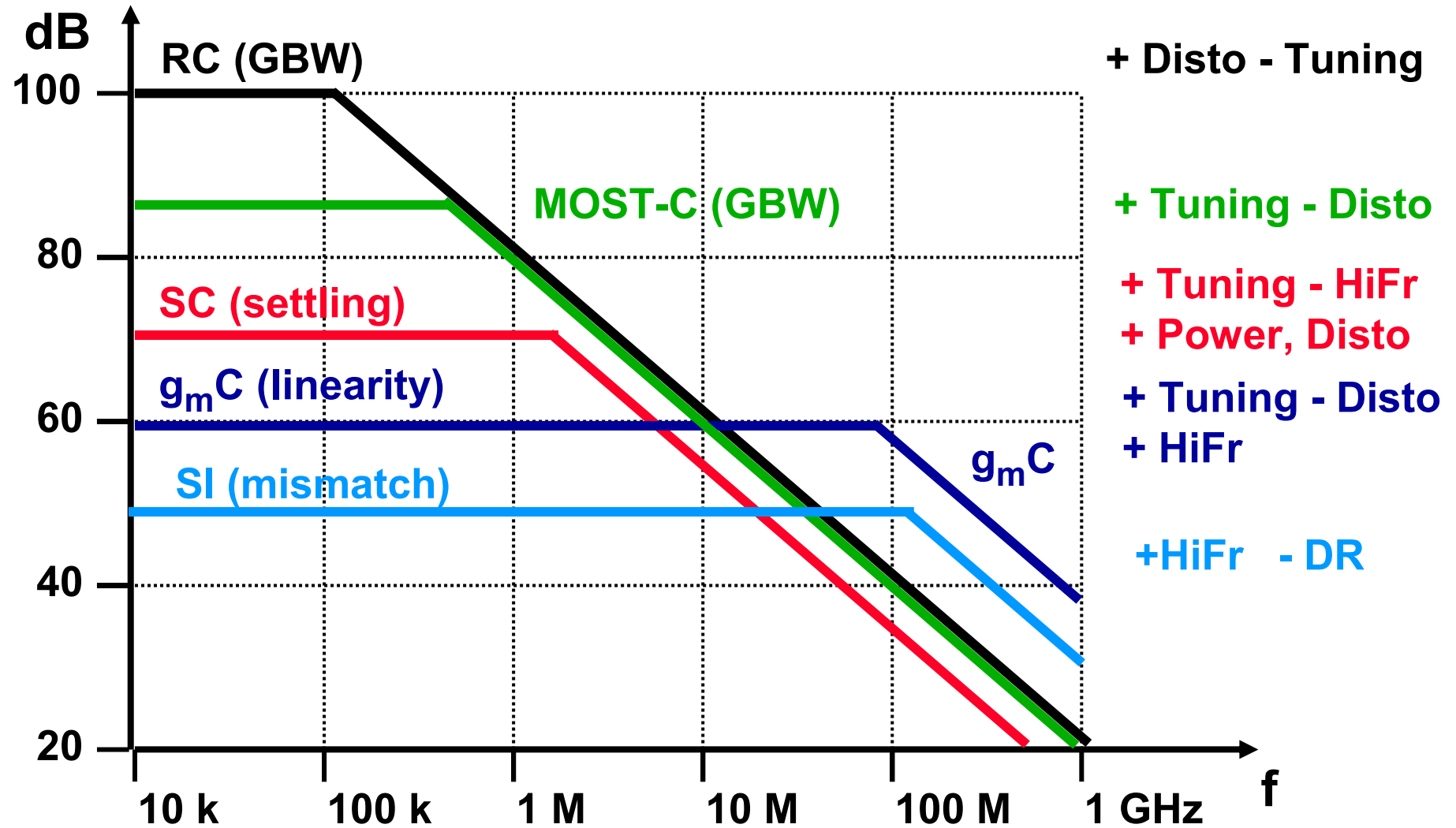


Table of contents

- ◆ Active RC filters
- ◆ MOSFET-C filters
- ◆ GmC filters
- ◆ Comparison

Ref.: Tsividis, Voorman, Integrated Cont.-time filters, IEEE Press 1993
J. Silva-Martinez, Kluwer 1993,
W. Dehaene, JSSC, July 1997, 977-988