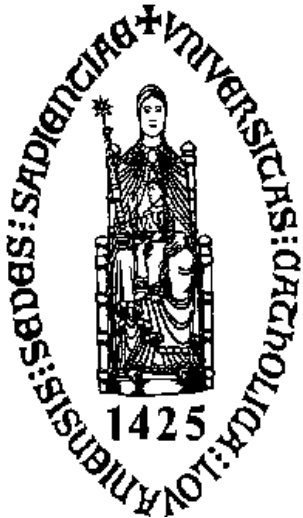


---

---

# Stability of Operational amplifiers



**Willy Sansen**

**KULeuven, ESAT-MICAS**

**Leuven, Belgium**

[willy.sansen@esat.kuleuven.be](mailto:willy.sansen@esat.kuleuven.be)



---

# Table of contents


---

- **Use of operational amplifiers**
- **Stability of 2-stage opamp**
- **Pole splitting**
- **Compensation of positive zero**
- **Stability of 3-stage opamp**

---

# Operational amplifiers do operations

---


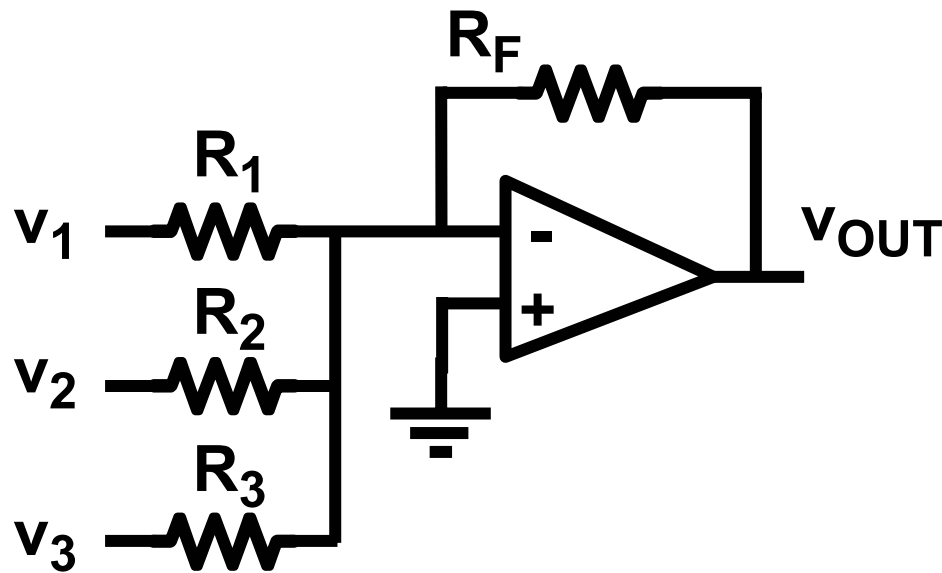


$$-\frac{V_{OUT}}{R_F} = \frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3}$$


Requires High gain  
High speed  
Low noise  
Low power

**Opamp specs :** Voltage gain is large  
Differential input voltage  $\approx 0$   
Input current = 0  
Bandwidth is high  
Gainbandwidth GBW is very, very high


# Single-ended or fully differential ?

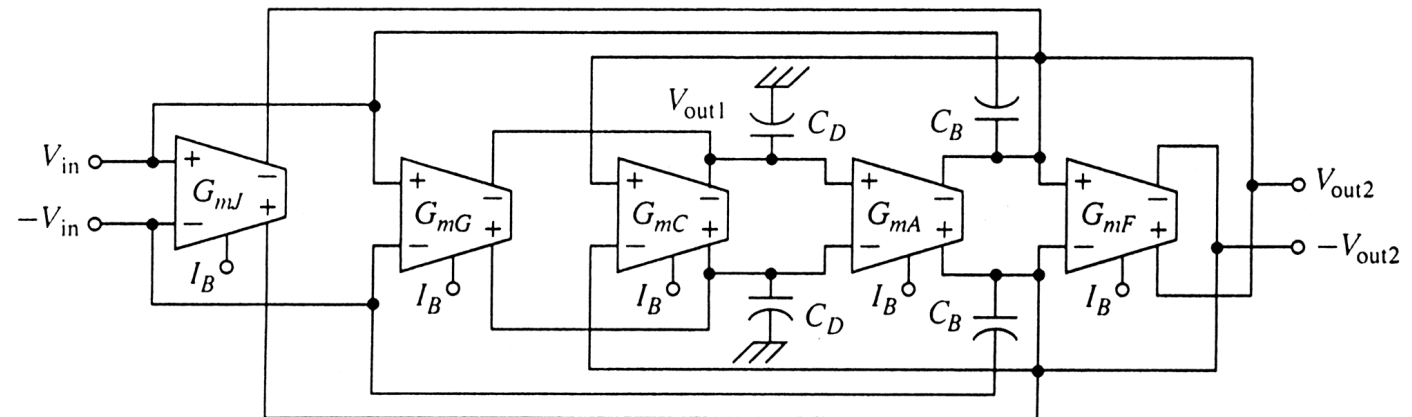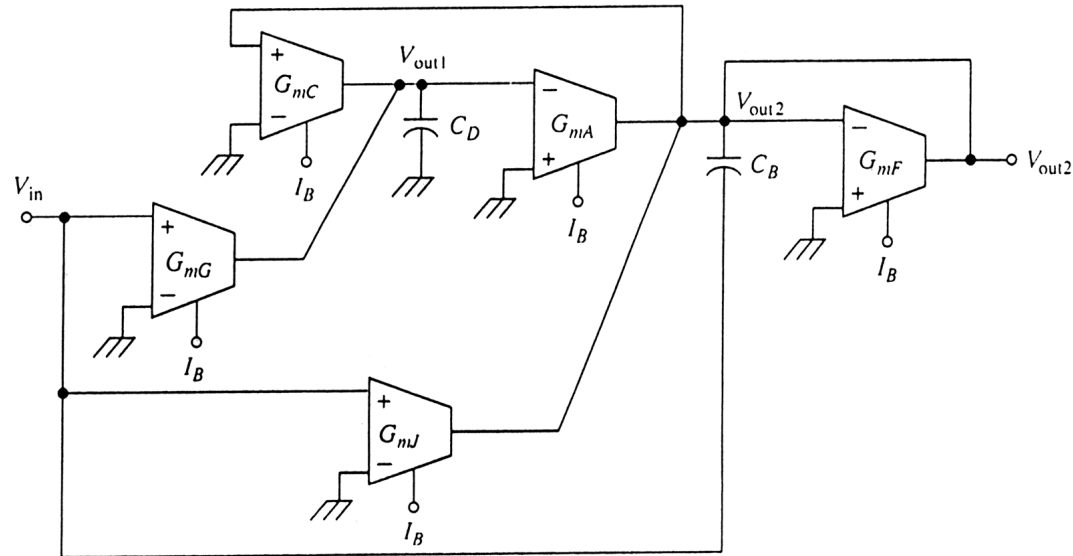

# Voltage input or current input ?

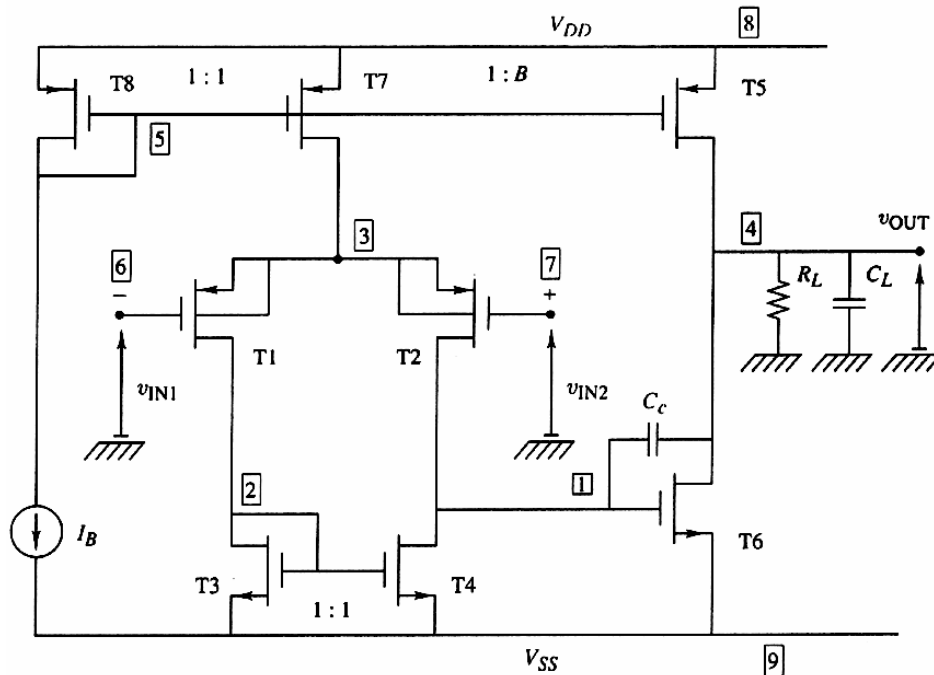

**Voltage input**  
**Current output**

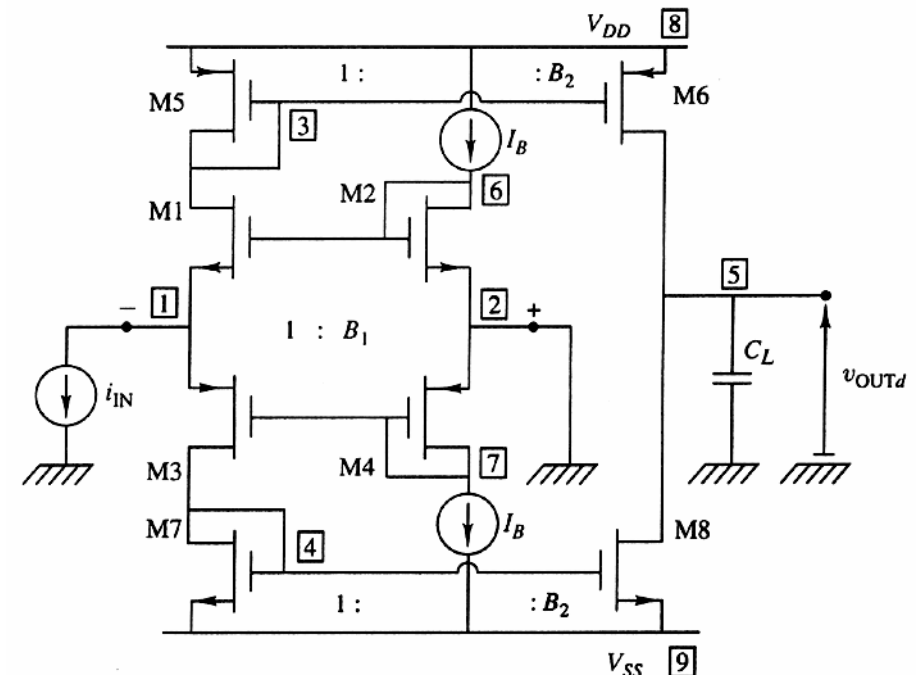


**Current input**  
**Current output**

# Classification

## Opamp

Operational  
amplifier

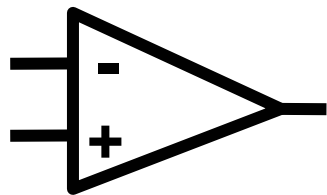


$$A_v = \frac{V_{OUT}}{V_{IN}}$$

$$A_v =$$

GBW

## OTA

Operational  
Transconduct.  
amplifier

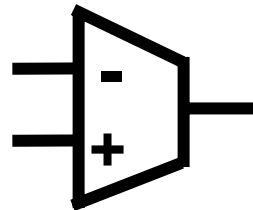


$$A_g = \frac{i_{OUT}}{V_{IN}}$$

$$= A_g R_L$$

## OCA

Operational  
Current  
amplifier

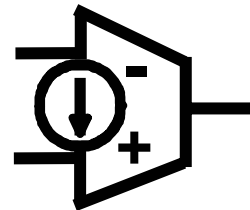


$$A_i = \frac{i_{OUT}}{i_{IN}}$$

$$= A_i \frac{R_L}{R_S}$$

## CM amp

Current  
Mode  
amplifier

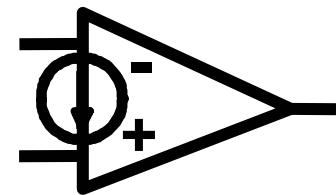


$$A_r = \frac{V_{OUT}}{i_{IN}}$$

$$= A_r \frac{1}{R_S}$$

---


# Feedback configurations

---

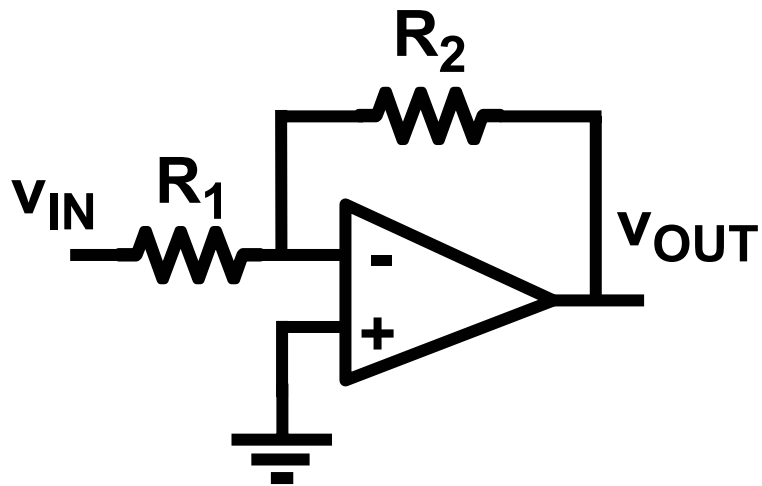


$$A_v = -\frac{R_2}{R_1}$$

$$R_{IN} = R_1$$

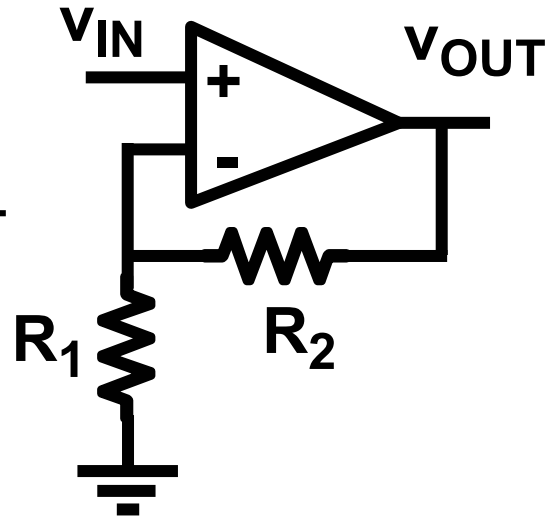

$$A_v = 1 + \frac{R_2}{R_1}$$

$$R_{IN} = \infty$$

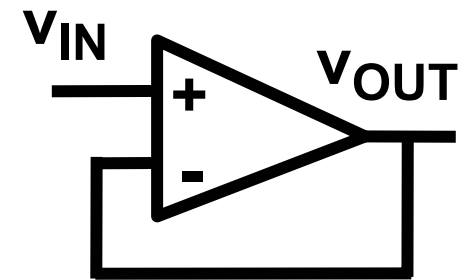



$$A_v = 1$$

$$R_{IN} = \infty$$

---

# Integrator

---

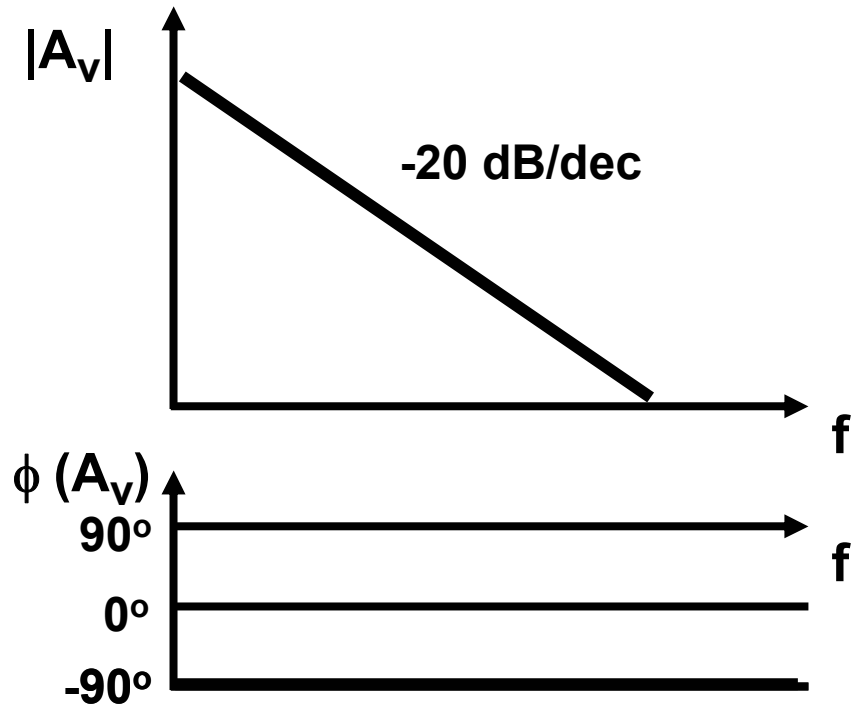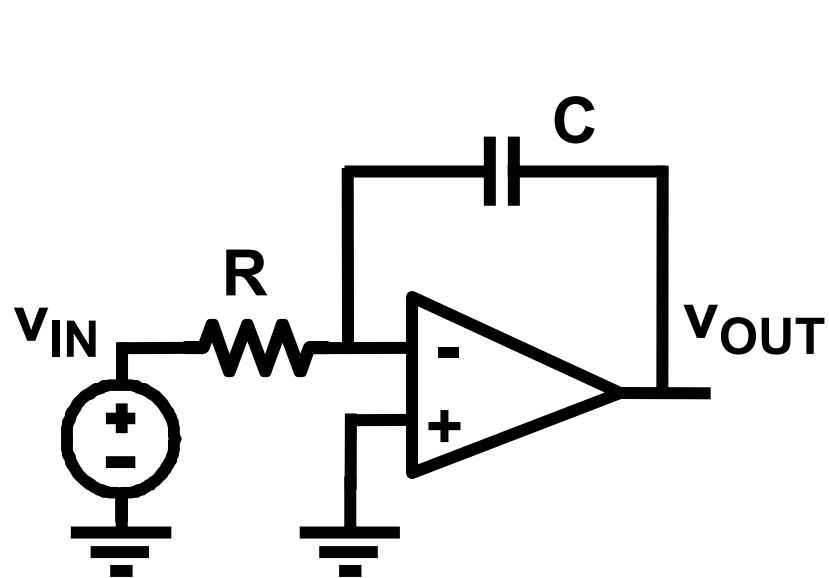

$$A_v = \frac{1}{j \frac{f}{f_p}}$$



$$f_p = \frac{1}{2\pi RC}$$



---



# Low-pass filter

---

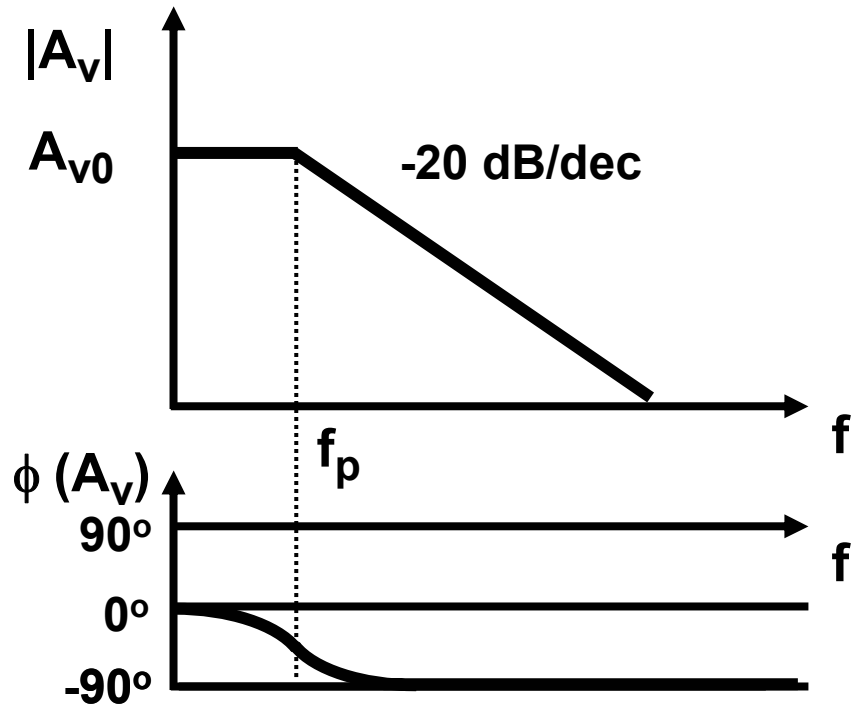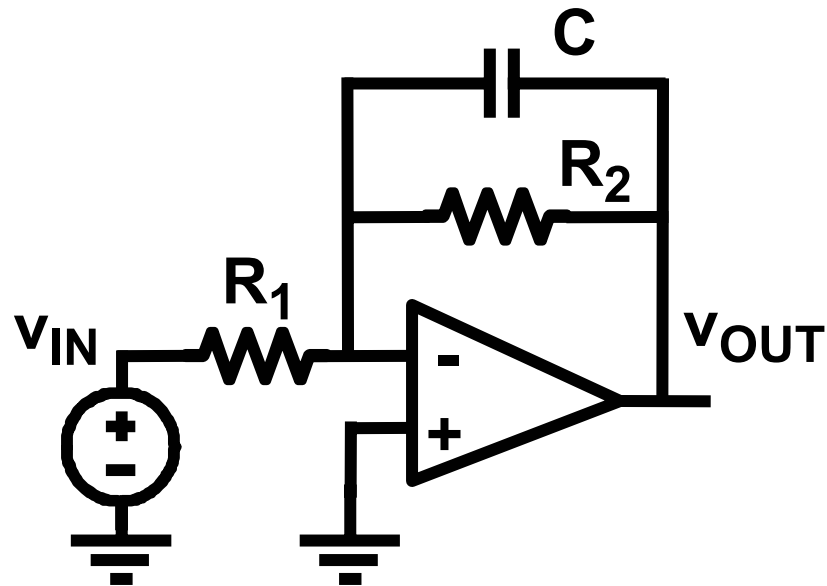

$$A_{v0} = -\frac{R_2}{R_1} \quad A_v = \frac{A_{v0}}{\left(1 + j \frac{f}{f_p}\right)} \quad f_p = \frac{1}{2\pi R_2 C}$$


# High-pass filter

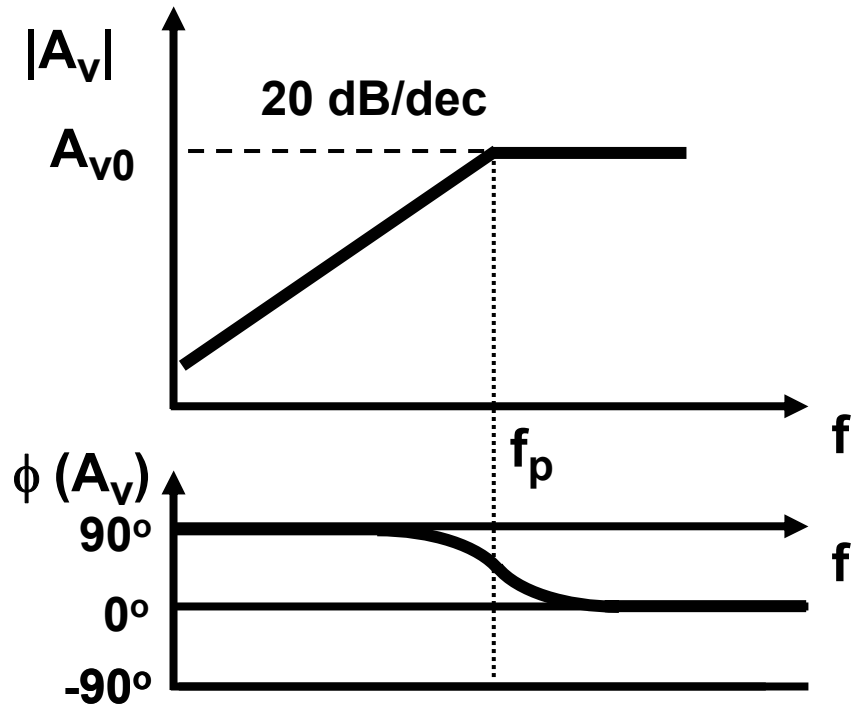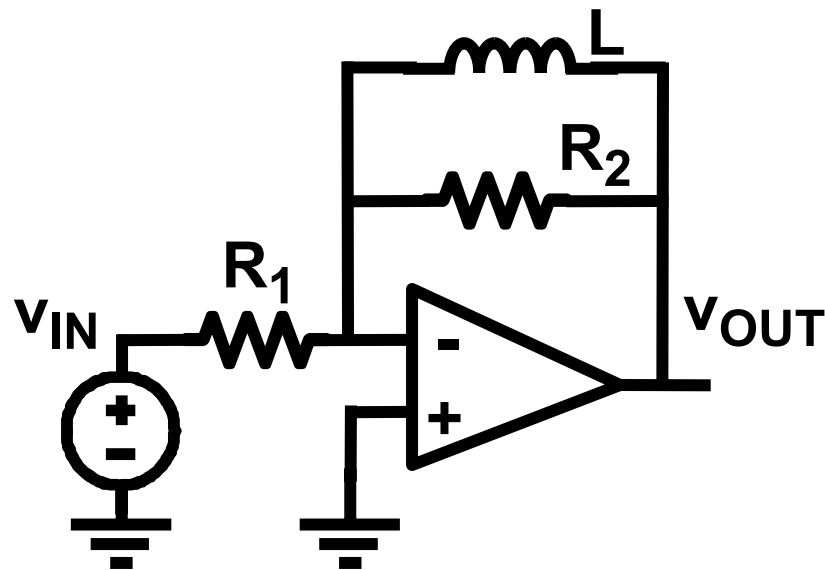

$$A_{V0} = -\frac{R_2}{R_1} \quad A_V = A_{V0} \frac{j \frac{f}{f_p}}{(1 + j \frac{f}{f_p})}$$

$$f_p = \frac{R_2}{2\pi L}$$

# High-pass filter

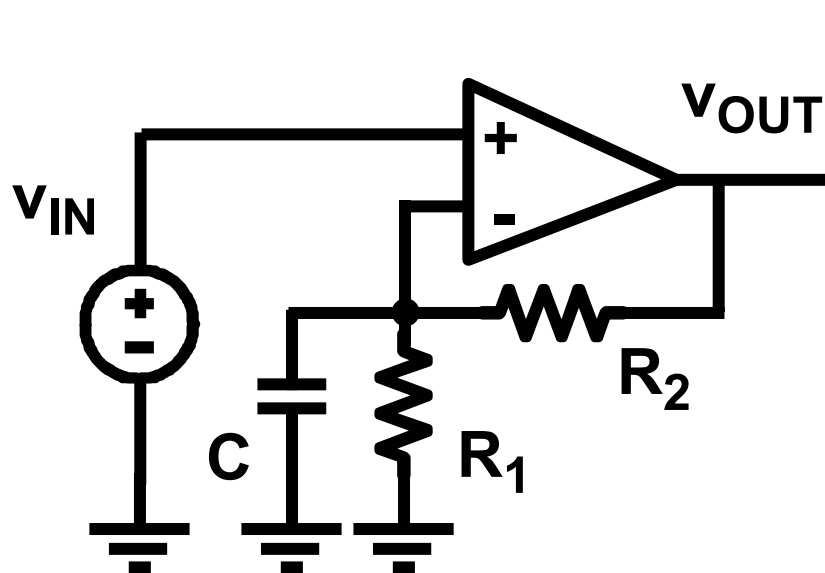


$$A_{v0} = 1 + \frac{R_2}{R_1}$$



$$A_v = A_{v0} \left( 1 + j \frac{f}{f_z} \right)$$

$$f_z = \frac{1}{2\pi RC}$$
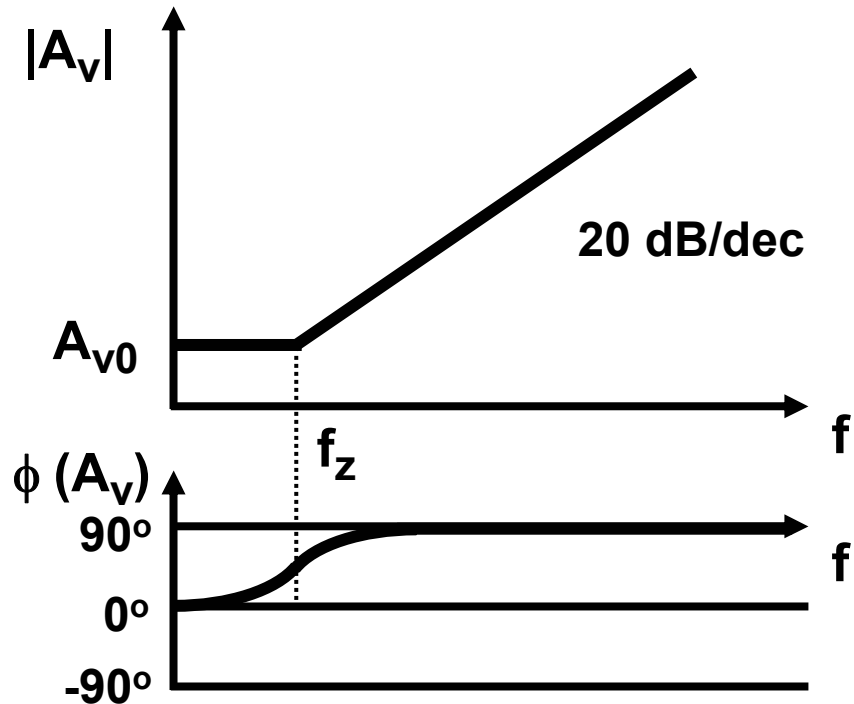
$$R = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$


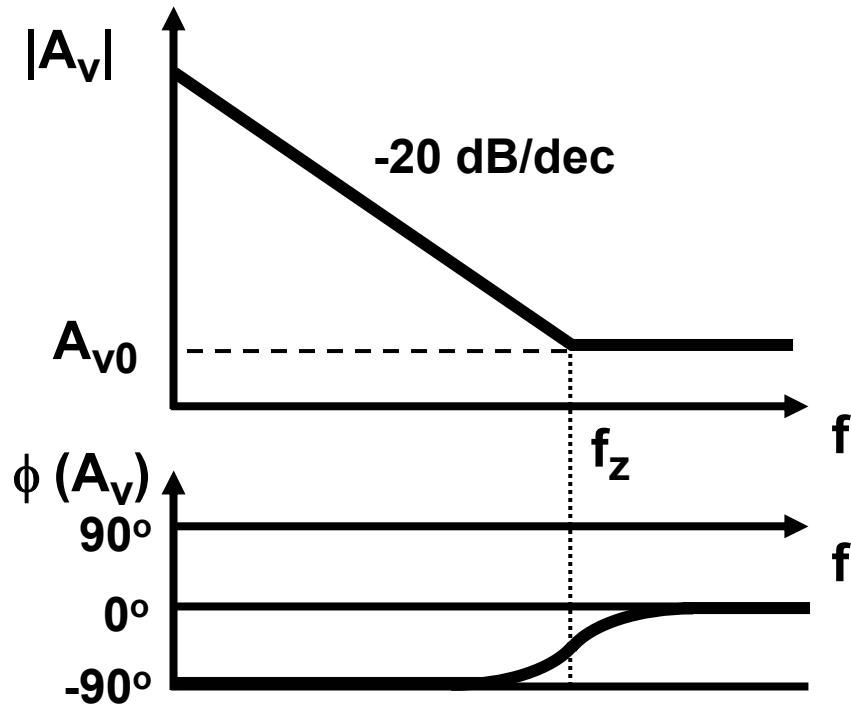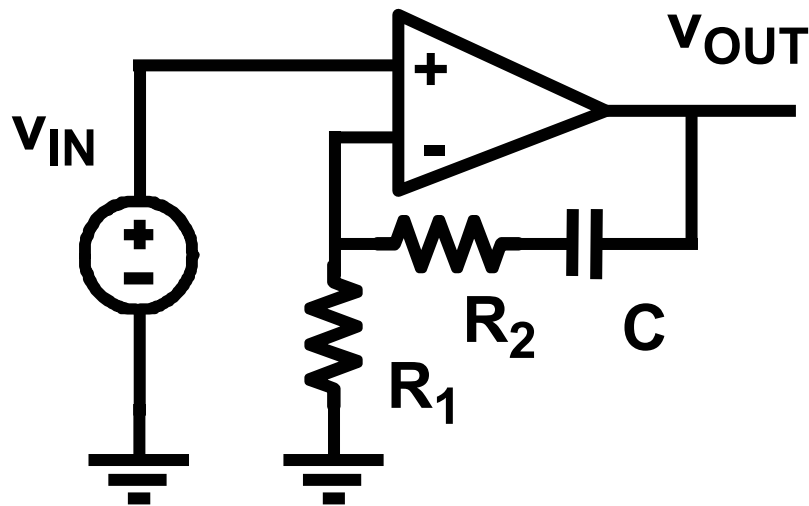
# Low-pass filter with finite attenuation




$$A_{v0} = 1 + \frac{R_2}{R_1} \quad A_v = A_{v0} \frac{(1 + j \frac{f}{f_z})}{j \frac{f}{f_z}}$$

$$f_z = \frac{1}{2\pi RC}$$

$$R = R_1 + R_2$$

# Exchange of gain and bandwidth

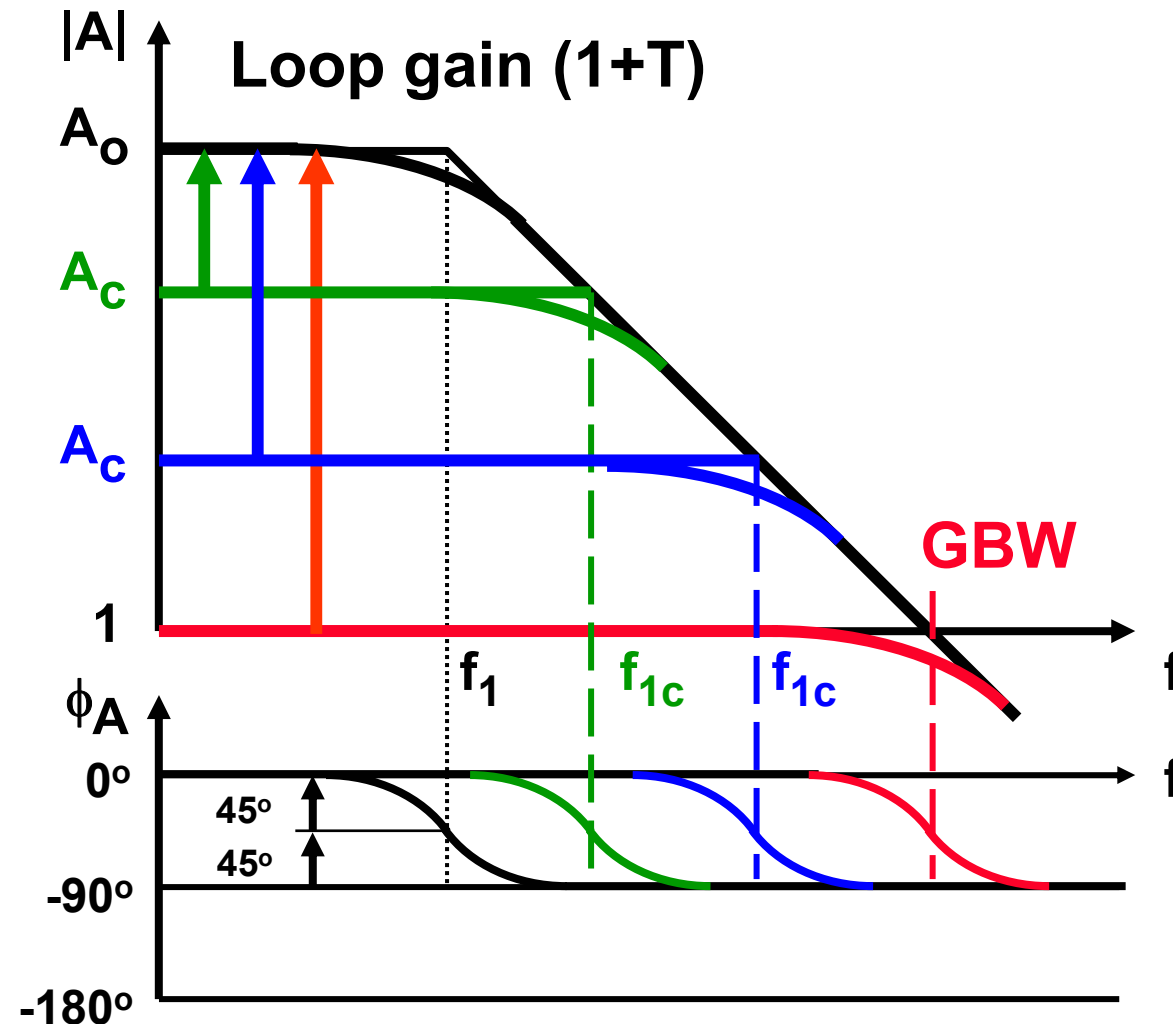

$A_o$  open loop gain

$A_c$  closed loop gain

$$A_o f_1 =$$

$$A_c f_{1c} =$$

$$A_c f_{1c} =$$


$$\text{GBW}$$



---

# Open- and closed-loop gain

---

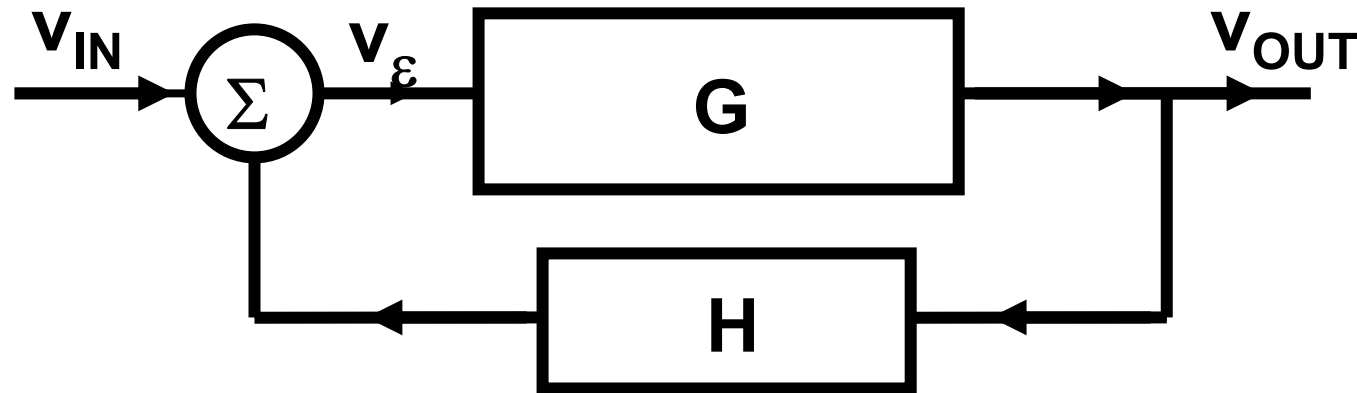

$$\left. \begin{aligned} V_{\varepsilon} &= V_{IN} - H V_{OUT} \\ V_{OUT} &= G V_{\varepsilon} \end{aligned} \right\} A_c = \frac{V_{OUT}}{V_{IN}} = \frac{G}{1 + GH} \approx \frac{1}{H}$$


if the loop gain  $GH = T \gg 1$

P. Gray, P.Hurst, S.Lewis, R. Meyer: Design of analog integrated circuits,  
4th ed., Wiley 2001

---

# What makes an opamp an opamp ?

---

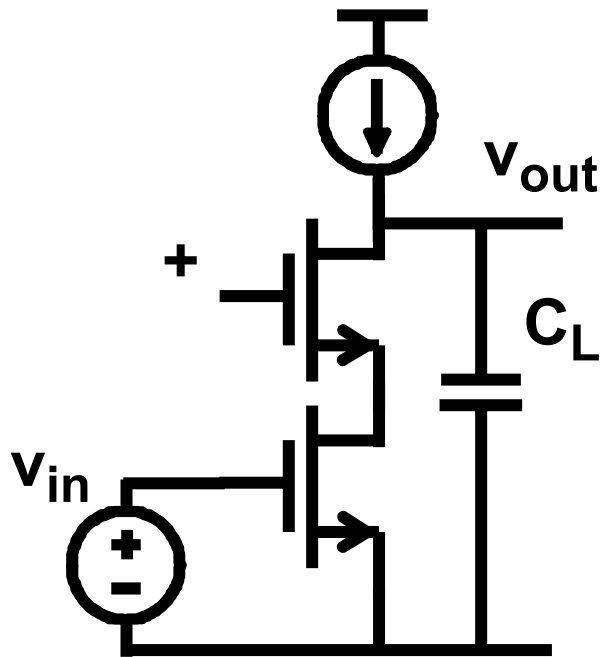


## Operational amplifier :

Single-pole amplifier

High impedance = high gain

Exchange Gain-Bandwidth

Stable for all gain values

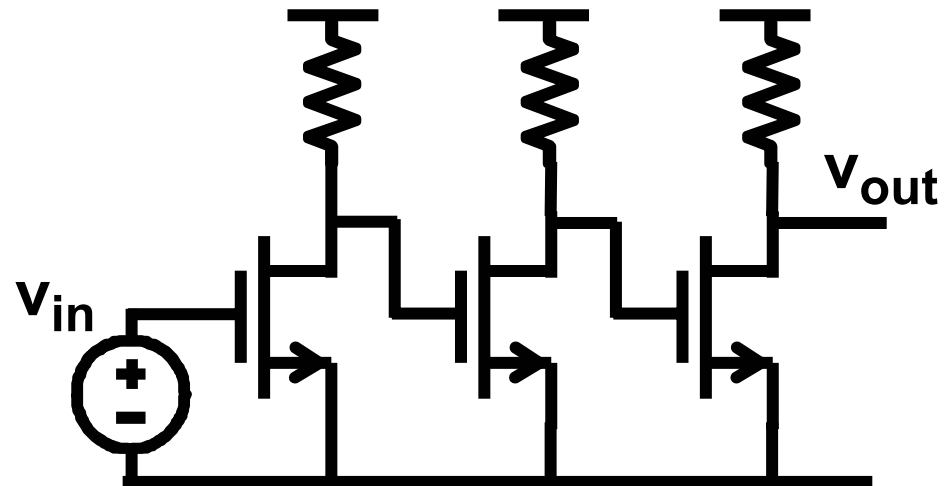

## Wideband amplifier :


Multiple-pole amplifier

Low impedances at nodes

Wide Bandwidth


Stable for one gain only

# Single-pole system

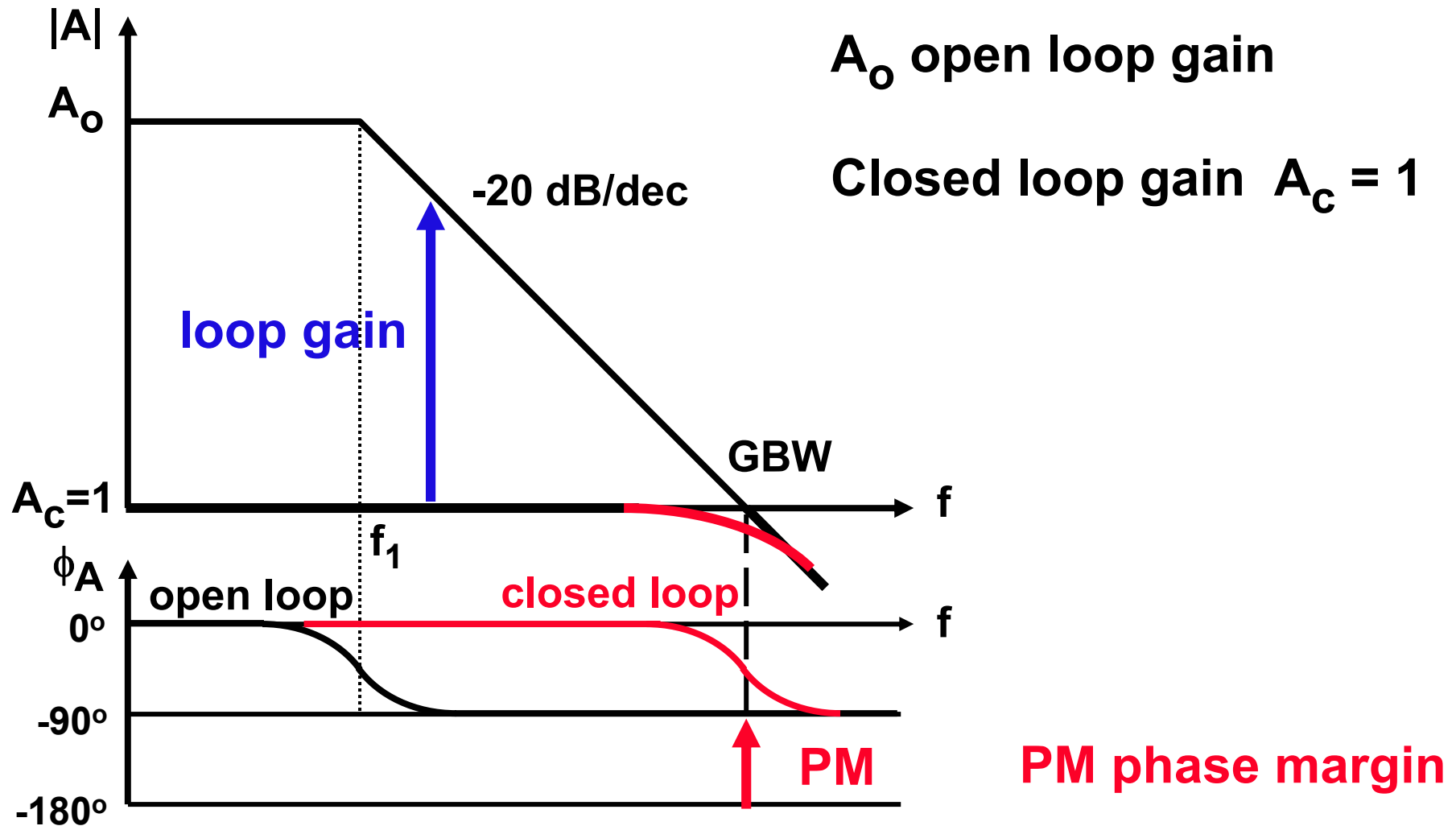




# Two-pole system

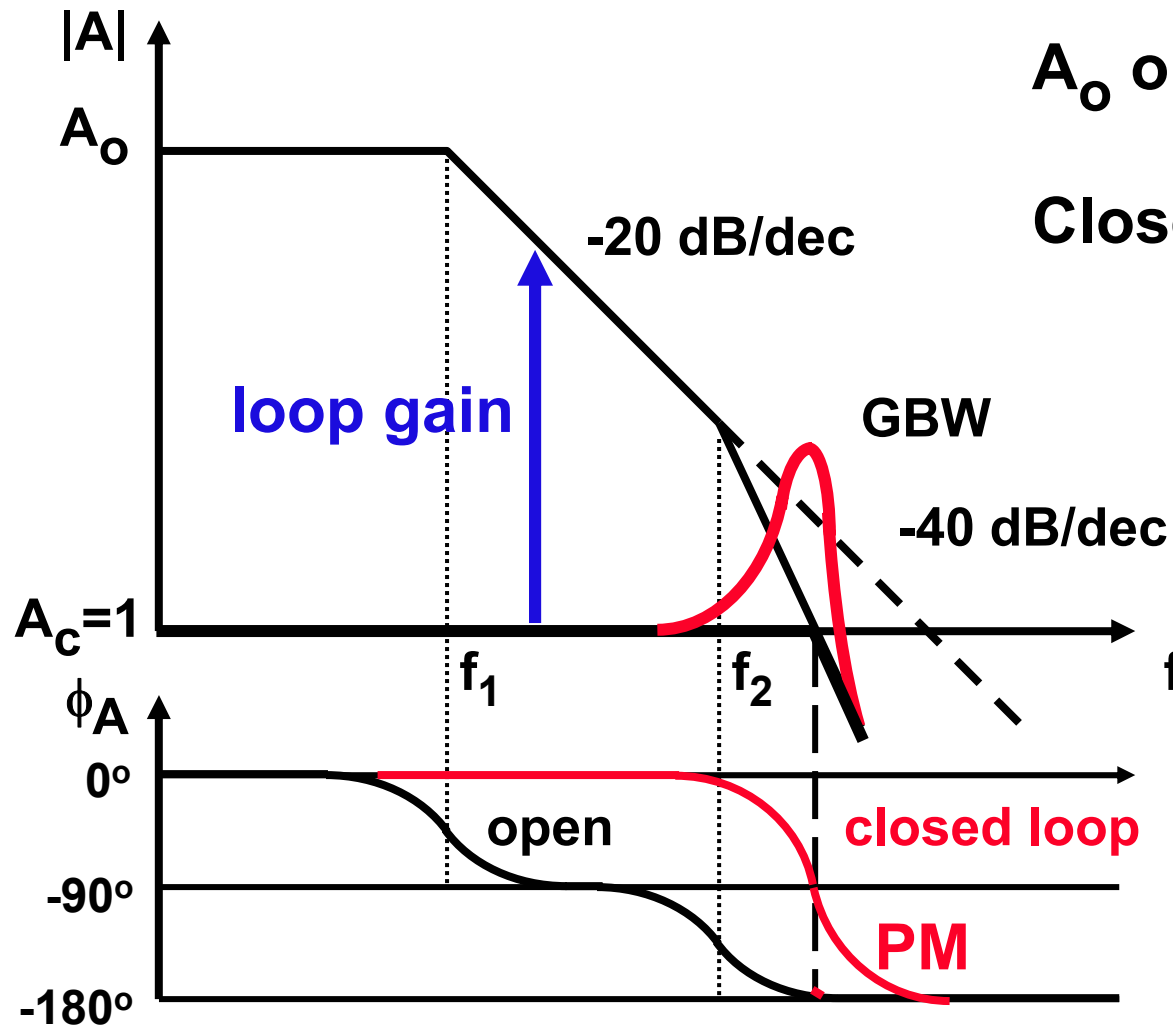


$A_o$  open loop gain

Closed loop gain  $A_c = 1$

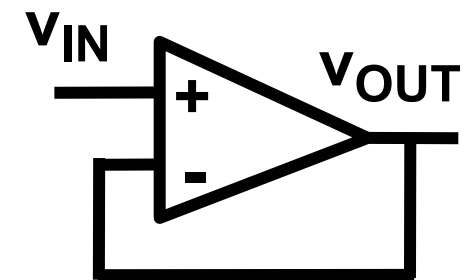


PM phase margin


# Higher loop gain gives less PM

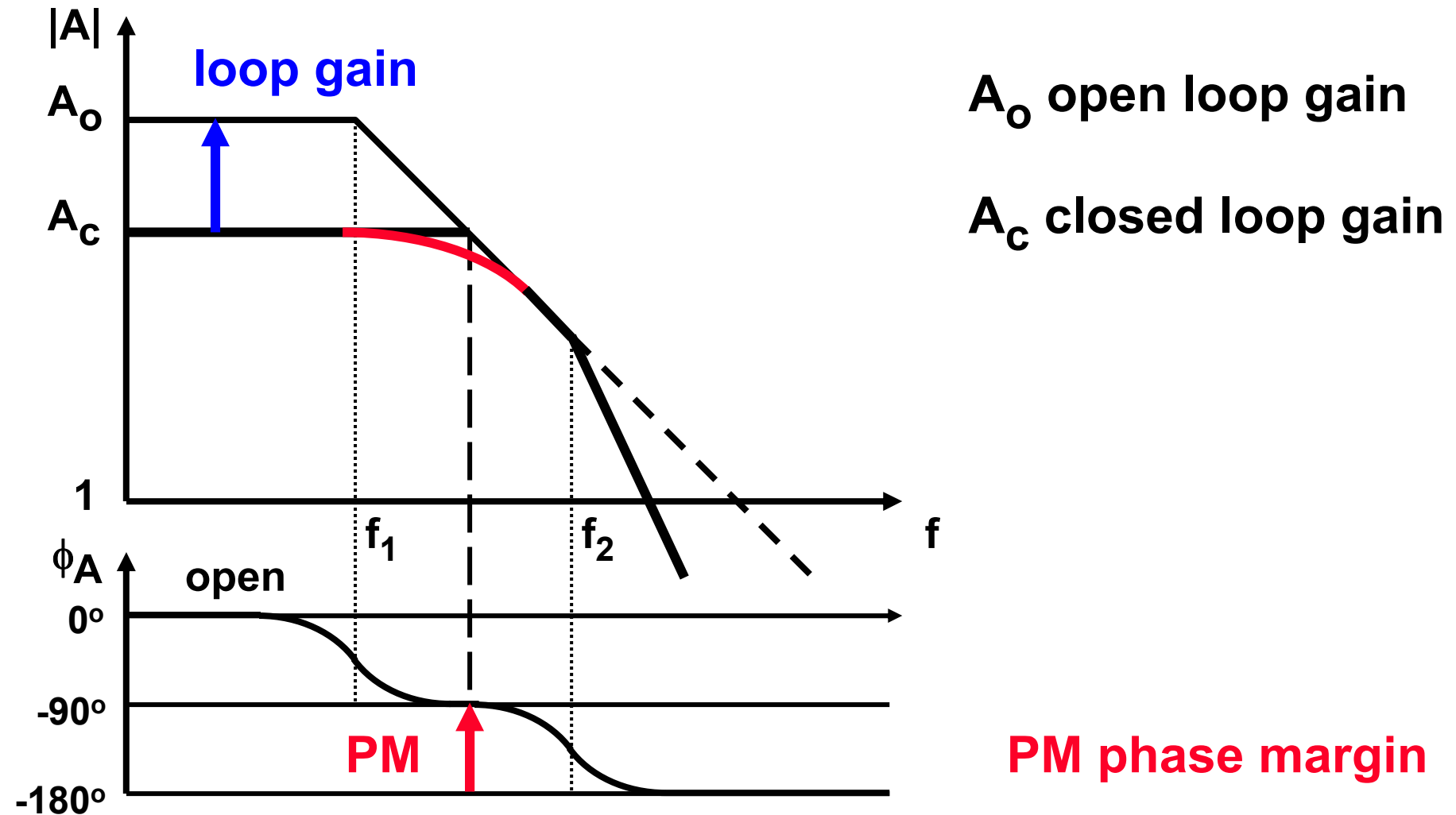


# Higher loop gain gives less PM

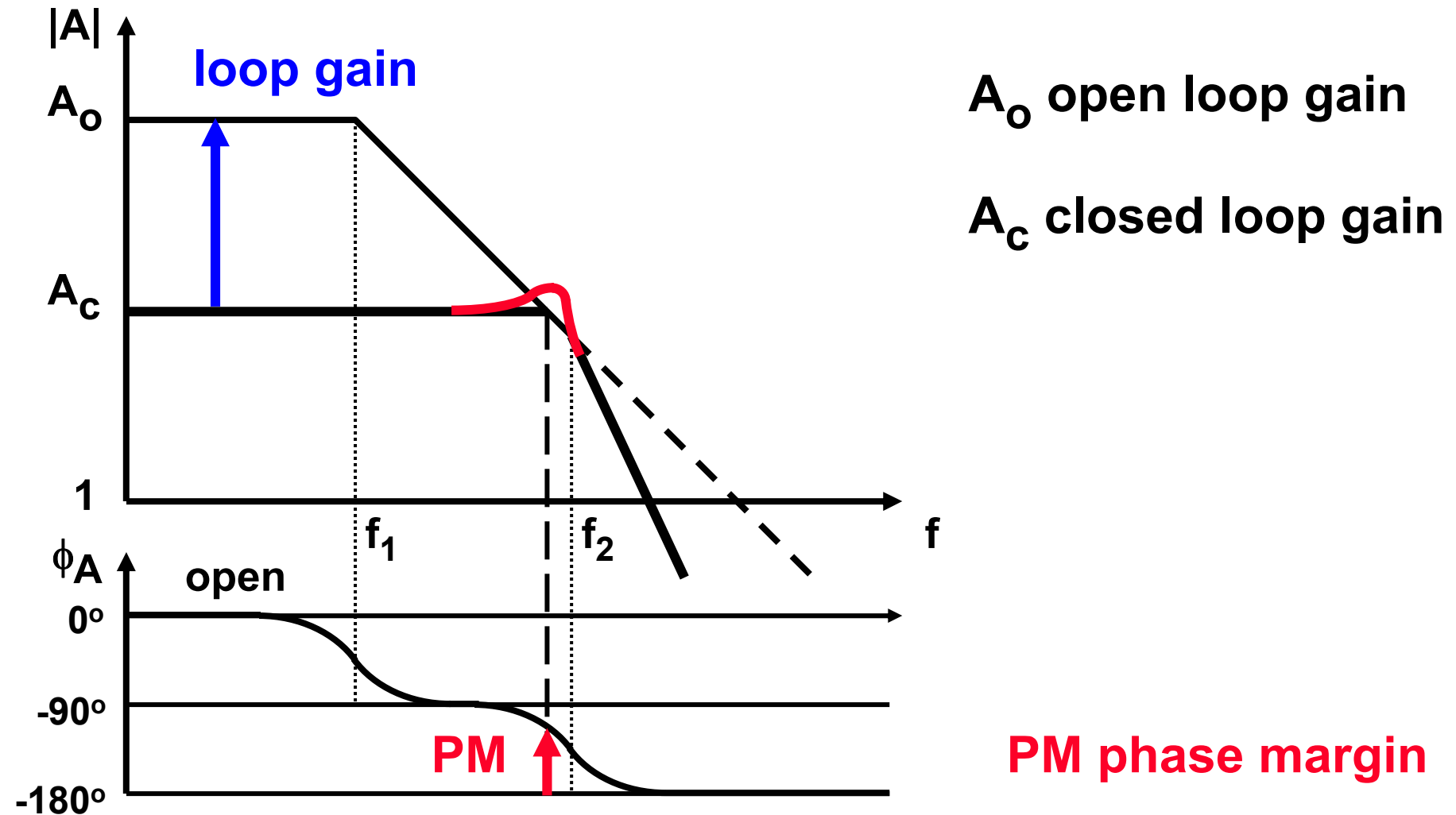

# Higher loop gain gives less PM

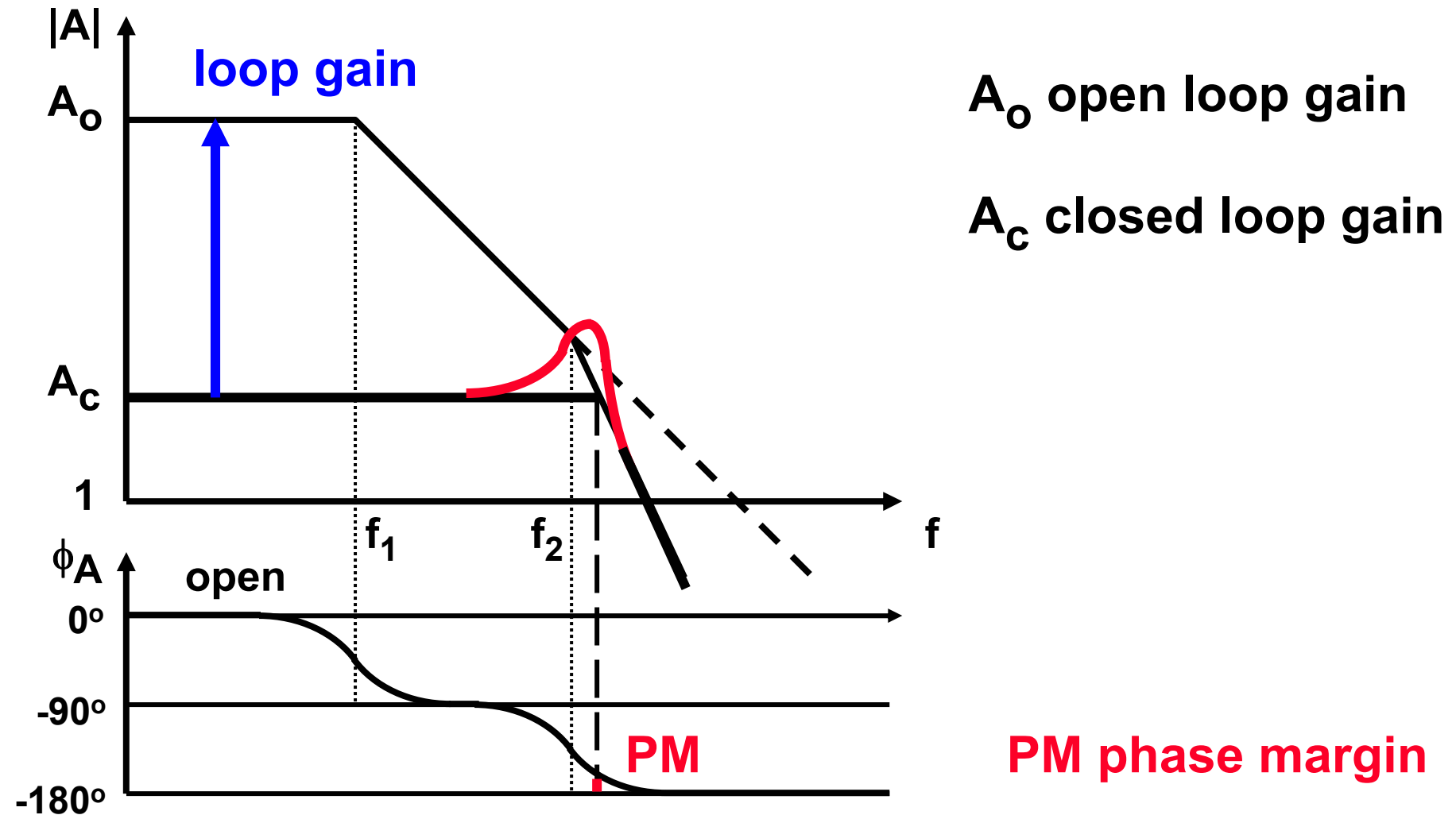

# Higher loop gain gives less PM

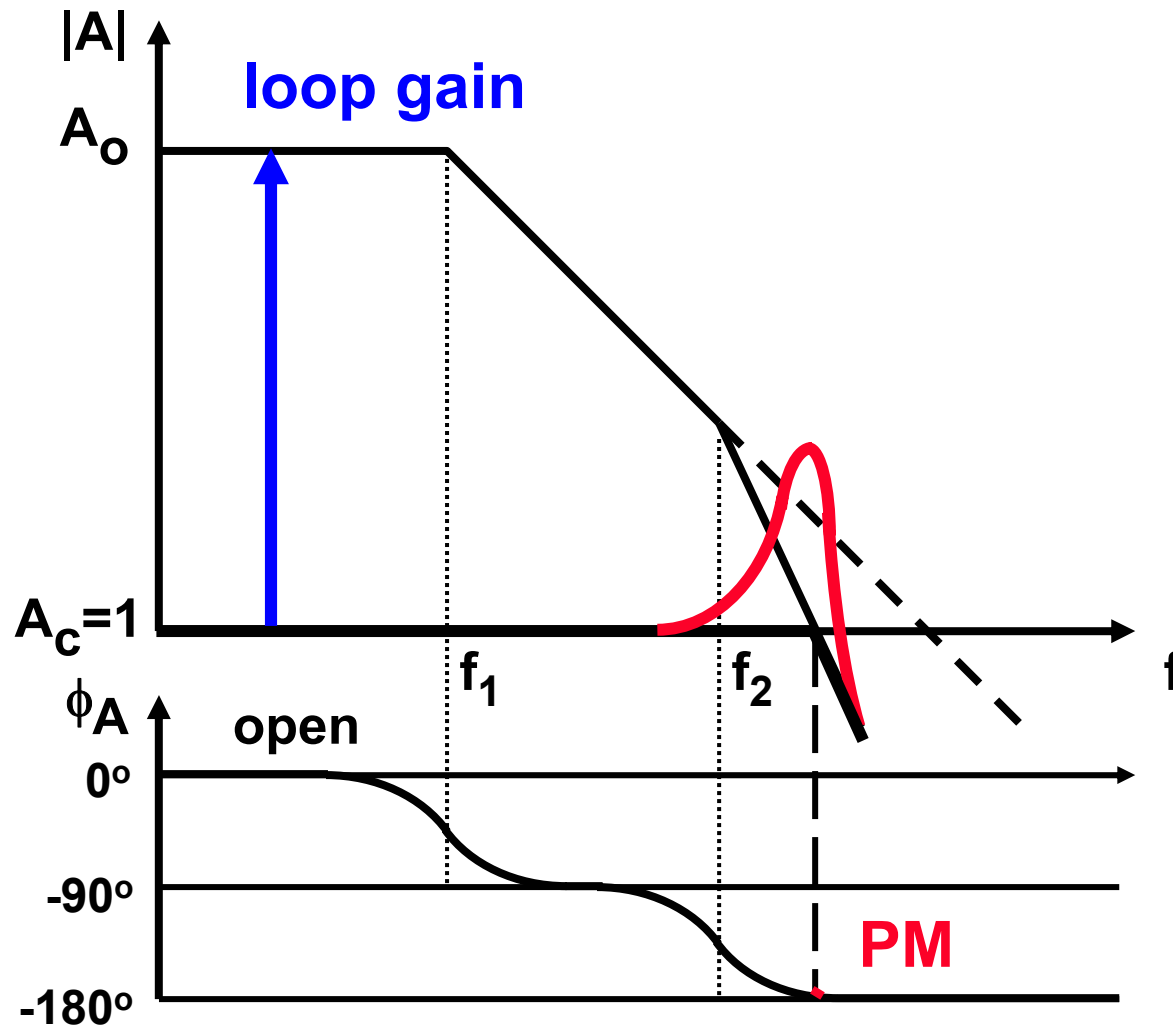

$A_o$  open loop gain

$A_c$  closed loop gain

**Worst case  
for  $A_c = 1$**


**PM phase margin**




---

## Increase PM by increasing $f_2$ : low $f_2$


---

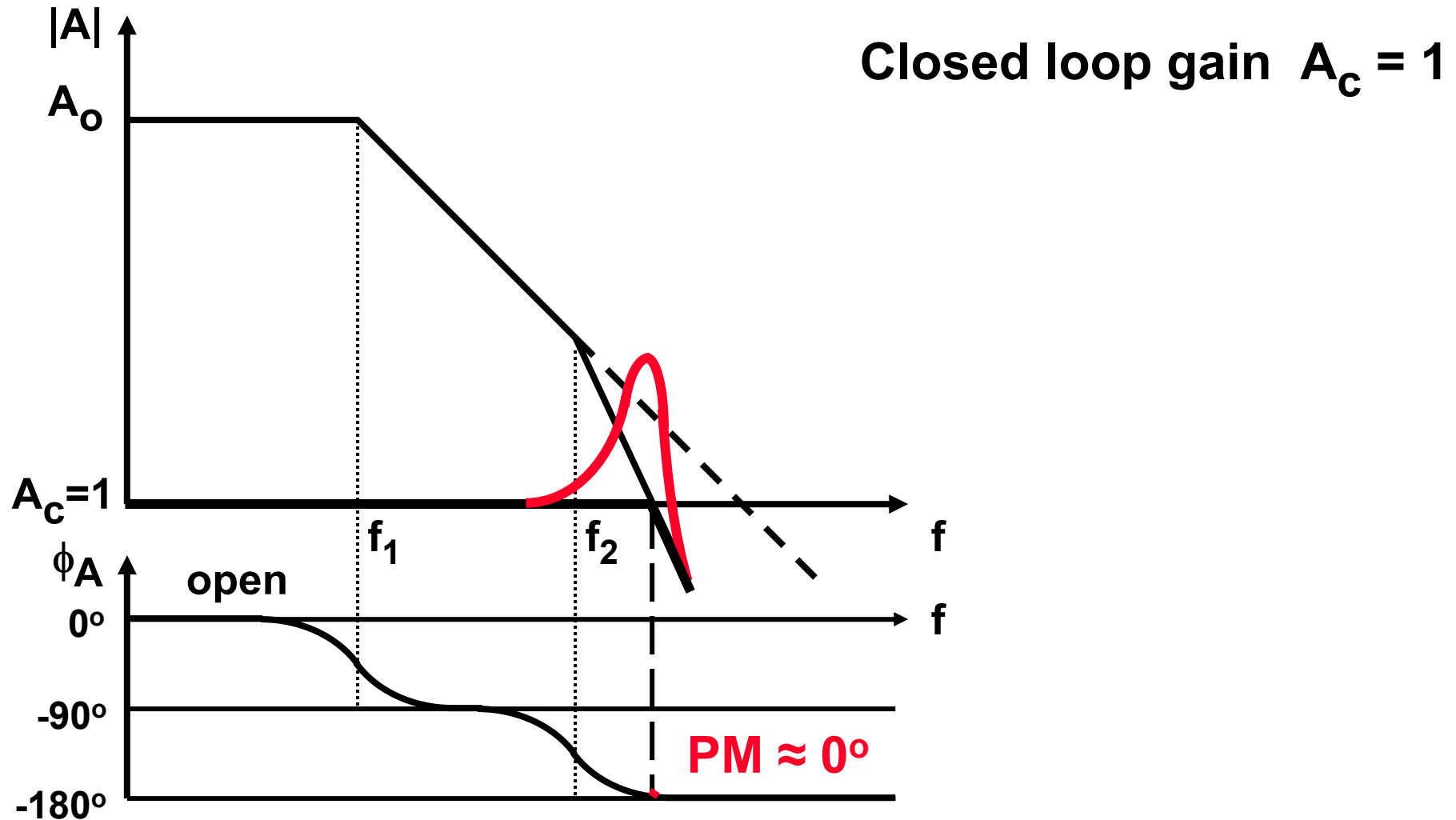

# Increase PM by increasing $f_2$

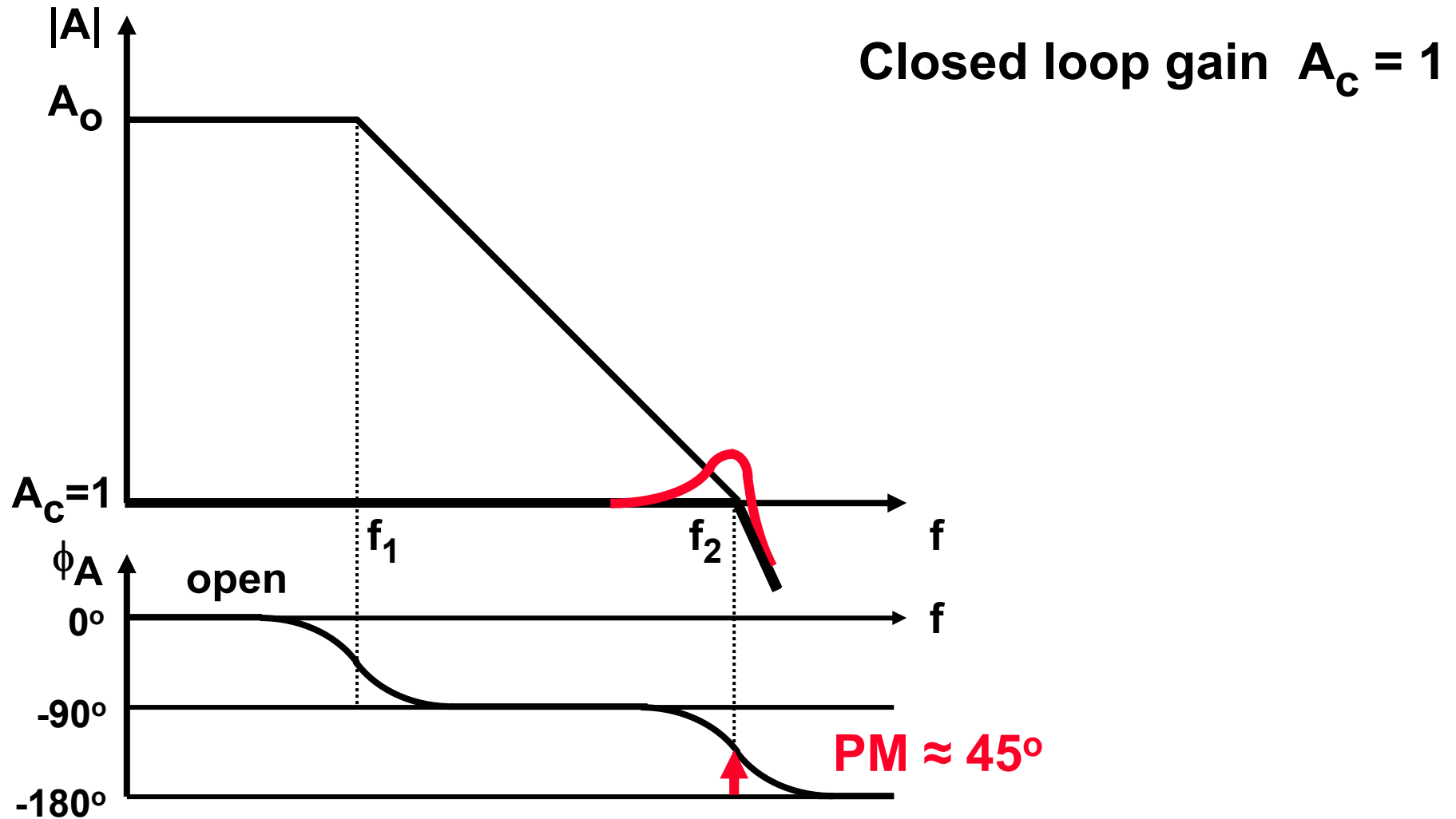
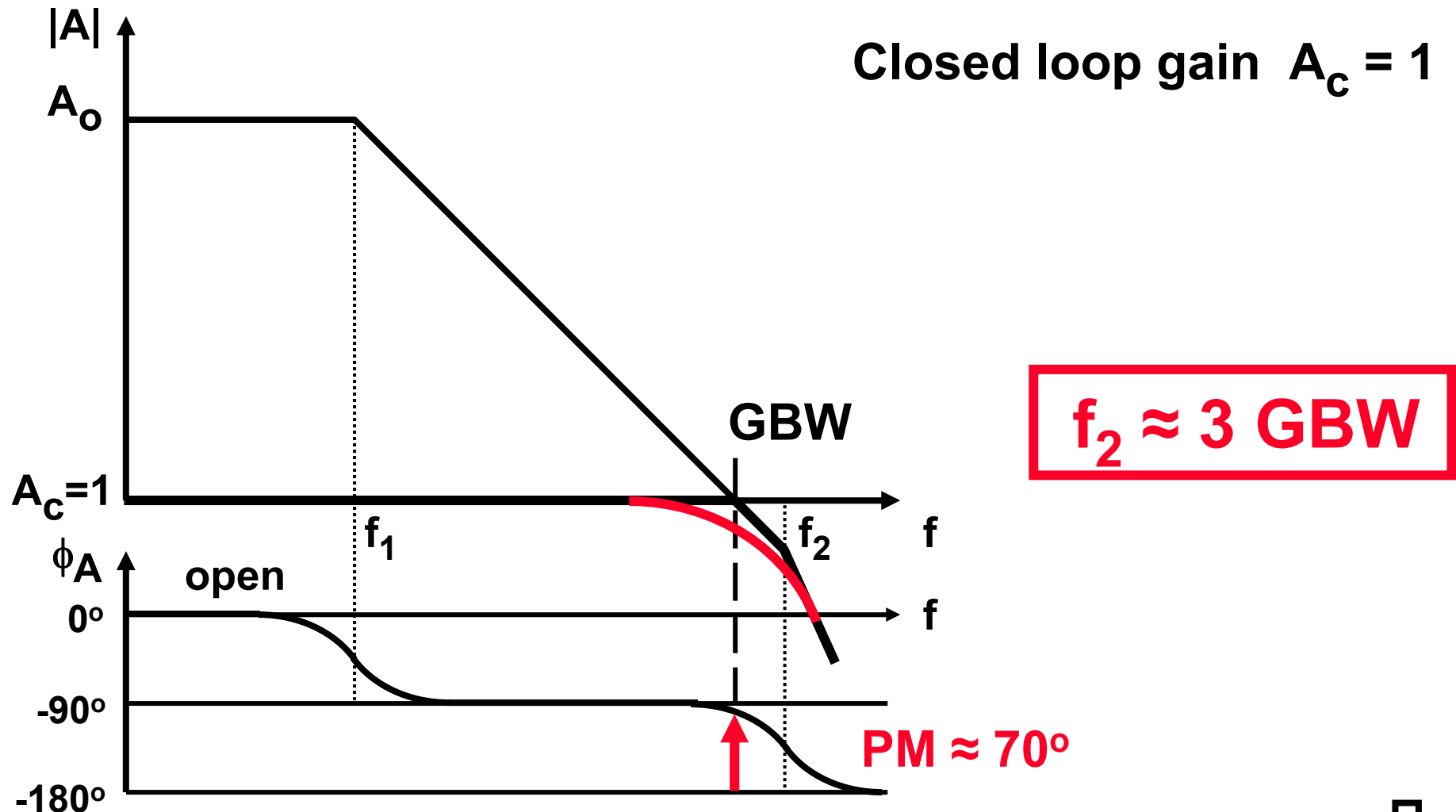
# Set PM by setting $f_2 \approx 3 \text{ GBW}$






---
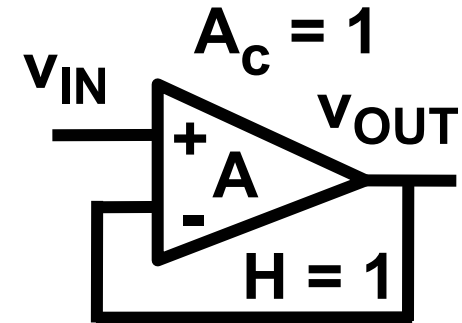
## Calculate PM for $f_2 \approx 3 \text{ GBW}$

---

Open loop gain  $A = \frac{A_o}{(1 + j \frac{f}{f_1})(1 + j \frac{f}{f_2})}$



Closed loop gain  $A_c = \frac{A}{1+A} \approx \frac{1}{1 + j \frac{f}{\text{GBW}} + j^2 \frac{f^2}{\text{GBW} f_2}}$

$\approx \frac{1}{1 + j 2\zeta \frac{f}{f_r} + j^2 \frac{f^2}{f_r^2}}$

$\zeta$  is the damping ( $=1/2Q$ )

$f_r$  is the resonant frequency

---


## Relation PM, damping and $f_2/\text{GBW}$

---

$$f_r = \sqrt{\text{GBW} f_2} \quad \text{PM (}^\circ\text{)} = 90^\circ - \arctan \frac{\text{GBW}}{f_2} = \arctan \frac{f_2}{\text{GBW}}$$

$\frac{f_2}{\text{GBW}}$	PM (°)	$\zeta = \frac{1}{2} \sqrt{\frac{f_2}{\text{GBW}}}$	$P_f$ (dB)	$P_t$ (dB)
0.5	27	0.35	3.6	2.3
1	45	0.5	1.25	1.3
1.5	56	0.61	0.28	0.73
2	63	0.71	0	0.37
3	72	0.87	0	0.04


# Amplitude response vs frequency

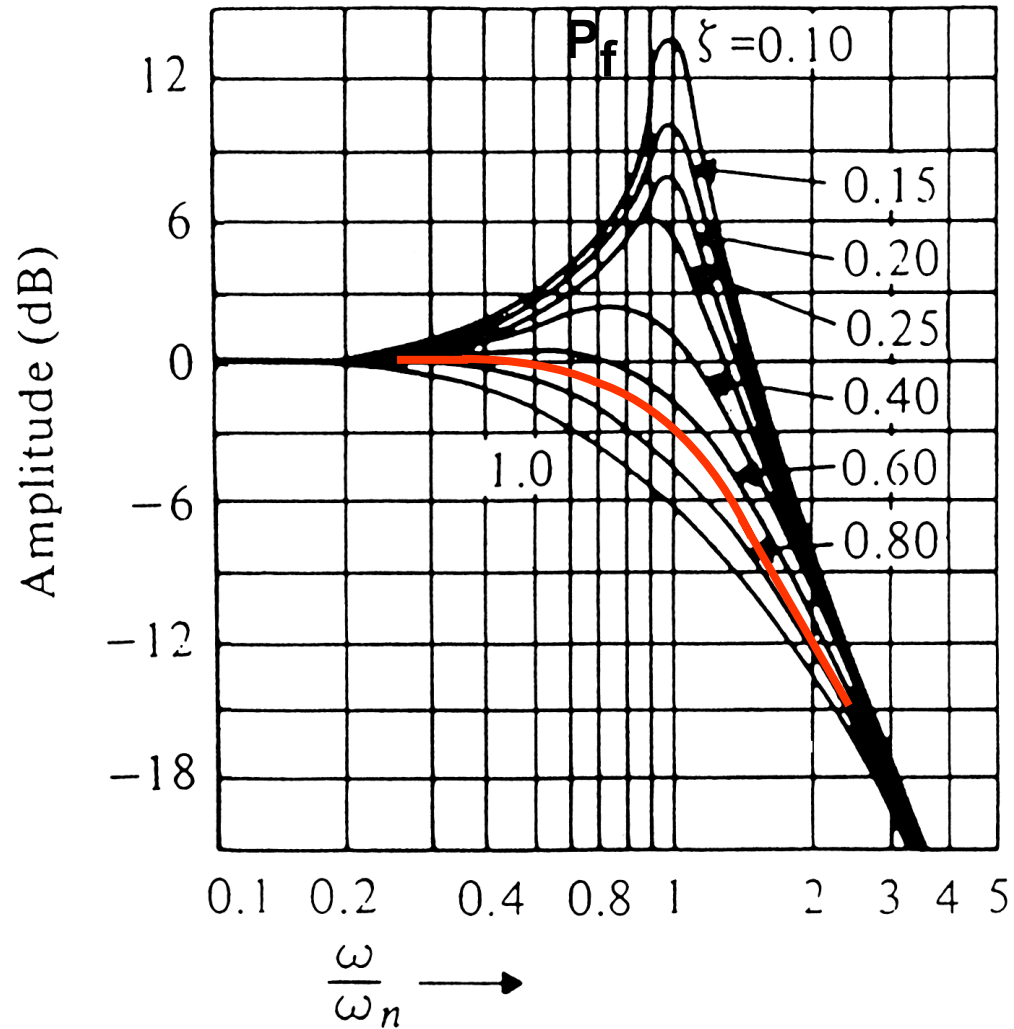

$$\zeta = Q = 0.7$$

$$P_f = \frac{1}{2 \zeta \sqrt{1 - \zeta^2}}$$

# Amplitude response vs time

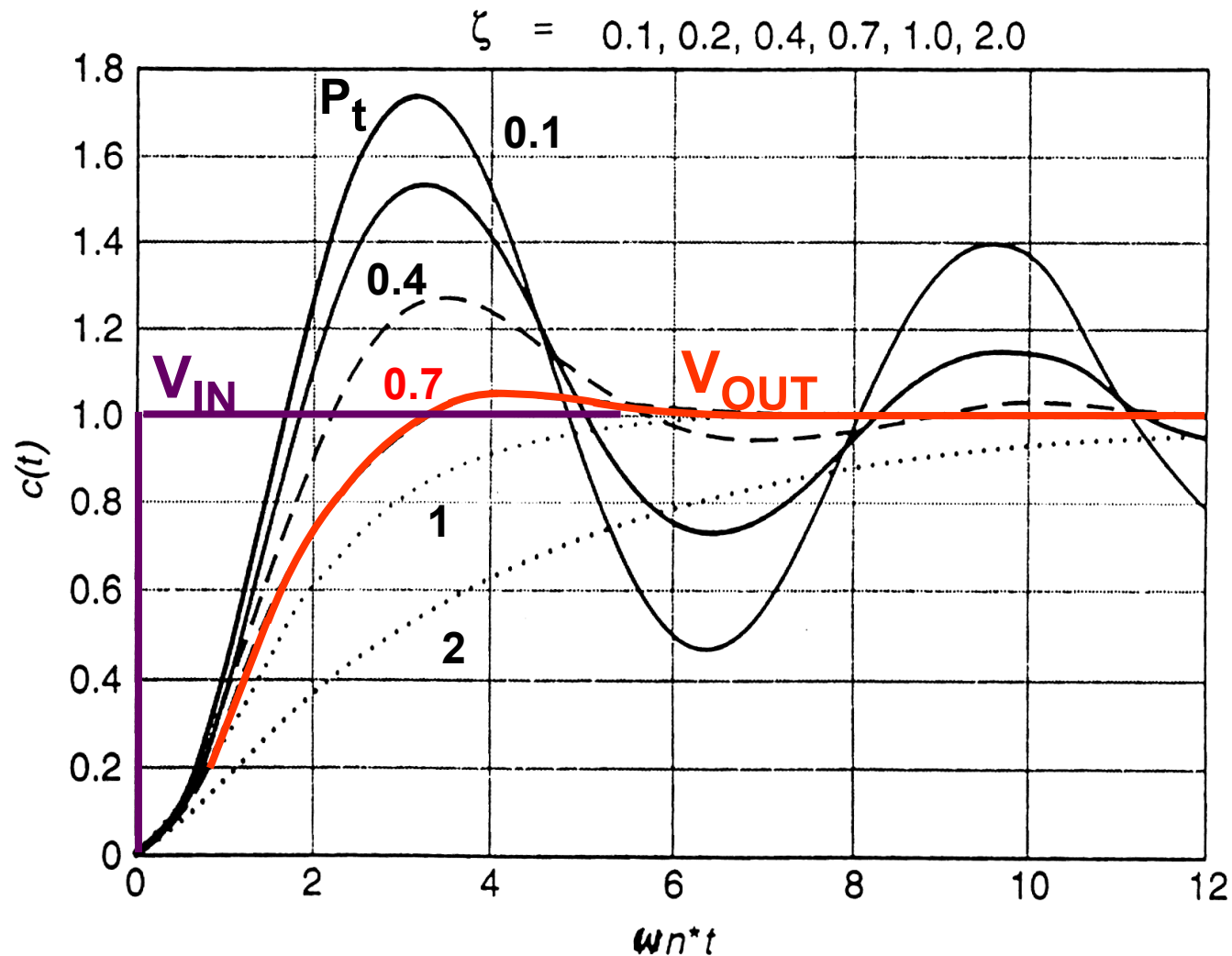

$$\zeta = Q = 0.7$$

$$P_t =$$

$$1 + e^{\frac{-\pi \zeta}{\sqrt{1 - \zeta^2}}}$$



---

# Table of contents

---

- Use of operational amplifiers
- Stability of 2-stage opamp
- Pole splitting
- Compensation of positive zero
- Stability of 3-stage opamp

# Generic 2-stage opamp

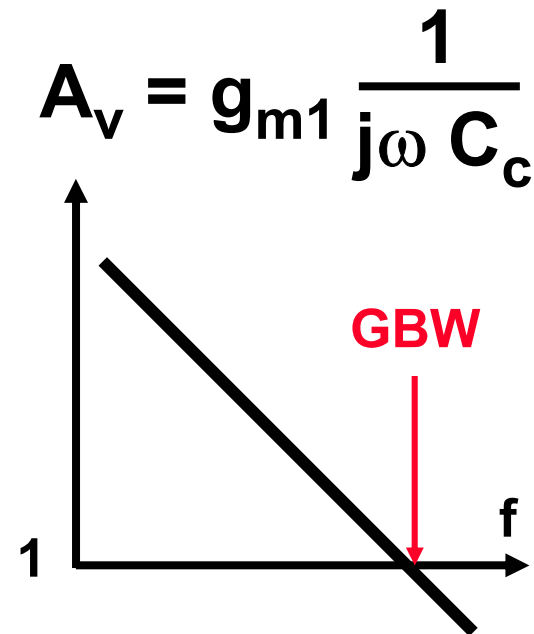
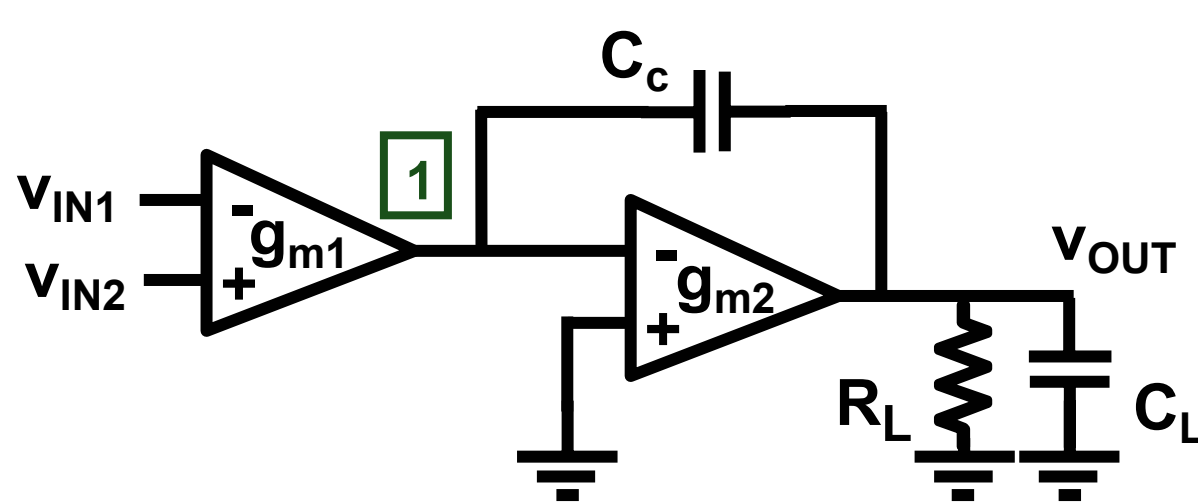


$$|A_v| = 1 \Rightarrow$$

$$\text{GBW} = \frac{g_{m1}}{2\pi C_c}$$

$$f_{nd} = \frac{g_{m2}}{2\pi C_L}$$

# Generic 2-stage opamp

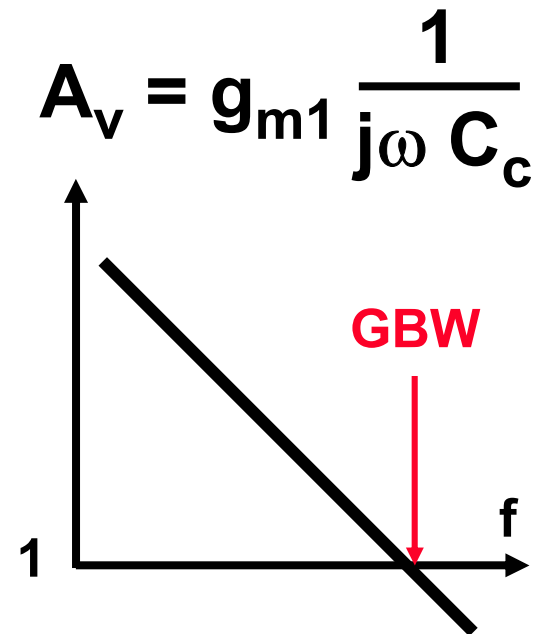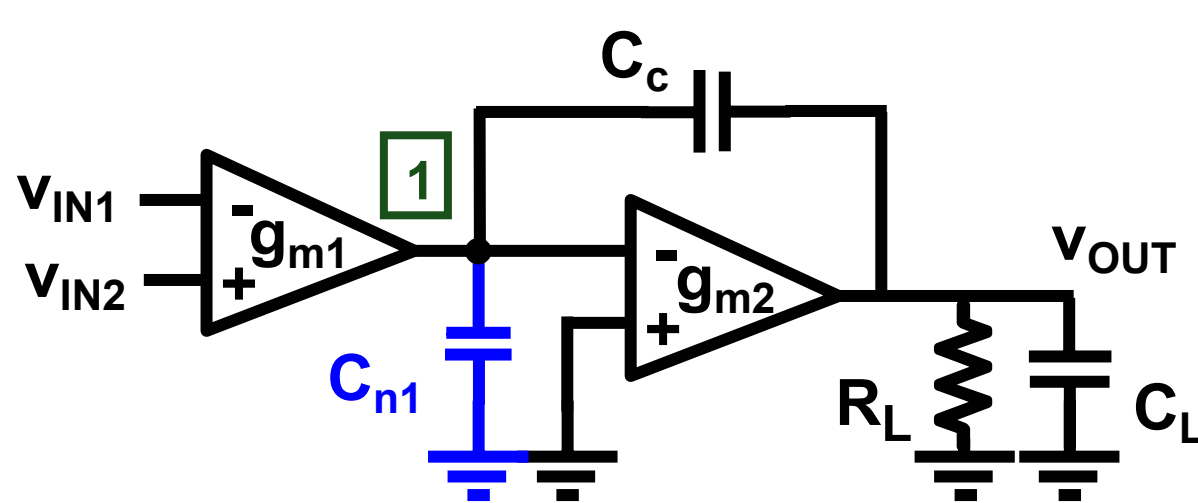

$$|A_v| = 1 \Rightarrow$$

$$\text{GBW} = \frac{g_{m1}}{2\pi C_c}$$

$$f_{nd} = \frac{g_{m2}}{2\pi C_L} \frac{1}{1 + \frac{C_{n1}}{C_c}}$$

---

## Elementary design of 2-stage opamp

---

$$\text{GBW} = \frac{g_{m1}}{2\pi C_c} \quad f_{nd} = 3 \text{ GBW} = \frac{g_{m2}}{2\pi C_L} \frac{1}{1 + \underbrace{\frac{C_{n1}}{C_c}}_{\approx 0.3}}$$

$$\frac{g_{m2}}{g_{m1}} \approx 4 \frac{C_L}{C_c}$$

**Larger current in 2nd stage !**

**GBW = 100 MHz for  $C_L = 2$  pF**

**Solution: choose  $C_c = 1$  pF**




---

# Table of contents


---

- Use of operational amplifiers
- Stability of 2-stage opamp
- Pole splitting
- Compensation of positive zero
- Stability of 3-stage opamp

# Generic 2-stage opamp : Miller OTA

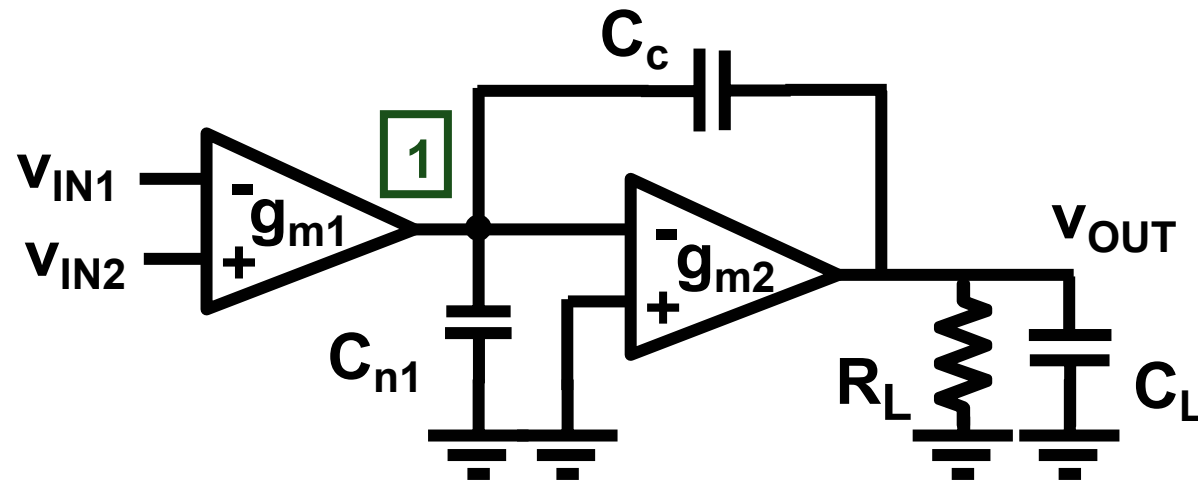


$$A_{v0} = -A_{v1}A_{v2}$$

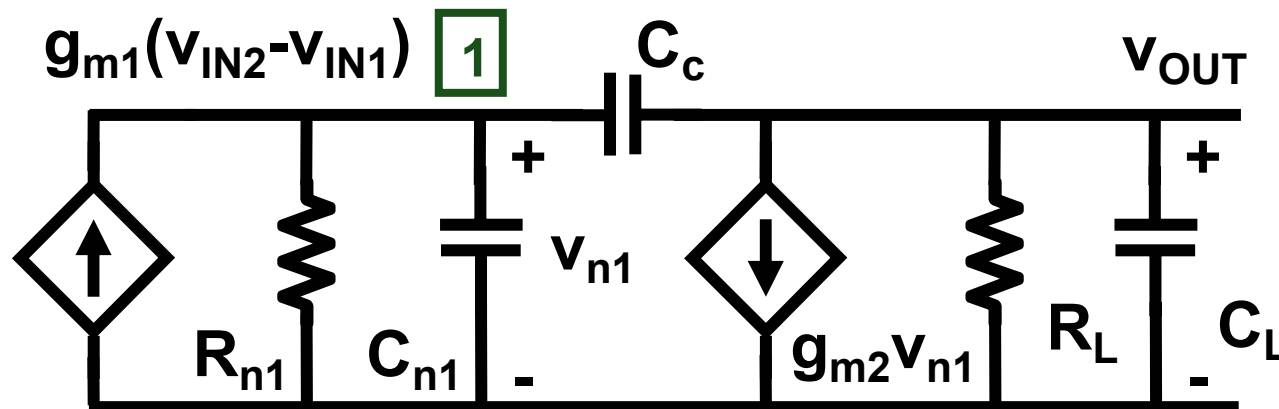

$$A_{v1} = g_{m1}R_{n1}$$

$$A_{v2} = -g_{m2}R_L$$

# Generic two-stage opamp

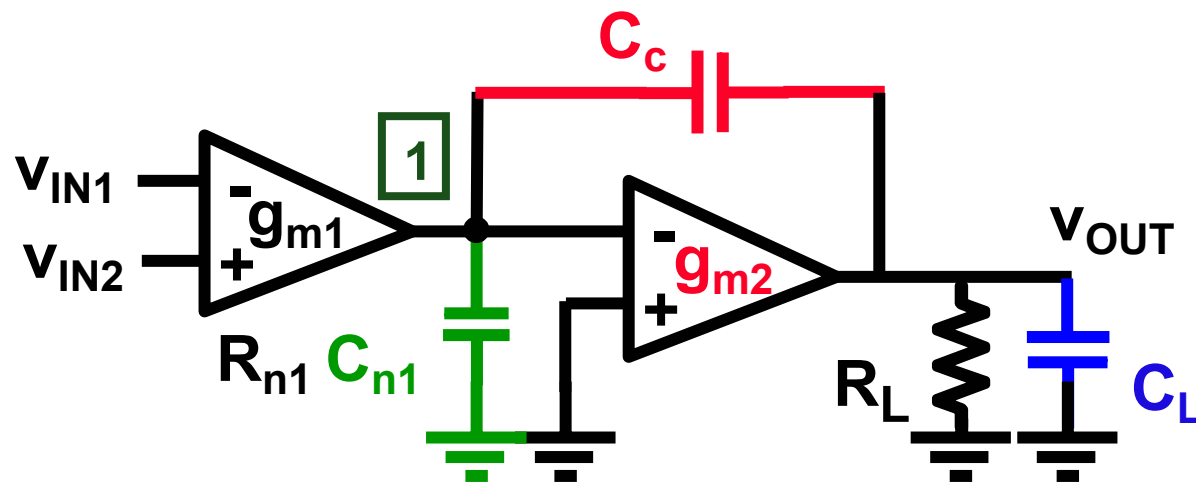

$$A_{v0} = -A_{v1}A_{v2}$$

$$A_{v1} = g_{m1}R_{n1}$$

$$A_{v2} = g_{m2}R_L$$

$$1 - \frac{C_c}{g_{m2}} s$$

$$A_v = A_{v0} \frac{1 - \frac{C_c}{g_{m2}} s}{1 + (R_{n1}C_{n1} + A_{v2}R_{n1}C_c + R_L C_L)s + R_{n1}R_L CC s^2}$$

$$CC = C_{n1}C_c + C_{n1}C_L + C_cC_L$$

---

# Approximate poles and zeros

---


$$A = A_0 \frac{1 - cs}{1 + as + bs^2}$$

$$\text{Zero } s = \frac{1}{c}$$

$$\text{Pole } s_1 = -\frac{1}{a}$$

$$s_2 = -\frac{a}{b} \quad \text{if } s_2 \gg s_1$$

# Miller OTA : pole splitting with $C_c$

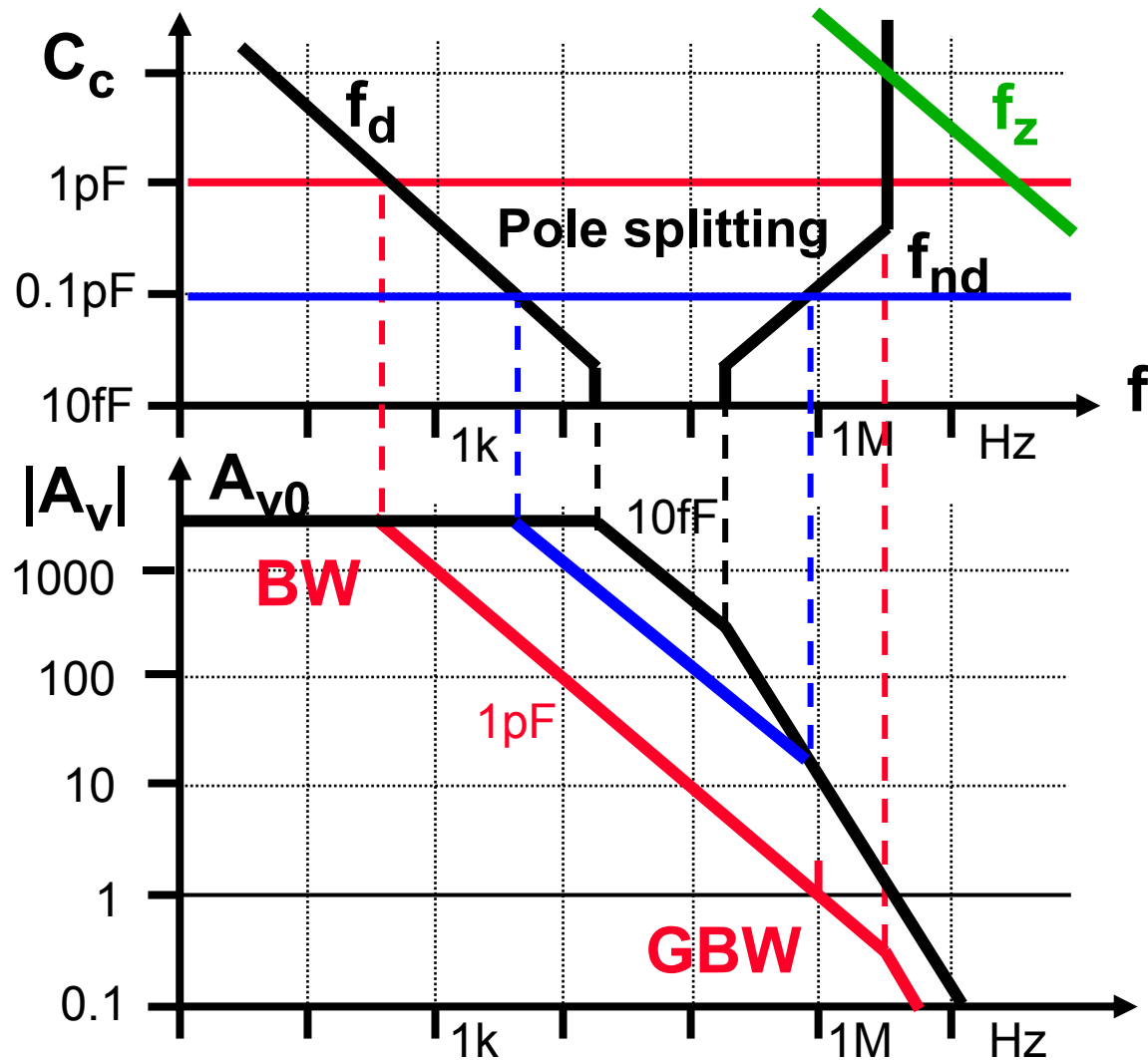

Pole splitting  
for high  $C_c$  :

$$f_d = \frac{1}{2\pi A_{v2} R_{n1} C_c}$$


$$f_z = \frac{g_{m2}}{2\pi C_c}$$

is a positive zero !

# Effect of positive zero

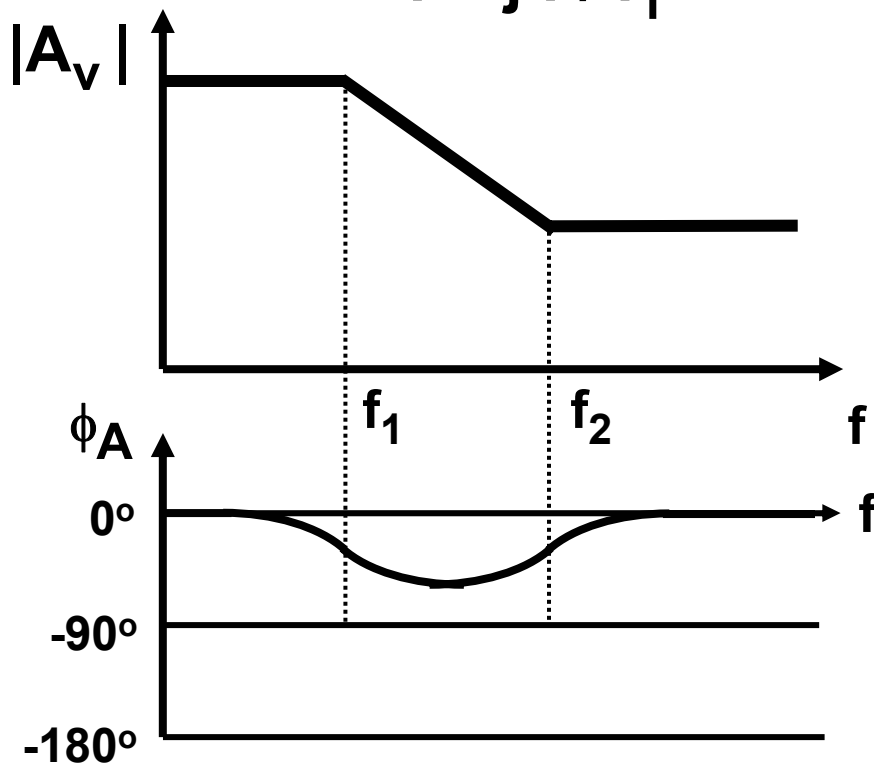
## Negative zero

$$A_v = A_{v0} \frac{1 + j f / f_2}{1 + j f / f_1}$$



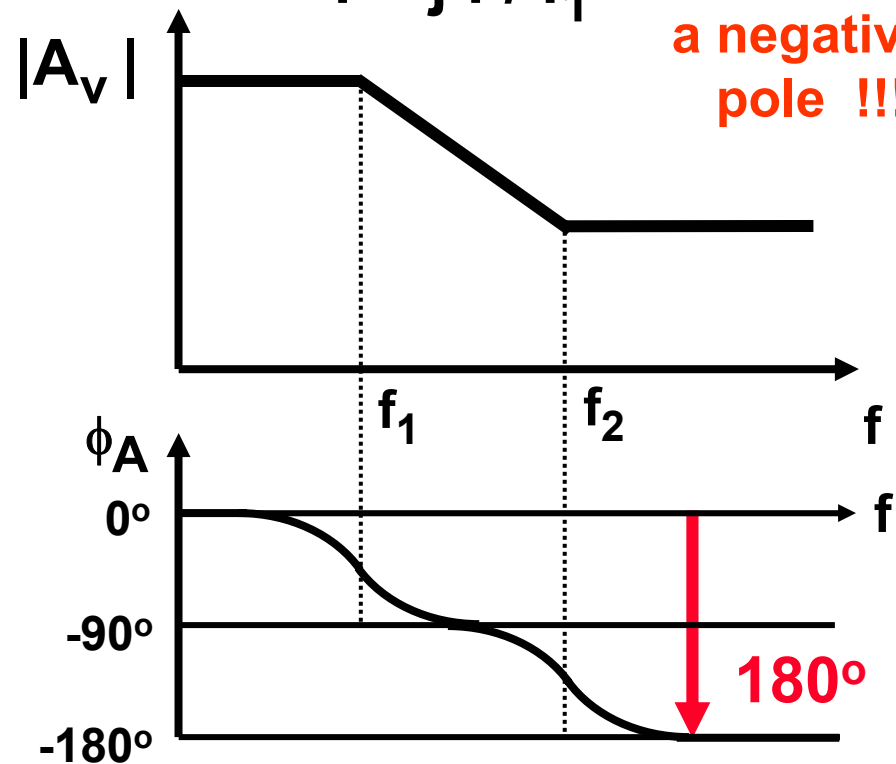
## Positive zero

$$A_v = A_{v0} \frac{1 - j f / f_2}{1 + j f / f_1}$$



For phase,  
a positive  
zero  
is like  
a negative  
pole !!!
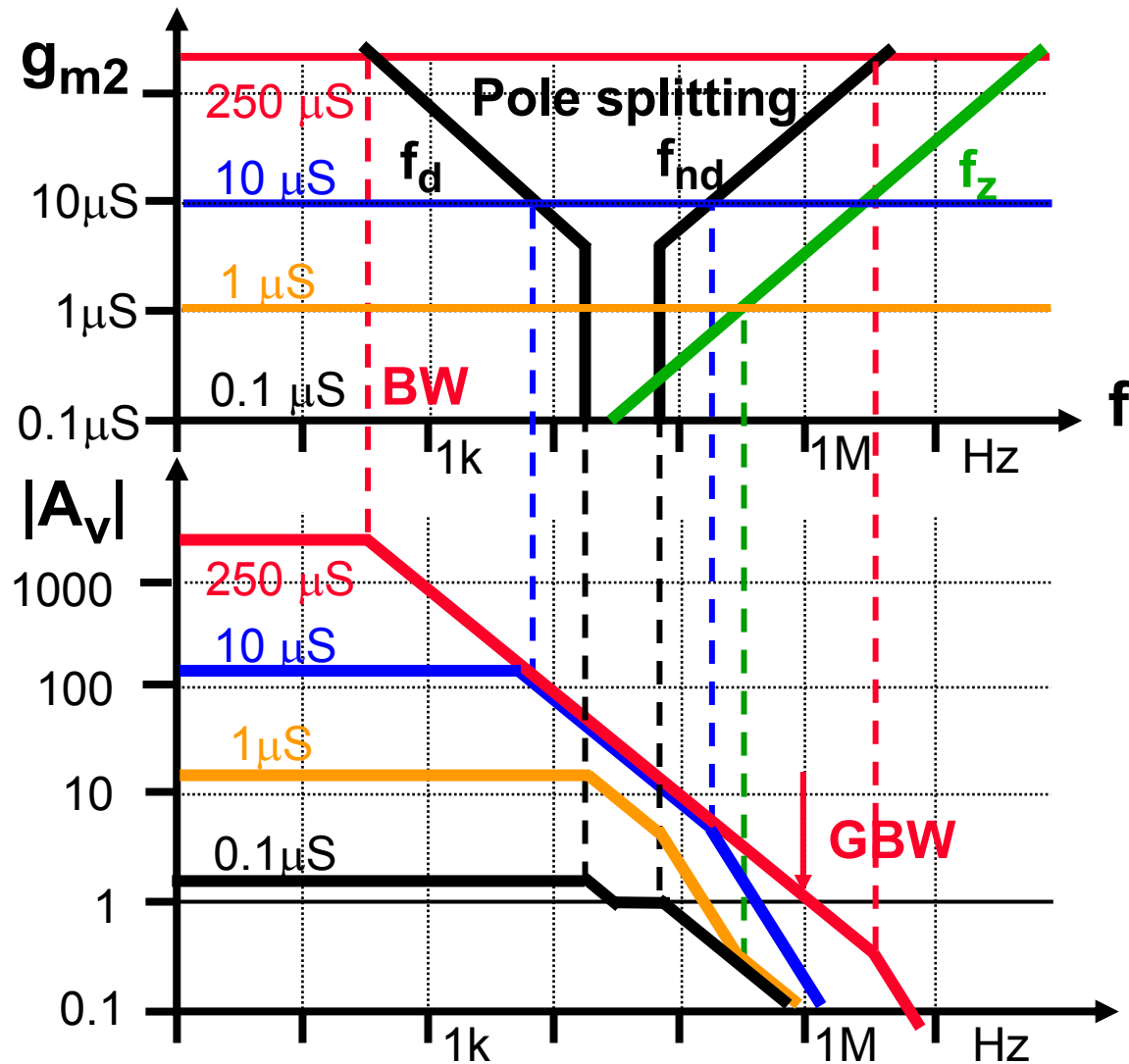
# Miller OTA : pole splitting with $g_{m2}$



Pole splitting  
for high  $g_{m2}$  :

$$f_d = \frac{1}{2\pi A_{v2} R_{n1} C_c}$$

$$f_z = \frac{g_{m2}}{2\pi C_c}$$

is a positive zero !



---

## Pole splitting by ...

---

$$\frac{g_{m2}}{g_{m1}} \approx 4 \frac{C_L}{C_c}$$

or  $g_{m2} C_c \approx 4 g_{m1} C_L$

**both  $g_{m2} C_c$**




---

# Table of contents


---

- **Use of operational amplifiers**
- **Stability of 2-stage opamp**
- **Pole splitting**
- **Compensation of positive zero**
- **Stability of 3-stage opamp**


# Positive zero because feedforward

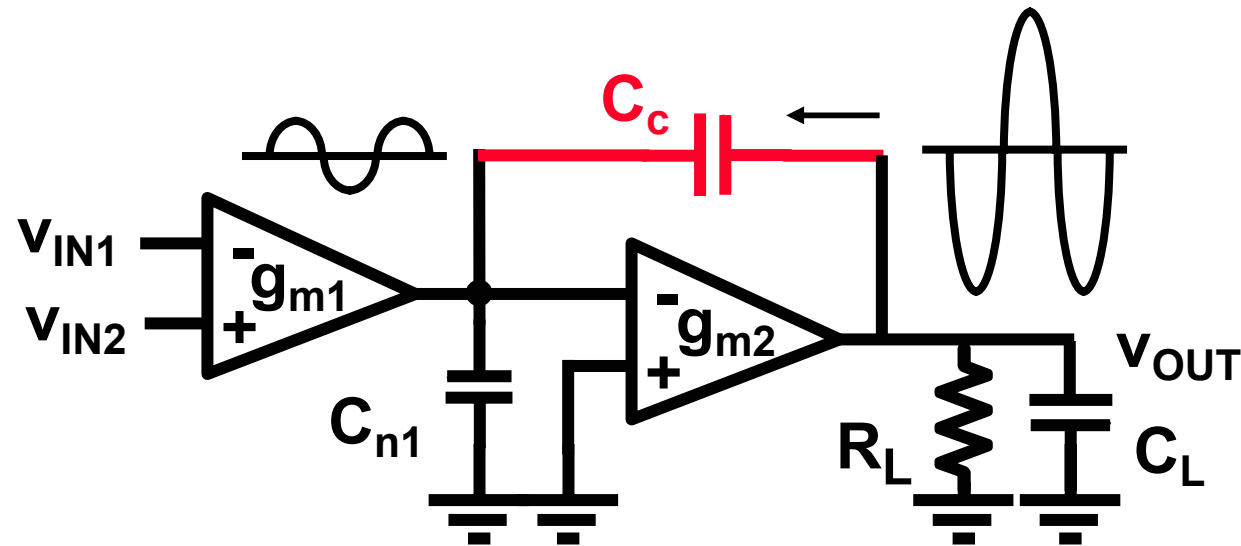

Miller effect  
Is feedback

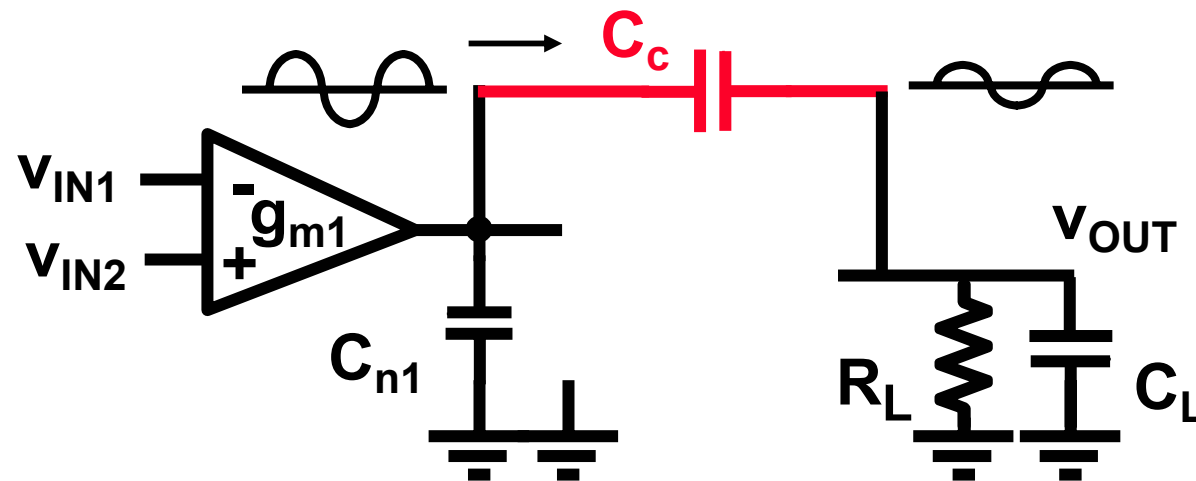

Feedforward

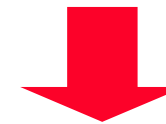


Cut !



---


# Cut feedforward through $C_c$ - 1

---

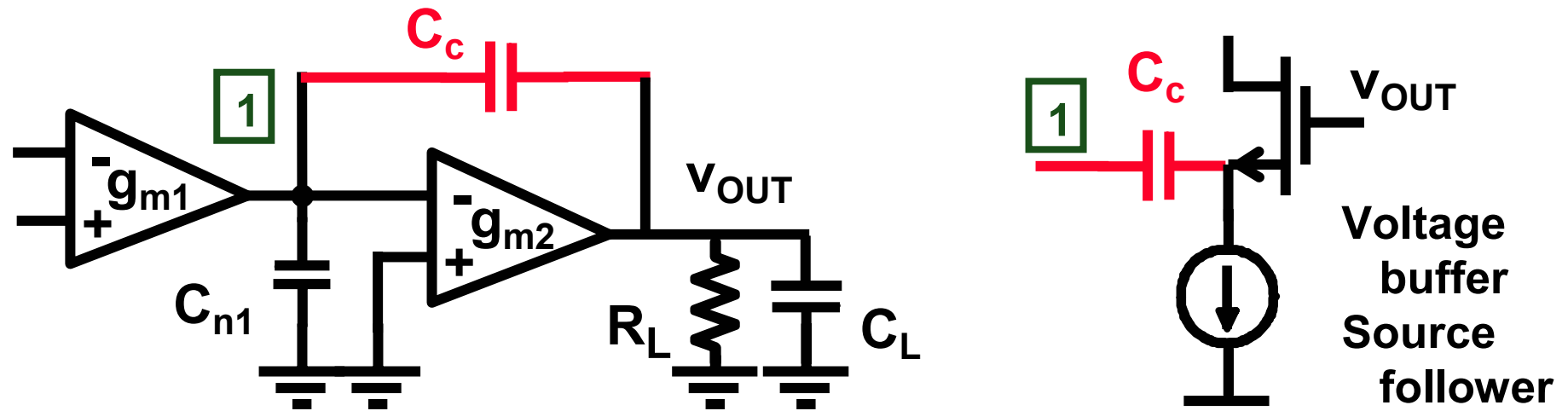



Ref. Tsividis, JSSC Dec.76, 748-753

## Cut feedforward through $C_c$ - 2

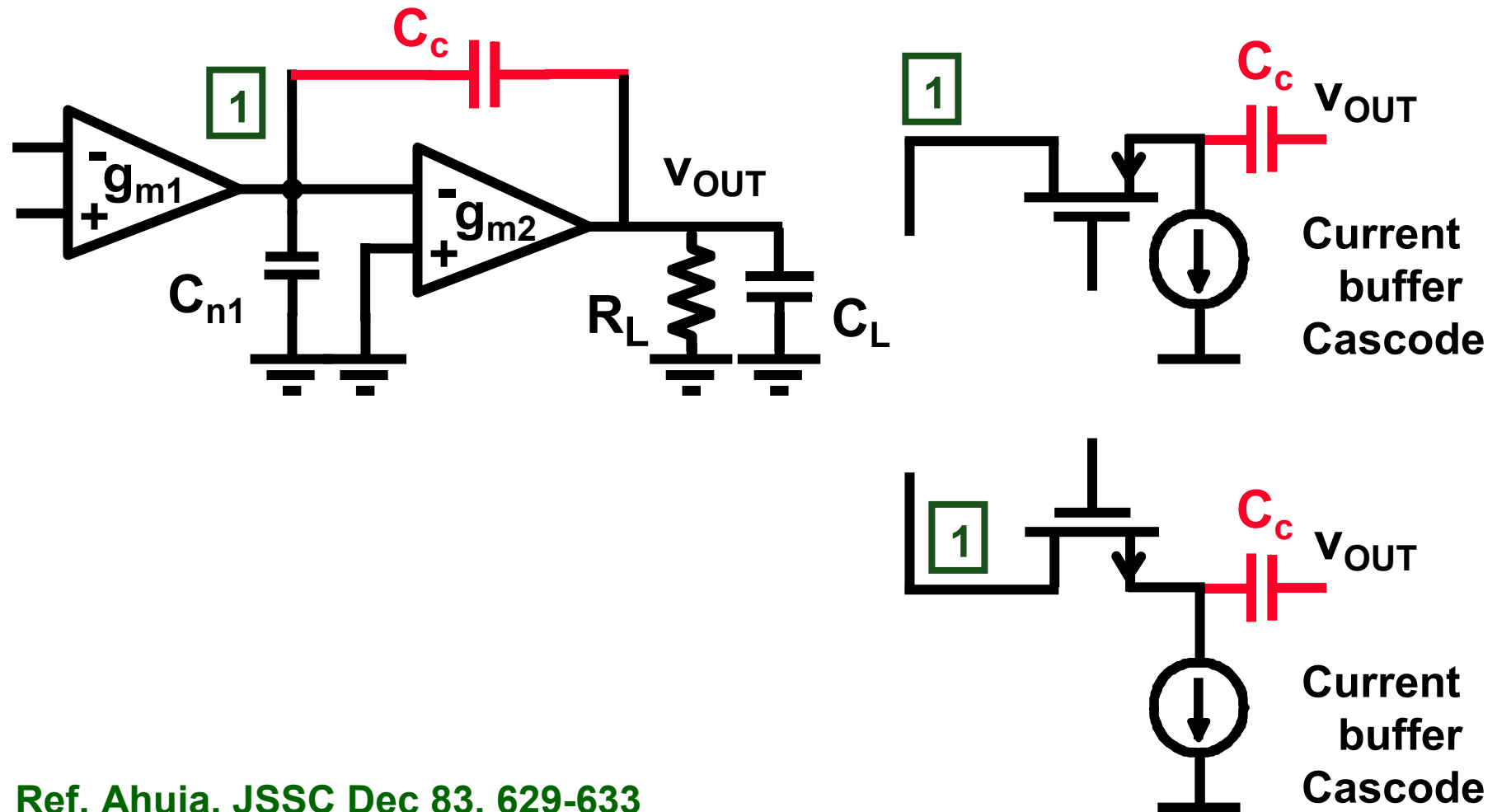


Ref. Ahuja, JSSC Dec 83, 629-633

# Compensation with cascodes

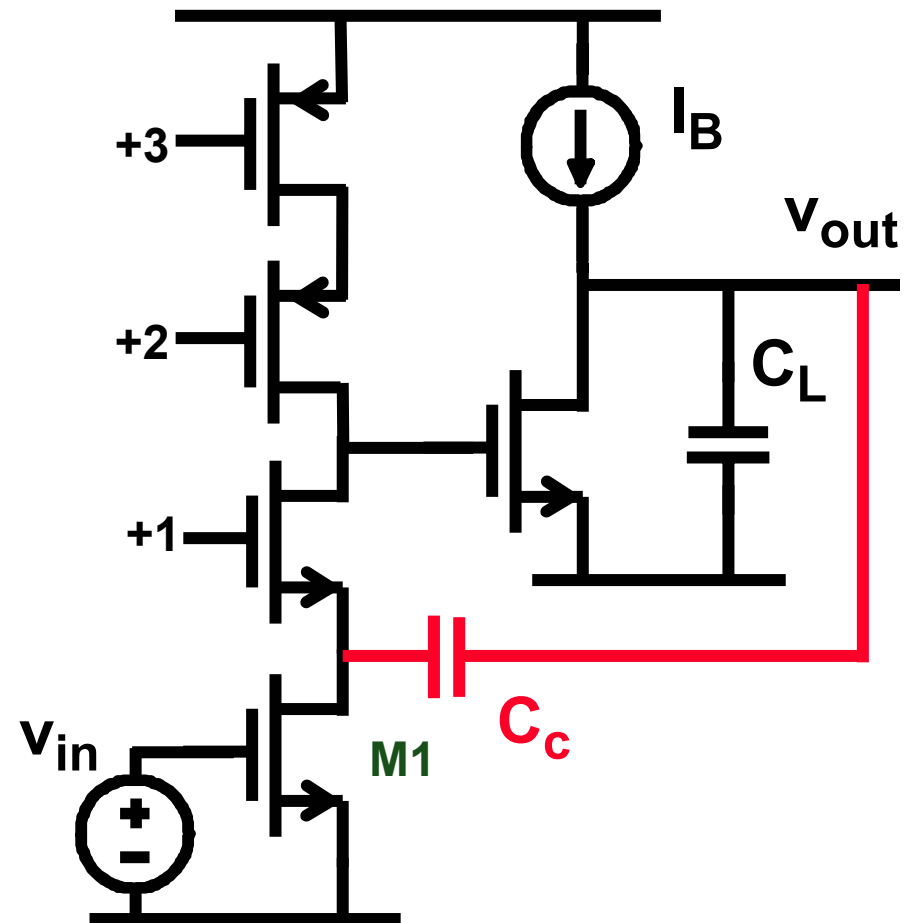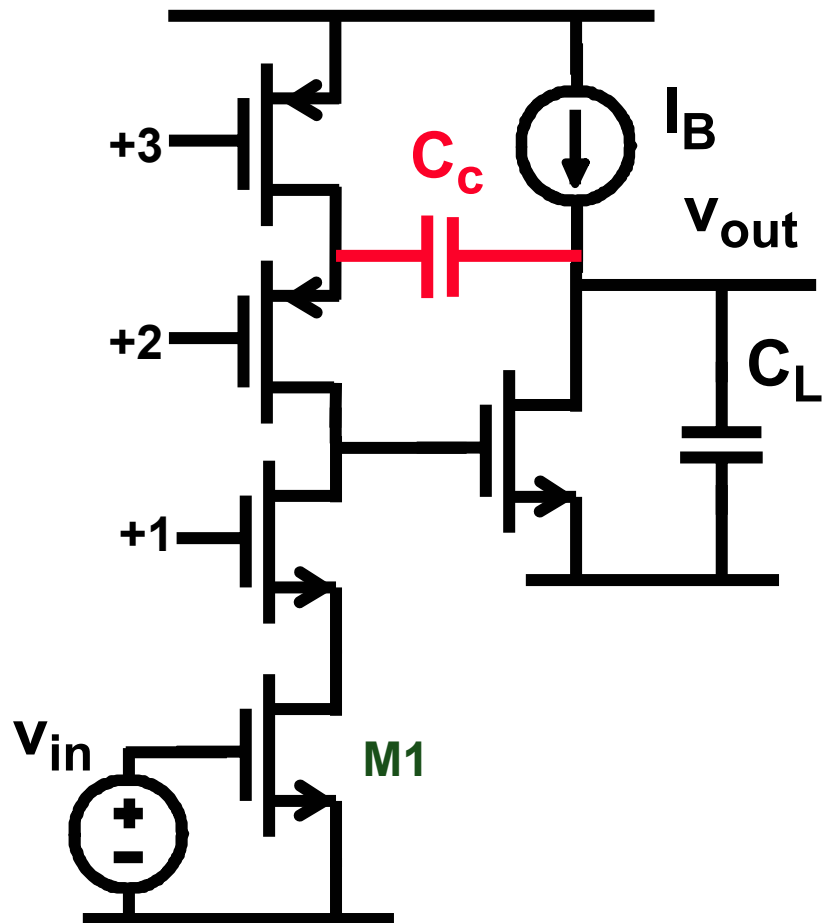

## Cut feedforward through $C_c$ - 3

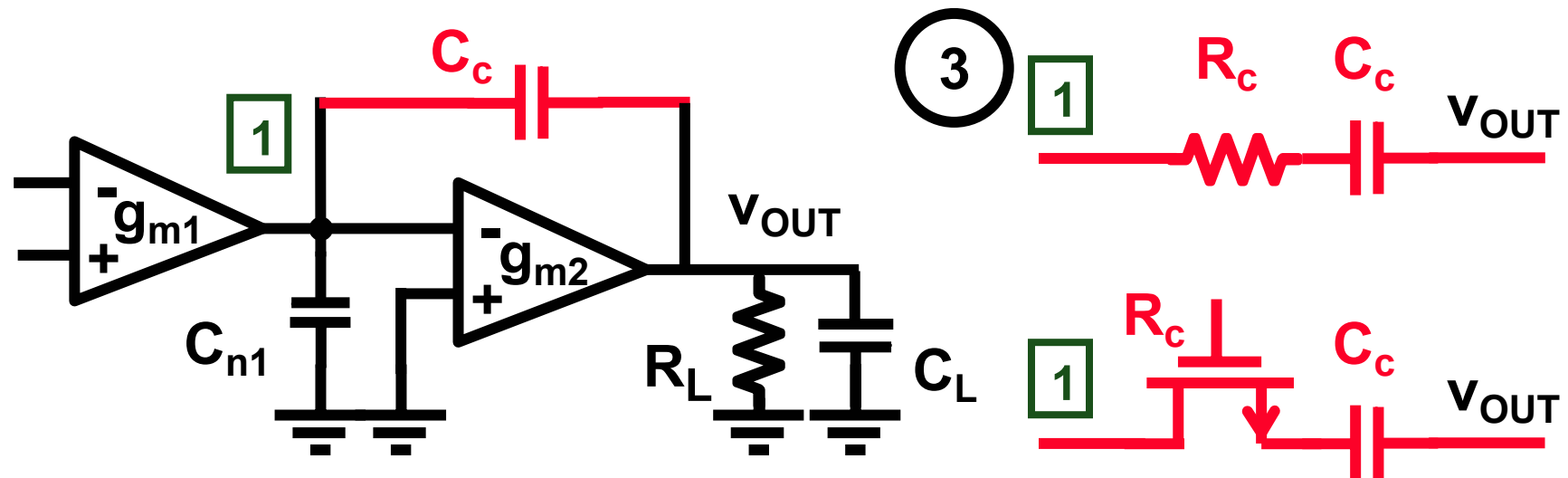

$$f_z = \frac{1}{2\pi C_c (1/g_{m2} - R_c)}$$

$R_c = 1/g_{m2}$  No zero

$R_c > 1/g_{m2}$  **Negative zero**

Ref. Senderovics, JSSC Dec 78, 760-766

---

## Negative zero compensation

---

$$R_c \gg 1/g_{m2} \quad \longrightarrow \quad f_z = - \frac{1}{2\pi C_c R_c}$$

$$f_z = 3 \text{ GBW} \quad \longrightarrow \quad R_c = \frac{1}{3 g_{m1}}$$

Final choice :

$$\frac{1}{g_{m2}} < R_c < \frac{1}{3g_{m1}}$$

---

## Exercise of 2-stage opamp

---

**GBW = 50 MHz for  $C_L = 2$  pF**

**Find  $I_{DS1}$ ;  $I_{DS2}$  ;  $C_c$  and  $R_c$  !**

**Choose  $C_c = 1$  pF  $> g_{m1} = 2\pi C_c \text{GBW} = 315 \mu\text{S}$**

$$I_{DS1} = 31.5 \mu\text{A} \quad \& \quad 1/g_{m1} \approx 3.2 \text{ k}\Omega$$

**$f_{nd} = 150$  MHz  $> g_{m2} = 2\pi C_L 4\text{GBW} = 8g_{m1} = 2520 \mu\text{S}$**

$$I_{DS2} = 252 \mu\text{A} \quad \& \quad 1/g_{m2} \approx 400 \Omega$$

$$400 \Omega < R_c < 1 \text{ k}\Omega : R_c = 1/\sqrt{2.5} \approx 400\sqrt{2.5} \approx 640 \Omega \pm 60\%$$



---

# Table of contents


---

- **Use of operational amplifiers**
- **Stability of 2-stage opamp**
- **Pole splitting**
- **Compensation of positive zero**
- **Stability of 3-stage opamp**

---

# 1-stage CMOS OTA

---

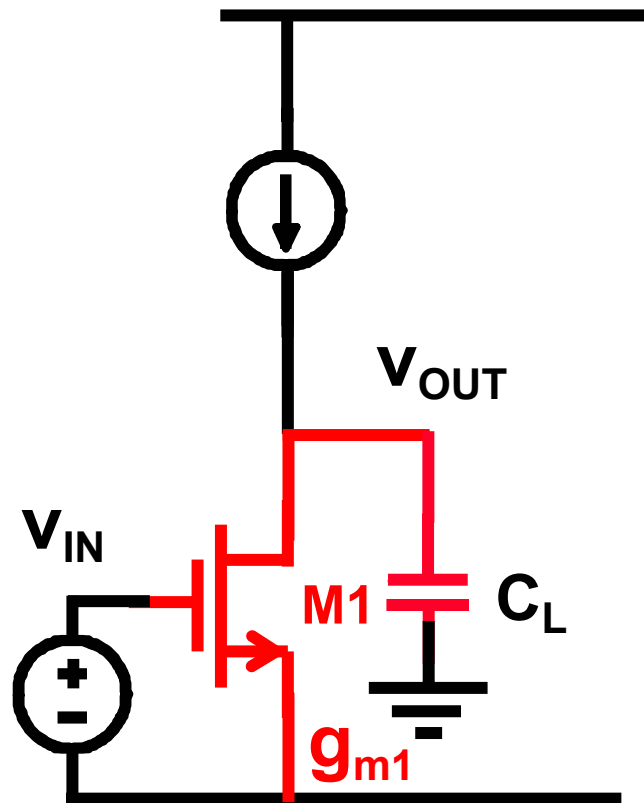


$$GBW = \frac{g_{m1}}{2\pi C_L}$$

---

## 2-stage Miller CMOS OTA

---

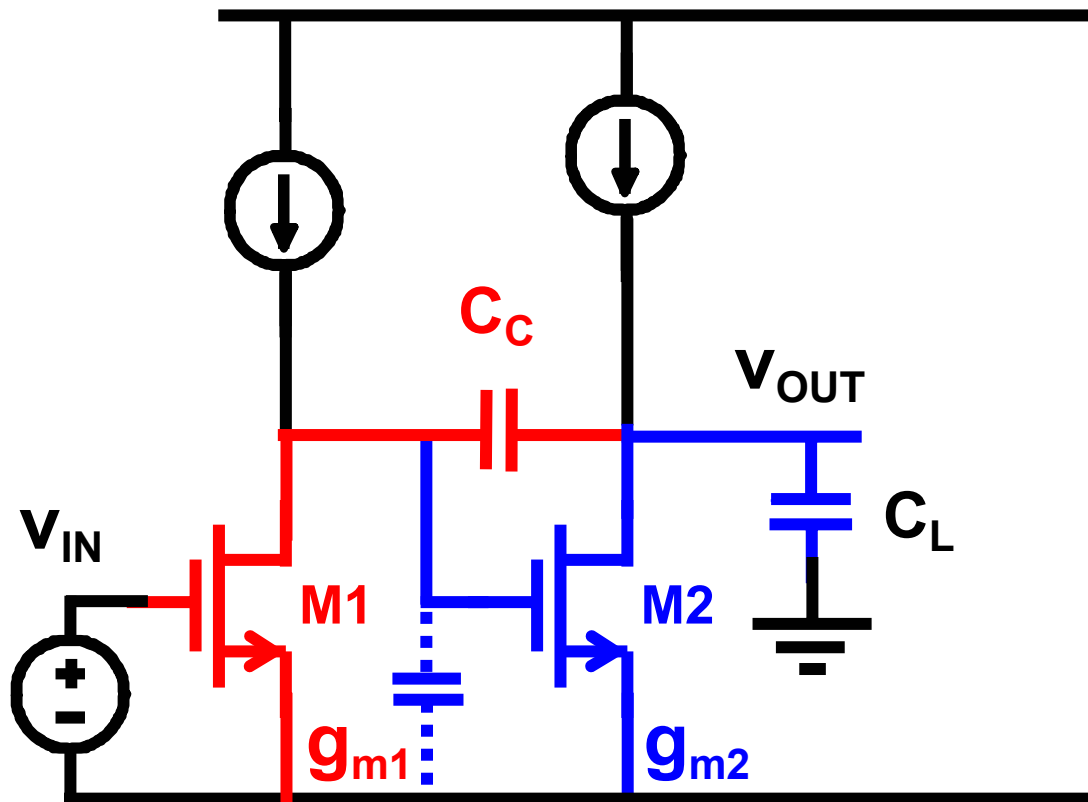

$$GBW = \frac{g_{m1}}{2\pi C_C}$$


$$f_{nd1} = \frac{g_{m2}}{2\pi C_L}$$

$$f_{nd1} = 3 \text{ GBW}$$

---

## 3-stage Nested Miller CMOS OTA

---

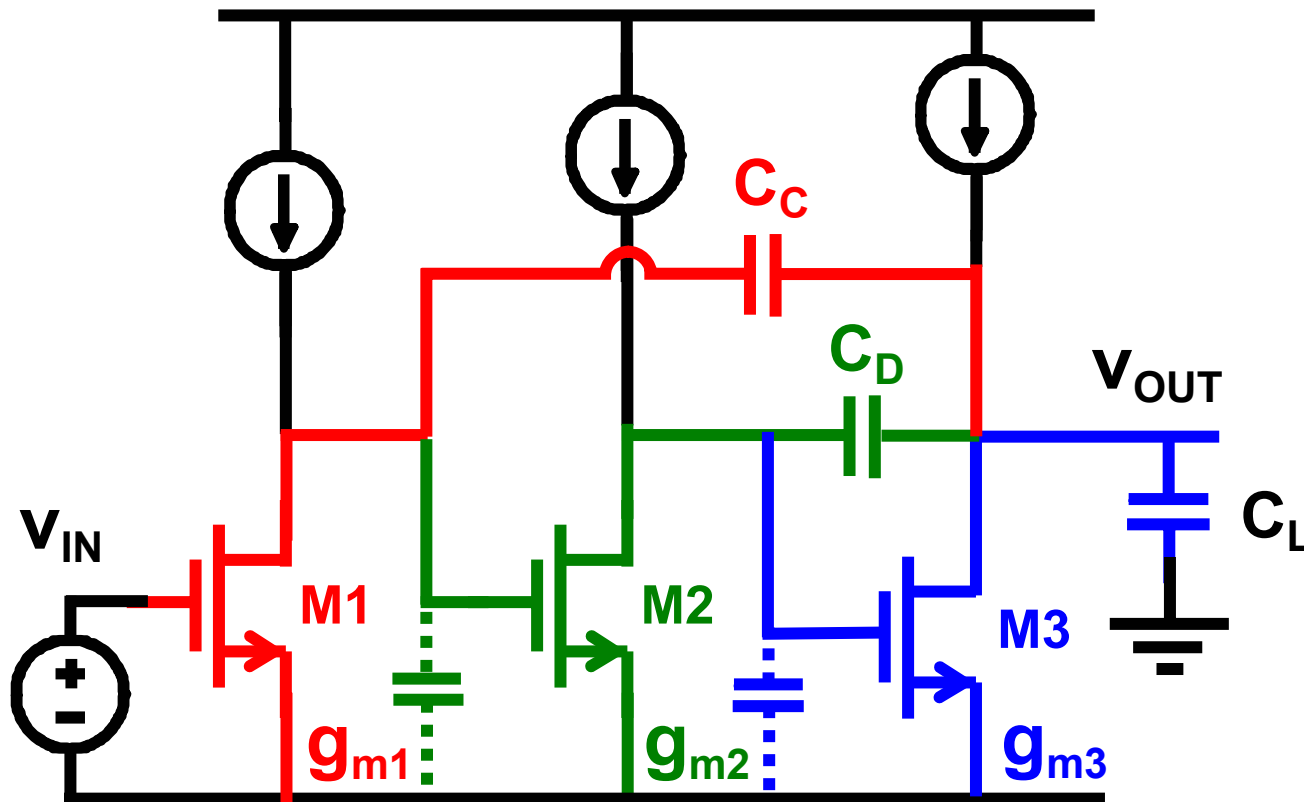

$$GBW = \frac{g_{m1}}{2\pi C_C}$$


$$f_{nd1} = \frac{g_{m2}}{2\pi C_D}$$

$$f_{nd2} = \frac{g_{m3}}{2\pi C_L}$$

$$f_{nd1} = 3 \text{ GBW}$$


$$f_{nd2} = 5 \text{ GBW}$$

# Nested Miller with differential pair

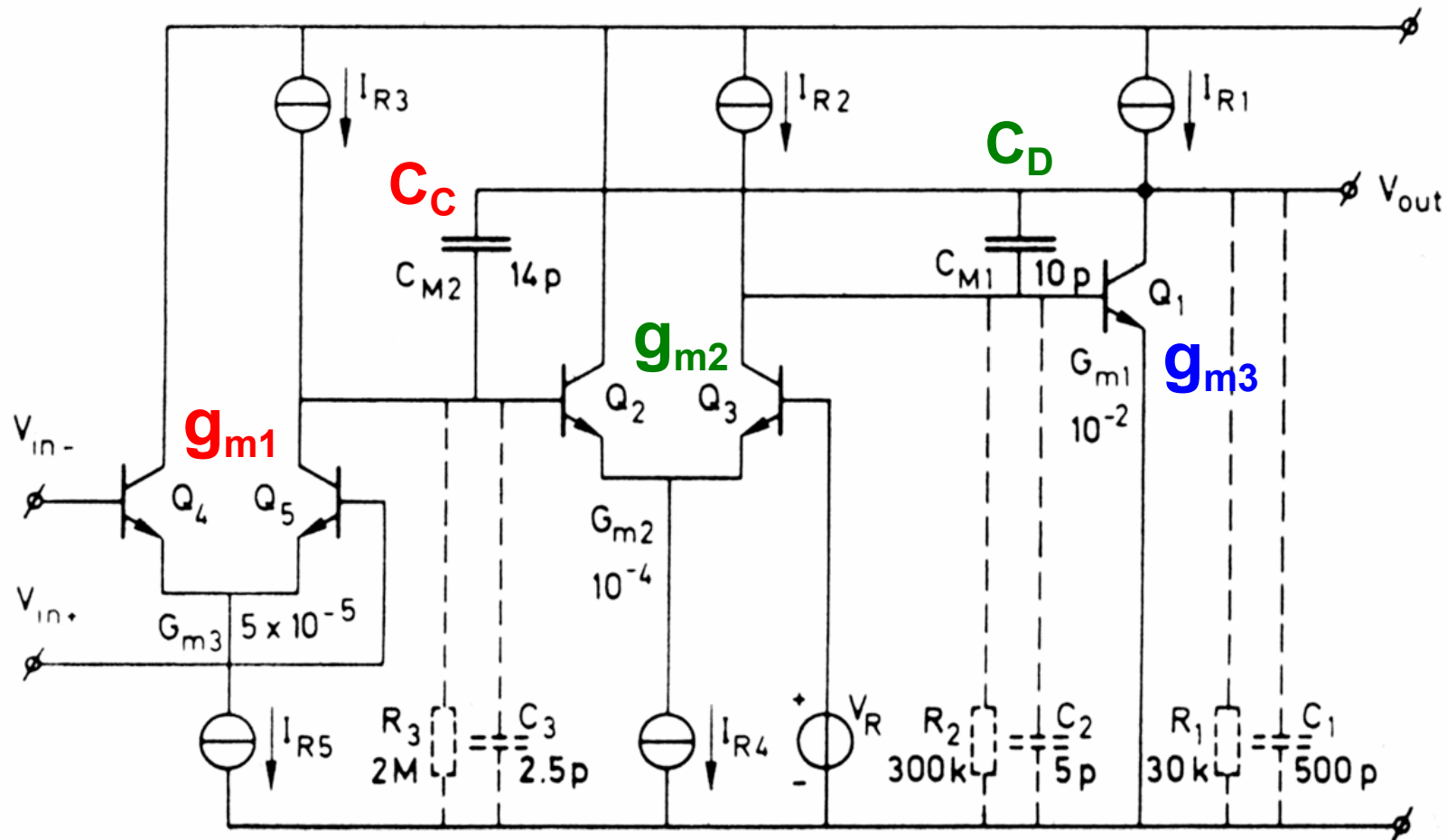


Huijsing, JSSC Dec.85, pp.1144-1150

# Relation between the $f_{nd}$ 's

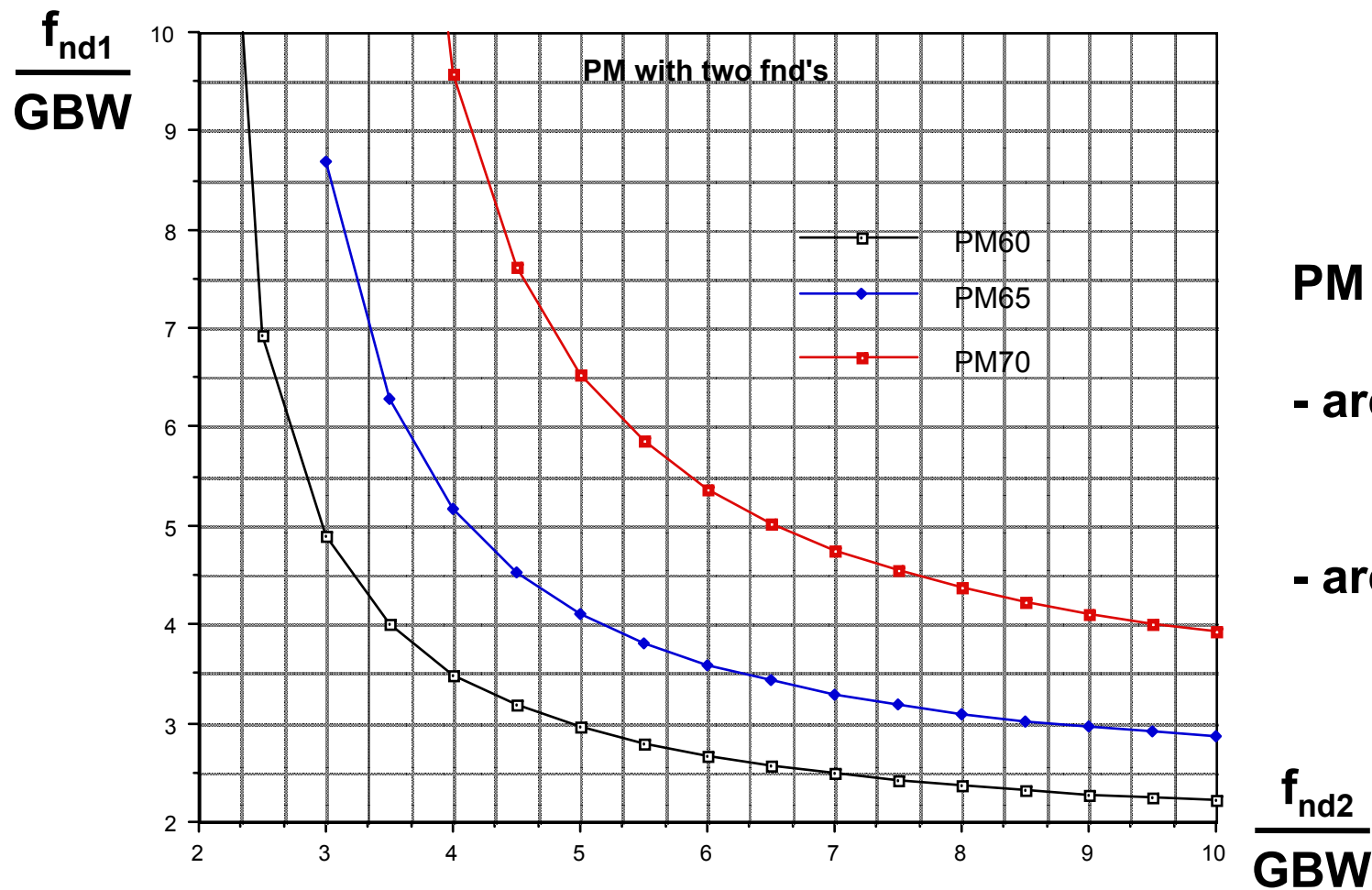

# Relation $f_{nd}$ 's and power

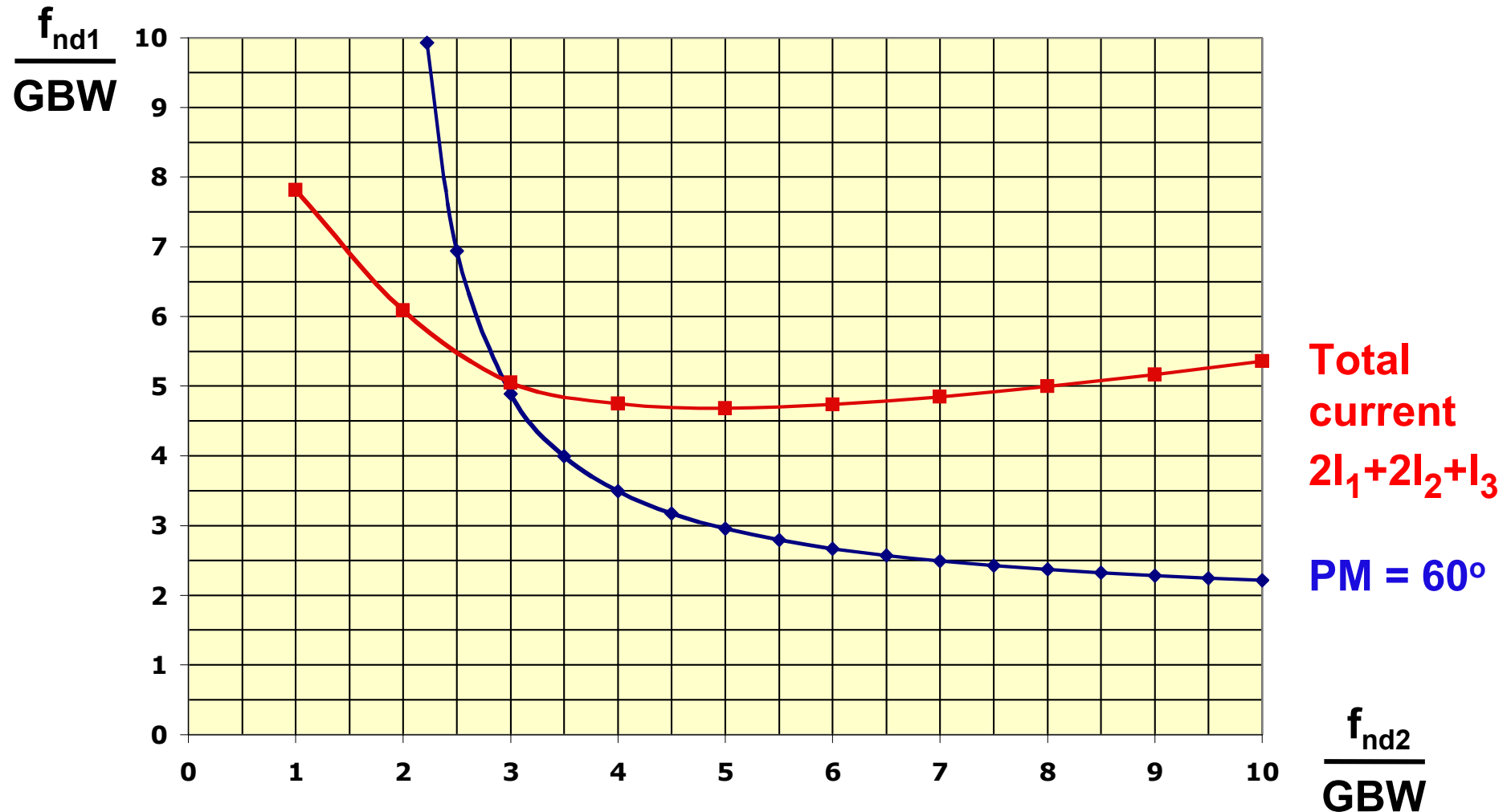

---

## Elementary design of 3-stage opamp

---

$$\text{GBW} = \frac{g_{m1}}{2\pi C_C}$$

$$f_{nd1} = 3 \text{ GBW} = \frac{g_{m2}}{2\pi C_D}$$

**Choose  $C_D \approx C_C$  !**

$$f_{nd2} = 5 \text{ GBW} = \frac{g_{m3}}{2\pi C_L}$$

$$\frac{g_{m2}}{g_{m1}} \approx 3 \quad \frac{g_{m3}}{g_{m1}} \approx 5 \frac{C_L}{C_C}$$

**Even larger current in output stage !**



---

## Exercise of 3-stage opamp

---

**GBW = 50 MHz for  $C_L = 2$  pF**

**Find  $I_{DS1}$ ;  $I_{DS2}$ ;  $I_{DS3}$ ;  $C_C$  and  $C_D$  !**

**Choose  $C_C = C_D = 1$  pF  $\Rightarrow g_{m1} = 2\pi C_C \text{GBW} = 315 \mu\text{S}$**

$$I_{DS1} = 31 \mu\text{A}$$

**$f_{nd1} = 150$  MHz  $\Rightarrow g_{m2} = 2\pi C_D 3\text{GBW} = 3g_{m1} = 945 \mu\text{S}$**

$$I_{DS2} = 95 \mu\text{A}$$

**$f_{nd2} = 250$  MHz  $\Rightarrow g_{m3} = 2\pi C_L 5\text{GBW} = 10g_{m1} = 3150 \mu\text{S}$**

$$I_{DS3} = 315 \mu\text{A}$$

---

## Comparison 1, 2 & 3 stage designs

---

**GBW = 50 MHz for  $C_L = 2$  pF**

**Single stage :**  $I_{DS1} = 31 \mu A$   $I_{TOT} = 2I_{DS1} = \mathbf{62 \mu A}$

**Two stages :** Choose  $C_C = 1$  pF

$I_{DS1} = 31 \mu A$   $I_{DS2} = 252 \mu A$   $I_{TOT} = 2I_{DS1} + I_{DS2} = \mathbf{314 \mu A}$

**Three stages :** Choose  $C_C = C_D = 1$  pF

$I_{DS1} = 31 \mu A$   $I_{DS2} = 95 \mu A$   $I_{DS3} = 315 \mu A$

$I_{TOT} = 2I_{DS1} + 2I_{DS2} + I_{DS3} = \mathbf{567 \mu A}$

---

# Table of contents

---

- **Use of operational amplifiers**
- **Stability of 2-stage opamp**
- **Pole splitting**
- **Compensation of positive zero**
- **Stability of 3-stage opamp**