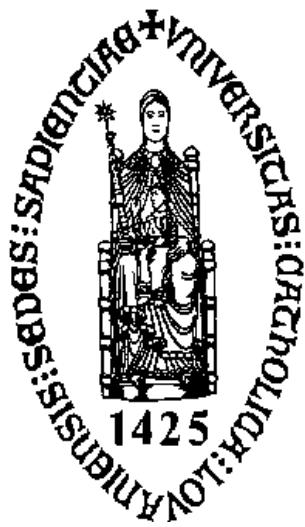

Design of Multistage Operational amplifiers



Willy Sansen

**KULeuven, ESAT-MICAS
Leuven, Belgium**

willy.sansen@esat.kuleuven.be



Table of contents

- Design procedure
- Nested-Miller designs
- Low-power designs
- Comparison

Ref.: W. Sansen : Analog Design Essentials, Springer 2006


Why three-stage amplifiers ?

- 1. Each MOST only gives $g_m r_o \approx 15$ or 24 dB :
High gain requires three stages !**

- 2. For drivers (small R_L) : $g_m R_L$ is very low :
High gain requires three stages !**

- 3. For low V_{DD} , no cascoding but cascading !
High gain requires three stages !**


No cascoding but cascading !

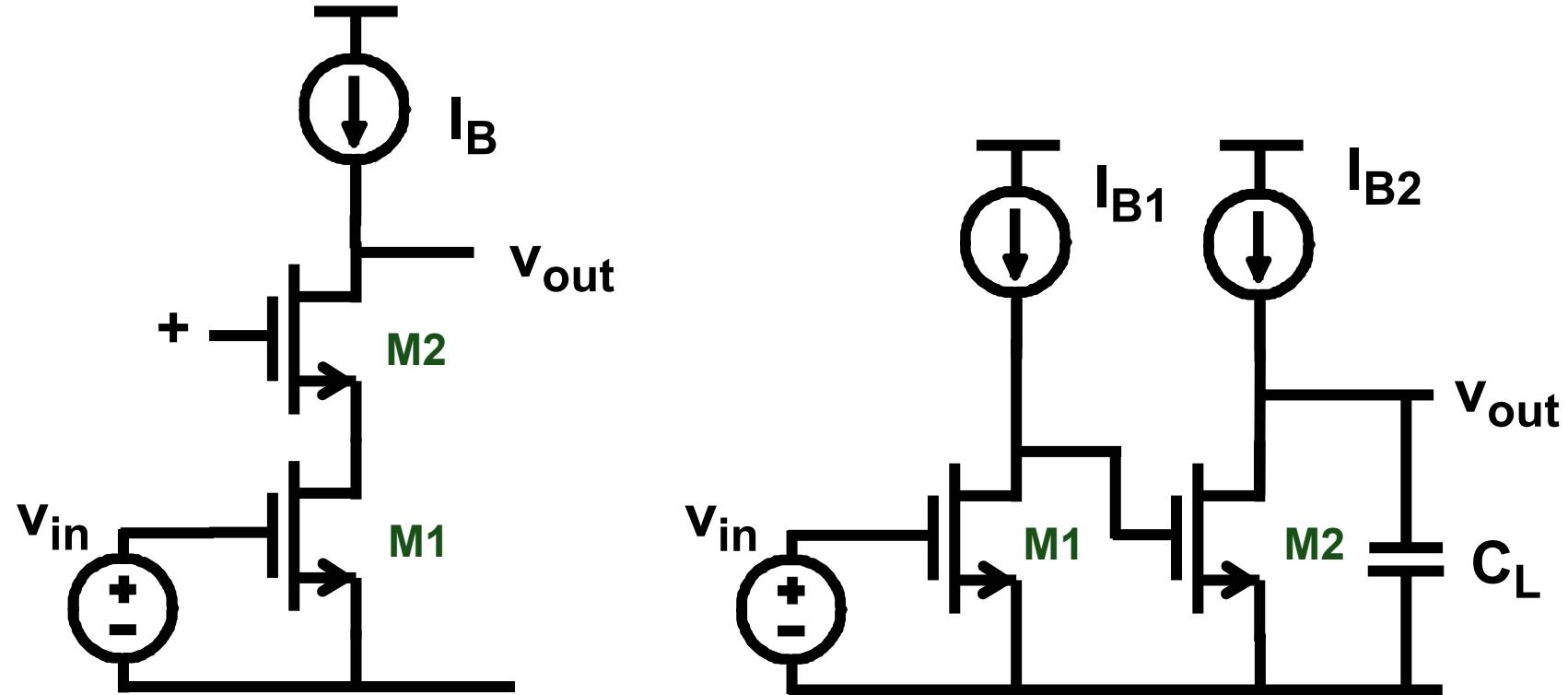

$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2$$

$$A_v = (g_m r_{DS})_1 (g_m r_{DS})_2$$


Cascode versus cascade

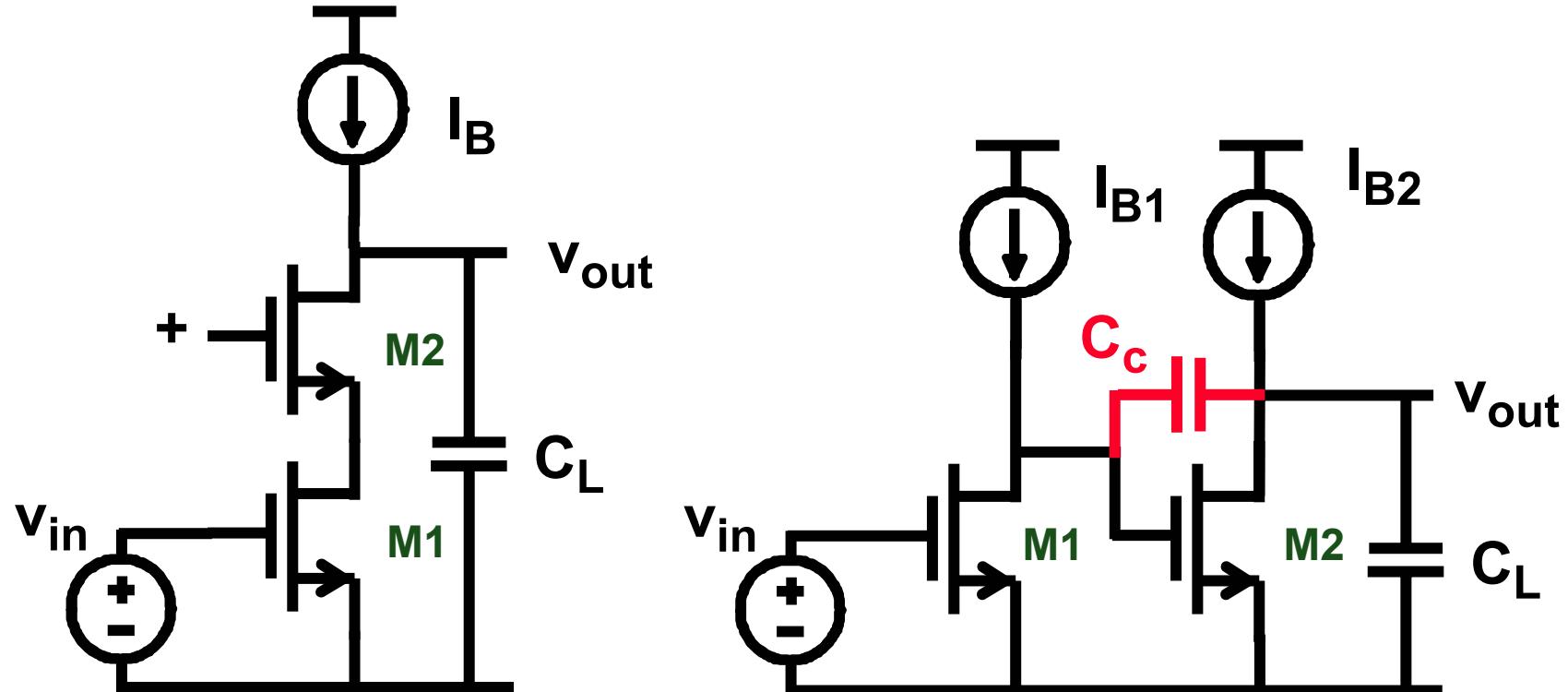

$$\text{GBW} = \frac{g_{m1}}{2\pi C_L}$$


$$\text{GBW} = \frac{g_{m1}}{2\pi C_c} < \frac{g_{m2}}{2\pi C_L}$$

1-stage CMOS OTA

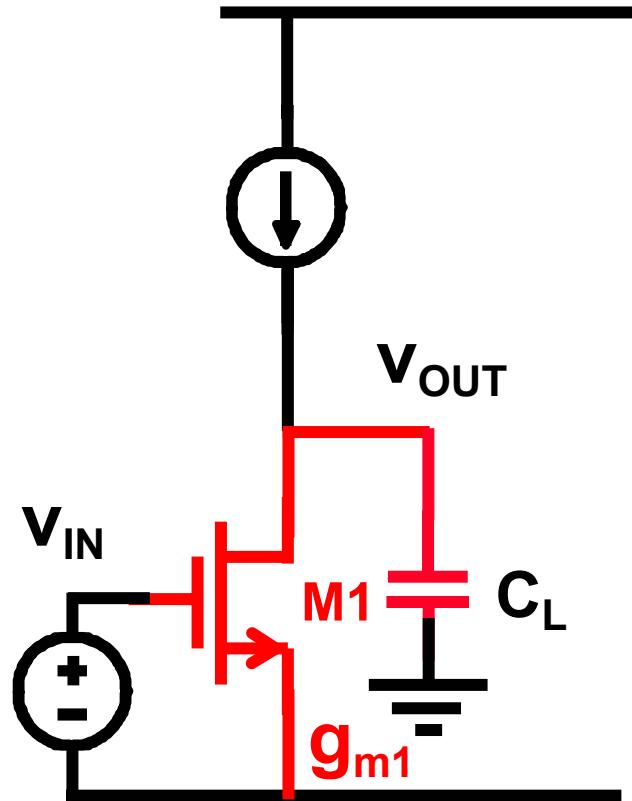

$$\text{GBW} = \frac{g_{m1}}{2\pi C_L}$$

2-stage Miller CMOS OTA

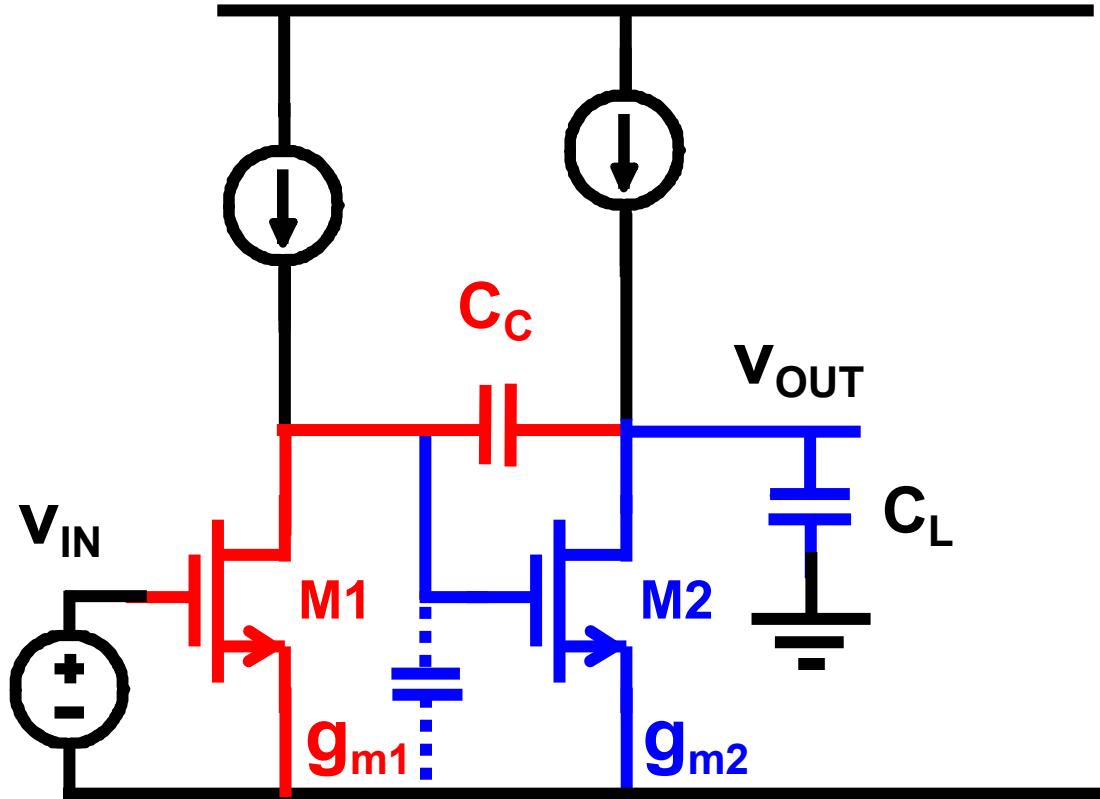


$$\text{GBW} = \frac{g_{m1}}{2\pi C_C}$$

$$f_{nd1} = \frac{g_{m2}}{2\pi C_L}$$

$$f_{nd1} = 3 \text{ GBW}$$

3-stage Nested Miller CMOS OTA

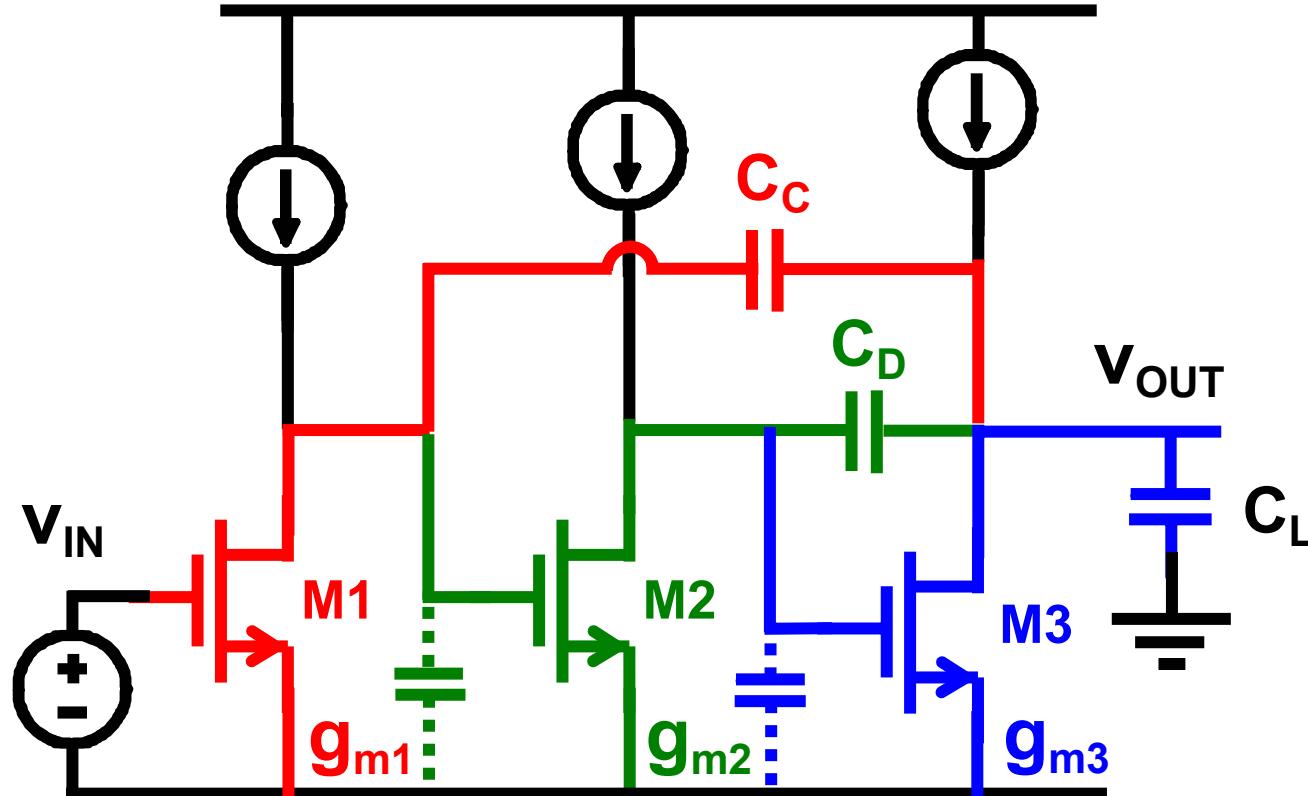

$$\text{GBW} = \frac{g_{m1}}{2\pi C_C}$$


$$f_{nd1} = \frac{g_{m2}}{2\pi C_D}$$

$$f_{nd2} = \frac{g_{m3}}{2\pi C_L}$$

$$f_{nd1} = 3 \text{ GBW}$$

$$f_{nd2} = 5 \text{ GBW}$$

3-pole opamp : phase margin PM

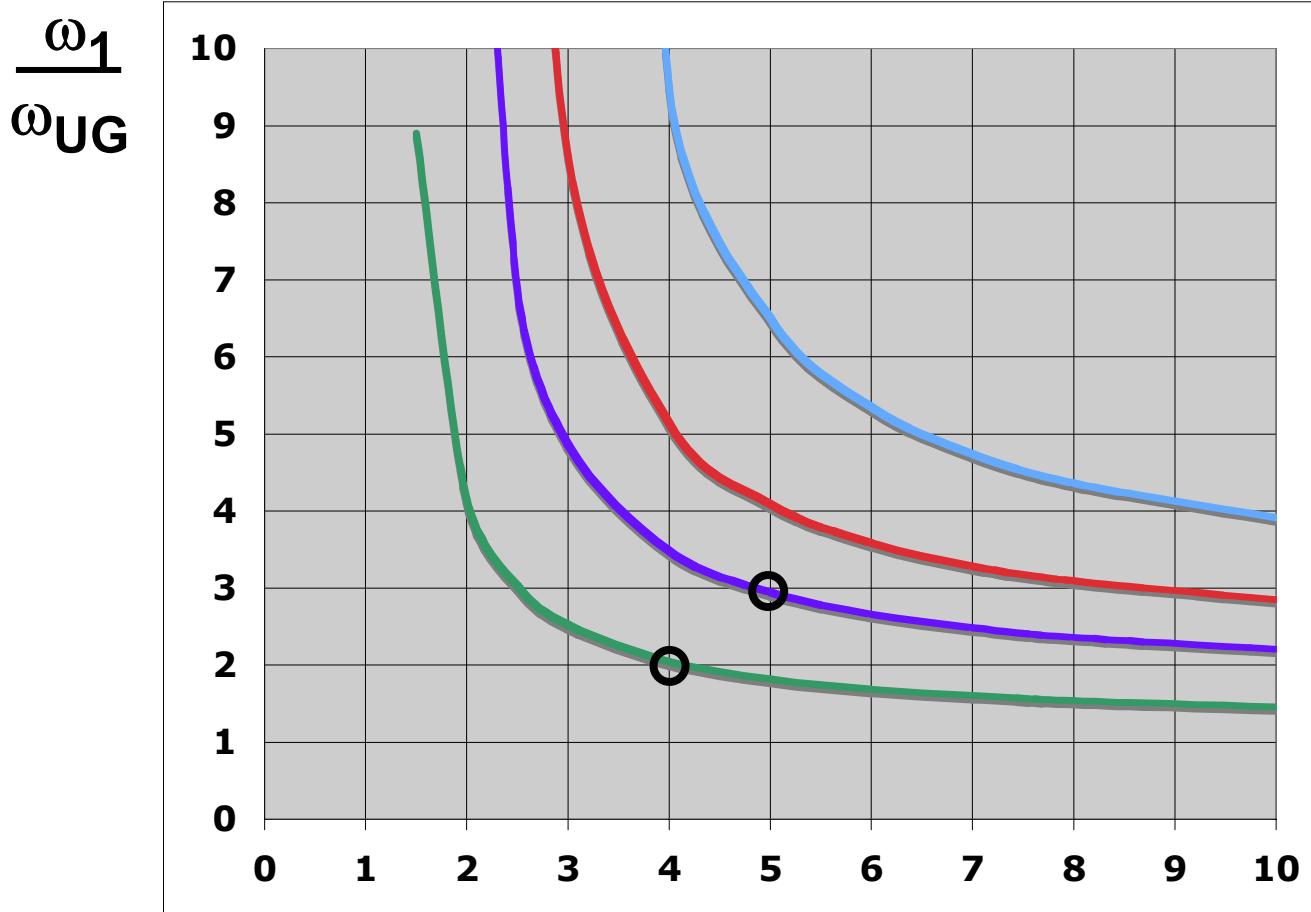


$\text{PM} \approx$
 $90^\circ - \arctan\left(\frac{\omega_{UG}}{\omega_1}\right)$
 $- \arctan\left(\frac{\omega_{UG}}{\omega_2}\right)$

70°
 65°
 60°
 50° PM

$\frac{\omega_2}{\omega_{UG}}$

Three-pole opamp

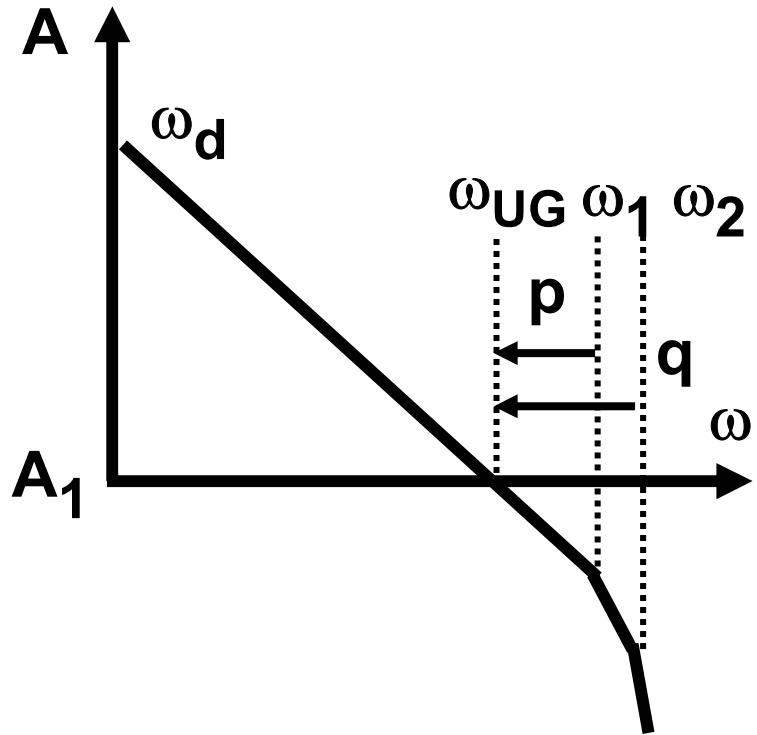

$$p = \omega_1 / \omega_{UG}$$
$$q = \omega_2 / \omega_{UG}$$

Open loop gain

$$A = \frac{\omega_{UG}}{s} \frac{1}{\left(1 + \frac{s}{\omega_1}\right) \left(1 + \frac{s}{\omega_2}\right)}$$

Closed loop gain (Unity gain)

$$A_1 = \frac{A}{1+A} \approx$$

$$\frac{1}{1 + \frac{s}{\omega_{UG}} + \left(\frac{1}{p} + \frac{1}{q}\right) \left(\frac{s}{\omega_{UG}}\right)^2 + \frac{1}{pq} \left(\frac{s}{\omega_{UG}}\right)^3}$$

3-pole opamp: $\omega_1 = 3 \omega_{UG}$ $\omega_2 = 5 \omega_{UG}$


Open loop

Three poles:

$$\omega_d$$

$$\omega_1 \ 3x$$

$$\omega_2 \ 5x$$

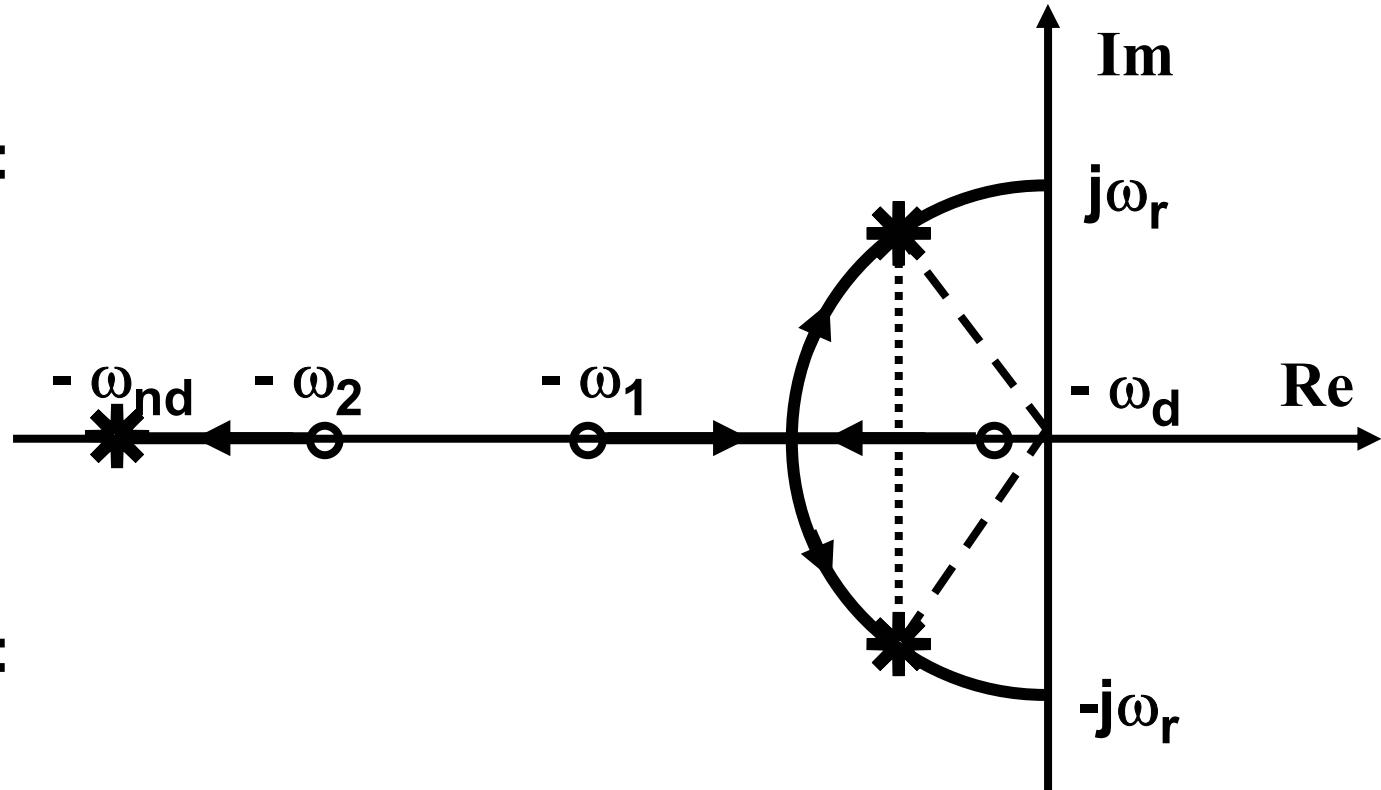

Unity gain


Three poles:

$$\omega_d$$


$$\omega_{nd} \ 6x$$

$$\begin{aligned}\omega_r \quad &1 \pm j1.2 \ x \\ &1.6 \ 50^\circ\end{aligned}$$

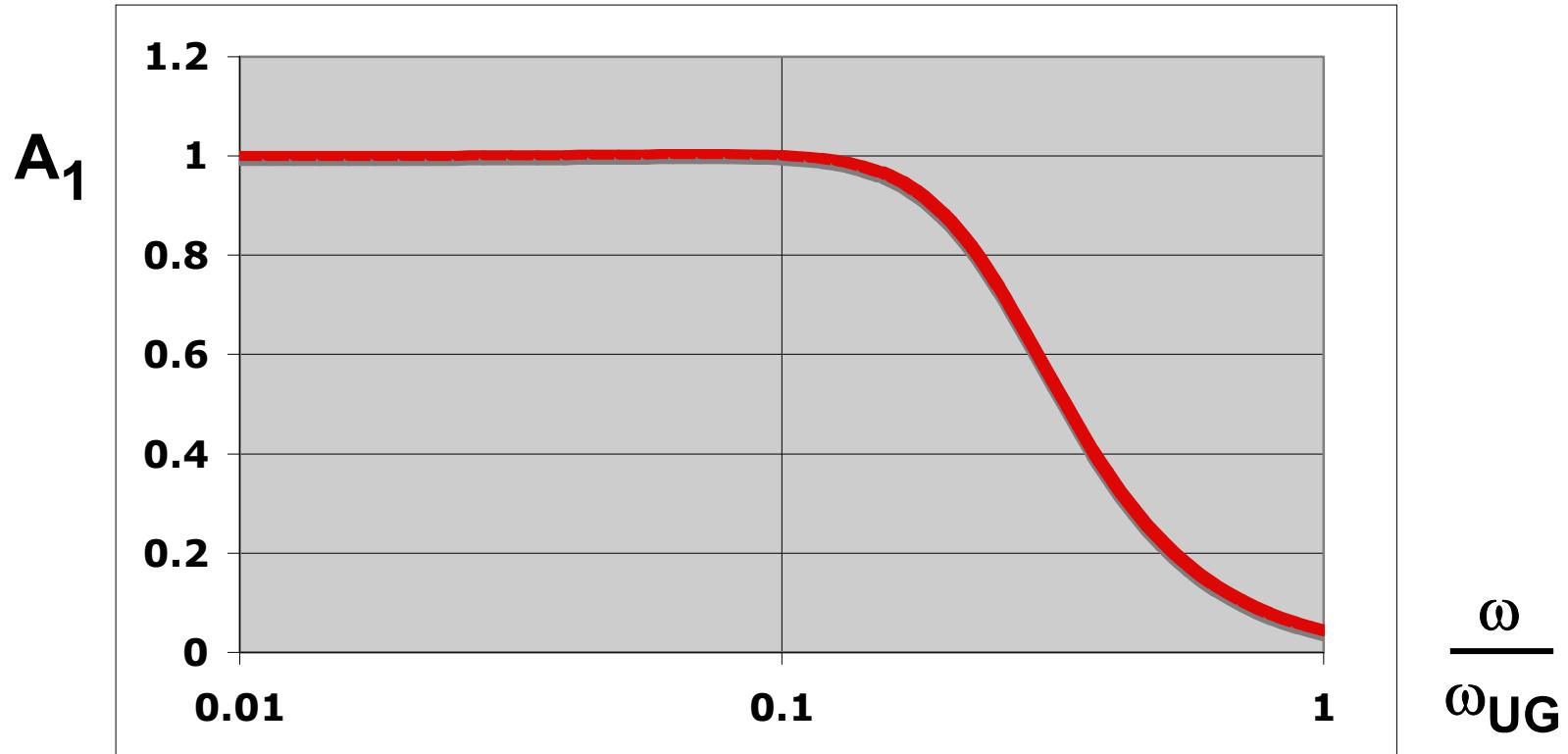
Three-stage with 3/5 on 60° PM with unity gain



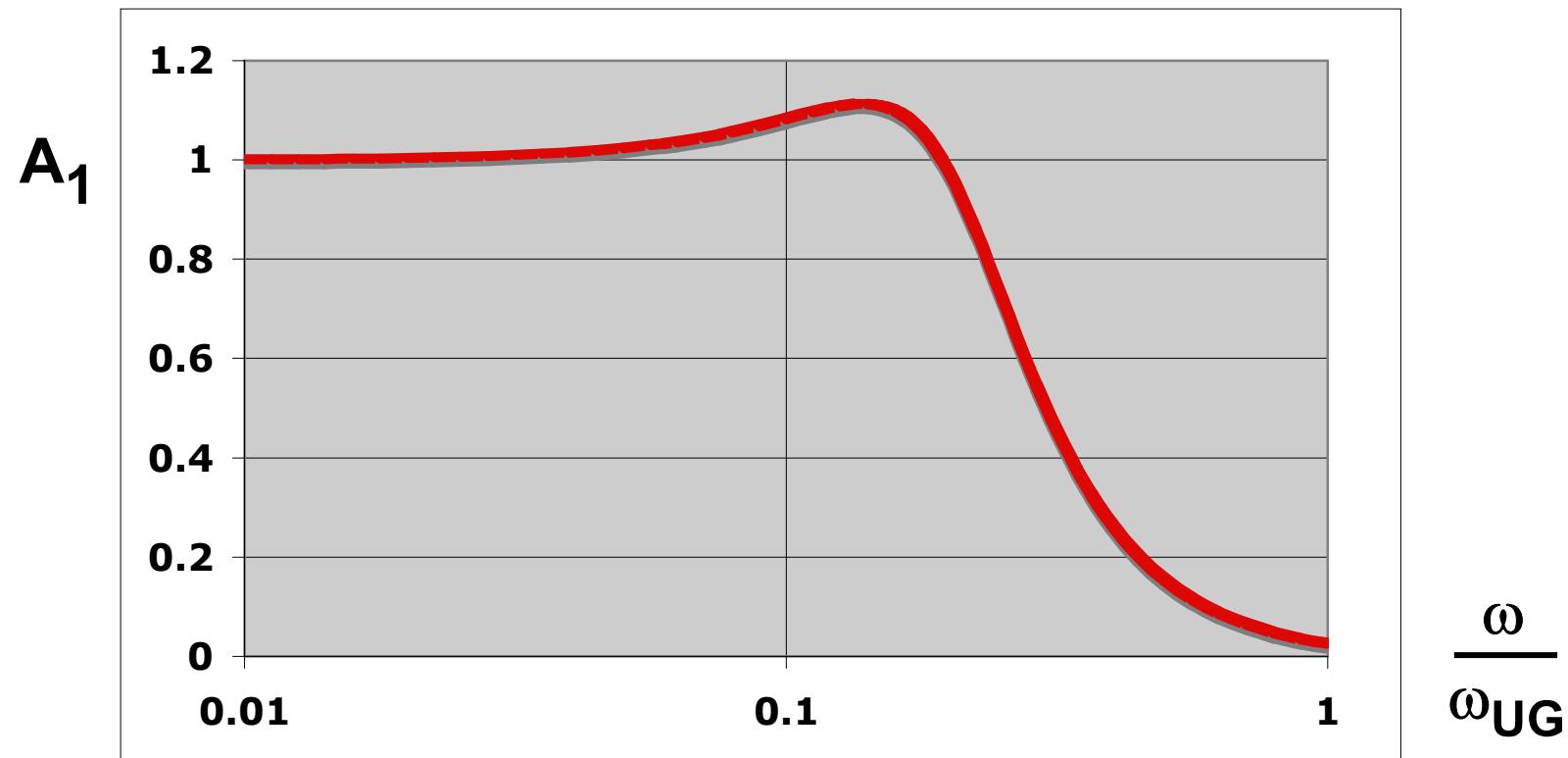Three-stage with 2/4 on 50° PM with unity gain



Three-pole opamp with complex poles

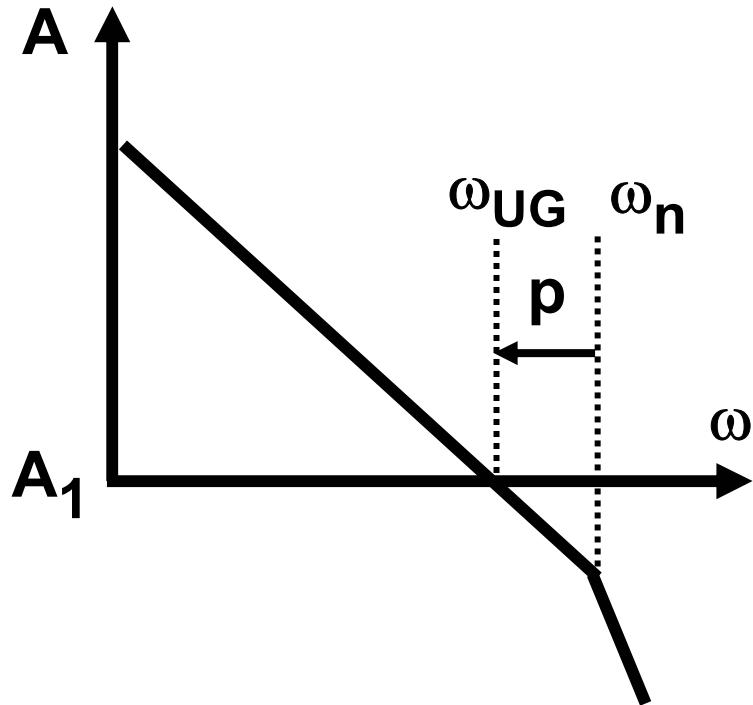

Two parameters:

ζ damping ($=1/2Q$)

$p = \omega_n / \omega_{UG}$

Open loop gain


$$A = \frac{\omega_{UG}}{s} \frac{1}{1 + 2\zeta \frac{s}{\omega_n} + \left(\frac{s}{\omega_n}\right)^2}$$

Closed loop gain (Unity gain)


$$A_1 = \frac{A}{1+A} \approx$$

$$\frac{1}{1 + \frac{s}{\omega_{UG}} + \frac{2\zeta}{p} \left(\frac{s}{\omega_{UG}}\right)^2 + \frac{1}{p^2} \left(\frac{s}{\omega_{UG}}\right)^3}$$

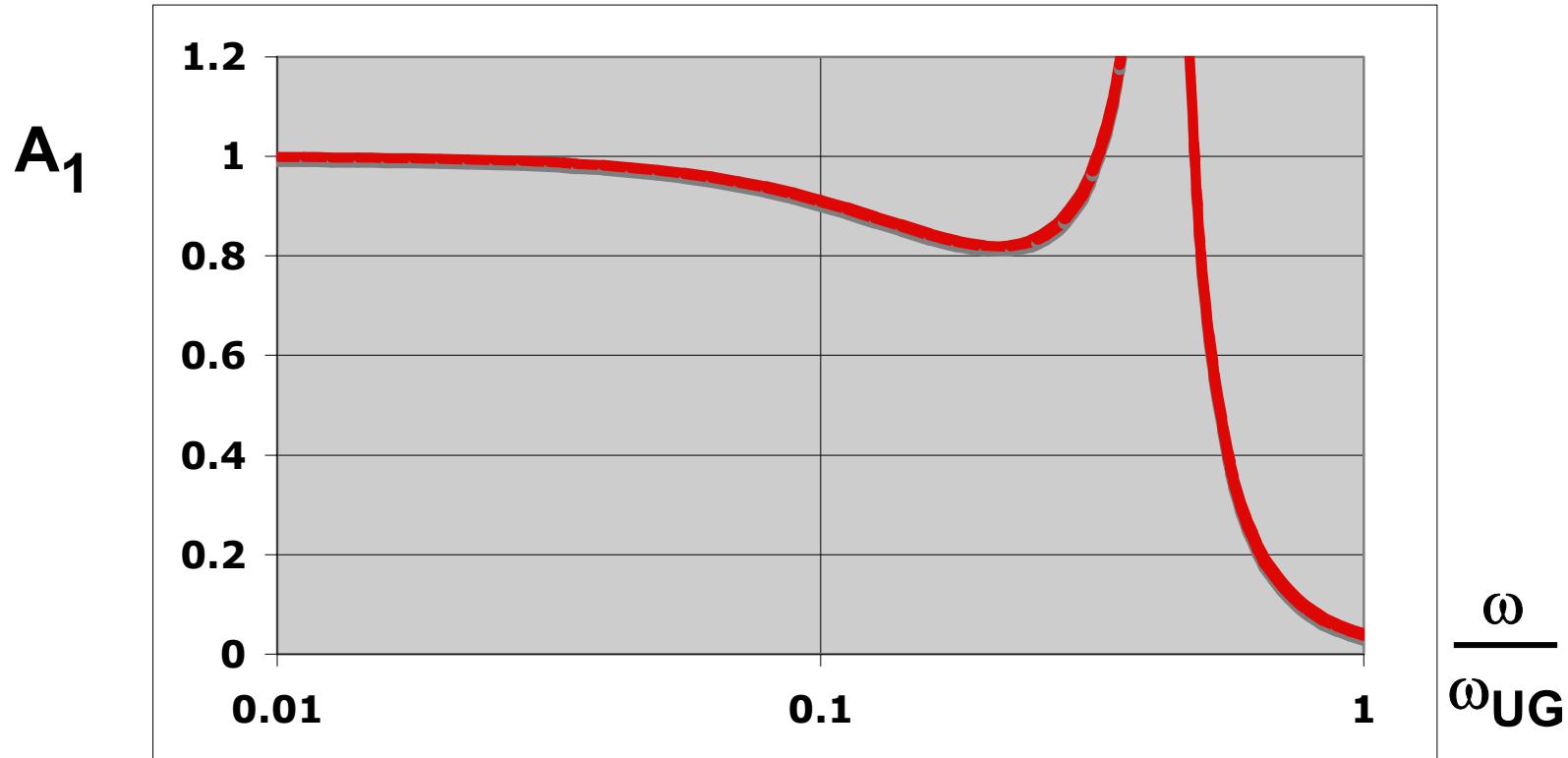
Unity-gain 3-pole opamp: $\zeta = 0.28$ $p = 2.828$



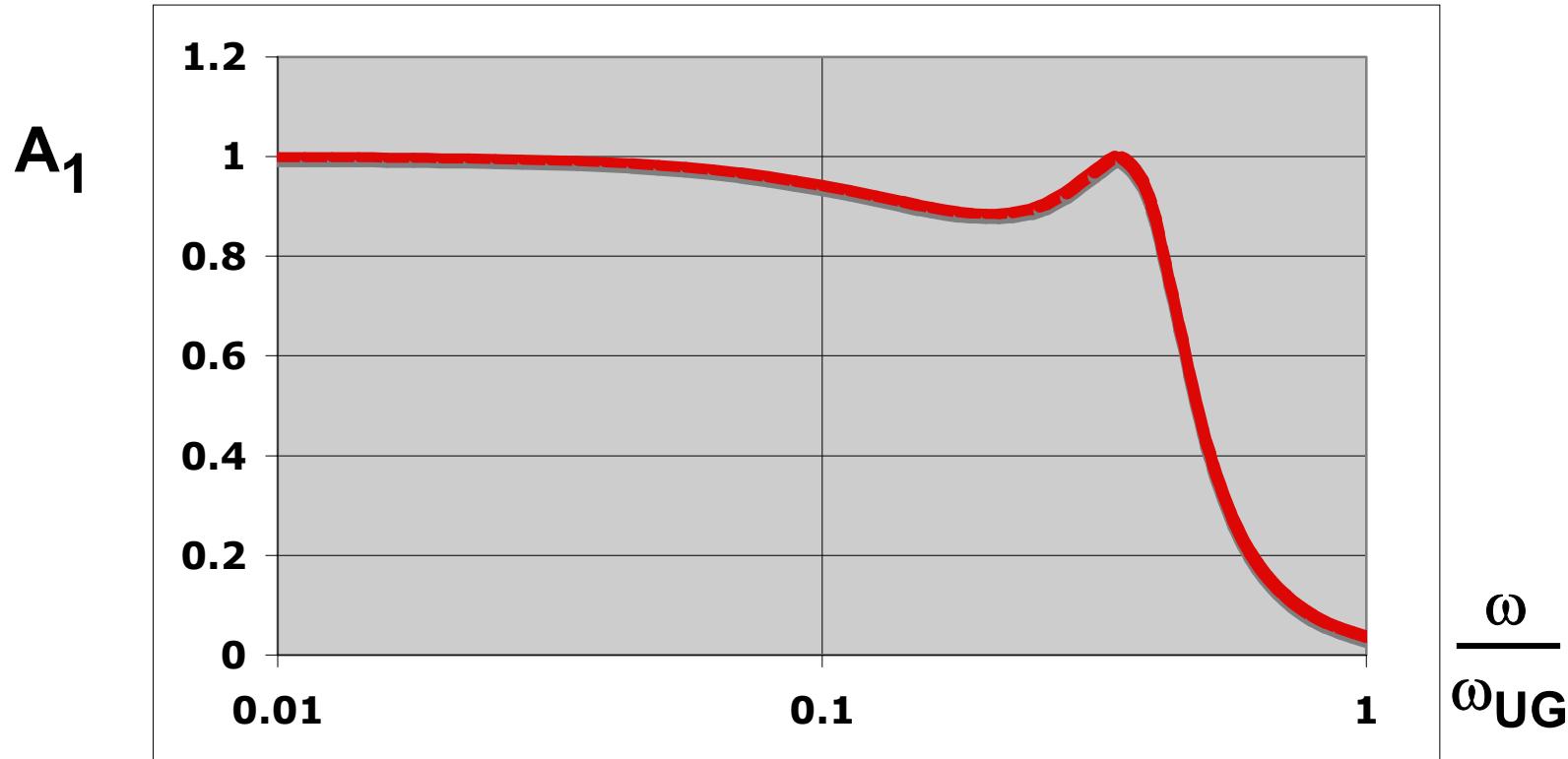Unity-gain 3-pole opamp: $\zeta = 0.44$ $p = 2.828$



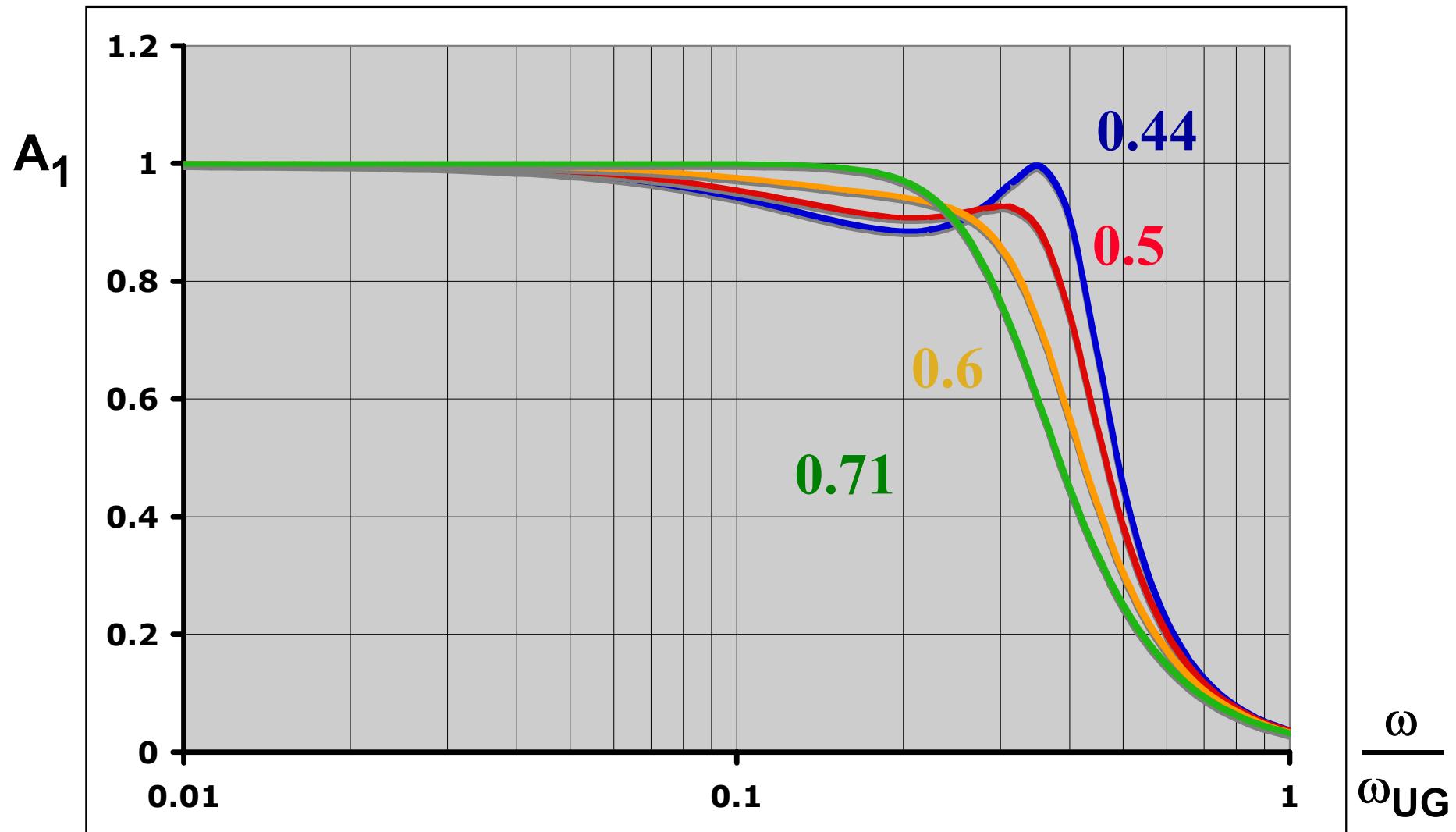
Unity-gain 3-pole opamp : $\zeta = \dots$ $p = 2.828$



Unity-gain 3-pole opamp: $\zeta = 0.71$ $p = 2.828$

Closed loop

Butterworth response :
maximally flat

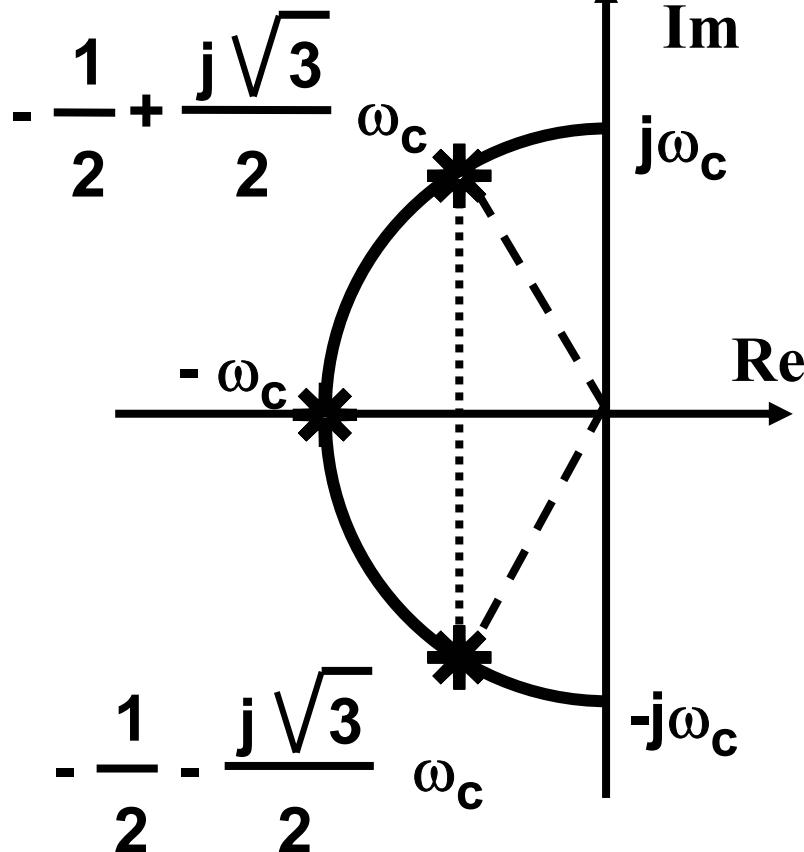



Poles :

$$\omega_{-3dB} = \frac{\omega_c}{2}$$


Table of contents

- Design procedure
- Nested-Miller designs
- Low-power designs
- Comparison

Three-stage configuration

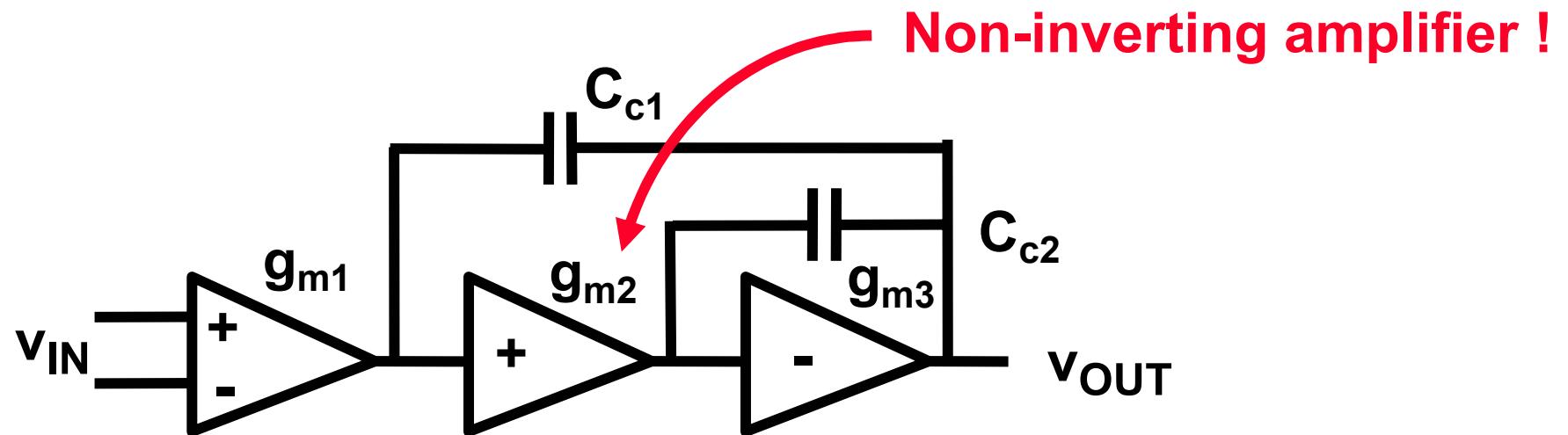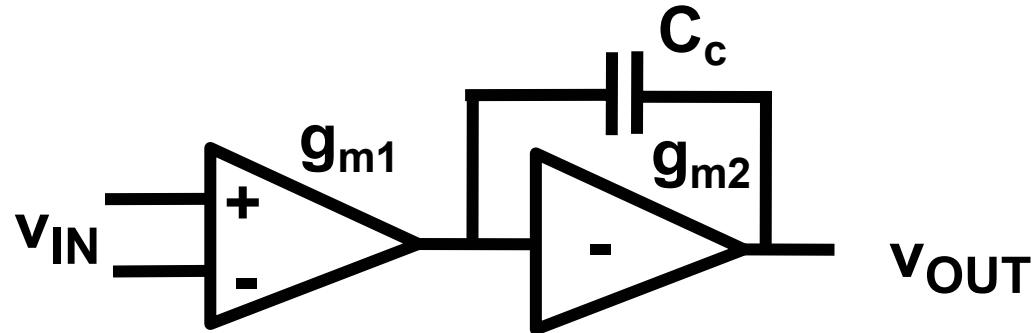

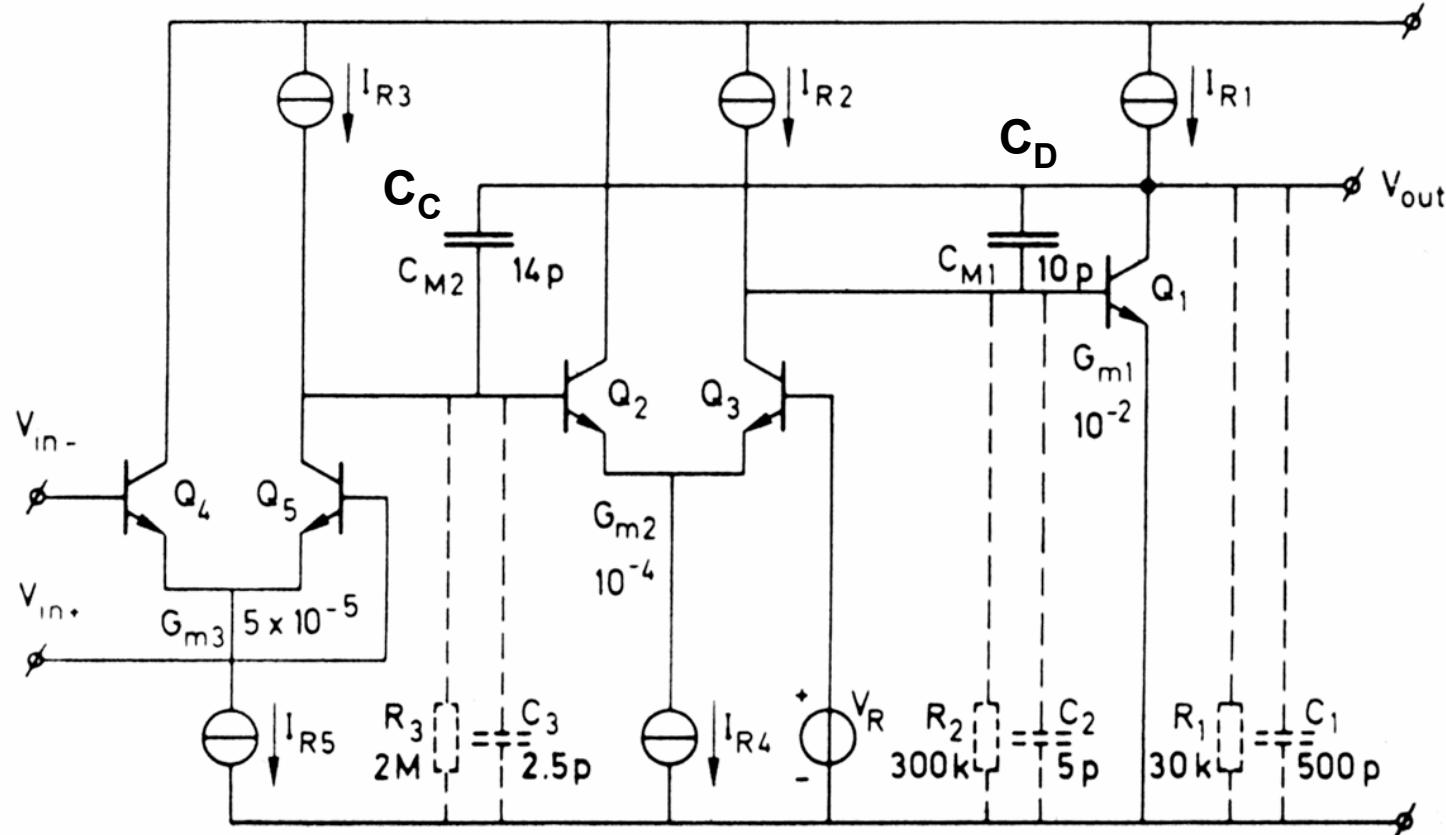
Nested Miller with differential pair as 2nd stage




$$\text{GBW} = \frac{g_{m4}}{2\pi C_C}$$

Huijsing, JSSC Dec.85, pp.1144-1150

Two ways to non-inverting gain

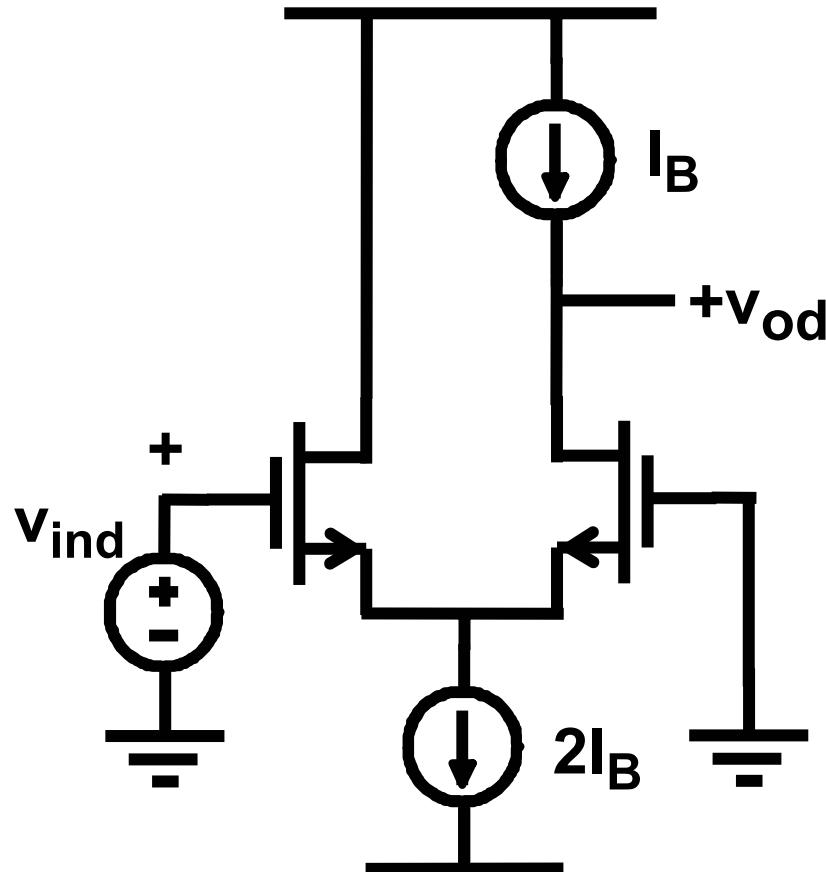


Differential pair

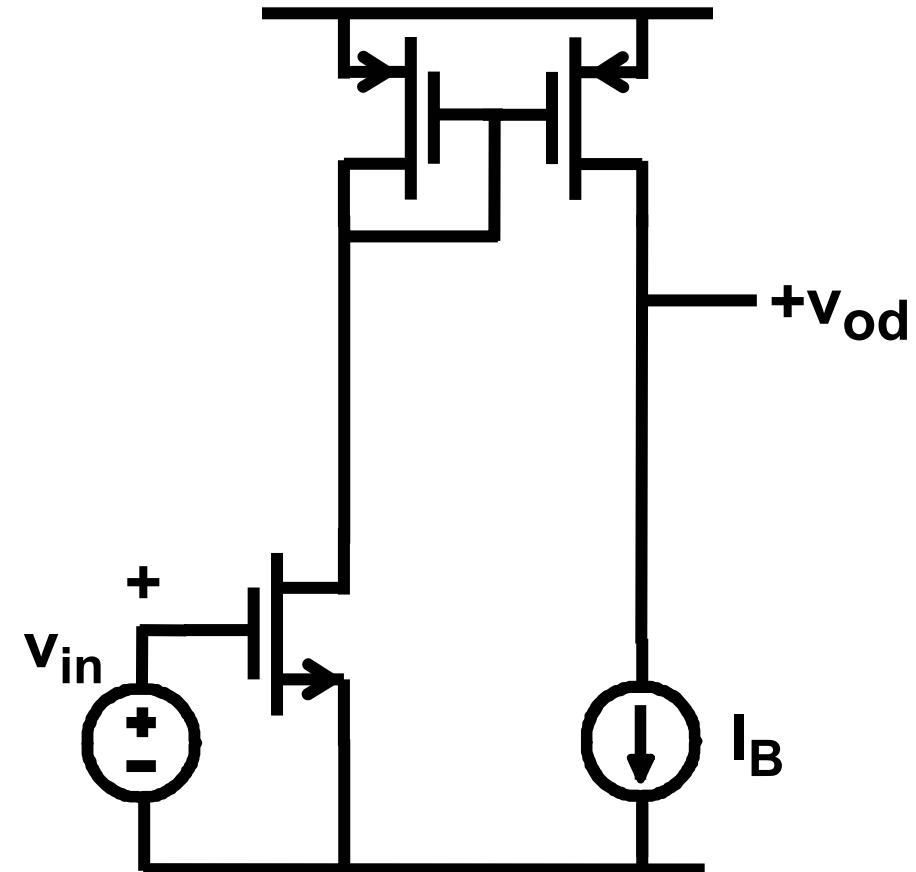


Current mirror

Two types of current mirroring

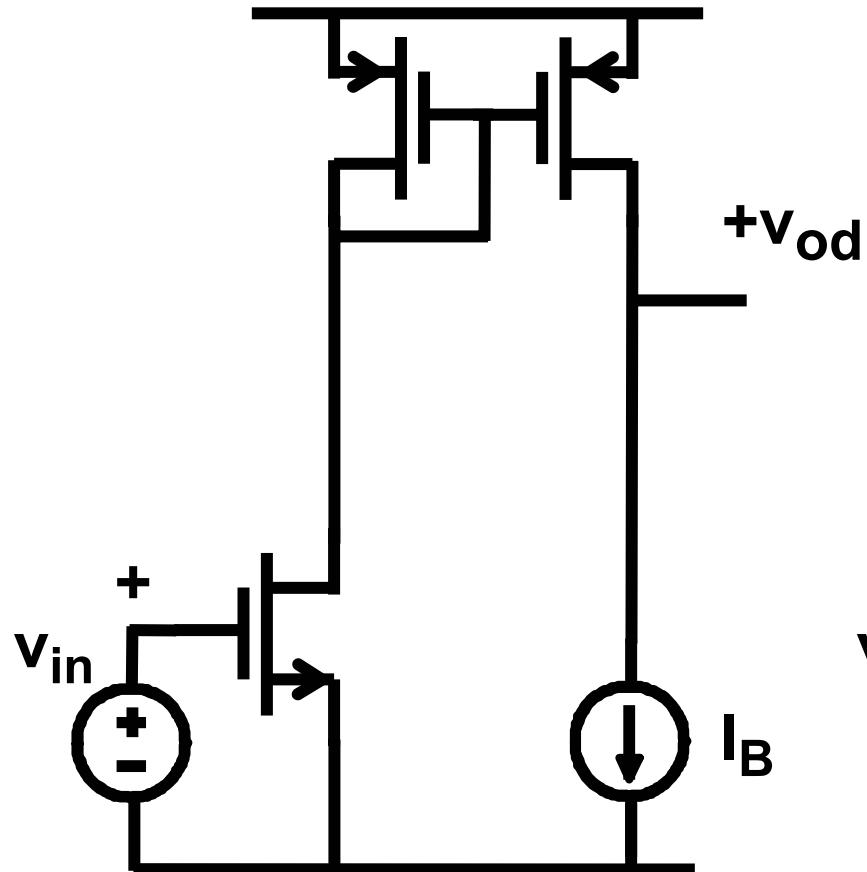


Current mirror 1

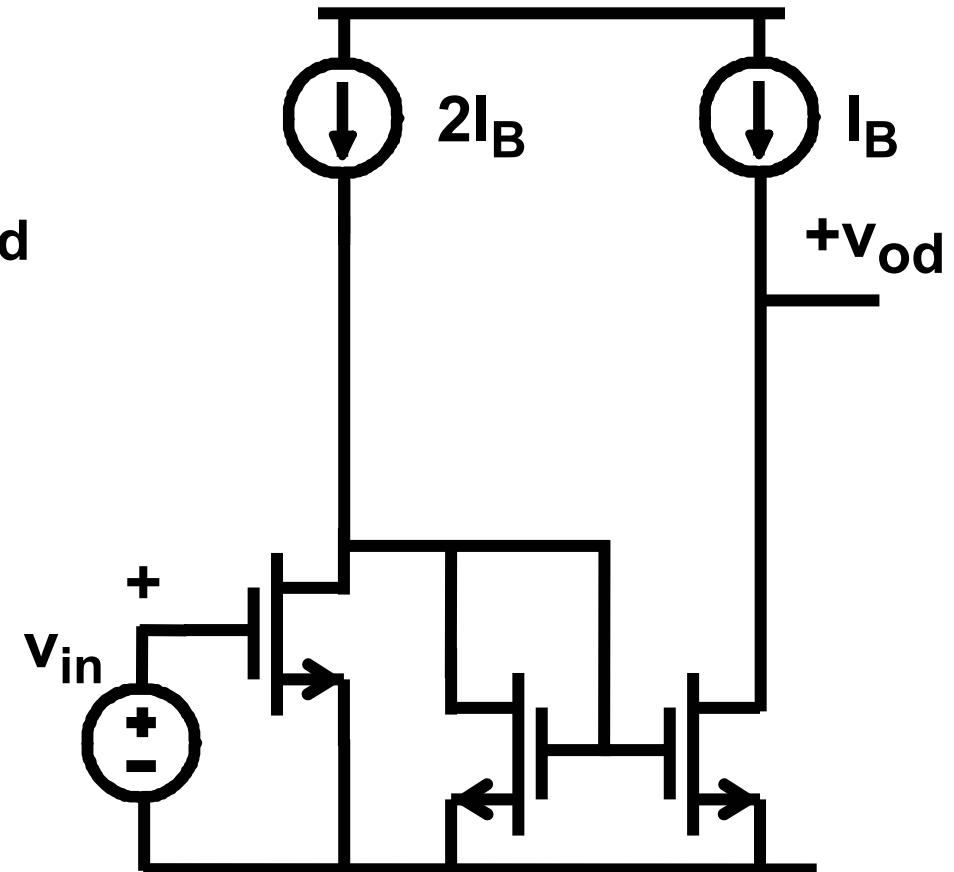


Current mirror 2 (only nMOS)

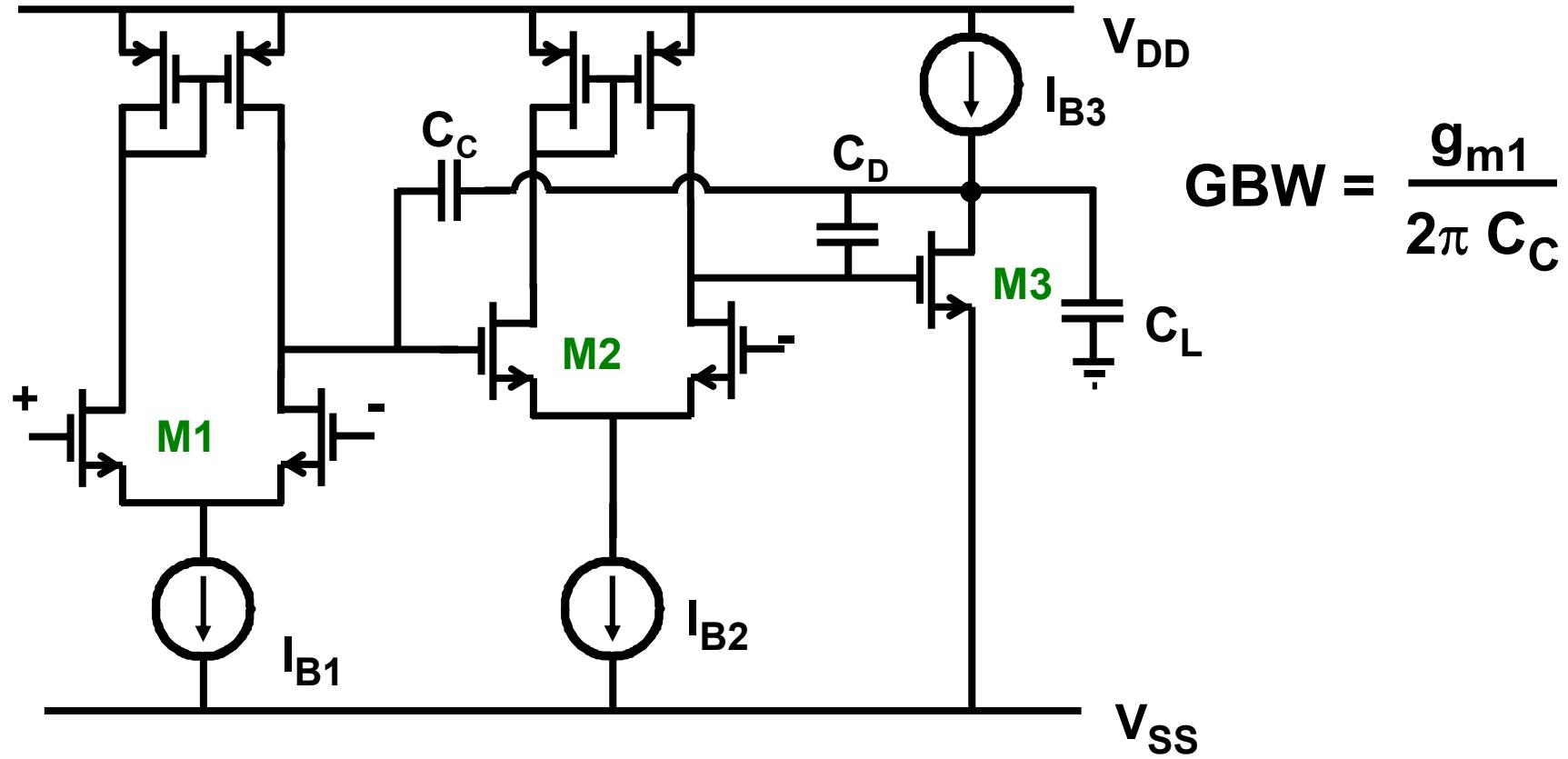Nested Miller with differential pair as 2nd stage



“Huijsing”

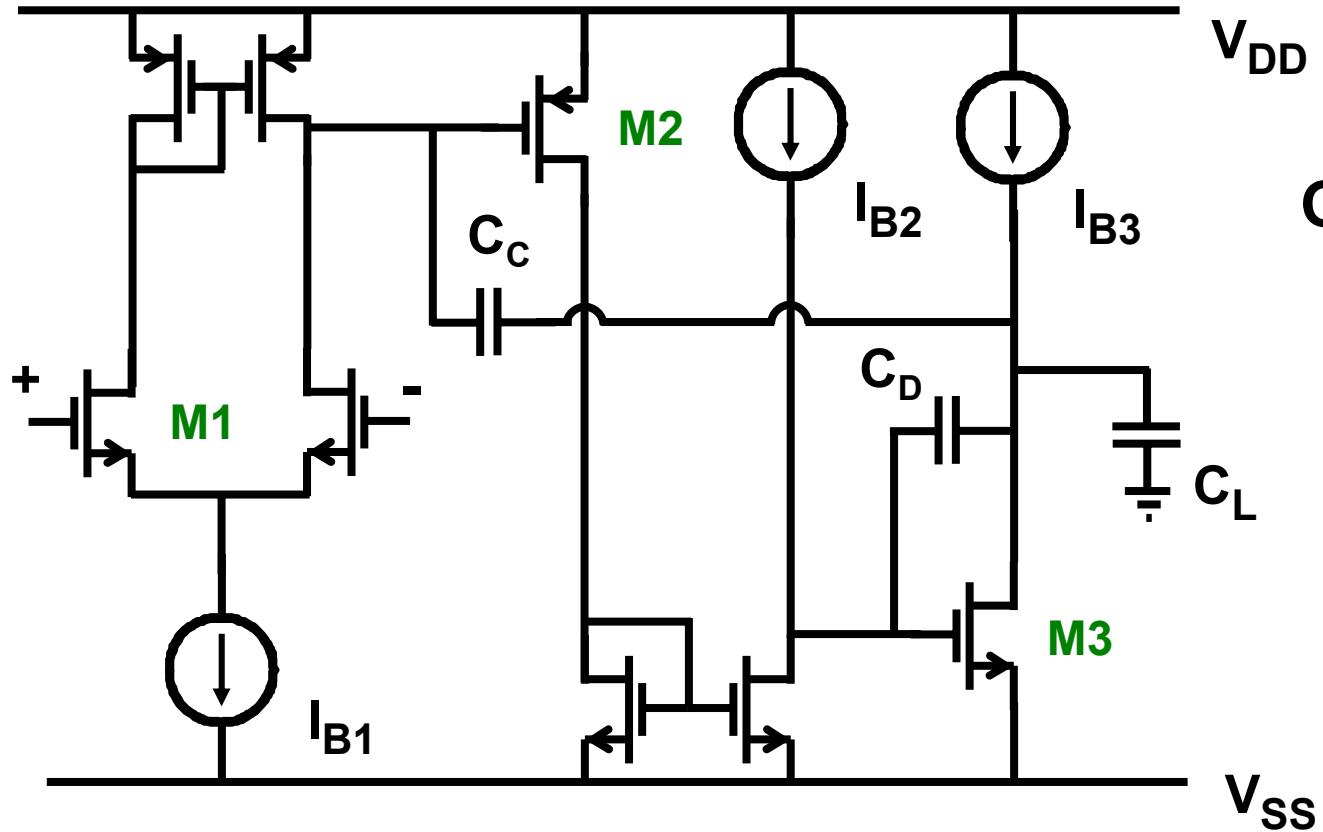
Nested Miller with current mirror as 2nd stage




$$\text{GBW} = \frac{g_m}{2\pi C_C}$$

“Nested Miller”

Comparison of power consumption

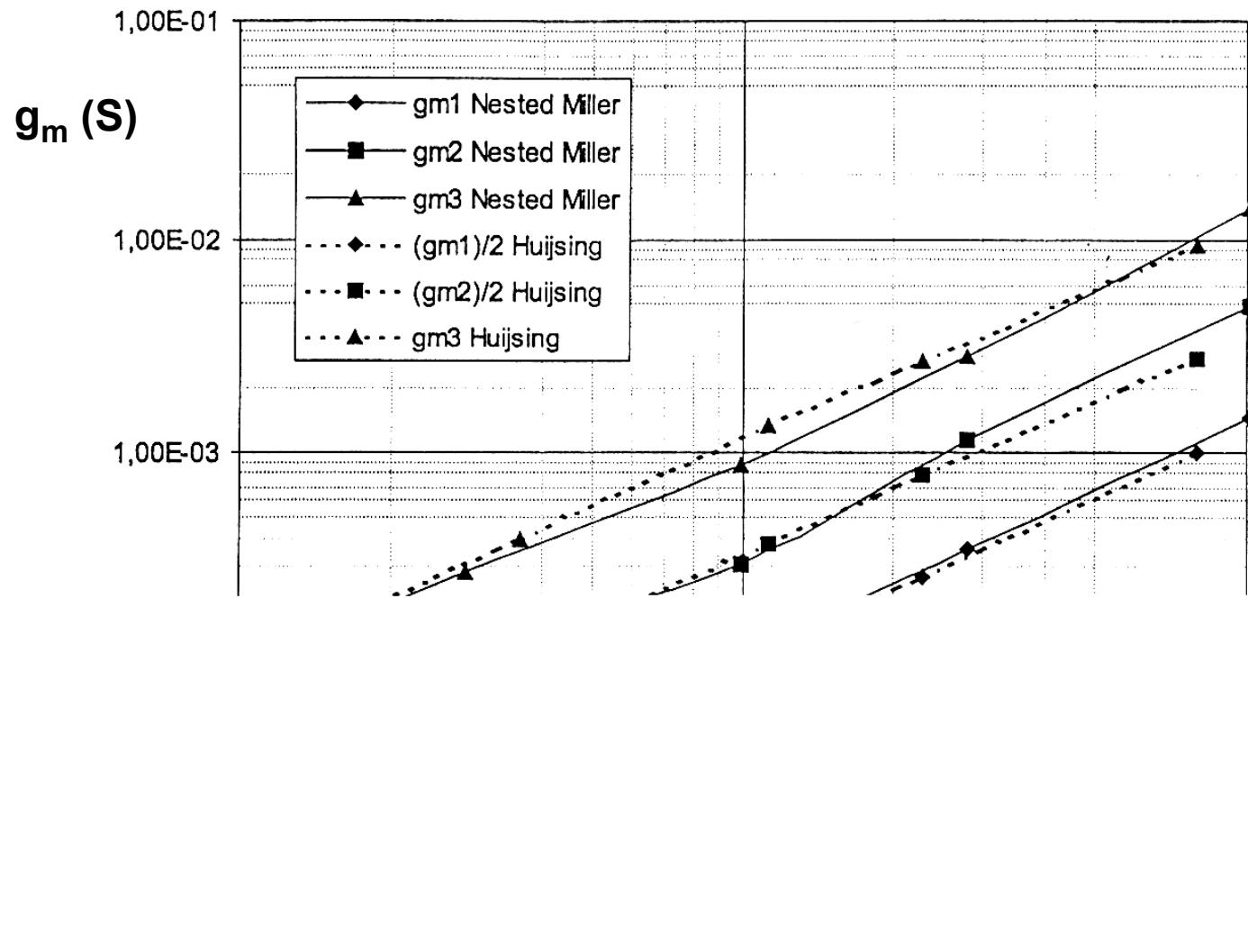

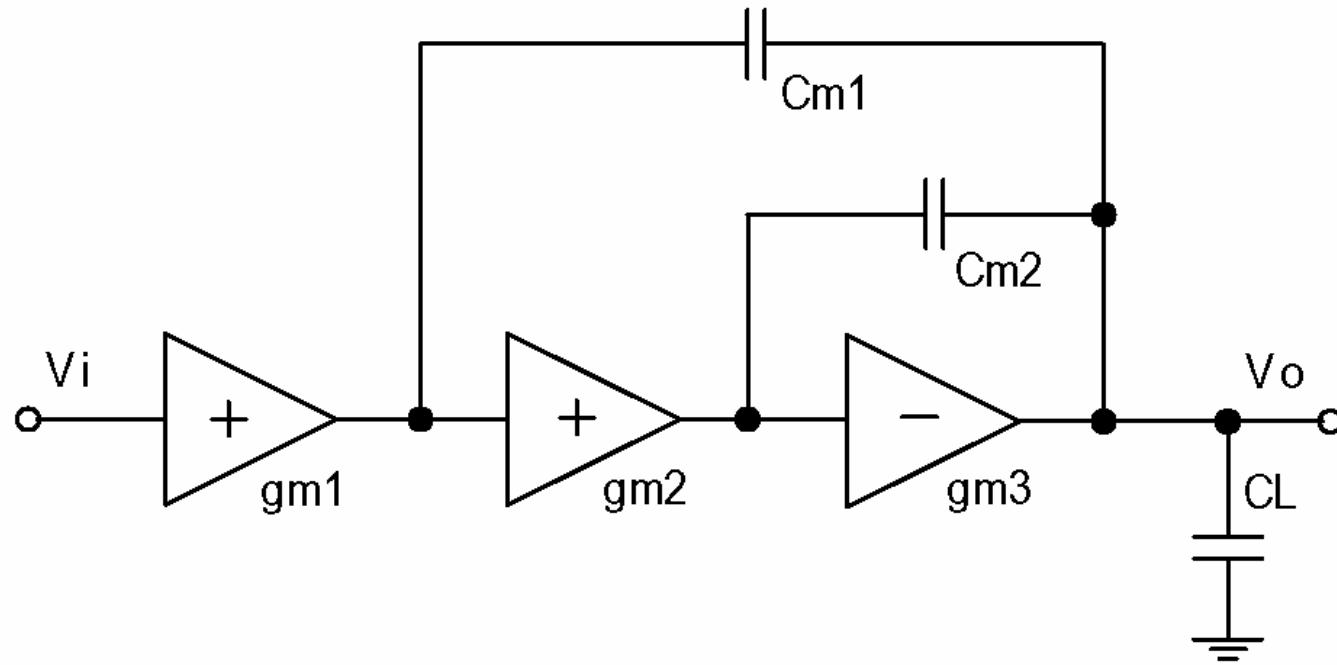Nested-Miller Frequency compensation - NMC



Huijsing, JSSC Dec.85, pp.1144-1150

NMC equations in open loop

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_3} + \frac{s^2}{\omega_3 \omega_4} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_2} \right)}$$

$$\omega_1 = \frac{g_{m2}}{C_{m2}}$$

$$\omega_2 = \frac{g_{m3}}{C_L}$$

$$A_{dc} = g_{m1} g_{m2} g_{m3} R_1 R_2 R_3$$

$$\omega_3 = - \frac{g_{m3}}{C_{m2}}$$

$$\omega_d = - \frac{1}{C_{m1} g_{m2} g_{m3} R_1 R_2 R_3}$$

$$\omega_4 = \frac{g_{m2}}{C_{m1}}$$

$$\omega_{UG} = \frac{g_{m1}}{C_{m1}}$$

NMC stability

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_3} + \frac{s^2}{\omega_3 \omega_4} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_2} \right)}$$

$$\omega_1 = \frac{g_{m2}}{C_{m2}}$$

$$\omega_2 = \frac{g_{m3}}{C_L}$$

$$g_{m1} < g_{m2} < g_{m3}$$

Butterworth 3rd order : $\zeta = 0.7$; $p = 2.8$


$$\omega_2 = 2 \quad \omega_1 = 4 \quad \omega_{UG}$$

Zero's negligible

$$\omega_3 = - \frac{g_{m3}}{C_{m2}}$$

$$\omega_4 = \frac{g_{m2}}{C_{m1}}$$

Nested Gm-C compensation NGCC

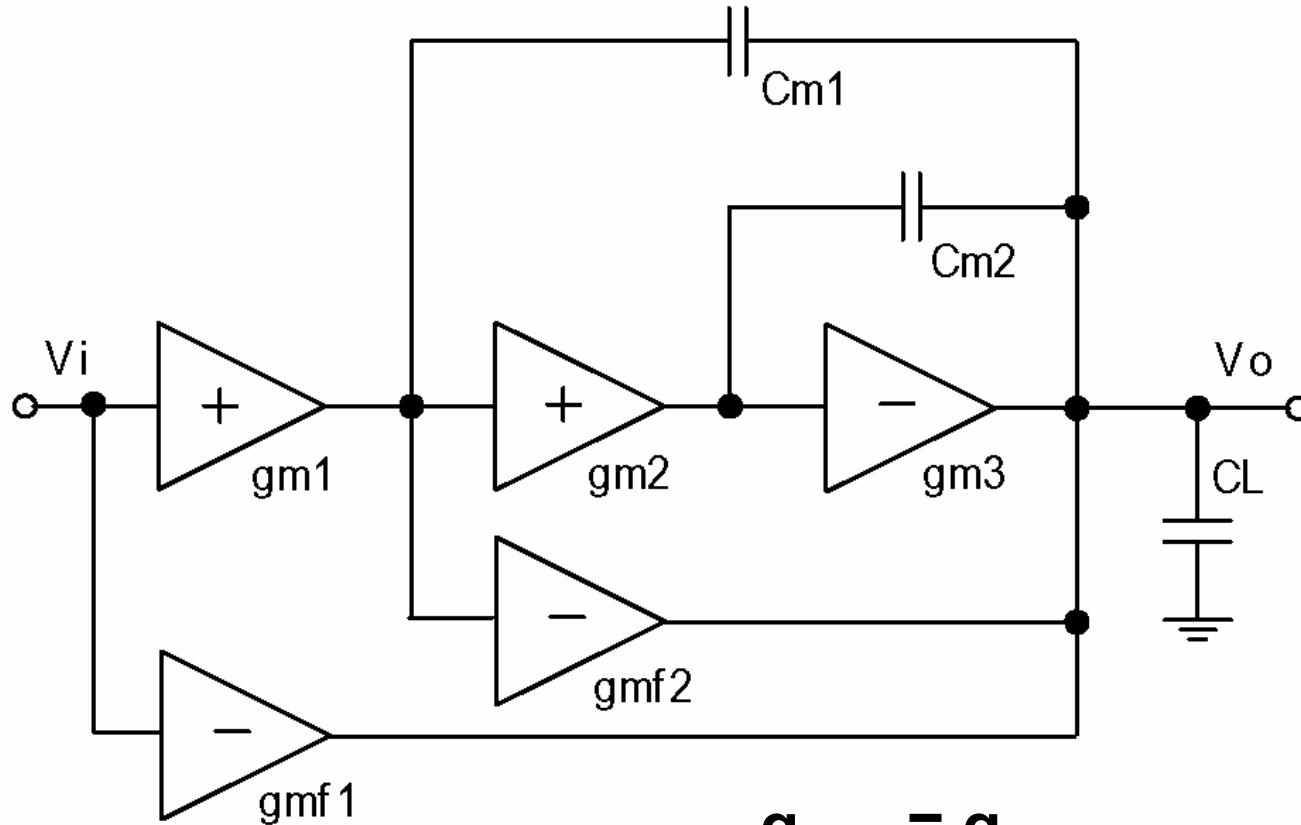

$$g_{mf1} = g_{m1}$$


$$g_{mf2} = g_{m2}$$

$$\omega_1 \approx \frac{g_{m2}}{C_{m2}}$$

$$\omega_2 \approx \frac{g_{m3}}{C_L}$$

You, JSSC Dec.97, 2000-2011

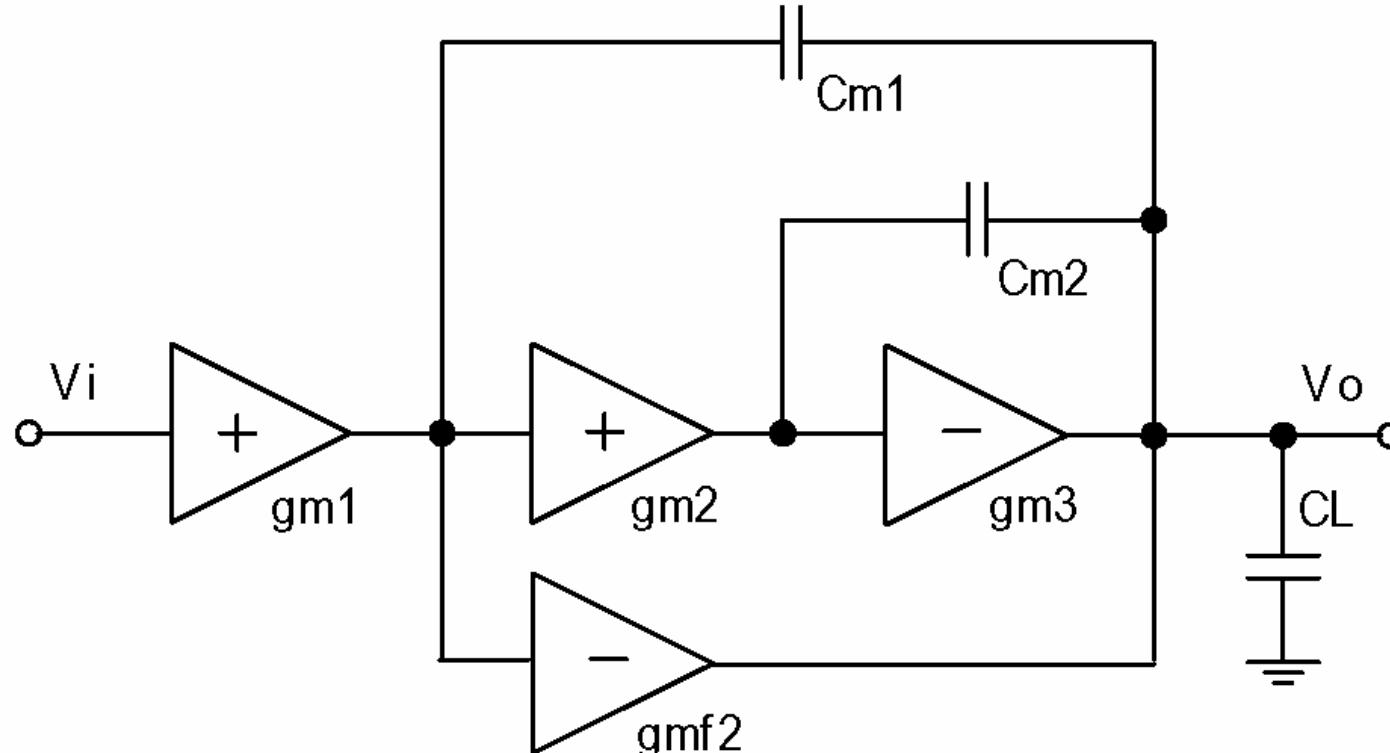Nested-Miller with single Feedforward - NMCF



$$\omega_z \approx \frac{g_{m2}}{C_{m2}}$$


$$\omega_1 \approx \frac{g_{m2}}{2C_{m2}}$$

$$\omega_2 \approx \frac{2g_{m3}}{C_L}$$

$$g_{mf2} = g_{m3}$$

Leung, CAS April 01, 388-394

Multipath Nested-Miller - MNMC

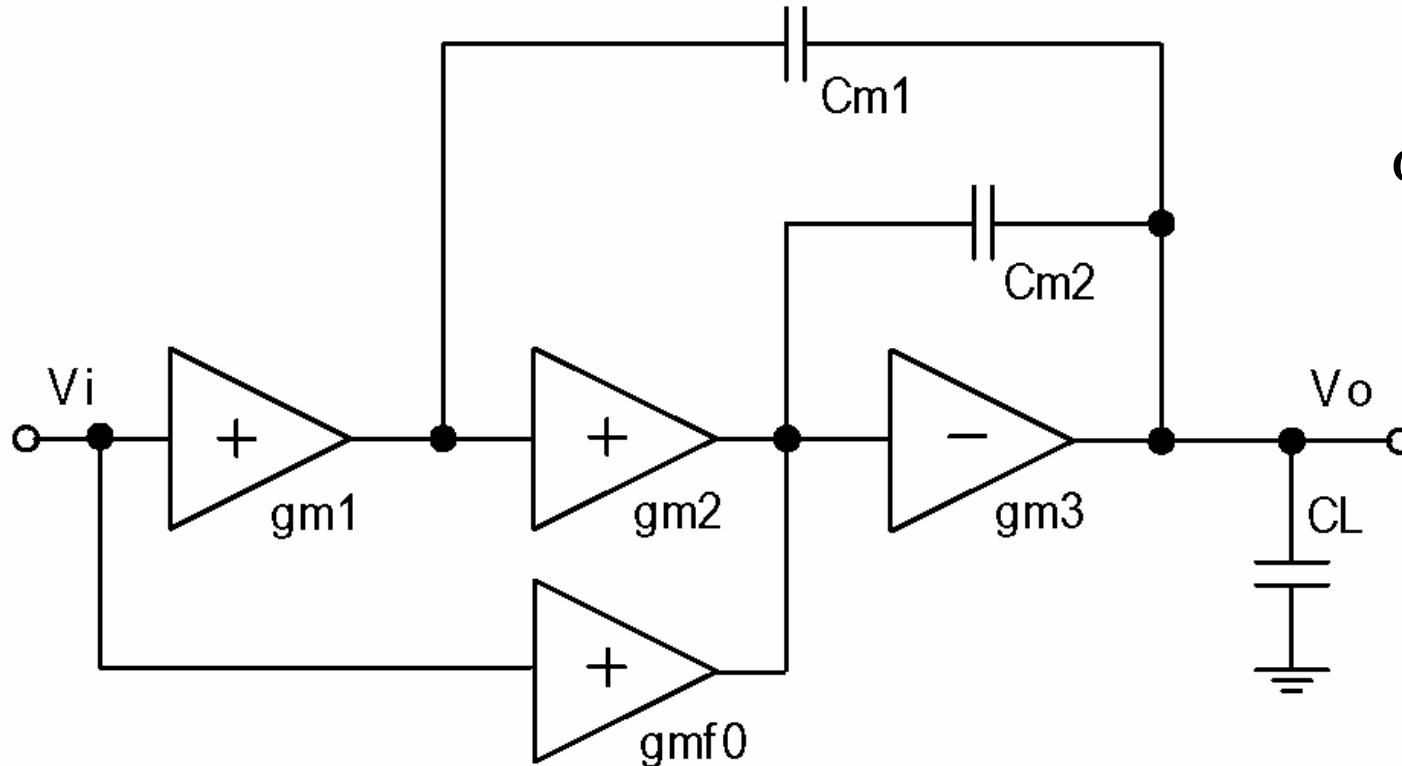

$$\omega_z \approx \frac{g_{m1} g_{m2}}{g_{mf0} C_{m1}}$$

$$\omega_1 \approx \frac{g_{m2}}{C_{m2}}$$

$$\omega_2 \approx \frac{g_{m3}}{C_L}$$

Eschauzier, JSSC Dec.92, pp.1709-1717


Comparison Nested-Miller solutions

| Topology | Stages | PM | $GB=2\pi GBW$ | T_{eL} | $T_{eL} / T_{eL} (\text{NMC})$ |
|----------|--------|--------------------|---------------------------|---------------|--------------------------------|
| Single | One | $<90^\circ$ | (g_m/C_L) | 1.0 | 4.0 |
| SMC | Two | $<63^\circ$ | $0.5(g_{m2}/C_L)$ | 0.5 | 2.0 |
| NMC | Three | $\approx 60^\circ$ | $0.25(g_{m3}/C_L)$ | 0.25 | 1.0 |
| NGCC | Three | $\approx 60^\circ$ | $0.25(g_{m3}/C_L)$ | 0.25 | 1.0 |
| NMCF | Three | $>60^\circ$ | $<0.5(g_{m3}/C_L)$ | <0.5 | <2.0 |
| MNMC | Three | $\approx 63^\circ$ | $\approx 0.5(g_{m3}/C_L)$ | ≈ 0.5 | ≈ 2.0 |

Table of contents

- Design procedure
- Nested-Miller designs
- Low-power designs
- Comparison

Nested Gm and nulling Res. NMC - NGRNMC

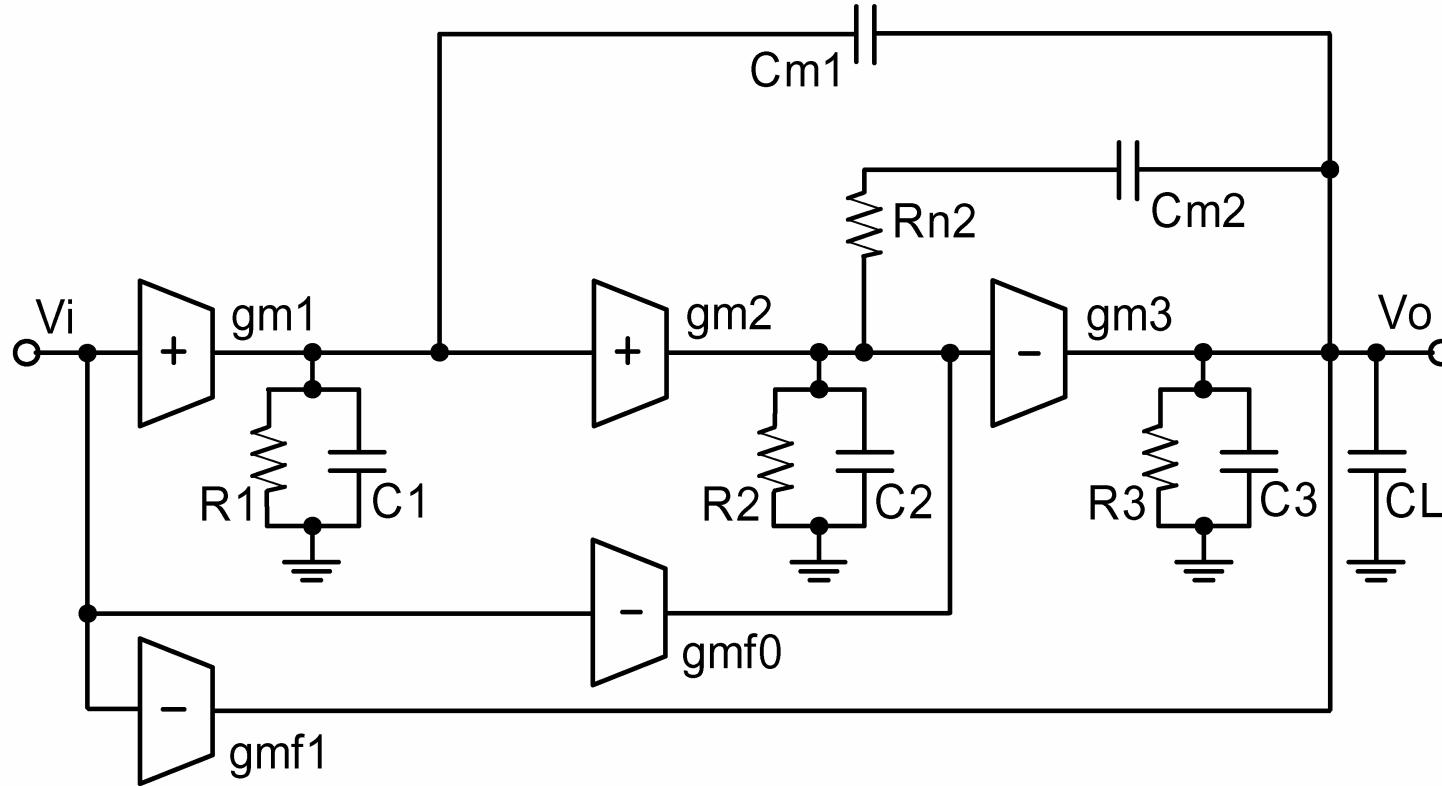

$$\omega_1 \approx \frac{1}{R_{n2}C_{m2}}$$

$$\omega_2 \approx \frac{g_{m2}g_{m3}R_{n2}}{C_L}$$


$GBW / GBW_{NMC} \approx 6.8$

$$g_{mf1} = g_{m1}$$


$$g_{mf0} = \dots$$

Peng, CICC 2002, 329-332

NGRNMC schematic

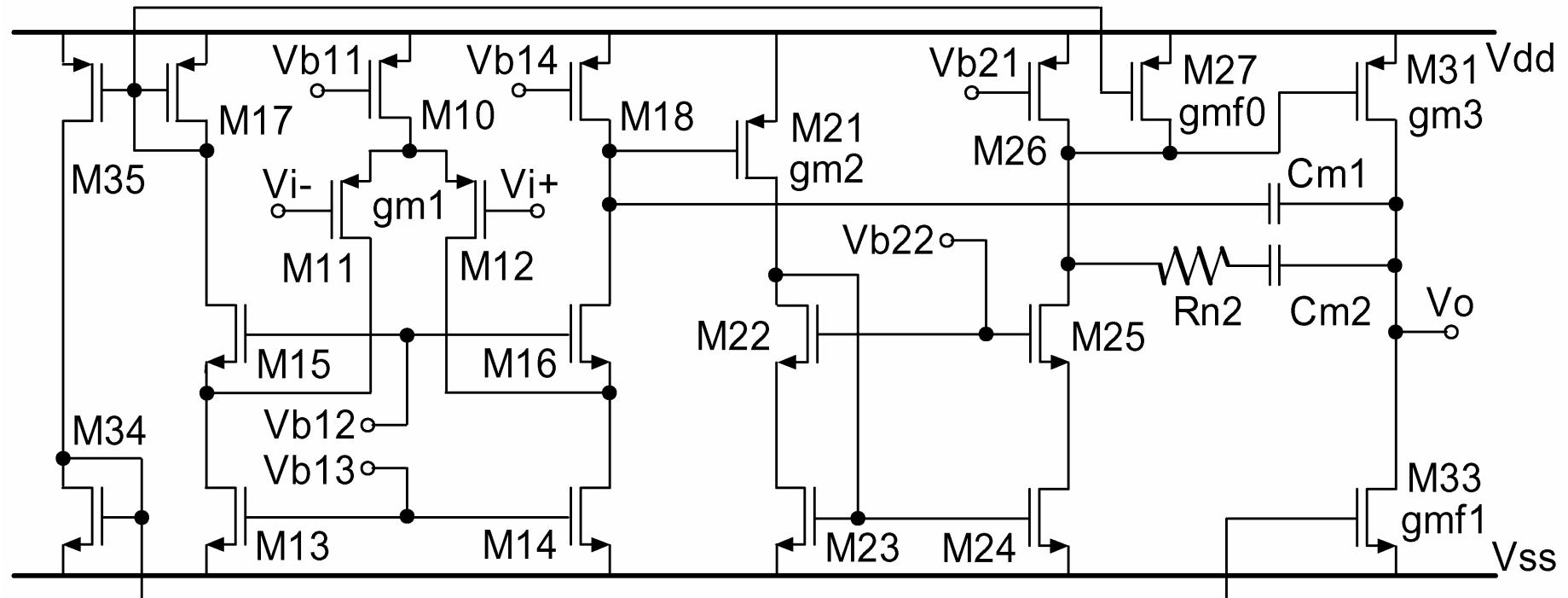

Positive Feedback Compensation - PFC

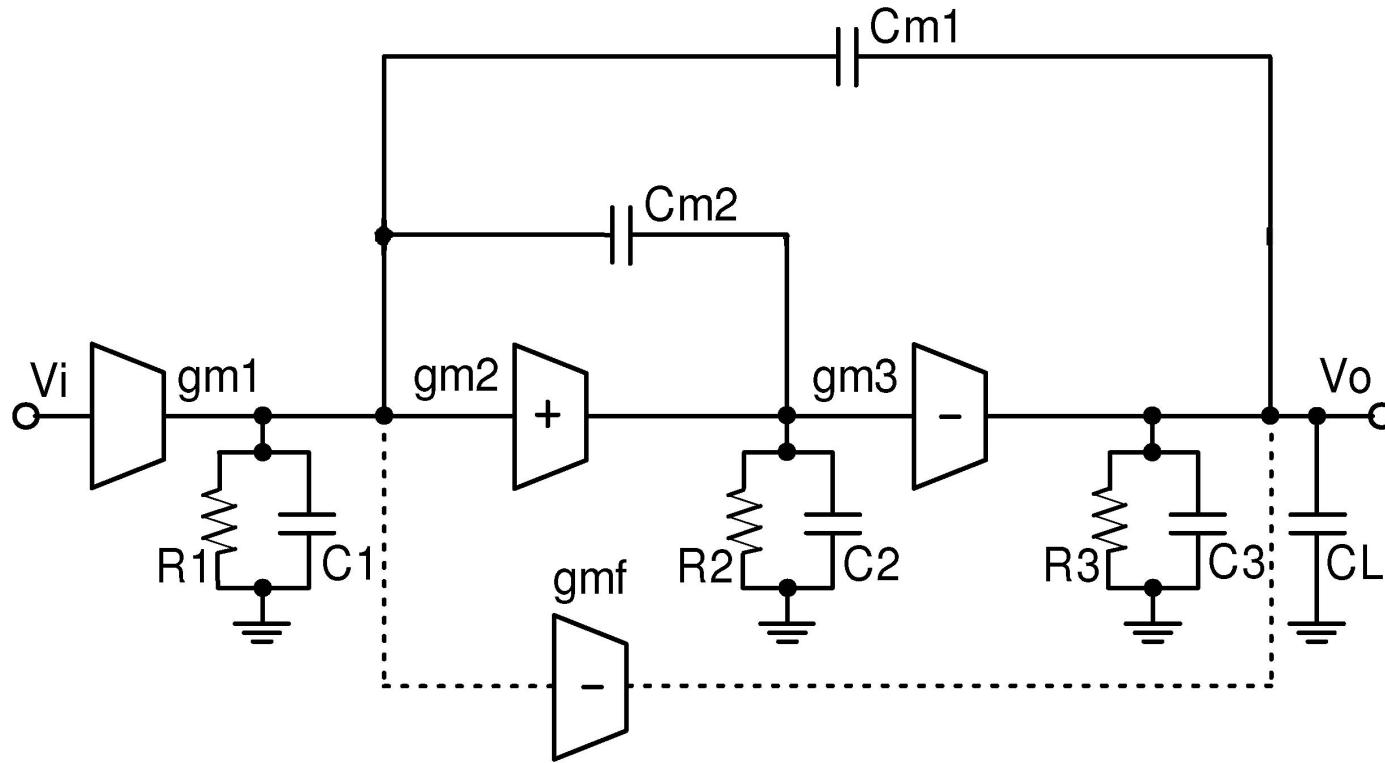

$$GBW / GBW_{NMC} \approx 6$$

Ramos, CICC 2002, 333-336

PFC Equations

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_3} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_2} \right)}$$

$$A_{dc} = g_{m1} g_{m2} g_{m3} R_1 R_2 R_3$$

$$\omega_d = - \frac{1}{C_{m1} g_{m2} g_{m3} R_1 R_2 R_3}$$

$$\omega_{UG} = \frac{g_{m1}}{C_{m1}}$$


$$\omega_1 = \frac{g_{m2}}{2C_{m2}}$$

$$\omega_2 = \frac{2g_{m3}}{C_L}$$


$$\omega_3 = - \frac{2g_{m3}}{C_{m1}}$$

Stability : $\frac{2g_{m3}}{C_L} > \frac{g_{m2}}{C_{m1}}$

PFC schematic

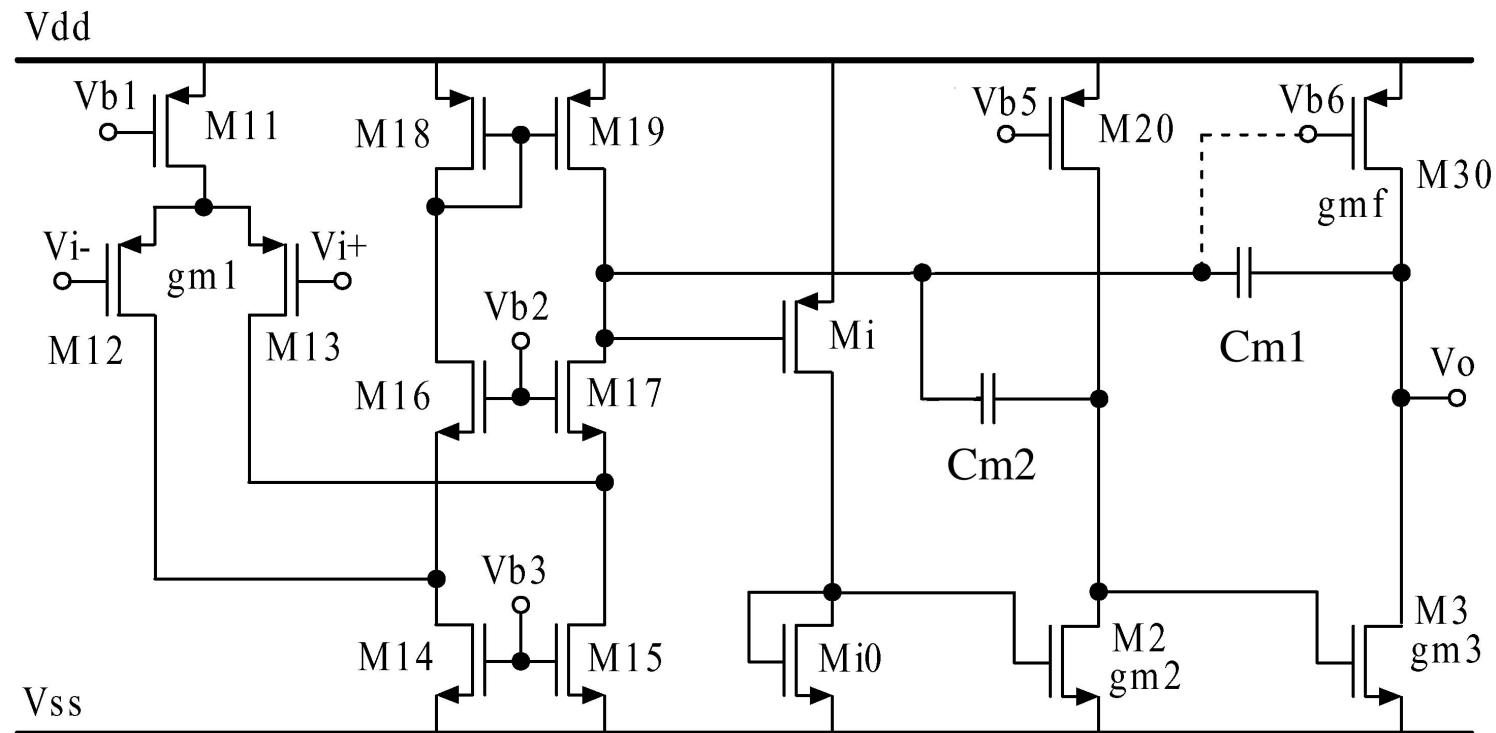

AC Boosting Compensation - ACBC

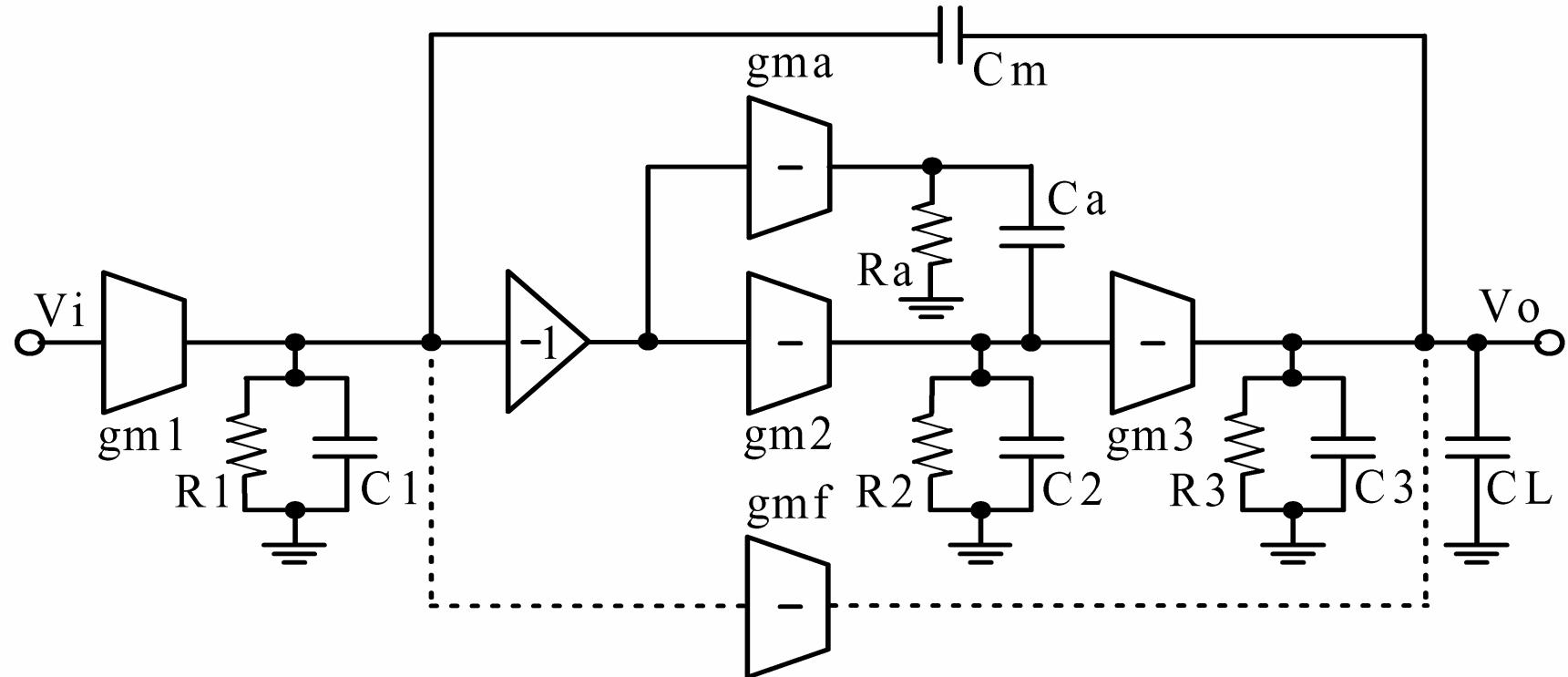

$$A_{2h} = (g_{m2} + g_{ma}) R_a$$

Peng, JSSC Nov.04, 2074-2079

ACBC equations

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_4} + \frac{s^3}{\omega_1 \omega_3 \omega_4} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_2} + \frac{s^3}{\omega_1 \omega_2 \omega_3} \right)}$$

$$\omega_1 = \frac{1}{A_{2h}} \frac{g_{m2}}{C_a}$$

$$\omega_2 = A_{2h} \frac{g_{m3}}{C_L}$$

$$A_{dc} = g_{m1} g_{m2} g_{m3} R_1 R_2 R_3$$

$$\omega_3 = \frac{1}{R_a C_2}$$

$$\omega_d = - \frac{1}{C_{m1} g_{m2} g_{m3} R_1 R_2 R_3}$$

$$\omega_4 = - A_{2h} \frac{g_{m3}}{C_m}$$

$$\omega_{UG} = \frac{g_{m1}}{C_{m1}}$$

$$A_{2h} = (g_{m2} + g_{ma}) R_a$$

ACBC stability

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_4} + \frac{s^3}{\omega_1 \omega_4 \omega_3} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} \right) \left(1 + \frac{s}{\omega_2} \right) \left(1 + \frac{s}{\omega_3} \right)}$$

$$\omega_1 = \frac{1}{A_{2h}} \frac{g_{m2}}{C_a}$$

$$\omega_2 = A_{2h} \frac{g_{m3}}{C_L}$$

$$\omega_3 = \frac{1}{R_a C_2}$$

Stability : $\omega_3 > \omega_2 > \omega_1$

Pole and zero at ω_1 cancel


Design : $\omega_2 \approx 2 \omega_{UG}$ for 60° PM

$$\omega_4 = -A_{2h} \frac{g_{m3}}{C_m}$$


GBW / GBW_{NMC} ≈ 17

$$A_{2h} = (g_{m2} + g_{ma}) R_a$$

ACBC schematic

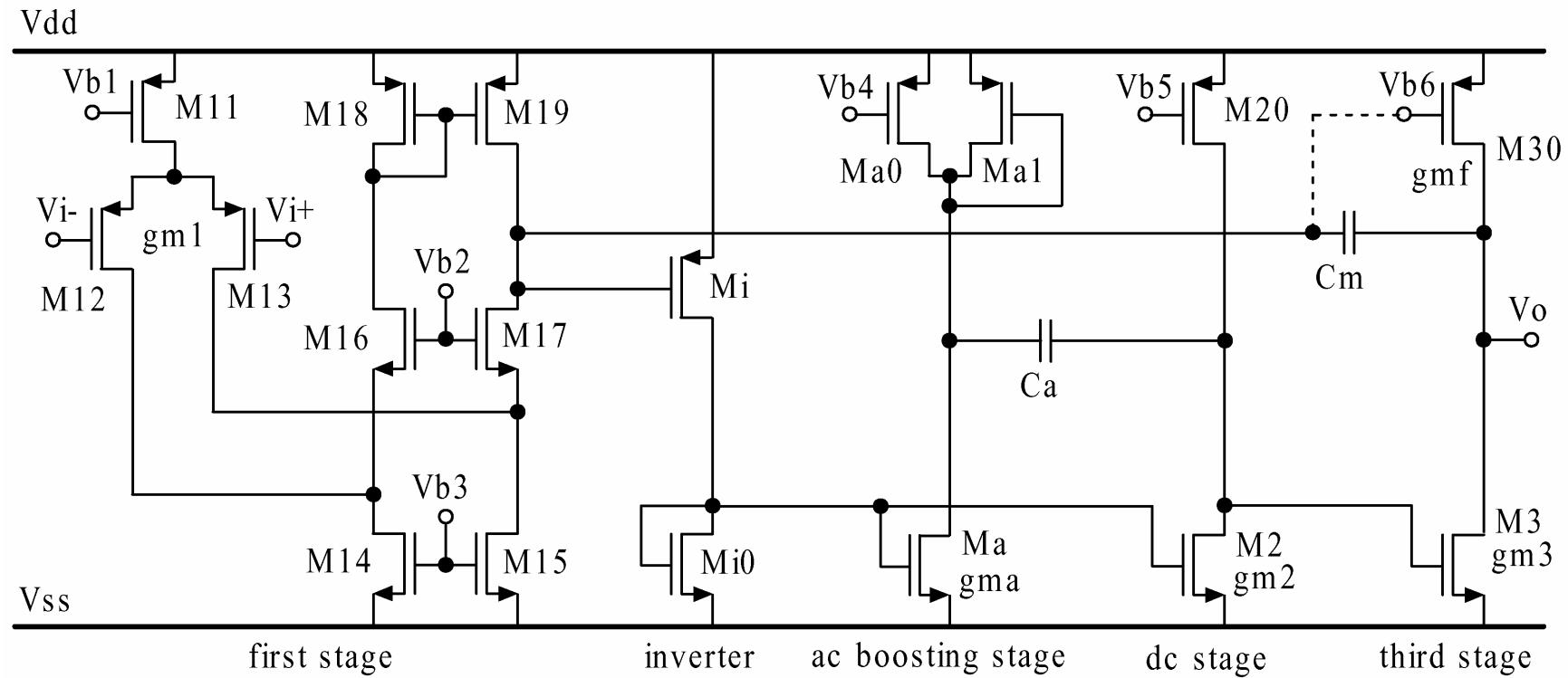


ACBC results

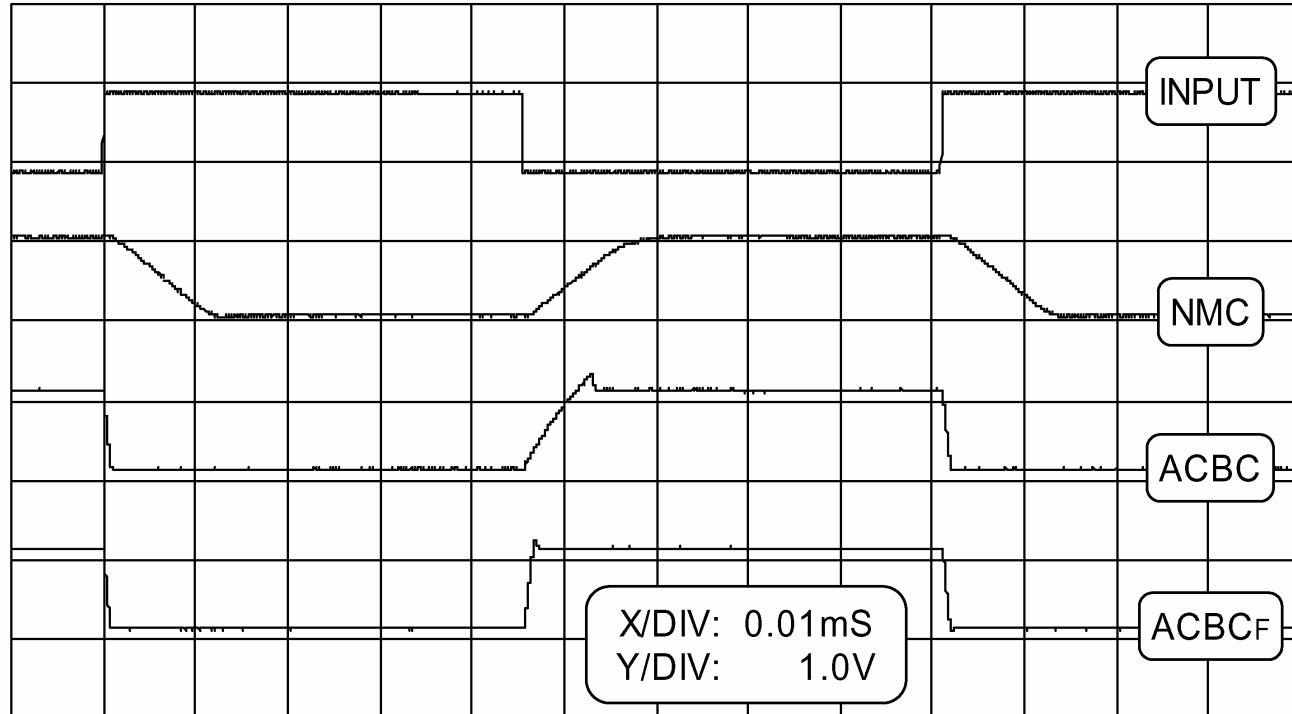

2 MHz
500 pF
0.16 mA

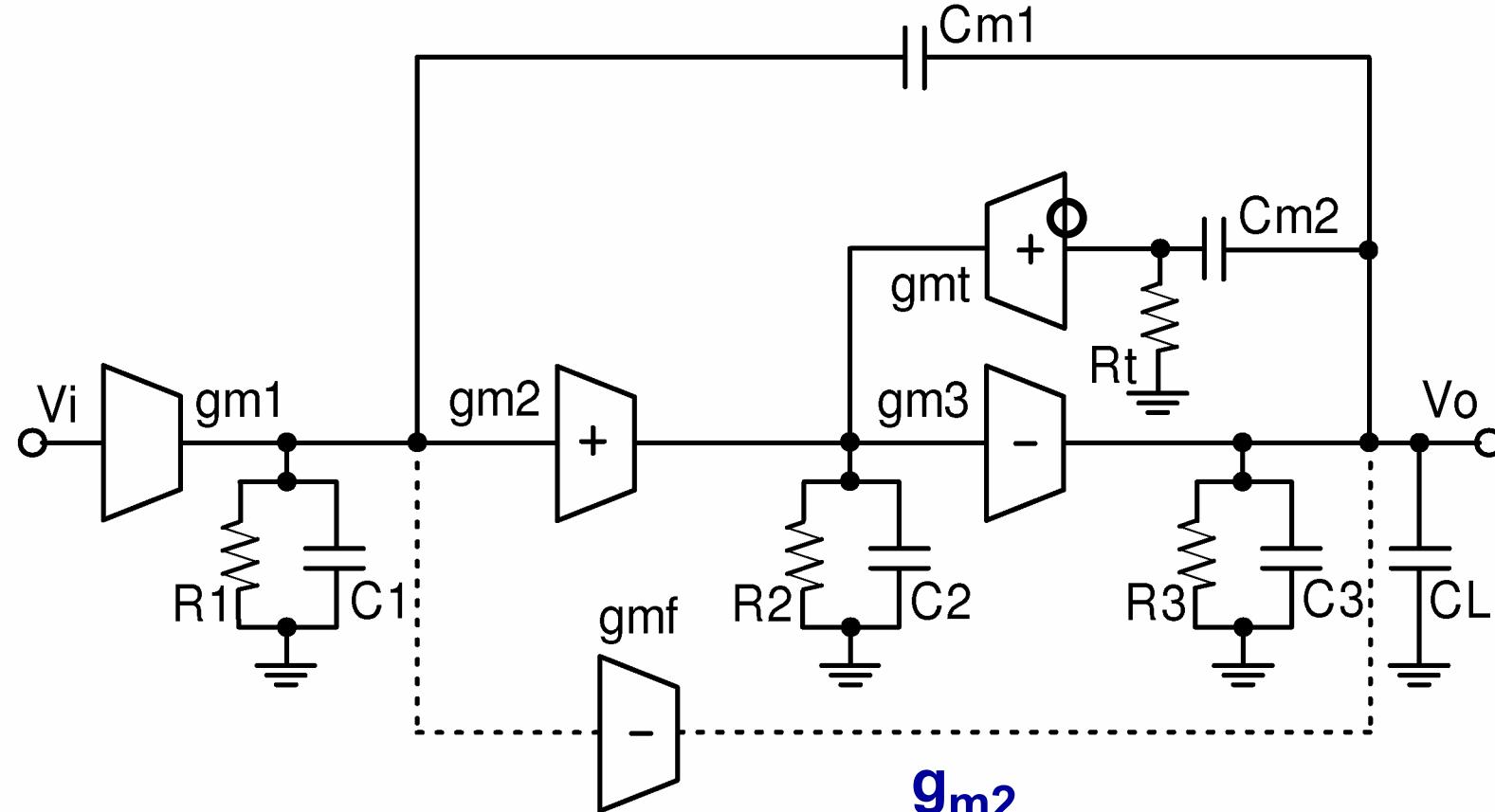0.2 V/ μ s
1.2 V/ μ s_F

Transcond. with Cap. Feedback Comp.- TCFC



$$k_t = \frac{g_{m2}}{g_{mt}}$$

Peng, JSSC July 05, 1514-1520

TCFC equations

$$A_v(s) = \frac{A_{dc} \left(1 + \frac{s}{\omega_2} + \frac{s^2}{\omega_2^2} + \frac{s^3}{\omega_2^2 \omega_4} \right)}{\left(1 + \frac{s}{\omega_d} \right) \left(1 + \frac{s}{\omega_1} + \frac{s^2}{\omega_1 \omega_2} + \frac{s^3}{\omega_1 \omega_2 \omega_3} \right)}$$

$$\omega_1 = \frac{1}{1+k_t} \frac{g_{m2}}{C_{m2}}$$

$$A_{dc} = g_{m1} g_{m2} g_{m3} R_1 R_2 R_3$$

$$\omega_d = - \frac{1}{C_{m1} g_{m2} g_{m3} R_1 R_2 R_3}$$

$$\omega_3 = (1+k_t) \frac{C_{m2}}{C_2} \frac{g_{m3}}{C_L}$$

$$\omega_{UG} = \frac{g_{m1}}{C_{m1}}$$

$$k_t = \frac{g_{m2}}{g_{mt}}$$

$$\omega_4 = - k_t \frac{C_{m2}}{C_2} \frac{g_{m3}}{g_{m1}} \omega_{UG}$$

TCFC stability

Stability ($k_t = 2$):

$$\frac{C_{m2}}{C_2} \frac{g_{m3}}{C_L} > \omega_{UG} \text{ since } C_{m2} > C_2$$

$$\omega_1 = \frac{1}{1+k_t} \frac{g_{m2}}{C_{m2}}$$

Design :

$\omega_3 > \omega_1$ since $C_{m2} > C_2$; then $p_{nd} = -\omega_1$

$$\omega_2 = \frac{1}{k_t} \frac{g_{m2}}{C_{m2}}$$

set $\omega_1 \approx 2 \omega_{UG}$ for 60° PM

$\omega_4 > \omega_{UG}$; then $z_{nd} = -\omega_2$

is $(1+k_t)/k_t$ larger than ω_1

$$\omega_3 = (1+k_t) \frac{C_{m2}}{C_2} \frac{g_{m3}}{C_L}$$

$$\omega_4 = -k_t \frac{C_{m2}}{C_2} \frac{g_{m3}}{g_{m1}} \omega_{UG}$$

GBW / GBW_{NMC} ≈ 41

TCFC schematic


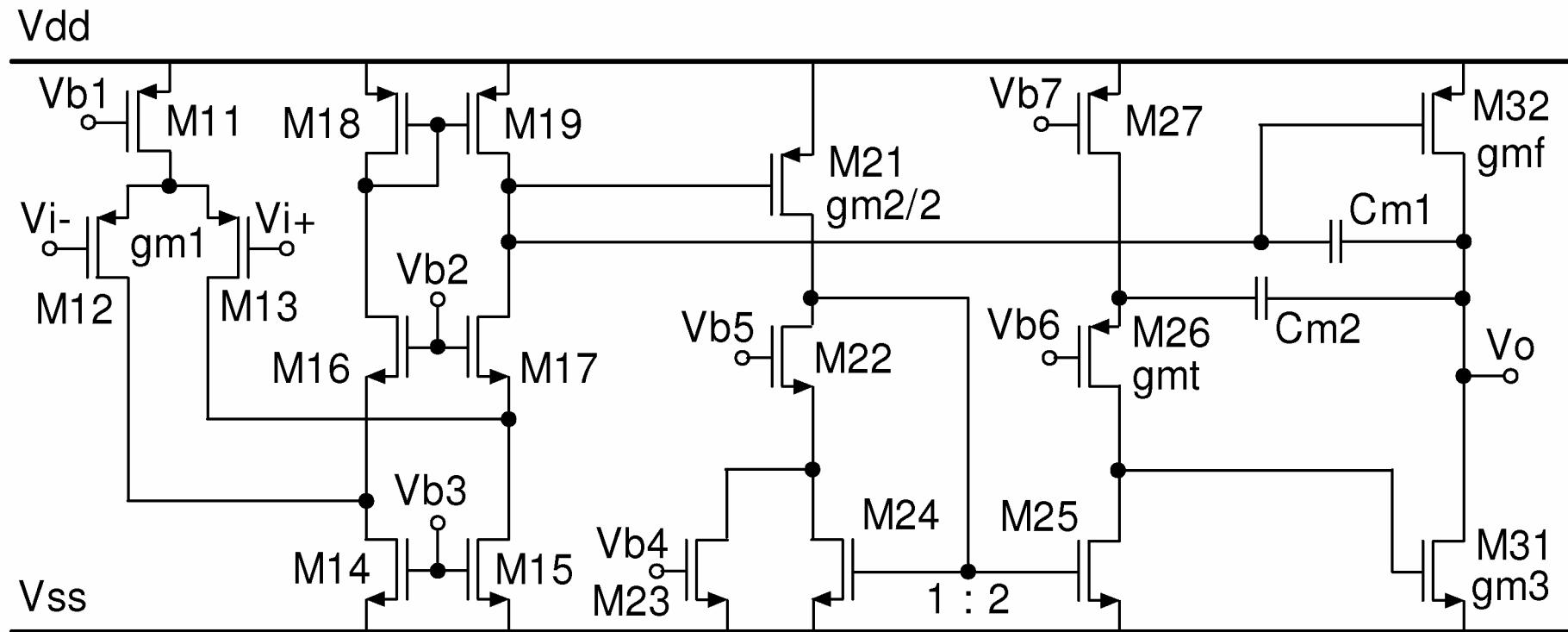


Table of contents

- Design procedure
- Nested-Miller designs
- Low-power designs
- Comparison

TCFC and other 3-stage opamps

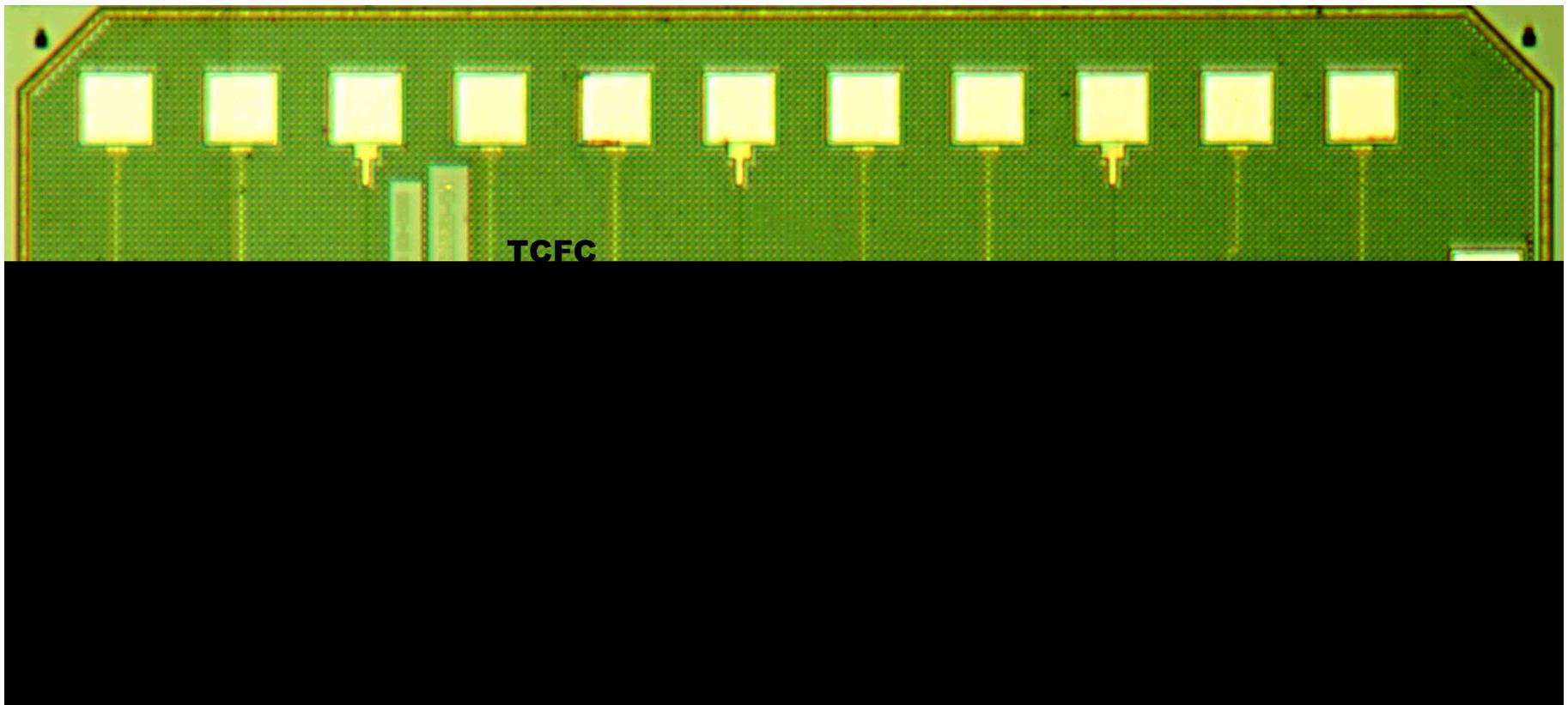

Comparison

No Capacitance

Nested Miller comp.

NMC with nulling R


Miller C Substitutions

AC Boosting comp.

Transconductance
Capacitance FC

| | | IFOMs $\frac{MHz \cdot pF}{mA}$ | IFOML $\frac{V/\mu S \cdot pF}{mA}$ | FOMs $\frac{MHz \cdot pF}{mW}$ | FOML $\frac{V/\mu S \cdot pF}{mW}$ | Tech. |
|-------------------|----------|------------------------------------|--|-----------------------------------|---------------------------------------|--------------------------|
| NCs | | | | | | |
| NCFF | [Tha03] | 536 | - | 214 | - | $\frac{0.5\mu m}{CMOS}$ |
| NMs | | | | | | |
| NMC | [Esc92] | 632 | 211 | 79 | 26 | $\frac{3GHz f_t}{BJT}$ |
| MNMC | [Esc92] | 1053 | 368 | 132 | 46 | $\frac{3GHz f_t}{BJT}$ |
| NMCF | [Leu01a] | 600 | 246 | 300 | 123 | $\frac{0.8\mu m}{CMOS}$ |
| NGCC | [You97] | 36 | 148 | 18 | 74 | $\frac{2\mu m}{CMOS}$ |
| HNMC | [Esc94] | 134 | 134 | 89 | 89 | $\frac{0.8\mu m}{CMOS}$ |
| MHNMC | [Esc94] | 401 | 467 | 267 | 311 | $\frac{0.8\mu m}{CMOS}$ |
| DNMC | [Per93] | 250 | 188 | 50 | 38 | $\frac{1.5\mu m}{CMOS}$ |
| MRs | | | | | | |
| NMCNR | [Leu01a] | 410 | 168 | 205 | 84 | $\frac{0.8\mu m}{CMOS}$ |
| IRNMC | [Ho03] | 626 | 444 | 209 | 148 | $\frac{0.6\mu m}{CMOS}$ |
| EFC | [Ng99] | 817 | 1200 | 272 | 400 | $\frac{0.6\mu m}{CMOS}$ |
| NGRNMC | [Peng03] | 700 | 490 | 280 | 196 | $\frac{0.35\mu m}{CMOS}$ |
| MSs | | | | | | |
| PFC | [Ram03b] | 1915 | 709 | 1276 | 473 | $\frac{0.35\mu m}{CMOS}$ |
| DFCFC | [Leu01a] | 1238 | 628 | 619 | 314 | $\frac{0.8\mu m}{CMOS}$ |
| ACBs | | | | | | |
| ACBC | [Peng04] | 5981 | 2215 | 2991 | 1108 | $\frac{0.35\mu m}{CMOS}$ |
| ACBC _F | [Peng04] | 5864 | 3086 | 2932 | 1543 | $\frac{0.35\mu m}{CMOS}$ |
| TCFs | | | | | | |
| AFC | [Ahu83] | 326 | - | 33 | - | $\frac{4\mu m}{CMOS}$ |
| AFFC | [Lee03b] | 2700 | 894 | 1350 | 447 | $\frac{0.8\mu m}{CMOS}$ |
| DLPC | [Lee03a] | 3818 | 1800 | 2545 | 1200 | $\frac{0.6\mu m}{CMOS}$ |
| TCFC | [Peng05] | 14250 | 5175 | 9500 | 3450 | $\frac{0.35\mu m}{CMOS}$ |

Transient responses in unity gain

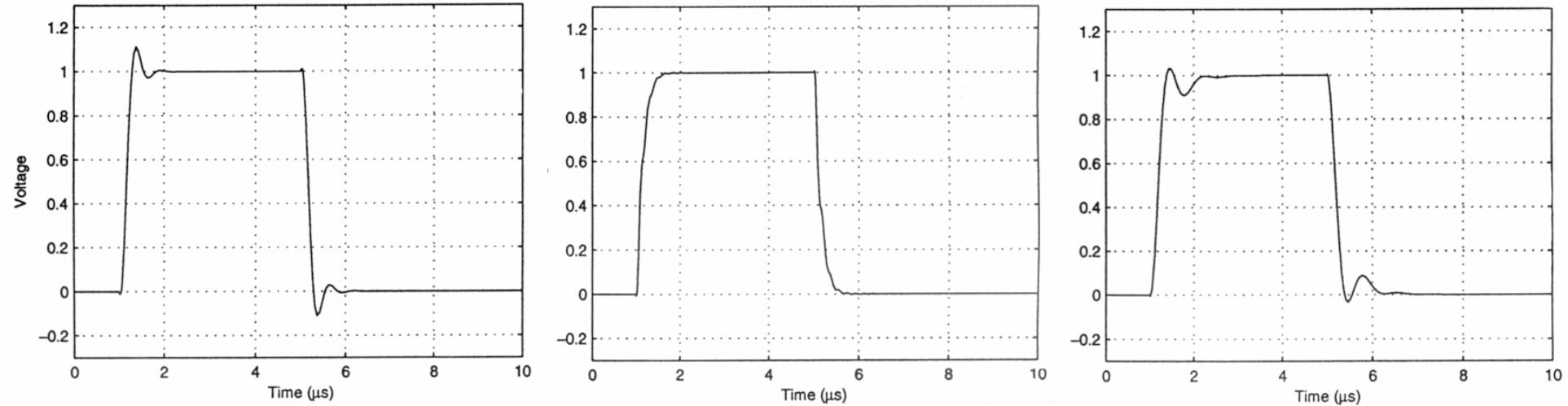

NMC

TCFC

PFC

All GBW ≈ 1 MHz and $C_L = 100$ pF

Same $C_{m1} = 18$ pF ; $C_{m2} = 3$ pF; minimum currents.

References

- J. Huijsing, D. Linebarger, “Low-voltage operational amplifier with rail-to-rail input and output ranges” *IEEE J. Solid-State Circuits*, vol. 20, pp. 1144-1150, Dec. 1985.
- R. Eschauzier, L. Kerklaan, and J. Huijsing, “A 100-MHz 100-dB operational amplifier with multipath nested Miller compensation structure,” *IEEE J. Solid-State Circuits*, vol. 27, pp. 1709-1717, Dec. 1992.
- S. Pernici, G. Nicollini, R. Castello, “A CMOS low-distortion fully differential power amplifier with double nested Miller compensation”, *IEEE J. Solid-State Circuits*, vol. 28, pp. 758-763, July 1993.
- F. You, S. H. K. Embabi and E. Sánchez-Sinencio, “Multistage amplifier topologies with nested Gm-C compensation,” *IEEE J. Solid-State Circuits*, vol. 32 pp. 2000-2011, Dec. 1997.
- K. N. Leung and P. K. T. Mok, “Nested Miller compensation in low-power CMOS design,” *IEEE Trans. Circuits Syst. II*, vol. 48, pp. 388-394, Apr. 2001.
- K. N. Leung and P. K. T. Mok, W. H. Ki, and J. K. O. Sin, “Three-stage large capacitive load amplifier with damping-factor-control frequency compensation,” *IEEE J. Solid-State Circuits*, vol. 35, pp. 221–230, Feb. 2000.
- H. Lee and P. K. T. Mok, “Active-feedback frequency-compensation technique for low-power multistage amplifiers,” *IEEE J. Solid-State Circuits*, vol. 38, pp. 511-520, Mar. 2003.
- X. Peng and W. Sansen, “Nested feedforward gm-stage and nulling resistor plus nested Miller compensation for multistage amplifiers”, CICC, May 2002, pp. 329-332.
- J. Ramos and M. Steyaert, “Three stage amplifier with positive feedback compensation scheme,” in *Proc. IEEE Custom Integrated Circuits Conf.*, Orlando, FL, May 2002, pp. 333-336.
- X. Peng and W. Sansen, “AC boosting compensation schema for low-power multistage amplifiers”, *IEEE J. Solid-State Circuits*, vol. 39, pp. 2074-2079, Nov. 2004.
- X. Peng and W. Sansen, “Transconductance with capacitances feedback compensation for multi-stage amplifiers”, *IEEE J. Solid-State Circuits*, vol. 40, pp.1514-1520, July 2005.

Table of contents

- Design procedure
- Nested-Miller designs
- Low-power designs
- Comparison