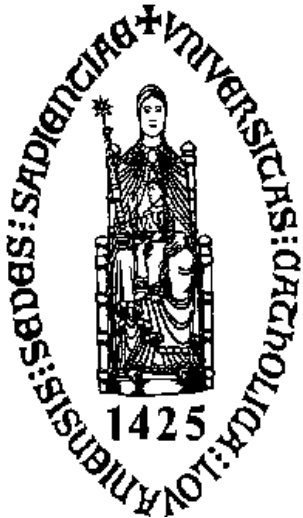

Important opamp configurations



Willy Sansen

KULeuven, ESAT-MICAS

Leuven, Belgium


willy.sansen@esat.kuleuven.be



Table of contents

- **Simple CMOS OTA**
- CMOS Miller OTA
- Symmetrical CMOS OTA
- Folded cascode OTA
- Other opamps

Simple CMOS OTA

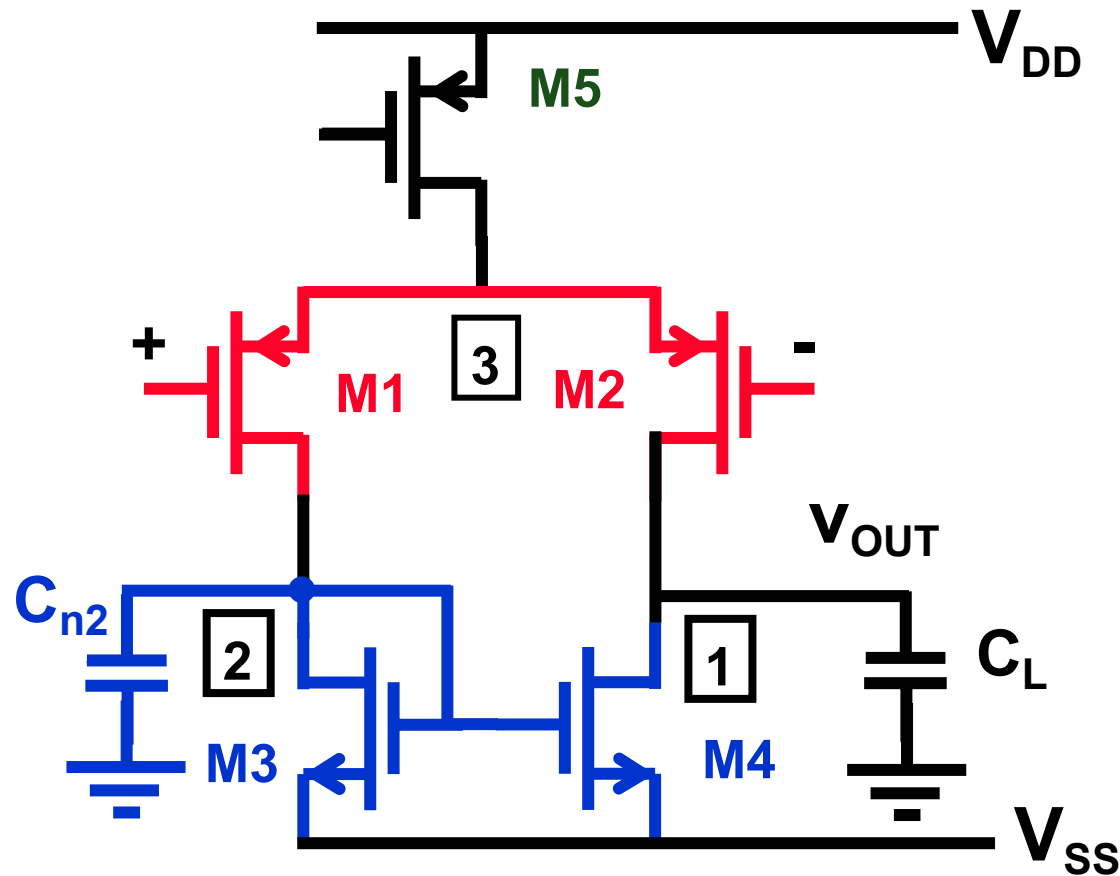

Differential pair
Current mirror



$$GBW = \frac{g_{m1}}{2\pi C_L}$$

$$f_{nd} = \frac{g_{m3}}{2\pi C_{n2}}$$

$$f_{nd} \approx \frac{f_{T3}}{4} \quad ?$$


$$C_{n2} = 2C_{GS3} + C_{DB3} + C_{DB1} \approx 4C_{GS3}$$

Simple CMOS OTA : f_{nd}

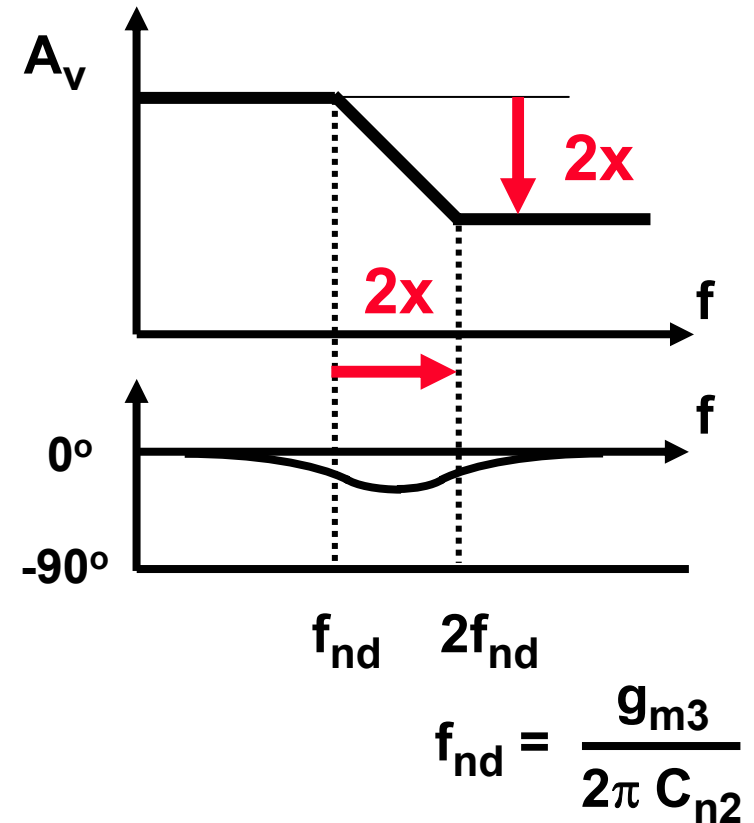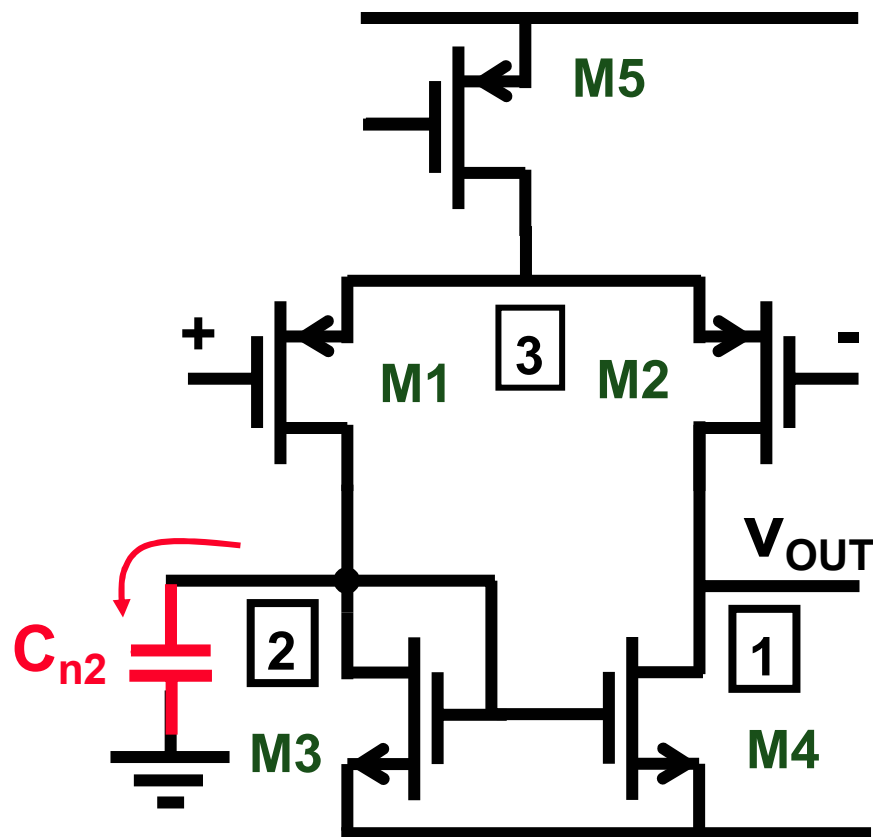

$$PM = 90^\circ - \arctan \frac{GBW}{f_{nd}} + \arctan \frac{GBW}{2 f_{nd}} \approx 85^\circ$$

Telescopic CMOS OTA

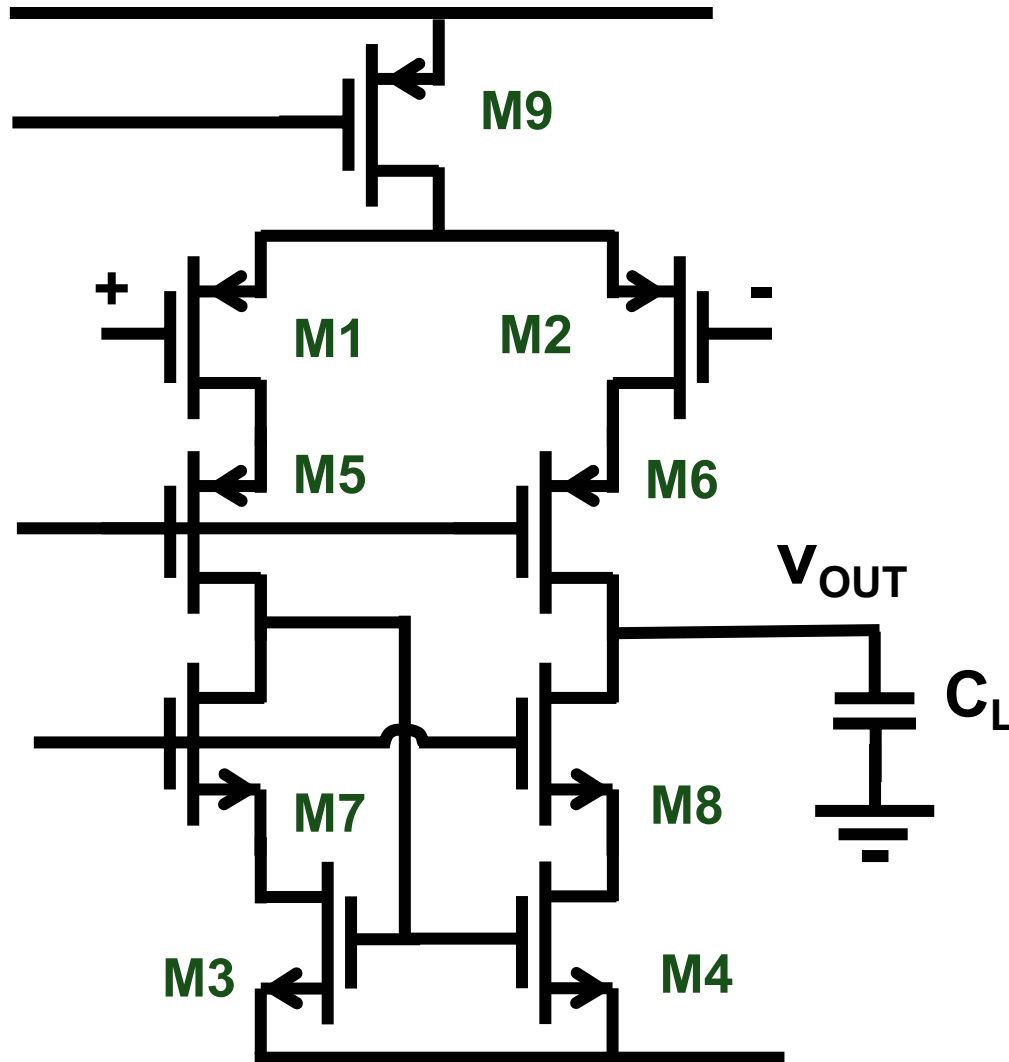

More gain
At low frequencies

$$GBW = \frac{g_{m1}}{2\pi C_L}$$

Gulati, JSSC Dec.98, 2010-2019

Cascodes increase gain at low frequencies


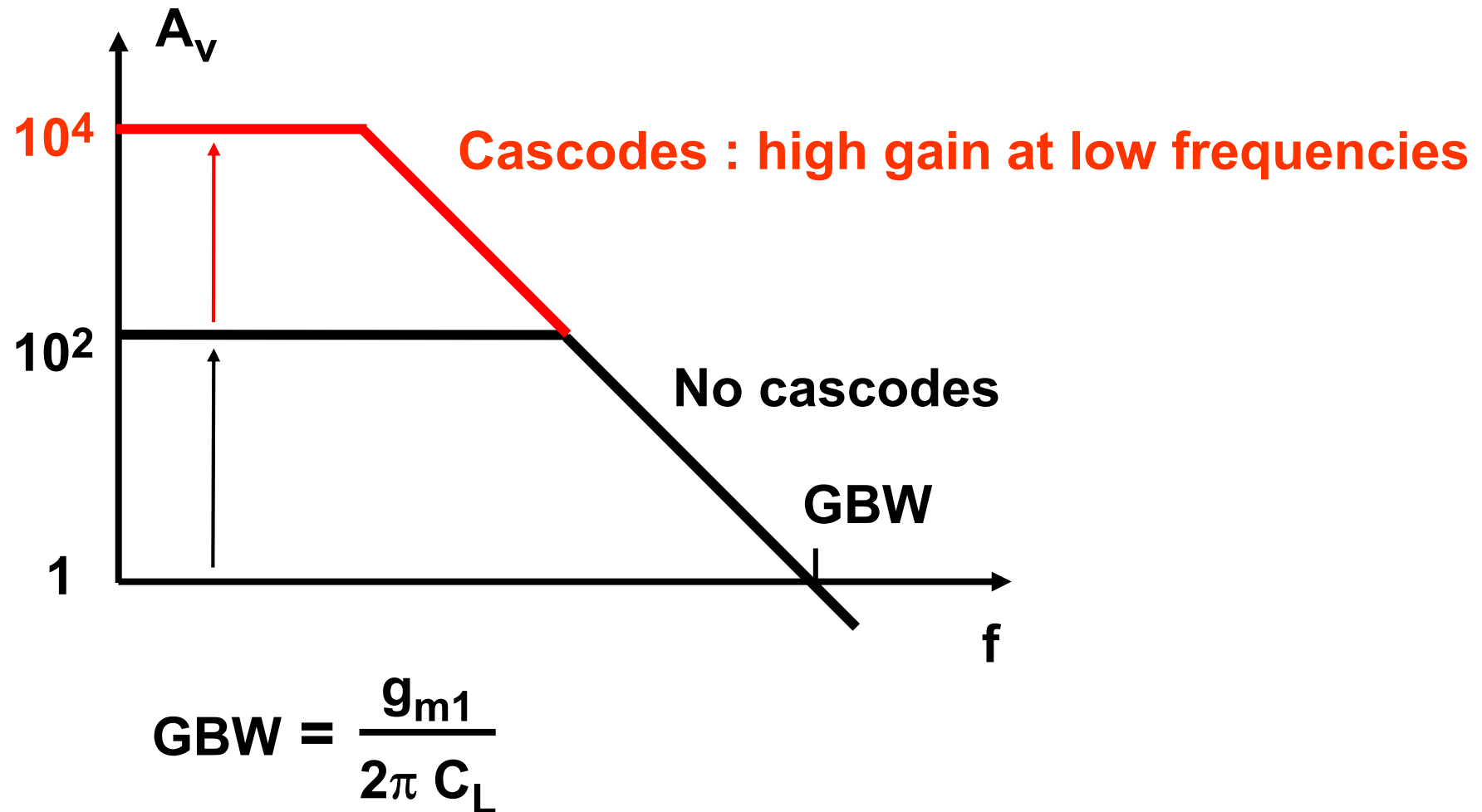


Table of contents

- Simple CMOS OTA
- CMOS Miller OTA
- Symmetrical CMOS OTA
- Folded cascode OTA
- Other opamps

Miller CMOS OTA

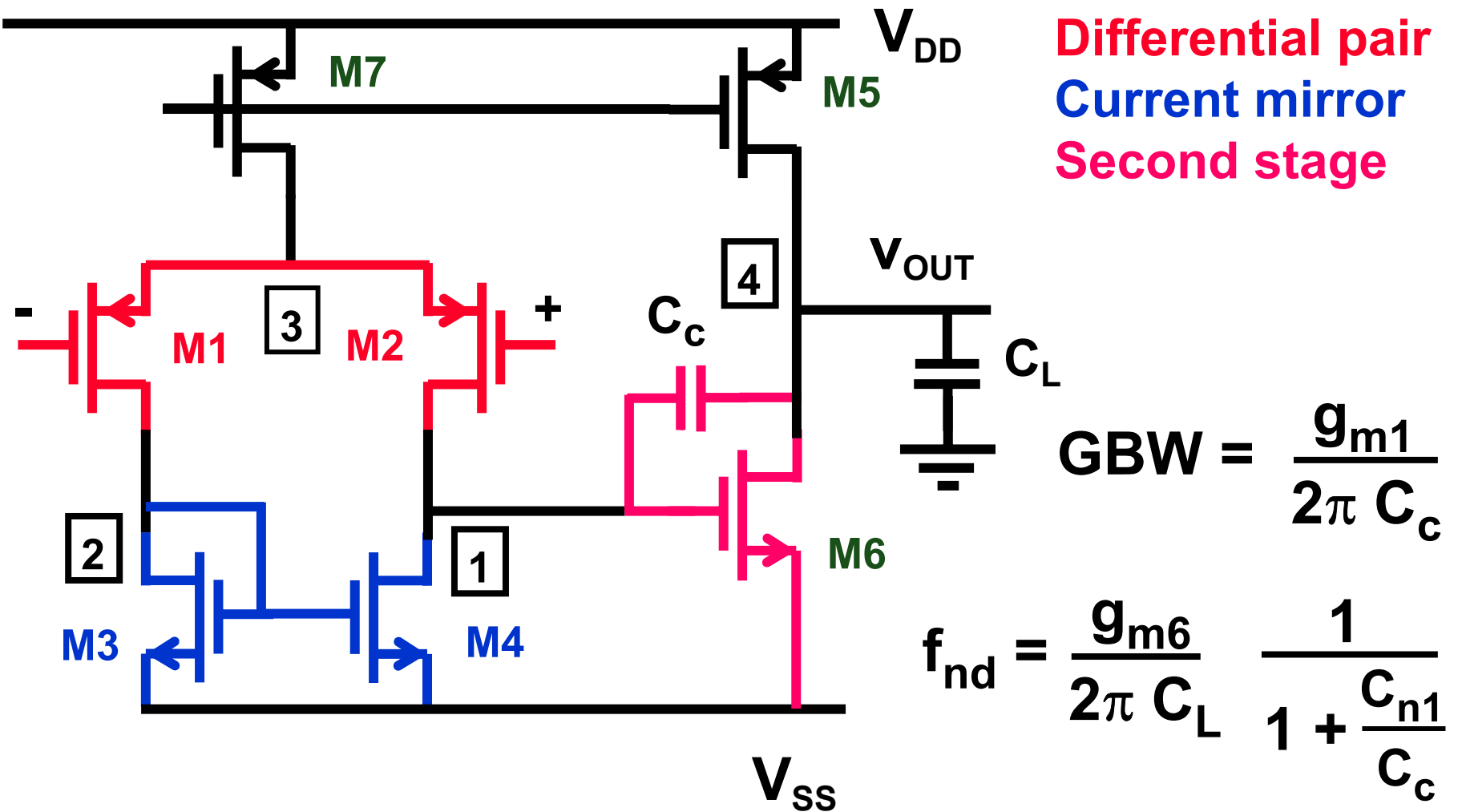

Miller BiCMOS OTA


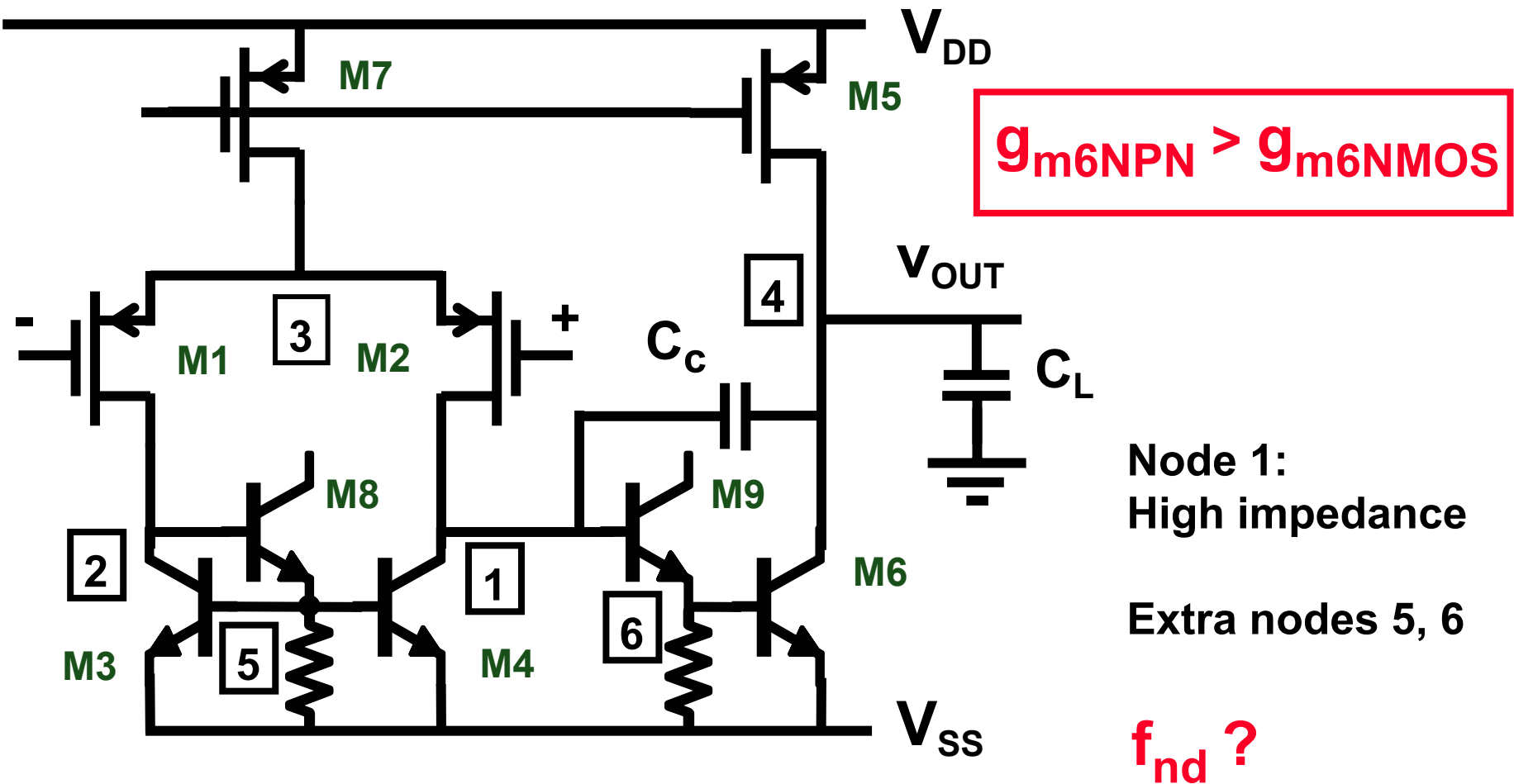



Table of contents

- Simple CMOS OTA
- CMOS Miller OTA
- Symmetrical CMOS OTA
- Folded cascode OTA
- Other opamps

Symmetrical CMOS OTA

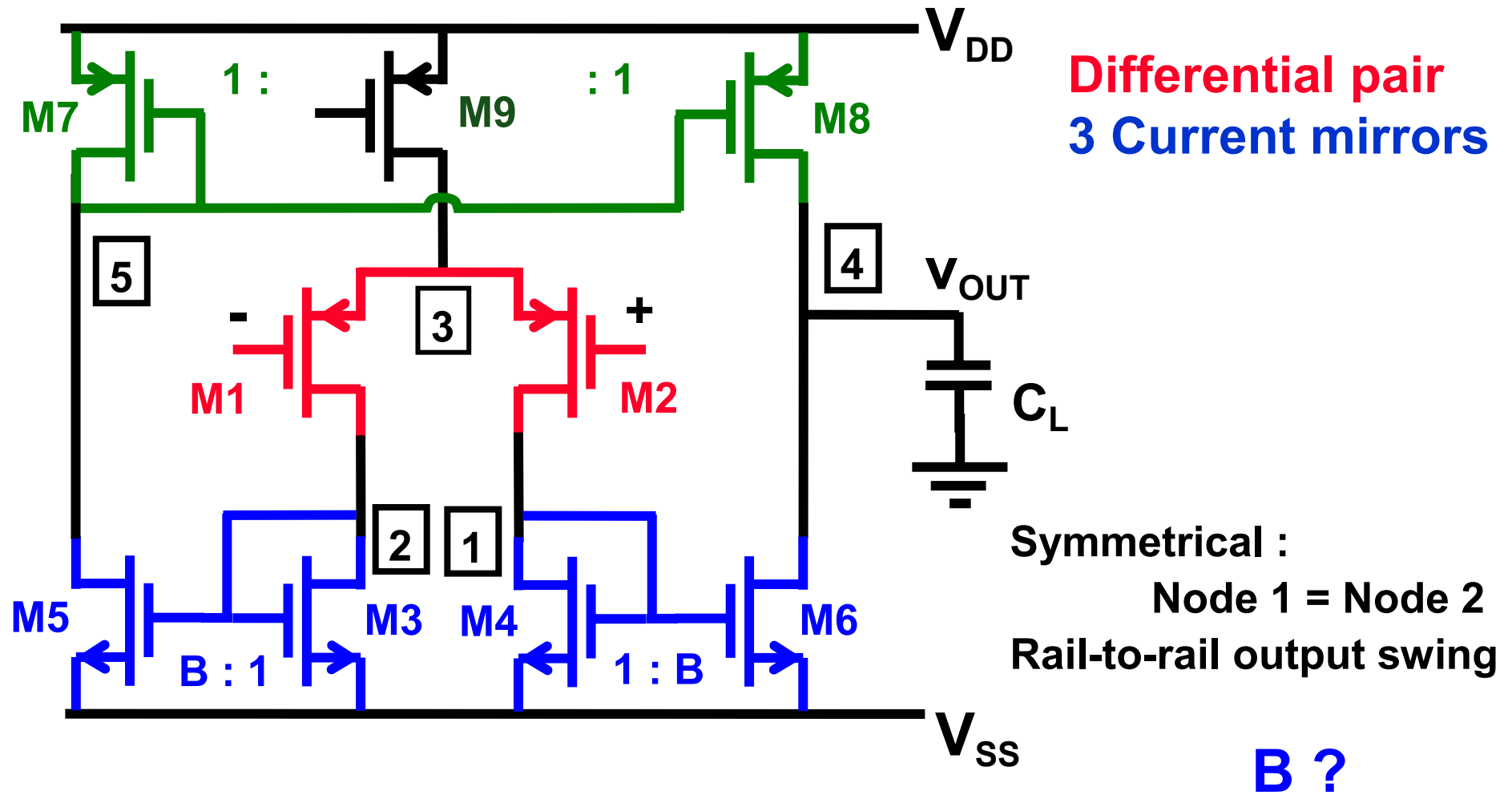

Symmetrical CMOS OTA : GBW

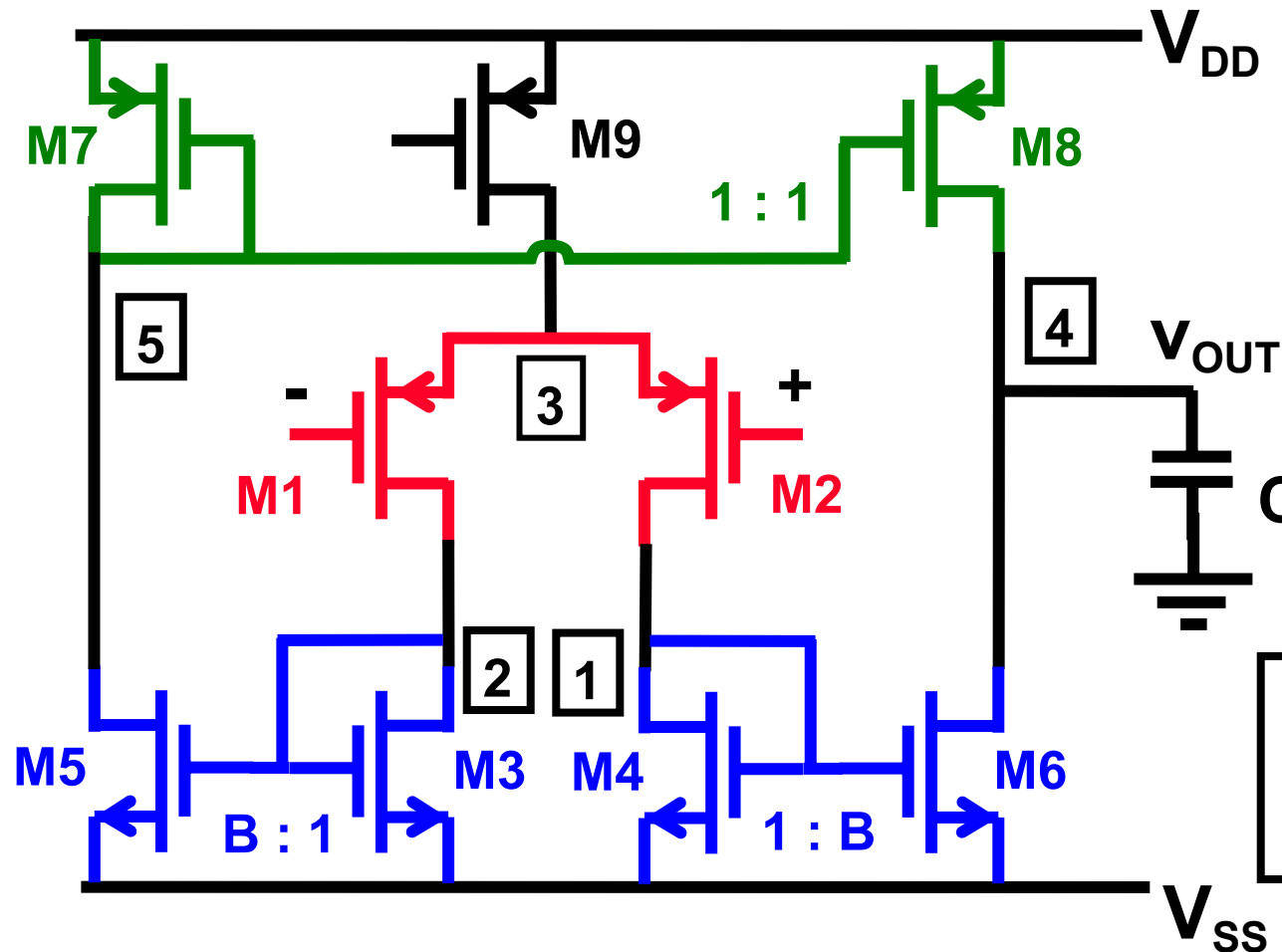

$$A_v = g_{m1} B R_{n4}$$

$$= \frac{2V_{En} L_6}{V_{GS1} - V_T}$$


$$\text{if } L_8 > L_6$$

$$BW = \frac{1}{2\pi R_{n4} C_L}$$



$$GBW = B \frac{g_{m1}}{2\pi C_L}$$

B ?

Symmetrical CMOS OTA : $f_{nd1,2}$

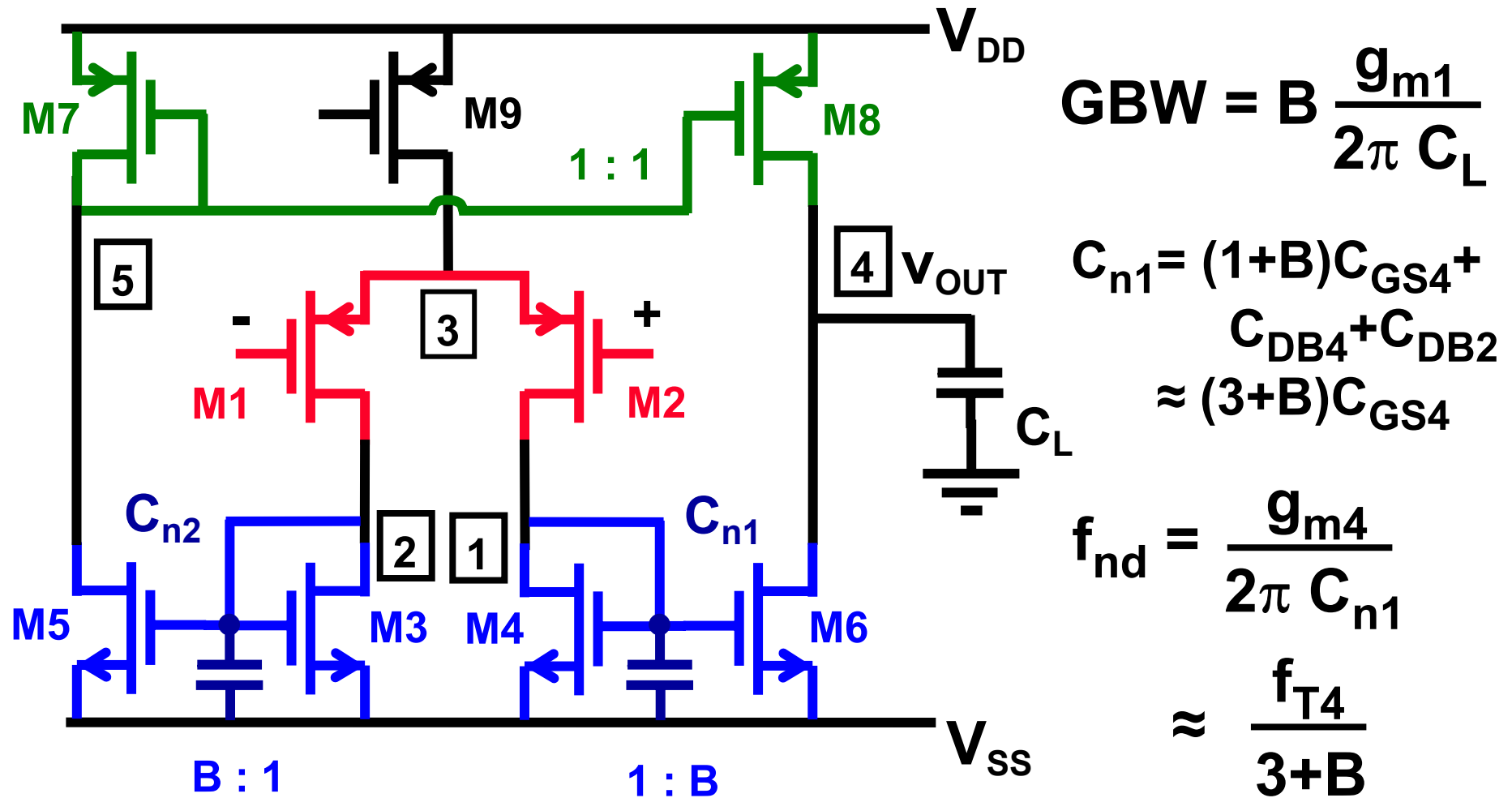


Pole at output of a differential pair

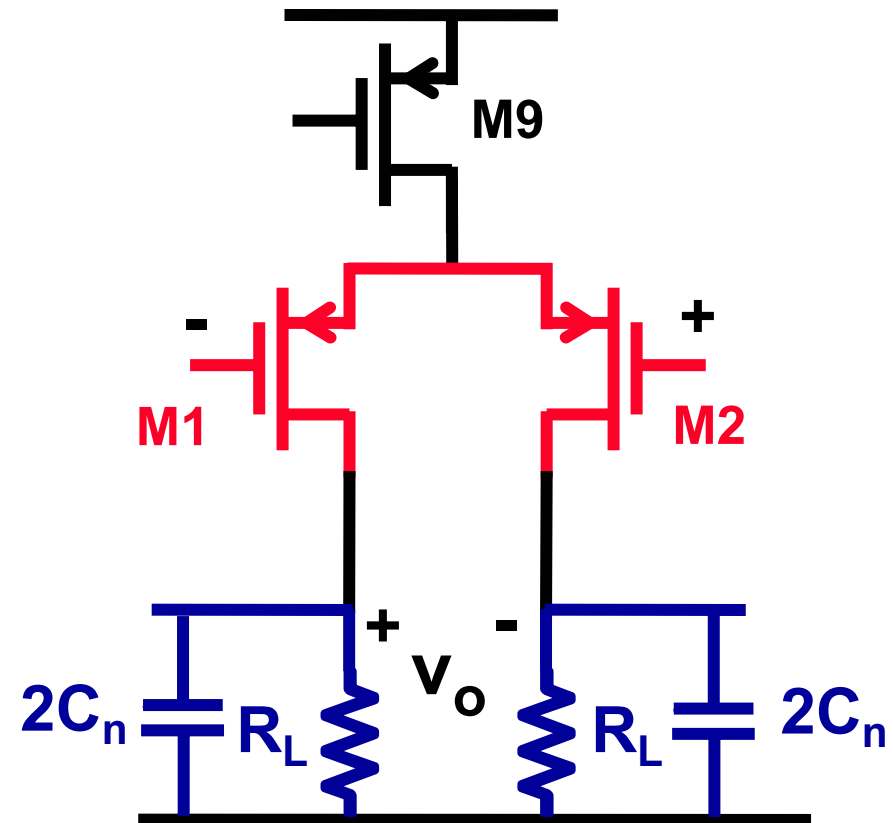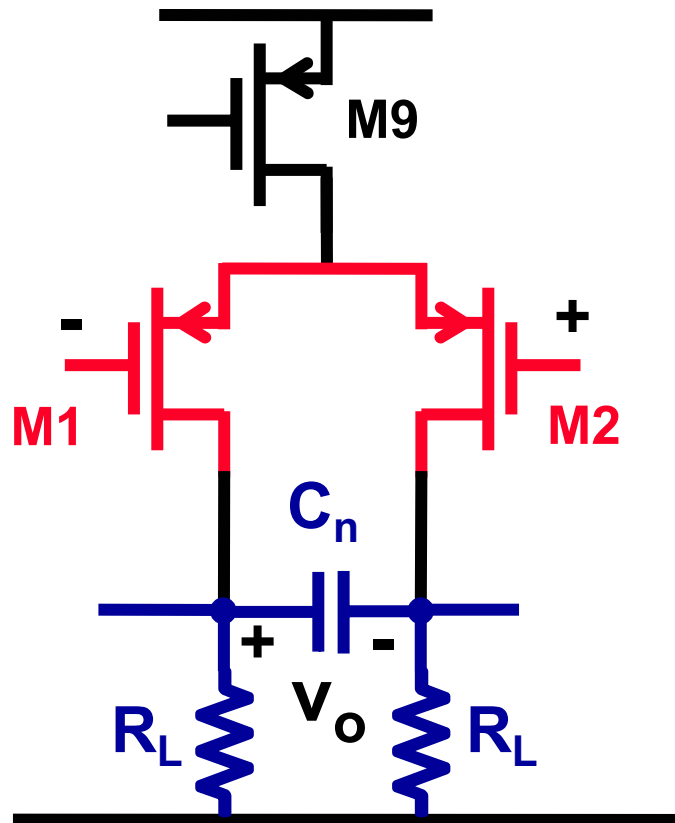


$$\text{One single pole : } f_p = \frac{1}{2\pi \cdot 2R_L C_n}$$

Symmetrical CMOS OTA : f_{nd5}

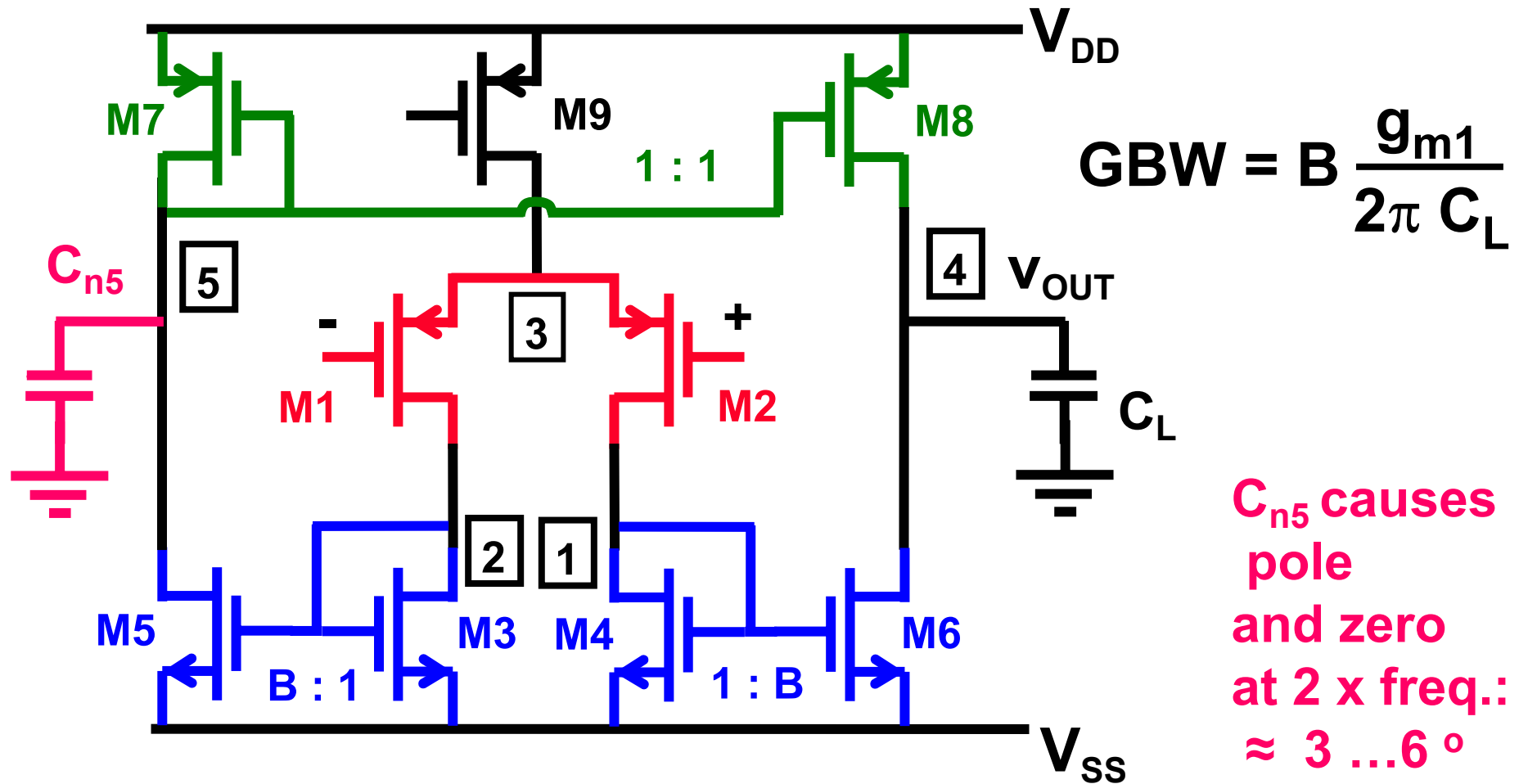

Symmetrical CMOS OTA : Design Example

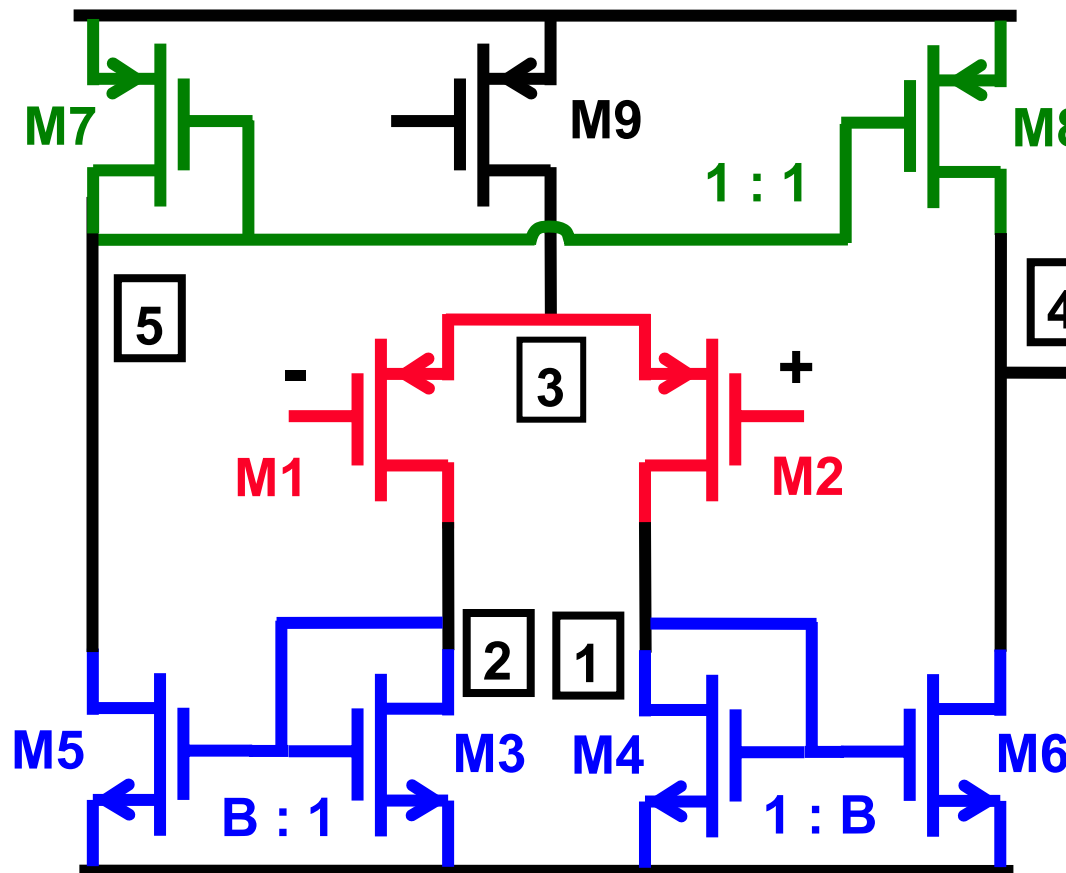

$$GBW = B \frac{g_{m1}}{2\pi C_L}$$

$$f_{nd} \approx \frac{f_{T4}}{3+B}$$

$$C_L = 2 \text{ pF}$$

$$GBW = 200 \text{ MHz}$$


$$V_{GS} - V_T = 0.5 \text{ V}; L = 1 \text{ } \mu\text{m}$$

$$f_{T4} = 5 \text{ GHz}$$

$$f_{nd} = 0.6 \text{ GHz}$$

$$B \approx 5$$

Symmetrical BiCMOS OTA

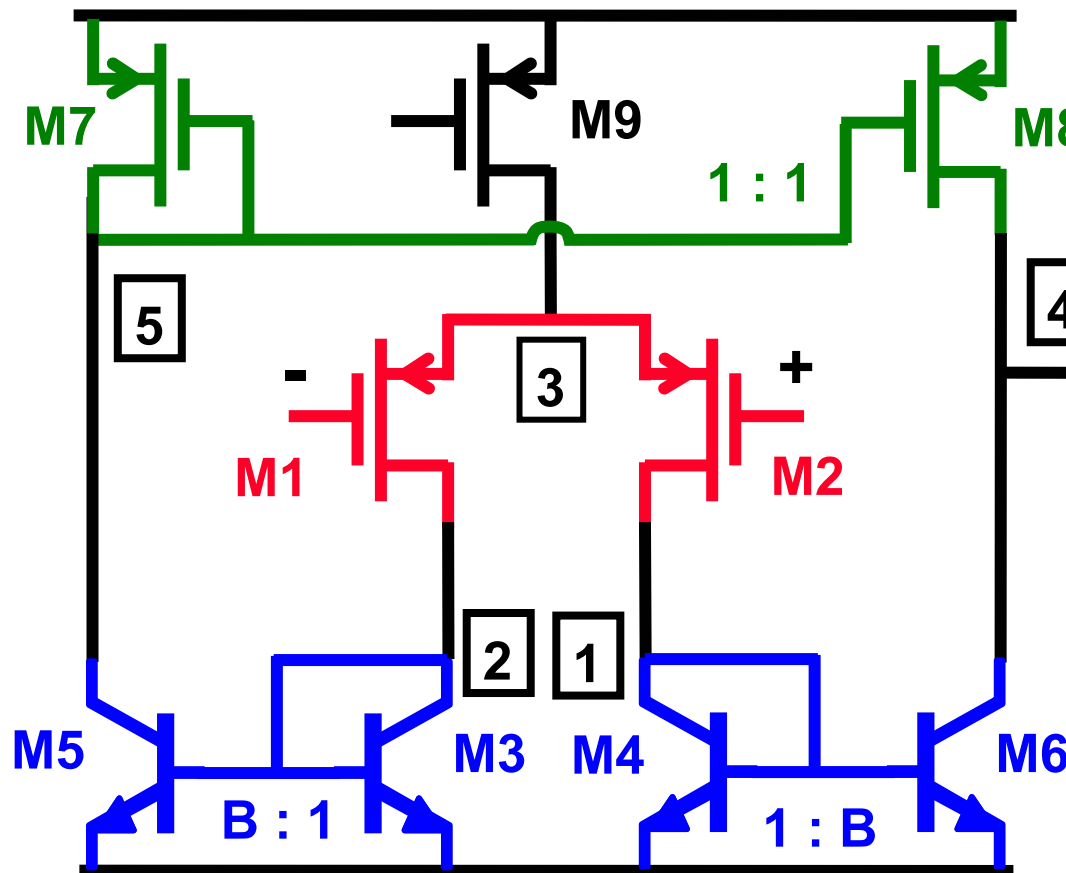

$$\text{GBW} = B \frac{g_{m1}}{2\pi C_L}$$


$$f_{nd} \approx \frac{f_{T4}}{3+B}$$

$g_{m4NPN} > g_{m4NMOS}$

$C_{CS4NPN} > C_{DB4NMOS}$

BiCMOS > CMOS ?

Symmetrical CMOS OTA with cascodes

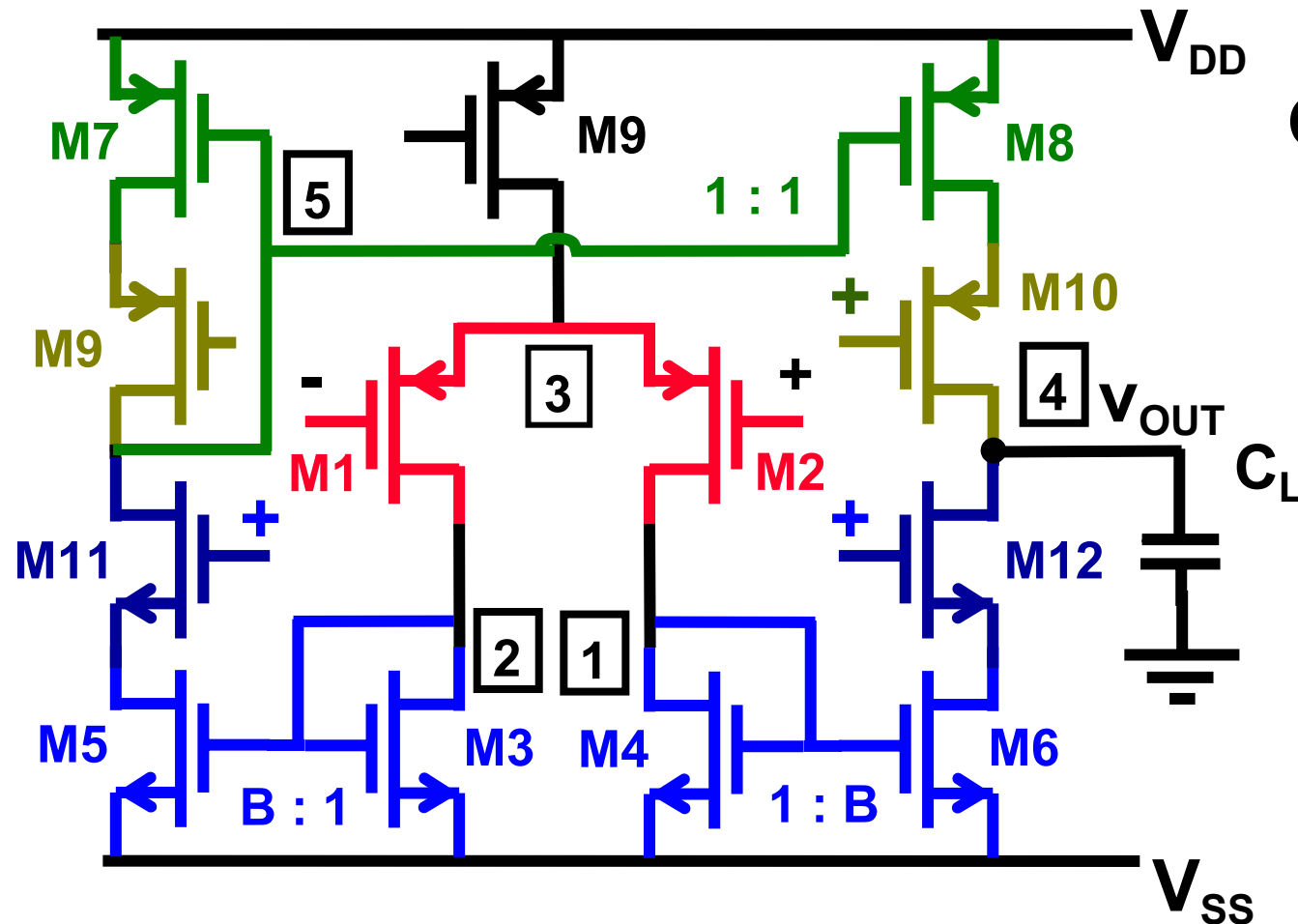


$$GBW = B \frac{g_{m1}}{2\pi C_L}$$

GBW same
but
 A_v is 100* x
higher !!!


* $g_m r_o \approx 100$

Symmetrical Miller CMOS OTA

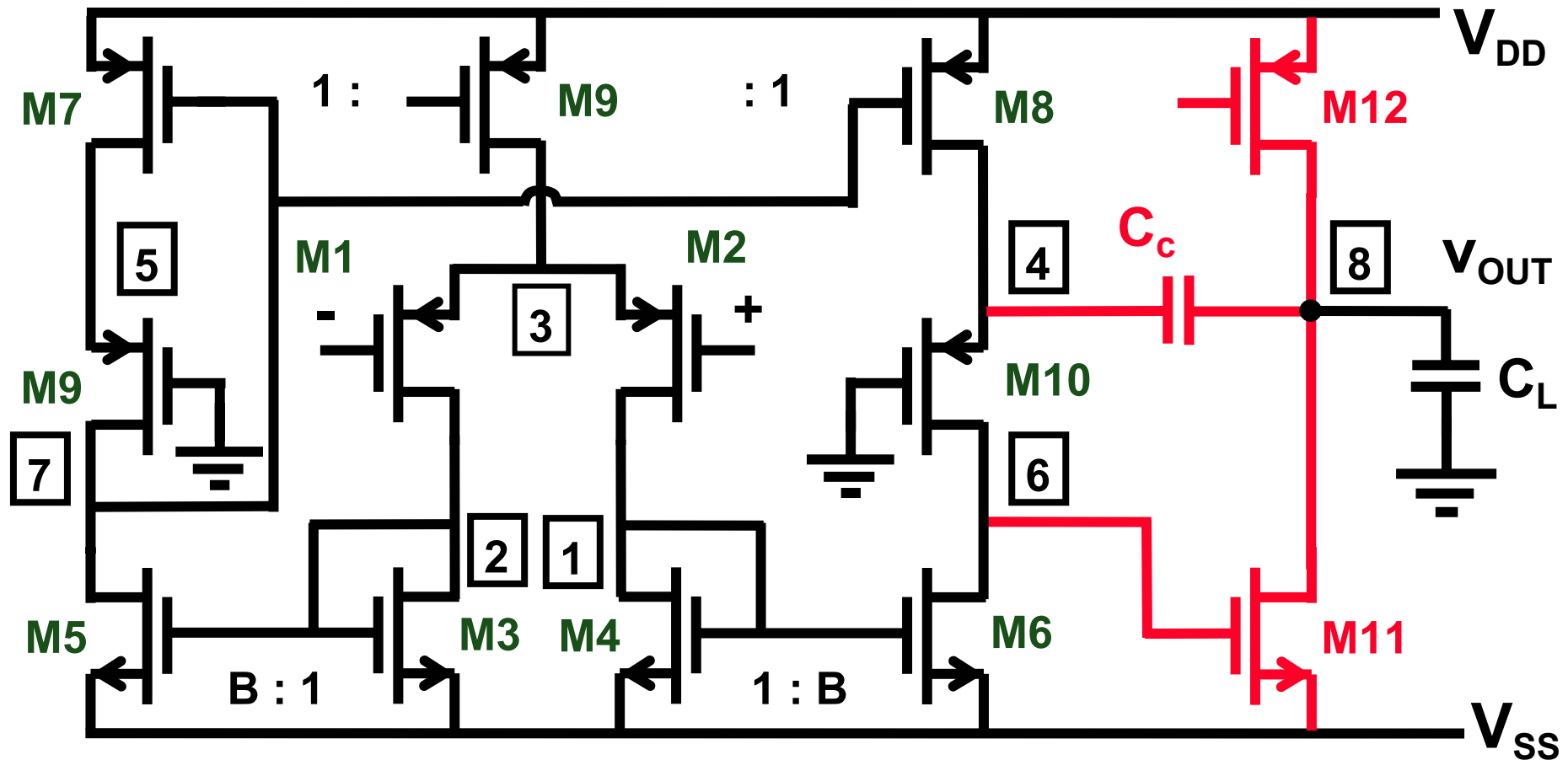

$$GBW = B \frac{g_{m1}}{2\pi C_c} \quad \text{No zero!} \quad \square$$

Bipolar transistor symmetrical amplifier

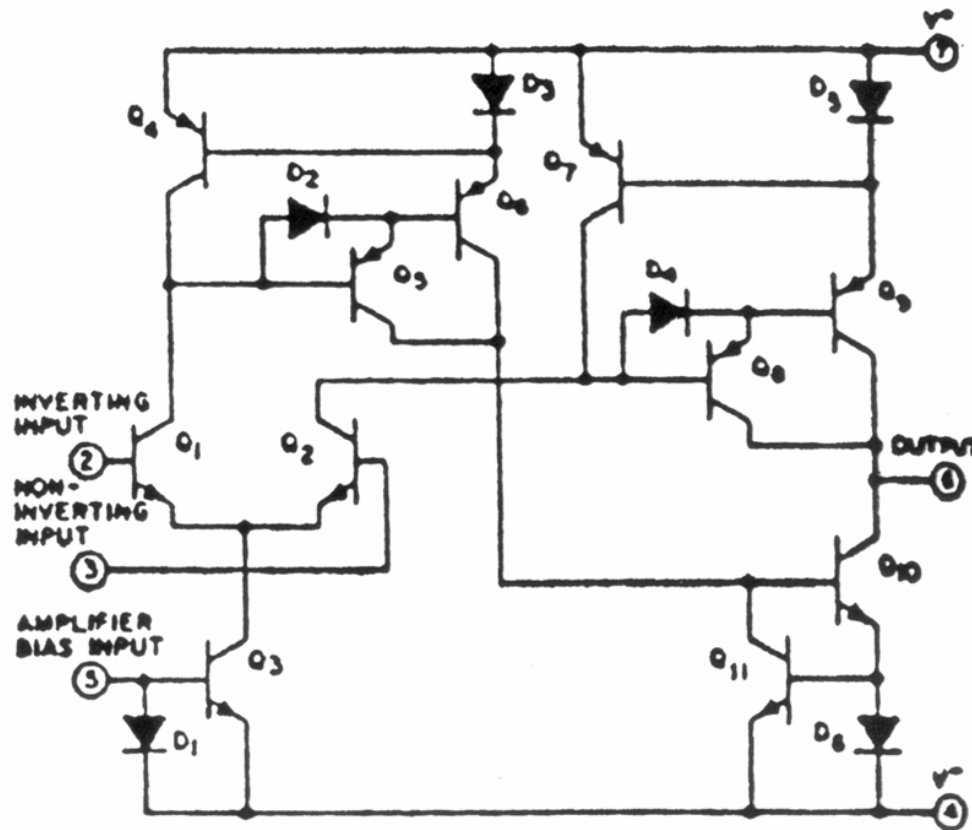


CA3080

0.12 MHz

1.2 V/μs

I₃ = 10 μA

Gain enhancement by current starving

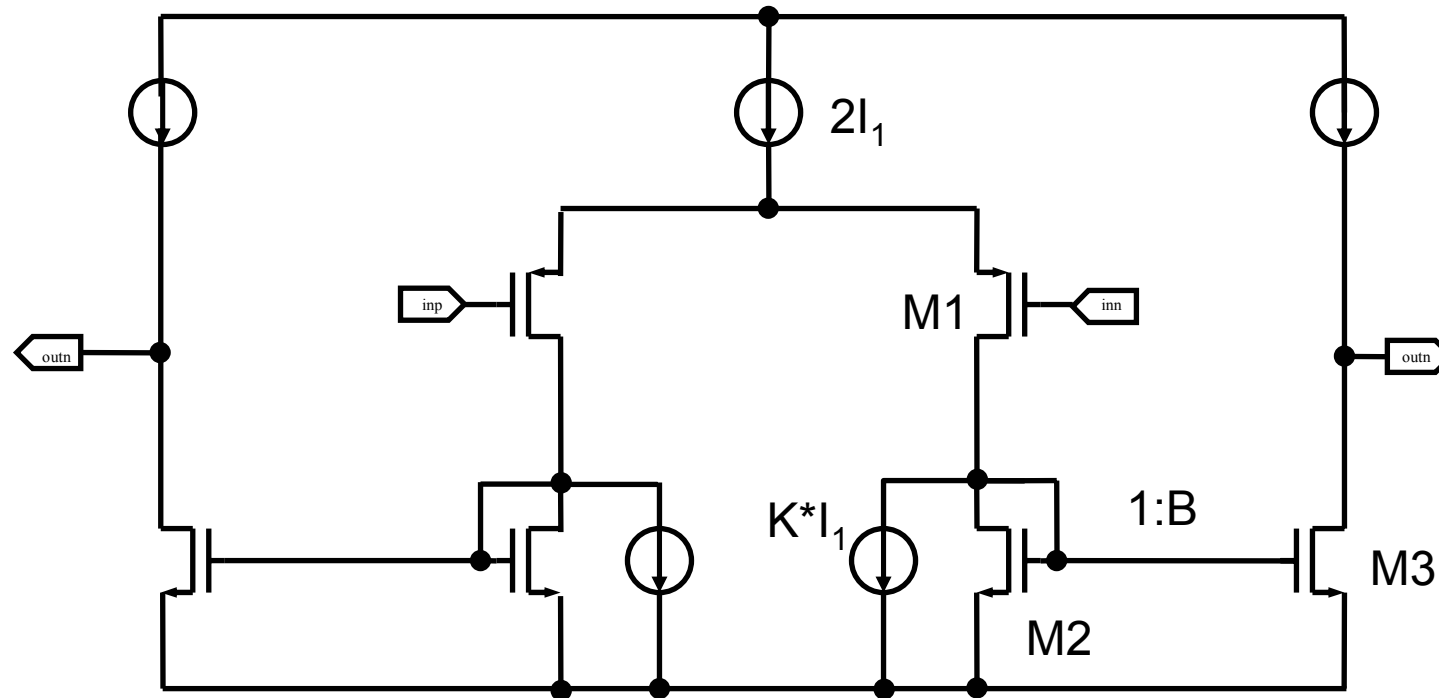


$$A = \frac{2}{(1 - k)(V_{GS} - V_T)_1 \cdot \lambda_3} = \frac{A_0}{1 - k}$$

Yao, ..., JSSC Nov.04, 1809-1818


Table of contents

- **Simple CMOS OTA**
- **CMOS Miller OTA**
- **Symmetrical CMOS OTA**
- **Folded cascode OTA**
- **Other opamps**


Folded cascode CMOS OTA

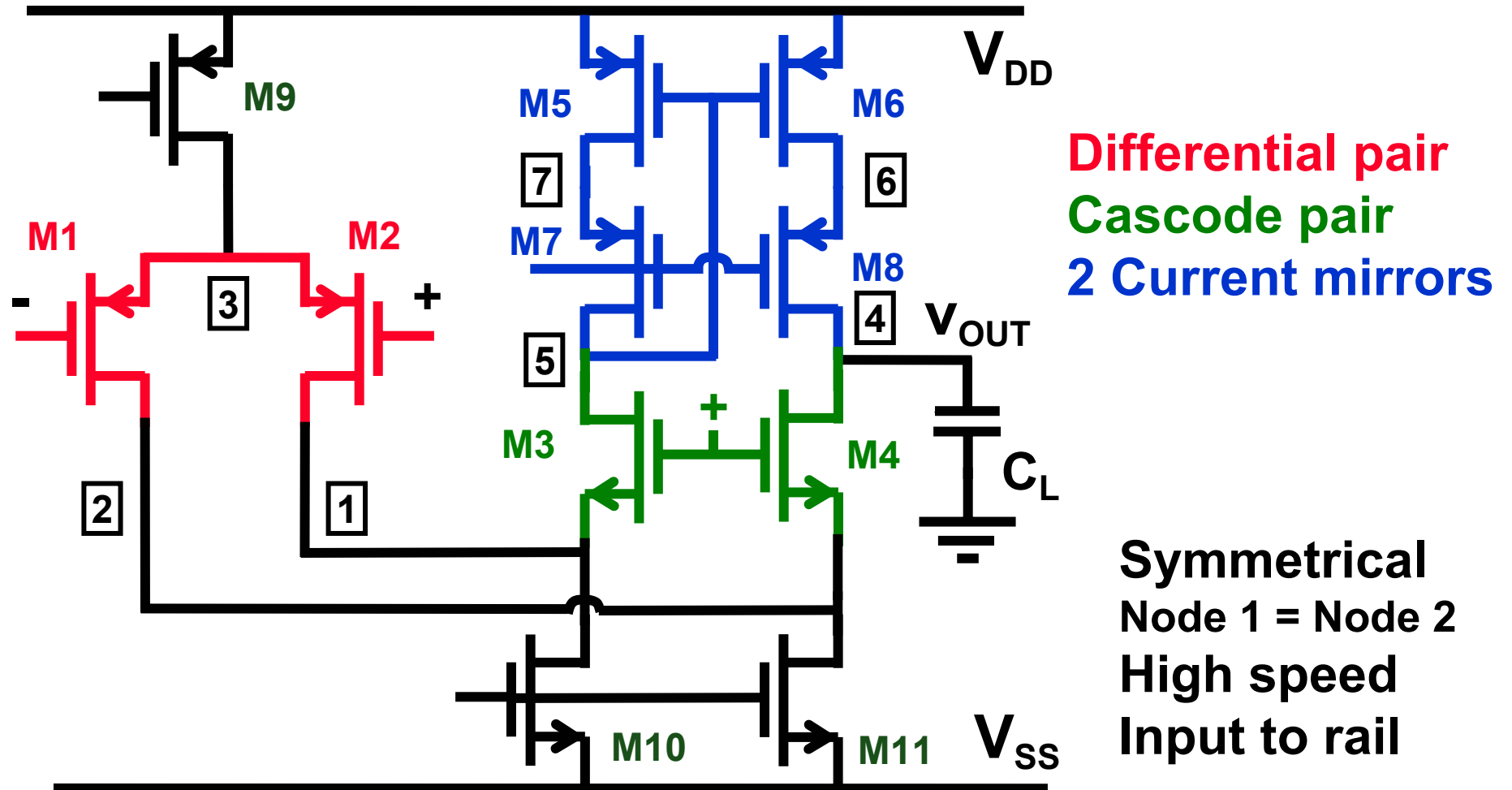


Folded cascode CMOS OTA : DC

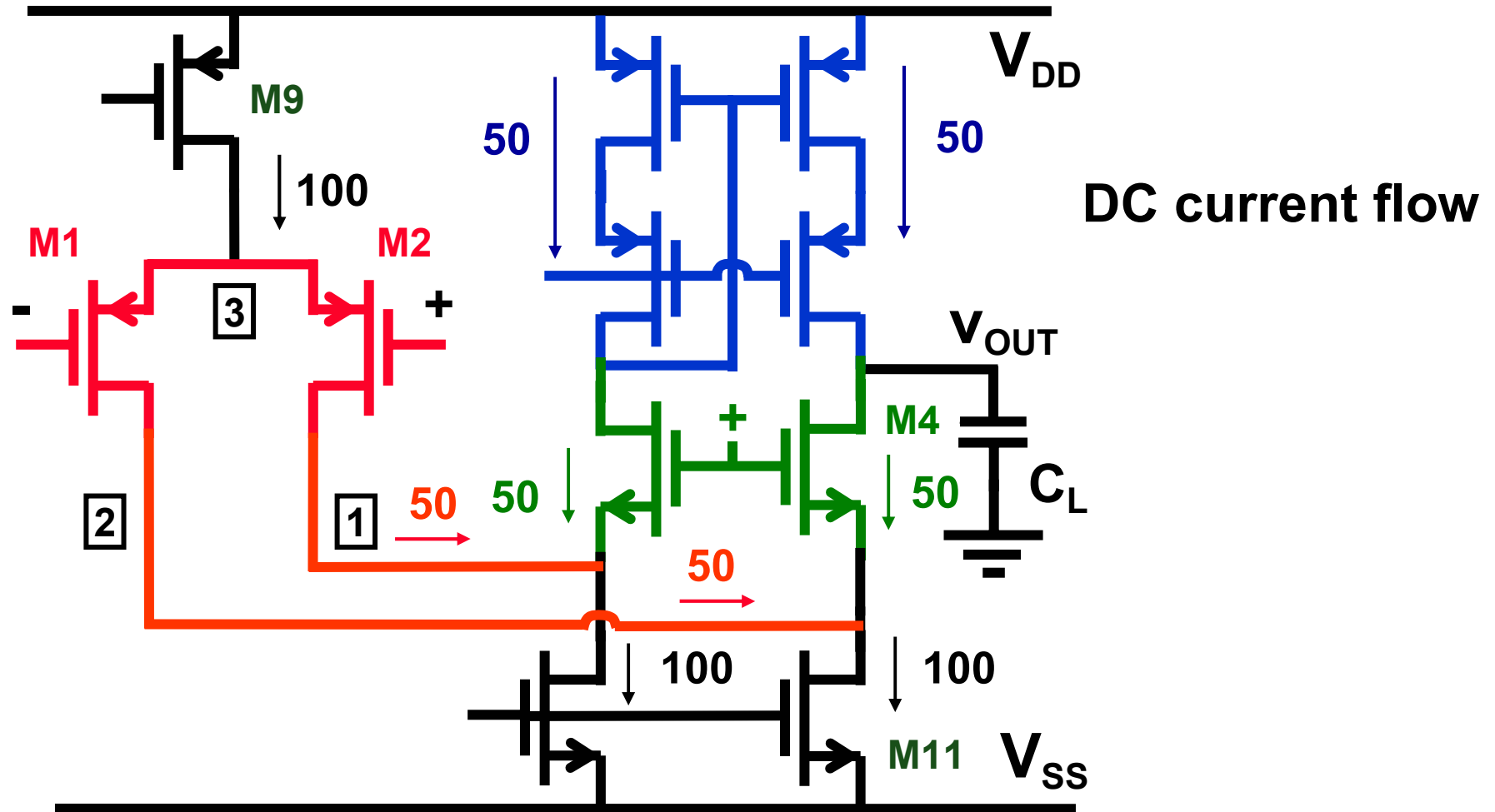

Folded cascode CMOS OTA :

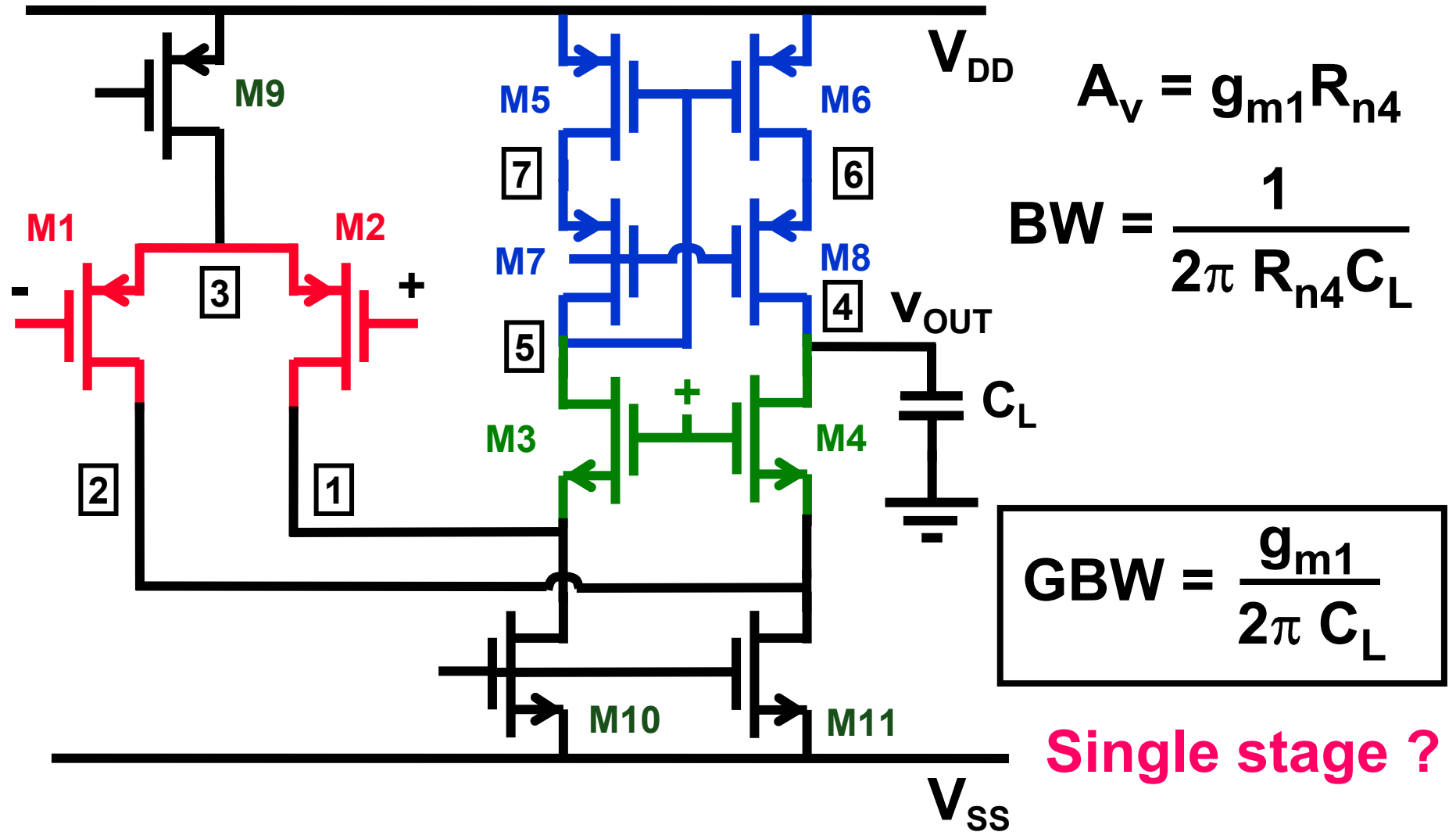

Folded cascode CMOS OTA :

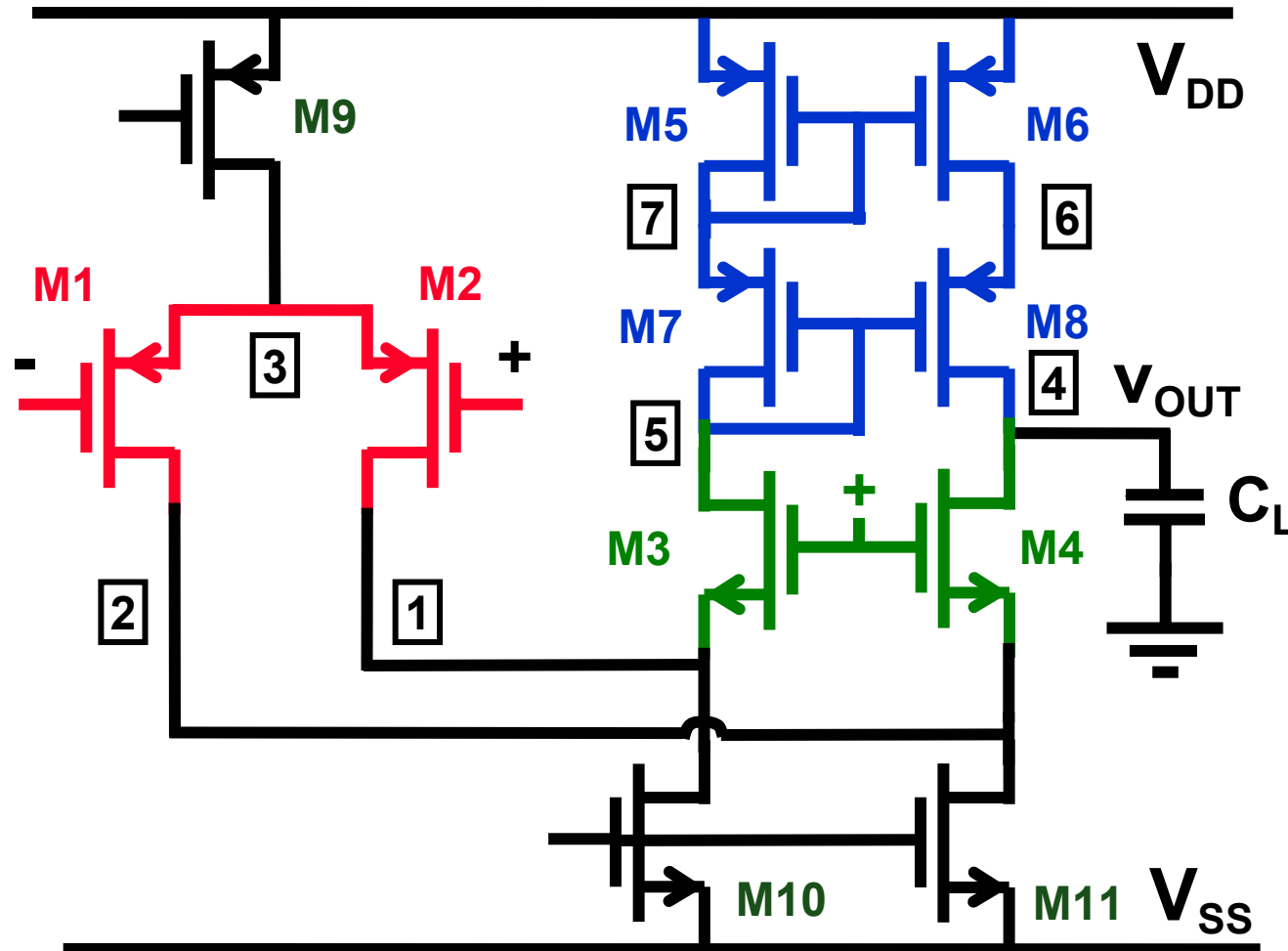

$$GBW = \frac{g_{m1}}{2\pi C_L}$$


$$C_{n1} = C_{GS3} + C_{DB1} + C_{DB10} \approx 3 C_{GS3}$$

$$f_{nd} = \frac{g_{m3}}{2\pi C_{n1}}$$

$$\approx \frac{f_{T3}}{3} \text{ Hi !}$$

□

Folded cascode CMOS OTA :

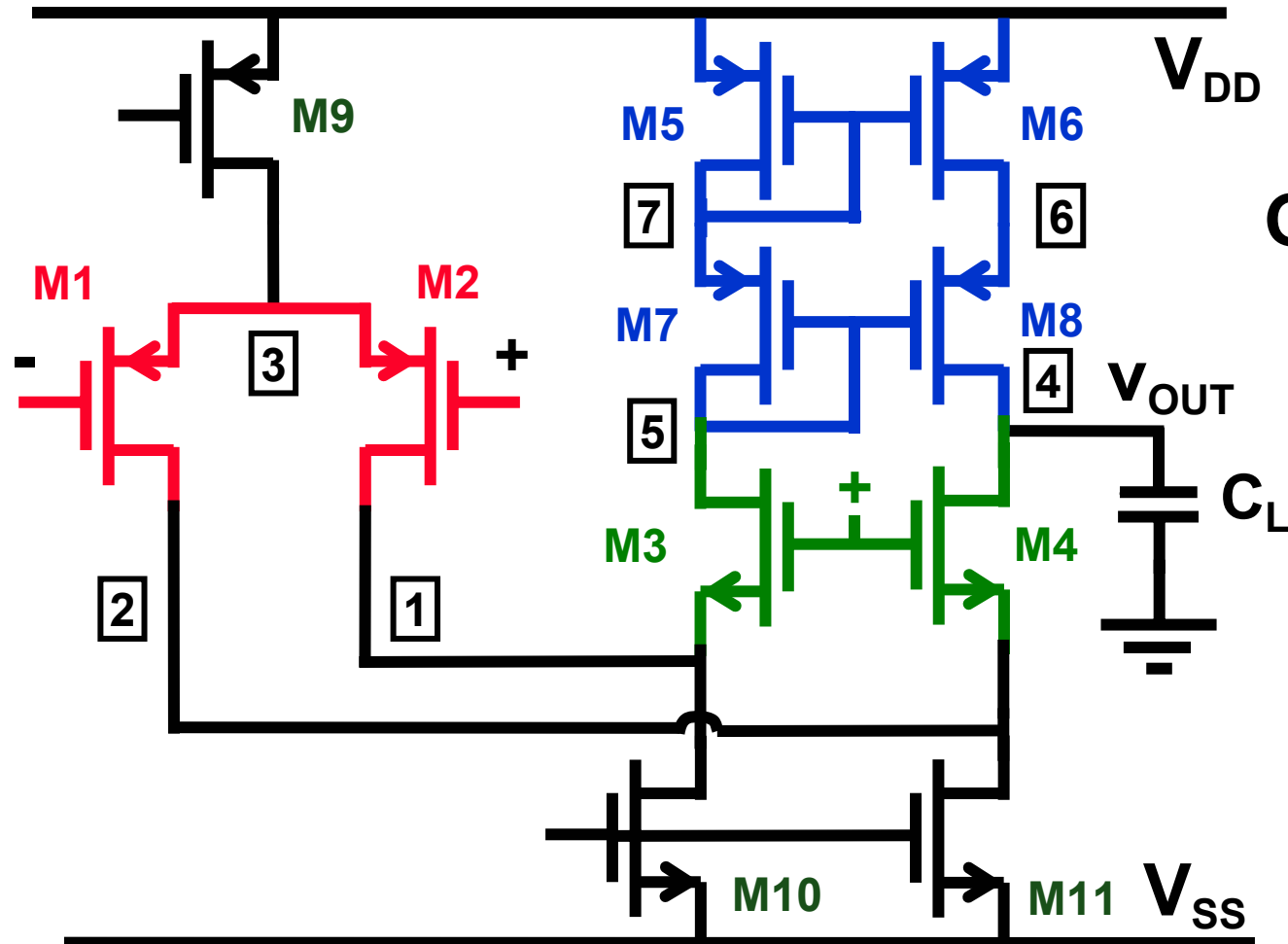


$$GBW = \frac{g_{m1}}{2\pi C_L}$$

C_{n5}, C_{n7}, C_{n6}
Cause pole
and zero
at 2 x freq.:
 $\approx 5 \dots 10^\circ$

Ref Mallya, JSSC Dec 89, 1737-1740

Folded cascode BiCMOS OTA

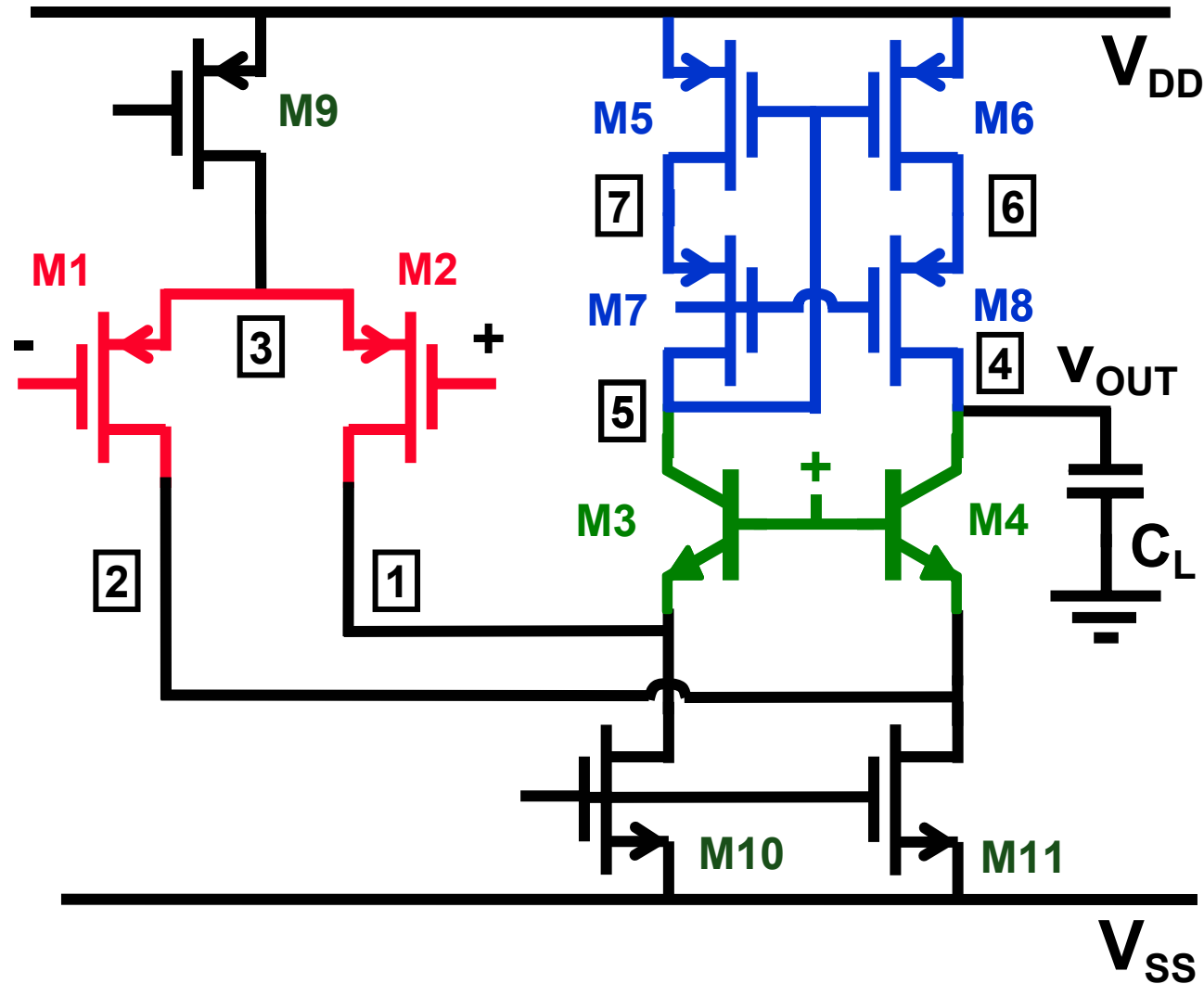


$$GBW = \frac{g_{m1}}{2\pi C_L}$$

$$f_{nd} = \frac{g_{m3}}{2\pi C_{n1}} \approx \frac{f_{T3NPN}}{3}$$


Higher !



Folded cascode OTA: input to V_{SS} rail

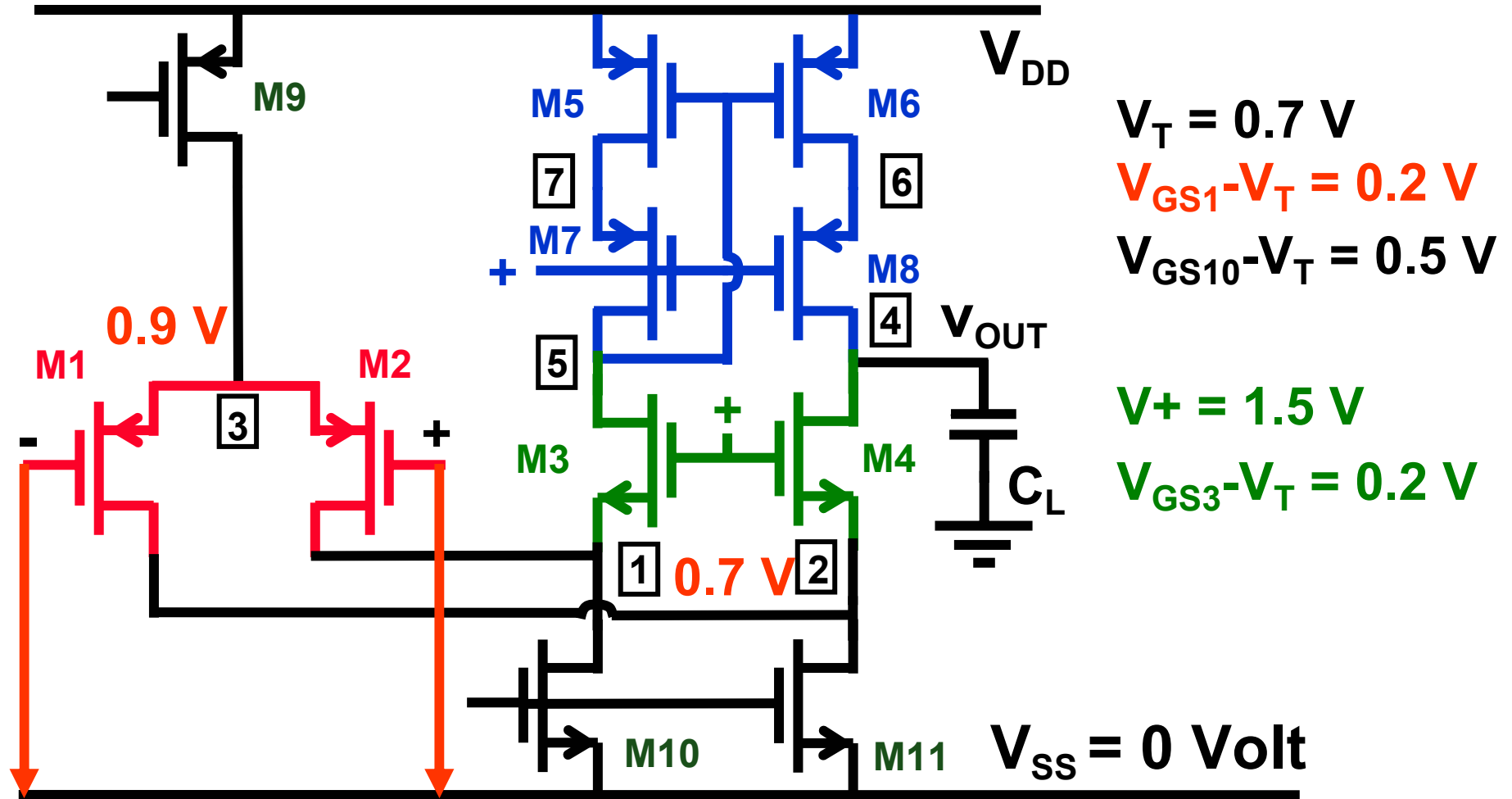


Folded cascode OTA with 2nd stage

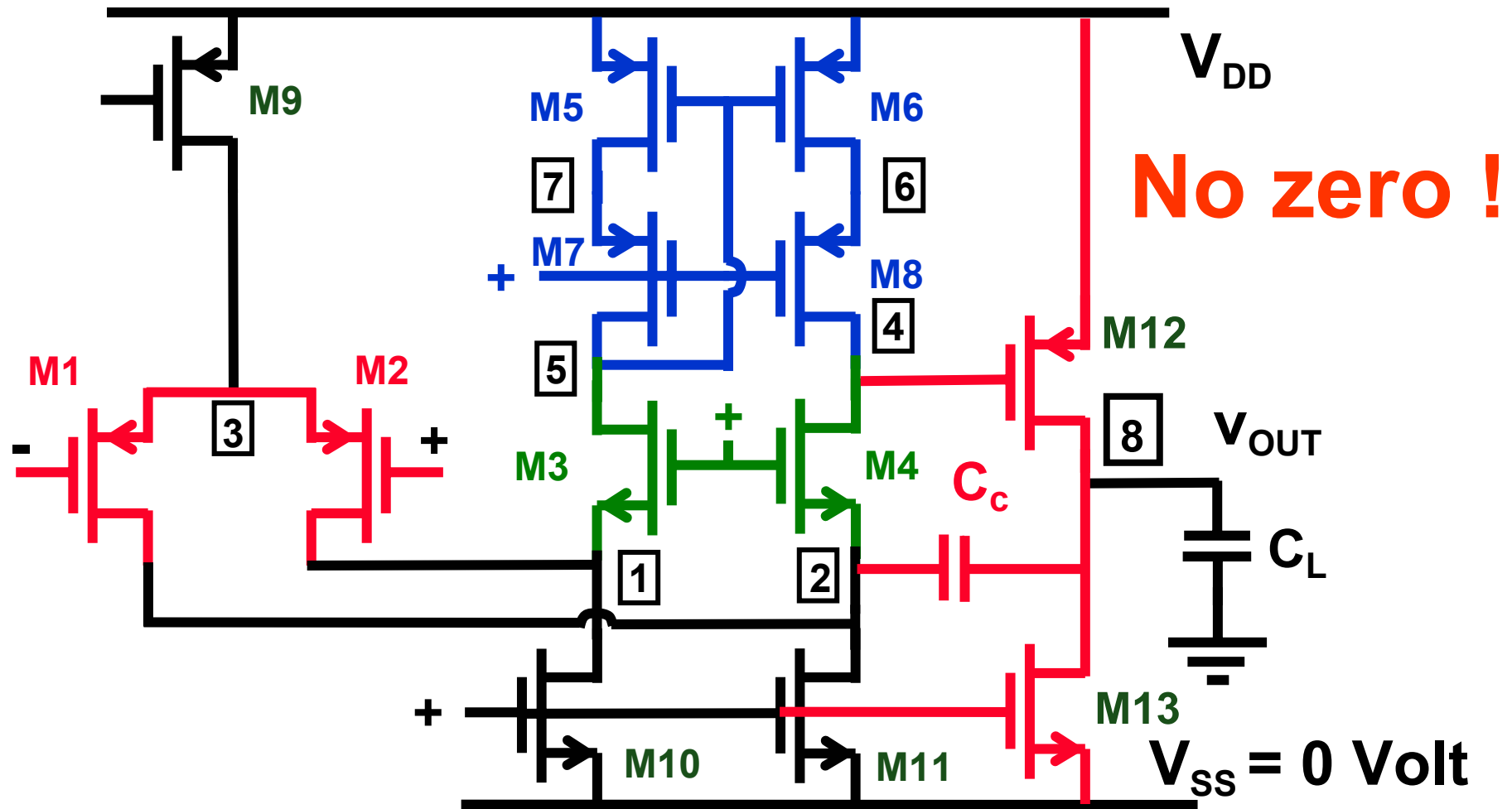


Ribner, JSSC Dec.84, 919-925



Conventional folded cascode OTA

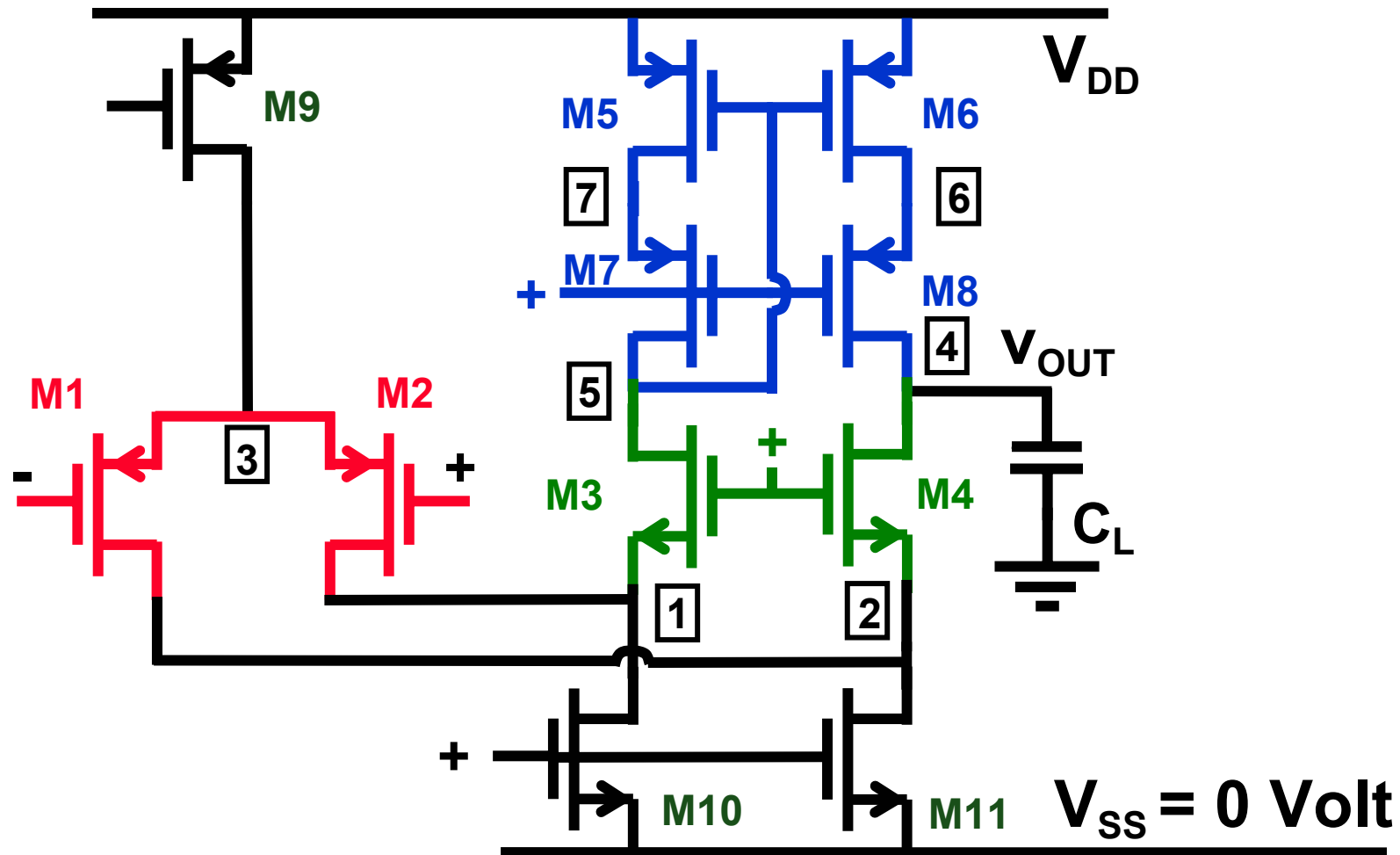

Alternative folded cascode OTA

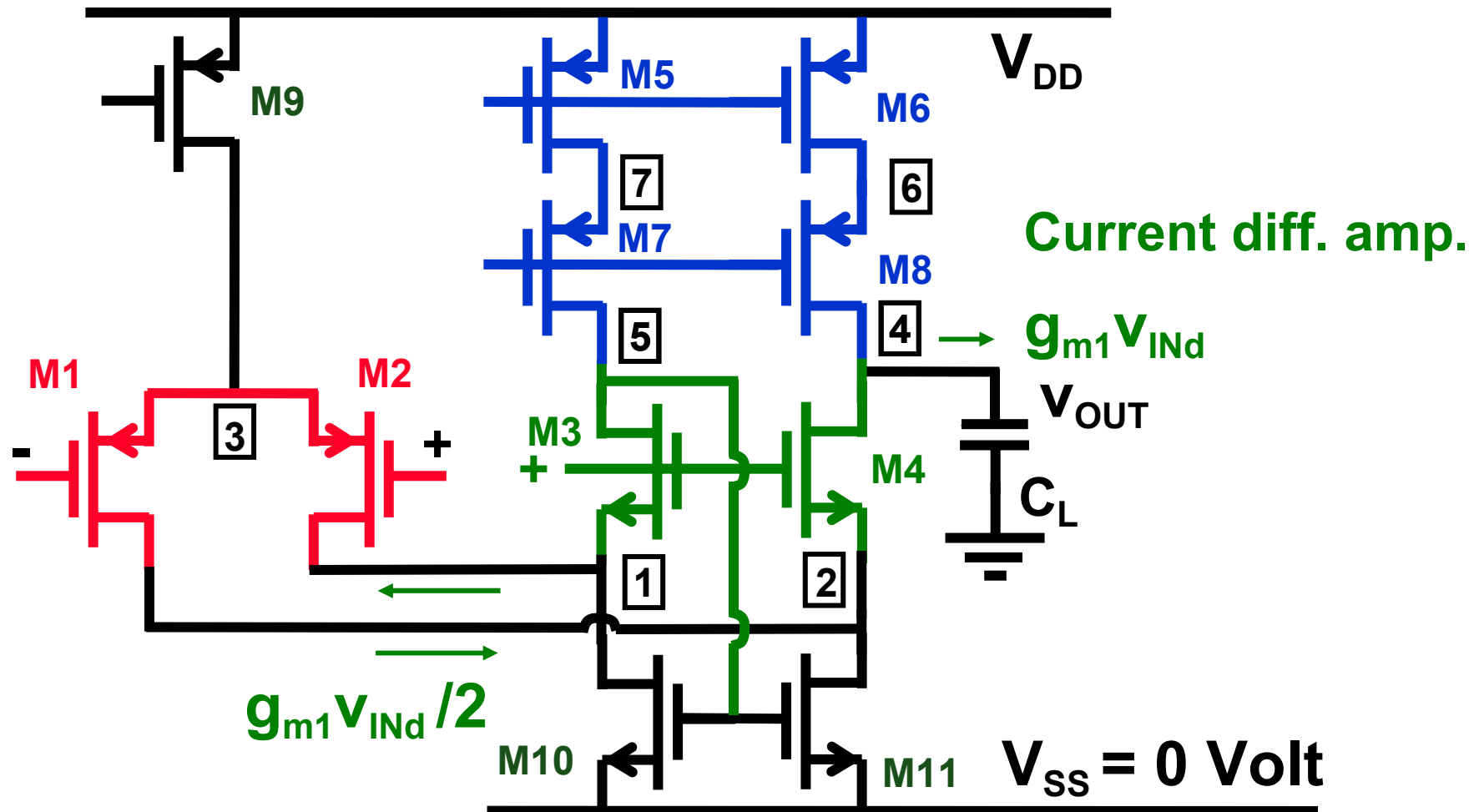

Comparison amplifiers


	I_{TOT} mA	$\frac{\overline{dv_{in,eq}^2}}{8/3 kT df}$ g_{m1}	Swing
Volt. OTA (4 Ts)	0.25	4	avg.
Symmetrical (B= 3)	0.33	16	max.
Telescopic	0.25	4	small
Folded casc.	0.5	4	avg.
Miller 2-stage ($C_L/C_c = 2.5$)	1.1	4	max.

GBW = 100 MHz $C_L = 2$ pF $V_{GS} - V_T = 0.2$ V Fully differential

Table of contents

- **Simple CMOS OTA**
- **CMOS Miller OTA**
- **Symmetrical CMOS OTA**
- **Folded cascode OTA**
- **Other opamps**

Sub-1 Volt OTA

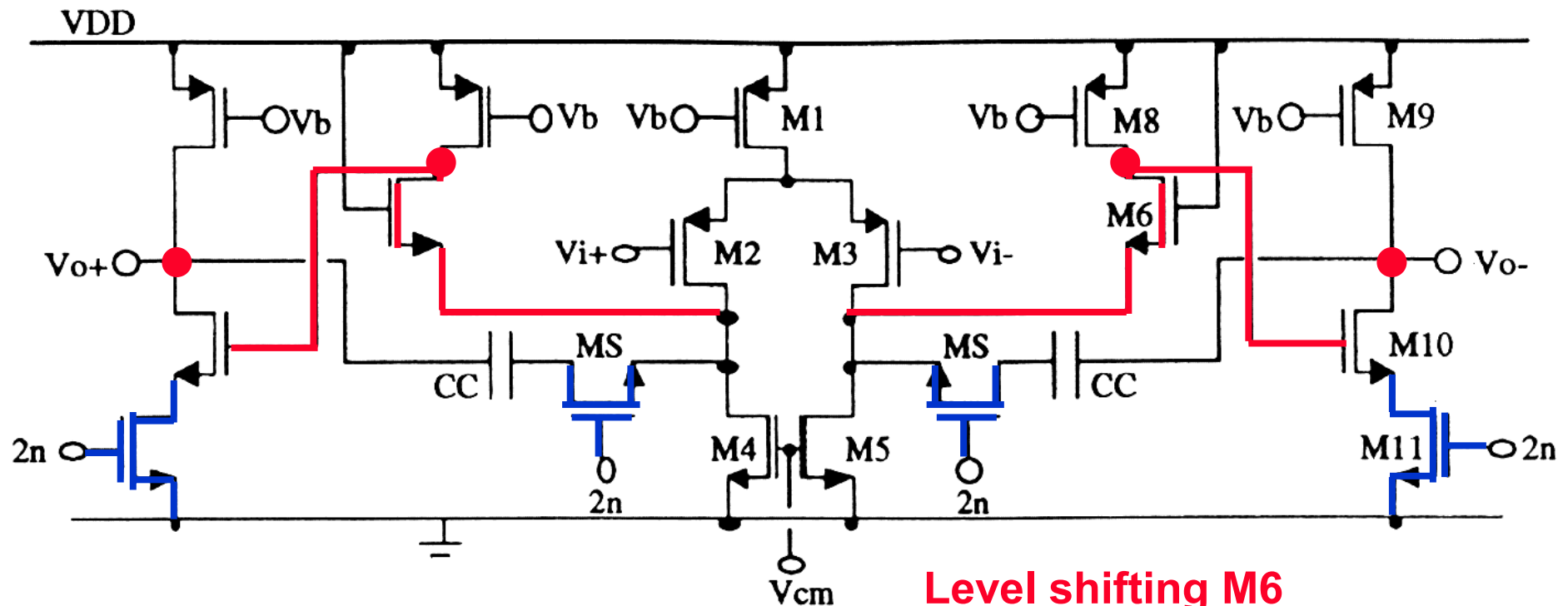

1 V 80 μ W (min: $V_T + 2V_{DSsat}$)

Fully differential

75 dB 30 MHz (0.1 pF)

< 100 ns


Level shifting M6

4 Switches 2n :

Only 2nd stage switched off !

Baschirotto, .. JSSC Dec.97, pp.1979-1986

LM 4250

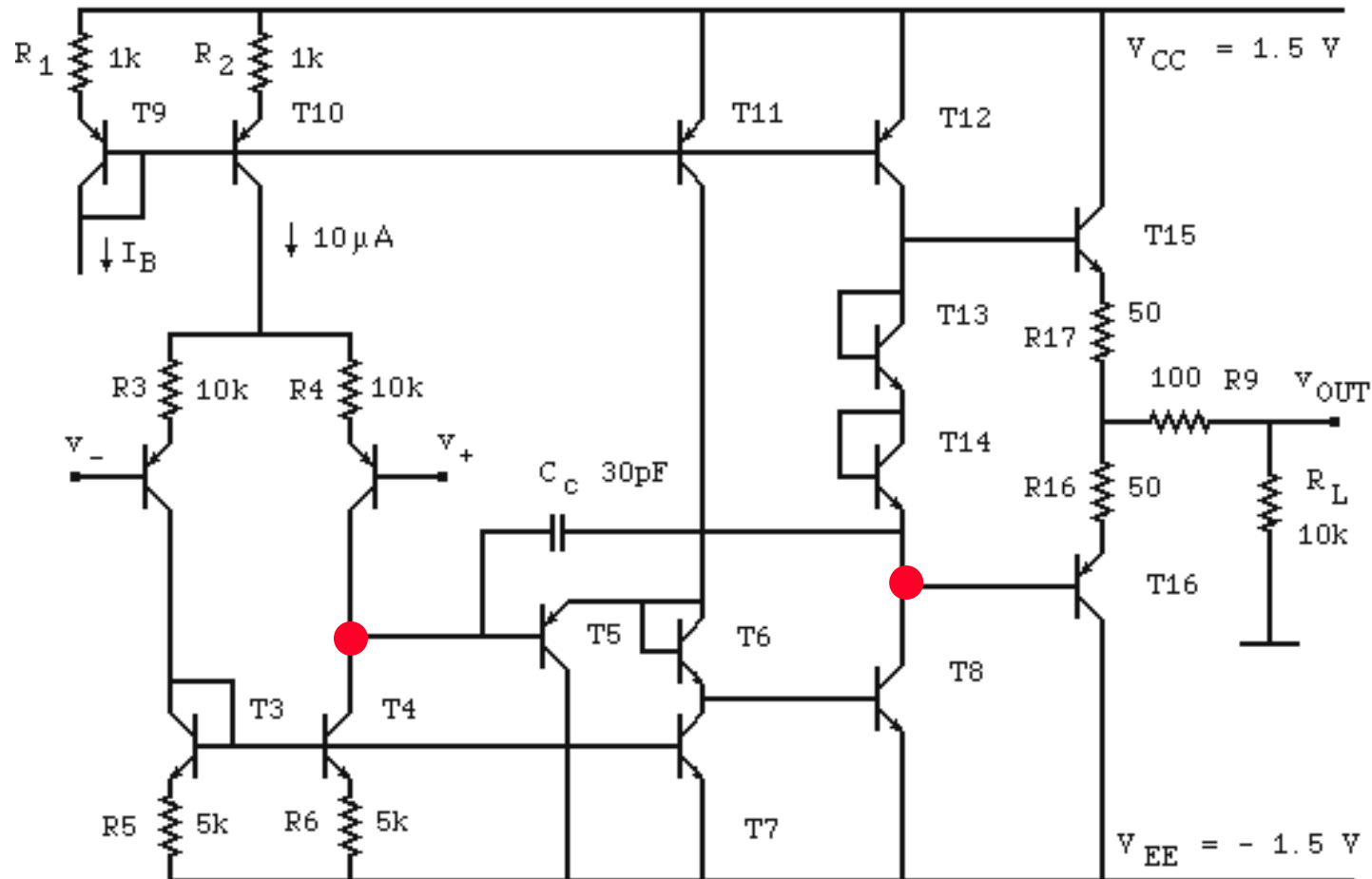

GBW = 0.25 MHz


SR = 0.2 V/ μs

$I_1 = 10\text{ }\mu\text{A}$


$I_{TOT} = 90\text{ }\mu\text{A}$

38 nV_{RMS}/ $\sqrt{\text{Hz}}$

Increased input transconductance - 1

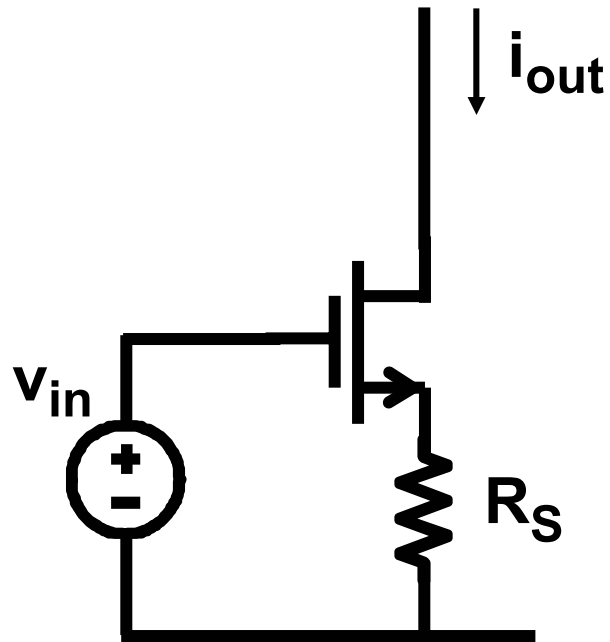


$$g_{mR} = \frac{g_m}{1 + g_m R_S}$$

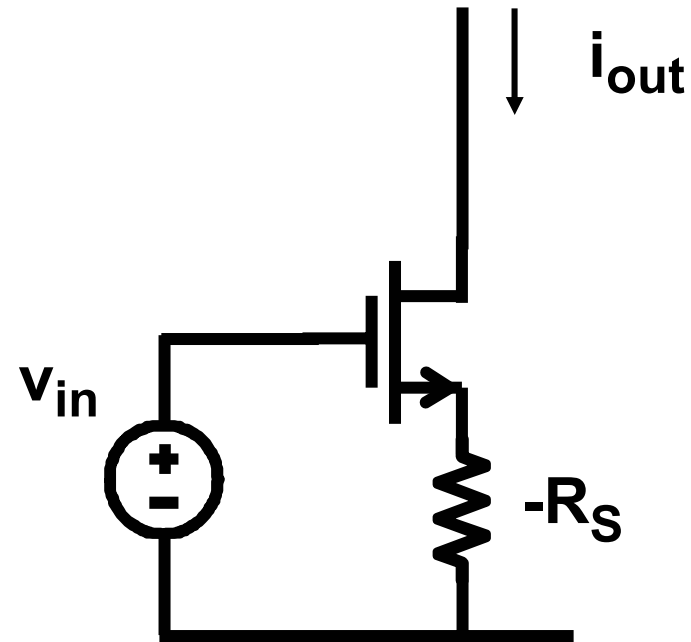


$$g_{mR} = \frac{g_m}{1 - g_m R_S}$$

Increased input transconductance - 2

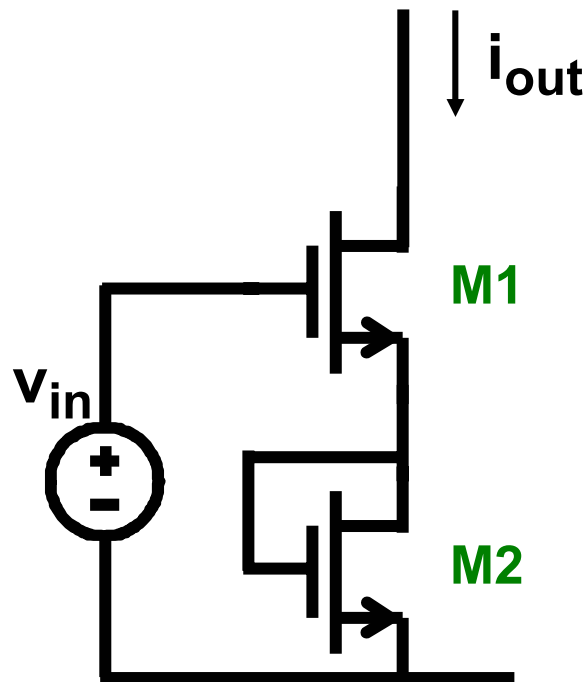

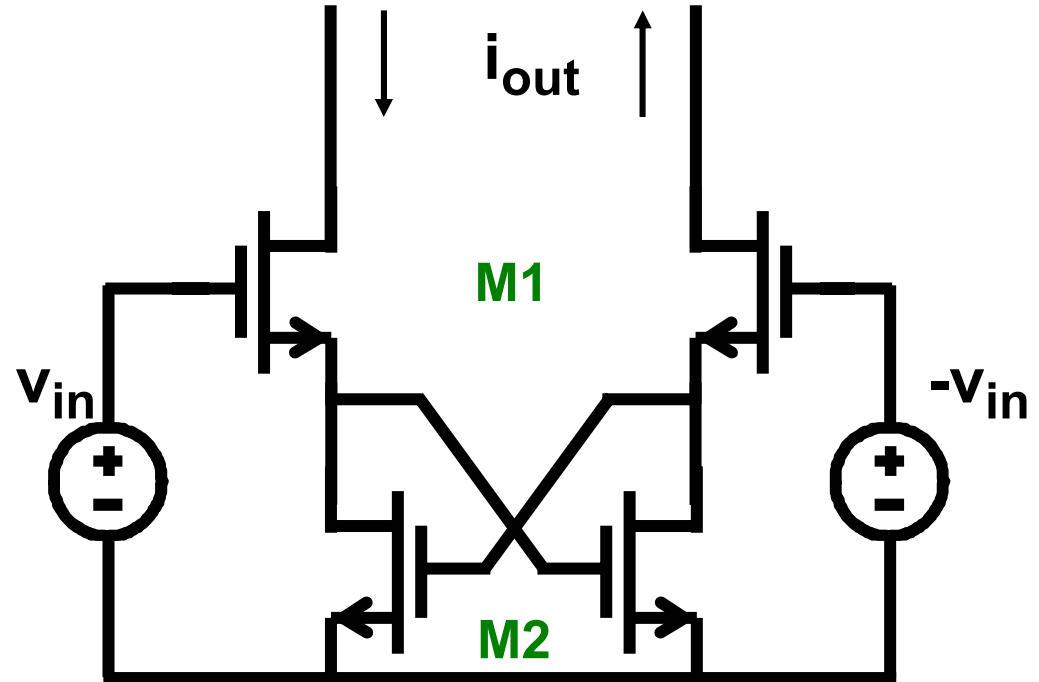
$$g_m = \frac{g_{m1}}{1 + \frac{g_{m1}}{g_{m2}}}$$



$$g_m = \frac{g_{m1}}{1 - \frac{g_{m1}}{g_{m2}}}$$

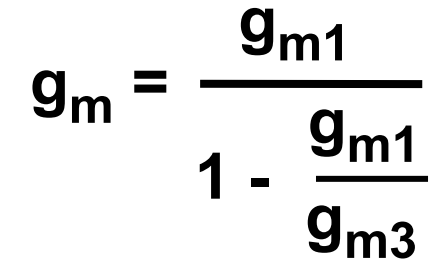Ref.: Castello, JSSC June 1990, pp. 669-676 M5,M6 for overdrive !




$$g_m \approx 3 g_{m1}$$

$$\text{GBW} = \frac{3 g_m}{2\pi C_L}$$

$$\approx \frac{9 g_{m1}}{2\pi C_L}$$

Transconductor with C_{DG} compen.

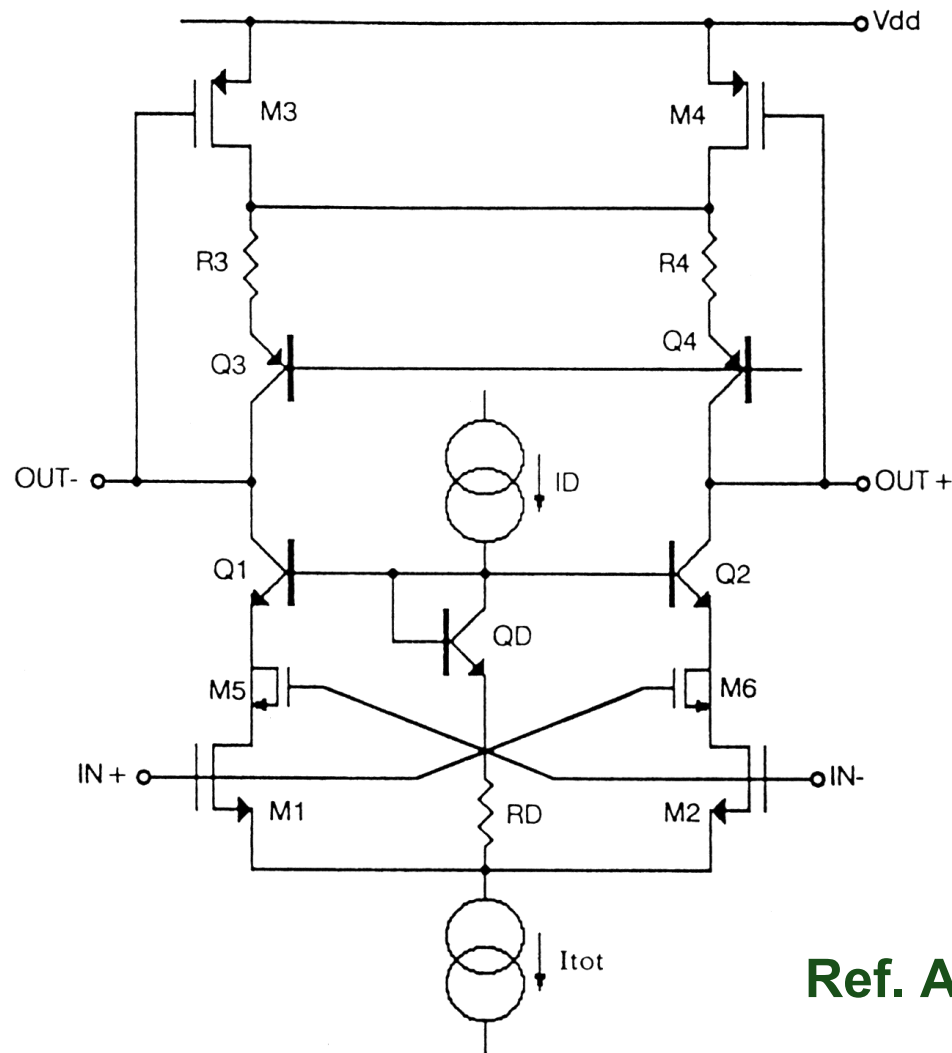


$$V_{DS1} = R_D I_D \approx 0.2 \text{ V}$$

$$I_{DS1} = \beta_1 V_{DS1} (V_{GS1} - V_T)$$

$$g_{m1} = \beta_1 V_{DS1} \text{ is constant}$$

Ref. Alini, JSSC, Dec.92, pp.1905-1915

Ref. : Wu etal, JSSC Jan.1994, pp.63-66

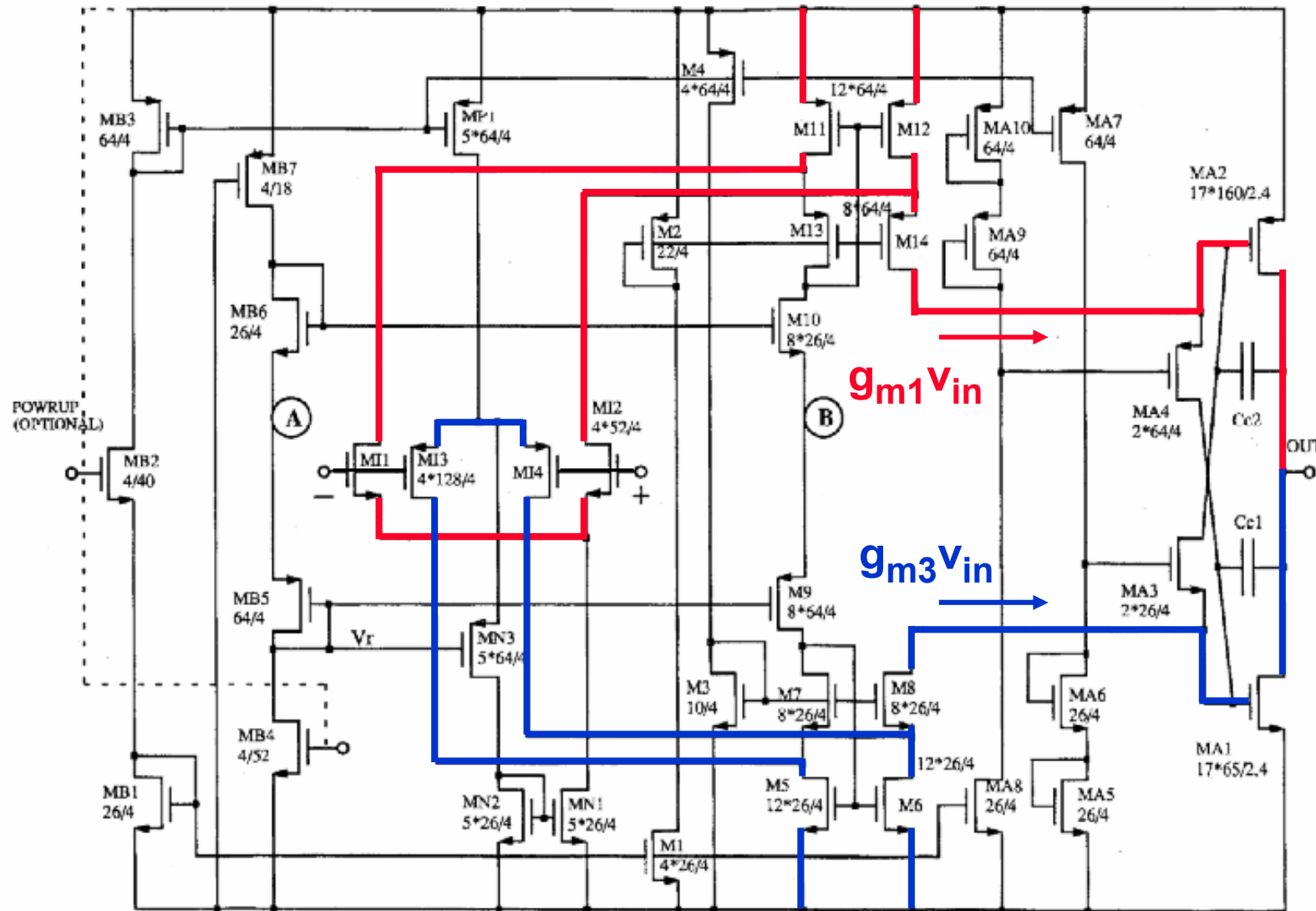

14 MHz
/ 11pF


5.6 MHz
/ 100pF

4 V/ μ s



36 nV/ $\sqrt{\text{Hz}}$

5 V
0.4 mA

Problem: unequal g_{mtot}

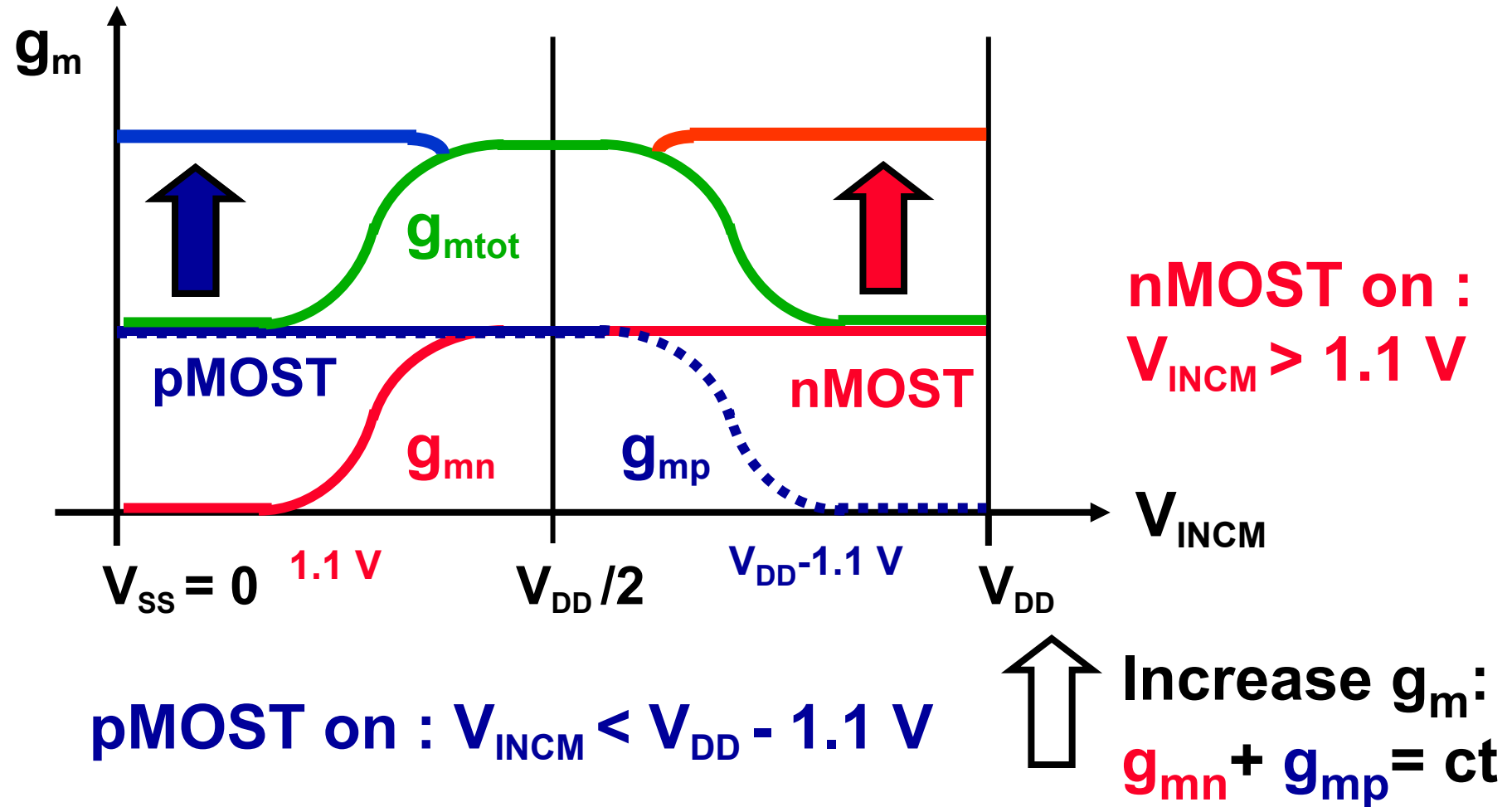

Wu : input rail-to-rail stage

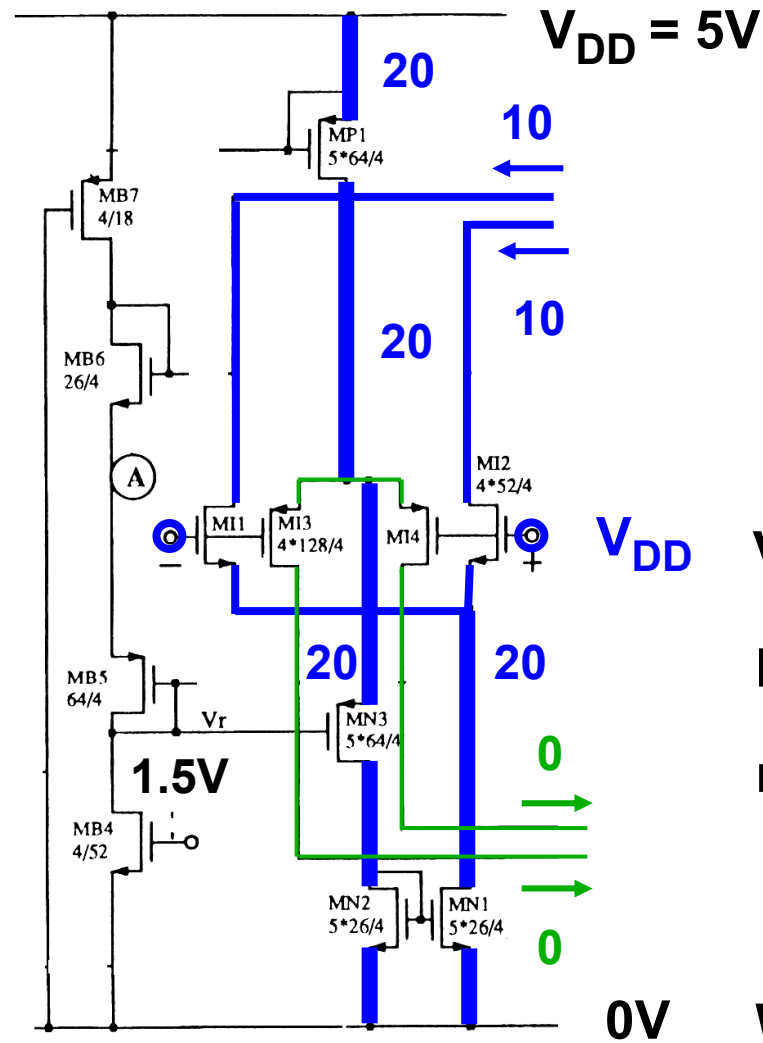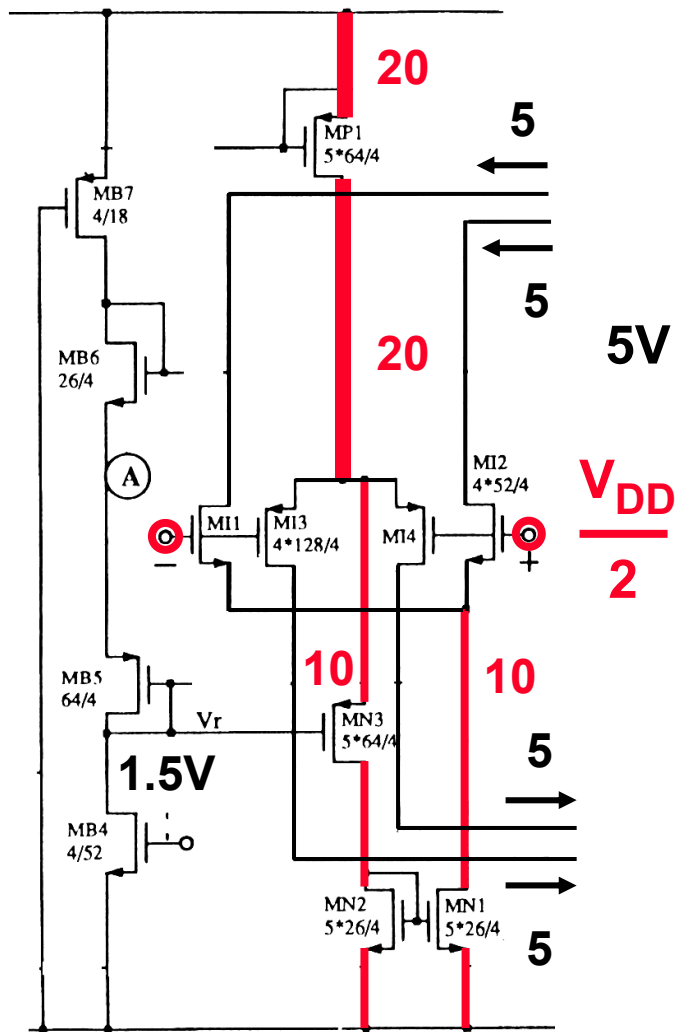

V₊ high :
pMOSTs off !




nMOSTs :

$$I_{DS1} \times 2$$

$g_{m1} \times 2$

Weak inv.

Wu : output stage : gain

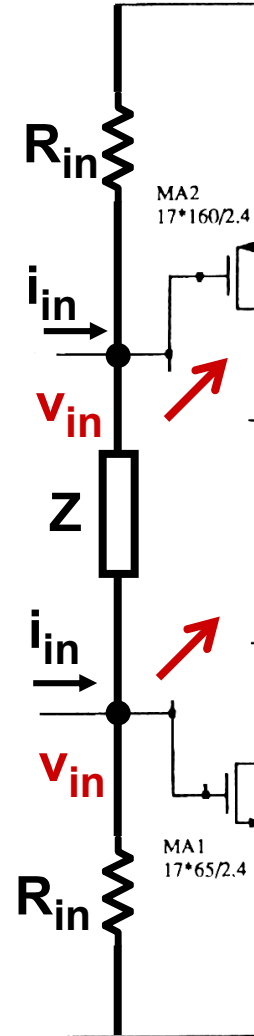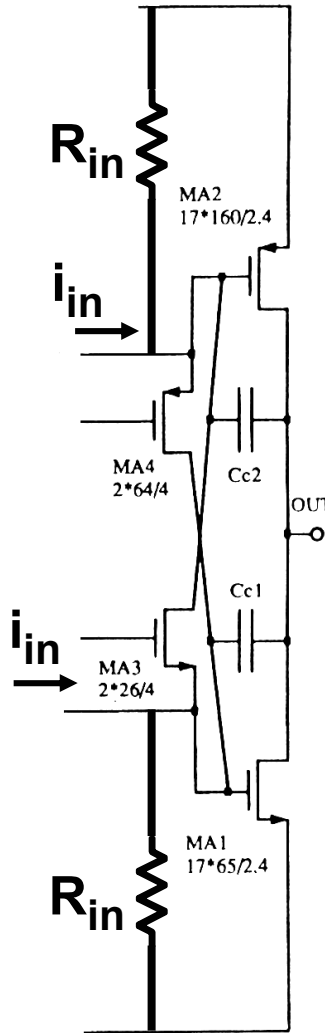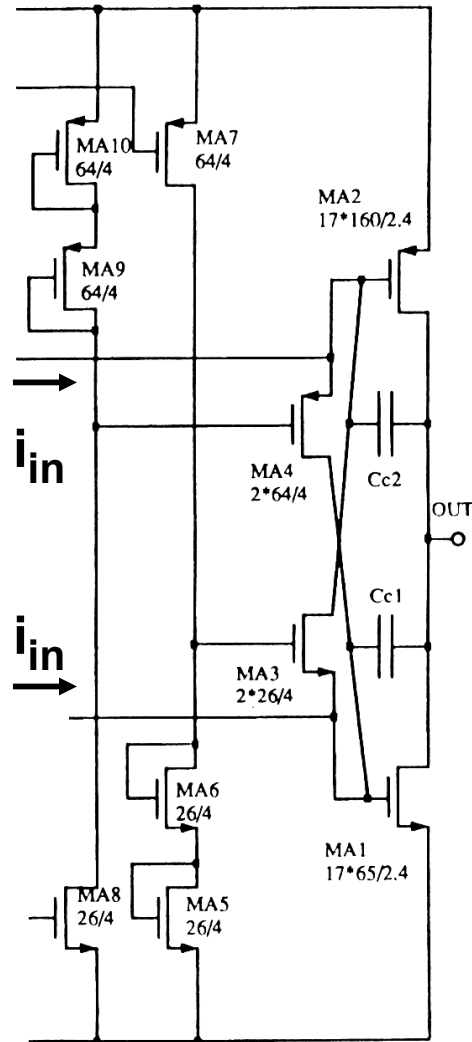

$$i_{in} = g_{m1} v_{+-}$$


$$\frac{v_{in}}{i_{in}} = R_{in}$$

$$\frac{v_{out}}{v_{in}} = 2g_{mA1}R_L$$

$$\frac{v_{out}}{i_{in}} = -2R_{in}g_{mA1}R_L$$

$$A_v = 2g_{m1}R_{in}g_{mA1}R_L$$

Wu : output quiescent current control

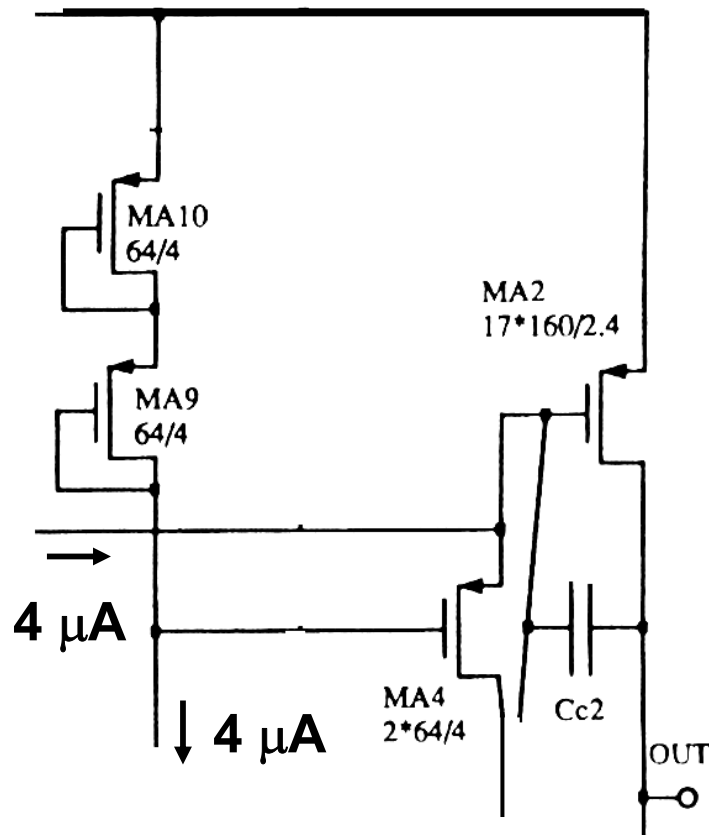

$$V_{GS2} + V_{GS4} = V_{GS9} + V_{GS10}$$


$$M_4 = 2 M_{10} \text{ \& \; } M_9 = M_{10}$$

$$V_{GS2} - V_T = \sqrt{\frac{I_{DS2}}{K'_p W/L_2}}$$

$$\frac{I_{DS2}}{I_{DS9}} = \frac{W/L_2}{W/L_9} \left(2 - \frac{1}{\sqrt{2}}\right) \approx 91$$


$$I_{DS2} \approx 364 \mu\text{A} \text{ since } I_{DS9} \approx 4 \mu\text{A}$$

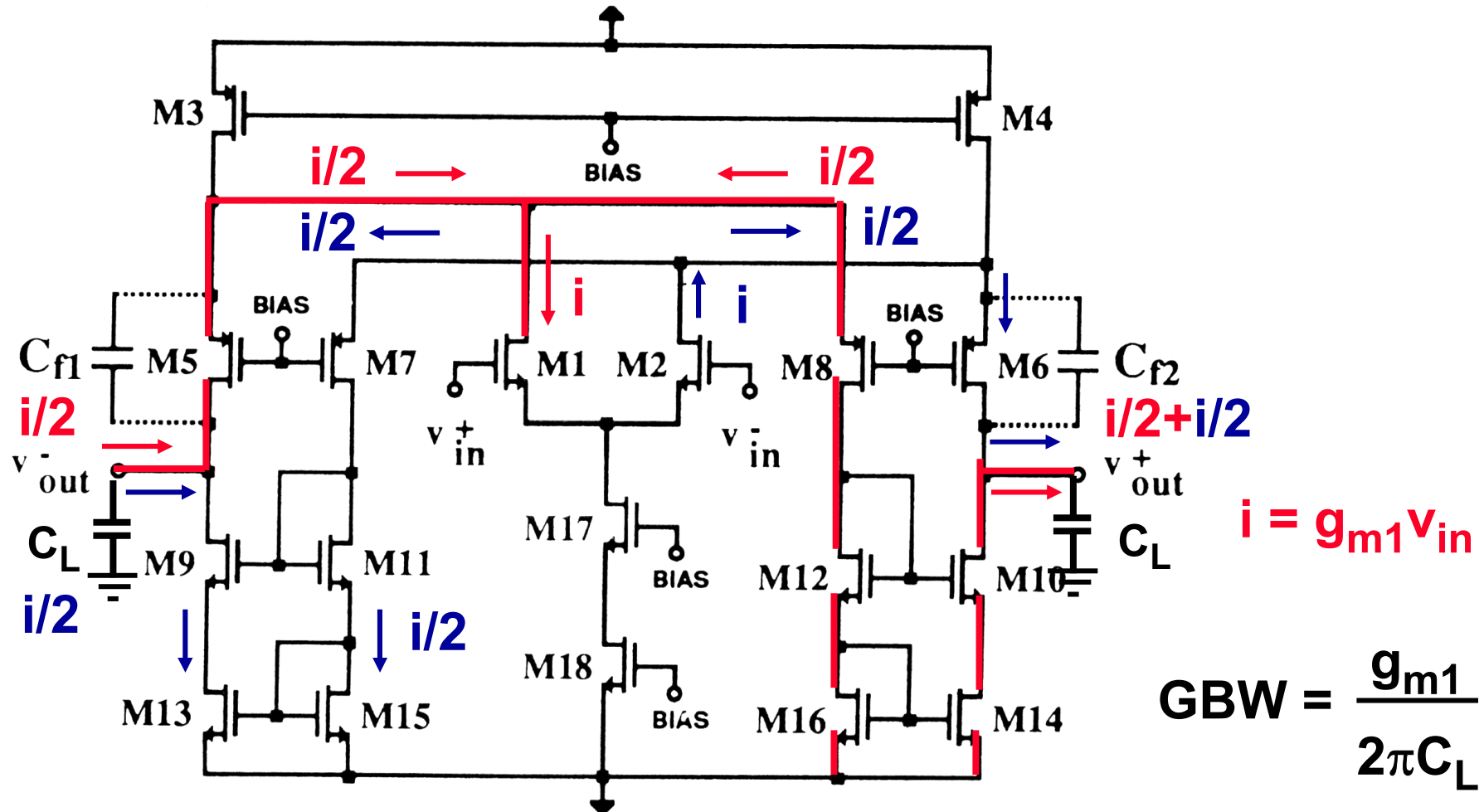Enhanced full-differential folded-cascode



Ref. Nakamura, JSSC April 1992, pp.563-568

Bipolar opamp LM-124

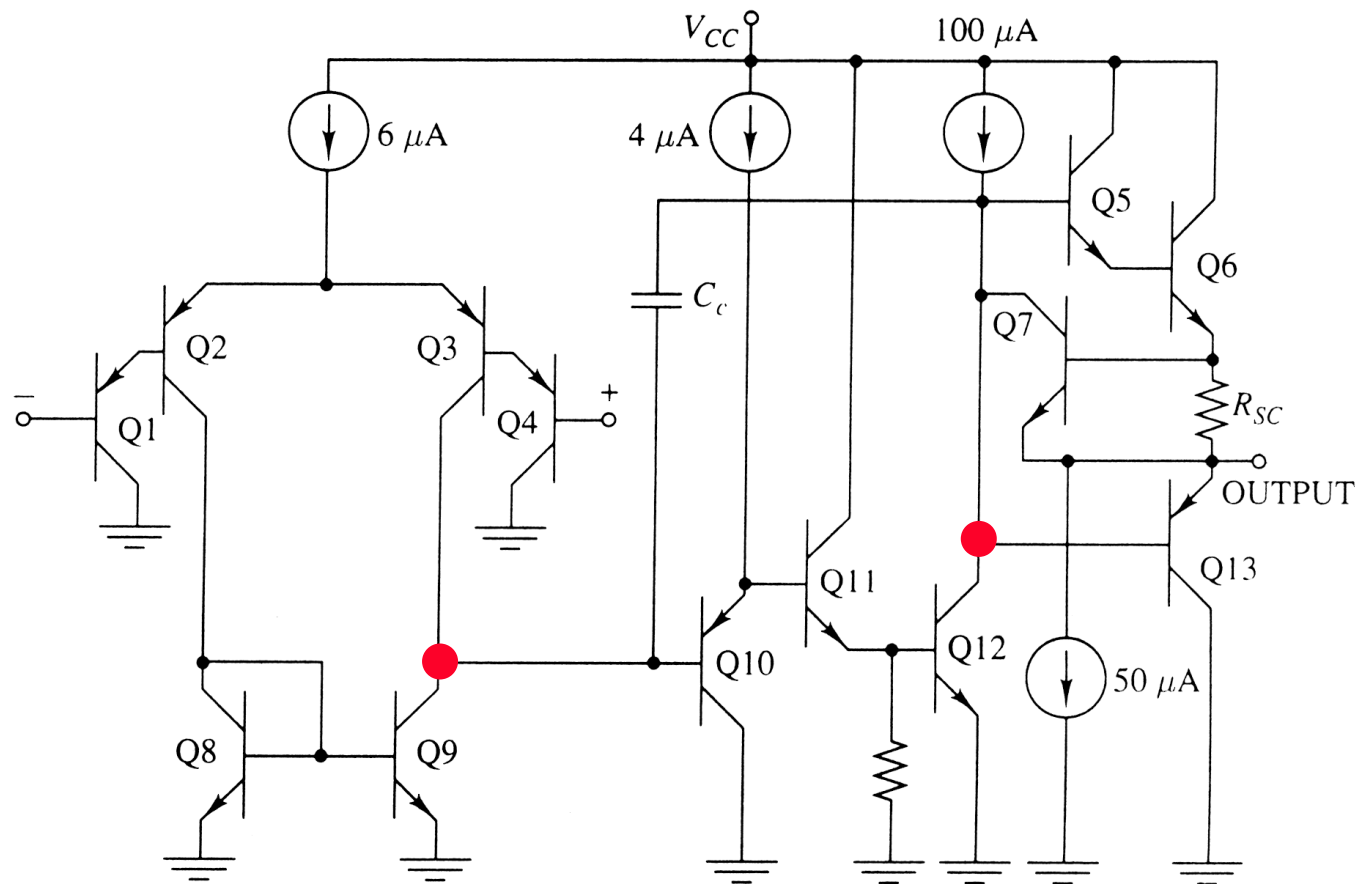

GBW = 0.5 MHz



SR = 0.4 V/ μs

$I_1 = 3 \mu\text{A}$

$I_{TOT} = 650 \mu\text{A}$

68 nV_{RMS}/ $\sqrt{\text{Hz}}$

BiFET opamp TL-070

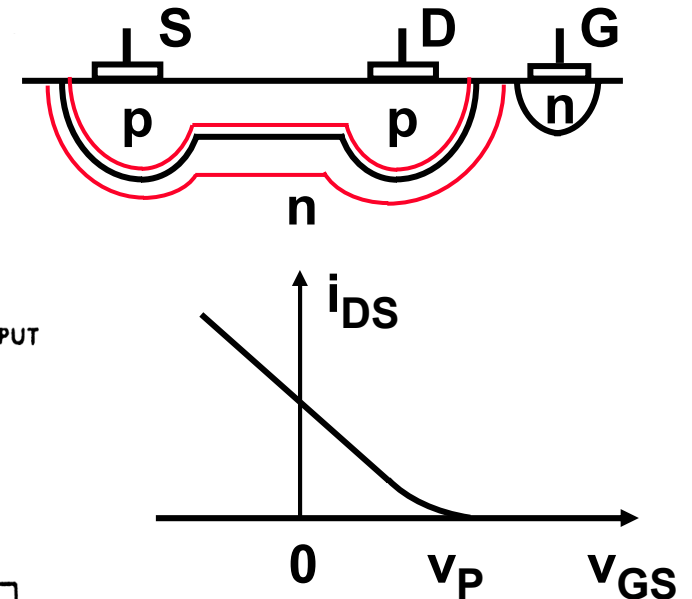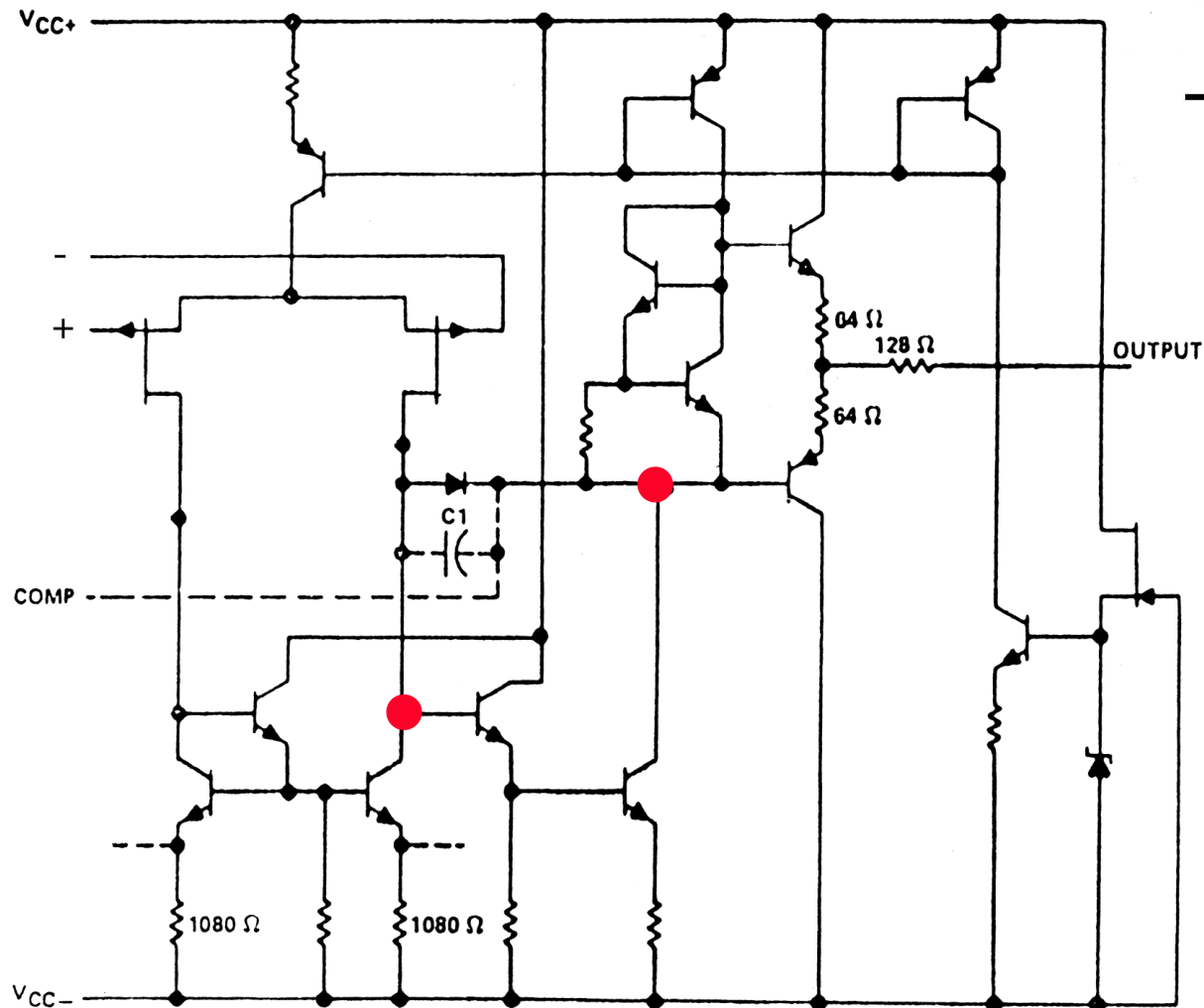

GBW = 3 MHz


SR = 13 V/ μ s

$I_1 = 100 \mu\text{A}$

$I_{\text{TOT}} = 1400 \mu\text{A}$

$18 \text{ nV}_{\text{RMS}}/\sqrt{\text{Hz}}$

Bipolar 2-stage opamp 741

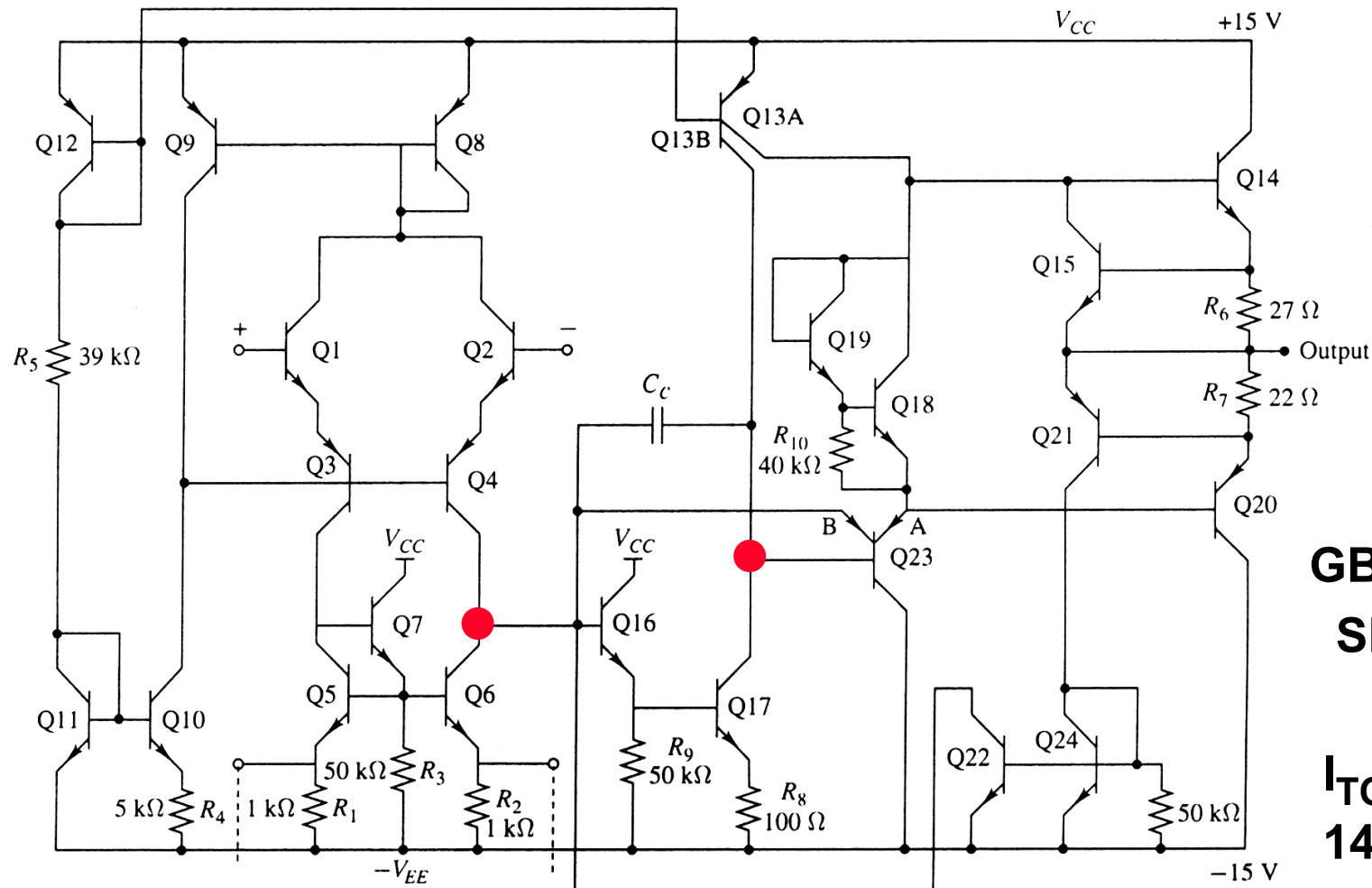

GBW = 0.8 MHz


SR = 0.7 V/ μ s

$I_1 = 10 \mu\text{A}$


$I_{\text{TOT}} = 1100 \mu\text{A}$

$14 \text{ nV}_{\text{RMS}}/\sqrt{\text{Hz}}$

Two-stage opamp OP-97

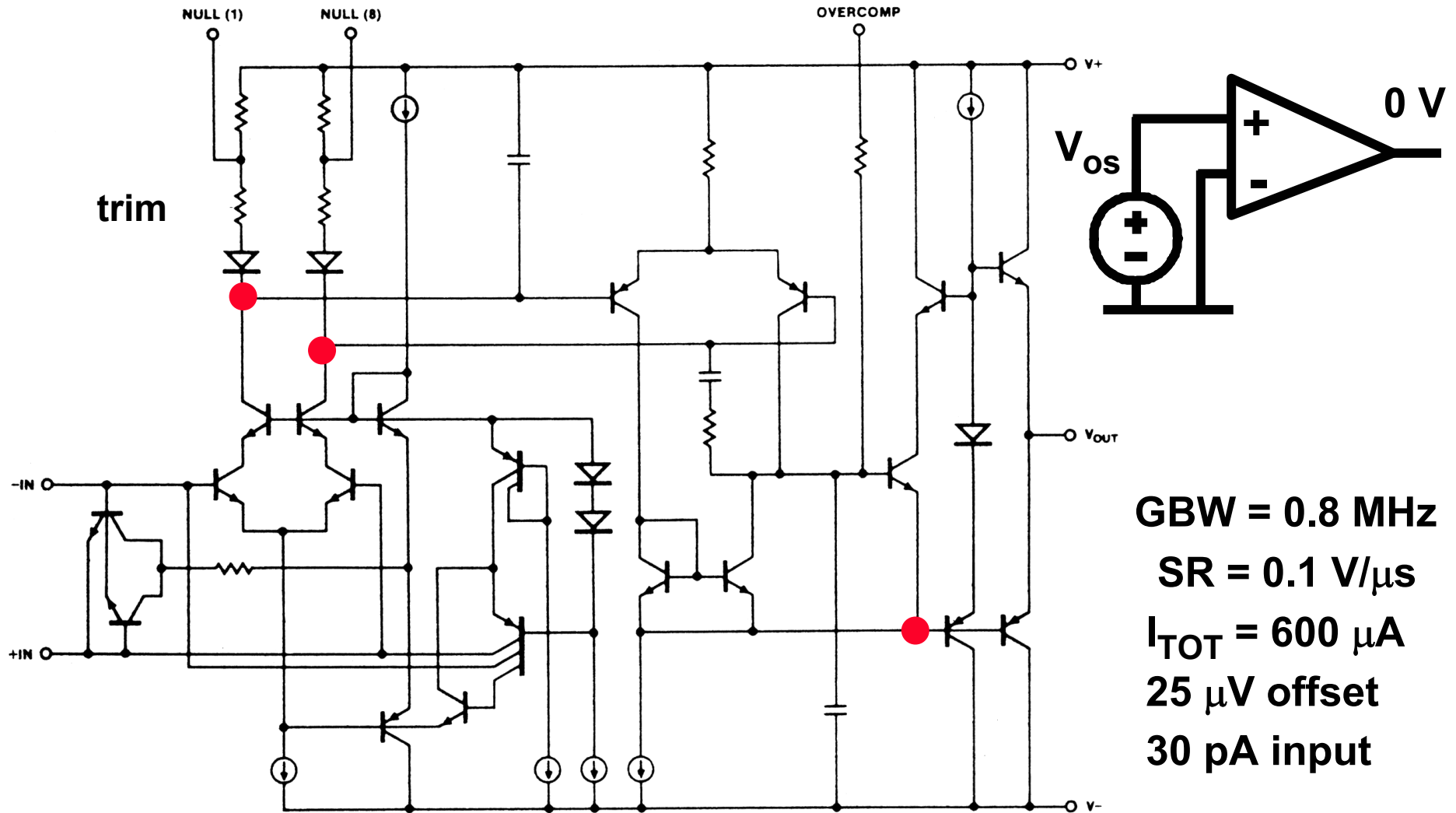

Bootstrap for high gain A_{v2}

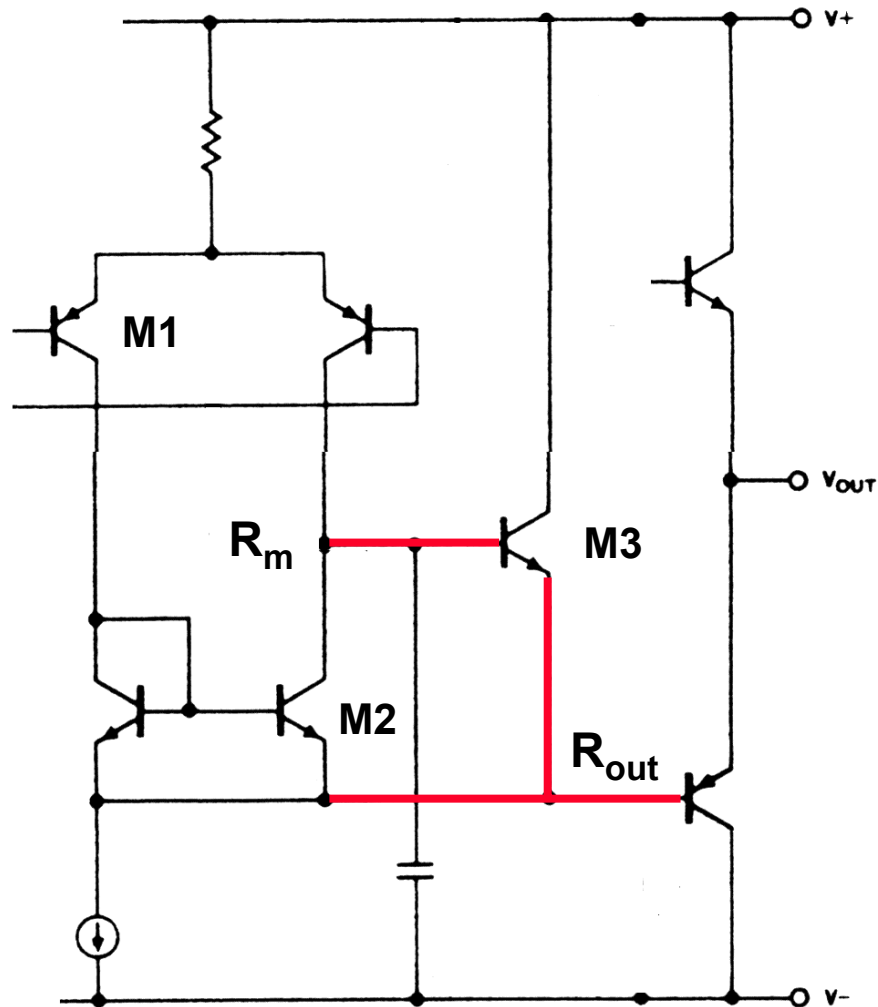

$$R_m \rightarrow \times \beta_3$$

$$R_{out} \rightarrow \times \frac{1}{\beta_3}$$

$$A_{v2} \approx g_{m1} r_{o2} \times \beta_3$$

Same GBW !

Ref. De Man JSSC June 77, pp.217-222

Table of contents

- **Simple CMOS OTA**
- **CMOS Miller OTA**
- **Symmetrical CMOS OTA**
- **Folded cascode OTA**
- **Other opamps**