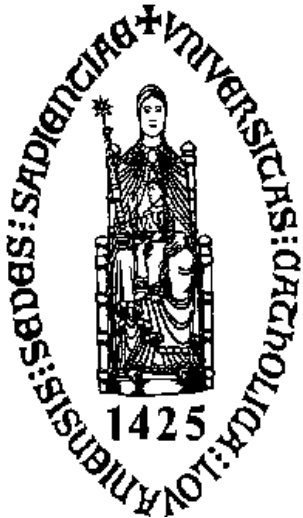


---

---

# Rail-to-rail input and output amplifiers



**Willy Sansen**

**KULeuven, ESAT-MICAS**

**Leuven, Belgium**

[willy.sansen@esat.kuleuven.be](mailto:willy.sansen@esat.kuleuven.be)



---

# Table of contents

---

- **Why rail-to-rail ?**

- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rtr amplifiers and comparison**

---

## **Why rail-to-rail amplifiers ?**


---

- **For low supply voltages : use full range for maximum dynamic range**
- **Fully differential signal processing**
- **Rail-to-rail output is always required**
- **But not necessarily rail-to-rail-input !**

---

# Symmetrical CMOS OTA




---

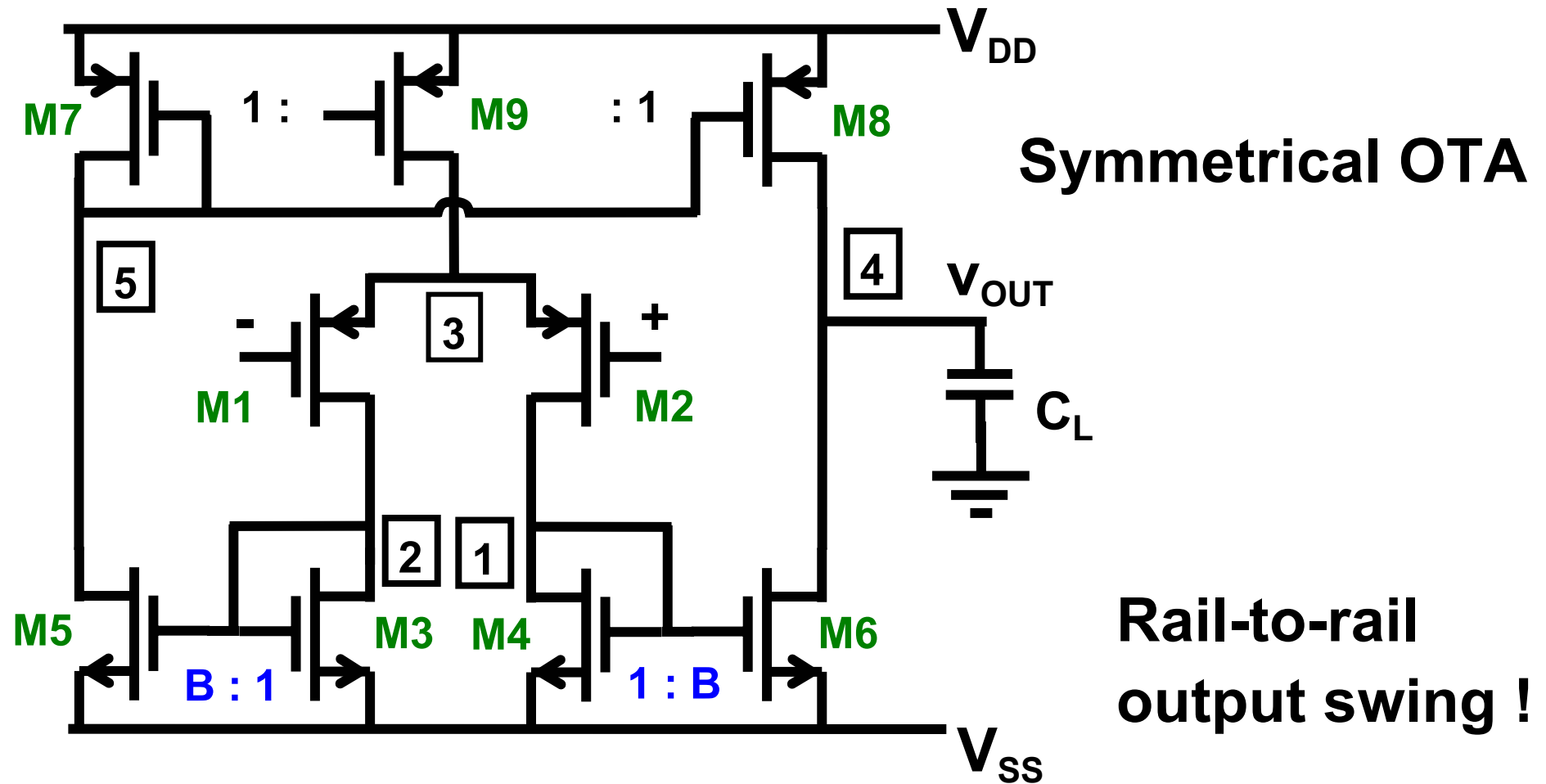


---

## When rail-to-rail input ?

---

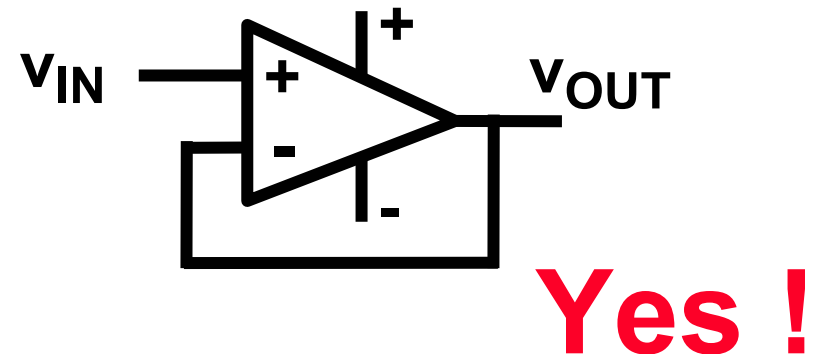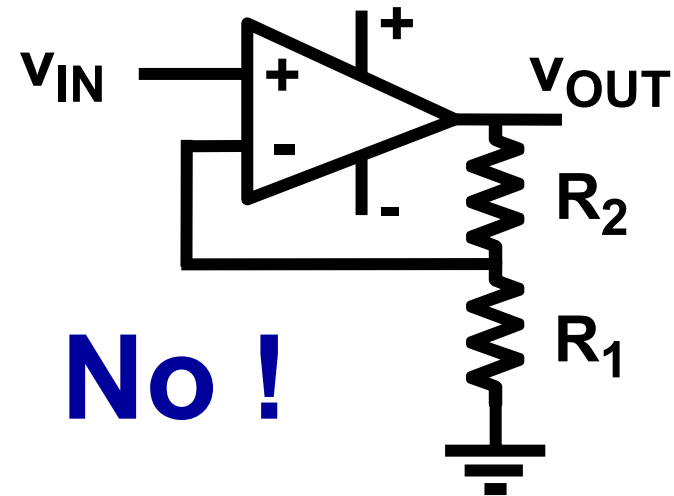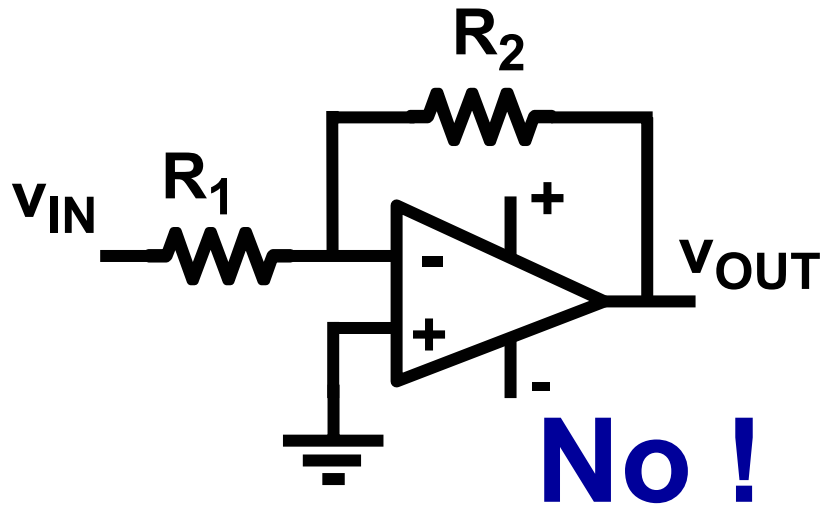

## Rail-to-rail input for CMFB

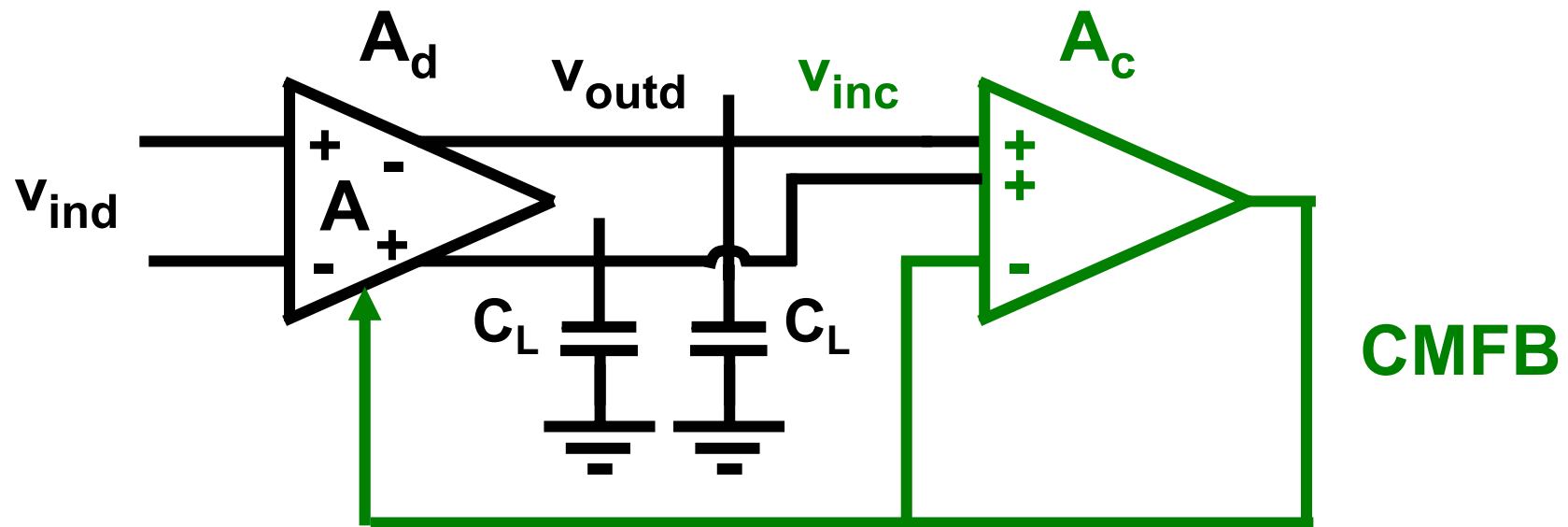

**For a rail-to-rail output swing in fully-differential amplifiers  
A CMFB amplifier is required  
With rail-to-rail input capability !**

---


# Table of contents

---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**
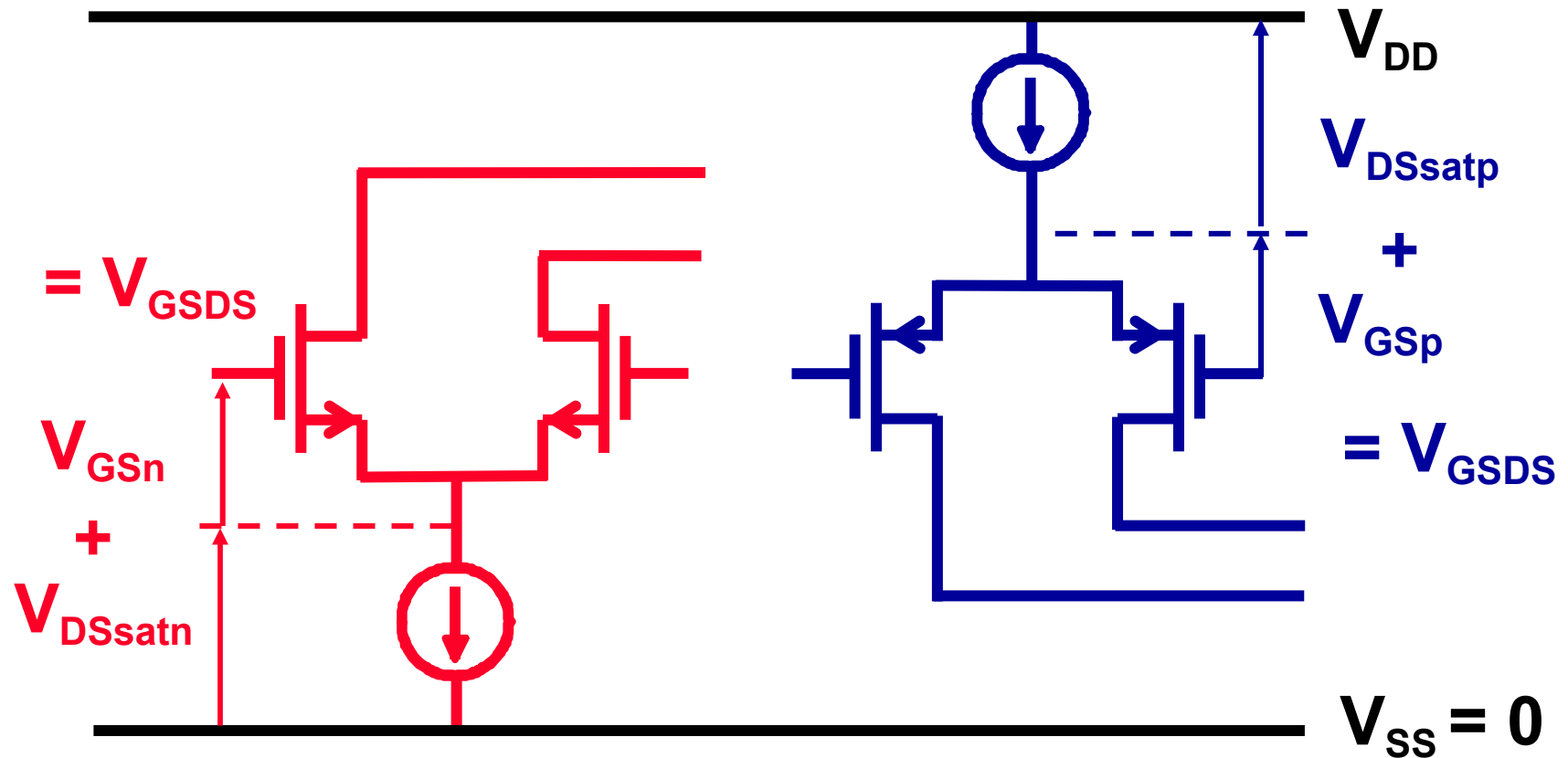
# Problem ?

$$V_{GS} \approx 0.9 \text{ V} \quad \& \quad V_{DSsat} \approx 0.2 \text{ V} \quad \gg \gg \quad V_{GSDS} = 1.1 \text{ V}$$




$$V_{INCM} > 1.1 \text{ V}$$

$$V_{INCM} < V_{DD} - 1.1 \text{ V}$$



## Problem : limited input CM range

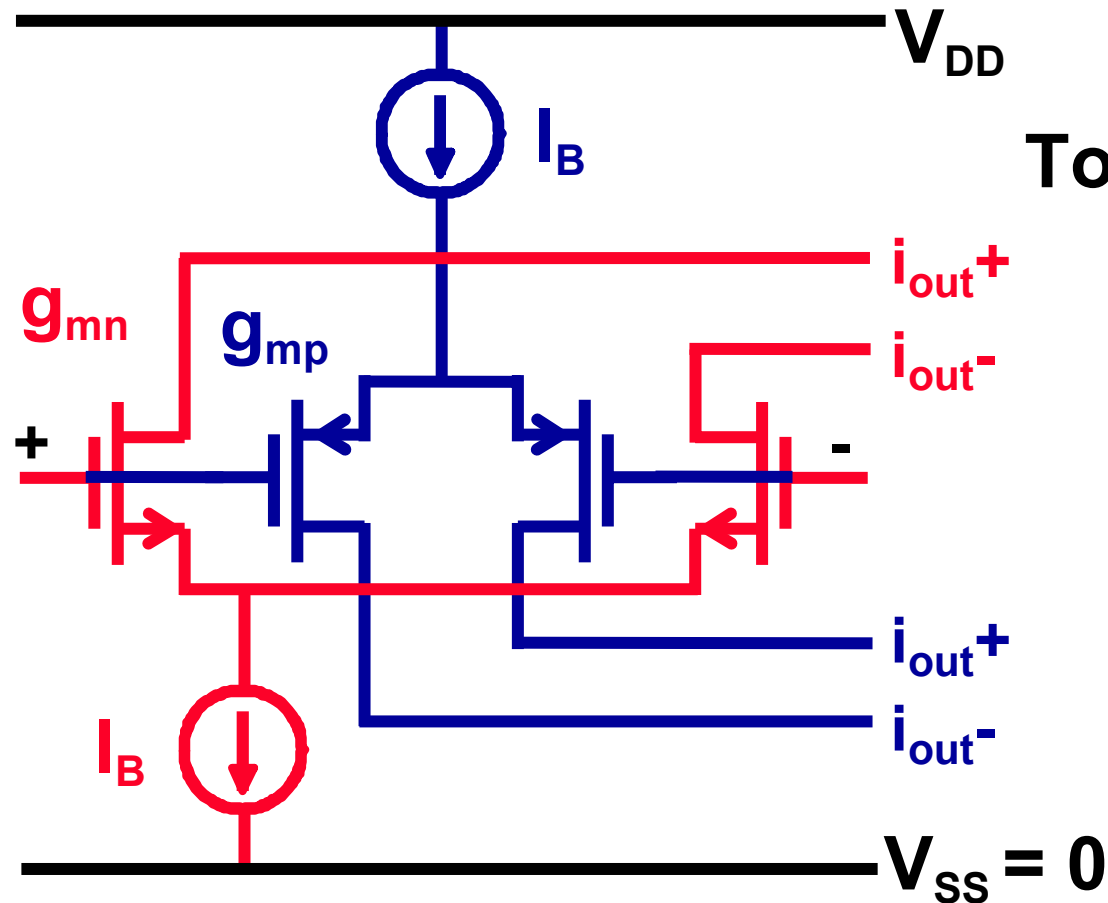

To be operational :

$$V_{INCM} > 1.1 \text{ V}$$

$$V_{INCM} < V_{DD} - 1.1 \text{ V}$$


$$V_{DDmin} = 2.2 \text{ V}$$




---

## Problem: unequal $g_{mtot}$

---

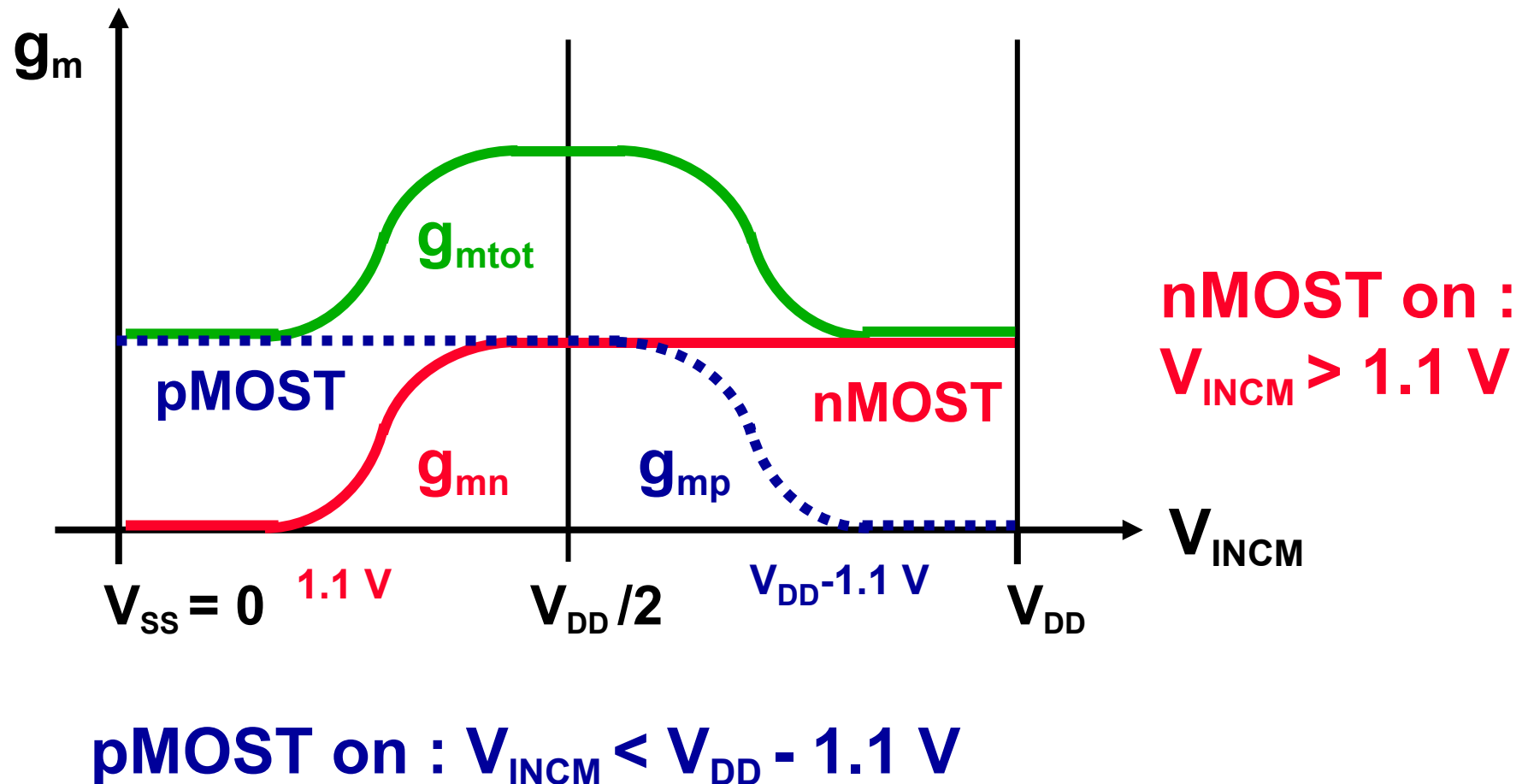

## Solution : $g_m$ equalization

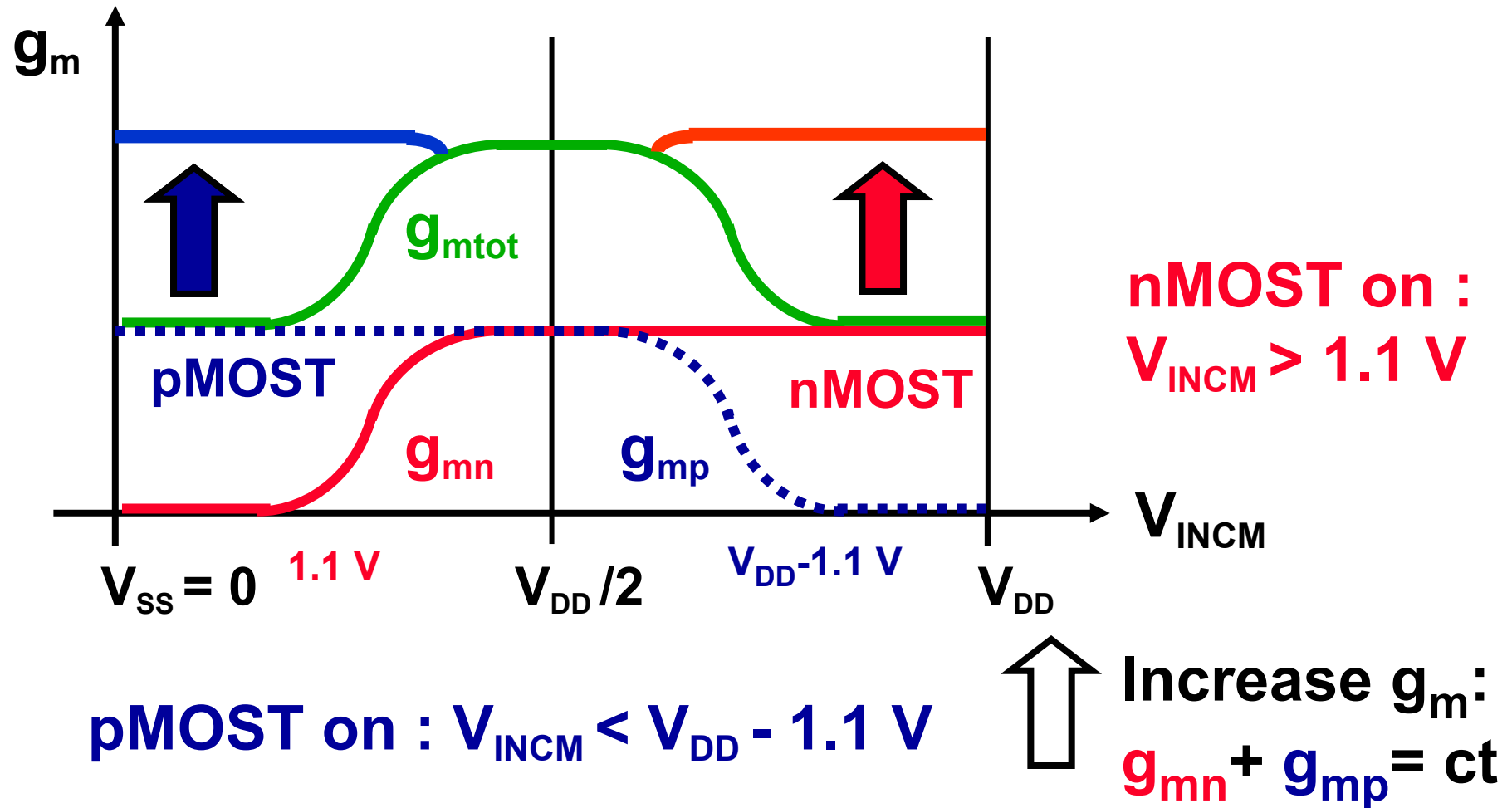

---

## Equalize $g_{mtot}$ in strong inversion

---

$$g_{mn} + g_{mp} = ct1$$


$$\sqrt{2 K'_n \frac{W_n}{L_n} I_{Bn}} + \sqrt{2 K'_p \frac{W_p}{L_p} I_{Bp}} = ct1$$

$$\sqrt{K'_n I_{Bn}} + \sqrt{K'_p I_{Bp}} = ct2$$


$$\sqrt{I_{Bn}} + \sqrt{I_{Bp}} = ct3$$

$$3 \times \text{Current mirror} : \sqrt{1} + \sqrt{1} = \sqrt{0} + \sqrt{4} \quad > \quad 4 - 1 = 3$$


# 3x Current mirror for nMOSTs

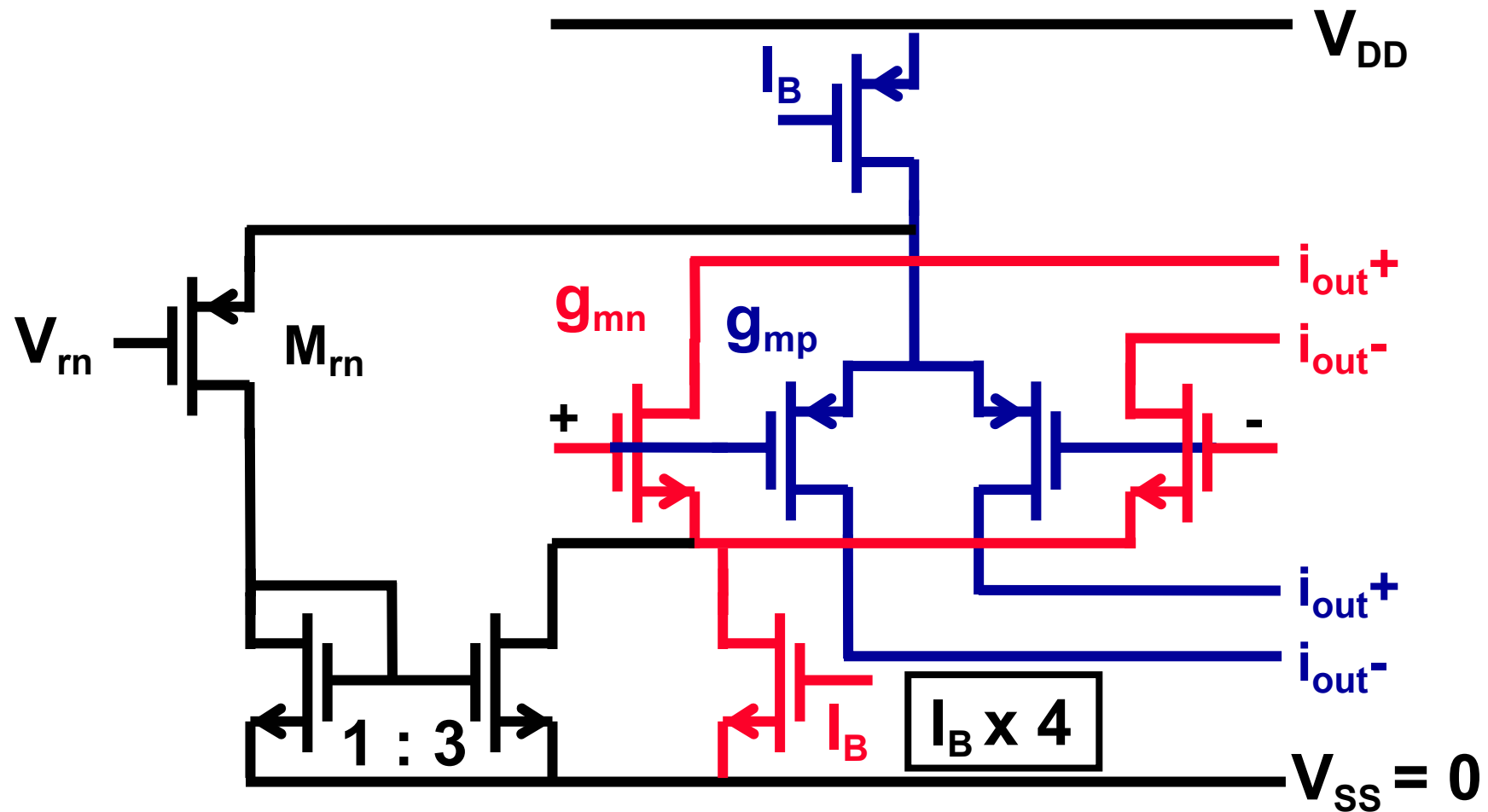

## 3x Current mirror for all MOSTs

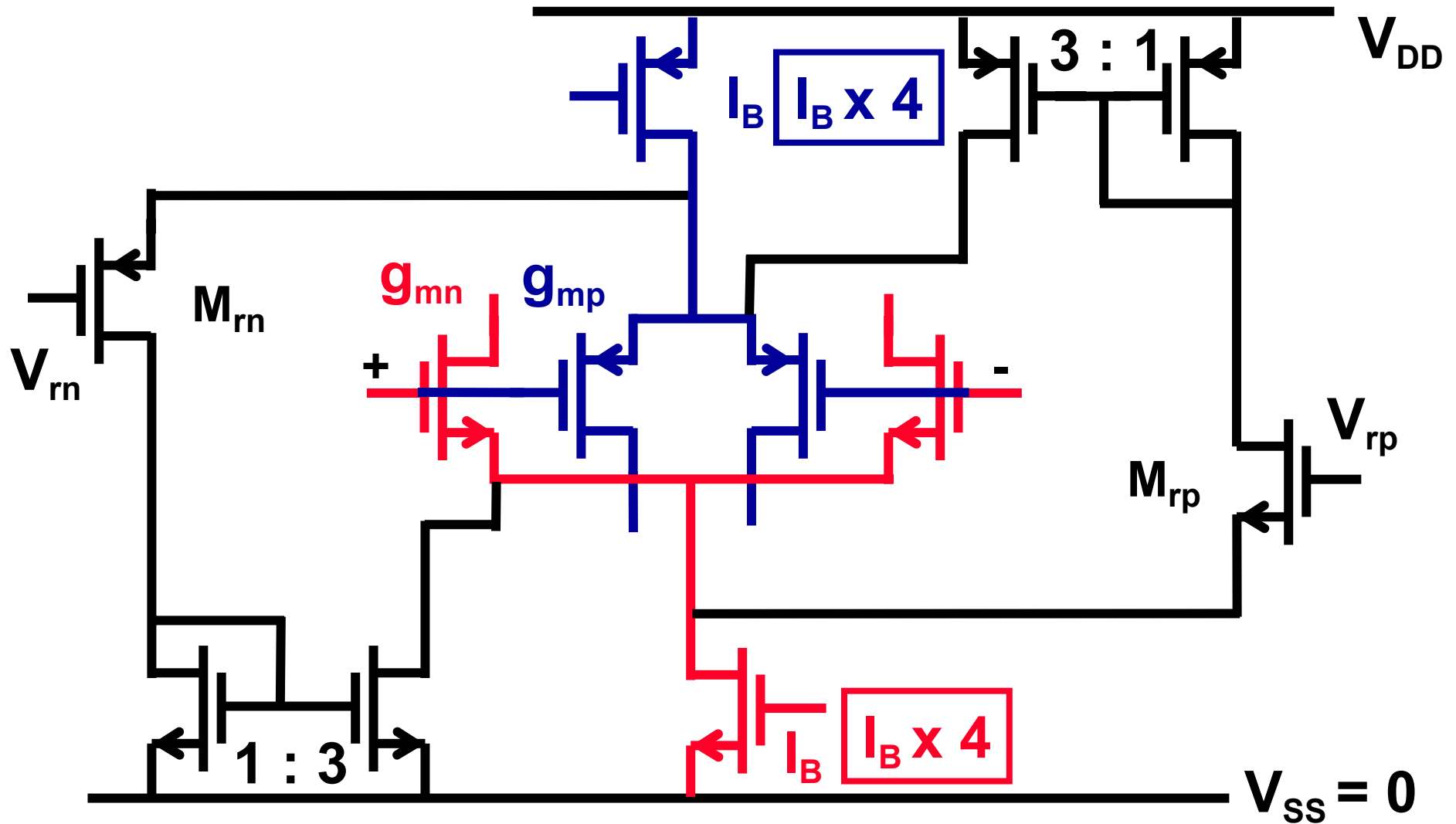


# 3x Current mirror : performance

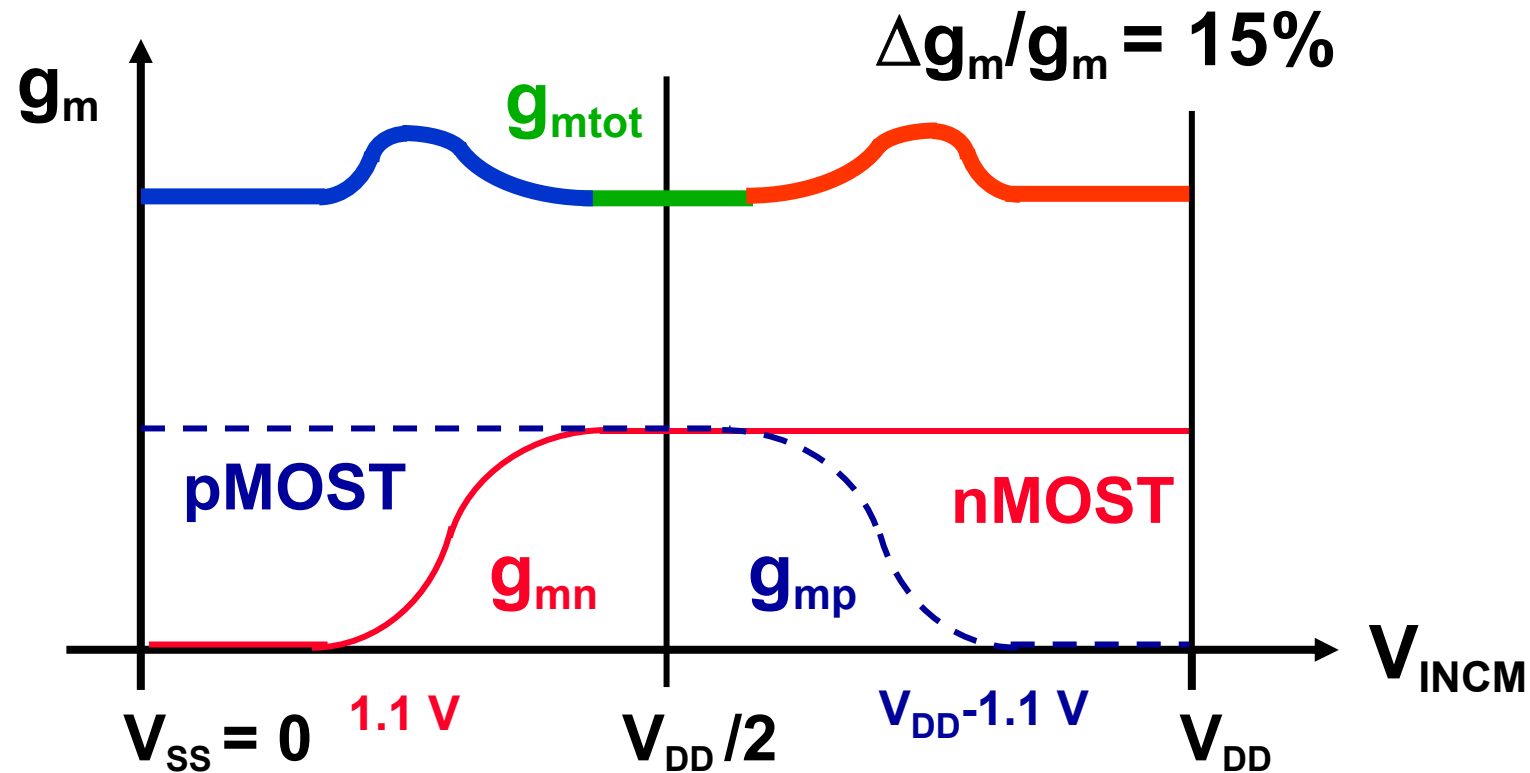

$$g_{mtot} \sim \sqrt{(4 - 3x) I_B} + \sqrt{x I_B} \quad \Delta g_m/g_m = 15\% \quad (x=1/3)$$

# Rail-to-rail opamp

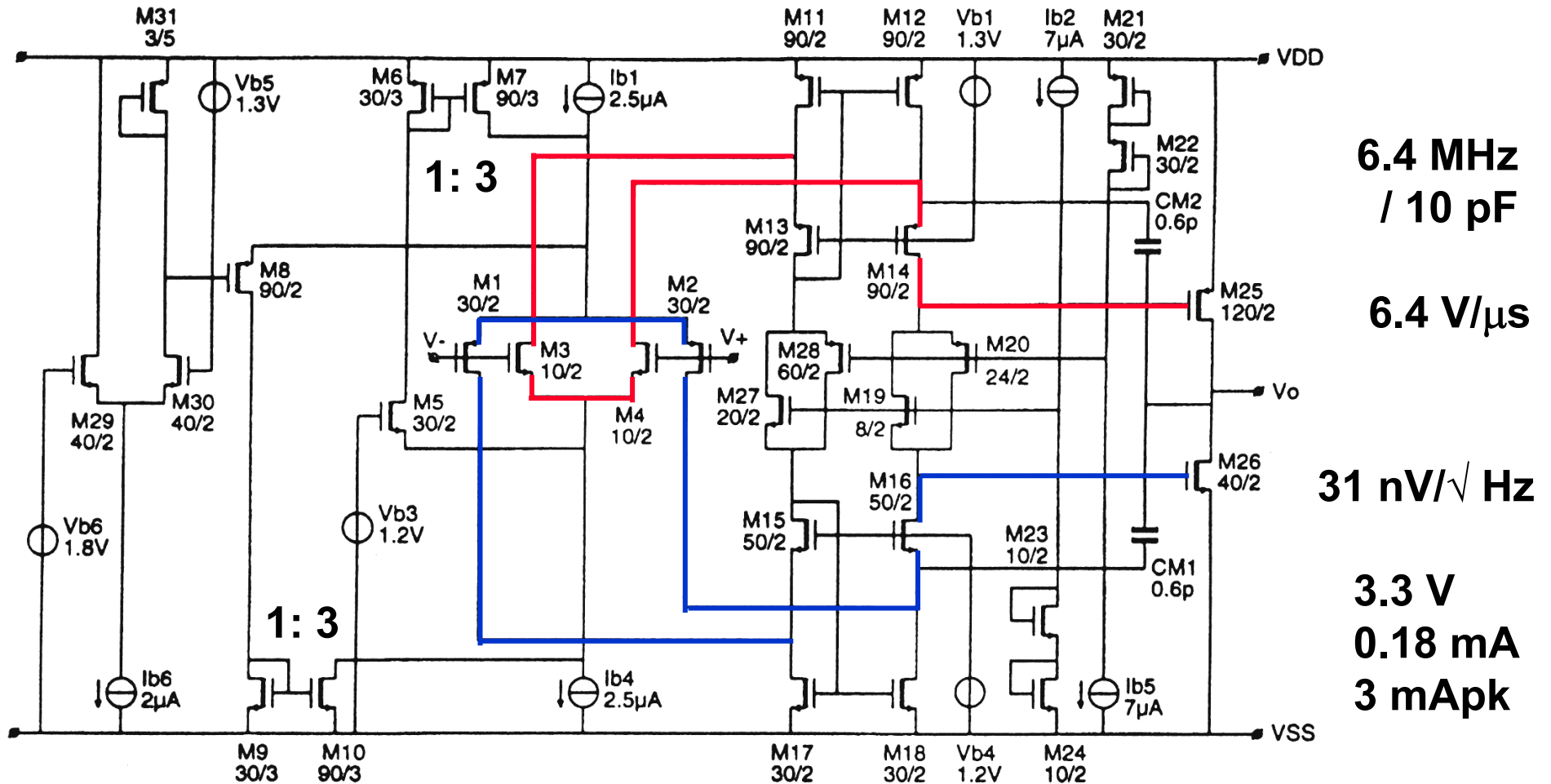

Ref. Hogervorst, JSSC Dec.1994, 1505-1512






---

# Table of contents

---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**


# Zener diodes

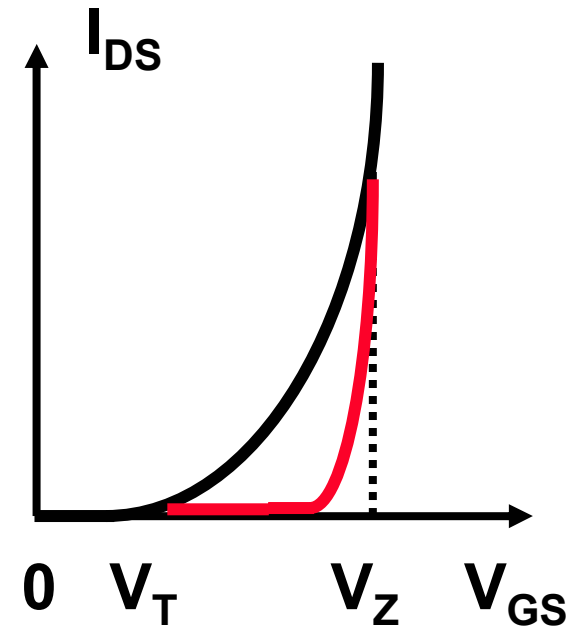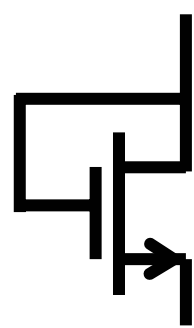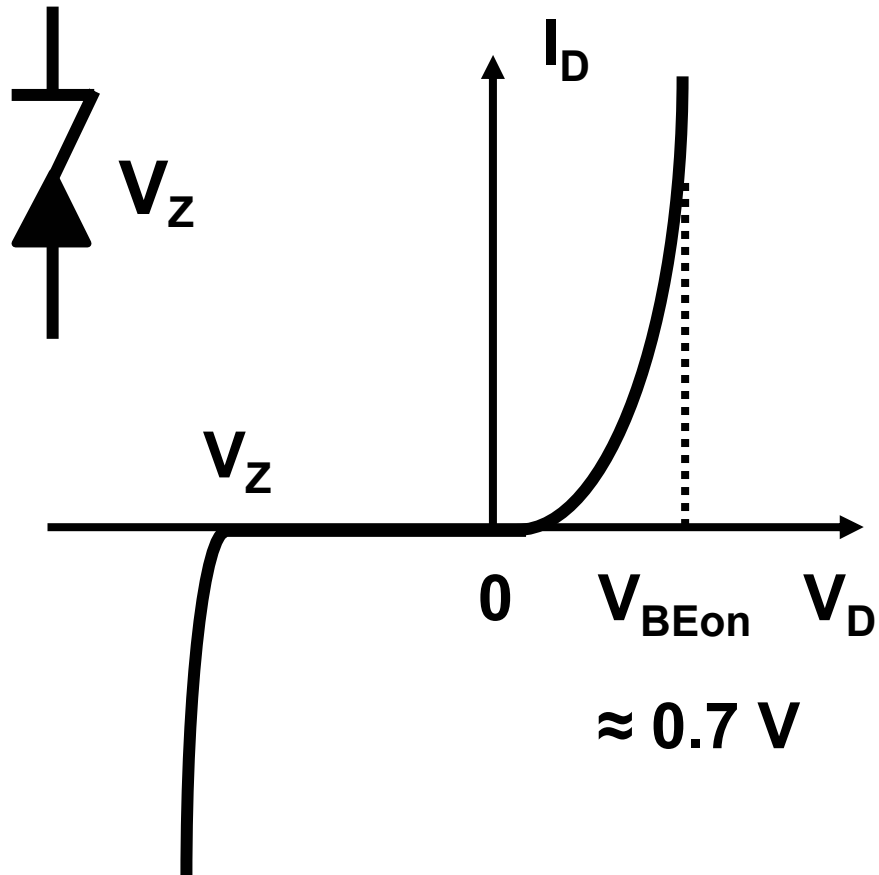


**Electronic Zener**



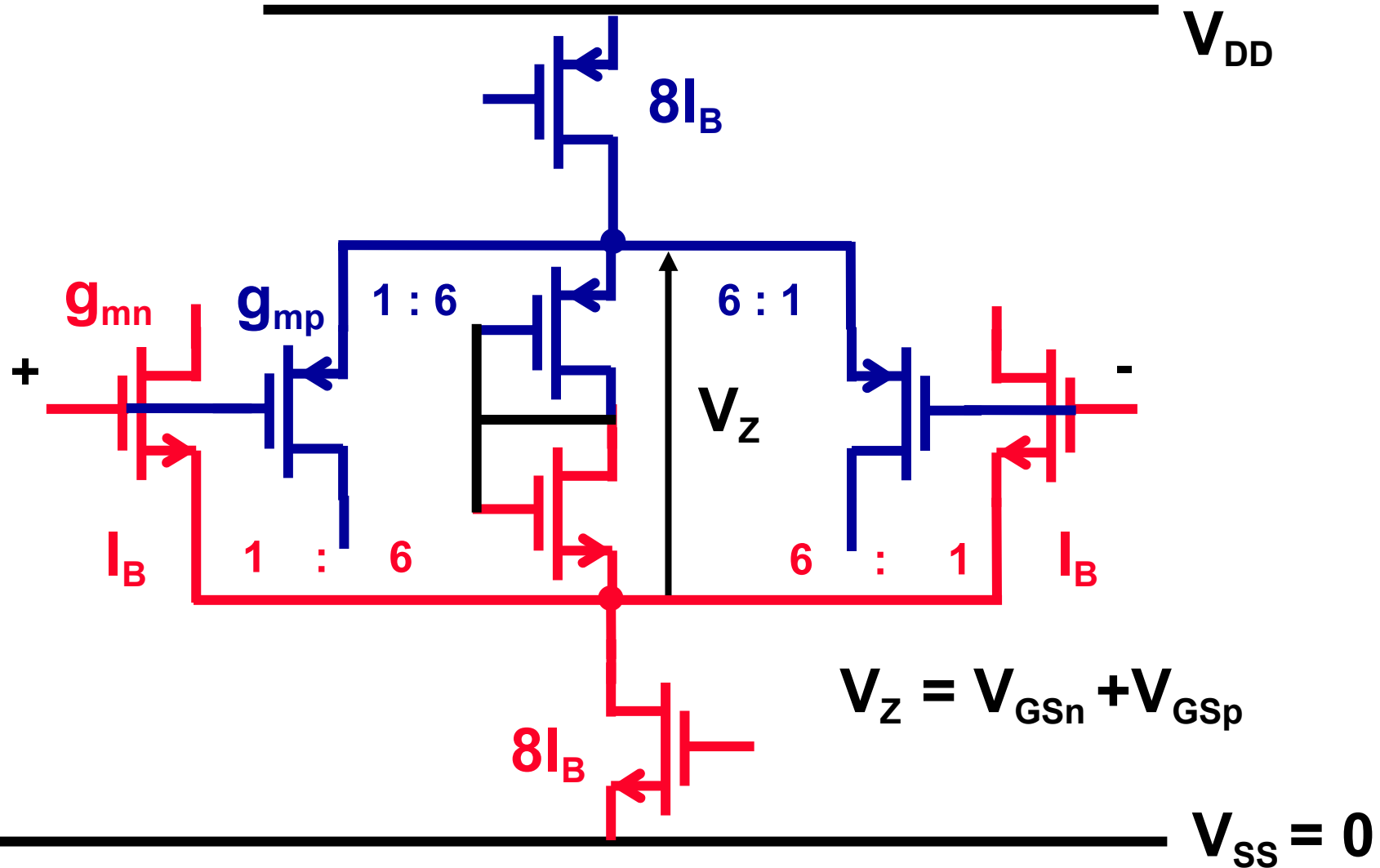
# Rail-to-rail amplifier with Zener diode


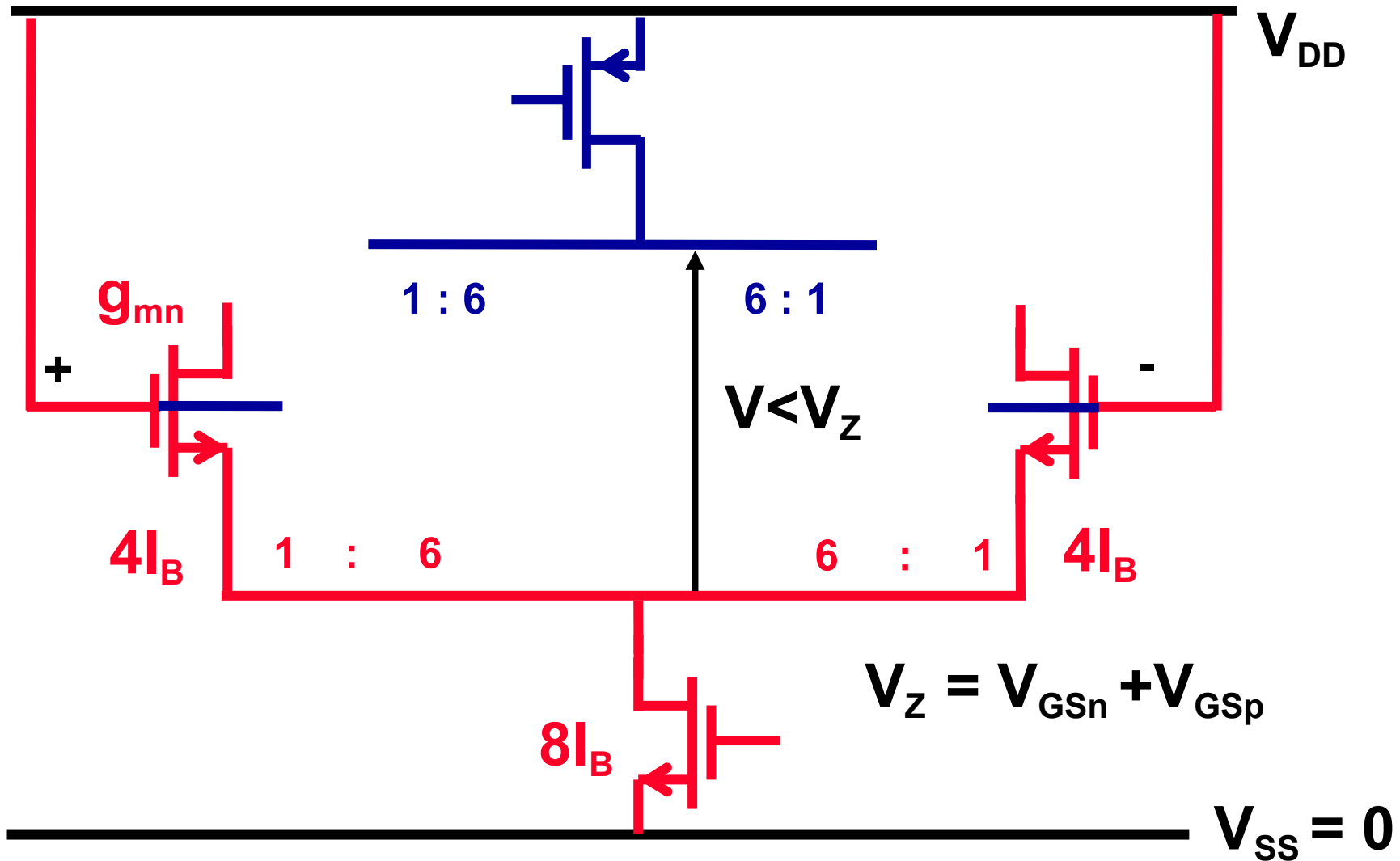
# Rail-to-rail amplifier with Zener diode




# Rtr amp. with electronic Zener

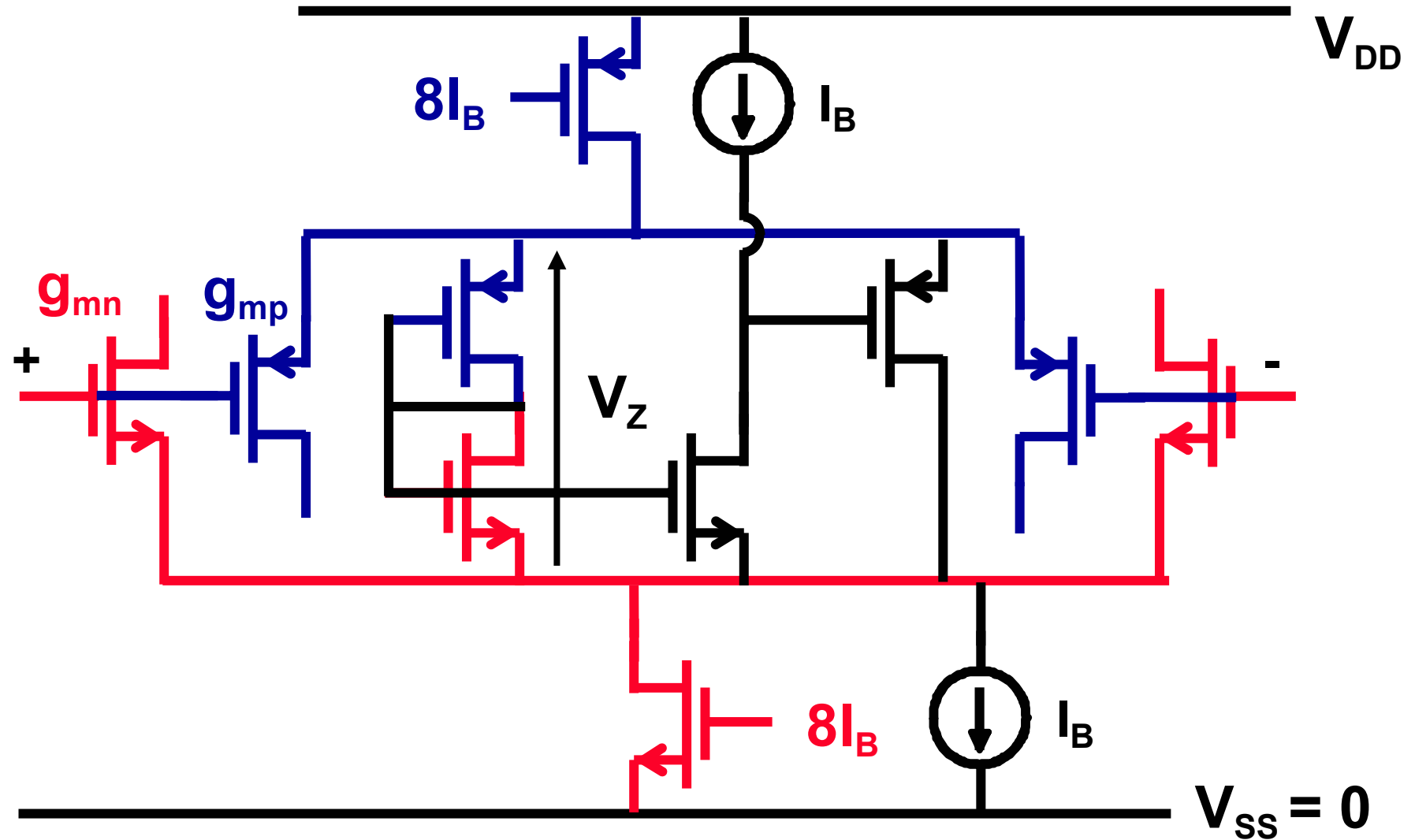

---

# Rail-to-rail amp. with Zener : performance

---

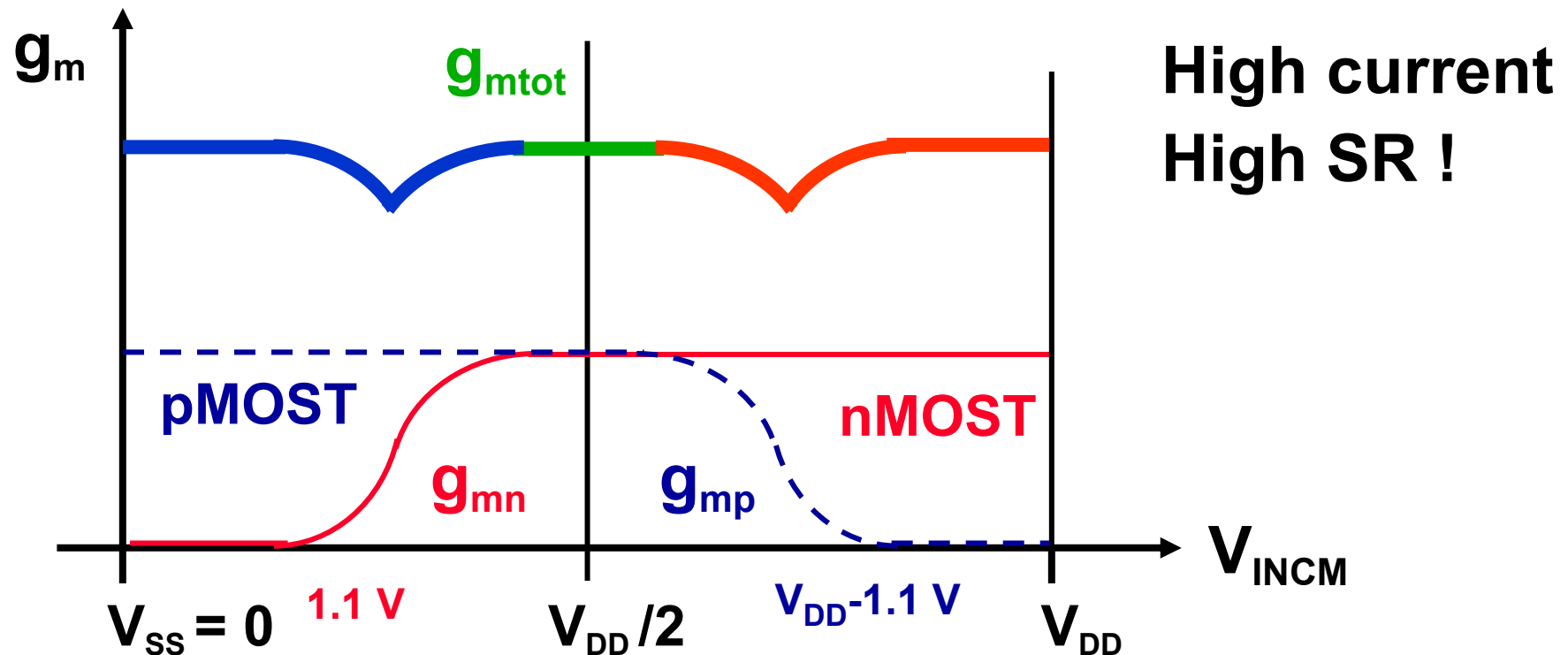

**Zener:  $\Delta g_m / g_m = 25\%$     Electronic Zener:  $\Delta g_m / g_m = 6\%$**

Ref. Hogervorst, JSSC July 1996, 1035-1040

---

# Table of contents

---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**

---

## Equalize $g_{mtot}$ in weak inversion

---

$$g_{mn} + g_{mp} = ct$$


$$\frac{I_{Bn}}{2 n_n kT/q} + \frac{I_{Bp}}{2 n_p kT/q} = ct$$

$$I_{Bn} + \frac{n_n}{n_p} I_{Bp} = ct$$

$$n = 1 + \frac{C_D (V_{BS})}{C_{ox}}$$



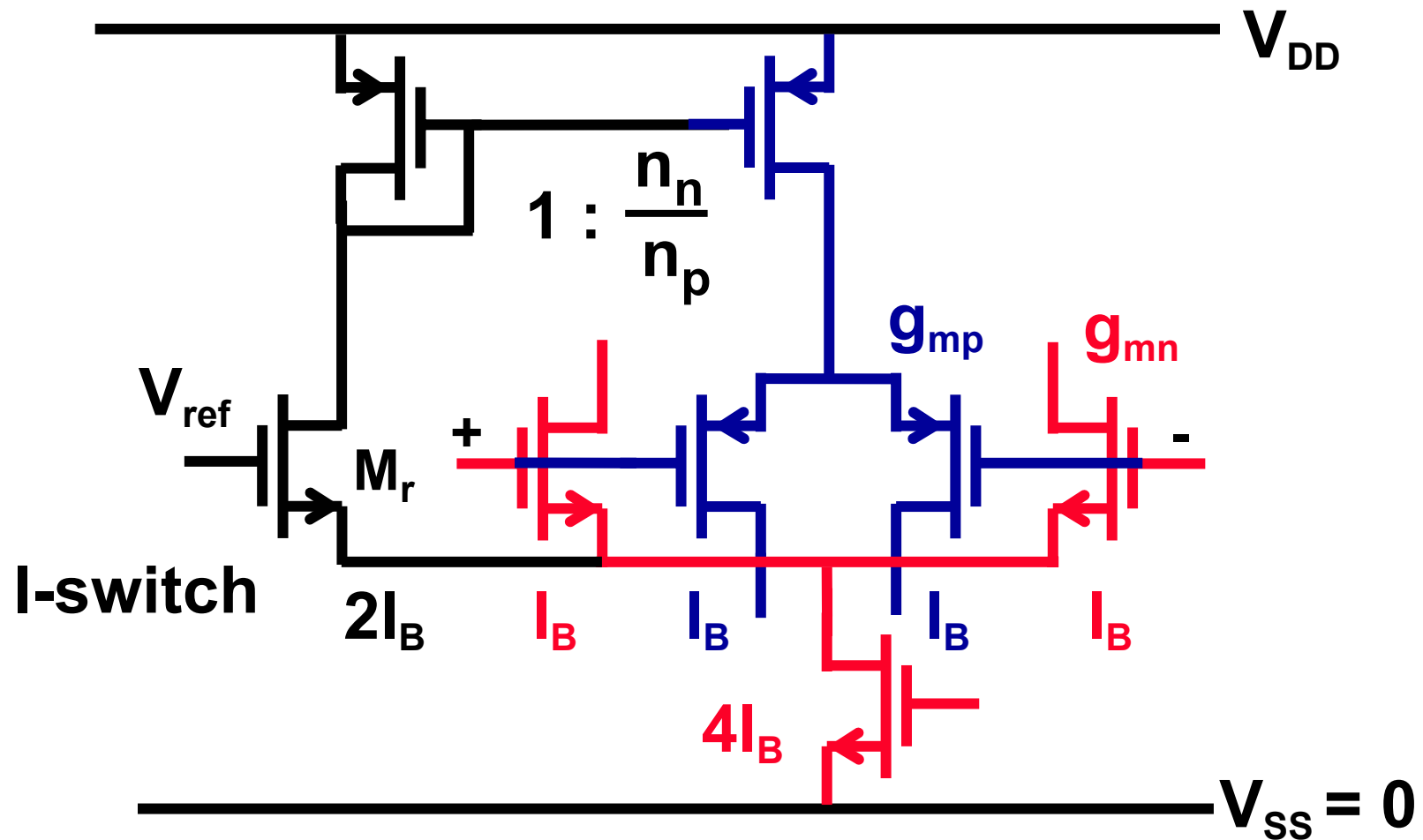
# Rail-to-rail amplifier with current switch



---

# Rtr amp. with I-switch : performance


---

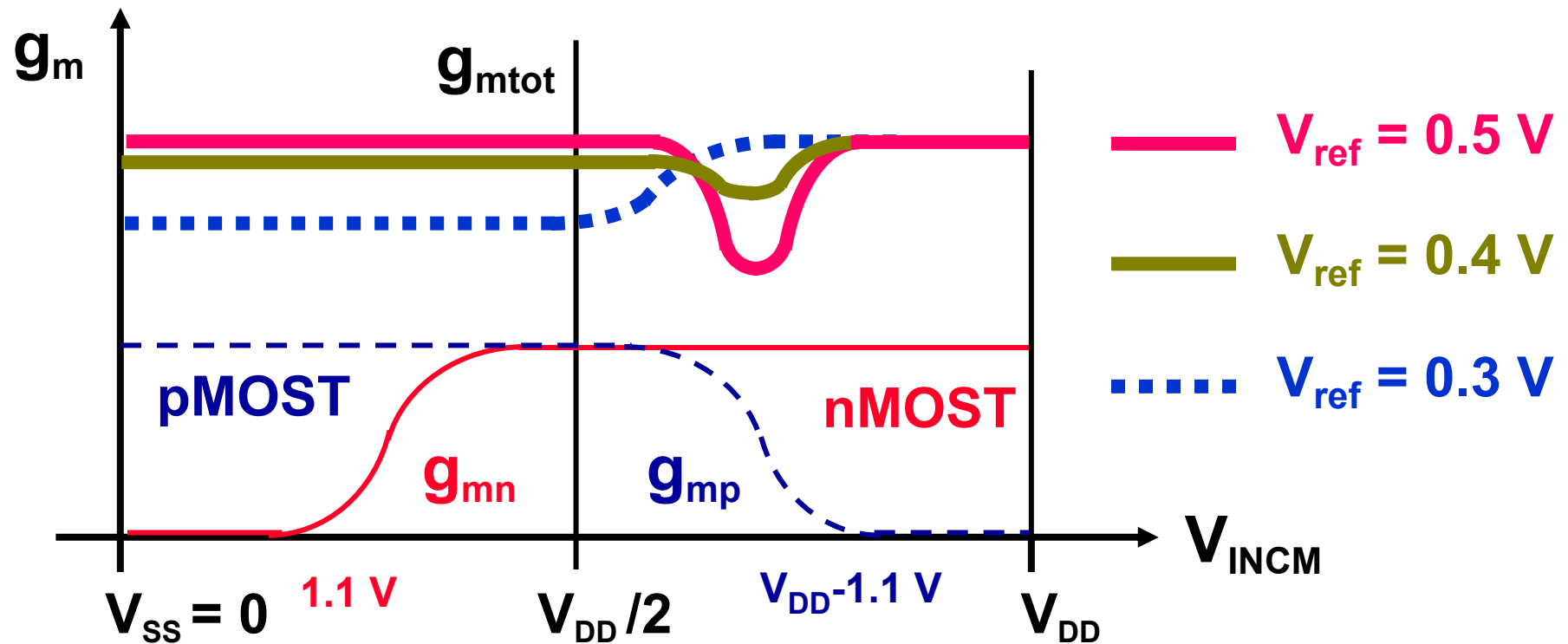

**Current switch :  $V_{ref}$  very critical !**



Ref. : Wu etal, JSSC Jan.1994, pp.63-66


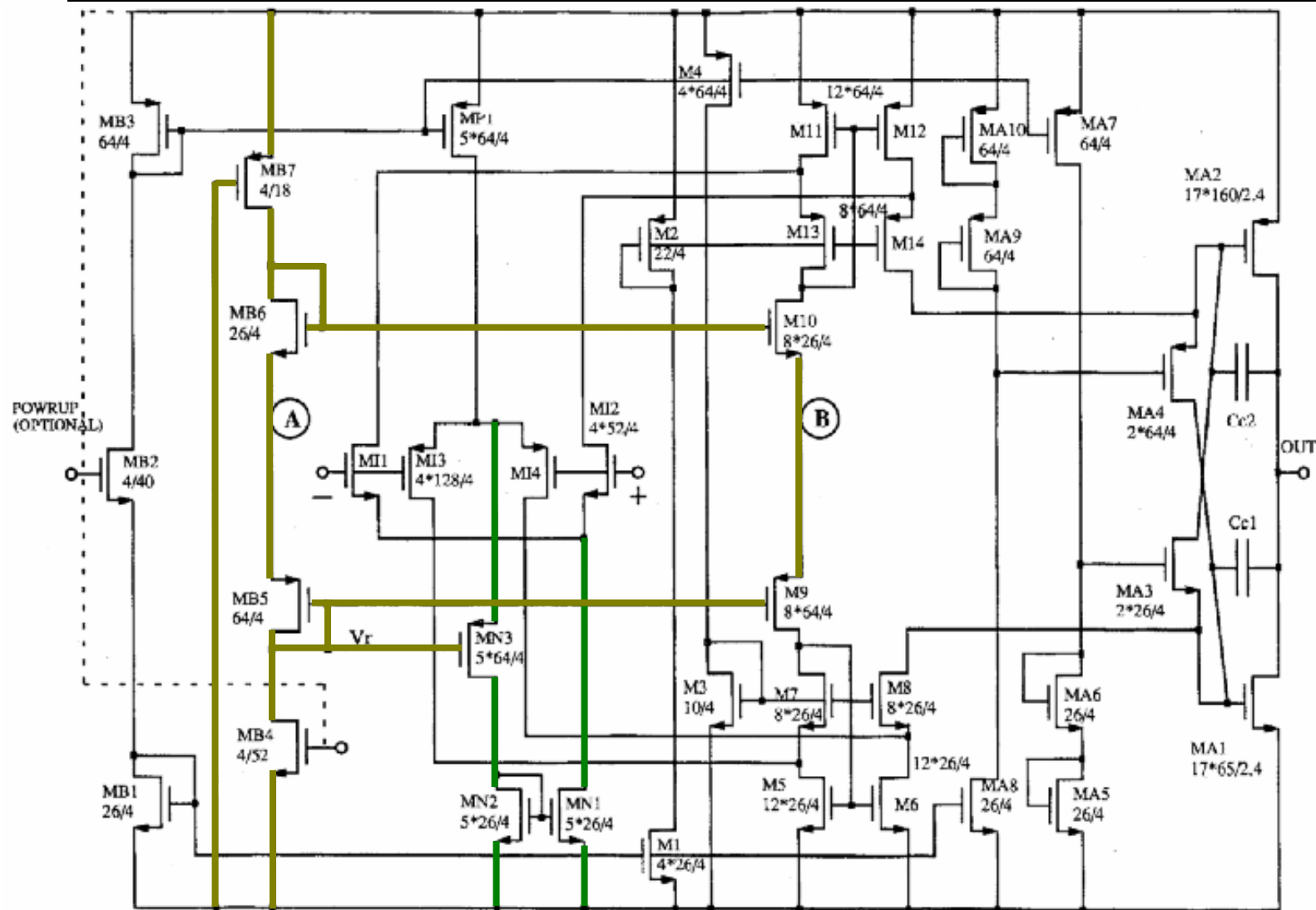


Biasing :

$$I_{DS} \times 2$$

$$g_m \times 2$$

# Input rail-to-rail stage

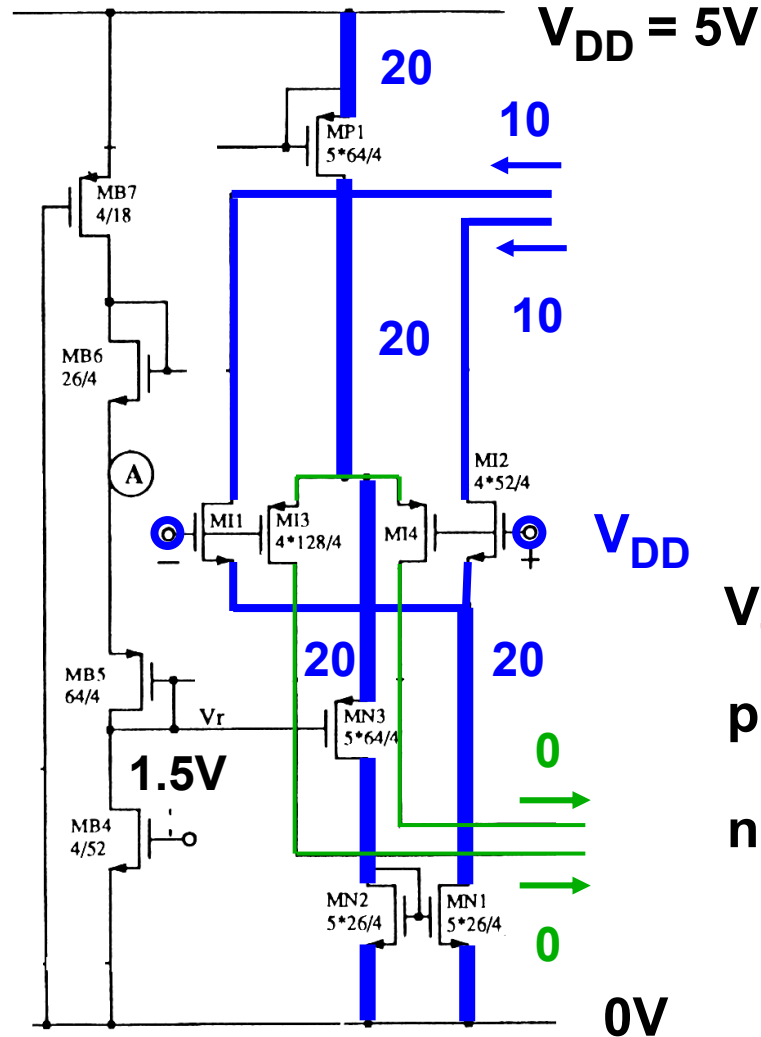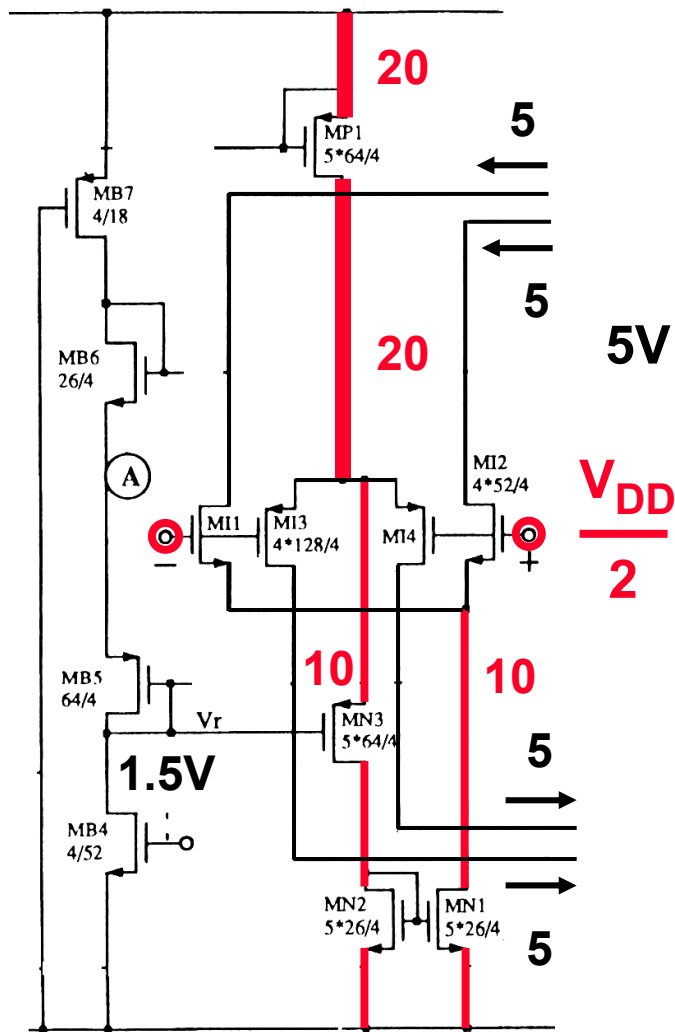

$V_{+}$  high :


pMOSTs off !

nMOSTs :


$$I_{DS1} \times 2$$

$$g_{m1} \times 2$$

# Current regulator FB loop

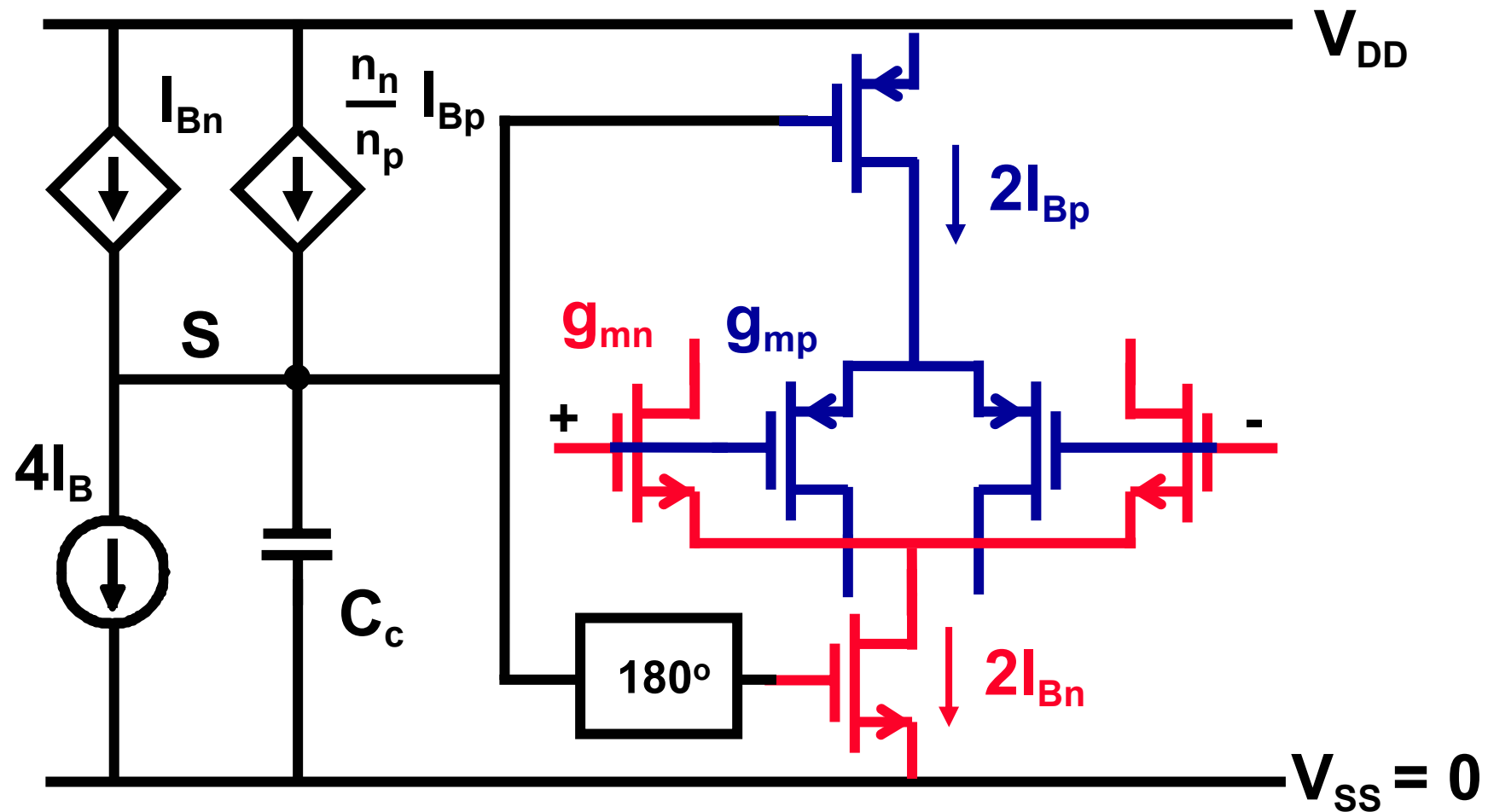

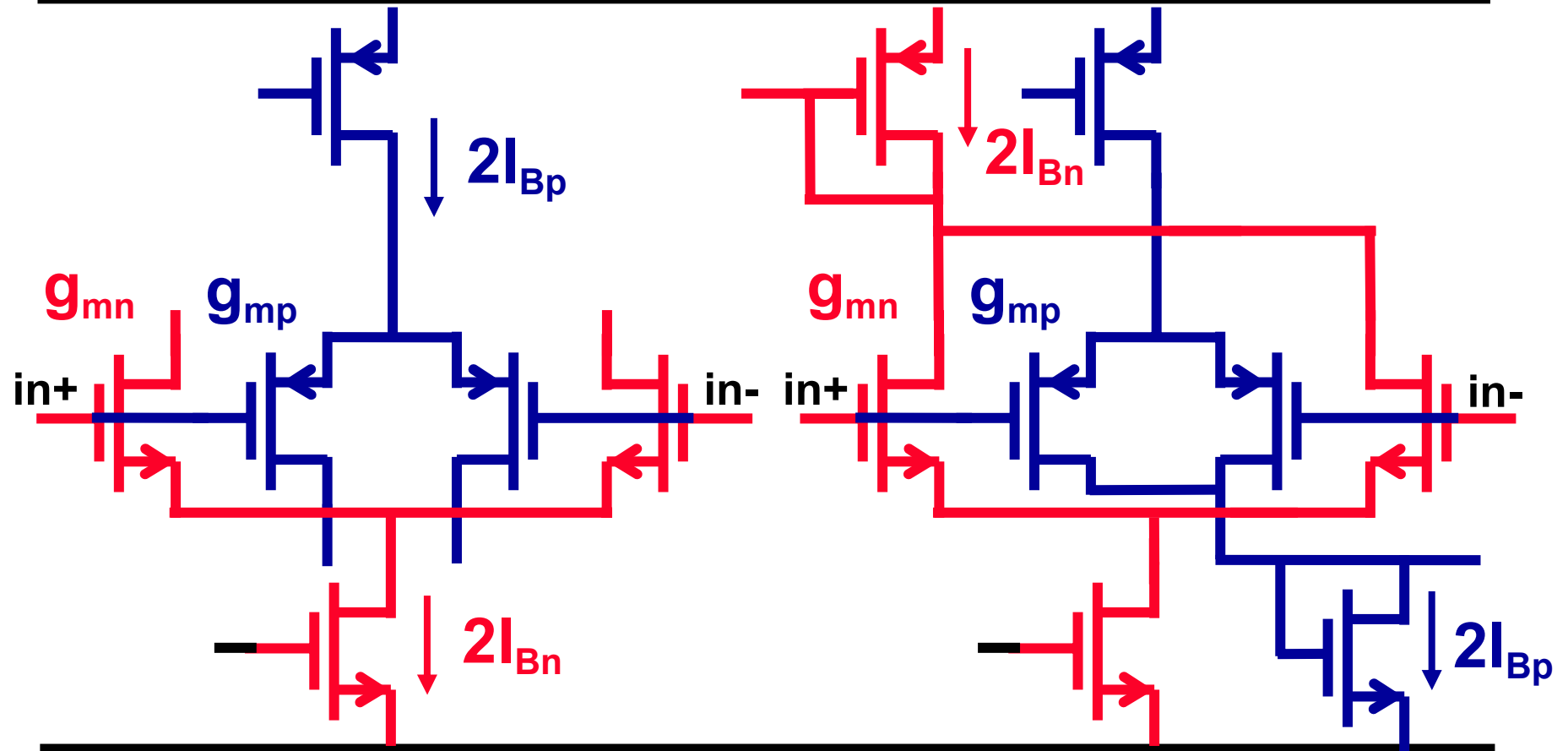
# Current regulator FB loop : replica biasing



---


# Replica biasing with one transistor

---

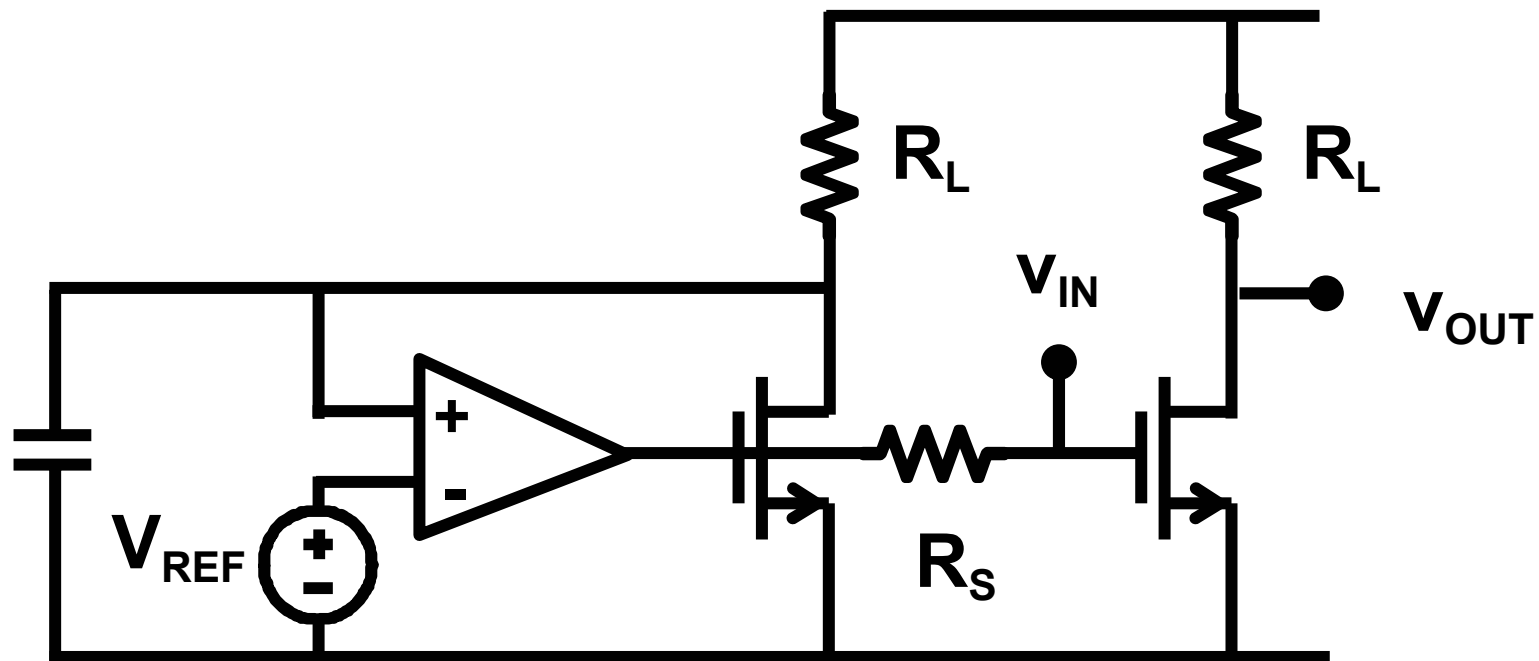



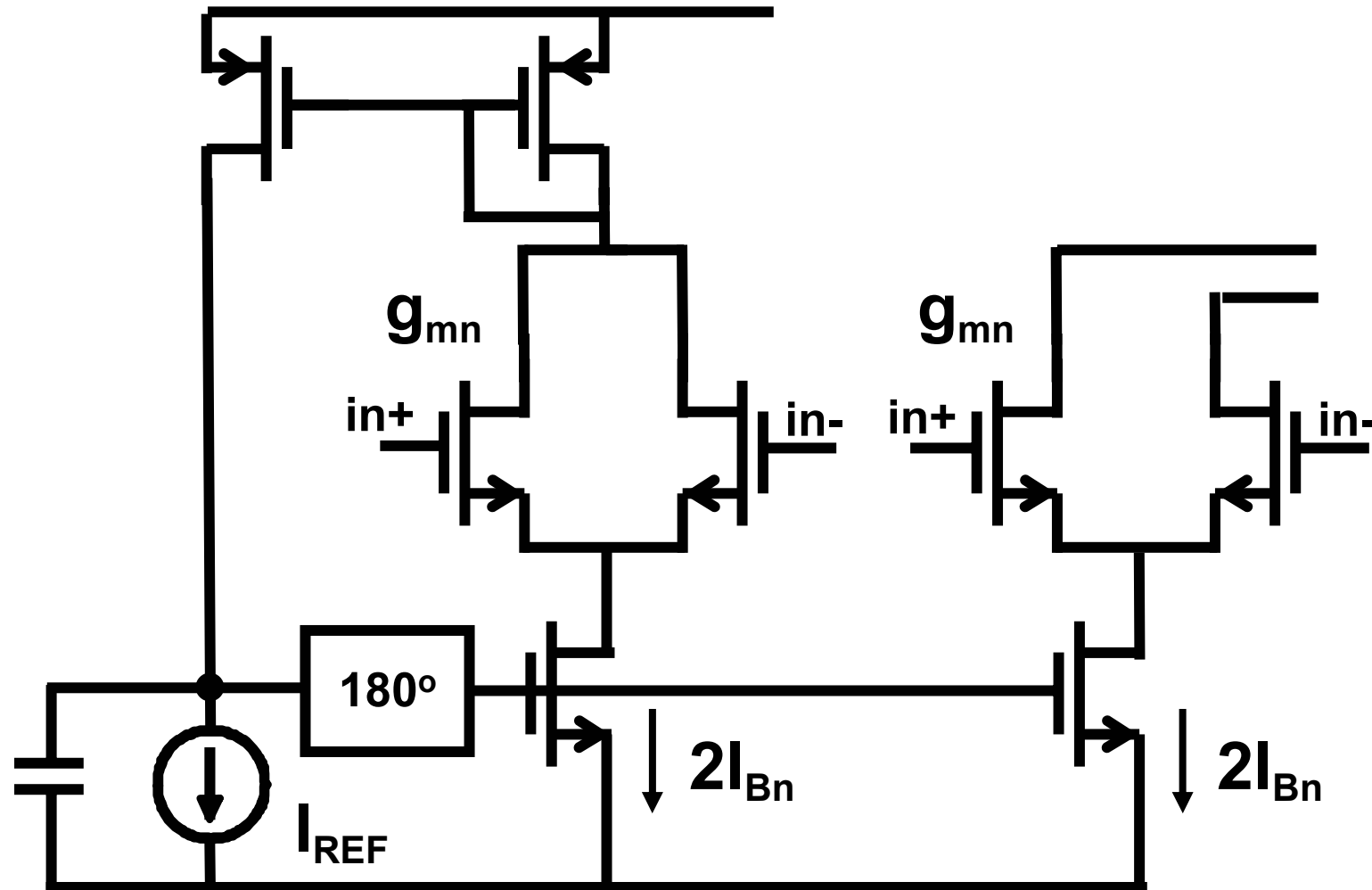
## Replica biasing with differential pair




---

# Current regulator rail-to-rail amplifier

---

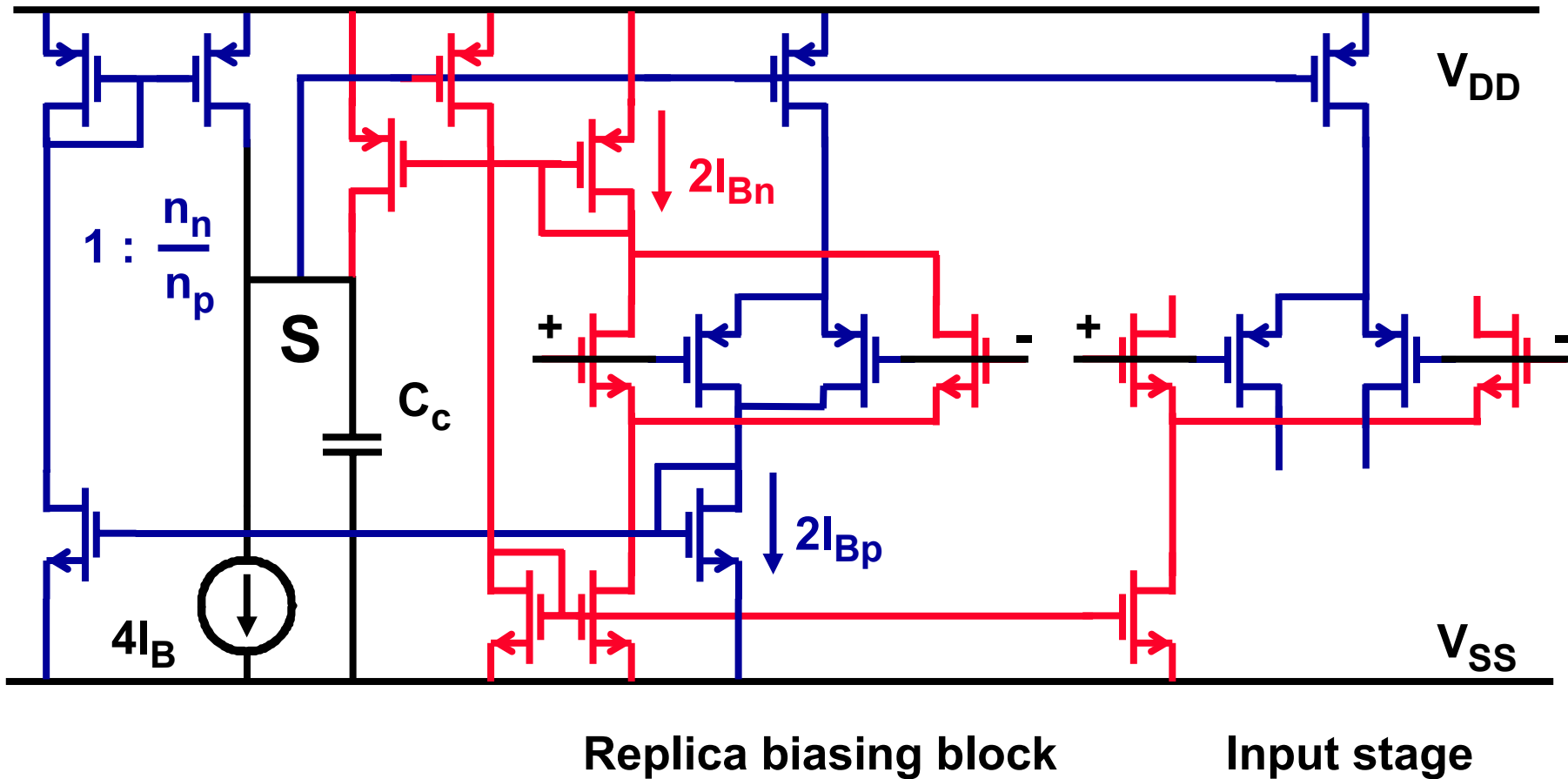

# I-regulator rtr amplifier

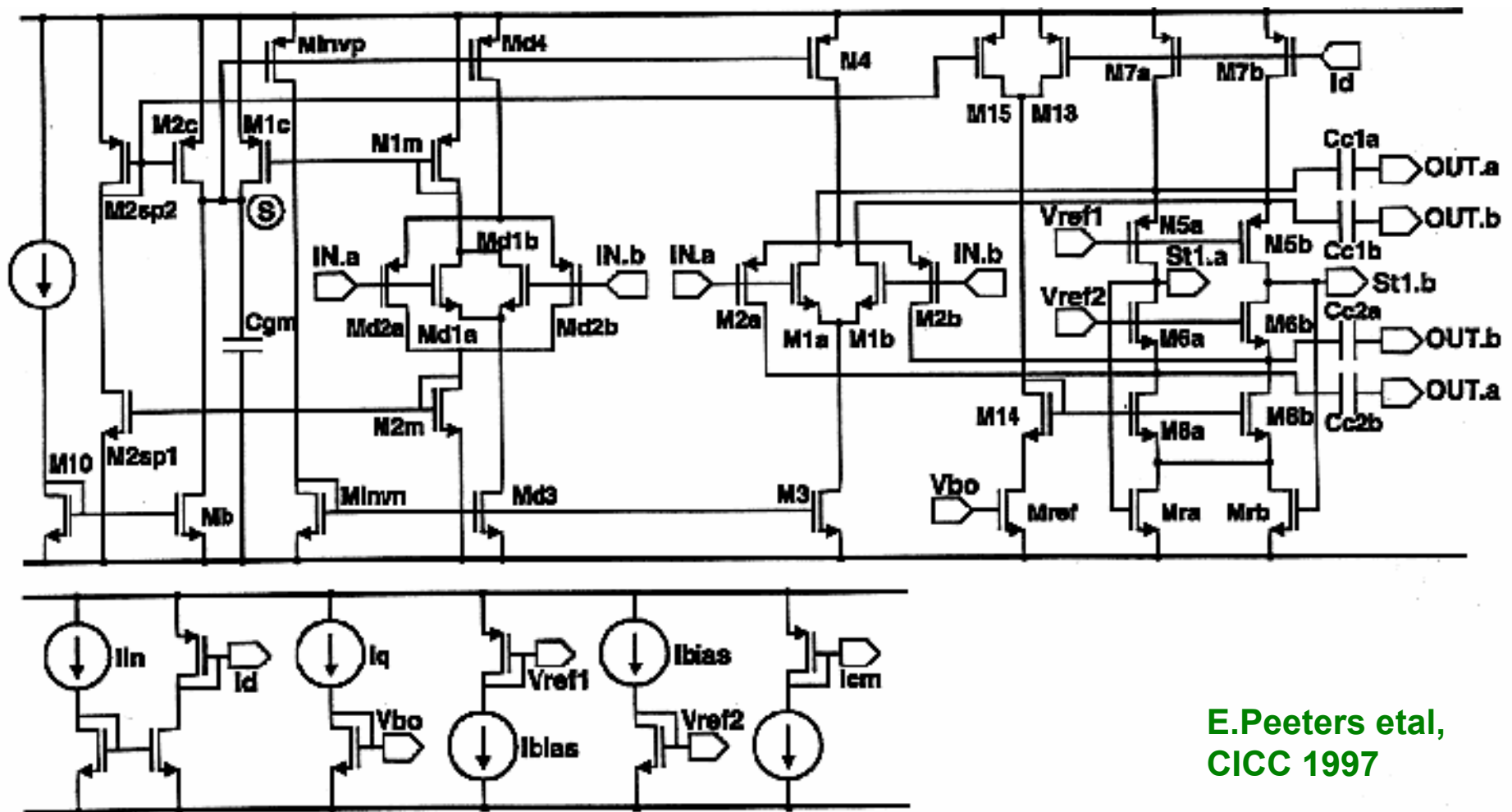

E.Peeters et al,  
CICC 1997


[illegible]

**Willy Sansen 10-05 1136**


---

**Output stage**

---

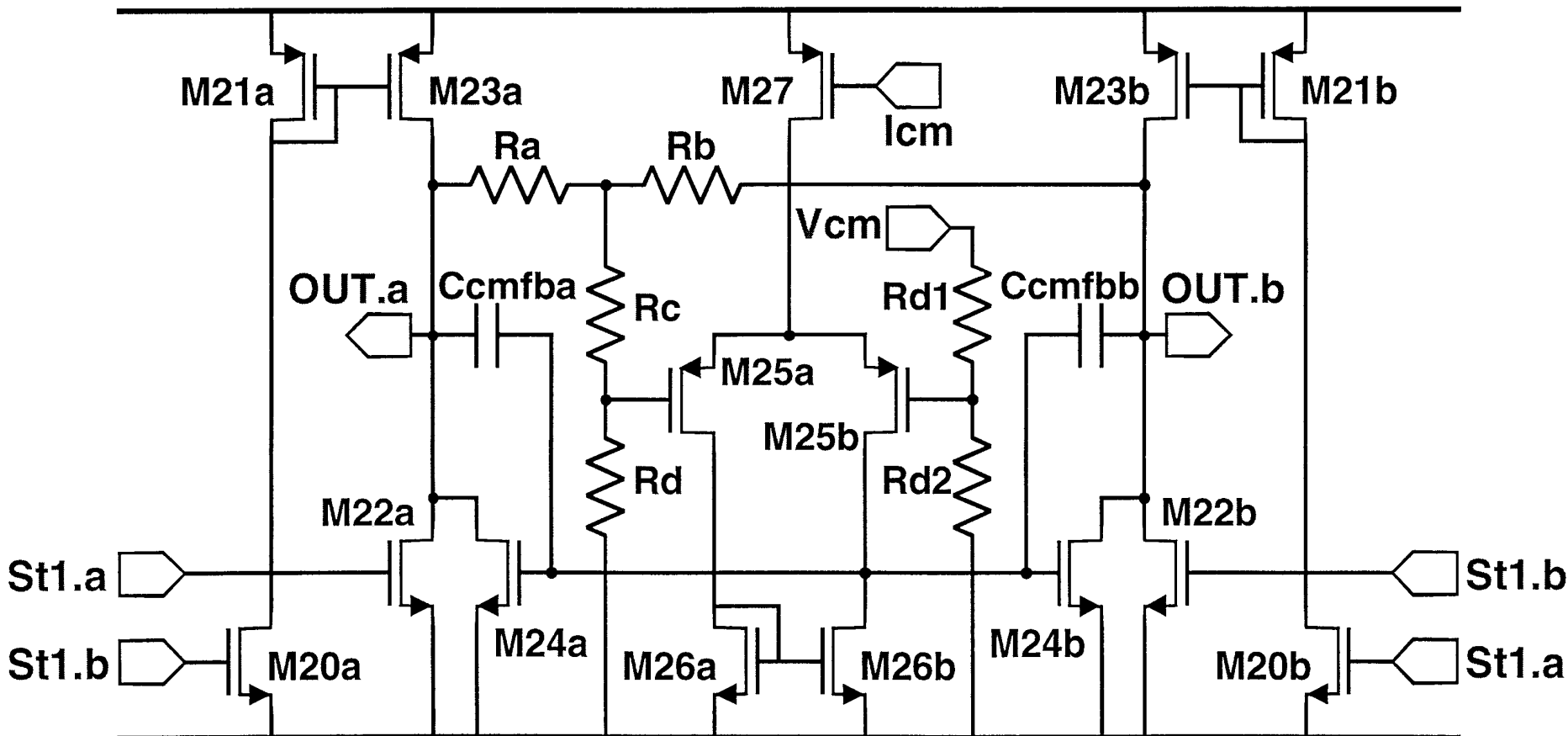
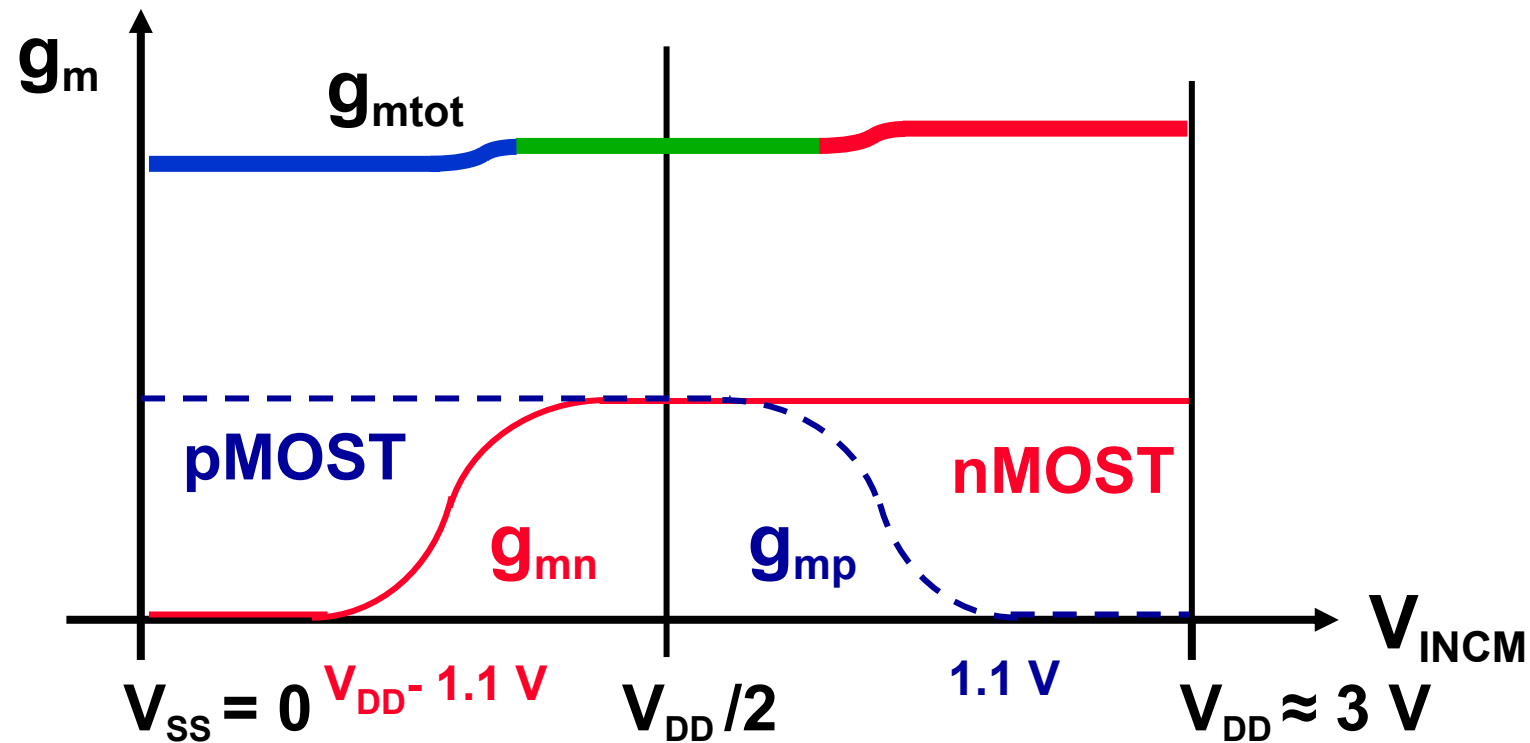
# Current-regulator rtr amp. : performance




n - mismatch :  $\Delta g_m / g_m \approx 4\%$

---

## Current-regulator rtr amp. : towards 1.5 V

---

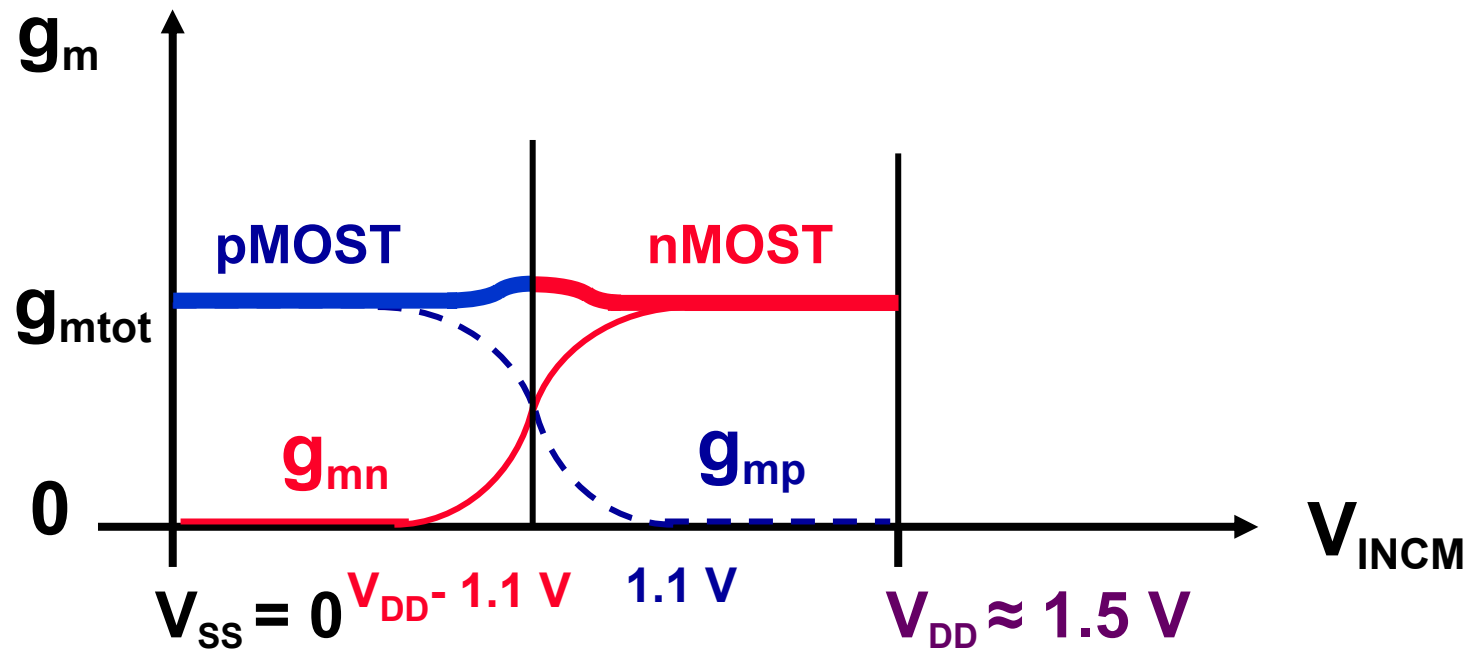


n - mismatch :  $\Delta g_m / g_m \approx 4\%$

---

# GBW error

---

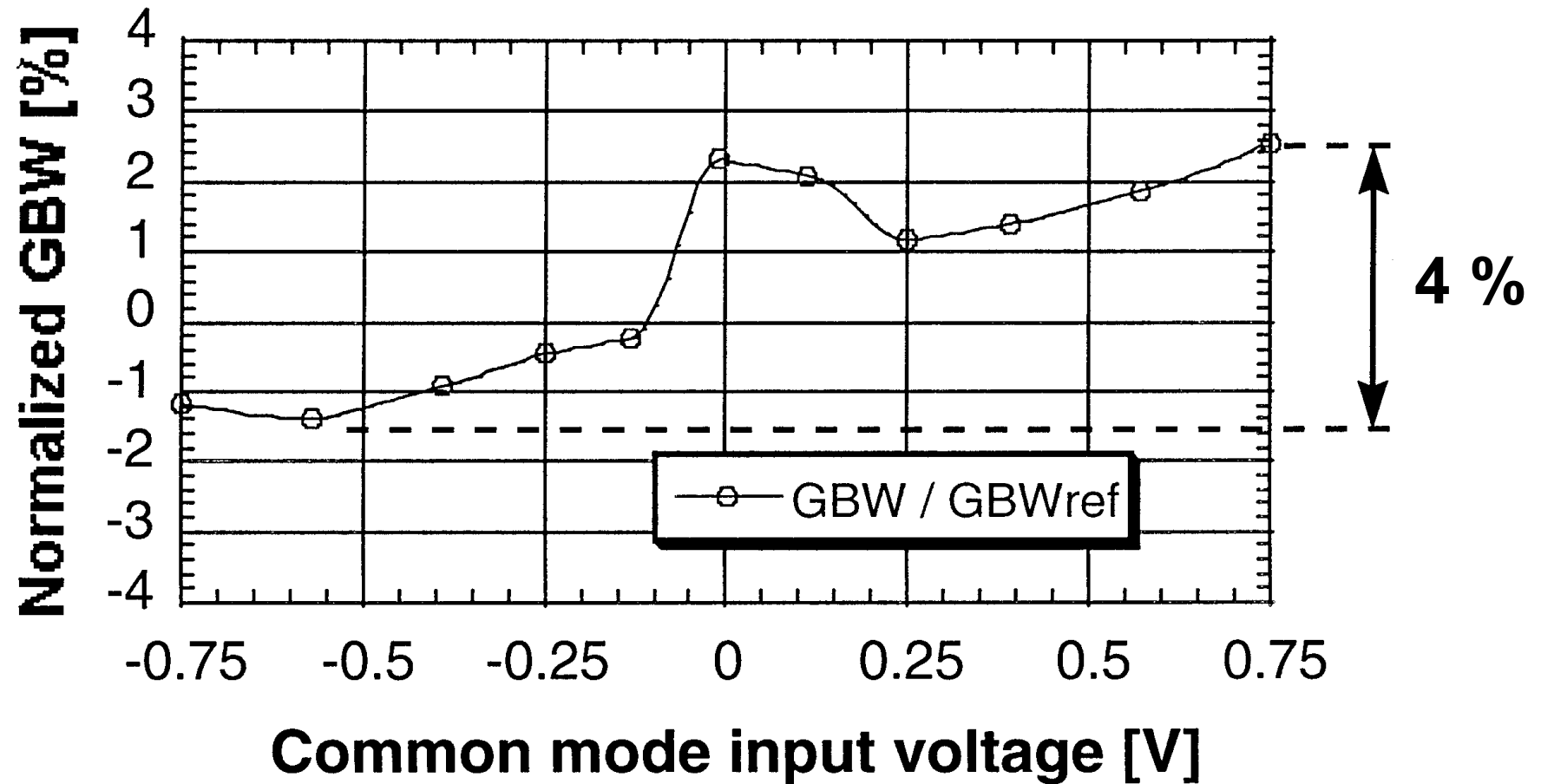




---

# Input offset voltage


---

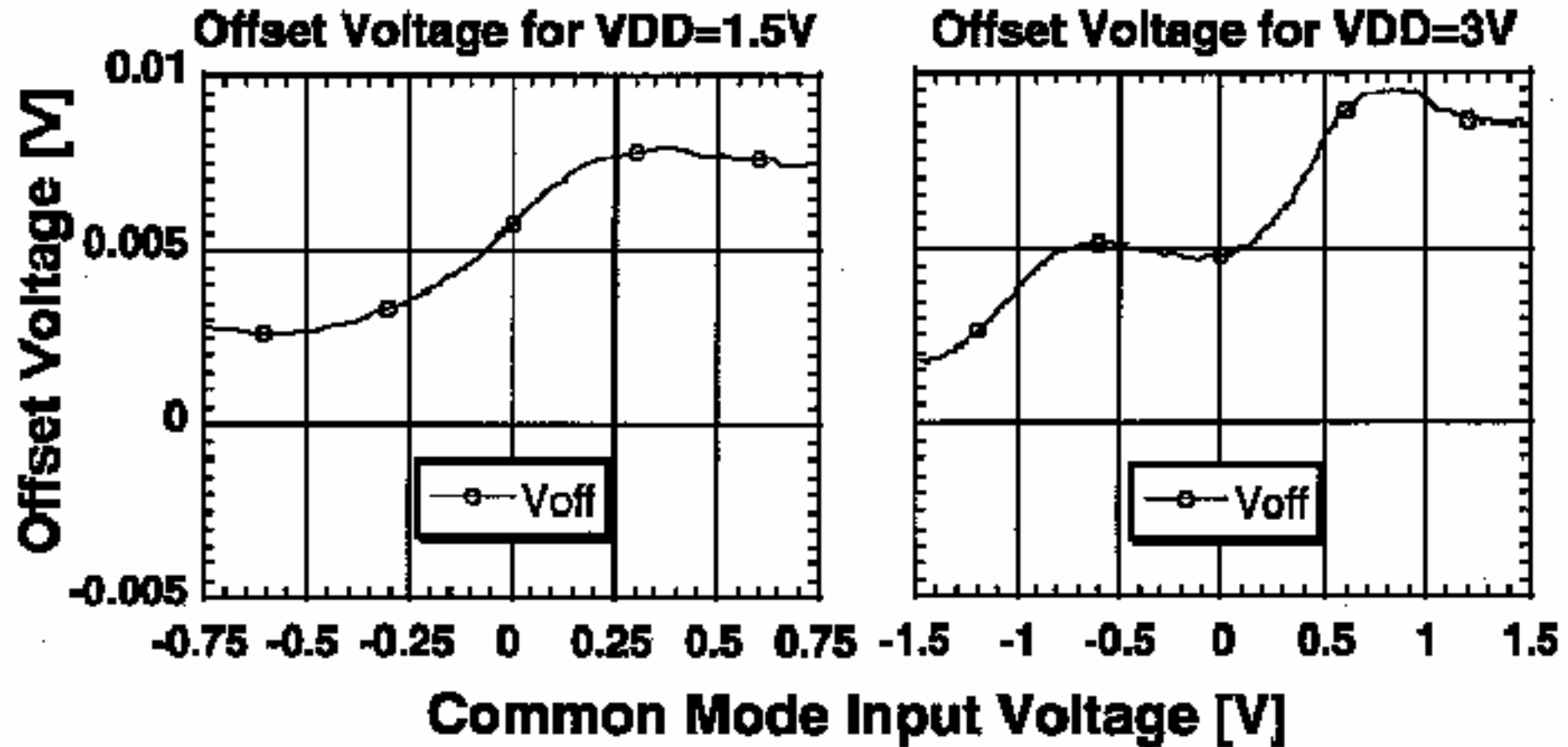

---

# Rail-to-rail Opamp with Current regulator

---

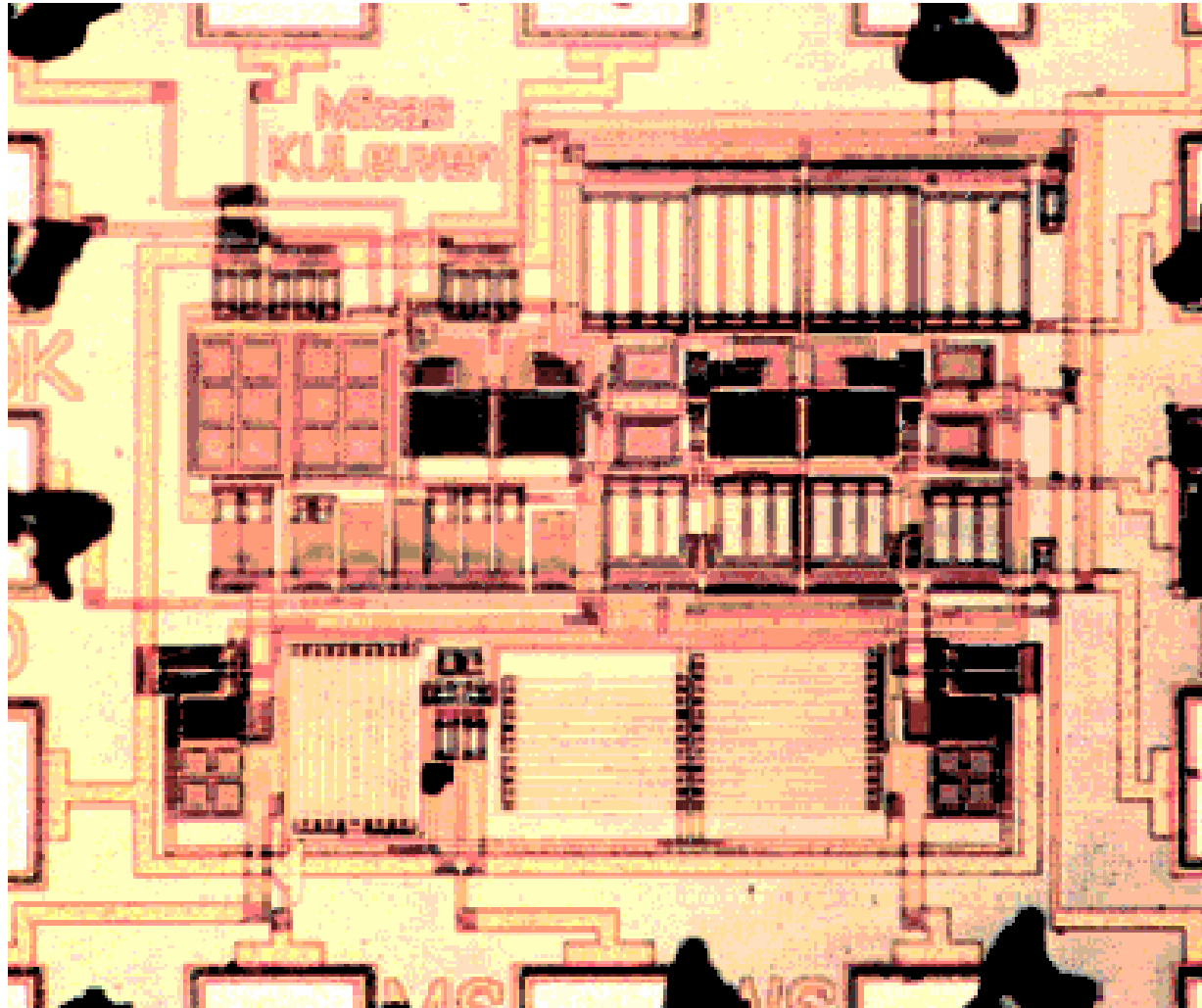

$$V_{DD} = 1.5 \text{ V}$$

$$I_{TOT} = 0.2 \text{ mA}$$

$$\Delta g_m / g_m = 4 \%$$

$$GBW = 4.3 \text{ MHz}$$

$$C_L = 15 \text{ pF}$$

E.Peeters et al, CICC 1997

---

# Table of contents


---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**

# Internal $V_{DD}$ Regulator

Weak inversion :

$$I_{Bn} + \frac{n_n}{n_p} I_{Bp} = ct$$

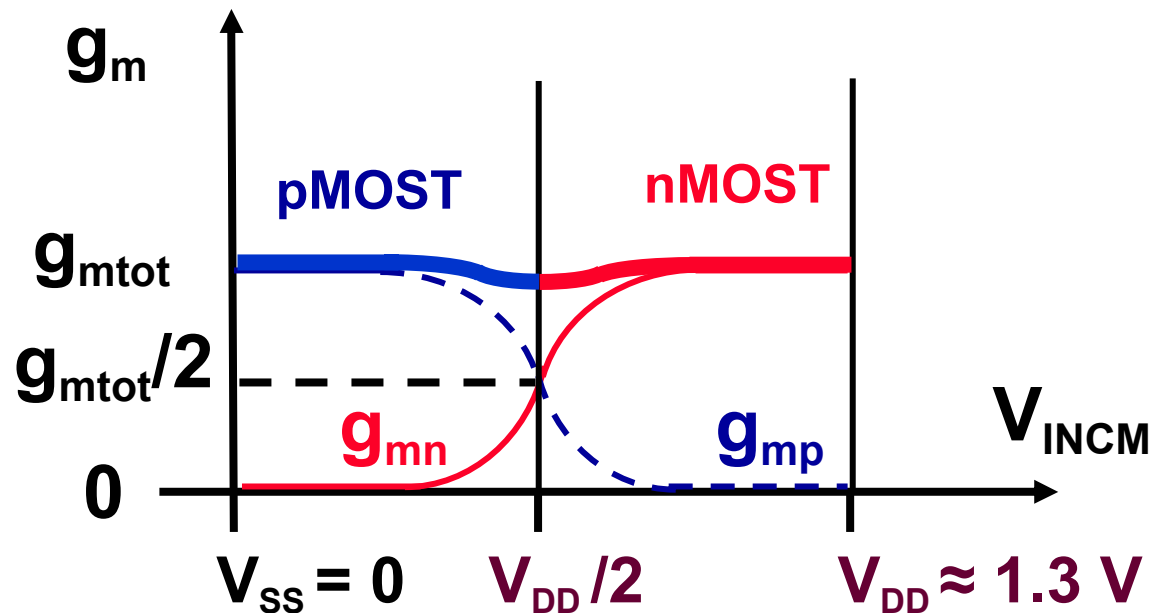


Minimum  $V_{DD}$  ?

Minimum  $V_{GS} + V_{DSsat}$  ?


Independent of  $\Delta V_T$ 's !

n - mismatch and  $g_{mtot}$  dip :  $\Delta g_m / g_m \approx 15 \%$

# Regulating $V_{DD}$ : total schematic

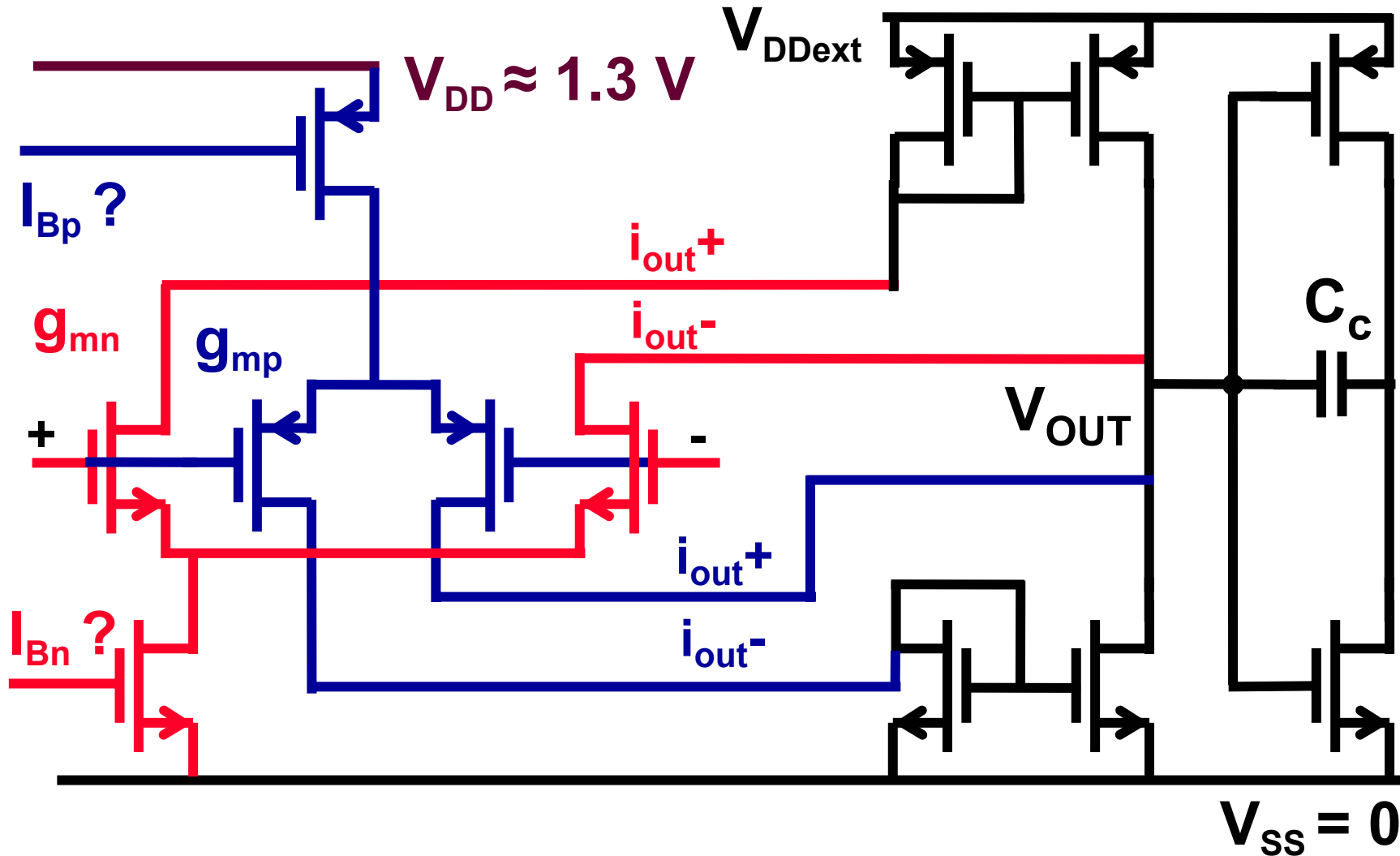


# Replica biasing block

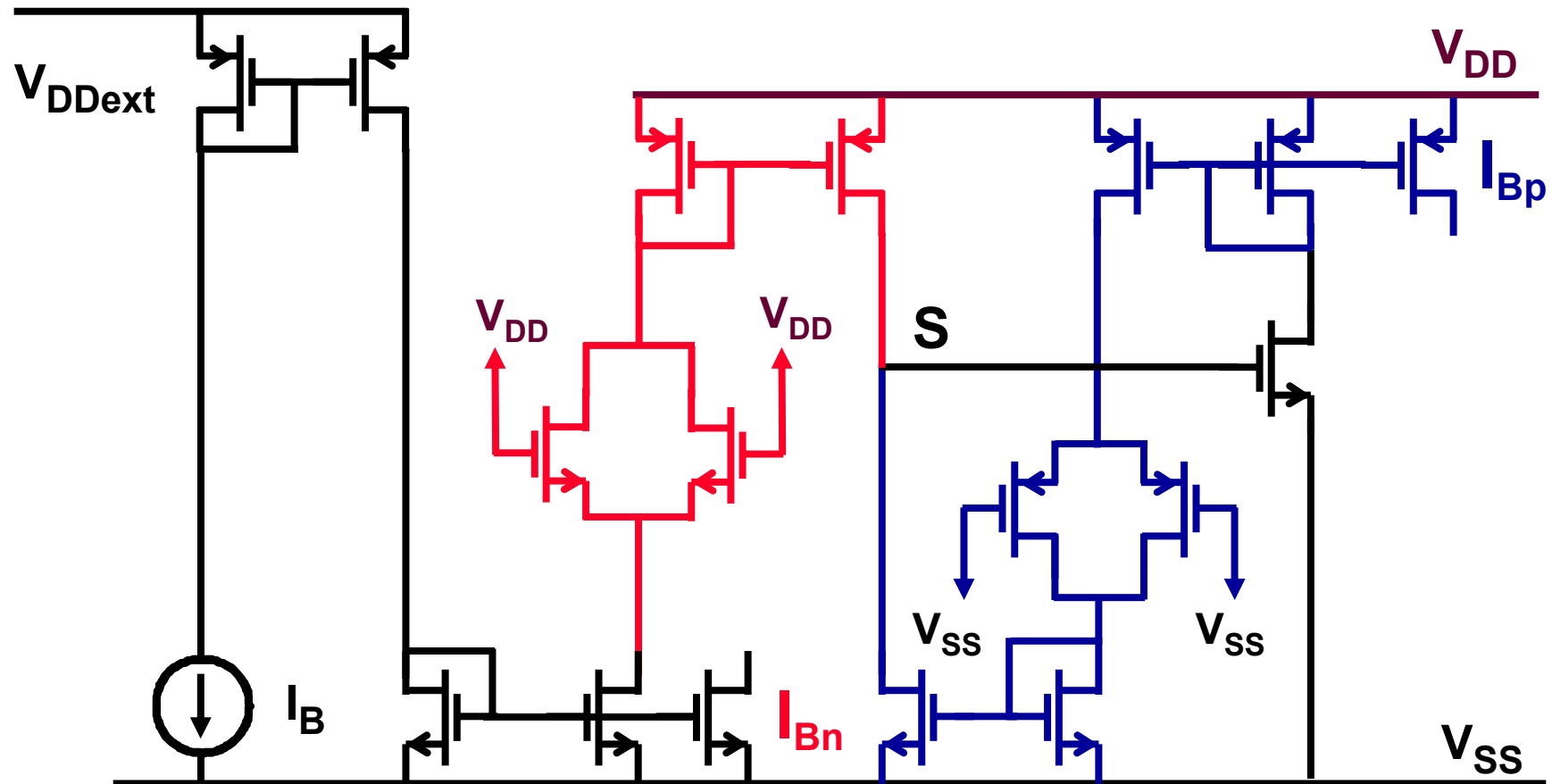


Ferri, .. JSSC Oct.97, 1563-1567

# Internal $V_{DD}$ regulator

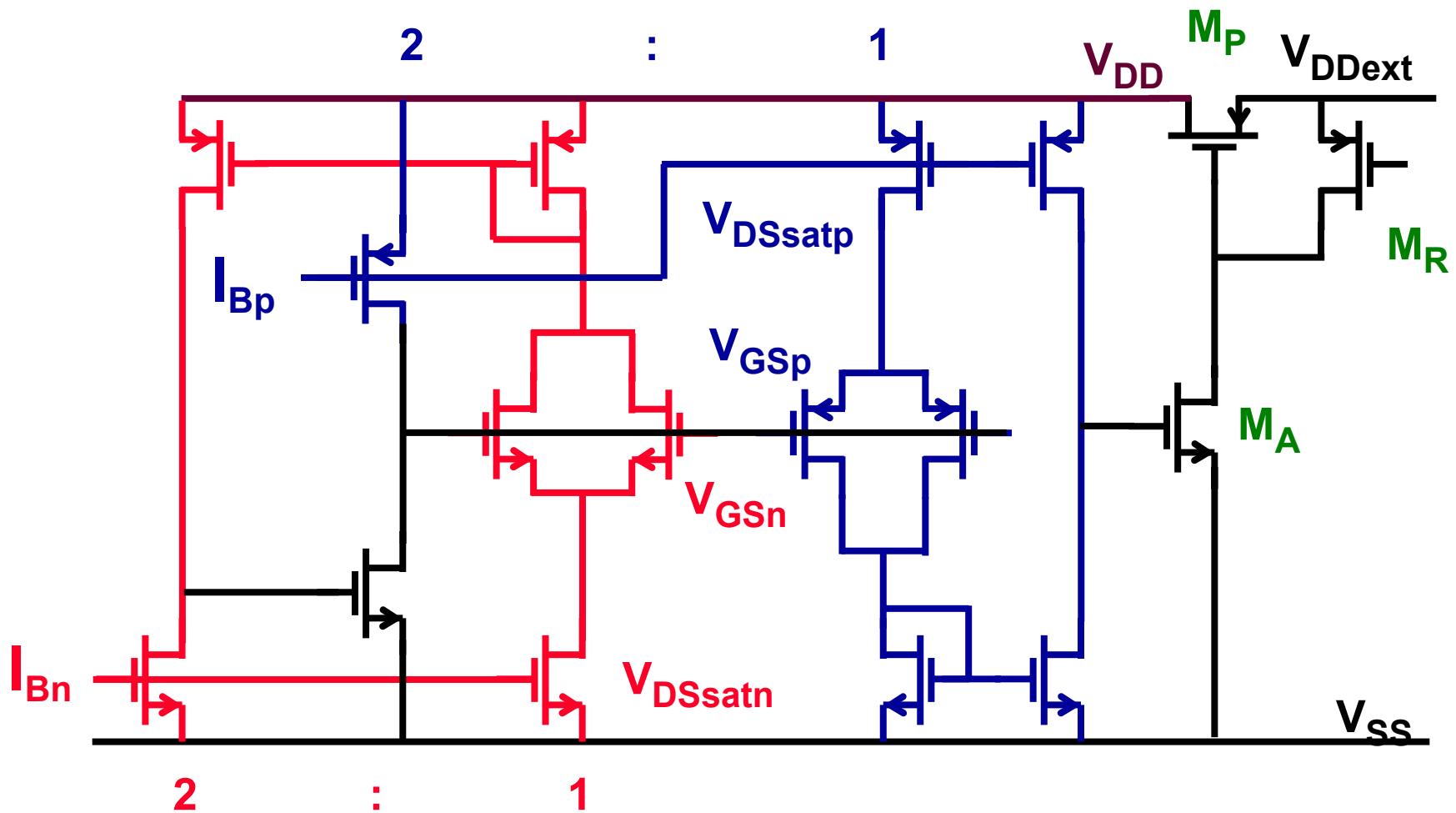

## Total amplifier schematic

## Vext

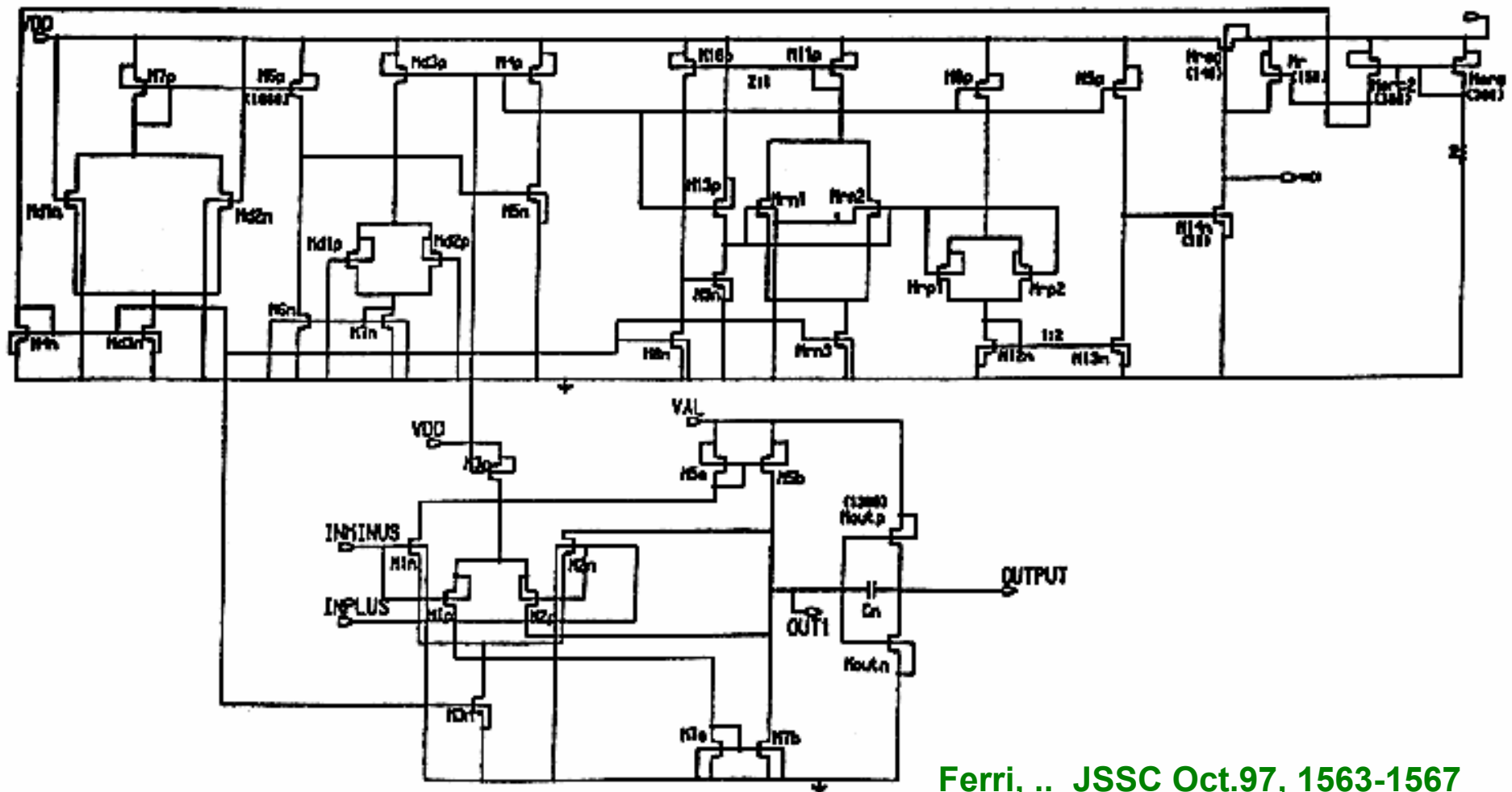


**Ferri, .. JSSC Oct.97, 1563-1567**



---

# Internal supply voltage


---

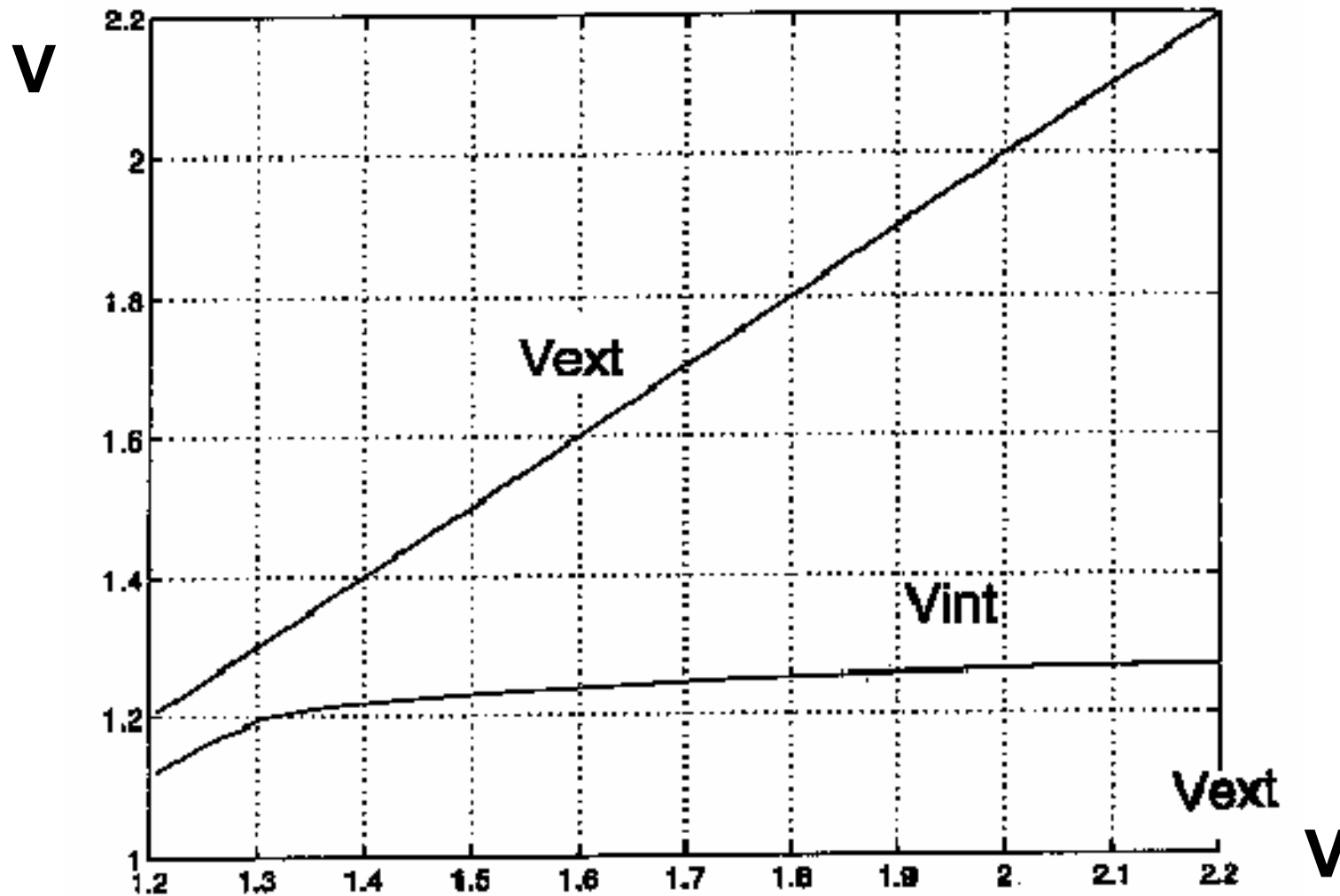

---

# GBW error

---

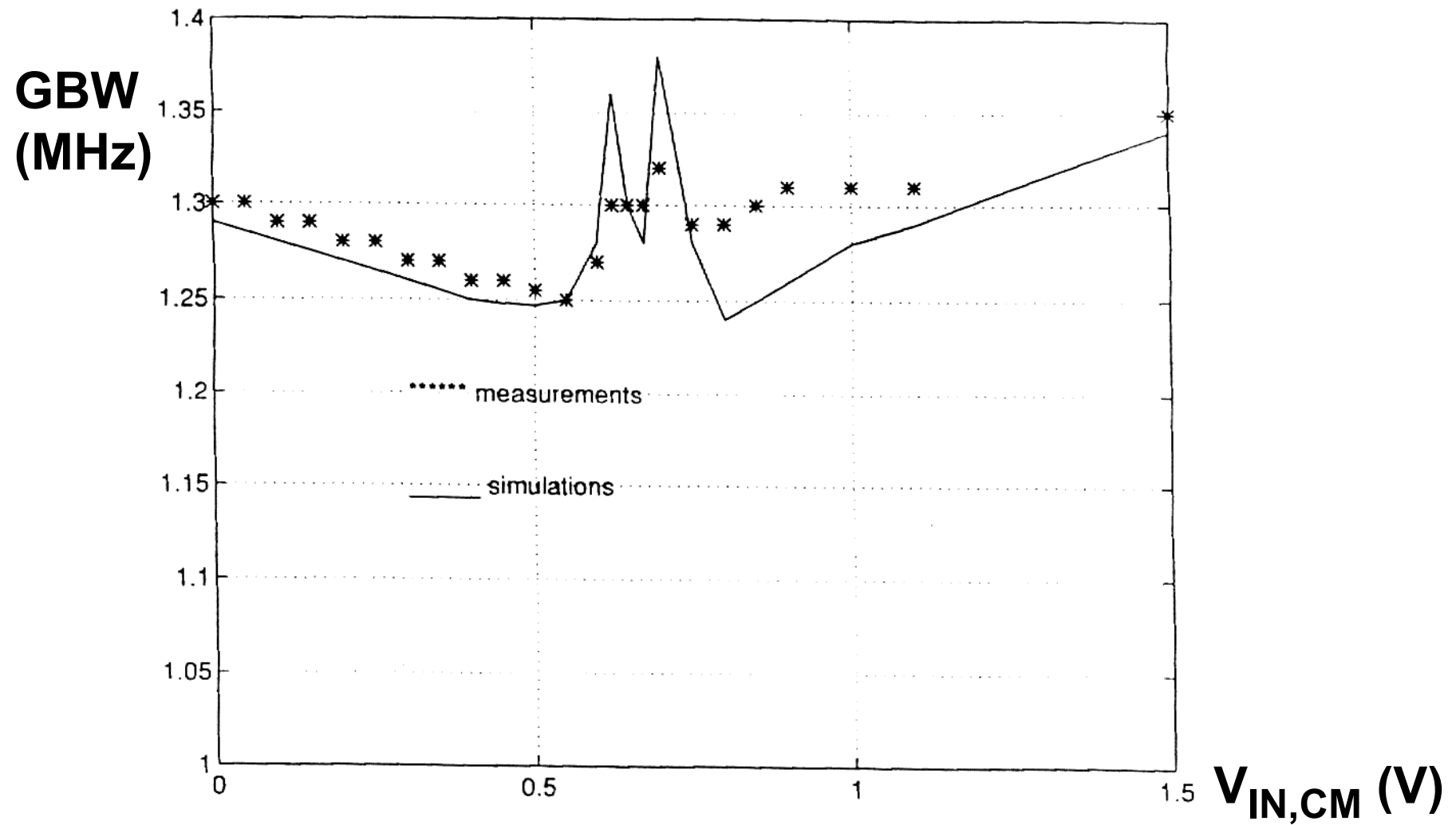

---

## Rail-to-rail amp. with $V_{DD}$ regulator : Specs

---

$$V_{DDmin} = 1.3 \text{ V}$$

$$GBW = 1.3 \text{ MHz in } C_L = 15 \text{ pF}$$

$$g_{m1} = 200 \text{ } \mu\text{S}$$

$$I_{DSn1} = 10 \text{ } \mu\text{A}$$

$$W/L_{in} = 830$$

$$I_{TOT} = 354 \text{ } \mu\text{A}$$

$$V_{in,eq} = 25 \text{ nV}_{RMS}/\sqrt{\text{Hz}}$$


$$V_{in,offset} = 0.8 \text{ mV } (3\sigma = 0.2 \text{ mV})$$

Ferri, .. JSSC Oct.97, 1563-1567

---

# Rtr Opamp with $V_{DD}$ -regulator

---

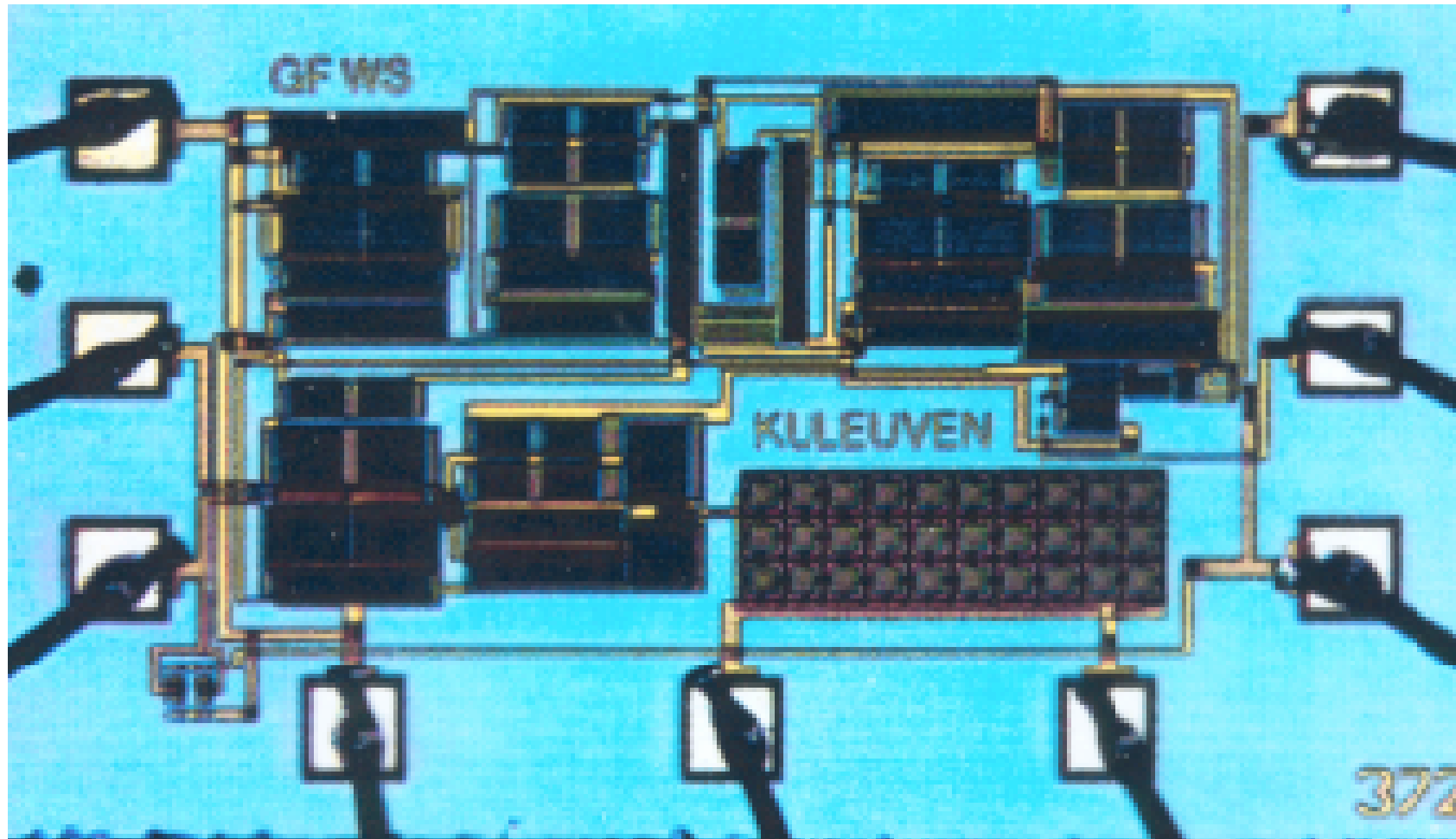

---

## Rail-to-rail with $V_{DD}$ regulator : min $V_{DD}$

---

$$\begin{aligned} V_{DDmin} &= 2 (V_{GS} + V_{DSsat}) \\ &= 2 (V_{GS} - V_T + V_T + V_{GS} - V_T) \\ &= 2 [V_T + 2(V_{GS} - V_T)] \\ &= 2 [0.6 + 2(0.15)] = 1.8 \text{ V} \\ \\ &= 2 [0.3 + 2(0.10)] = 1.0 \text{ V} \quad !!!! \end{aligned}$$


---

# Table of contents

---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**
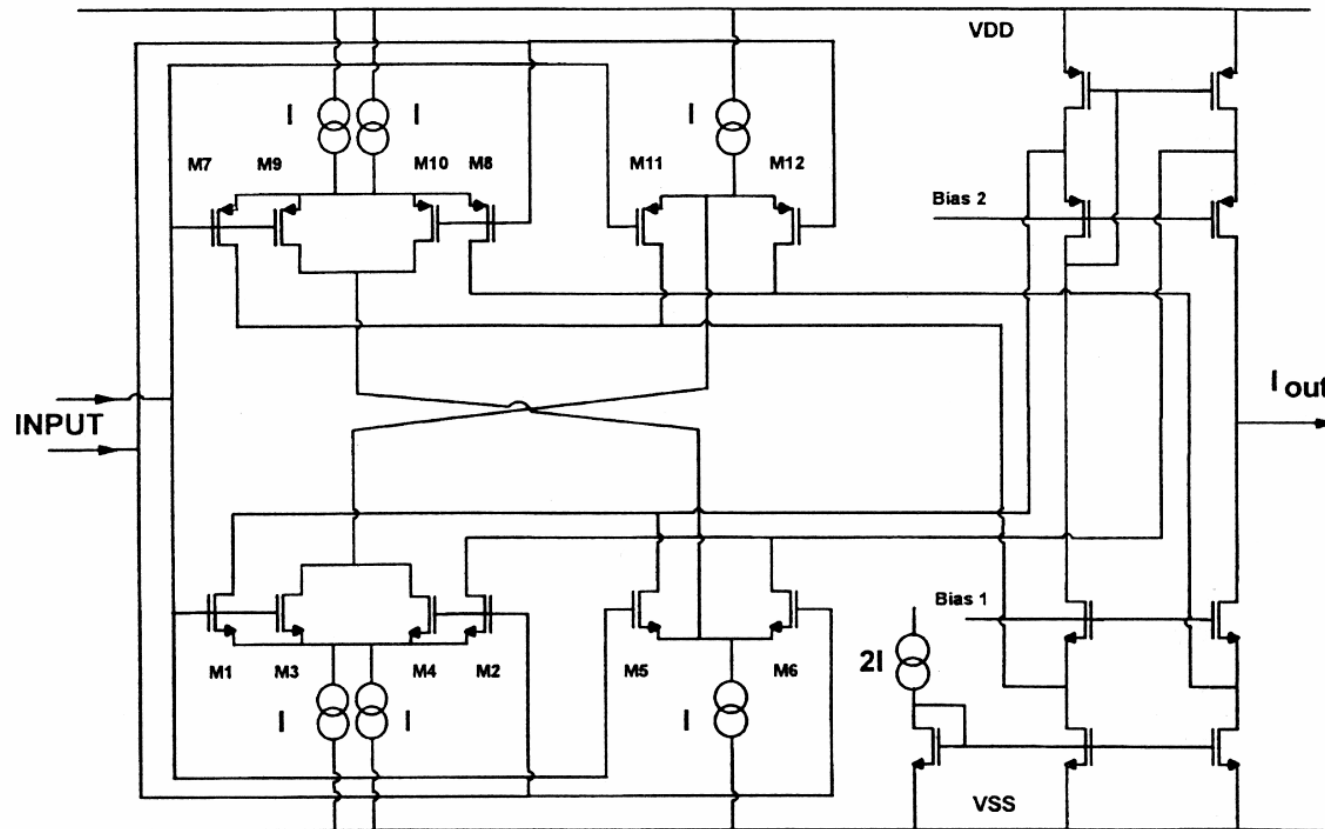
# Rail-to-rail opamp with current summation



3.3 V

2.3 mW

(2.2 V min.)

$G_m \pm 10\%$

THD :

-55 dB


40 MHz

9 mW

0.5  $\mu\text{m}$  CMOS

Redman-White, JSSC May 97, 701-712

# Opamp with voltage multiplier

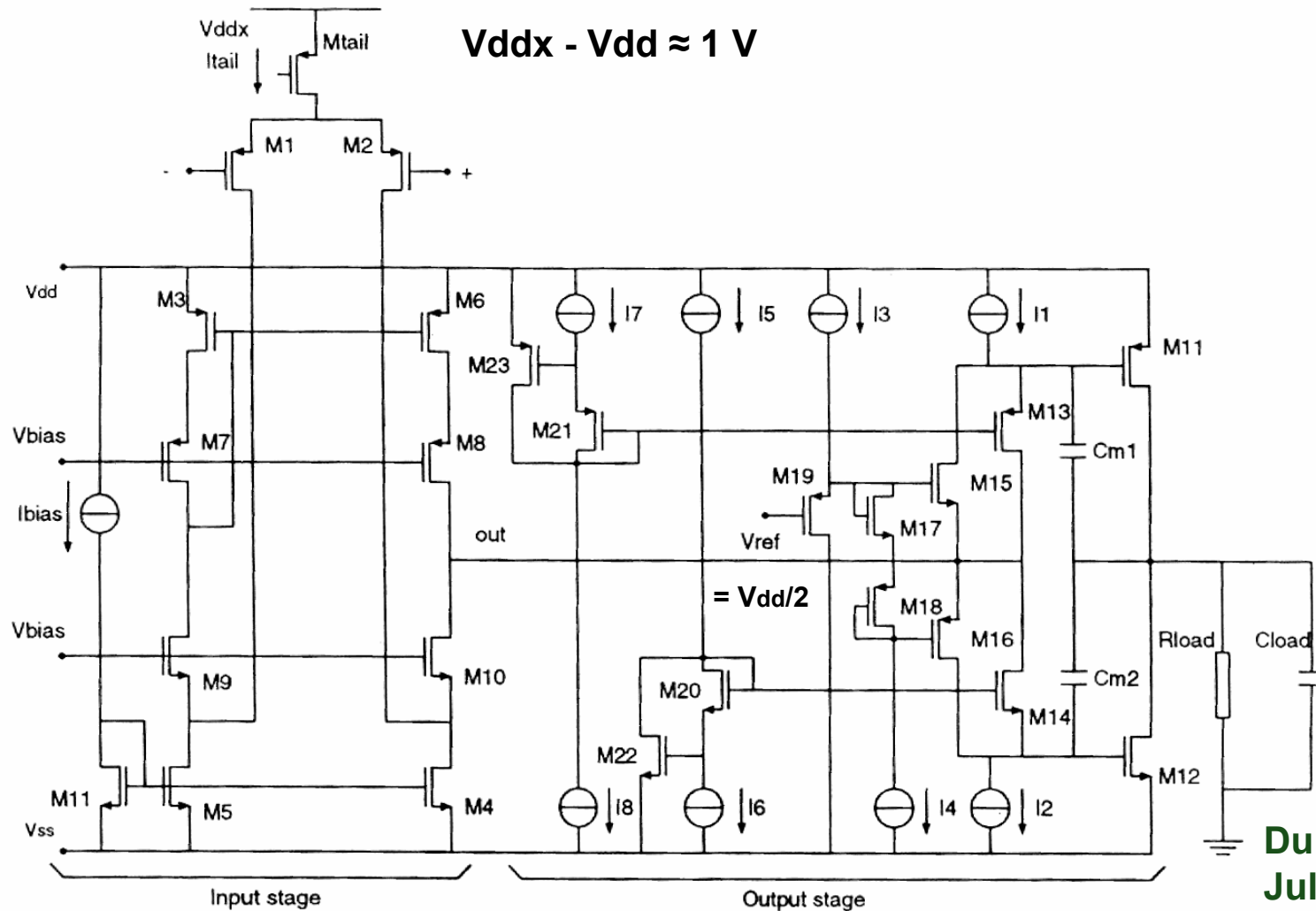

$V_{ddx} - V_{dd} \approx 1 \text{ V}$

1.8 - 3.3 V

0.75 mA

6.5 MHz

On 3 V :

2.8 V<sub>ptpt</sub>

THD :

-90 dB / 10k $\Omega$


-81 dB / 32  $\Omega$

0.5  $\mu\text{m}$  CMOS

Duisters, .., JSSC  
July 98, pp.947-955



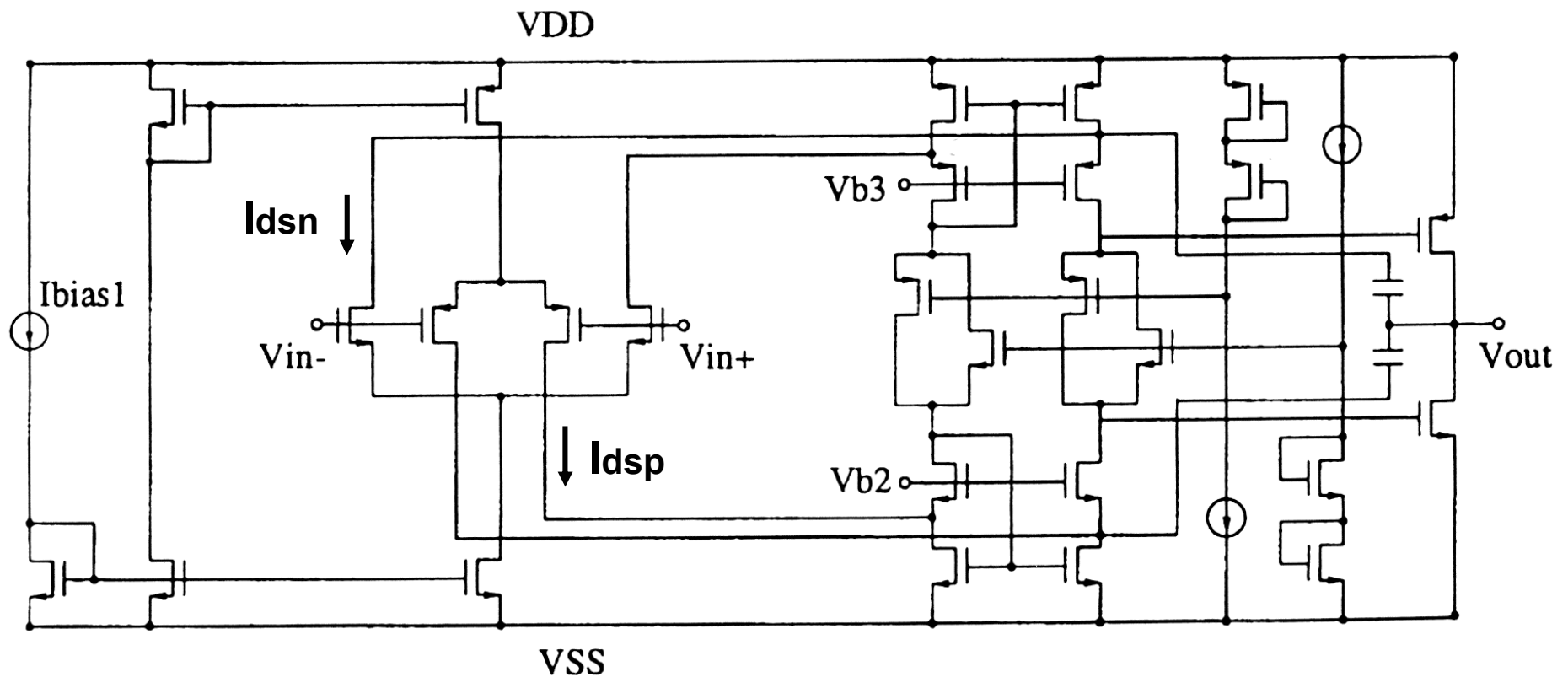
# Rail-to-rail opamp with differential signal proc.



Ref.Lin, AICSP 1999, 153-162


**Ref.Lin, AICSP 1999, 153-162**

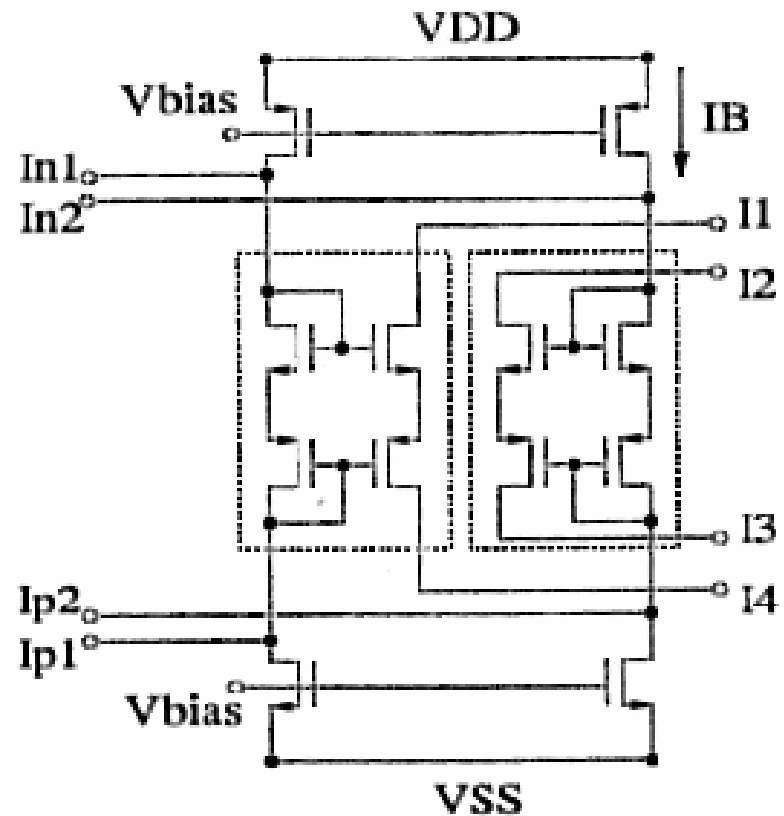


---

# Maximum-current selecting circuit

---

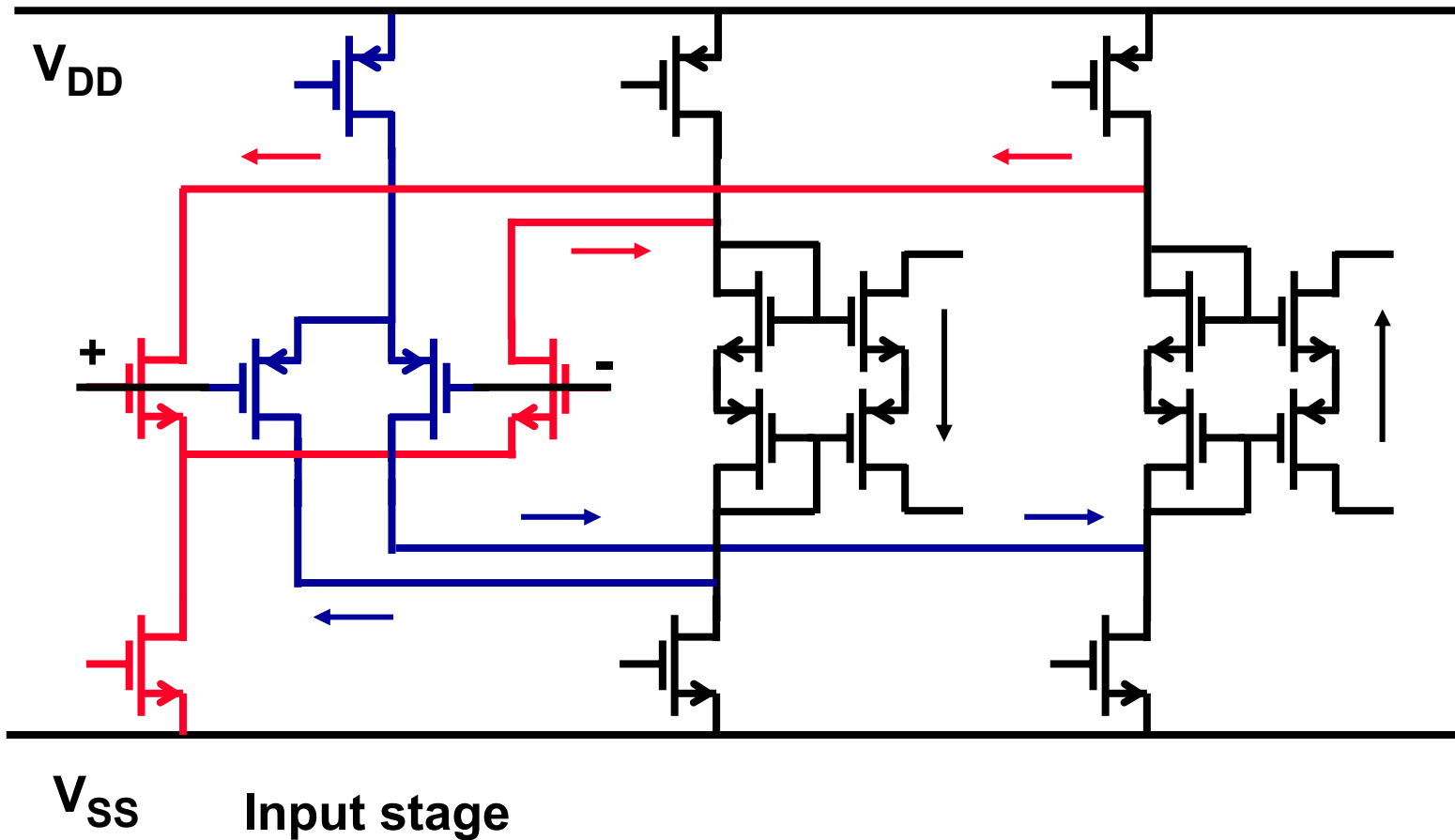

# Transconductance equalizer circuit

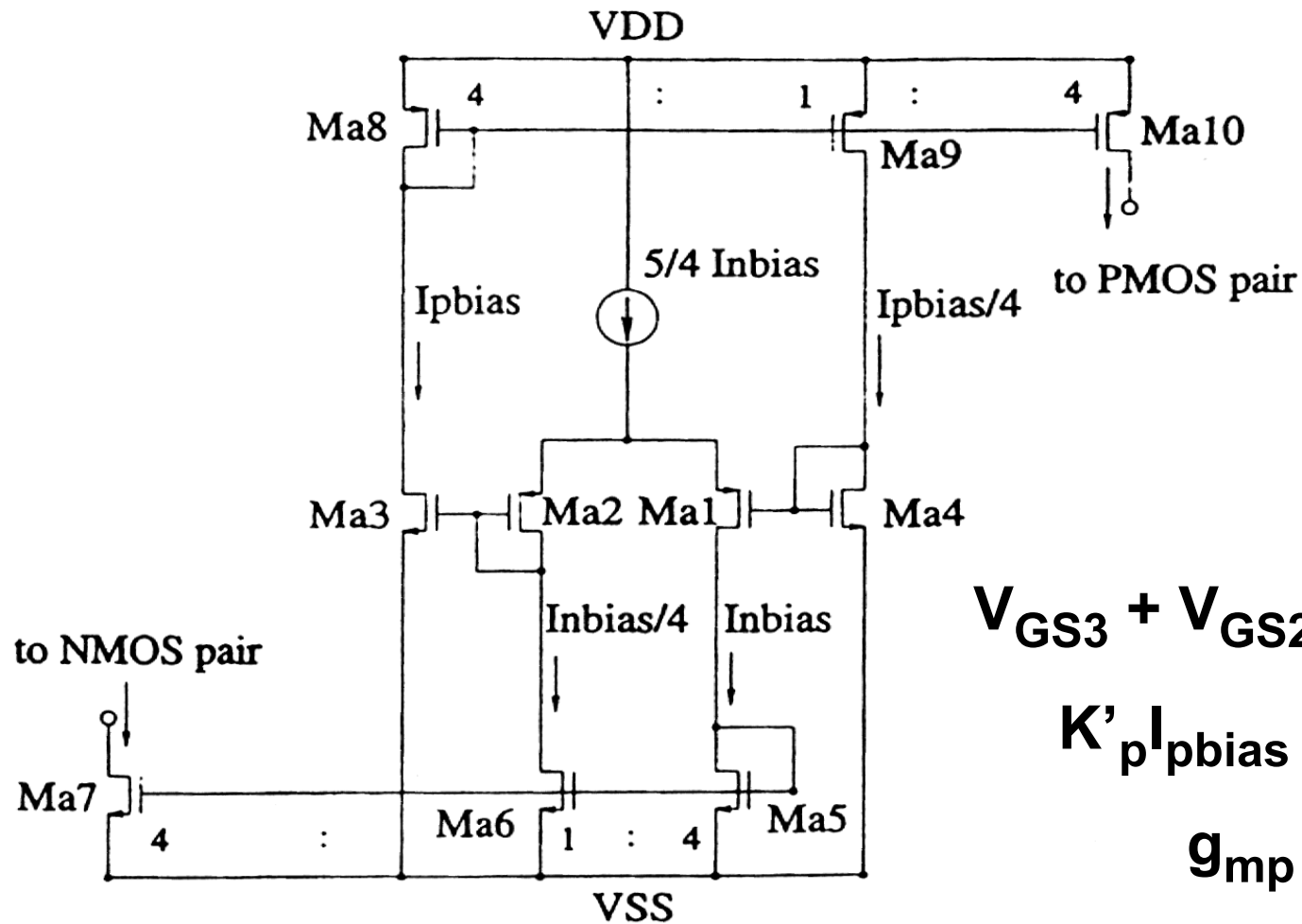


$$V_{GS3} + V_{GS2} = V_{GS1} + V_{GS4}$$

$$K'_p I_{pbias} = K'_n I_{nbias}$$

$$g_{mp} = g_{mn}$$

Ref.Lin, AICSP 1999, 153-162

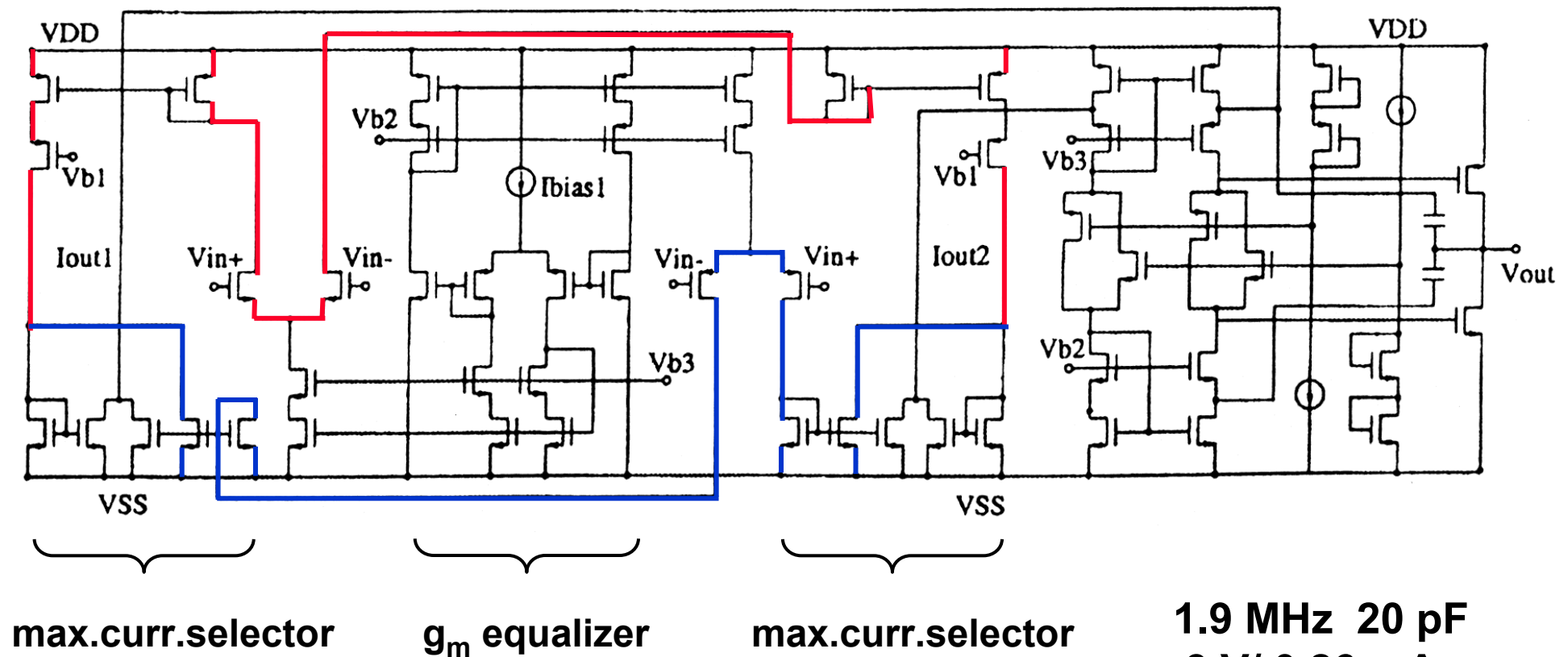
# Rail-to-rail opamp with max.-current selector



1.9 MHz 20 pF  
3 V/ 0.26 mA

Ref.Lin, AICSP 1999, 153-162
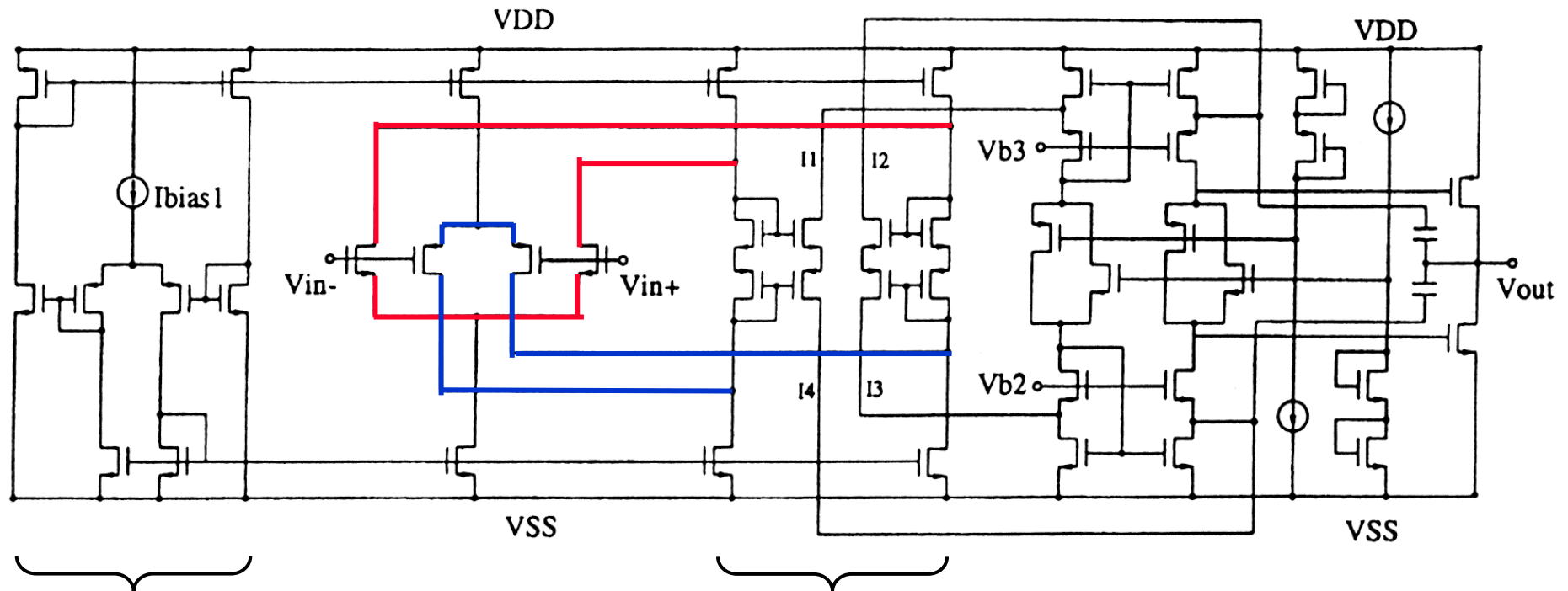
# Rail-to-rail opamp with max.-current selector



$g_m$  equalizer


max.curr.selector

1.9 MHz 20 pF  
3 V/ 0.26 mA


Ref.Lin, AICSP 1999, 153-162

# Rail-to-rail opamp on 1 Volt Supply

$$V_{DD} = 1 \text{ V}$$

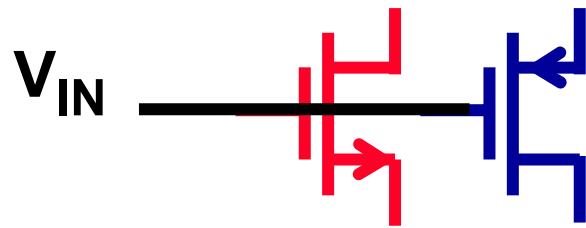

0 V

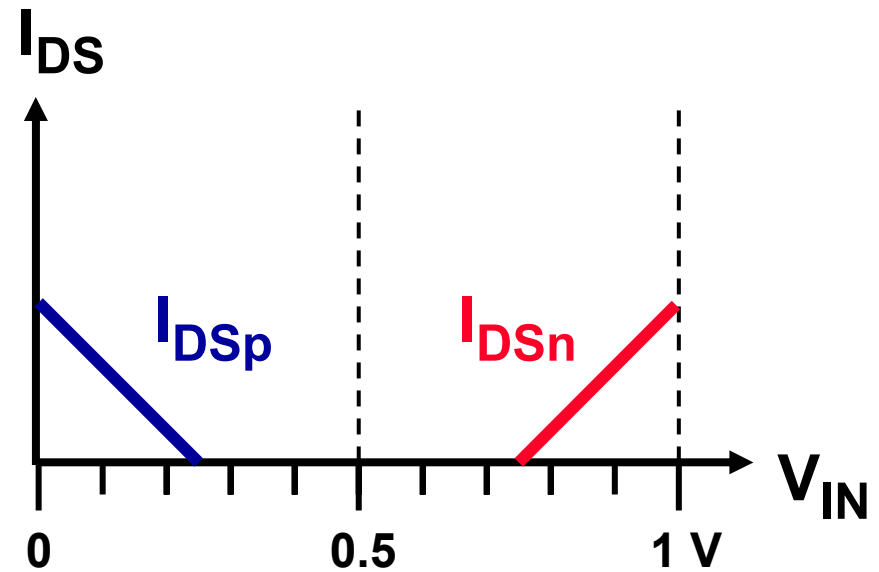


Ref. Duque-Carrillo, JSSC Jan.2000, 33-43

---

# Rail-to-rail opamp on 1 Volt




---

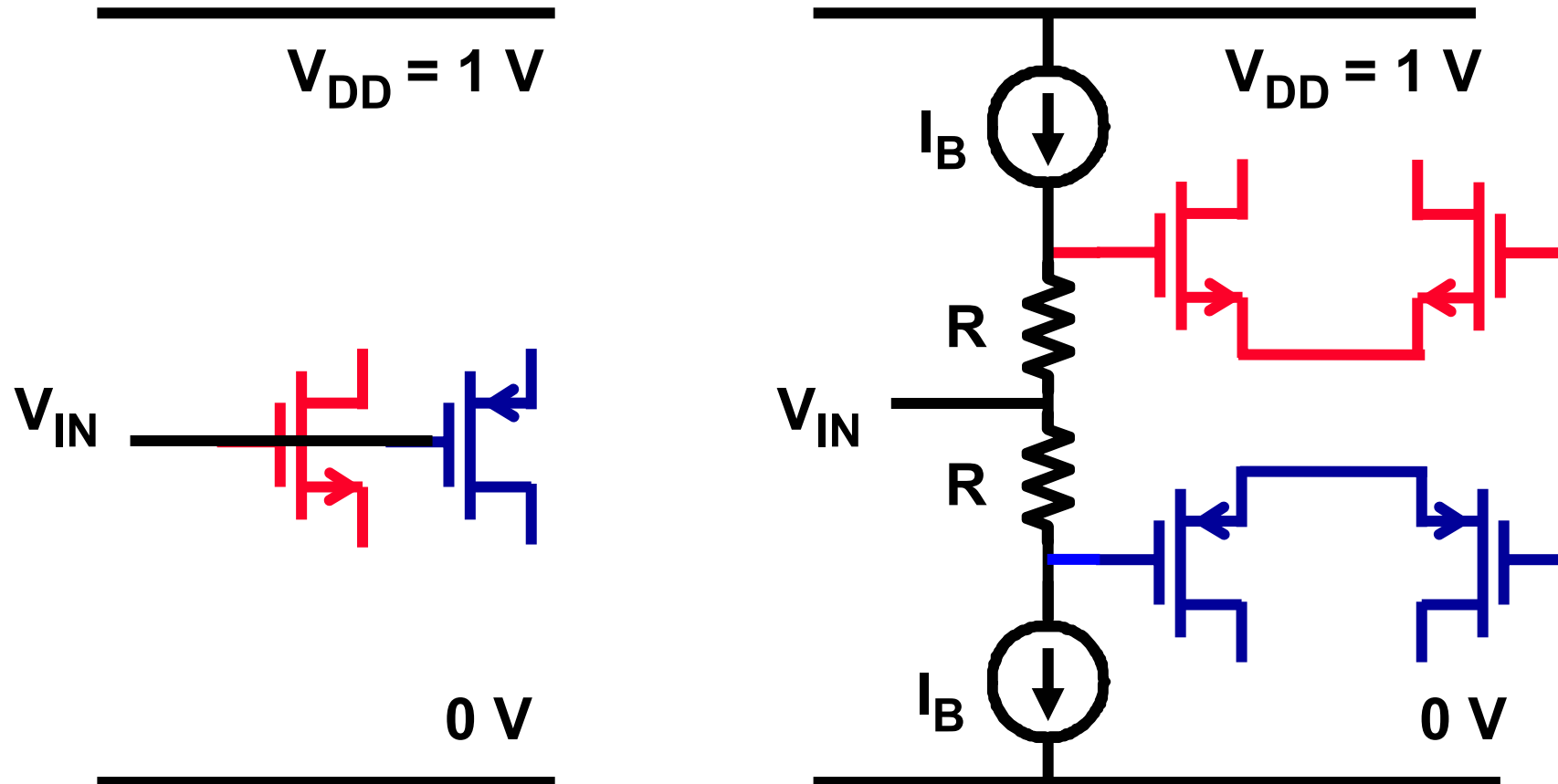

Ref.Duque-Carrillo, JSSC Jan.2000, 33-43




# Rail-to-Rail opamp on 1 Volt

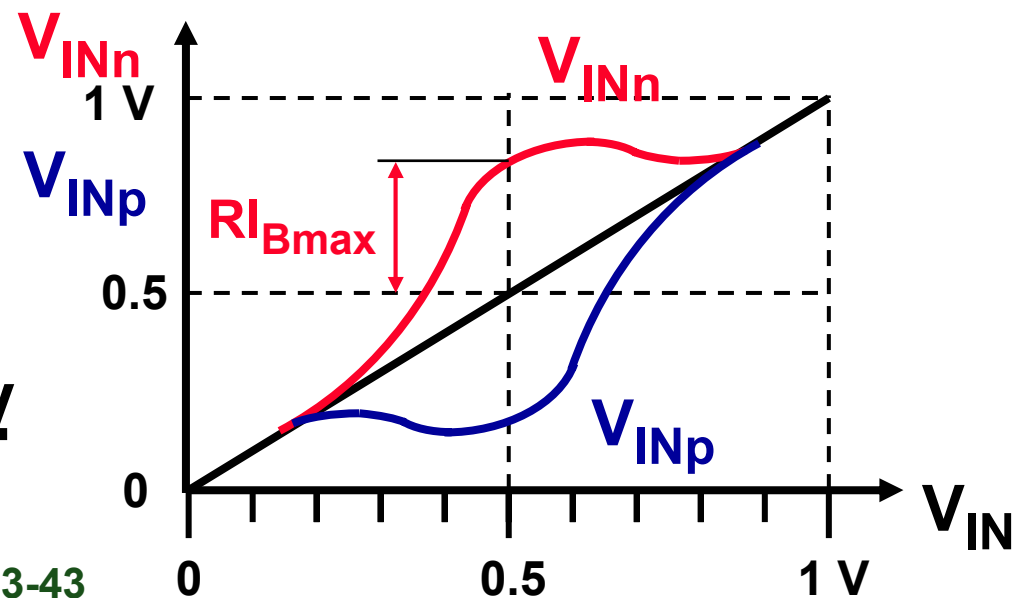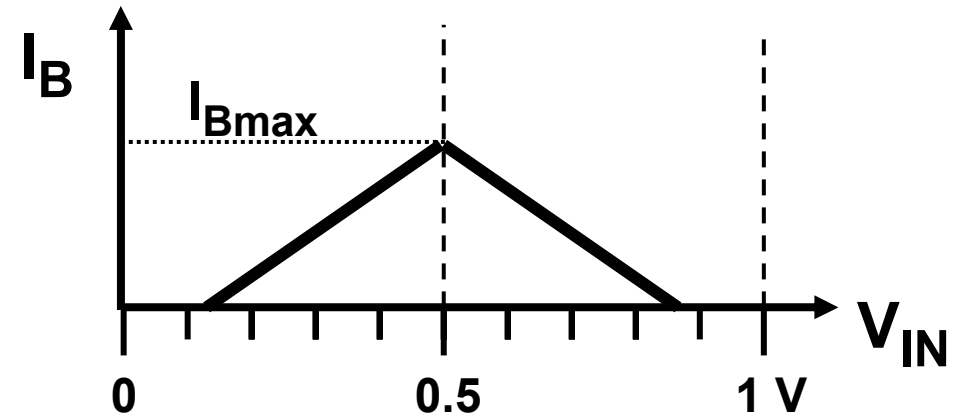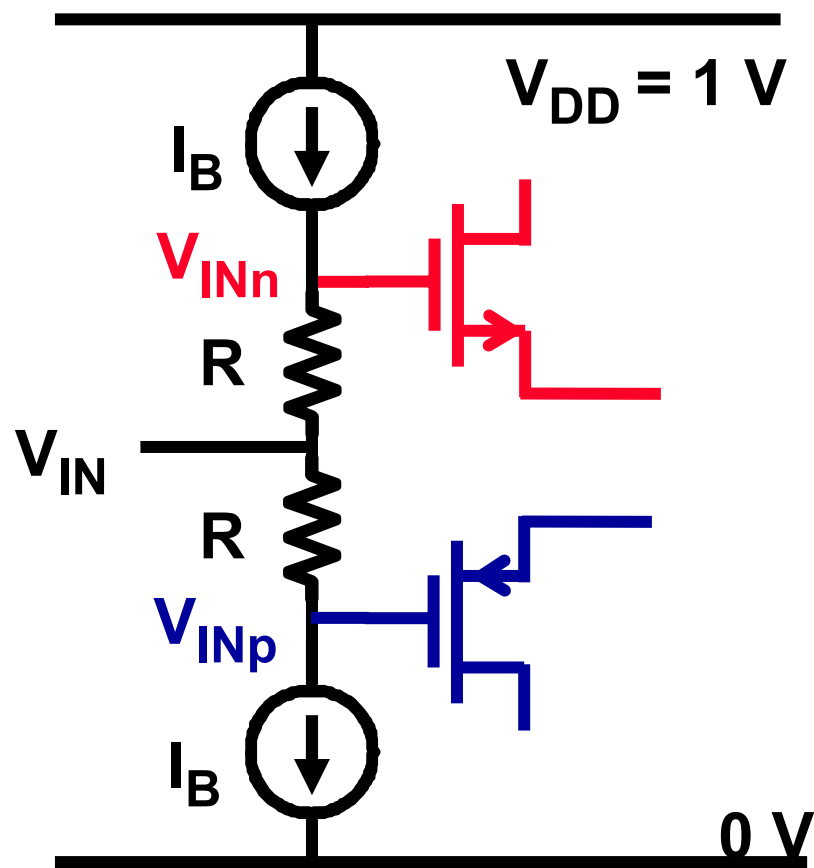

Ref. Duque-Carrillo, JSSC Jan. 2000, 33-43

# RtR opamp : full opamp schematic

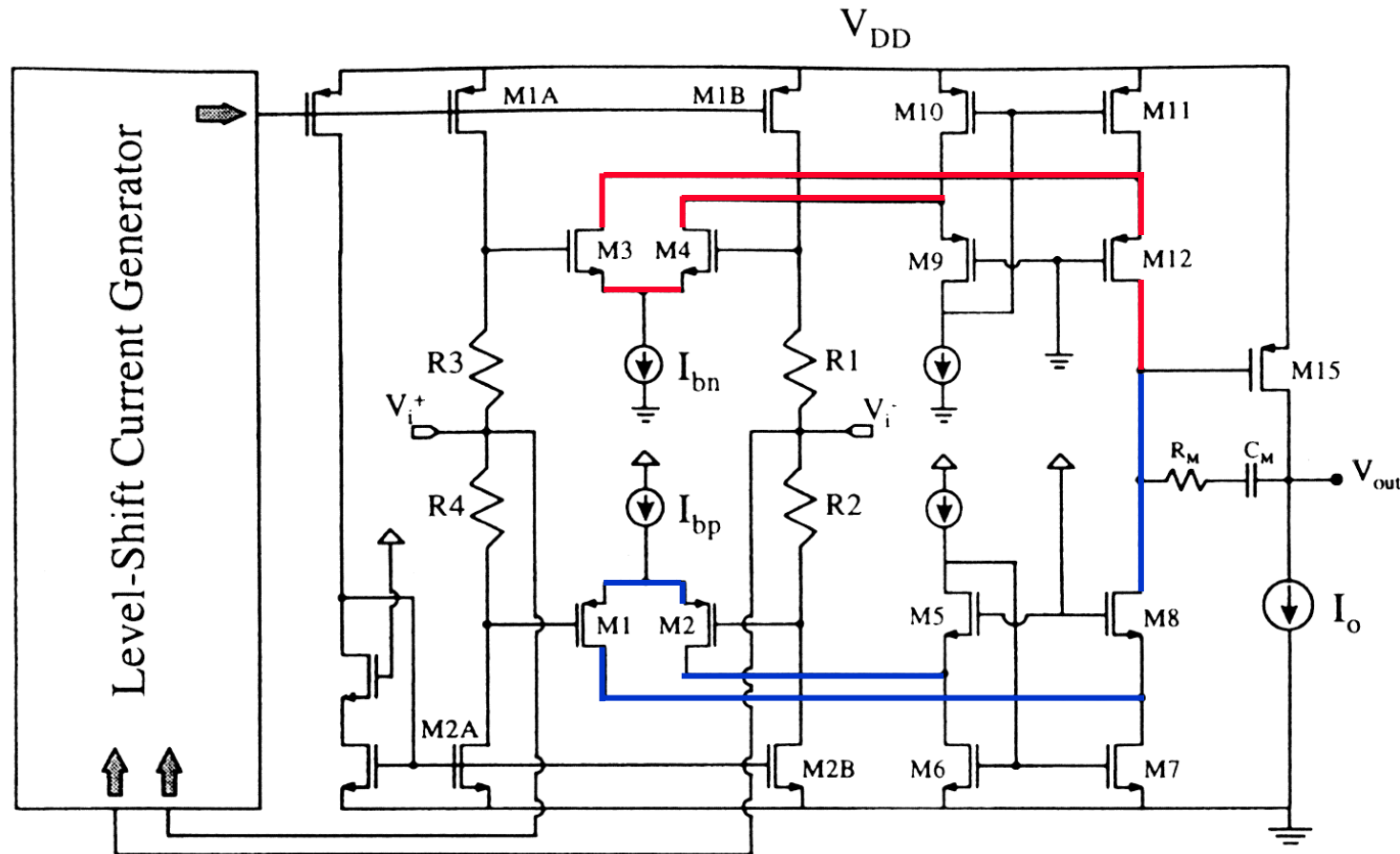

**2 MHz**

**15 pF**

**1 V**


**0.4 mA**

**$I_{\text{offset}}$   
 $< 1 \mu\text{A}$**

Ref.Duque-Carrillo, JSSC Jan.2000, 33-43

**$R \uparrow$   $I_{\text{offset}} \downarrow$  noise  $\uparrow$**

# RtR opamp : current generator

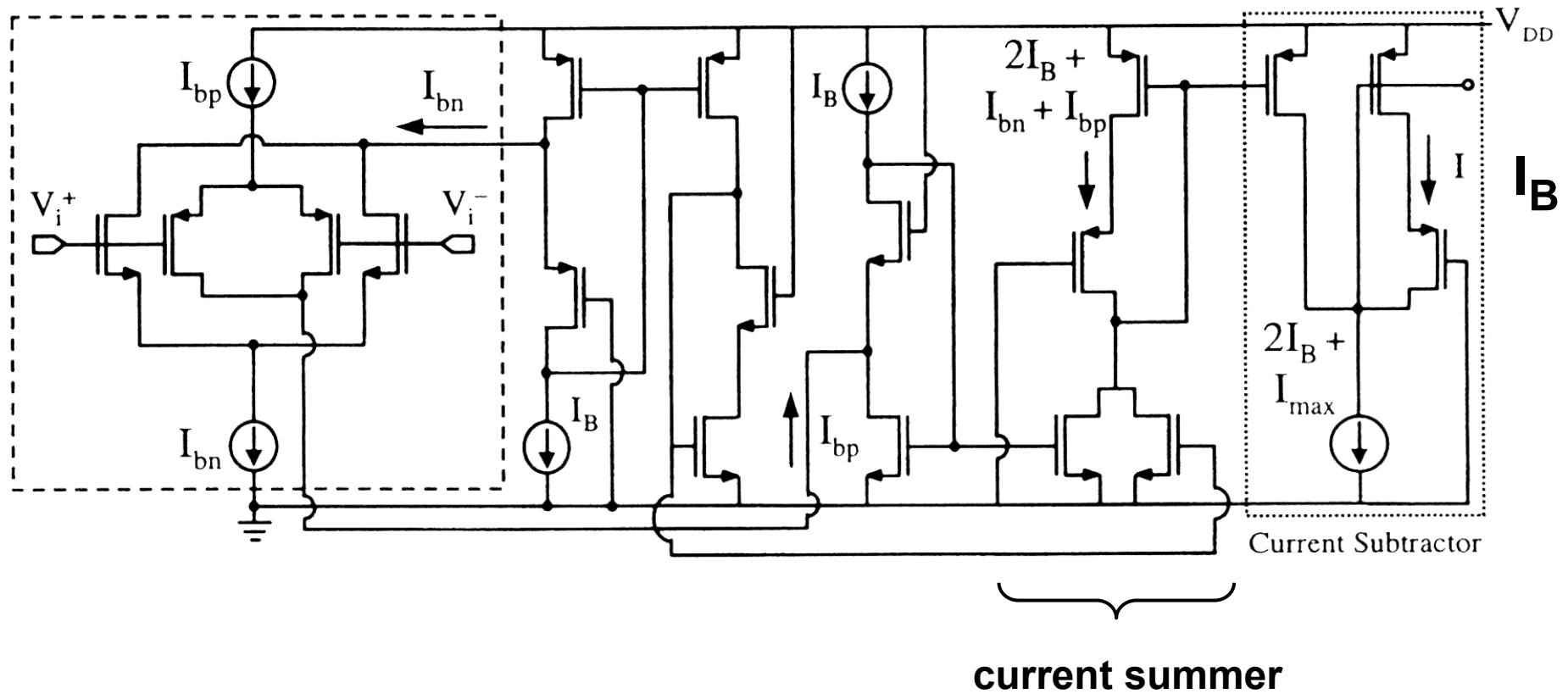

Ref.Duque-Carrillo, JSSC Jan.2000, 33-43

# Comparison rail-to-rail input amplifiers

Type	Ref.	$\Delta g_m/g_m$ %	GBW MHzpF/mW	$I_{TOT}$ $\mu A$	$V_{DDmin}$ V
3x Curr.mirr.	JSSC-12-94	15	110	150	3
Electr. Zener	JSSC-7-96	6	70	215	2.7
Curr.switch	AICSP-5-94	8	1.1	500	3.3
Curr.regulat.	CICC 97	4	210	200	1.5
Regulat. VDD	JSSC-10-97	6	43	350	1.3
MOST translin.	AICSP-6-94	8	4.2	800	2.5
Improv.CMRR	JSSC-2-95	9	3	1400	5
Max. current	AICSP-1-99	10	77	260	3
Resistive input	JSSC-1-00	x	75	400	1

---

# Table of contents

---

- **Why rail-to-rail ?**
- **3 x Current mirror rtr amplifiers**
- **Zener diode rtr amplifiers**
- **Current regulator rtr amplifier on 1.5 V**
- **Supply regulating rtr amplifier on 1.3 V**
- **Other rail-to-rail amplifiers**

---

# References

---

**T. Duisters, et al, "A -90 dB THD rail-to-rail input opamp using a new local charge pump in CMOS", IEEE Journal Solid-State Circuits, Vol. SC-33, pp. 947-955, July 1998.**

**R. Duque-Carillo, et al, "A 1 V rail-to-rail operational amplifier in standard CMOS technology", IEEE Journal Solid-State Circuits, Vol. SC-35, pp. 33-43, Jan. 2000.**

**G.Ferri, W.Sansen, "A rail-to-rail constant-gm low-voltage CMOS operational transconductance amplifier", IEEE Journal Solid-State Circuits, Vol. SC-32, pp. 1563-1567, Oct.1997.**

**R. Hogervorst, et al, "A compact power-efficient 3V CMOS rail-to-rail input/output operational amplifier for VLSI cell libraries", IEEE Journal Solid-State Circuits, Vol. SC-29, pp. 1504-1512, Dec.1994.**

**R. Hogervorst, et al, "Compact CMOS constant-gm rail-to-rail input stage with gm-control by an electronic Zener diode", IEEE Journal Solid-State Circuits, Vol. SC-31, pp. 1035-1040, July 1996.**

**R. Lin, et al, "A compact power-efficient 3V CMOS rail-to-rail input/output operational amplifier for VLSI cell libraries", Analog Integrated Circuits and Signal Processing, Kluwer Ac., pp. 153-162, Jan.1999.**

---

# References

---

**E. Peeters, etal, "A compact power-efficient 3V CMOS rail-to-rail input/output operational amplifier for VLSI cell libraries", CICC 1997.**

**W. Wu, etal, "Digital-compatible high-performance operational amplifier with rail-to-rail input and output stages", IEEE Journal Solid-State Circuits, Vol. SC-29, pp. 63-66, Jan 1994.**